

## DPP - Daily Practice Problems

### Chapter-wise Sheets

Date :  Start Time :  End Time :

# PHYSICS

CP21

SYLLABUS : Alternating Current

**Max. Marks : 180**    **Marking Scheme : (+4) for correct & (-1) for incorrect answer**    **Time : 60 min.**

**INSTRUCTIONS :** This Daily Practice Problem Sheet contains 45 MCQs. For each question only one option is correct. Darken the correct circle/ bubble in the Response Grid provided on each page.

1. In a series resonant LCR circuit, the voltage across  $R$  is 100 volts and  $R = 1 \text{ k}\Omega$  with  $C = 2\mu\text{F}$ . The resonant frequency  $\omega$  is 200 rad/s. At resonance, the voltage across  $L$  is
    - (a)  $2.5 \times 10^{-2} \text{ V}$
    - (b) 40 V
    - (c) 250 V
    - (d)  $4 \times 10^{-3} \text{ V}$
  2. An alternating voltage  $V = V_0 \sin \omega t$  is applied across a circuit. As a result, a current  $I = I_0 \sin (\omega t - \pi/2)$  flows in it. The power consumed per cycle is
    - (a) zero
    - (b)  $0.5 V_0 I_0$
    - (c)  $0.707 V_0 I_0$
    - (d)  $1.414 V_0 I_0$
  3. For the circuit shown in the fig., the current through the inductor is 0.9 A while the current through the condenser is 0.4 A. Then
    - (a) current drawn from generator  $I = 1.13 \text{ A}$
    - (b)  $\omega = 1/(1.5 LC)$
    - (c)  $I = 0.5 \text{ A}$
    - (d)  $I = 0.6 \text{ A}$
- $V = V_0 \sin \omega t$
5. A coil of inductance 300 mH and resistance  $2\Omega$  is connected to a source of voltage 2V. The current reaches half of its steady state value in
    - (a) 0.1 s
    - (b) 0.05 s
    - (c) 0.3 s
    - (d) 0.15 s
  6. In an A.C. circuit, a resistance of  $R$  ohm is connected in series with an inductance  $L$ . If phase angle between voltage and current be  $45^\circ$ , the value of inductive reactance will be
    - (a)  $R/4$
    - (b)  $R/2$
    - (c)  $R$
    - (d)  $R/5$
  7. A bulb is rated at 100 V, 100 W, it can be treated as a resistor. Find out the inductance of an inductor (called choke coil) that should be connected in series with the bulb to operate the bulb at its rated power with the help of an ac source of 200 V and 50 Hz.
    - (a)  $\frac{\pi}{\sqrt{3}} \text{ H}$
    - (b) 100 H
    - (c)  $\frac{\sqrt{2}}{\pi} \text{ H}$
    - (d)  $\frac{\sqrt{3}}{\pi} \text{ H}$
  8. An ac source of angular frequency  $\omega$  is fed across a resistor  $r$  and a capacitor  $C$  in series. The current registered is  $I$ . If now the frequency of source is changed to  $\omega/3$  (but maintaining the same voltage), the current in the circuit is found to be halved. The ratio of reactance to resistance at the original frequency  $\omega$  is
    - (a)  $\sqrt{\frac{3}{5}}$
    - (b)  $\sqrt{\frac{2}{5}}$
    - (c)  $\sqrt{\frac{1}{5}}$
    - (d)  $\sqrt{\frac{4}{5}}$

**RESPONSE GRID**


- |  |  |  |  |
|--|--|--|--|
| 1. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 2. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 3. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 4. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d |
| 6. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 7. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 8. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d | 5. <input type="radio"/> a <input type="radio"/> b <input type="radio"/> c <input type="radio"/> d |

Space for Rough Work

# Mastering Physics With Physics Guruji

9. Large transformers, when used for some time, become hot and are cooled by circulating oil. The heating of transformer is due to
- heating effect of current alone
  - hysteresis loss alone
  - both the hysteresis loss and heating effect of current
  - none of the above

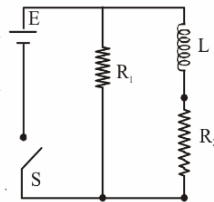
10. An inductor of inductance  $L = 400$  mH and resistors of resistance  $R_1 = 2\Omega$  and  $R_2 = 2\Omega$  are connected to a battery of emf 12 V as shown in the figure. The internal resistance of the battery is negligible. The switch  $S$  is closed at  $t = 0$ . The potential drop across  $L$  as a function of time is



- $\frac{12}{t}e^{-3t}$  V
  - $6(1 - e^{-t/0.2})$  V
  - $12e^{-5t}$  V
  - $6e^{-5t}$  V
11. An ideal coil of 10H is connected in series with a resistance of  $5\Omega$  and a battery of 5V. 2second after the connection is made, the current flowing in ampere in the circuit is
- $(1 - e^{-1})$
  - $(1 - e)$
  - $e$
  - $e^{-1}$
12. In an A.C. circuit, the current flowing in inductance is  $I = 5 \sin(100t - \pi/2)$  amperes and the potential difference is  $V = 200 \sin(100t)$  volts. The power consumption is equal to
- 1000 watt
  - 40 watt
  - 20 watt
  - Zero
13. In an oscillating LC circuit the maximum charge on the capacitor is  $Q$ . The charge on the capacitor when the energy is stored equally between the electric and magnetic field is
- $\frac{Q}{2}$
  - $\frac{Q}{\sqrt{3}}$
  - $\frac{Q}{\sqrt{2}}$
  - $Q$
14. A fully charged capacitor  $C$  with initial charge  $q_0$  is connected to a coil of self inductance  $L$  at  $t = 0$ . The time at which the energy is stored equally between the electric and the magnetic fields is:
- $\frac{\pi}{4}\sqrt{LC}$
  - $2\pi\sqrt{LC}$
  - $\sqrt{LC}$
  - $\pi\sqrt{LC}$
15. For an LCR series circuit with an A.C. source of angular frequency  $\omega$

- circuit will be capacitive if  $\omega > \frac{1}{\sqrt{LC}}$
- circuit will be inductive if  $\omega = \frac{1}{\sqrt{LC}}$
- power factor of circuit will be unity if capacitive reactance equals inductive reactance
- current will be leading voltage if  $\omega > \frac{1}{\sqrt{LC}}$

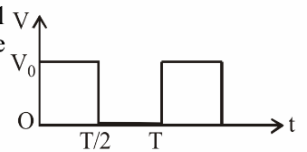16. The r.m.s. value of potential difference  $V$  shown in the figure is




- $V_0$
  - $V_0/\sqrt{2}$
  - $V_0/2$
  - $V_0/\sqrt{3}$
17. Which of the following statements is/are incorrect?
- If the resonance is less sharp, not only is the maximum current less, the circuit is close to resonance for a larger range  $\Delta\omega$  of frequencies and the tuning of the circuit will not be good.
  - Less sharp the resonance less is the selectivity of the circuit or *vice-versa*.
  - If quality factor is large, i.e.,  $R$  is low or  $L$  is large, the circuit is more selective.
  - Below resonance, voltage leads the current while above it, current leads the voltage.
18. A lamp consumes only 50% of peak power in an a.c. circuit. What is the phase difference between the applied voltage and the circuit current?

- $\frac{\pi}{6}$
- $\frac{\pi}{3}$
- $\frac{\pi}{4}$
- $\frac{\pi}{2}$

19. A step down transformer reduces 220 V to 110 V. The primary draws 5 ampere of current and secondary supplies 9 ampere. The efficiency of transformer is

- 20%
- 44%
- 90%
- 100%

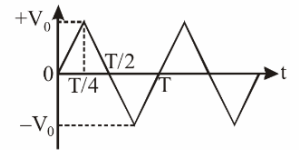20. The voltage time (V-t) graph for triangular wave having peak value  $V_0$  is as shown in figure. The rms value of  $V$  in time interval from  $t = 0$  to  $T/4$  is



$\frac{V_0}{\sqrt{x}}$  then find the value of  $x$ .

- 5
- 4
- 7
- 3

21. The tuning circuit of a radio receiver has a resistance of  $50\Omega$ , an inductor of 10 mH and a variable capacitor. A 1 MHz radio wave produces a potential difference of 0.1 mV. The values of the capacitor to produce resonance is (Take  $\pi^2 = 10$ )

- 2.5 pF
- 5.0 pF
- 25 pF
- 50 pF

22. In an alternating current circuit in which an inductance and capacitance are joined in series, current is found to be maximum when the value of inductance is 0.5 henry and the value of capacitance is  $8\mu\text{F}$ . The angular frequency of applied alternating voltage will be

- 5000 rad/sec
- 4000 rad/sec
- $2 \times 10^5$  rad/sec
- 500 rad/sec

23. A coil has resistance 30 ohm and inductive reactance 20 ohm at 50 Hz frequency. If an ac source, of 200 volt, 100 Hz, is connected across the coil, the current in the coil will be



- 4.0A
- 8.0A
- $\frac{20}{\sqrt{13}}$  A
- 2.0A

**RESPONSE  
GRID**


- |                     |                     |                     |                     |                     |
|---------------------|---------------------|---------------------|---------------------|---------------------|
| 9. (a) (b) (c) (d)  | 10. (a) (b) (c) (d) | 11. (a) (b) (c) (d) | 12. (a) (b) (c) (d) | 13. (a) (b) (c) (d) |
| 14. (a) (b) (c) (d) | 15. (a) (b) (c) (d) | 16. (a) (b) (c) (d) | 17. (a) (b) (c) (d) | 18. (a) (b) (c) (d) |
| 19. (a) (b) (c) (d) | 20. (a) (b) (c) (d) | 21. (a) (b) (c) (d) | 22. (a) (b) (c) (d) | 23. (a) (b) (c) (d) |

Space for Rough Work

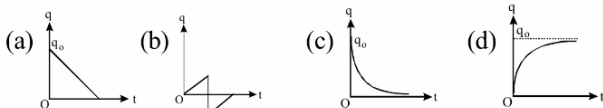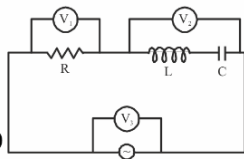
24. In the figure shown, three AC voltmeters are connected. At resonance
- (a)  $V_2 = 0$     (b)  $V_1 = 0$   
 (c)  $V_3 = 0$     (d)  $V_1 = V_2 \neq 0$
25. A.C. power is transmitted from a power house at a high voltage as
- (a) the rate of transmission is faster at high voltages  
 (b) it is more economical due to less power loss  
 (c) power cannot be transmitted at low voltages  
 (d) a precaution against theft of transmission lines
26. A transformer has an efficiency of 80%. It works at 4 kW and 100 V. If secondary voltage is 240 V, the current in primary coil is
- (a) 0.4 A    (b) 4 A    (c) 10 A    (d) 40 A
27. A  $12 \Omega$  resistor and a 0.21 henry inductor are connected in series to an a.c. source operating at 20 volt, 50 cycle. The phase angle between the current and source voltage is
- (a)  $30^\circ$     (b)  $40^\circ$     (c)  $80^\circ$     (d)  $90^\circ$
28. In LCR series circuit fed by a DC source, how does the amplitude of charge oscillations vary with time during discharge ?



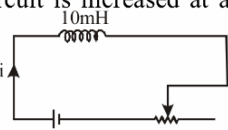29. The primary and secondary coil of a transformer have 50 and 1500 turns respectively. If the magnetic flux  $\phi$  linked with the primary coil is given by  $\phi = \phi_0 + 4t$ , where  $\phi$  is in webers,  $t$  is time in seconds and  $\phi_0$  is a constant, the output voltage across the secondary coil is
- (a) 120 volts    (b) 220 volts  
 (c) 30 volts    (d) 90 volts
30. The primary winding of a transformer has 100 turns and its secondary winding has 200 turns. The primary is connected to an A.C. supply of 120 V and the current flowing in it is 10 A. The voltage and the current in the secondary are
- (a) 240 V, 5 A    (b) 240 V, 10 A  
 (c) 60 V, 20 A    (d) 120 V, 20 A
31. The resistance in the following circuit is increased at a particular instant. At this instant the value of resistance is  $10 \Omega$ . The current in the circuit will be now
- (a)  $i = 0.5 \text{ A}$     (b)  $i > 0.5 \text{ A}$     (c)  $i < 0.5 \text{ A}$     (d)  $i = 0$
32. The current in a LR circuit builds up to  $\frac{3}{4}$ th of its steady state value in 4s. The time constant of this circuit is
- (a)  $\frac{1}{\ln 2} \text{ s}$     (b)  $\frac{2}{\ln 2} \text{ s}$     (c)  $\frac{3}{\ln 2} \text{ s}$     (d)  $\frac{4}{\ln 2} \text{ s}$



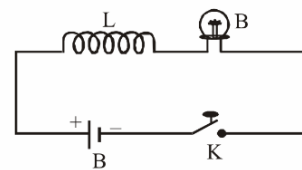
33. An LCR series circuit is connected to a source of alternating current. At resonance, the applied voltage and the current flowing through the circuit will have a phase difference of
- (a)  $\pi$     (b)  $\frac{\pi}{2}$     (c)  $\frac{\pi}{4}$     (d) 0
34. What is the value of inductance L for which the current is maximum in a series LCR circuit with  $C = 10 \mu\text{F}$  and  $\omega = 1000 \text{ s}^{-1}$  ?
- (a) 1 mH  
 (b) cannot be calculated unless R is known  
 (c) 10 mH  
 (d) 100 mH
35. In the circuit of Fig, the bulb will become suddenly bright if



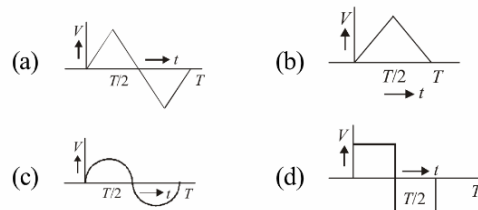- (a) contact is made or broken  
 (b) contact is made  
 (c) contact is broken  
 (d) won't become bright at all
36. The voltage of an ac source varies with time according to the equation  $V = 100 \sin 100 \pi t \cos 100 \pi t$  where  $t$  is in seconds and  $V$  is in volt. Then
- (a) the peak voltage of the source is 100 volt  
 (b) the peak voltage of the source is 50 volt  
 (c) the peak voltage of the source is  $100/\sqrt{2}$  volt  
 (d) the frequency of the source is 50 Hz
37. The current ( $I$ ) in the inductance is varying with time according to the plot shown in figure.



Which one of the following is the correct variation of voltage with time in the coil?




**RESPONSE GRID**

24. (a)(b)(c)(d)	25. (a)(b)(c)(d)	26. (a)(b)(c)(d)	27. (a)(b)(c)(d)	28. (a)(b)(c)(d)
29. (a)(b)(c)(d)	30. (a)(b)(c)(d)	31. (a)(b)(c)(d)	32. (a)(b)(c)(d)	33. (a)(b)(c)(d)
34. (a)(b)(c)(d)	35. (a)(b)(c)(d)	36. (a)(b)(c)(d)	37. (a)(b)(c)(d)	



Space for Rough Work

# Mastering Physics With Physics Guruji

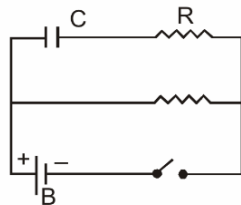38. Using an A.C. voltmeter the potential difference in the electrical line in a house is read to be 234 volt. If the line frequency is known to be 50 cycles/second, the equation for the line voltage is  
 (a)  $V = 165 \sin(100 \pi t)$  (b)  $V = 331 \sin(100 \pi t)$   
 (c)  $V = 220 \sin(100 \pi t)$  (d)  $V = 440 \sin(100 \pi t)$
39. In the circuit shown, when the switch is closed, the capacitor charges with a time constant  
 (a)  $RC$   
 (b)  $2RC$   
 (c)  $\frac{1}{2}RC$   
 (d)  $RC \ln 2$
40. A  $100 \mu\text{F}$  capacitor in series with a  $40\Omega$  resistance is connected to a 110 V, 60 Hz supply.  
 What is the maximum current in the circuit?  
 (a) 3.24A (b) 4.25A (c) 2.25A (d) 5.20A
41. The core of any transformer is laminated so as to  
 (a) reduce the energy loss due to eddy currents  
 (b) make it light weight  
 (c) make it robust and strong  
 (d) increase the secondary voltage



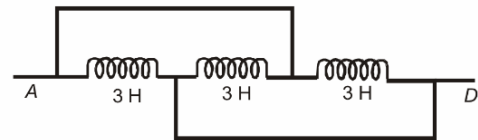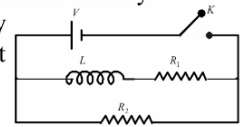42. An AC generator of 220 V having internal resistance  $r = 10\Omega$  and external resistance  $R = 100\Omega$ . What is the power developed in the external circuit?  
 (a) 484 W (b) 400 W (c) 441 W (d) 369 W
43. What is increased in step-down transformer?  
 (a) Voltage (b) Current  
 (c) Power (d) Current density
44. In the circuit shown below, the key  $K$  is closed at  $t = 0$ . The current through the battery is  
 (a)  $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$  at  $t = 0$  and  $\frac{V}{R_2}$  at  $t = \infty$   
 (b)  $\frac{V}{R_2}$  at  $t = 0$  and  $\frac{V(R_1 + R_2)}{R_1R_2}$  at  $t = \infty$   
 (c)  $\frac{V}{R_2}$  at  $t = 0$  and  $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$  at  $t = \infty$   
 (d)  $\frac{V(R_1 + R_2)}{R_1R_2}$  at  $t = 0$  and  $\frac{V}{R_2}$  at  $t = \infty$
45. The inductance between  $A$  and  $D$  is



- (a) 3.66H (b) 9H (c) 0.66H (d) 1H

<b>RESPONSE GRID</b>	38. (a) (b) (c) (d)	39. (a) (b) (c) (d)	40. (a) (b) (c) (d)	41. (a) (b) (c) (d)	42. (a) (b) (c) (d)
	43. (a) (b) (c) (d)	44. (a) (b) (c) (d)	45. (a) (b) (c) (d)		

DAILY PRACTICE PROBLEM DPP CHAPTERWISE CP21 - PHYSICS			
Total Questions	45	Total Marks	180
Attempted		Correct	
Incorrect		Net Score	
Cut-off Score	50	Qualifying Score	70
Success Gap = Net Score – Qualifying Score			
Net Score = (Correct × 4) – (Incorrect × 1)			

Space for Rough Work