

# Mastering Physics With Physics Guruji

## DPP - Daily Practice Problems

### Chapter-wise Sheets

Date :  Start Time :  End Time :

# PHYSICS

CP17


SYLLABUS : Current Electricity

**Max. Marks : 120**    **Marking Scheme :** (+4) for correct & (−1) for incorrect answer    **Time : 60 min.**

**INSTRUCTIONS :** This Daily Practice Problem Sheet contains 30 MCQs. For each question only one option is correct. Darken the correct circle/ bubble in the Response Grid provided on each page.


1. Variation of current passing through a conductor as the voltage applied across its ends is varied as shown in the adjoining diagram. If the resistance ( $R$ ) is determined at the points  $A, B, C$  and  $D$ , we will find that

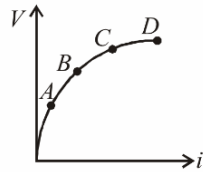- (a)  $R_C = R_D$
- (b)  $R_B > R_A$
- (c)  $R_C > R_B$
- (d)  $R_A > R_B$



2. Twelve resistors each of resistance  $16 \Omega$  are connected in the circuit as shown. The net resistance between AB is

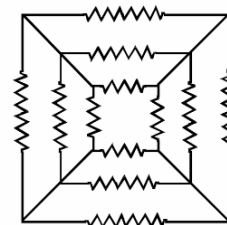- (a)  $1 \Omega$
- (b)  $2 \Omega$
- (c)  $3 \Omega$
- (d)  $4 \Omega$



3. The masses of the three wires of copper are in the ratio of  $1 : 3 : 5$  and their lengths are in the ratio of  $5 : 3 : 1$ . The ratio of their electrical resistance is

- (a)  $1 : 3 : 5$
- (b)  $5 : 3 : 1$
- (c)  $1 : 25 : 125$
- (d)  $125 : 25 : 1$

**RESPONSE GRID**

1. (a) (b) (c) (d)    2. (a) (b) (c) (d)    3. (a) (b) (c) (d)


Space for Rough Work

# Mastering Physics With Physics Guruji


P-66

DPP/ CP17

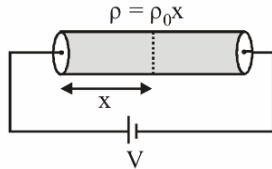4. A cylindrical solid of length  $L$  and radius  $a$  is having varying resistivity given by  $\rho = \rho_0 x$ , where  $\rho_0$  is a positive constant and  $x$  is measured from left end of solid. The cell shown in the figure is having emf  $V$  and negligible internal resistance. The electric field as a function of  $x$  is best described by




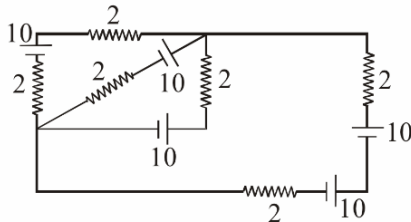- (a)  $\frac{2V}{L^2}x$                       (b)  $\frac{2V}{\rho_0 L^2}x$   
 (c)  $\frac{V}{L^2}x$                       (d) None of these
5. All batteries are having emf 10 volt and internal resistance negligible. All resistors are in ohms. Calculate the current in the right most  $2\Omega$  resistor.




- (a)  $\frac{25}{12}A$     (b)  $\frac{25}{6}A$     (c)  $\frac{12}{25}A$     (d)  $\frac{6}{25}A$
6.  $n$  equal resistors are first connected in series and then connected in parallel. What is the ratio of the maximum to the minimum resistance?  
 (a)  $n$     (b)  $1/n^2$     (c)  $n^2$     (d)  $1/n$
7. A battery is charged at a potential of 15V for 8 hours when the current flowing is 10A. The battery on discharge supplies a current of 5A for 15 hours. The mean terminal voltage during discharge is 14V. The "watt-hour" efficiency of the battery is  
 (a) 87.5%    (b) 82.5%    (c) 80%    (d) 90%
8. You are given a resistance coil and a battery. In which of the following cases is largest amount of heat generated?  
 (a) When the coil is connected to the battery directly  
 (b) When the coil is divided into two equal parts and both the parts are connected to the battery in parallel

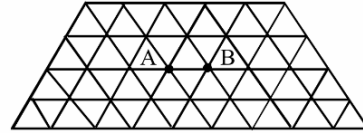- (c) When the coil is divided into four equal parts and all the four parts are connected to the battery in parallel  
 (d) When only half the coil is connected to the battery
9. There is an infinite wire grid with cells in the form of equilateral triangles. The resistance of each wire between neighbouring joint connections is  $R_0$ . The net resistance of the whole grid between the points A and B as shown is



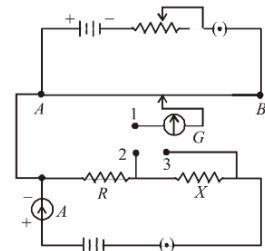- (a)  $R_0$     (b)  $\frac{R_0}{2}$     (c)  $\frac{R_0}{3}$     (d)  $\frac{R_0}{4}$
10. A potentiometer circuit is set up as shown. The potential gradient, across the potentiometer wire, is  $k$  volt/cm and the ammeter, present in the circuit, reads 1.0 A when two way key is switched off. The balance points, when the key between the terminals (i) 1 and 2 (ii) 1 and 3, is plugged in, are found to be at lengths  $l_1$  cm and  $l_2$  cm respectively. The magnitudes, of the resistors  $R$  and  $X$ , in ohms, are then, equal, respectively, to




- (a)  $k(l_2 - l_1)$  and  $k l_2$   
 (b)  $k l_1$  and  $k(l_2 - l_1)$   
 (c)  $k(l_2 - l_1)$  and  $k l_1$   
 (d)  $k l_1$  and  $k l_2$
11. If voltage across a bulb rated 220 Volt-100 Watt drops by 2.5% of its rated value, the percentage of the rated value by which the power would decrease is :  
 (a) 20%    (b) 2.5%    (c) 5%    (d) 10%
12. The resistance of the coil of an ammeter is  $R$ . The shunt required to increase its range  $n$ -fold should have a resistance  
 (a)  $\frac{R}{n}$     (b)  $\frac{R}{n-1}$     (c)  $\frac{R}{n+1}$     (d)  $nR$
13. A conducting wire of cross-sectional area  $1 \text{ cm}^2$  has  $3 \times 10^{23}$  charge carriers per  $\text{m}^3$ . If wire carries a current of 24 mA, then drift velocity of carriers is  
 (a)  $5 \times 10^{-2} \text{ m/s}$                       (b) 0.5 m/s  
 (c)  $5 \times 10^{-3} \text{ m/s}$                       (d)  $5 \times 10^{-6} \text{ m/s}$


<b>RESPONSE GRID</b>	4. (a)(b)(c)(d)	5. (a)(b)(c)(d)	6. (a)(b)(c)(d)	7. (a)(b)(c)(d)	8. (a)(b)(c)(d)
	9. (a)(b)(c)(d)	10. (a)(b)(c)(d)	11. (a)(b)(c)(d)	12. (a)(b)(c)(d)	13. (a)(b)(c)(d)

Space for Rough Work

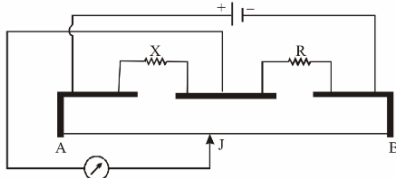14. The figure shows a meter-bridge circuit,  $X = 12\Omega$  and  $R = 18\Omega$ . The jockey  $J$  is at the null point. If  $R$  is made  $8\Omega$ , through the jockey  $J$  have to be moved by  $4 \times A$  cm to obtain null point again then find the value of  $A$ .



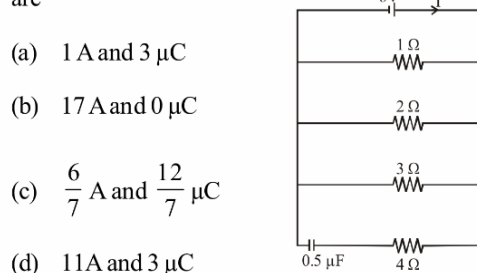- (a) 2      (b) 5      (c) 8      (d) 6
15. In the given circuit diagram the current through the battery and the charge on the capacitor respectively in steady state are



- (a) 1 A and  $3 \mu\text{C}$   
 (b) 17 A and  $0 \mu\text{C}$   
 (c)  $\frac{6}{7}$  A and  $\frac{12}{7} \mu\text{C}$   
 (d) 11 A and  $3 \mu\text{C}$
16. The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter the change in the resistance of the wire will be  
 (a) 200%    (b) 100%    (c) 50%    (d) 300%
17. Drift velocity  $V_d$  varies with the intensity of electric field as per the relation

- (a)  $V_d \propto E$                       (b)  $V_d \propto \frac{1}{E}$   
 (c)  $V_d = \text{constant}$             (d)  $V_d \propto E^2$

18. Product of conductivity and resistivity of a metallic conductor depends on  
 (a) Area of cross-section    (b) Temperature  
 (c) Pressure                      (d) None of these
19. The electric resistance of a certain wire of iron is  $R$ . If its length and radius are both doubled, then  
 (a) the resistance and the specific resistance, will both remain unchanged  
 (b) the resistance will be doubled and the specific resistance will be halved


- (c) the resistance will be halved and the specific resistance will remain unchanged  
 (d) the resistance will be halved and the specific resistance will be doubled

20. The length of a wire of a potentiometer is 100 cm, and the e.m.f. of its standard cell is  $E$  volt. It is employed to measure the e.m.f. of a battery whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $\ell = 30$  cm from the positive end, the e.m.f. of the battery is

- (a)  $\frac{30E}{100.5}$                       (b)  $\frac{30E}{(100 - 0.5)}$   
 (c)  $\frac{30(E - 0.5i)}{100}$                       (d)  $\frac{30E}{100}$

where  $i$  is the current in the potentiometer wire.

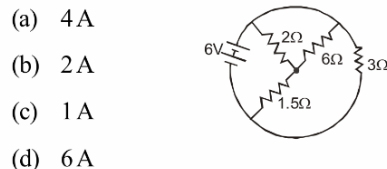21. If current flowing in a conductor changes by 1% then power consumed will change by  
 (a) 10%    (b) 2%    (c) 1%    (d) 100%
22. The total current supplied to the circuit by the battery is



- (a) 4 A  
 (b) 2 A  
 (c) 1 A  
 (d) 6 A
23. The e.m.f. developed in a thermo-couple is given by

$$E = \alpha T + \frac{1}{2} \beta T^2$$

where  $T$  is the temperature of hot junction, cold junction being at  $0^\circ\text{C}$ . The thermo electric power of the couple is

- (a)  $\alpha + \frac{\beta}{2} T$                       (b)  $\alpha + \beta T$   
 (c)  $\frac{\alpha T^2}{2} + \frac{\beta T^3}{6}$                       (d)  $\alpha / 2\beta$

24. To get maximum current in a resistance of 3 ohms, one can use  $n$  rows of  $m$  cells (connected in series) connected in parallel. If the total number of cells is 24 and the internal resistance of a cell is 0.5 ohms then  
 (a)  $m = 12, n = 2$                       (b)  $m = 8, n = 3$   
 (c)  $m = 2, n = 12$                       (d)  $m = 6, n = 4$

**RESPONSE  
GRID**

14. (a) (b) (c) (d)    15. (a) (b) (c) (d)    16. (a) (b) (c) (d)    17. (a) (b) (c) (d)    18. (a) (b) (c) (d)  
 19. (a) (b) (c) (d)    20. (a) (b) (c) (d)    21. (a) (b) (c) (d)    22. (a) (b) (c) (d)    23. (a) (b) (c) (d)  
 24. (a) (b) (c) (d)

Space for Rough Work

# Mastering Physics With Physics Guruji


P-68

**DPP/ CP17**

25. See the electric circuit shown in the figure.

Which of the following equations is a correct equation for it?

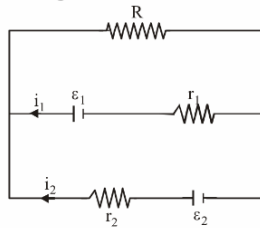
- (a)  $\epsilon_2 - i_2 r_2 - \epsilon_1 - i_1 r_1 = 0$
- (b)  $-\epsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$
- (c)  $\epsilon_1 - (i_1 + i_2)R + i_1 r_1 = 0$
- (d)  $\epsilon_1 - (i_1 + i_2)R - i_1 r_1 = 0$



26. In a neon gas discharge tube  $\text{Ne}^+$  ions moving through a cross-section of the tube each second to the right is  $2.9 \times 10^{18}$ , while  $1.2 \times 10^{18}$  electrons move towards left in the same time; the electronic charge being  $1.6 \times 10^{-19}$  C, the net electric current is

- (a) 0.27 A to the right
- (b) 0.66 A to the right
- (c) 0.66 A to the left
- (d) zero

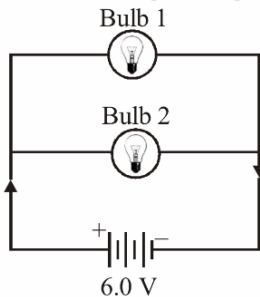27. A 6.0 volt battery is connected to two light bulbs as shown in figure. Light bulb 1 has resistance 3 ohm while light bulb 2 has resistance 6 ohm. Battery has negligible internal resistance. Which bulb will glow brighter?




- (a) Bulb 1 will glow more first and then its brightness will become less than bulb 2
- (b) Bulb 1
- (c) Bulb 2
- (d) Both glow equally

28. A car battery has e.m.f. 12 volt and internal resistance  $5 \times 10^{-2}$  ohm. If it draws 60 amp current, the terminal voltage of the battery will be

- (a) 15 volt
- (b) 3 volt
- (c) 5 volt
- (d) 9 volt

29. Two rods are joined end to end, as shown. Both have a cross-sectional area of  $0.01 \text{ cm}^2$ . Each is 1 meter long. One rod is of copper with a resistivity of  $1.7 \times 10^{-6}$  ohm-centimeter, the other is of iron with a resistivity of  $10^{-5}$  ohm-centimeter. How much voltage is required to produce a current of 1 ampere in the rods?

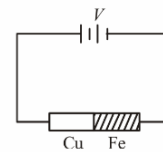- (a) 0.117 V
- (b) 0.00145 V
- (c) 0.0145 V
- (d)  $1.7 \times 10^{-6}$  V



30. Two sources of equal emf are connected to an external resistance  $R$ . The internal resistance of the two sources are  $R_1$  and  $R_2$  ( $R_1 > R_2$ ). If the potential difference across the source having internal resistance  $R_2$  is zero, then

- (a)  $R = R_2 - R_1$
- (b)  $R = R_2 \times (R_1 + R_2) / (R_2 - R_1)$
- (c)  $R = R_1 R_2 / (R_2 - R_1)$
- (d)  $R = R_1 R_2 / (R_1 - R_2)$

**RESPONSE  
GRID**

25. (a)(b)(c)(d)    26. (a)(b)(c)(d)    27. (a)(b)(c)(d)    28. (a)(b)(c)(d)    29. (a)(b)(c)(d)  
30. (a)(b)(c)(d)

## DAILY PRACTICE PROBLEM DPP CHAPTERWISE CP17 - PHYSICS

Total Questions	30	Total Marks	120
Attempted		Correct	
Incorrect		Net Score	
Cut-off Score	40	Qualifying Score	50
Success Gap = Net Score – Qualifying Score			
Net Score = (Correct × 4) – (Incorrect × 1)			

Space for Rough Work