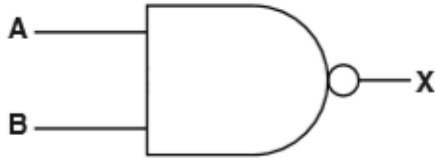


Past Papers May/June 2015 to 2018:

- 📖 Logic Circuits,
- 📖 Boolean Algebra
- 📖 Flip Flops
- 📖 Kanugh Maps

(9608/32/M/J/16)


Q1/- (a) Complete the truth table for this NAND gate:



A	B	X
0	0	
0	1	
1	0	
1	1	

[1]

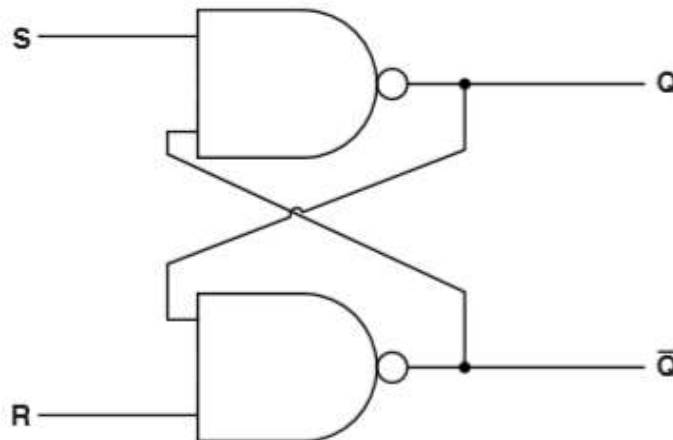A SR flip-flop is constructed using two NAND gates.



(b) (i) Complete the truth table for the SR flip-flop.

	S	R	Q	Q̄
Initially	1	0	0	1
R changed to 1	1	1		
S changed to 0	0	1		
S changed to 1	1	1		
S and R changed to 0	0	0		

[4]

(ii) One of the combinations in the truth table should not be allowed to occur.
State the values of S and R that should not be allowed. Justify your choice.

S = R =

.....
.....
.....
.....[3]

Another type of flip-flop is the JK flip-flop.

(c) (i) Give one extra input present in the JK flip-flop.

.....
.....[1]

(ii) Give one advantage of the JK flip-flop.

.....
.....[1]


(d) Describe the role of flip-flops in a computer.

.....
.....
.....[2]



Q.2 (9608/32/M/J/15)

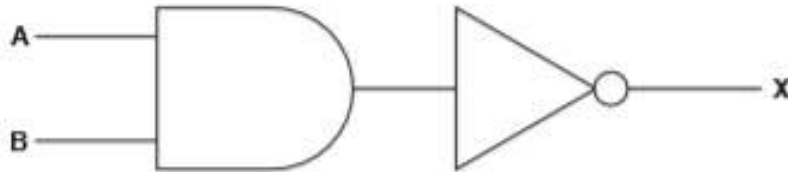
(a) (i) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

[1]

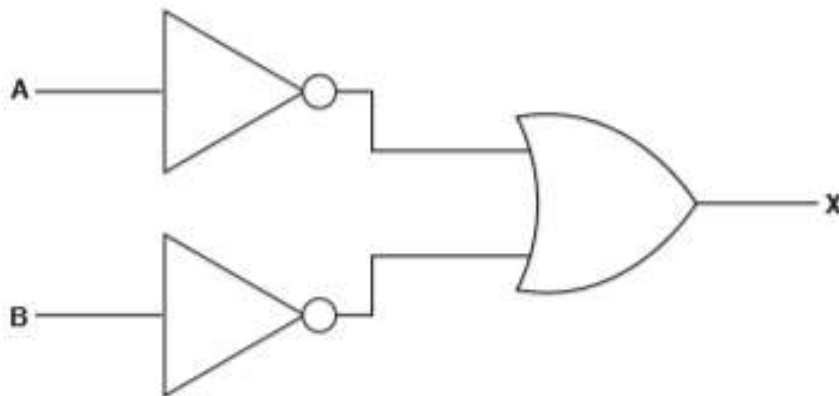(ii) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

[1]

.....[1]

(b) A student decides to write an equation for X to represent the full behaviour of each logic circuit.

(i) Write the Boolean expression that will complete the required equation for X for each circuit:


Circuit 1: X =

Circuit 2: X =[2]

(ii) Write the De Morgan's Law which is shown by your answers to part (a) and part

(b)(i).....[1]

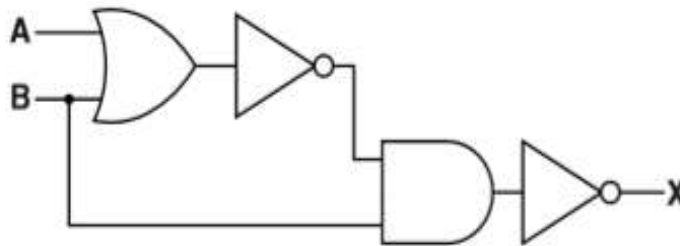(c) Write the Boolean algebraic expression corresponding to the following logic circuit:




.....[3]

(d) Using De Morgan's laws and Boolean algebra, simplify your answer to part (c). Show all your working.

.....
.....
.....
.....
.....
.....
.....[3]

(9608/31/M/J/17)

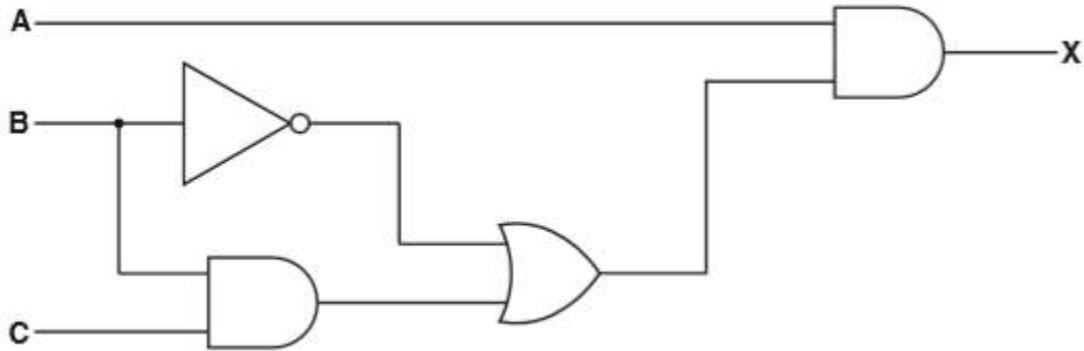3. Consider the following logic circuit, which contains a redundant logic gate.



(a) Write the Boolean algebraic expression corresponding to this logic circuit. $X =$

.....[3]

(b) Complete the truth table for this logic circuit.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

(c) (i) Complete the Karnaugh Map (K-map) for the truth table in part (b).

		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the expression in **part (a)**.

(ii) Draw loop(s) around appropriate groups to produce an optimal sum-of-products. [2]

(iii) Write a simplified sum-of-products expression, using your answer to part (ii).

X =
.....[2]

(d) One Boolean identity is:

$$A + \bar{A} \cdot B = A + B$$

Simplify the expression for X in part (a) to the expression for X in part (c)(iii). You should use the given identity.

.....
.....
.....
.....[2]

(9608/31/M/J/18)

4 (a) A Boolean expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(i) Write the Boolean expression for the truth table as a sum-of-products.

X =
.....[2]

(ii) Complete the Karnaugh Map (K-map) for the truth table in part (a)(i).

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the function in part (a)(i).

(iii) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the table in part (a)(ii).

[2]

(iv) Write the simplified sum-of-products expression for your answer to part (a)(iii).

X =

.....

[2]

(b) A logic circuit with four inputs produces the following truth table.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

- (i) Complete the K-map that corresponds to the truth table.

AB

CD				

[4]

- (ii) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the table in part (b)(i). [2]
- (iii) Write the simplified sum-of-products expression for your answer to part (b)(ii).

X =

.....[2]

Answers:

1.

(a)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1									
A	B	X																								
0	0	1																								
0	1	1																								
1	0	1																								
1	1	0																								
(b) (i)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>S</th> <th>R</th> <th>Q</th> <th>\bar{Q}</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	S	R	Q	\bar{Q}	1	0	0	1	1	1	0	1	0	1	1	0	1	1	1	0	0	0	1	1	1 1 1 1
S	R	Q	\bar{Q}																							
1	0	0	1																							
1	1	0	1																							
0	1	1	0																							
1	1	1	0																							
0	0	1	1																							
(ii)	<p>$S = 0 R = 0$</p> <p>Produces $Q = 1, \bar{Q} = 1$ // Q and \bar{Q} have same value But Q and \bar{Q} should be complements of each other Becomes unstable</p>	1 1 1 1 Max 3																								
(c) (i)	Clock (pulse)	1																								
(ii)	<p>All four possibilities are valid The 1-1 combination changes output to logical complement Unstable state avoided Invalid state cannot occur // the flip-flop is stable</p>	1 1 1 1 Max 1																								
(d)	Memory // data storage Stores a single bit	1 1																								

2.

(a) (i)	<table border="1"> <thead> <tr> <th colspan="3">Circuit 1</th> </tr> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Circuit 1			A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
	Circuit 1																			
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
(ii)	<table border="1"> <thead> <tr> <th colspan="3">Circuit 2</th> </tr> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Circuit 2			A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
Circuit 2																				
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
(b) (i)	<ul style="list-style-type: none"> • circuit 1: $\overline{A.B}$ • circuit 2: $\overline{A+B}$ 	1 1																		
(ii)	$\overline{A.B} \equiv \overline{A+B}$	1																		
(c)	$\overline{\overline{(A+B).B}}$ Mark as follows: $\overline{(A+B)}$ $\overline{.B}$ bar over whole expression	1 1 1																		
(d)	$\overline{\overline{(A+B).B}}$ $= \overline{(A+B) + \overline{B}}$ $= (A+B) + \overline{B}$ $= A + (B + \overline{B})$ $= A + 1$ $= 1$ allow f.t. from (c)	1 1 1 1 1 [max 3]																		
		Total: 11																		

Question	Answer	Marks																																														
3(a)	$X = A.(\bar{B} + (B . C))$ $B.C$ $\bar{B} + B.C$ $A.$	1 1 1	3																																													
3(b)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Working Space</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr> </tbody> </table> <p>1 mark first four entries, 1 mark for the last four entries</p>	A	B	C	Working Space	X	0	0	0		0	0	0	1		0	0	1	0		0	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		1		2
A	B	C	Working Space	X																																												
0	0	0		0																																												
0	0	1		0																																												
0	1	0		0																																												
0	1	1		0																																												
1	0	0		1																																												
1	0	1		1																																												
1	1	0		0																																												
1	1	1		1																																												
3(c)(i)	<table style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th colspan="2"></th> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="2">C</th> <th>0</th> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <th>1</th> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table>			AB						00	01	11	10	C	0	0	0	0	1	1	0	0	1	1		1																						
		AB																																														
		00	01	11	10																																											
C	0	0	0	0	1																																											
	1	0	0	1	1																																											
3(c)(ii)	<table style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th colspan="2"></th> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="2">C</th> <th>0</th> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <th>1</th> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table>			AB						00	01	11	10	C	0	0	0	0	1	1	0	0	1	1		2																						
		AB																																														
		00	01	11	10																																											
C	0	0	0	0	1																																											
	1	0	0	1	1																																											
3(c)(iii)	$X = A.\bar{B} + A.C$ 1 1		2																																													
3(d)	$X = A.(\bar{B} + (B . C))$ $X = A.(\bar{B} + C)$ $X = A.\bar{B} + A.C$	1 1 (dependent mark – must be correct outcome from previous line)	2																																													

Question	Answer	Marks																																	
4(a)(i)	2 marks all products correct, 1 mark 2 or 3 products correct $X = \bar{A}.B.\bar{C} + \bar{A}.B.C + A.\bar{B}.\bar{C} + A.\bar{B}.C$	2																																	
4(a)(ii)	1 mark for all correct bits <div style="text-align: center;"> <table border="1"> <tr> <td colspan="2"></td> <td colspan="4">AB</td> </tr> <tr> <td colspan="2"></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td rowspan="2">C</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> </table> </div>			AB						00	01	11	10	C	0	0	1	0	1	1	0	1	0	1	1										
		AB																																	
		00	01	11	10																														
C	0	0	1	0	1																														
	1	0	1	0	1																														
4(a)(iii)	1 mark for each correct loop <div style="text-align: center;"> <table border="1"> <tr> <td colspan="2"></td> <td colspan="4">AB</td> </tr> <tr> <td colspan="2"></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td rowspan="2">C</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> </table> </div>			AB						00	01	11	10	C	0	0	1	0	1	1	0	1	0	1	2										
		AB																																	
		00	01	11	10																														
C	0	0	1	0	1																														
	1	0	1	0	1																														
4(a)(iv)	1 mark per bullet – allow follow through from 4(a)(iii) <input type="checkbox"/> $\bar{A}.B$ <input type="checkbox"/> $A.\bar{B}$ $X = \bar{A}.B + A.\bar{B}$	2																																	
4(b)(i)	1 mark per bullet max 2 <input type="checkbox"/> Correct column headings and row headings – values only <input type="checkbox"/> Correct column headings and row headings – order 1 mark for 2 correct rows/columns, 2 marks for 4 correct rows/columns (based on headings) max 2 <div style="text-align: center;"> <table border="1"> <tr> <td colspan="2"></td> <td colspan="4">AB</td> </tr> <tr> <td colspan="2"></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td rowspan="4">CD</td> <td>00</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>01</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>11</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>10</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> </table> </div>			AB						00	01	11	10	CD	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	4
		AB																																	
		00	01	11	10																														
CD	00	0	1	1	0																														
	01	0	1	1	0																														
	11	0	1	0	0																														
	10	0	1	0	0																														
4(b)(ii)	1 mark for each correct loop <div style="text-align: center;"> <table border="1"> <tr> <td colspan="2"></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td rowspan="4">CD</td> <td>00</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>01</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>11</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>10</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> </tr> </table> </div>			00	01	11	10	CD	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	2						
		00	01	11	10																														
CD	00	0	1	1	0																														
	01	0	1	1	0																														
	11	0	1	0	0																														
	10	0	1	0	0																														

4(b)(iii)	1 mark per bullet $\bar{A}.B$ $+B.\bar{C}$ $X = \bar{A}.B + B.\bar{C}$	2
-----------	--	----------