

Resonance & Fourier components (3-1)


$f_0 \approx 15 \text{ kHz}$ for easy numbers.

put in $f_{sq} = 5 \text{ kHz}$, $\times \sqrt{1/3} f_0$ so that

we have $V_{sq} = A \left(\sin(2\pi f_{sq} t) + \frac{1}{3} \sin(6\pi f_{sq} t) + \frac{1}{9} \sin(10\pi f_{sq} t) \right)$

$$|\Phi(\omega)| = \begin{bmatrix} 3.5 \cdot 10^{-9} & f_{sq} \rightarrow \text{blocked} \\ 8.5 \cdot 10^{-8} & 3f_{sq} \rightarrow \text{passed} \\ 1.1 \cdot 10^{-8} & 5f_{sq} \rightarrow \text{blocked} \end{bmatrix}$$

Decay.

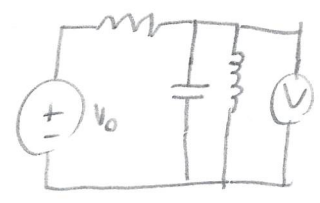

$V_0 = V_R + V_C = V_R + V_L$


$= RI + \frac{1}{C} \int Idt = RI + L \dot{I}$

take time derivative

$0 = R \dot{I} + \frac{1}{C} I_C = R \dot{I} + L \ddot{I}_L$ also,

$I = I_C + I_L \Rightarrow \dot{I} = \dot{I}_C + \dot{I}_L$

Diodes. (3-6)

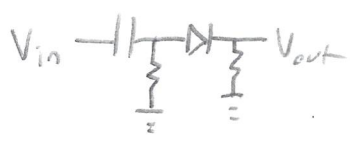


Idealized diodes: $V_D < 0.6, I = 0$
 $V_D \geq 0.6, I = \text{anything}$

Real diode: has some physical parameters

- IV curve \rightarrow see dohasheet
- capacitance!

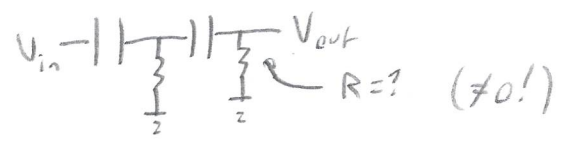Question for class: what happens if you remove $2.2 \text{ k}\Omega$?



Setting up HW3 problems.

1. Transfer function. Ex. high pass from my lecture on 19/4/11. $\tau = RC$

$$V_{in} \rightarrow \begin{array}{c} \text{---} \\ | \\ C \\ | \\ \text{---} \\ | \\ R \\ | \\ \text{---} \\ \text{---} \end{array} V_{out} \quad \tilde{\Phi}(\omega) = \frac{R}{R + i\omega C} \cdot \left(\frac{i\omega C}{i\omega C} \right) = \frac{i\omega C}{1 + i\omega C}$$

Then, in frequency/spectral domain, $\tilde{V}_{out}(\omega) = \tilde{V}_{in}(\omega) \tilde{\Phi}(\omega)$

Fourier transform. (Hint is very useful!)

$$\begin{aligned} V_{in}(t) = A \sin \omega_0 t &\Rightarrow \tilde{V}_{in}(\omega) = A \int_{-\infty}^{\infty} dt e^{-i\omega t} \sin(\omega_0 t) \\ &= A \int_{-\infty}^{\infty} dt \frac{e^{i\omega_0 t} - e^{-i\omega_0 t}}{2i} e^{-i\omega t} \\ &= A \frac{\pi}{i} \left[\frac{1}{2\pi} \int_{-\infty}^{\infty} dt e^{-i(\omega - \omega_0)t} - \frac{1}{2\pi} \int_{-\infty}^{\infty} dt e^{-i(\omega + \omega_0)t} \right] \\ &= A \frac{\pi}{i} [\delta(\omega - \omega_0) - \delta(\omega + \omega_0)] \end{aligned}$$

2. Circuit response. Table at end of Laplace 1.2 (also 19/4/11).

See Laplace transforms notes (2) attached!

Stepped input example.

"

1.2

"

"

3. Fourier series of a square wave. Fourier notes Eq. 1.10 +

$$\begin{aligned} \tilde{C}_n &= \frac{1}{T} \left[\int_{-T/2}^0 dt (-1) e^{-ik\omega_0 t} + \int_0^{T/2} dt (+1) e^{ik\omega_0 t} \right] \\ &= \frac{1}{i k \omega_0 T} \left[-e^{-ik\omega_0 t} \Big|_{-T/2}^0 + e^{ik\omega_0 t} \Big|_0^{T/2} \right] \\ &= \frac{1}{i k \omega_0 T} \left[-1 + e^{ik\omega_0 T/2} + e^{-ik\omega_0 T/2} - 1 \right] = \frac{1}{i k \omega_0 T} \left[2 - 2 \cos(k\omega_0 T/2) \right] \Rightarrow \frac{4}{\pi} \cdot \left(1, \frac{1}{3}, \frac{1}{5}, \dots \right) \end{aligned}$$

$\omega_0 T = 2\pi, \quad \cos(n\pi) = \begin{cases} 1 & \text{odd} \\ 0 & \text{even} \end{cases}$


Phys 120 "guest" lecture: Laplace transforms (2)

19/4/11

Time evolution of circuit elements:

Element	$t=0^+$	$t=\infty$
R		
L		
C		
I		
V		

Stepped input.

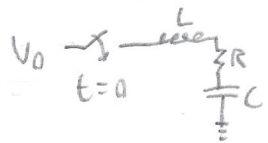

$$-V_0 + LI + RI + \frac{1}{C} \int_0^t dt' + V_C(0^-) \quad (t)$$

Transforming

$$-V_0/s + sLI + RI + \frac{I}{Cs} + \frac{V_C(0^-)}{s} = 0 \quad (s)$$

Solve,

$$I(s) = \frac{V_0}{L} \frac{1}{s^2 + 2ks + \omega_0^2} \quad k = R/2L$$

$$\omega_0 = 1/\sqrt{LC}$$

with roots a & a^* . $a = -k + i\sqrt{\omega_0^2 - k^2}$

$$I(s) = \frac{V_0}{L} \frac{1}{(s-a)(s-a^*)}$$

$$I(t) = \frac{V_0}{L} \frac{1}{2\pi i} \int_C ds \frac{e^{st}}{(s-a)(s-a^*)}$$