

Comparator basics.

311 411 + BJT



The comparator is NOT designed to output anything but the two DC levels hooked to the "collector" or "emitter".

Differences in specsSlew rate (411) \Leftrightarrow Response time (311)

$$\sim 10 \text{ V}/\mu\text{s}$$

$$\sim 150 \text{ ns for max } \Delta V \sim 30 \text{ V}$$

$$\rightarrow \frac{30 \text{ V}}{150 \text{ ns}} = \boxed{200 \text{ V}/\mu\text{s}} \quad (20 \times 411!)$$

Comparable to slew rate.

Output currents

	411: $I_o \leq 25 \text{ mA}$	at $V_{out} = 10 \text{ V}$
	10 mA	12.5 V
	0 mA	15 V
<hr/>		
311:	100 mA	5 V
	45 mA	10 V
	40 mA	15 V


311 can drive significantly more current! This is useful, but its fast response is very useful, especially in the primary application of comparators — digital logic! We'll see more of this in

Lab 10.

Schmitt trigger.

The positive feedback with attenuation gives this circuit a "memory" of sorts, by reacting to a threshold crossing with an instantaneous change in the threshold level.

This change is called hysteresis.

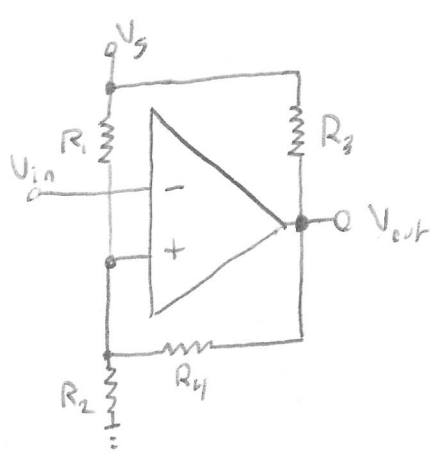


KCL: $\frac{V_+ - V_S}{R_1} + \frac{V_+ - 0}{R_2} + \frac{V_+ - V_{out}}{R_4} = 0$ (V_+ node)

$V_{out} = 0$: $V_+^0 = \frac{R_4 R_2}{R_2 R_1 + R_4 R_1 + R_4 R_2} V_S$
 $= \frac{R_2}{R_1 + R_2} \left[1 - \frac{R_1}{R_4} \frac{R_2}{R_1 + R_2} \right] V_S + \mathcal{O}(R_4^{-2})$



$V_{out} \neq 0$: $V_+^1 = \left[\frac{R_2 R_4 (2R_1 + R_4)}{(R_4 R_2 + R_1 R_4 + R_1 R_2)(R_1 + R_4) - R_1 R_2 R_3} \right] V_S$
 $= \frac{R_2}{R_1 + R_2} \left[1 + \frac{R_1}{R_4} \right] V_S \approx V_+^0 + \frac{R_1}{R_4} \left(1 - \frac{R_2}{R_1 + R_2} \right)$

Hysteresis.

Rising input:

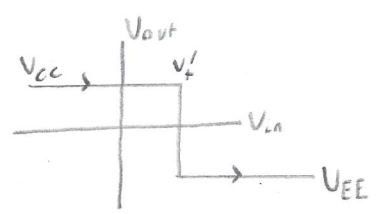

Falling input:

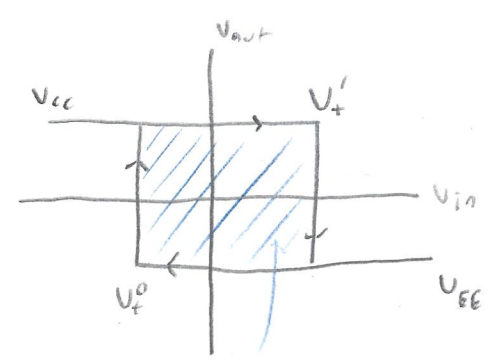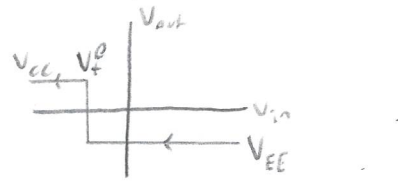

Hysteresis region!

This prevents oscillations in the output caused by noise at the input.