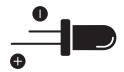












FOLD
&
PAPER CLIP

WHAT YOU NEED

-  LED
-  Battery
-  Paper Clip
-  Copper Tape
-  Regular Tape

HOW TO

- 1) Fold along the dotted lines. (.....)
- 2) Lay your  copper tape along the pathways. (—————)
- 3) Fold the legs of your  LED outward.
- 4)  Tape down the LED to the paper.
- 5) Secure the legs with the  regular tape.
- 6) Place your  battery between the two flaps of paper.
- 7) Secure with the  Paper Clip.

HINTS

Copper Tape

Apply the conductive copper tape as one continuous line.
Copper tape which is broken up won't conduct well.
There's no need to put any regular tape on top of the copper tape.

LEDs

The long legs are Positive and the short legs are Negative. They need to match up with the Positive and Negative from the battery.



If your LED is taped down and does not turn on, flip the battery in your holder.



What's Your **BIG** idea?

