



Designing Your Own Amplifier

by Norman H. Crowhurst

Part V: Feedback Amplifiers

THERE are so many matters to consider in the design of a feedback amplifier that discussion of them will get rather confusing unless we use a practical amplifier for illustration. In this article let us work with the schematic diagram in Fig. 1, which shows the outline of a circuit with the components identified by numbers, and complete the design of this feedback amplifier step by step, filling in the values as we determine them. In this way we shall be sure to cover the practical problems that have to be solved.

A good feedback amplifier cannot be obtained by designing a reasonably good amplifier and then adding feedback for good measure. This approach, believe it or not, can sometimes produce an amplifier with greater distortion than one that does not employ feedback. The first thing to do is to go through the amplifier, starting at the output, and calculate the operating conditions for the tubes and the maximum levels they will handle, incorporating or allowing for feedback as we go.

Output Stage

Let's assume that we are designing a good 20-watt amplifier. For self-biased 6L6's in the output stage, the tube data manual shows the following tabulation of operating conditions for 24 watts output, with an optimum load of 9,000 ohms.

6L6's IN CLASS AB₁ (Values for 2 Tubes)

	Zero Signal	Maximum Signal
Plate voltage	360 v	360 v
Plate current	88 ma	100 ma
Screen voltage	270 v	270 v
Cathode resistor	250 Ω	250 Ω
Load	9 K	9 K
Power output	—	24 w
Harmonic dist.	—	4 %

We will assume that we shall use such an output circuit. That sets the cathode bias resistor, R17, at 250 ohms.

This 24 watts in the plate circuit will


be mean or average maximum watts, so the peak value will be twice this, or 48 watts. The formula $W = V^2/R$ can be altered to the form $V = \sqrt{WR}$, to determine the peak maximum-signal voltage across the primary winding of the output transformer. This is $\sqrt{48 \times 9,000}$ or 650. Then there will be a peak voltage of 325 volts on each half of the primary. We shall need this figure presently to calculate the inner feedback loop values of R15 and R16.

Next we move back to the grid circuit of the output stage. The total cathode current of the two 6L6's at maximum output is just under 120 ma. This current, in the 250-ohm bias resistor, will produce a bias of 29 volts at maxi-

prove convenient, because the feedback places extra demands on the paraphase action, as we shall see in a moment.

Using a plate-load resistor of 100 K, with a cathode resistor of 2.2 K and a plate supply of 250 volts at the junction of the three resistors R12, R13, and R14, will give a gain of approximately 13. These values will produce 3.7 volts bias with 1.7 ma plate current. The plate current of two tubes will be 3.4 ma and the drop in the common resistor, R14, will be 110 volts, from 360 to 250. This means that R14 should be about 33 K.

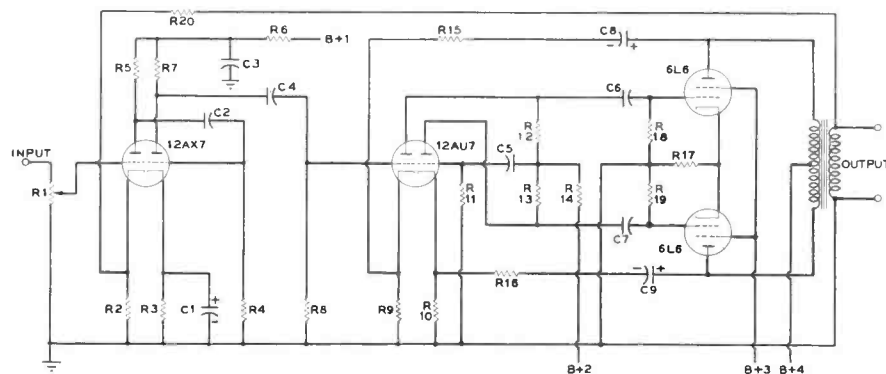Now we must digress a moment to consider the voltages involved in the inner feedback loop. The purpose of this loop is to reduce the plate resistance



imum signal; which means the peak drive to each grid for maximum output also needs to be 29 volts.

Drive Stage; Inner Loop

The 12AU7 tube, shown in the drive stage, is similar to the 6SN7 except that it happens to be of the miniature type. In the article on the design of phase inverters it was found that a floating paraphase circuit could quite successfully provide a drive of about 29 volts to each output tube grid with a plate supply of 250 volts. We can obtain a good safety margin here by utilizing the plate supply for the 6L6's for the B+ to the 12AU7 tube, which is 360 volts. This will

Fig 1. Schematic for a feedback amplifier, whose design is developed in the text. The inner feedback loop uses components C8, C9, R9, R10, R15 and R16. Over-all feedback loop uses R2 and R20.

of the output stage to a point at which variations in output load impedance will not cause appreciable changes in the outer-loop feedback, thereby improving stability under varying load conditions. The plate resistance of the tubes is not listed, because it varies widely over the operating distance of the load line. A good estimate, however, would be that its average value throughout a signal cycle will not vary much more than

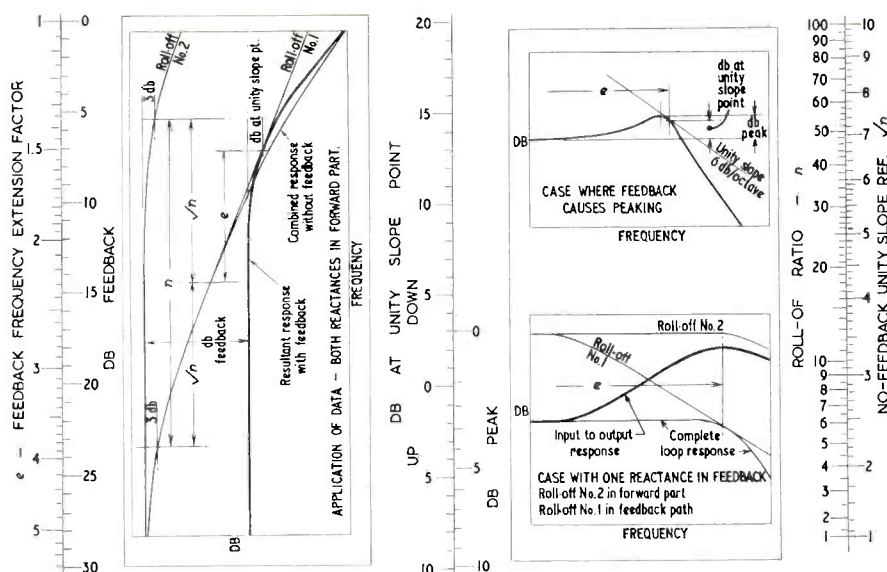


Fig. 2. This alignment chart is useful for computing the performance of feedback loops over two stages, or using two reactances contributing to rolloff at each end of the response. Use of a straight-edge across the scales gives all the information necessary to evaluate either low-frequency or high-frequency response. Diagrams show significance of quantities for high-frequency rolloffs.

about five times the optimum load resistance. Thus, if we can reduce this effective ratio by 5:1, using the inner loop, a change of load impedance from optimum value to open circuit will only change the outer-loop feedback by a 2:1 factor. This is an economic point to choose: further reduction will make unreasonable demands on the drive stage that will not produce commensurate advantage in the outer-loop stability; less reduction will sacrifice much in potential outer-loop stability.

Having settled that we need a 5:1 gain reduction by this inner loop, we can figure values and voltages. A gain of 13 from grid to plate of 12AU7 means that its grid-to-cathode swing has to be $29/13 = 2.2$ volts approximately. To reduce gain by 5:1, the grid-to-ground voltage must be $5 \times 2.2 = 11$ volts, while the cathode-to-ground voltage will be the difference, 8.8 volts. To get 8.8 volts across the cathode resistors, R9 and R10, from the 325 volts on the output tube plates, the feedback resistors R15 and R16 must be $2.2 \text{ K} \times 325/8.8 = 81 \text{ K}$. The nearest preferred value is 82 K, which will be close enough.

A voltage of 325 across a resistance of 82 K works out to almost 1 watt peak dissipation, so 1-watt resistors should be used. This indicates that these feedback resistors will absorb about 1 watt of available output, so if the output transformer is reasonably good, there should still be 20 watts left at the secondary.

The left-hand half of the 12AU7

will get its 11 volts grid-to-ground drive from the previous stage, but the right-hand half gets it from the floating paraphase junction.

The junction of the three plate resistors coupled to the grid of the second half of the 12AU7 by C5 has to produce a swing of 11 volts to match that of the first half; this must be produced by having the plate current swing of the first half greater than that of the second half by a sufficient amount to produce 11 volts swing in R14.

With our assumed plate-load resistors, 100 K, and a plate swing of 29 volts, each tube should have a swing of about 0.35 ma. To get a swing of 11 volts across the 33-K resistor R14, we need a difference in swing of 0.33 ma. If we choose values such that the average swing is 0.35 ma, and the difference in swing is 0.33 ma, we will need a swing of 0.52 ma on the first half tube and 0.18 ma on the second half tube. This you can figure by algebra or by any method you prefer.

The first, or left-hand, half of the 12AU7 must produce $29 - 11$ volts across R12, because the 11 volts is in phase with this output; the current swing is 0.52 ma, so R12 should be $18/0.52 = 35 \text{ K}$. 33 K at 5% would be near enough. For the right-hand half, the current swing is to be 0.18 ma; the voltage swing, $29 + 11 = 40$ volts, so R13 must be $40/0.18 = 220 \text{ K}$. This will provide equal drive for both output grids. The operating conditions of the two halves of the 12AU7 will differ slightly, but any residual differences can now be taken care of by feedback, using close-tolerance values for resistors R9, R10, R15, and R16.

Thus we have now calculated the important values associated with the 12AU7 and 6L6 tubes. The grid resistors, R18 and R19, can be 330 K. This will be an approximate compromise between shunting down the 12AU7 too much and providing too high a resistance in the grid circuits of the 6L6 tube. The grid resistor, R11, can be 1 M Ω , to avoid shunting to any appreciable extent the 11 volts provided by the difference current. We shall consider R8 in the design of the 12AX7 amplifier stage.

First Stage; Over-all Feedback

Turning to the 12AX7 data we find that, with a plate resistor of 100 K, a plate-supply voltage of 180 volts, and the following grid resistor of 470 K, each tube section gives a gain of 52 and a peak output of 32 volts. Since we require only a peak of 11 volts, this gives a margin of approximately 3:1; distortion should be well down even before feedback is applied. The cathode resistor recommended with the following grid resistor of 470 K is 2,200 ohms. This data was obtained from the RCA tube manual. Similar information

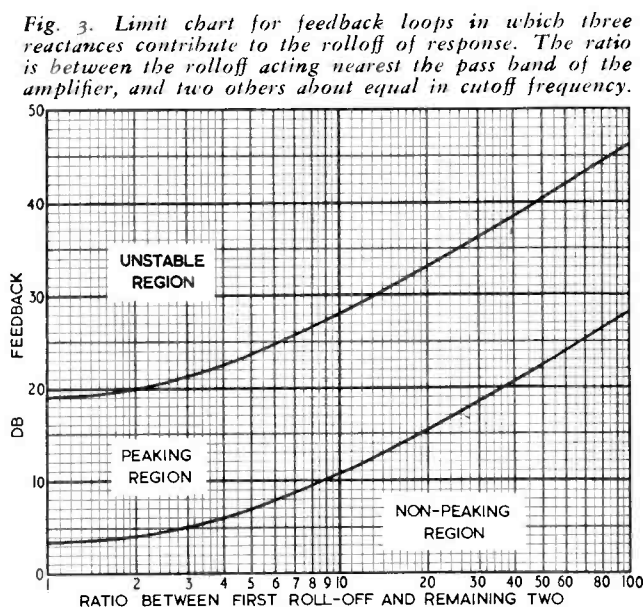


Fig. 3. Limit chart for feedback loops in which three reactances contribute to the rolloff of response. The ratio is between the rolloff acting nearest the pass band of the amplifier, and two others about equal in cutoff frequency.

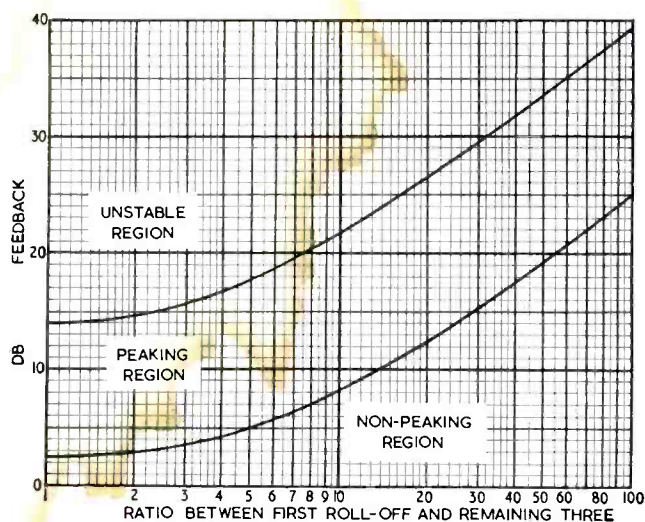


Fig. 4. Limit chart for feedback loops in which four reactances contribute to the rolloff at one end of the response.

could be obtained from any other manual, although the figures may differ a little, or data could be based on published curves as described in earlier articles.

Two stages, each giving a gain of 52, will produce a total over-all gain of about 2,700. If the output from these stages is to be 11 volts, the input must be about 4 mv.

We would like to end up with a damping factor of about 10. Therefore we must use about 20 db over-all feedback, which will reduce the gain by a ratio of 10:1 and increase the damping factor, at present approximately unity, by 10 times. This means that we will need to supply a signal of 36 mv peak across R2 from the secondary of the output transformer.

Assuming the output transformer is designed to match from 9,000 ohms to 16 ohms, the simplest way of calculating the voltage that should appear on its secondary is to figure out what voltage gives 20 watts across 16 ohms. This is 40 watts, since we are working in peak voltages, so the voltage will be $\sqrt{40 \times 16} = 25$ volts, approximately. Again working by voltage ratio, if we have 36 mv across 2.2 K ohms, R20 will need to be $25,000/36 \times 2.2 \text{ K} = 1.5 \text{ M}\Omega$.

This has given us all the resistance values in the circuit except R6, which we will consider later.

We now know that the amplifier will be driven to full output by an input of 40 mv peak, which is about 28 mv RMS. This is quite a convenient input, because it will produce full output on some low-level inputs. We might want to use a preamp, however, in which case 28 mv would be too small an input: most preamps have a normal output in the region of 1 volt. To take care of this we can insert a preset gain control

R1, for which a suitable value would be 250 K.

Low-Frequency Response of Inner Loop

Now we must tackle the question of suitable values of coupling and other capacitors. This is where the stability criterion and response factors of the feedback arrangement become important.

First we take the short-loop feedback; this includes, at the low-frequency end, the coupling capacitors C6 and C7 in the feedback loop. There are then two sets of reactor elements in this feedback loop. We want to keep the response of this section as flat as possible, and roll it off fairly sharply at the end of a band somewhat wider than the response band we ultimately require.

The charts in Fig. 2 are useful in the design of two-stage coupling arrangements with feedback. They give the response around the loop when the feedback is closed. To avoid any possibility of transient effects, the response should be not less than 6 db down on the scale on the left-hand side of the center line.

We are using a feedback ratio of 5:1, which represents 14 db. Aligning these two points, 14 db at the left, with 6 db in the center, we find that the rolloff ratio on the right-hand scale has to be almost 20. If C8 and C9 were not in the feedback loop—that is, if the output were taken across resistors R15 and R16 directly—then the rolloff would be 6 db down at a frequency determined by dividing the midway frequency, between the rolloffs given by C6 and C7 and their associated resistances, by the factor 2.24 (found on the left-hand side of the left-hand scale, opposite 14 db).

But C8 and C9 are in the feedback loop, and their reactance is included in series with the resistances R15 and R16 in determining the output voltage. So, if the low-frequency rolloff provided by C8 and C9 is 20 times that provided by

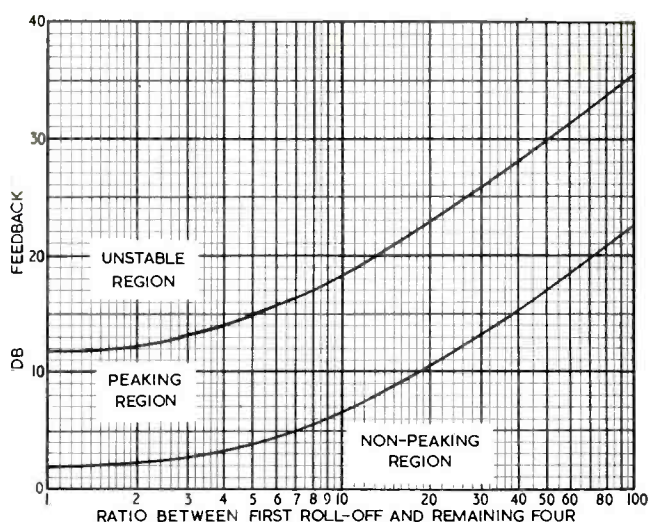


Fig. 5. Limit chart for feedback loops in which five reactances contribute to the rolloff at one end of the response.

C6 and C7, the resultant loop response would be about 6 db down at a frequency 2.24 times that of the rolloff at C6 and C7. But at this frequency the reactance of C8 and C9 would be about 9.5 times the resistance values of R15 and R16, which means there would be a boost of almost 20 db, added to the loss of 6 db, producing a resultant peak of about 14 db at this frequency.

To avoid this effect it is necessary to have the rolloff provided by C8 and C9 operate at a frequency lower than that provided by C6 and C7. Then we shall be perfectly safe, and the effective rolloff frequency will be much lower than that without feedback. Therefore, we pick values of C6 and C7 to give a rolloff at 20 cps. With R18 and R19 at 330 K, the reactance of C6 and C7 should be somewhere around 330 K at 20 cps. A suitable capacitor value is .025 μfd .

Now we need a value for C8 and C9 that will roll off at 1/20th of this frequency, or at 1 cps. The reactance required is 82 K; a capacitor to give a reactance of 82 K at 1 cps is 2 μfd . Small tubular electrolytics can be obtained with a capacitance of 2 μfd at a working voltage of 450 volts. These should be quite satisfactory for C8 and C9. The signal-voltage swing at this point is 325 volts peak, so any leakage current is not likely to introduce noticeable noise in the circuit. The 14 db of feedback over this output loop will reduce the effective rolloff point of C6 and C7 by a ratio of 5:1, so that now the rolloff of these two stages will be 3 db at about 4 cps.

To avoid unbalance, or phase shifts at the low-frequency end, C5 should roll off well below 4 cps in conjunction with the 1-M Ω grid resistor. A 0.25- μfd capacitor gives a reactance of 1 M Ω at about 0.65 cps. This should be quite

satisfactory for this position in the circuit.

High-Frequency Response of Inner Loop

The high-frequency end is not so simple to evaluate in exact terms. We can only make a guess at it. The plate resistance of the 12AU7 is listed at 7,700 ohms. This will be from each plate to ground, and the capacitance shunting this resistance will be that of the stray wiring including the coupling capacitors C6 and C7, which are quite small physically, and the grid input capacitance of the 6L6's. This should not add to more than about 50 μf d altogether, which has a reactance of 7,700 ohms at about 400 Kc.

To comply with the no-transient-distortion condition previously specified, we need to have a 20:1 ratio in high-frequency rolloff frequencies. In the output circuit, the 6L6 has a plate-to-plate load resistance of 9,000 ohms, which takes the form of 2,250 ohms from each plate to ground. The plate resistance will be about 10 times this value, or 22,500 ohms per tube. Assuming the amplifier is correctly loaded with its 9,000 ohms plate-to-plate, the impedance at each plate will be about 2,000 ohms to ground, or 8,000 ohms plate-to-plate. This should then be bypassed with a capacitor that will give a rolloff at 20 Kc. At 20 Kc a reactance of 8,000 ohms would be given by a .001- μf d capacitor, connected across the primary of the output transformer.

Without feedback this would give a rolloff of 3 db at 20 Kc. The effect of the feedback, with the staggered roll-

Now we can proceed to determine the circuit constants for the rest of the amplifier to suit the 20 db feedback applied over-all.

The reactances contributing to low-frequency rolloff are the coupling capacitor C2, the coupling capacitor C4, the pair of coupling capacitors already considered, C6 and C7, and the primary inductance of the output transformer. Thus the main feedback loop has four reactance stages that contribute to low-frequency rolloff. This means we can use the limit chart of Fig. 4 to determine the ratio of rolloff frequencies to be used (Figs. 3 and 5 are similar charts for three and five reactance stages, respectively). These charts give the ratio by which one cutoff frequency should be nearer the pass band of the amplifier than the remaining ones, in order to determine the criterion of stability and also the point at which peaking begins to occur.

If we can make one of the RC networks have a rolloff frequency about 50 times higher than the remaining three, we shall almost avoid peaking completely, and have a very good stability margin. As we have already made the output end of the amplifier look like an arrangement with a rolloff at 4 cps, we can proceed to make the rest of the amplifier look like this and arrange for one capacitor to roll off at 200 cps.

The primary inductance of the output transformer should not show a loss of more than 3 db at 4 cps at low levels, if it is not to distort at 20 cps, because pentode tubes run into distortion quite quickly with elliptical loads. If a high-quality output transformer is being used to avoid this distortion, the inductance

feedback provided is 20 db, so this will extend the rolloff downwards, by a factor of 10:1, to 20 cps. The rolloff at 20 cps will be considerably sharpened by the fact that it is not a single reactance rolloff, but that by now the other three reactances around the loop are contributing. It is a good feature to have a sharp rolloff below 20 cps to filter out rumble and other undesirable effects.

The 12AX7 stage will give an output of 32 volts peak successfully. The signal handled by the first tube section is normally only 52×4 mv peak, a little more than 200 mv. When the feedback disappears, because of the reactance of C2 at 20 cps, the voltage swing at the plate of the first half of the 12AX7 will rise to about 10 times this value, or a little over 2 volts, which is still well within the voltage-handling margin of the tube.

We can see now why C2 is the best place to put the smaller coupling capacitor. If C4 were used for this extra rolloff purpose, the signal amplitude at the plate of the second half of the 12AX7 would also be multiplied by 10 times at the bottom end of the frequency band, and there is not enough margin to allow for this. The signal there is already 11 volts peak; 10 times this would raise the signal to 110 volts peak, which the 12AX7 should certainly not be expected to deliver.

High-Frequency Response, Outer Loop

Applying the same reasoning to the high-frequency rolloff, there are four high-impedance points that will be shunted by different capacitance values: the first and second plates of the 12AX7, each plate of the 12AU7, which is in push-pull, and the plates of the 6L6's, also in push-pull.

The effective rolloffs of the last two have been modified by the inner-loop feedback arrangement so that both are effectively at 190 Kc. The plate resistance of the 12AX7 is quoted at 62.5 K, but for a higher operating level than is used here. An estimate of 100 K should be safe for this condition. The total capacitance in the grid circuit of the first 12AU7, with 14 db feedback effective, should not be more than about 10 μf d, which has a reactance of 100 K at about 160 Kc. This is reasonably consistent with the pattern so far.

Applying the same method as that used at the low-frequency end, the plate circuit of the first half of the 12AX7 should have a rolloff at about 1/50th of 160 Kc (taking the lower figure), or 3.2 Kc. A capacitor to give a reactance of 100 K at 3.2 Kc is 500 μf d; this we put across the second-stage grid resistor. With 20 db feedback

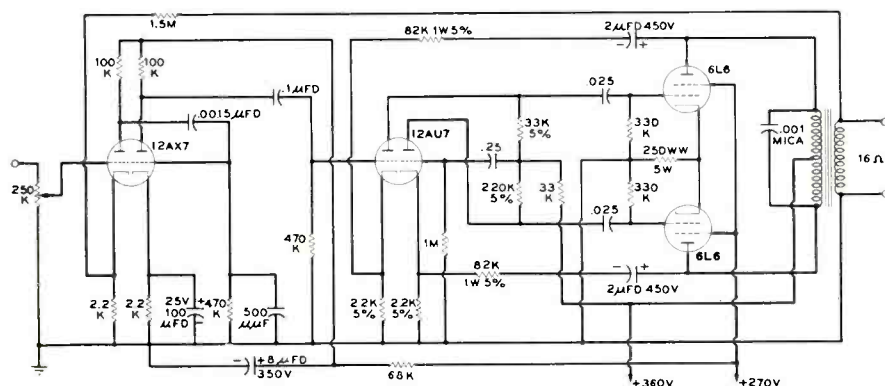


Fig. 6. The complete amplifier circuit, with circuit values and voltages shown.

off arrangement, is to increase the rolloff frequency to about 9.5 times 20 Kc for 6 db loss, or 190 Kc. There will then be no detectable loss at 20 Kc.

Low-Frequency Response, Outer Loop

We have the last two stages designed, complete with feedback, to give rolloffs of 3 db at 4 cps and 6 db at 190 Kc.

of the transformer should be satisfactory. It remains to set the rolloff provided by C4 at 4 cps also; a value of .08 μf d will provide a slight margin for error in tolerance.

Finally, we utilize C2 to provide the earlier rolloff at 200 cps. C2 should then be .0015 μf d, which gives a reactance of 520 K at 200 cps, again allowing a slight margin for tolerance error.

Does not this mean the entire amplifier will now roll off at 200 cps? The

Continued on page 45

AMPLIFIER DESIGN

Continued from page 30

the rolloff frequency will be pushed out to around 32 Kc.

We now have an amplifier with a response sensibly flat from 20 cps to beyond 20 Kc, and with a total of 34 db feedback in the two loops, which is fully effective from 200 cps to 3,200 cps. Beyond these frequencies the amount of feedback available rolls off slightly, but there is still not less than 14 db feedback over the output stage to the extreme limits of the band. As we have taken careful steps to see that the distortion in the absence of feedback is at a minimum, the amplifier should give very good performance.

Power Supply Components

The only components we now have left to specify are those in the power supply. R6 and C3 must reduce a supply voltage of 270 (the same as that for the output tube screen grids) and provide some decoupling. The B+ voltage we need for the 12AX7 tube is 180 volts, so we can allow a 90-volt drop in R6 at a total current drain of 1.2 ma (0.6 ma for each tube section). R6 is accordingly set at 75 K. In practice 68 K will serve, because the voltage here is not critical. C3 can be 8 μ fd, 350 volts working; this will give a reactance of less than 20 K down to 1 cps, and hence cannot interfere with the rolloff frequencies we have just calculated.

The cathode bypass capacitor C1, which is across 2.2 K, should be not less than 100 μ fd, 25 volts working. This will give a reactance of less than 1,600 ohms down to a frequency of 1 cps.

For the B+ supply we need a maximum of 360 volts at a total current drain of about 125 ma. This can be



provided by a power transformer with a 350-0-350 secondary winding, a 5U4 rectifier, and a capacitor-choke-capacitor filter, the design of which has been dealt with elsewhere in this magazine.¹

This article has discussed the complete design of a feedback amplifier, and has introduced all the factors to be considered, as painlessly as possible. From this it will be seen that, taken step by step, there is nothing very difficult about the design of such an amplifier. In the next article of this series, we shall take a step further and consider special kinds of output arrangements and the design factors involved in getting the best out of these circuits.

¹Marshall, Joseph. "Practical Audio Design", AUDIOCRAFT, Jan., Feb., Mar., 1956.

Mercury Living Presence

New HIGH FIDELITY Releases

WORLD PREMIERE RECORDING

VAUGHAN WILLIAMS Symphony No. 8 in D Minor BUTTERWORTH A Shropshire Lad; BAX Garden of Fand. Halle Orchestra, Sir John Barbirolli, conducting. MG 50115

DEBUSSY La Mer; Iberia; Prelude to "The Afternoon of a Faun". Detroit Symphony, Paul Paray conducting. MG 50101

BEETHOVEN Symphony No. 4 in B-flat; Symphony No. 5 in F Major. Minneapolis Symphony, Antal Dorati conducting. MG 50100

SESSIONS The Black Maskers; HOVHANNESS PRELUCE AND QUADRUPLE FUGUE; LO PRESTI The Masks. Eastman-Rochester Orchestra, Edward Hanson conducting. MG 50106

MARCHES FOR TWIRLING—music for baton twirlers. Eastman Wind Ensemble, Frederick Fennell conducting. MG 50113

AMERICA'S BEST SELLER

TCHAIKOVSKY 1812 Festival Overture (original scoring with cannon and bells); Capriccio Italien. MG 50054

HIGH FIDELITY CLASSICS LIVING PRESENCE

SPARKLING HI-FI SOUNDS

THE SPIRIT OF '76 Music for FIFES and DRUMS Based upon the Field Music of the U.S. ARMY from the Revolutionary War to the present day. MG 50111

RUFFLES AND FLOURISHES Music for FIELD TRUMPETS and DRUMS Based upon the Field Music of the Armed Forces from the Revolutionary War to the present day. MG 50112