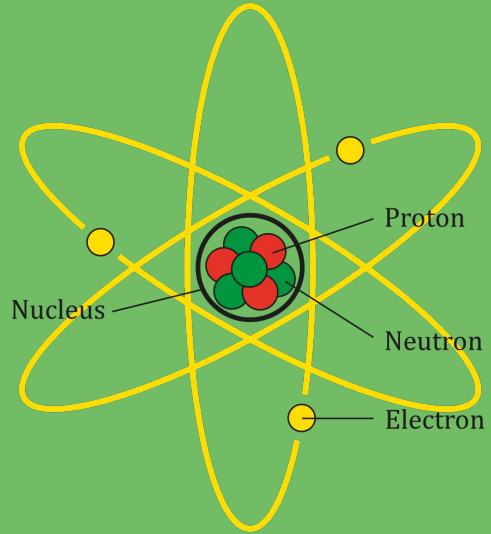


ScienceCraft 

Circuitry

Charge





- ✗ An atom consists of 3 major parts
- ✗ **Protons** have a positive charge
- ✗ **Neutrons** have no charge
- ✗ **Electrons** rotate around the nucleus and have a negative charge
 - ✗ Located in the **orbitals**

Particle	Relative Mass	Relative Charge	Charge / C	Mass / kg
Protons	1	+ 1	+ 1.6 x10 ⁻¹⁹	1.67 x10 ⁻²⁷
Neutrons	1	neutral	0	1.67 x10 ⁻²⁷
Electrons	0.0005	- 1	- 1.6 x10 ⁻¹⁹	9.11 x10 ⁻³¹




What is Electricity?

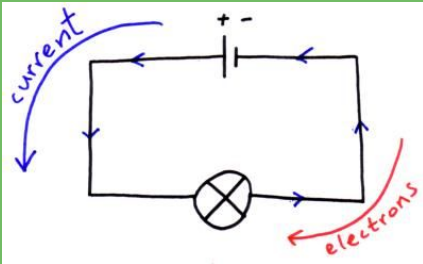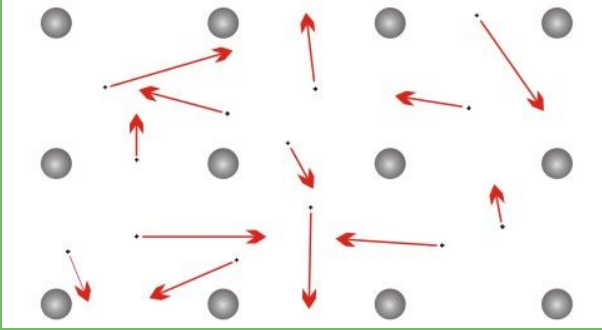


- ✘ **Electricity:** The flow of free electrons between atoms
- ✘ There are many careers working directly with electricity, such as:
 - ✘ **Electricians**, who install the physical hardware and circuitry
 - ✘ **Line Workers**, who install the “power grid” that carries electricity to houses from power plants
 - ✘ **Electrical Engineers**, who design and configure electronics

Conductors vs Insulators

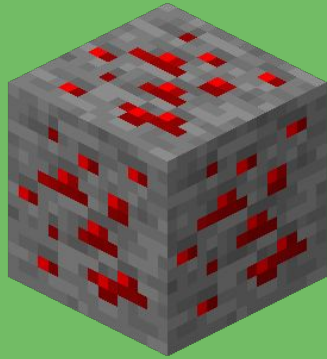


What do you think redstone is?

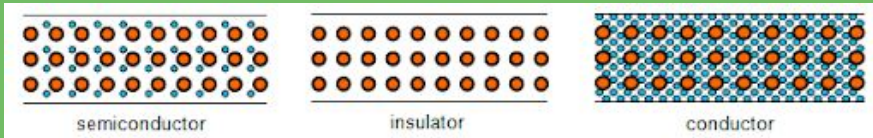


- ✗ **Conductors:** These allow electrons to flow freely through each atom
 - ✗ Generally these are metals such as copper, gold, or aluminium
- ✗ **Insulators:** These inhibit the flow of free electrons
 - ✗ Plastic and rubber tend to be insulators
- ✗ **Semiconductors:** The materials that conduct electricity, but significantly less than a conductor
 - ✗ Silicon is the most commonly cited semiconductor

How is electricity created?

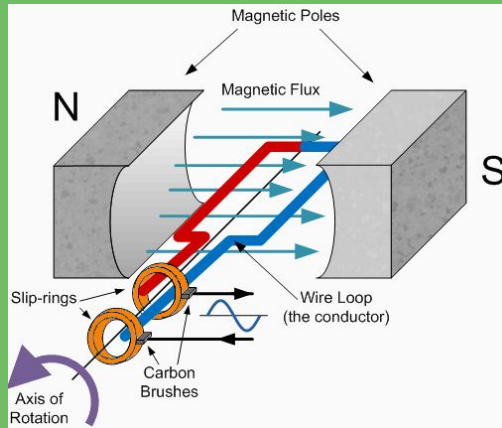


- ✘ **Electromagnetic Induction:** Consists of a conductor being spun in the middle of a magnetic field.
 - ✘ Forces electrons through a circuit, converting mechanical energy into electricity
- ✘ **Real life:** Windmills, solar power, nuclear power, coal, etc.. All of these produce **heat**, and this heat evaporates water, creating steam to spin the conductor.
- ✘ **Minecraft:** Can you name some power sources in Minecraft?

Voltage

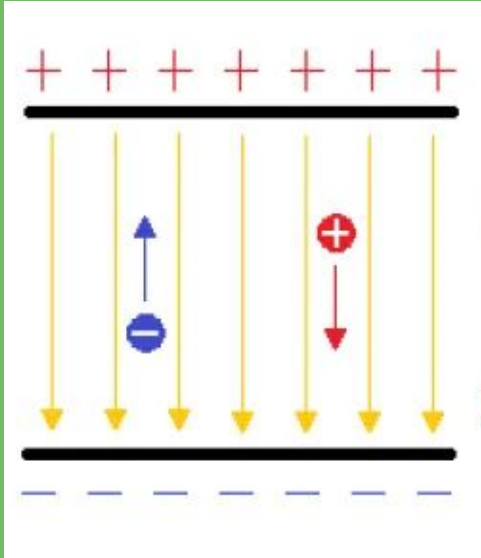

- ✘ **Voltage:** The force that controls the motion of free electrons
- ✘ Voltage is used in reference to the amount of **potential energy** present in a circuit.
 - ✘ Potential energy: The amount of energy that *can* be released within a circuit as a result of an object's charge or its position compared to other objects
- ✘ Can be compared to pressure, and is applied by the **power source**
- ✘ Measured in **Volts**


Resistance

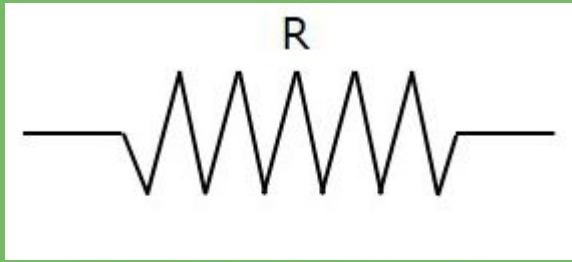

- ✗ When electrons travel through a conductor, they encounter friction and may slow down
- ✗ This effect is known as **resistance**
- ✗ Measured in **Ohms**
- ✗ Resistance is encountered in the **path** of a circuit
- ✗ If a circuit has no resistance, it will short circuit

Quantity	Symbol	Unit of Measurement	Unit Abbreviation
Current	I	Ampere ("Amp")	A
Voltage	E or V	Volt	V
Resistance	R	Ohm	Ω


Circuit Basics

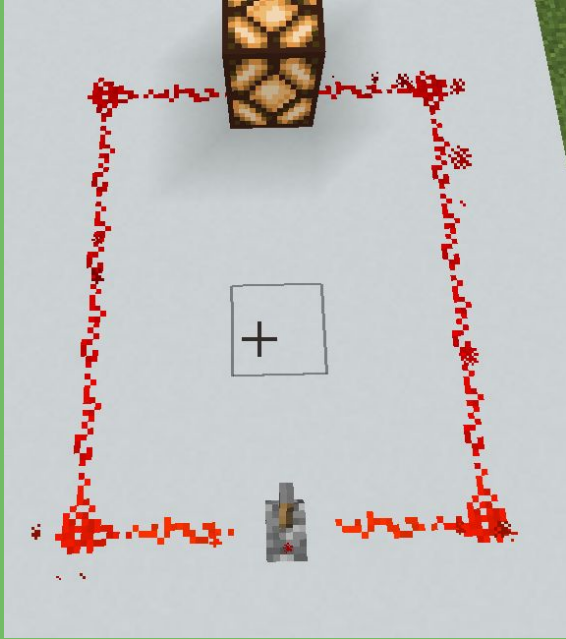

Can you identify power, path, and load?


- ✘ **Electronic Circuit:** Closed loop that electrical current flows through
 - ✘ Consists of **power, path, and load**
- ✘ **Power:** This is your power source, such as a battery. Electricity will flow through the positive and negative terminals of the source.
- ✘ **Path:** The wiring (generally conductors) that enables electricity to flow
- ✘ **Load:** An item on the circuit that consumes the power flowing through it

Ohm's Law

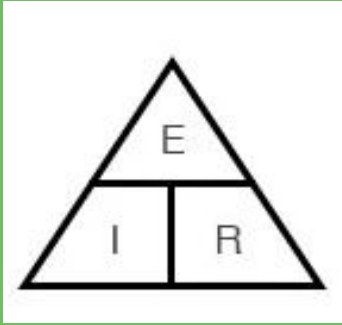


- ✘ $E = \text{Voltage (Volts)}$
- ✘ $I = \text{Current (Amperes)}$
- ✘ $R = \text{Resistance (Ohms)}$

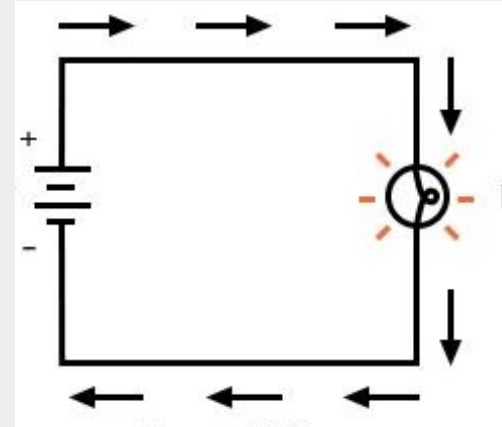- ✘ **Ohm's law** defines the relationship between current, voltage, and resistance.
- ✘ **$E = IR$**
- ✘ Voltage = Current * Resistance




Applying Ohm's Law

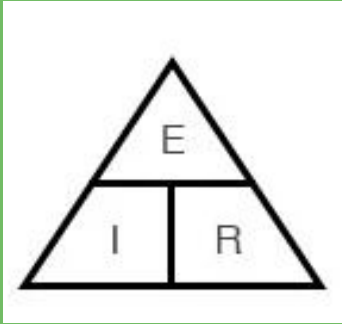


- ✗ E = Voltage (Volts)
- ✗ I = Current (Amperes)
- ✗ R = Resistance (Ohms)

$$E = I \times R$$


✗ Find I (Current)

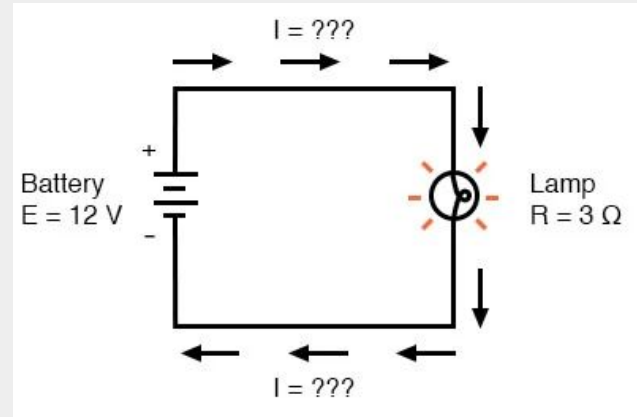

✗ Find R (Resistance)

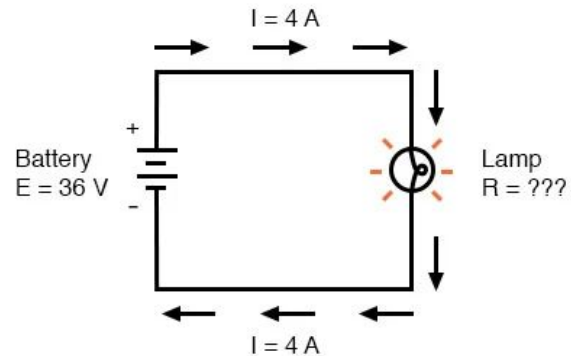

Challenge: Build a circuit

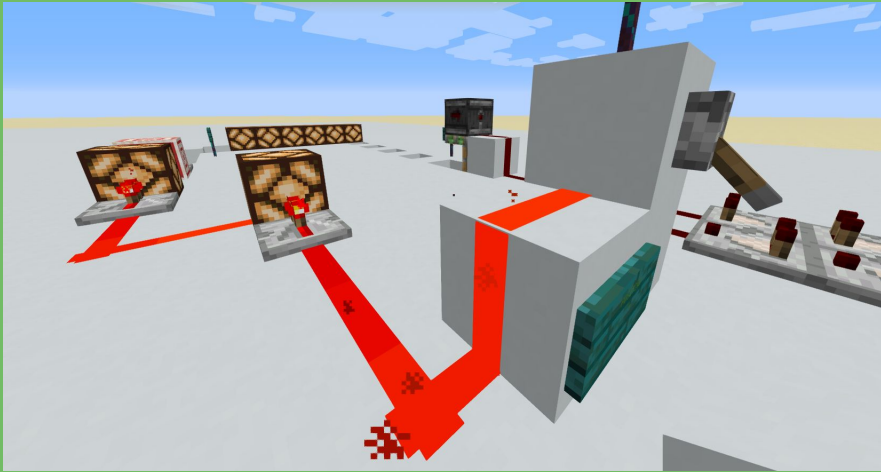

- ✘ Construct a **circuit** – it can be as simple or complicated as you want and can do anything.
- ✘ Try to include **labels** for positive and negative terminals, current, power, path, load, voltage, electron flow direction, and so on.

