

Physics JEEenious


LEARN • THINK • SOLVE • EXCEL

Advanced Test on: **Capacitor Circuit**


Duration: **40 min.**

Multi options correct type

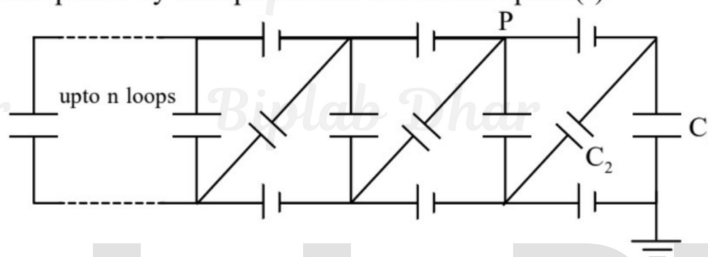- 1) In the diagram shown in the figure all capacitors are of same capacitance C and all cells are of same EMF V . The circuit is repeated by n loops. Choose the correct option(s):



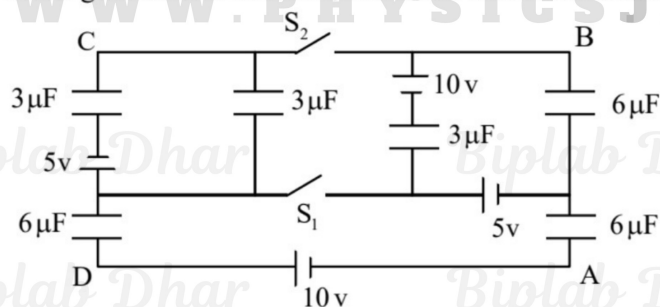
- (A) Potential of point P for $n = 3$ is $10V/7$
(B) Charge on capacitor C_1 for $n = 3$ is $3C/5$
(C) Charge on capacitor C_1 for $n = 4$ is $4C/9$
(D) Charge on capacitor C_2 for $n = 5$ is $6C/11$
- 2) In the given circuit switch S_1 and S_2 are closed simultaneously. Choose the correct option(s):



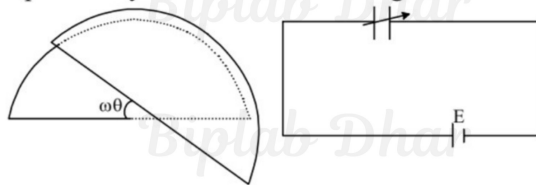- (A) Charge flown through the switch S_1 is $75 \mu C$
(B) Charge flown through the switch S_2 is $9 \mu C$
(C) Potential difference between A and B is steady state is $1V$
(D) Potential difference between D and B is steady state is $11V$

Comprehension type:

A variable condenser or also known as varco is a capacitor whose capacitance can be varied. One type is varied by turning one of its plates clockwise. Suppose that a varco consists of a pair of half circle plate with diameter D separated by a distance d . The varco plate is rotating with angular velocity ω . The other plate is fixed. The plates may have some initial charge.




This varco is connected in a circuit as shown. We will consider $t = 0$ to $t = \frac{\pi}{\omega}$.

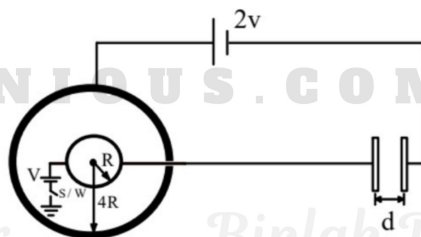- 3) If the current is constant
- The angular velocity is increasing with time
 - The angular velocity is decreasing with time
 - The angular velocity is constant with time
 - It is not possible
- 4) What torque needs to be applied to rotate the plate with constant small angular velocity?
- $\frac{\epsilon_0 E^2 D^2}{16d}$ clock wise
 - $\frac{\epsilon_0 E^2 D^2}{16d}$ anti clock wise
 - $\frac{\epsilon_0 E^2 D^2}{8d}$ clockwise
 - $\frac{\epsilon_0 E^2 D^2}{8d}$ anti clock wise

Comprehension Type:


A parallel plate capacitor is placed at a large separation from two concentric spherical metal shells. The inner shell has radius R and outer one radius $4R$. Separation between the parallel plate capacitors is $d = 3R/16$ and plates are circular discs of radius R (assume the separation to be small compared to R). The outer shell is connected with one of the plates of a parallel plate capacitor with a cell of EMF $2V$, and inner shell is connected with another plate of parallel plate capacitor with a conducting wire. The inner shell is also earthed with a cell of EMF V and a switch as shown in figure. Initially inner shell is given external charge CV . C is the capacitance of parallel plate capacitor. Now answer the following questions.




- 5) When switch is open find the potential of inner shell
- $2V/3$
 - $-\frac{V}{3}$
 - $-\frac{V}{6}$
 - None of these
- 6) When switch is closed find the potential of outer shell
- $4V/5$
 - $7V/5$
 - $4V/3$
 - none of these
- 7) When the switch is closed Find the charge flown through switch
- $\frac{2CV}{5}$
 - $\frac{7CV}{5}$
 - $\frac{3CV}{5}$
 - None of these

Matrix Match Type:

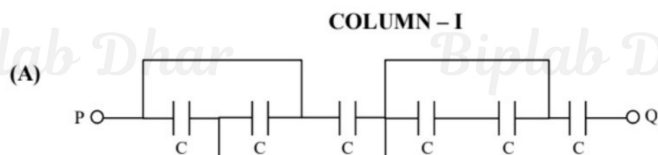- 8) Find equivalent capacitance between P and Q and match the followings:




All capacitors are of 8 micro farads

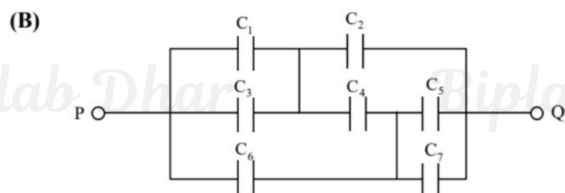


$C_1 = 23 \mu\text{F}$, $C_2 = 7 \mu\text{F}$

$C_3 = 12 \mu\text{F}$, $C_4 = 13 \mu\text{F}$, $C_5 = 1 \mu\text{F}$

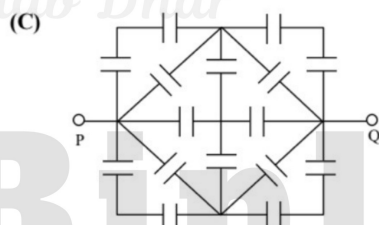$C_6 = 10 \mu\text{F}$, $C_7 = 1 \mu\text{F}$



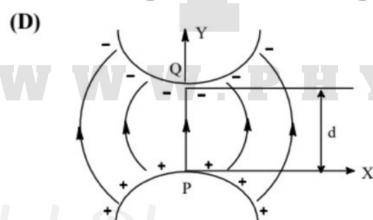All capacitors are of capacitance $3 \mu\text{F}$



Two conductors P and Q are carrying equal and opposite charges $+Q$ and $-Q$ and placed close to each other as shown. If electric field along Y axis is given by $E = \frac{Q}{A \epsilon_0} \left(1 + 6 \frac{y^2}{d^2} \right)$; where $\frac{A \epsilon_0}{d} = 15 \mu\text{F}$.

Find C_{eq} between P and Q.

COLUMN - I

COLUMN - II

(P) 5 micro-Farad

(Q) 6 micro-Farad

(R) 7.5 micro-Farad

(S) 10 micro-Farad