 


LOGIC GATES

BASIC GATES


NOT / INVERTER



TRUTH TABLE


INPUT	OUTPUT
A	$Y = A'$
0	1
1	0

AND

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A.B
0	0	0
0	1	0
1	0	0
1	1	0


OR

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A + B
0	0	0
0	1	1
1	0	1
1	1	1


SPECIAL PURPOSE LOGIC GATES

X-OR

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A XOR B
0	0	0
0	1	1
1	0	1
1	1	0


X-NOR

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1


UNIVERSAL LOGIC GATES

NAND

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	$Y = (A \cdot B)'$
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 


TRUTH TABLE		
INPUT		OUTPUT
A	B	$Y = (A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0


IMPLEMENTATION OF LOGIC GATES USING UNIVERSAL LOGIC GATES

BASIC GATES


NOT / INVERTER

 

AND

 

OR

 

TRUTH TABLE


INPUT	OUTPUT
A	$Y = A'$
0	1
1	0

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A.B
0	0	0
0	1	0
1	0	0
1	1	1

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A + B
0	0	0
0	1	1
1	0	1
1	1	1


Activate Window

X-OR

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A XOR B
0	0	0
0	1	1
1	0	1
1	1	0


X-NOR

 

TRUTH TABLE		
INPUT		OUTPUT
A	B	Y = A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

EX. 3) Design and verification of the truth tables of Half and Full adder circuits.


1. Half adder

 

TRUTH TABLE

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

1. FULL adder

 


TRUTH TABLE

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

EX 4). Design and verification of the truth tables of Half and Full subtractor circuits

1. Half SUBTRACTOR

 


TRUTH TABLE

A	B	D	Bo
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Activate Windows

1. FULL adder


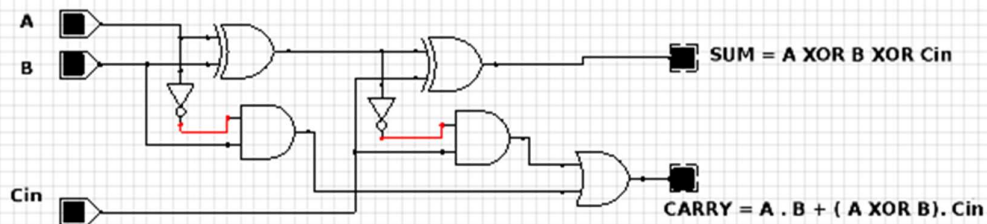


TRUTH TABLE

A	B	BIn	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


1 1 1 1 1

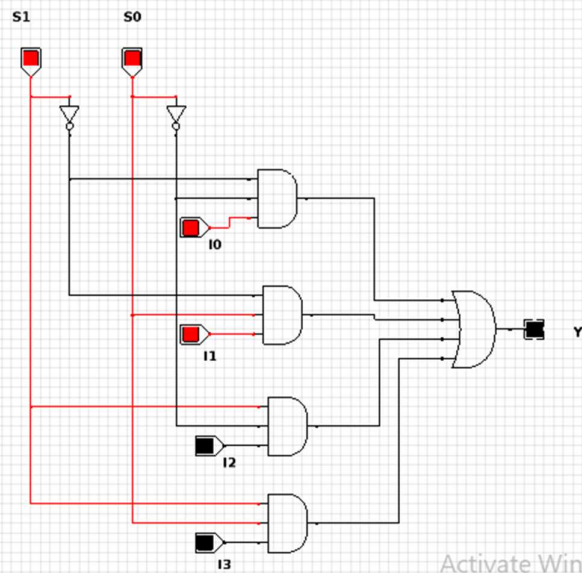 EX. 5) Design and implementation of 4:1 Multiplexer using logic gates




Activate Windows
Go to Settings to activate Windows.

ex.6 Design and implementation of 3:8 decoder using logic gates

 


PRACTICAL 8 : DESIGN SHIFT REGISTER USING FLIP FLOPS

1. SISO

 


CLK	SERIAL	Q3	Q2	Q1	Q0
	I/P				
0	1	0	0	0	0
1	0	1	0	0	0
2	1	0	1	0	0
3	0	1	0	1	0
4	-	0	1	0	1

2. SIPO

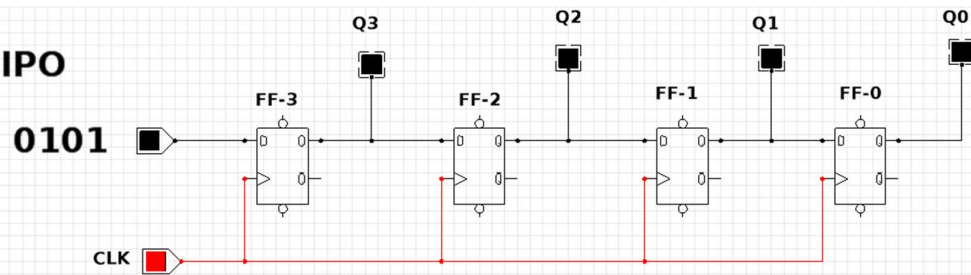


CLK	SERIAL	Q3	Q2	Q1	Q0
	I/P				
0	1	0	0	0	0
1	0	1	0	0	0
2	1	0	1	0	0
3	0	1	0	1	0
4	-	0	1	0	1

UNIVERSAL SHIFT REGISTER

 


S ₂ S ₁	OPERATION
0 0	NO CHANGE
0 1	SHIFT RIGHT
1 0	SHIFT LEFT
1 1	PARALLEL LOAD


BIDIRECTIONAL SHIFT REGISTER

 

 
PRACTICAL 9 : DESIGN RIPPLE UP AND RIPPLE DOWN COUNTER AND MOD-N COUNTER USING FF



2-BIT UP-DOWN ASYNCHRONOUS COUNTER

 

CASE

 


CASE-1 WHEN

M=0


M=0 : 1ST

CLOCK PULSE

→ Q₂Q₁= 00

 


 M=0 : 2ND CLOCK
PULSE $\rightarrow$ $Q_2Q_1 = 01$




M=0 : 3RD CLOCK
PULSE $\rightarrow$ $Q_2Q_1 = 10$

CASE - 2 : M=1 : CLOCK PULSE 1: $Q_2Q_1 = 11$

 


EX. 10 : Design of synchronous up and down counter using flip-flops


2 -BIT UP SYNCHRONOUS COUNTER

 


2-BIT DOWN SYNCHRONOUS COUNTER

 


2-BIT UP-DOWN SYNCHRONOUS COUNTER

 


MOD-6 SYNCHRONOUS UP COUNTER

 


MOD-10 SYNCHRONOUS UP COUNTER

 


3-bit ripple down counter using JK-FF

 


3-bit ripple up counter using JK-FF

 

 
3-bit synchronous down counter using JK-FF



3-bit synchronous up counter using JK-FF

 

4-bit shift register

 

Mod-6 ripple counter using JK-FF

