

Switch-Mode Power Supply Layout

BEST PRACTICES FOR PCBA DESIGN

Gerry Callahan

PCB Carolina 11/12/2025


Agenda

- Review of Switch-Mode Power Supply (SMPS)
- Why EMI and SI matter
 - Electro-Magnetic Interference
 - Signal Integrity
- Circuit Theory and Wave Theory
- When is a signal “High Frequency”
- SMPS and High Frequency
- Recommendations
 - Good Practices
 - PCB Stackups
- Questions and discussion

Types of SMPS Circuits


Buck-Mode SMPS

Simplified circuit (power only)

 


Buck-Mode SMPS

Current Flow

 


Boost-Mode SMPS

Simplified circuit (power only)

 

Boost-Mode SMPS

Current Flow

 

EMI and SI


EMI and SI

- Everything we sell must obey FCC rules.
- An SMPS inherently has high frequency.
- Any part of a circuit with high frequency could interfere with other circuit parts.
- The principles for avoiding EMI problems are very similar to maintaining good SI.

Good layout habits will pay off later

Circuit Theory and Wave Theory


Circuit Theory...

 

... is WRONG

Voltage and Magnetic Fields

 Stripline (Inner layer trace and return planes)




Original source:

RHARTLEY
ENTERPRISES
CONTROL OF NOISE, EMI & SI

Low Volume Fields (EM Wave), Completely Contained.

Voltage and Magnetic Fields

 Microstrip (Outer layer trace and return plane)




Original source:

RHARTLEY
ENTERPRISES
CONTROL OF NOISE, EMI & SI

Moderate Volume Fields (EM Wave), Mostly Contained.

Voltage, Current, and Waves

 
- How does the signal go from the source to the load?



Energy is in the Waves (traveling *between* the layers)


Path of Return Current

 - 2-Layer board, components and signals on top, “ground” plane on bottom



Path of Return Current

 - Same layout, except there's a cutout in the ground plane (between source and load)



Path of Return Current

- Same layout, except there's a cutout in the ground plane (under the trace)



E-M Fields around the ground break are a *mess*!

High Frequency

What makes “High Frequency”?

- Frequency ranges where it becomes a problem
- Edge rate v. Repetition rate

What makes “High Frequency”? (part 2)

- The **Rise Time** of a signal has an equivalent frequency:

$$f \approx 0.35 / t_r$$

- Frequency (repetition rate) tells you how often the problem happens
- Rise Time tells you how bad the problem is


Edge Rate is the important factor

Why focus on “Rise Time”?

- The concern is about EM energy radiating out of the circuit
- Large dV/dt can radiate an Electric Field
- Large di/dt can radiate a Magnetic Field
- In the far field, they are one signal that can interact with other circuits


EMI problems are usually found with high di/dt

Is a Square Wave “High Frequency”?

 



A Square Wave contains Sine Waves

Demonstration: Square Wave and Sine Wave

 


Sine wave on Spectrum Analyzer

  1 MHz output (different frequency range on SpecAn)



Square wave on Spectrum Analyzer

 1 MHz output (same extended frequency range on SpecAn as last Sine wave picture)




SMPS and High Frequency

Energy Paths in SMPS Circuits

- DC energy and AC energy are following different (but overlapping) paths
- The paths depend on the type of SMPS
- The Signal and Return Paths have a big impact
 - EMI
 - Efficiency
 - Stability


Buck-Mode SMPS

AC Current Loops (internal)

 


Buck-Mode SMPS

Showing Feedback

 

 
Demonstration: Best Layouts and Not-so-good Layouts



Identical circuit, different layouts


Circuit 1

Ground on Layer 4

 


Circuit 2

Same as 1, except Ground on Layer 2

 


Circuit 3

Flipped L & C; small polygon for Vout; special return path for Vfb

 


Circuit 4

Same as 3, except components spread out

 


Circuit 5

“Recommended” : Tight spacing, Full Polygon on Power Plane for Vout

 


Circuit 6

 “New Recommended” – Removed copper under L & C; Better path for Feedback resistors



Circuit 1 v 2

 
Does Ground on Layer 2 or 4 make a difference?



Closer Ground improves EMI by about 4 dB!

Circuit 2 v 3

 
Does Flipped L & C, Vout polygon, or special feedback return path make a difference?



No significant differences

Circuit 3 v 4

 
Does component spacing make a difference?



Tighter spacing improves EMI by about 2.5 dB

Circuit 4 v 5

 
Does Tight Spacing, and Large Vout Polygon on Power Plane, make a difference?



Tight Spacing and Power Polygon improves EMI by about 3 dB

Circuit 5 v 6

 Does removing copper under L & C, and new feedback path make a difference?



Removed Copper and New Feedback Path *slightly* improves EMI by about 1 dB

Recommendations

Good Practices – SMPS Specific

- Switchers definitely contain high frequencies
- Design for Return Path
 - Ground plane under the circuit is best
 - Layout critical signal paths first – power loops need to be tight
 - The Feedback circuit needs an unbroken return path (for SI)
- Filters (input and output) are important
 - Close to the noise sources
 - Keep frequency response in mind
- High (DC) current traces need to be wider, especially when they are long

Good Practices – from the SMPS measurements

- Ground Plane *directly* under circuit (adjacent layer) is most important
- Tight Component Spacing (reduced current loop area)
- Vout Polygon (on power plane) – probably helps
- Removing copper under L & C (component layer only) – may help
- Feedback path from power plane – may help
- Isolated return path – don't bother
- Small polygons for L & C node – don't bother


Good Practices

- Recognize what parts of your circuit contain high frequencies
- Design for the possibility of higher frequencies than originally planned
- Design for Return Path
 - Layout critical signals first
 - The slower signals can go around, and tolerate compromises
- Don't use high-speed parts unless needed
- Don't depend on “the way we've always done it” to still work in the future


Recommended PCB Stackup – 4 Layers

#	Name	Material	Type	Weight	Thickness	Dk
	Top Overlay		Overlay			
	Top Solder	Solder Resist	Solder Mask		0.4mil	3.5
1	Top		Signal	1oz	1.7mil	
	Dielectric 1	FR-4	Core		14mil	4.8
2	Ground		Signal	1oz	1.4mil	
	Dielectric 3		Prepreg		28mil	4.2
3	Power		Signal	1oz	1.4mil	
	Dielectric 2		Core		14mil	4.2
4	Bottom		Signal	1oz	1.4mil	
	Bottom Solder	Solder Resist	Solder Mask		0.4mil	3.5
	Bottom Overlay		Overlay			


Recommended PCB Stackup – 4 Layers

 


Recommended PCB Stackup – 4 Layers

 


Recommended PCB Stackup – 4 Layers

 


Recommended PCB Stackup – 6 Layers

 


Recommended PCB Stackup – 6 Layers

 

Recommended PCB Stackup – 8 Layers

 


Recommended PCB Stackup – 8 Layers

 

Questions and Discussion

Questions?

We're Done.

 

Questions?

quickmeme.com