

Lecture 2

01/23/23

Electric Charge

- Measured in coulombs
- Q or q is the typical variable for charge

Charge of an electron:


$$-1.6 \times 10^{-19} \text{ C}$$

Electric Current

- Rate of flow of an electric charge
- Measured in Amperes "amps" A
- I or i is used as the variable for current


$$i(t) = \frac{dq(t)}{dt}$$

$$1 \text{ A} = 1 \text{ C/s}$$

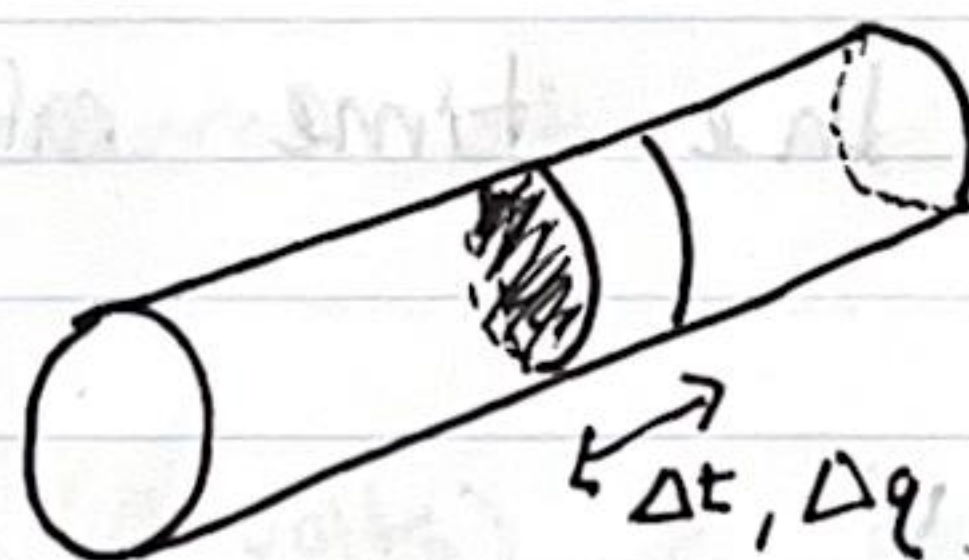


DC Current (Direct Current)
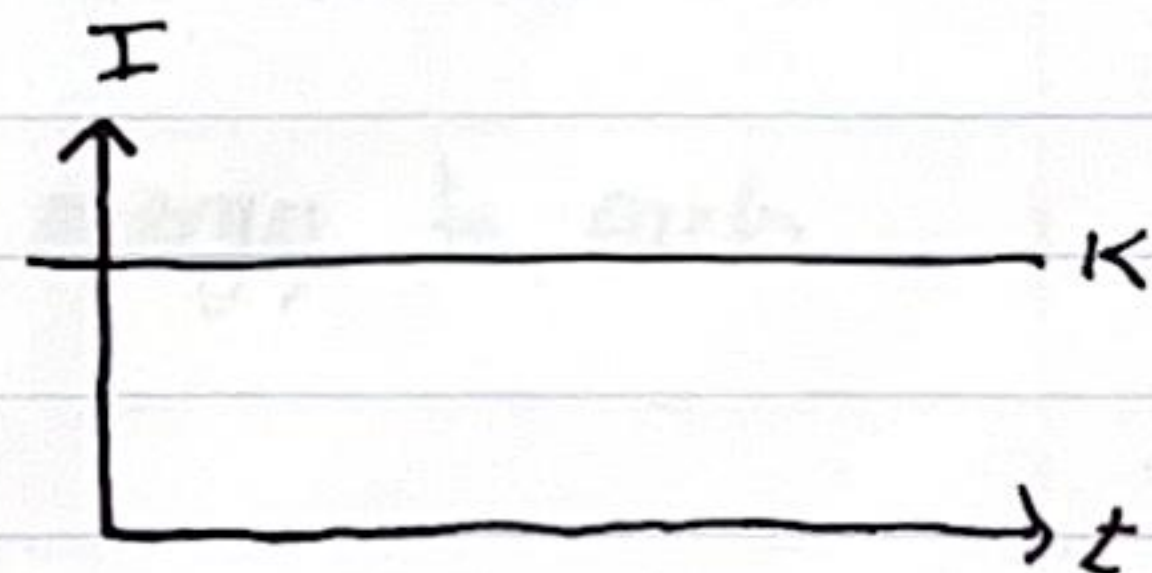
$$I = \frac{\Delta Q}{\Delta t} = K, \text{ a constant}$$



AC Current (Alternating Current)


$$i(t) = A \cos(\omega t)$$

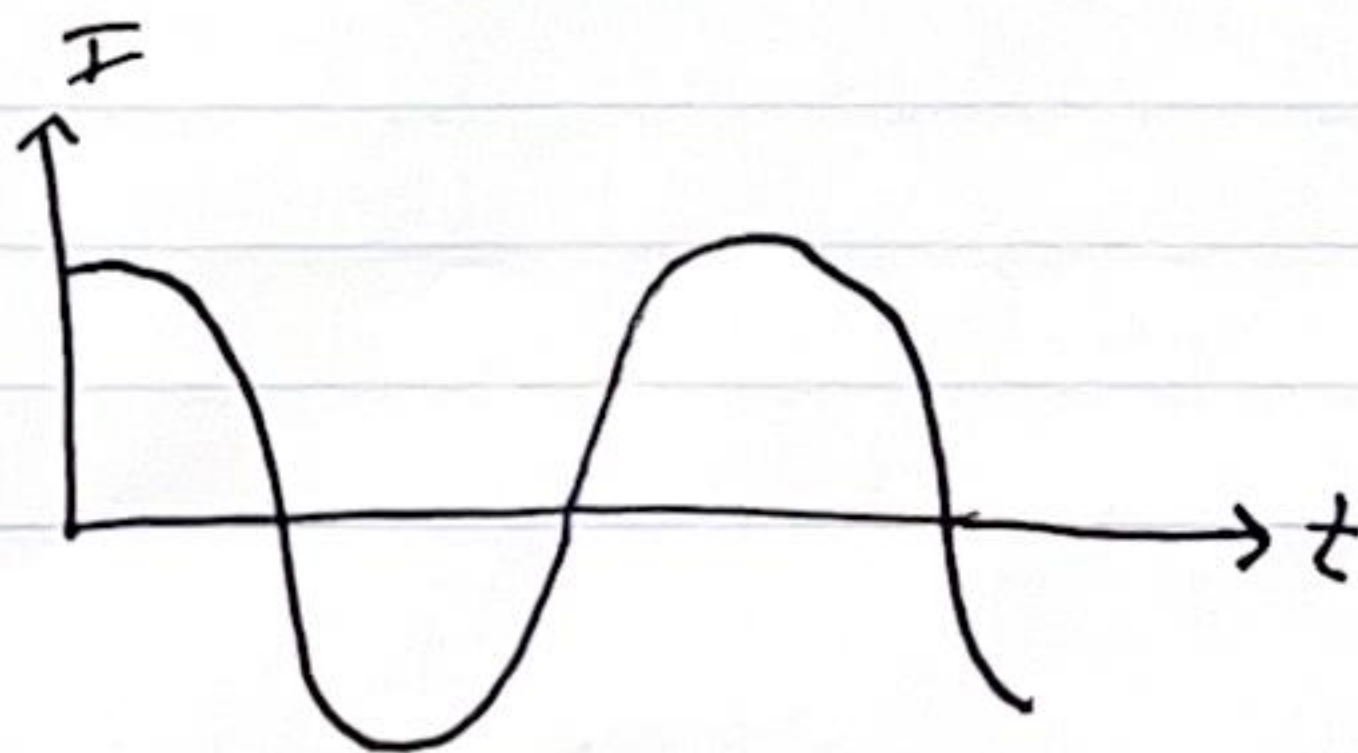

If the electrons are moving left to right in the wire, what direction is the electrical charge - left to right

Voltage

$$\Delta V = \frac{\Delta E}{\Delta Q}$$

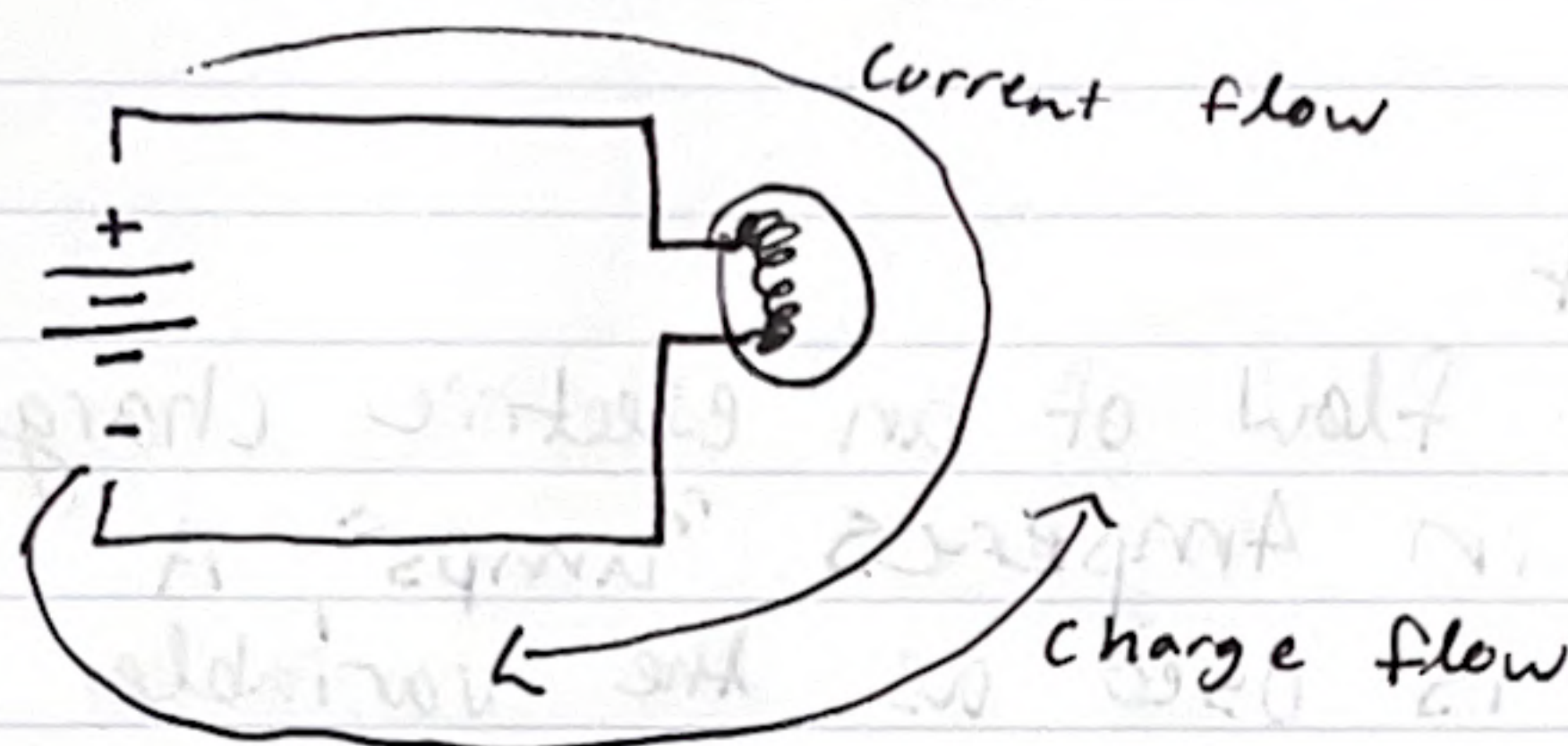

Power is the time rate of energy transfer

$$E = QV$$



Lecture 3

Jan 25, 2023

Parallel: Two branches in parallel are connected such that the current in the adjacent branch must split/combine. If

Measuring and Modeling Circuits

- Ammeter
- Voltmeter
- Current-Voltage (IV) plots
 - Ohm's law
 - Cylindrical Conductors/Resistors
 - IV for linear circuit models
- Voltage cannot be measured at one point - it is differential
- It would take no energy (0 volts) to move charge in an ideal conductor
- A 9V battery delivers 9 Joules of energy to each Coulomb of charge it moves

$$[V] = \frac{J}{C}$$

Lecture 5


Resistance of a conductor

$$R = \rho \frac{L}{A}$$



IV Characteristics

$$I = mV + b$$


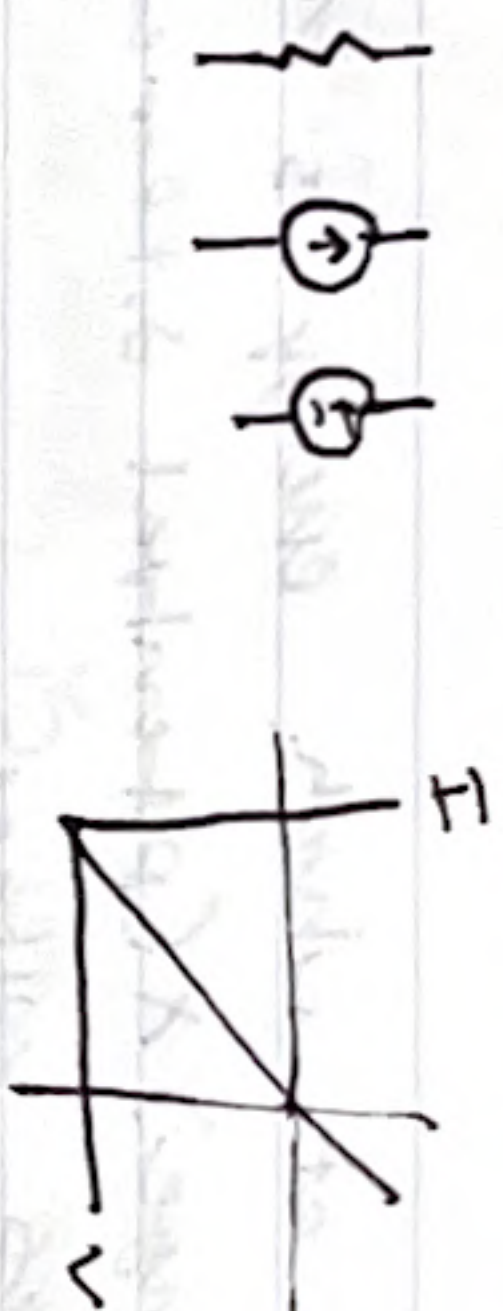


Ohm's law

$$I = \frac{V}{R}$$



Modelling

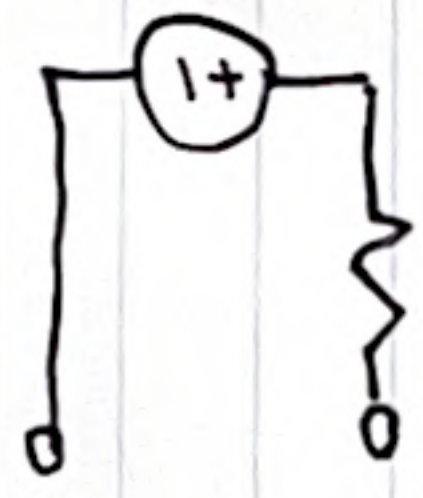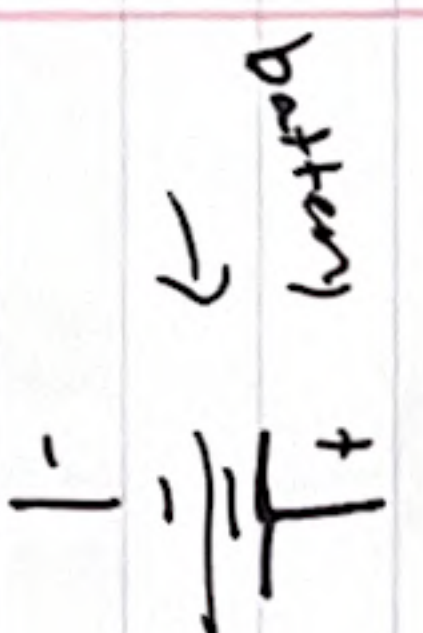

Thevenin Circuit

$$V_{open} = (R + r)I + rI = rI + V_{open}$$

$$V_{open} = (R + r)I$$

Voltage + Energy

- Energy is the ability to do work/heat measured in Joules
- Voltage is the work done per unit charge (J/C) against a static electric field to move charge between two points

$$V = \frac{\Delta E}{\Delta Q}$$

Power is the rate at which energy is transferred


- (rate of change) $\times$ (potential difference)
- current times voltage

$$P = \frac{\Delta E}{\Delta t} = \frac{\Delta Q}{\Delta t} V = I^2 R = \frac{V^2}{R} \quad (\text{Power is non-negative})$$

$$E_{\text{input}} = E_{\text{used}} + E_{\text{wasted}}$$

Electrical Energy Storage:

- Battery
- Capacitor

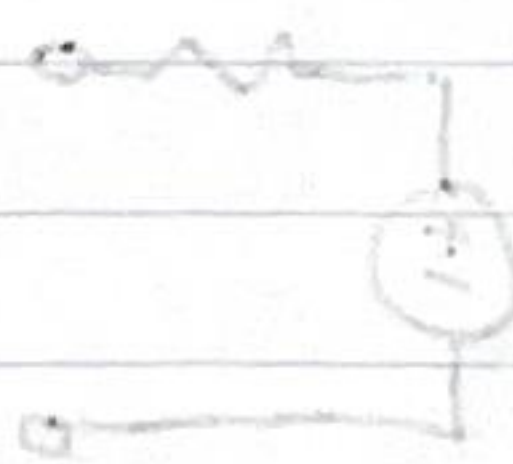

Efficiency

$$E_{\text{input}} = E_{\text{useful}} + E_{\text{waste}} = \eta(E_{\text{input}}) + (1-\eta)E_{\text{input}}$$

$$\eta(\text{etc}) = \text{Efficiency}$$

Lecture 6

$$P = \frac{\Delta E}{\Delta T} = \frac{\Delta Q}{\Delta t} V = IV \quad V = \frac{\Delta E}{\Delta Q}$$

$$P = I^2 R = \frac{V^2}{R}$$

$$C = \frac{Q}{V}$$

↑ capacitance

C , the capacitance, is the charge-to-voltage ratio of a capacitor.

$$E_{\text{capacitor}} = \frac{1}{2} CV^2$$

$$E = \frac{Q^2}{2C} = q$$

$$E_{\text{battery}} = E_{\text{cap}} + E_{\text{waste}}$$

$$\Delta E_{\text{waste}} \geq \frac{1}{2} CV^2$$

$$Q = It$$

Lecture 8

Resistor

$$P = IV = \frac{V^2}{R} = I^2 R \geq 0$$

$$I_{\max}^2 = \frac{P_{\max}}{R}; V_{\max}^2 = P_{\max} R$$

Capacitor

$$C = \frac{Q}{V}$$

$$E_{\text{capacitor}} = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

Battery

$$E_{\text{battery}} = CV^2 = QV$$

(?)

$$C = \frac{P t}{V}$$

$$[Q] = Ah$$

Kirchhoff's Current Law (KCL) - Conservation of Charge
Kirchhoff's Voltage Law (KVL) - Conservation of Energy

Node: point where two or more elements are connected

Branch: A two-terminal circuit element

Loop: A closed path in a circuit where two nodes are not traversed twice


Lecture 9

Voltage divide rule:

$$\frac{R_i}{R_{tot}} \left(\downarrow \right) = V_i$$

Current divider rule:

$$I_K = \frac{R_{eq}}{R_K} I$$

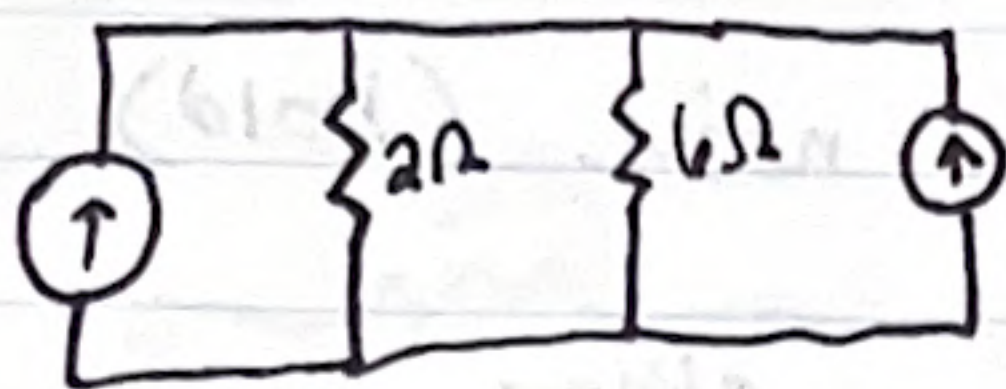


Superposition Theorem

• The total current in any part of a linear circuit equals the algebraic sum of the currents produced by each source separately. To evaluate the separate currents to be ~~added~~ combined, replace all other voltage sources by short circuits and all other current sources by open circuits.

The Node Method

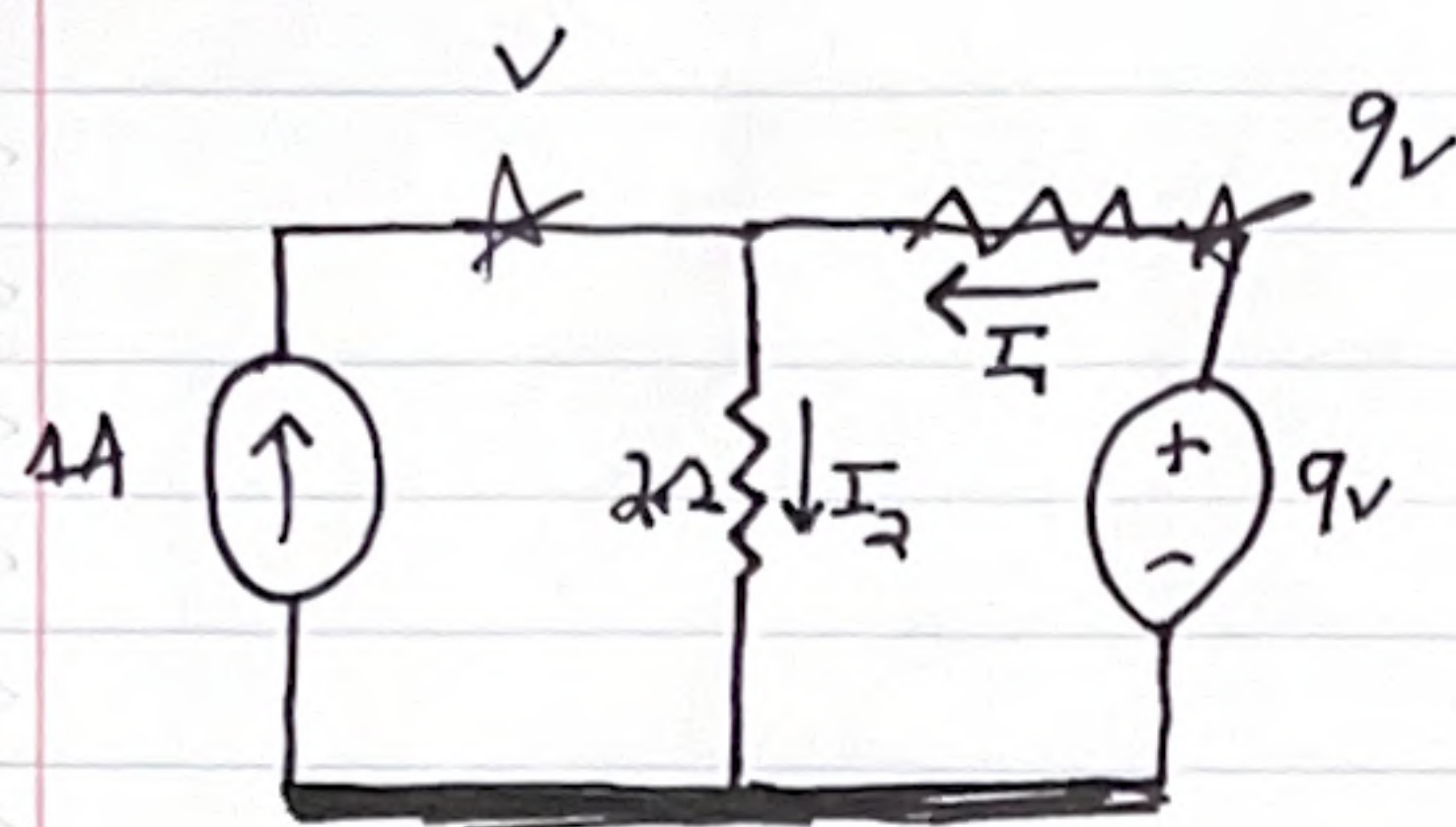1. Identify or pick "ground" (0V ref.)
- 2.
- 3.
- 4.



1. select a node (bold)

2. identify other nodes (~~A~~)

3. assign voltages

$$\text{KCL: } I + I_1 = I_2$$


$$1A + I_1 = I_2$$

$$\text{Ohm's: } 1 + \frac{9-V}{6} = \frac{V-0}{2}$$

$$9-V+6=3V$$


$$V = \frac{15}{4}V$$

Another example

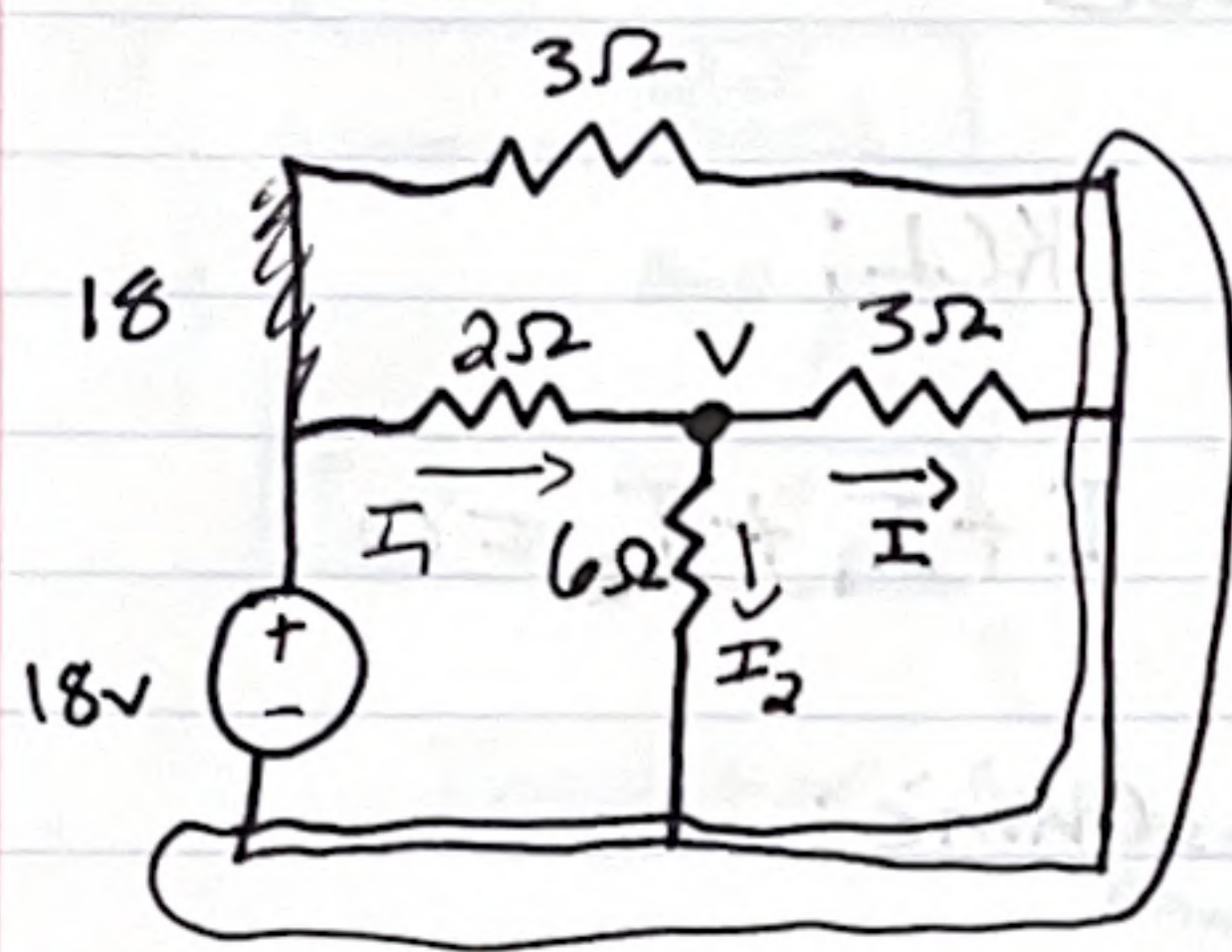

1. Identify ground node
2. Other nodes
3. assign voltages

Similar, but with another voltage source

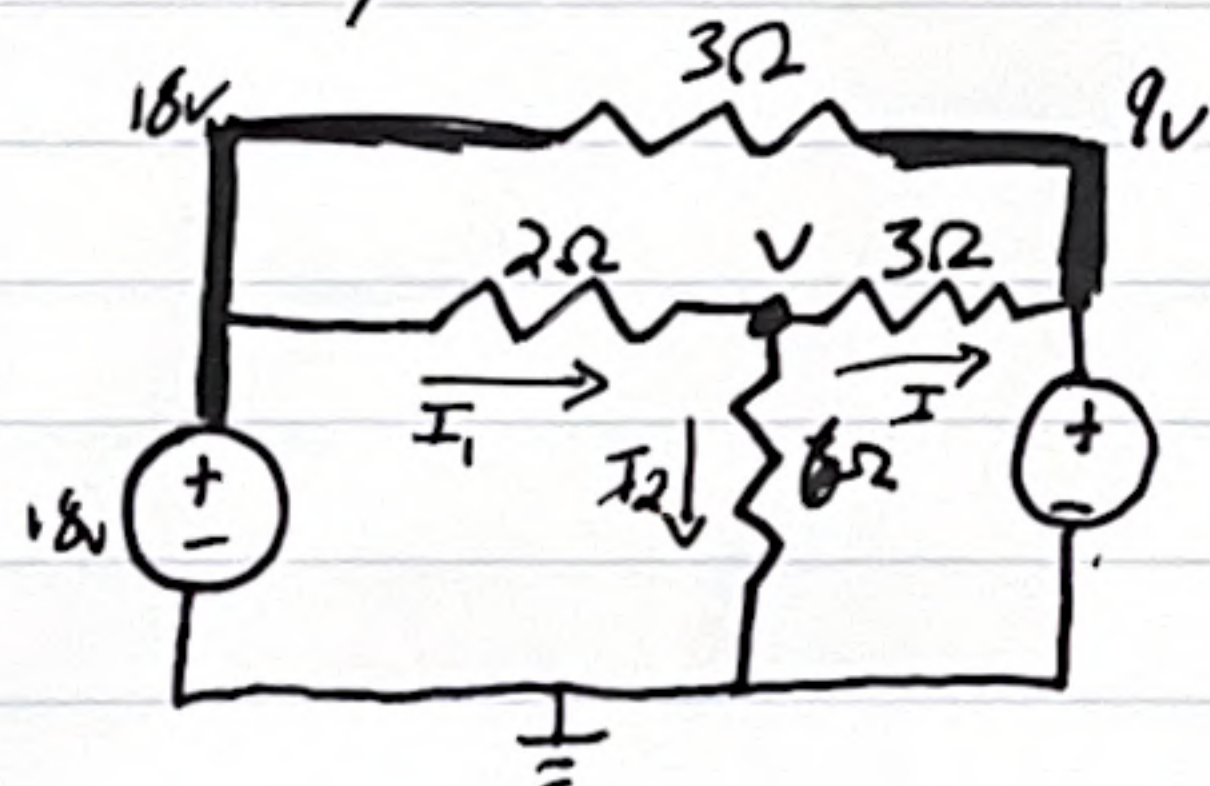

$$\text{KCL: } I_1 = I_2 + I$$


$$\frac{18 - V}{2} = \frac{V - 9}{3} + \frac{V}{6}$$

$$V = 12\text{V}$$

$$I = \frac{V - 9}{3}$$

$$I = 1\text{A}$$

Floating Voltage Source

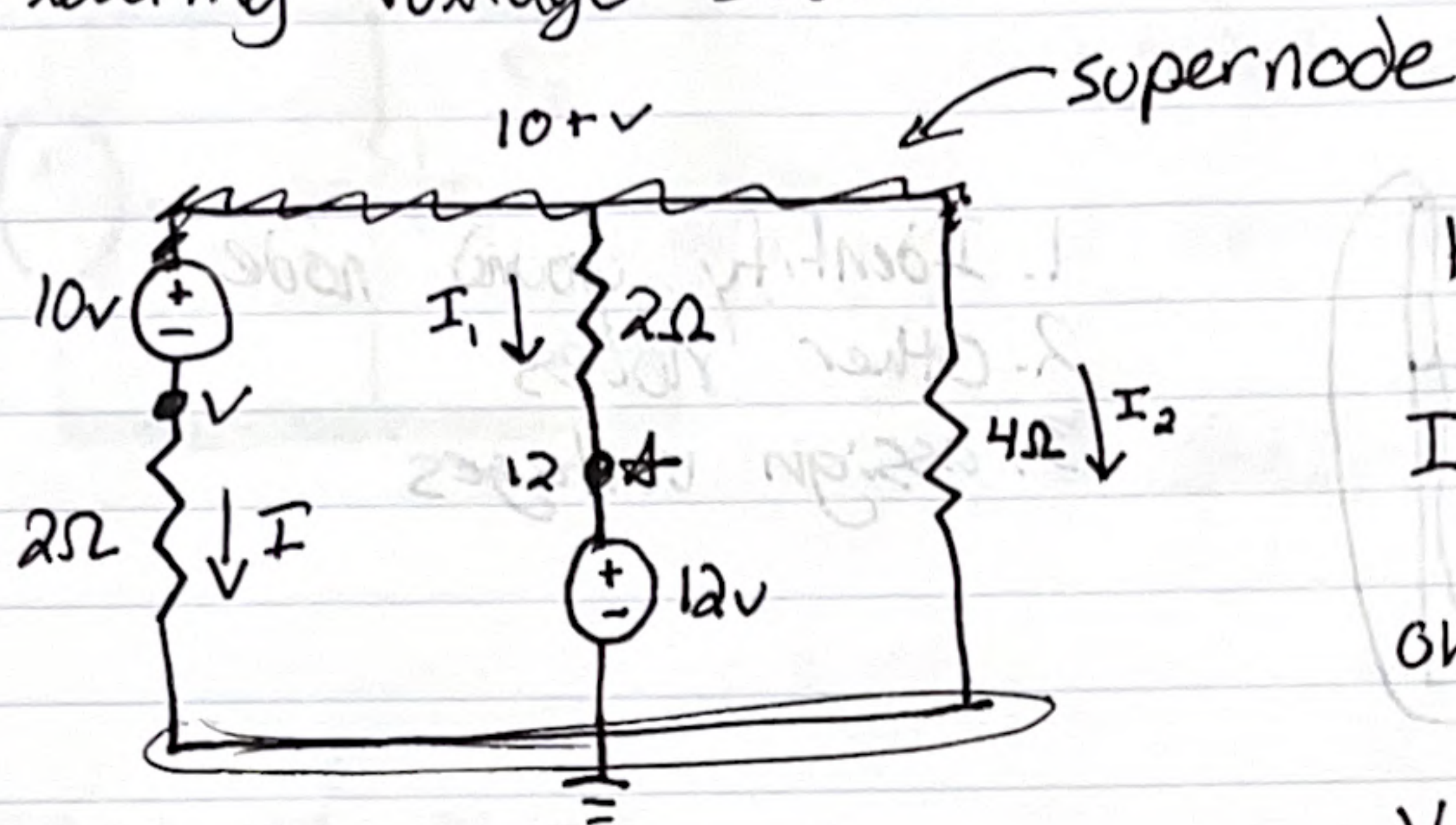

KCL:

$$I + I_1 + I_2 = 0$$

Ohm's:

$$\frac{V}{2} + \frac{10+V-12}{2\Omega}$$


KCL: $I_1 = I_2 + I$

$$\frac{V}{2} + \frac{10+V-12}{2} = \frac{V-12}{2}$$

$$V = 18V$$


$$I = \frac{V-12}{2}$$

$$I = 3A$$



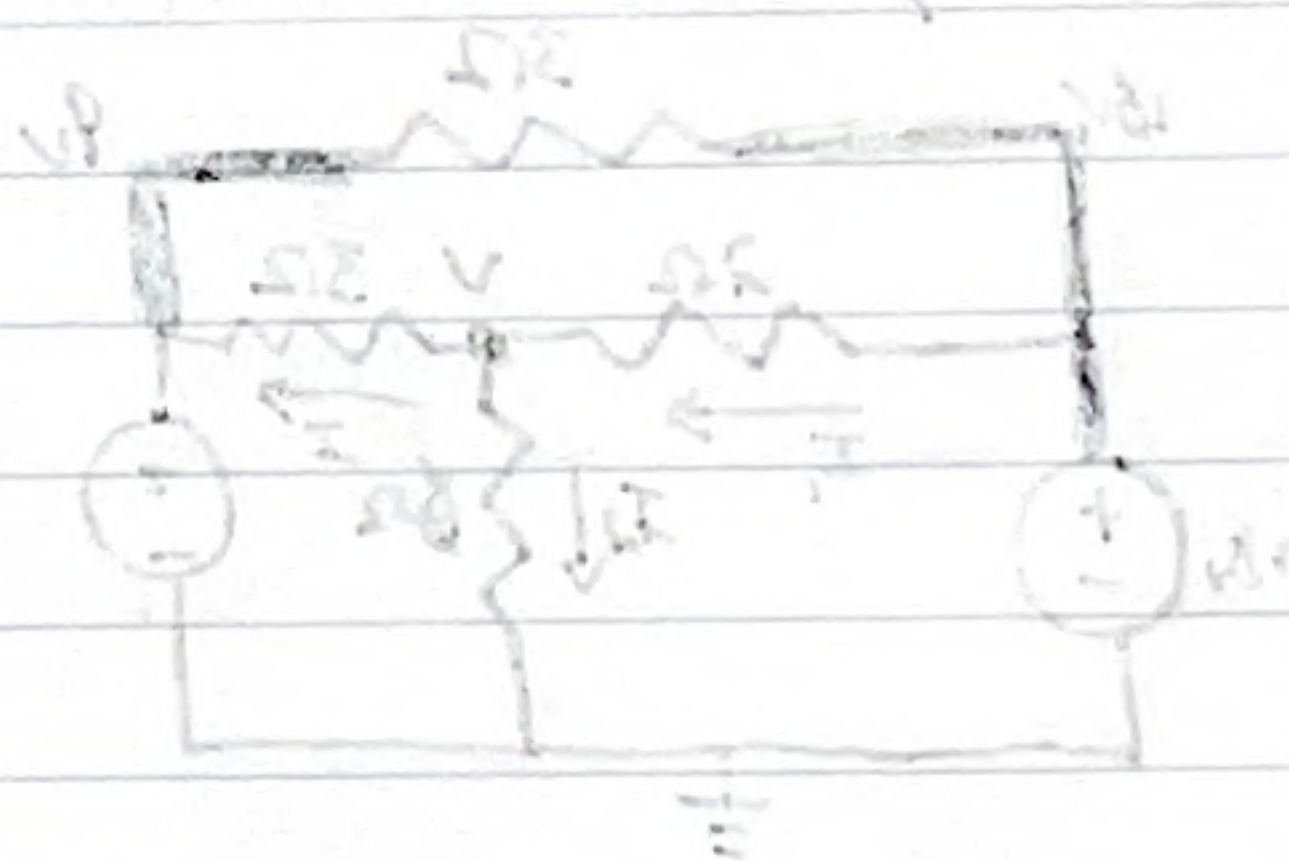


Lecture 16

Intro to Diodes

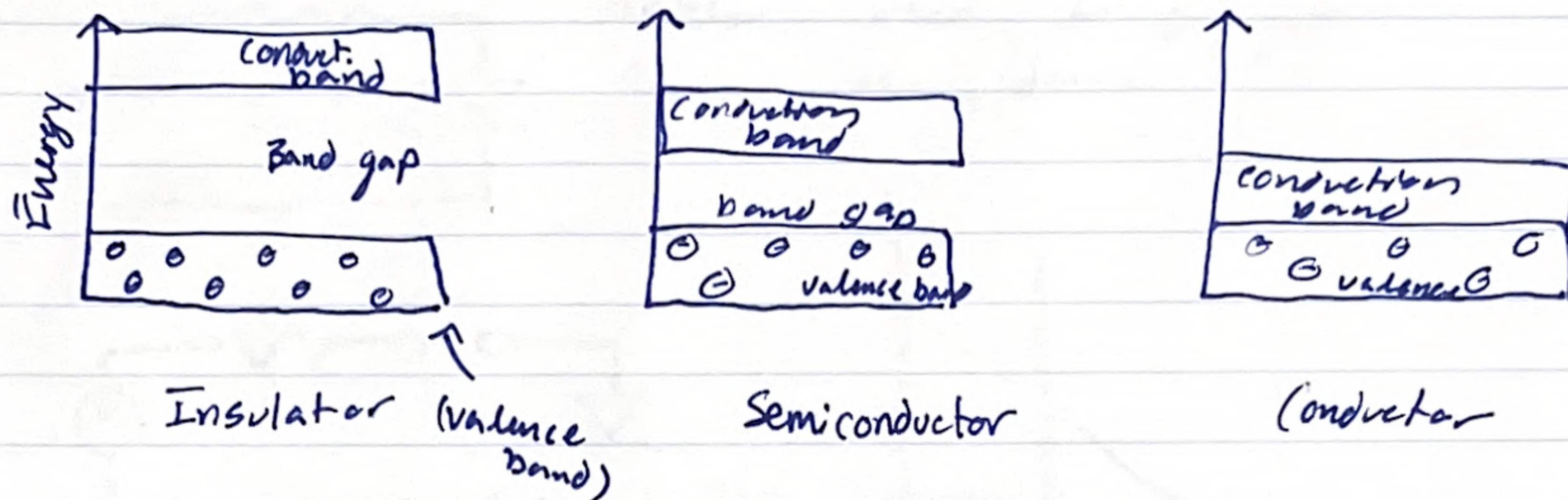



Lecture 17

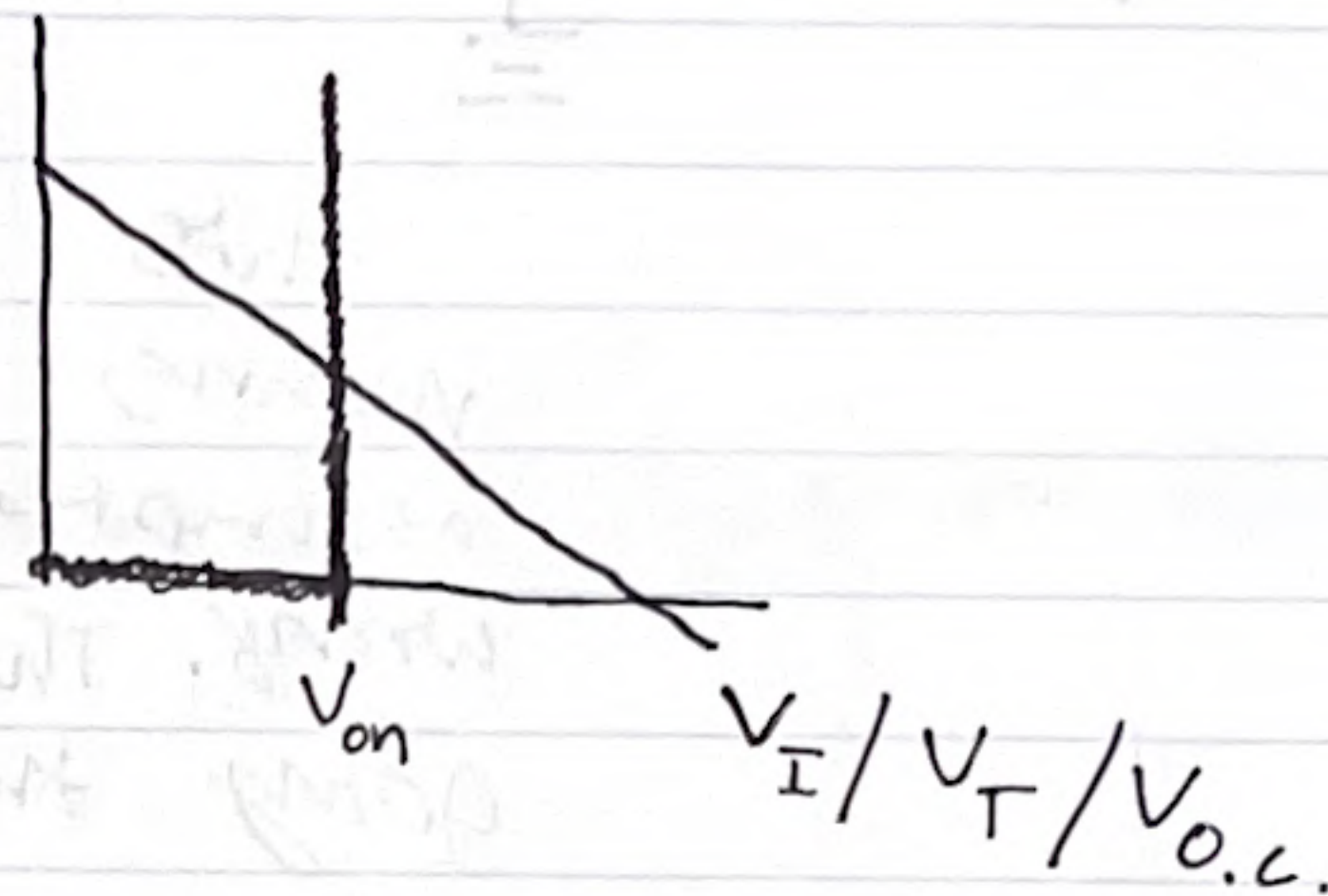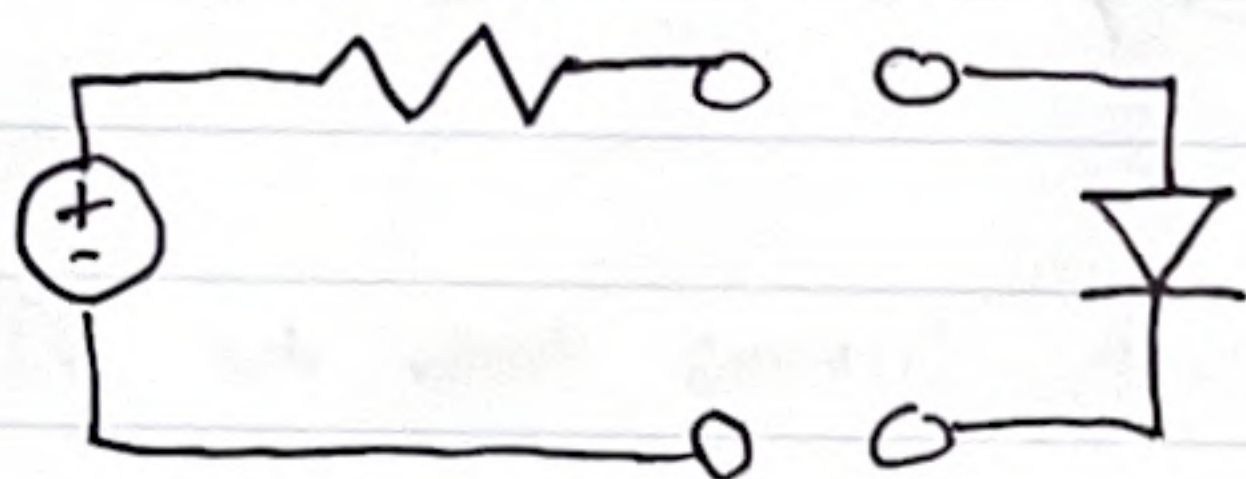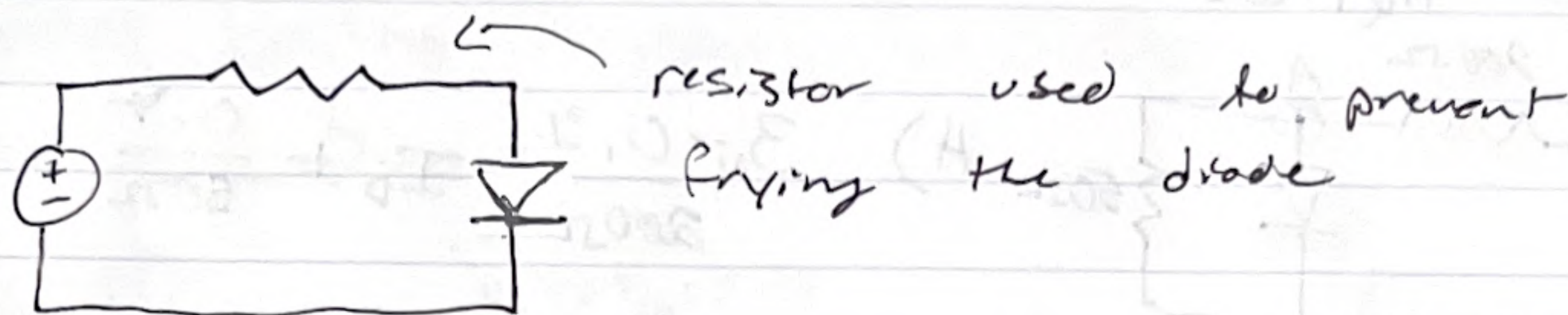

Voltage across some diodes remain const:

Ex:

Germanium
Red
Blue

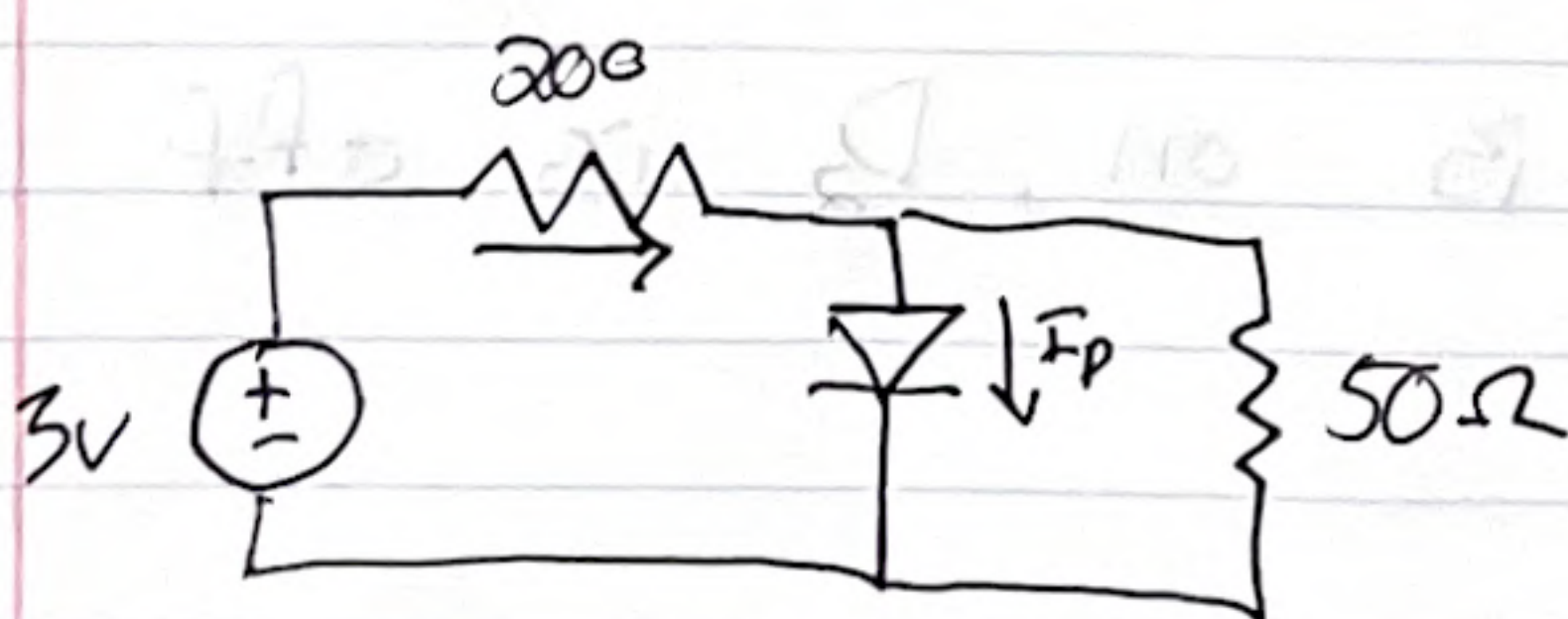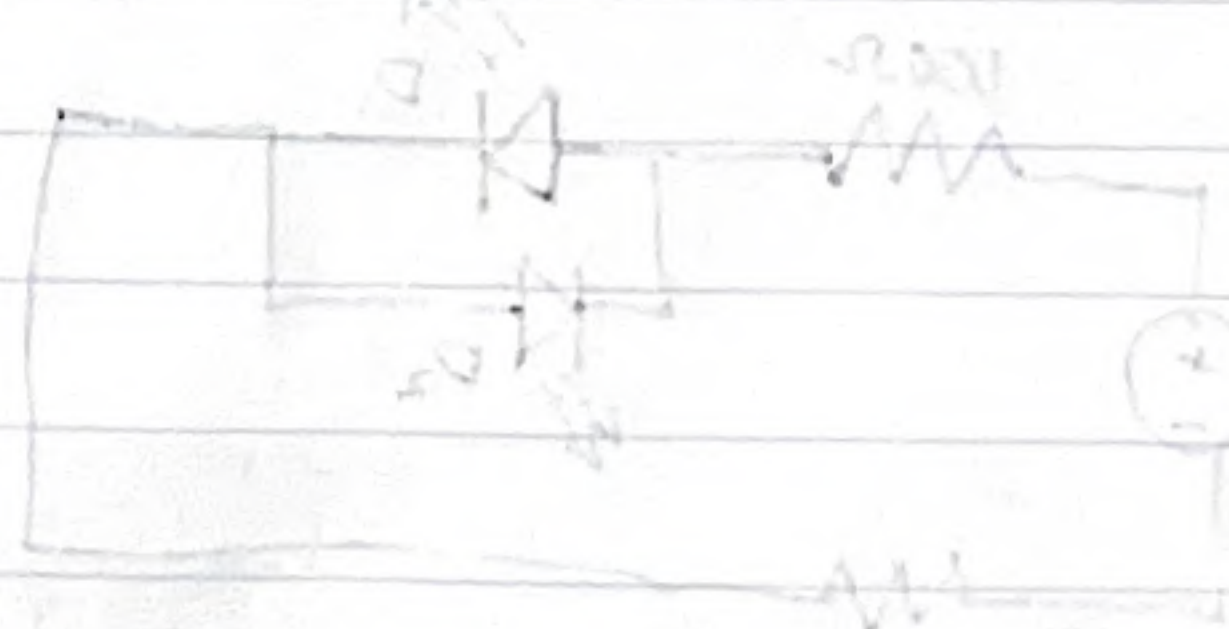

$$V_{on} = 0.7$$

What is the current through diode?

Use node method




A) $\frac{3V - 0.7V}{200\Omega} = I_D + \frac{0.7}{50\Omega}$

$= -2.5mA$

this means our assumption was wrong. There cannot be any current going through the diode!

0mA

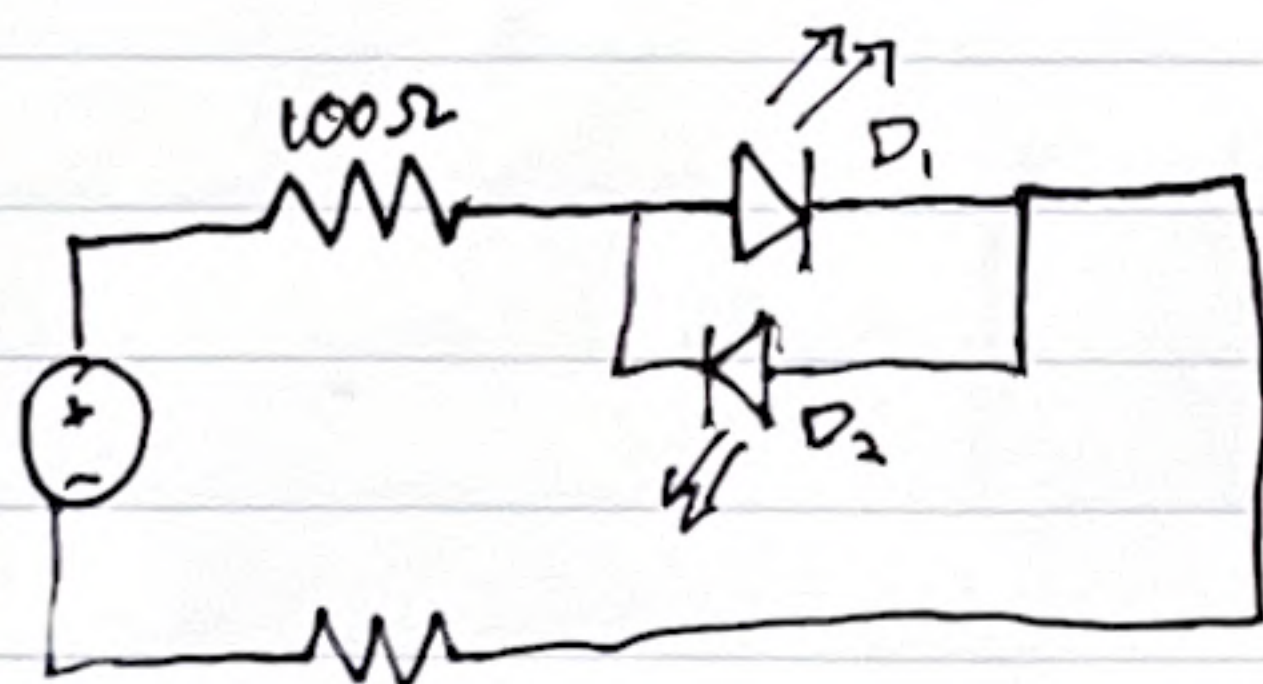


Make assumptions with diode!

Guess and check!

In this case D_1 is on, D_2 is off

Lecture

Current limiting resistors for LEDs

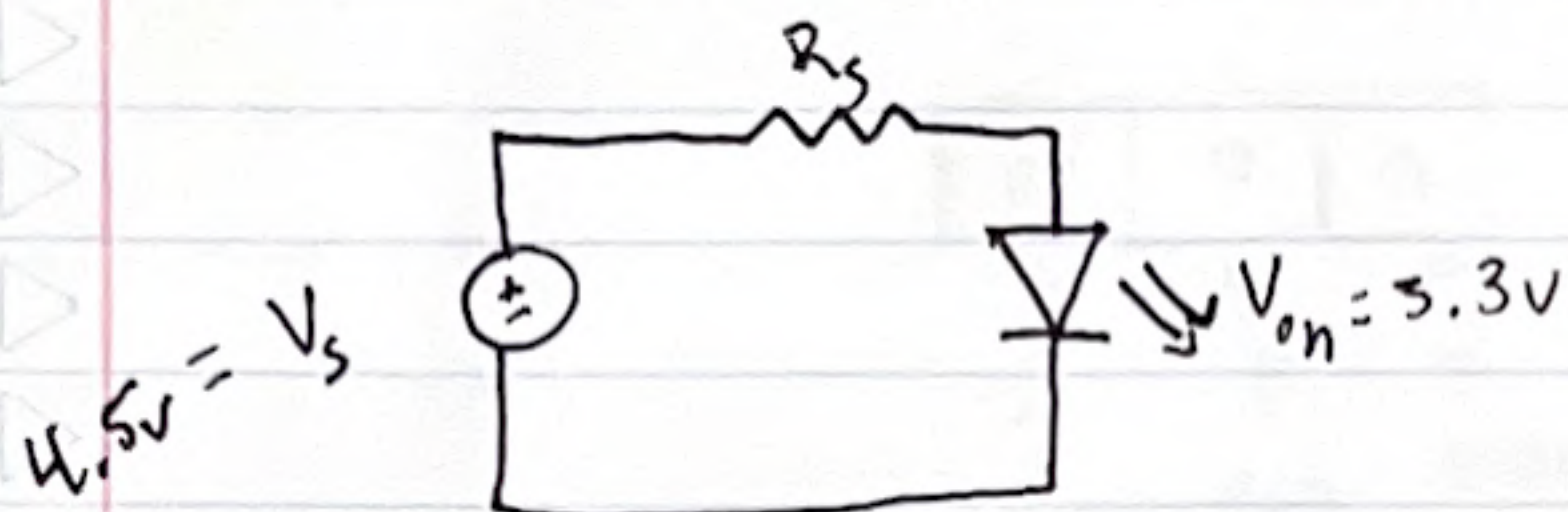

4/5/
.016

4/5/16

If we want current through the diode to be 16mA, what must R be

$$4.5V - I_c R_s - 3.3V = 0$$


$$4.5 - .016(R_s) - 3.3V = 0$$

$$1.2 = .016(R_s)$$

$$\frac{1.2V}{.016A} = 75\Omega$$



Which LED's will be on?
just RED!

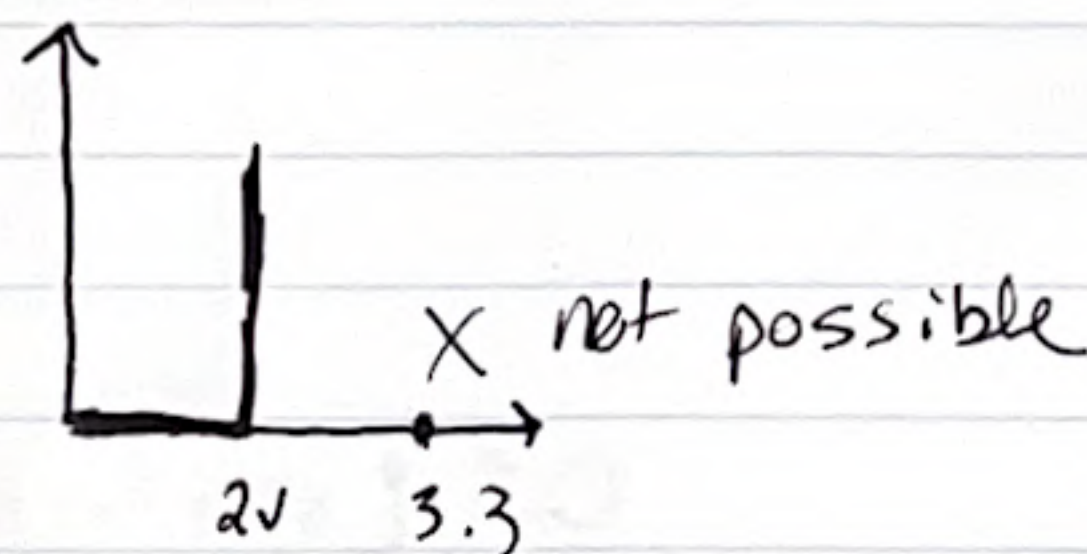


100


2/4

$$.1 = 2(I)$$


$$I = .05$$

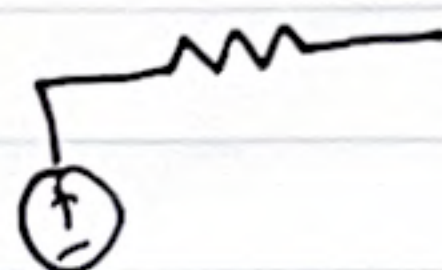


IV Characteristic of a 3-terminal device

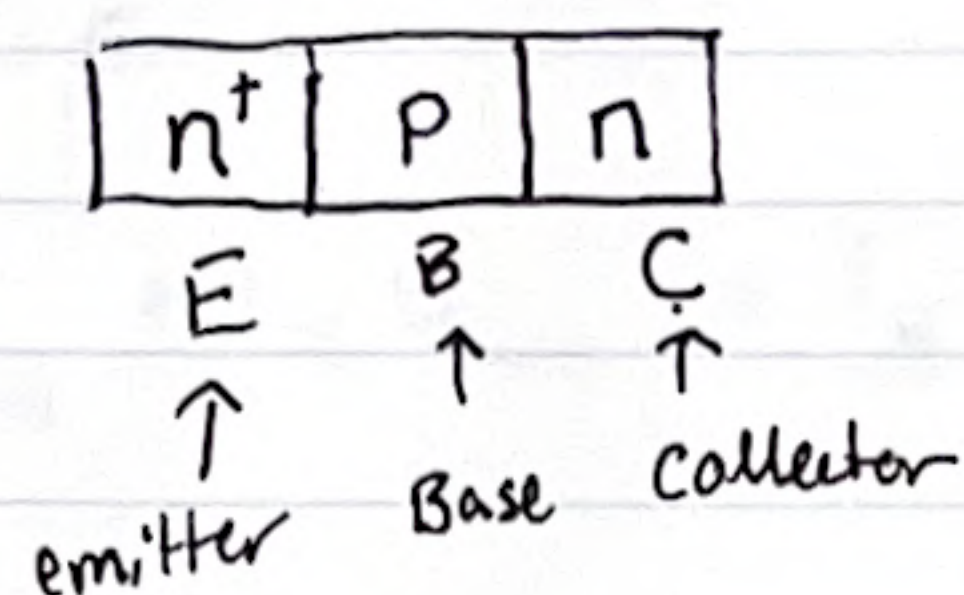

NPN model:

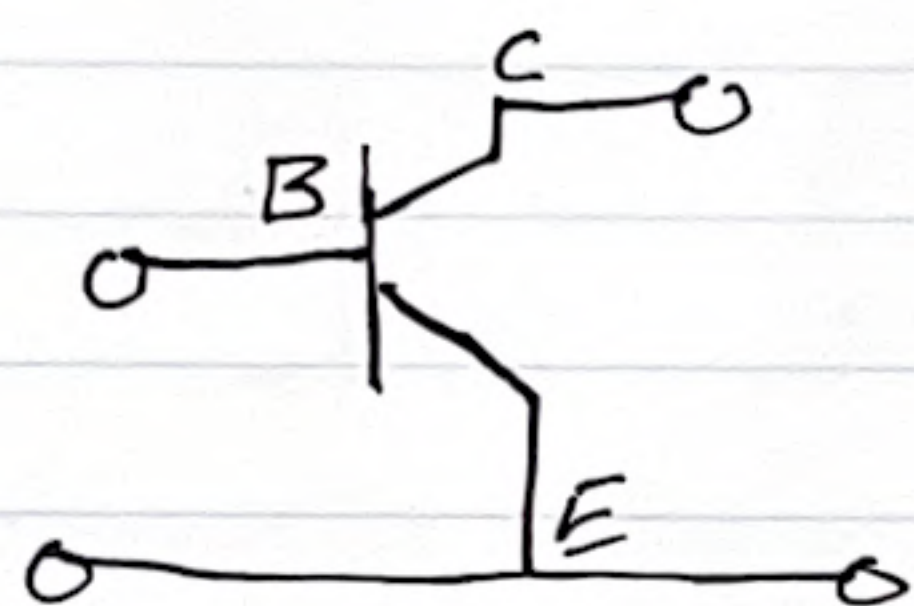

Acts like $\Rightarrow$

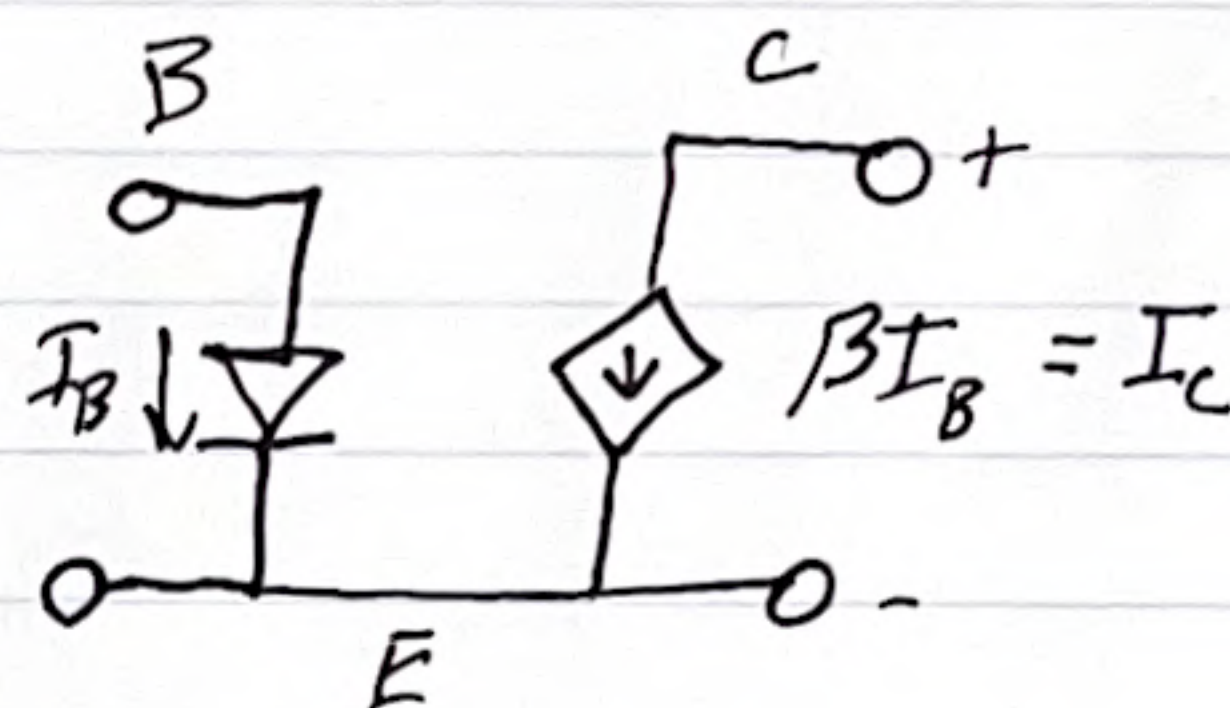

Power is consumed

Constraints:

$$\bullet \quad I_B \geq 0 \text{ and } \beta > 0 \Rightarrow \beta I_B \geq 0$$

$$\bullet \quad V_{out} \geq V_{min} \geq 0 \Rightarrow I_C \leq I_{max}$$

$$I_C = \min \{ \beta I_B, I_{max} \}$$

$$I_C = \min \{ \beta I_B, I_{max} \} \geq 0$$

Lecture 20

$$P_{BJT} = P_{BE} + P_{CE}$$

$$= I_B V_{BE,on} + I_C V_{out} = I_B V_{BE,on} + I_C V_{CE} \geq 0$$


Lecture 21

Recap:


$$0 \leq I_C = \min \begin{cases} \beta I_B = \beta (V_{in} - V_{BE, on}) \\ I_{C, sat} = \frac{V_{CC} - V_{CE, sat}}{R_C} \end{cases}$$

↑
collector current

$$V_{out} = V_{CE} = V_{CC} - I_C R_C$$

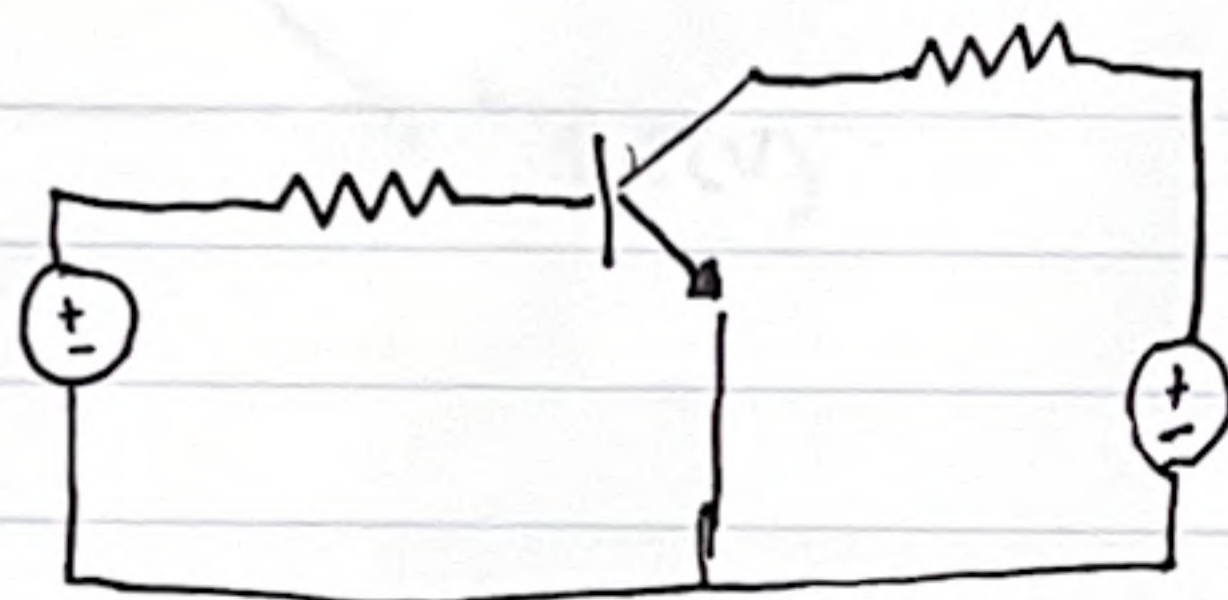

BJT Exercise:

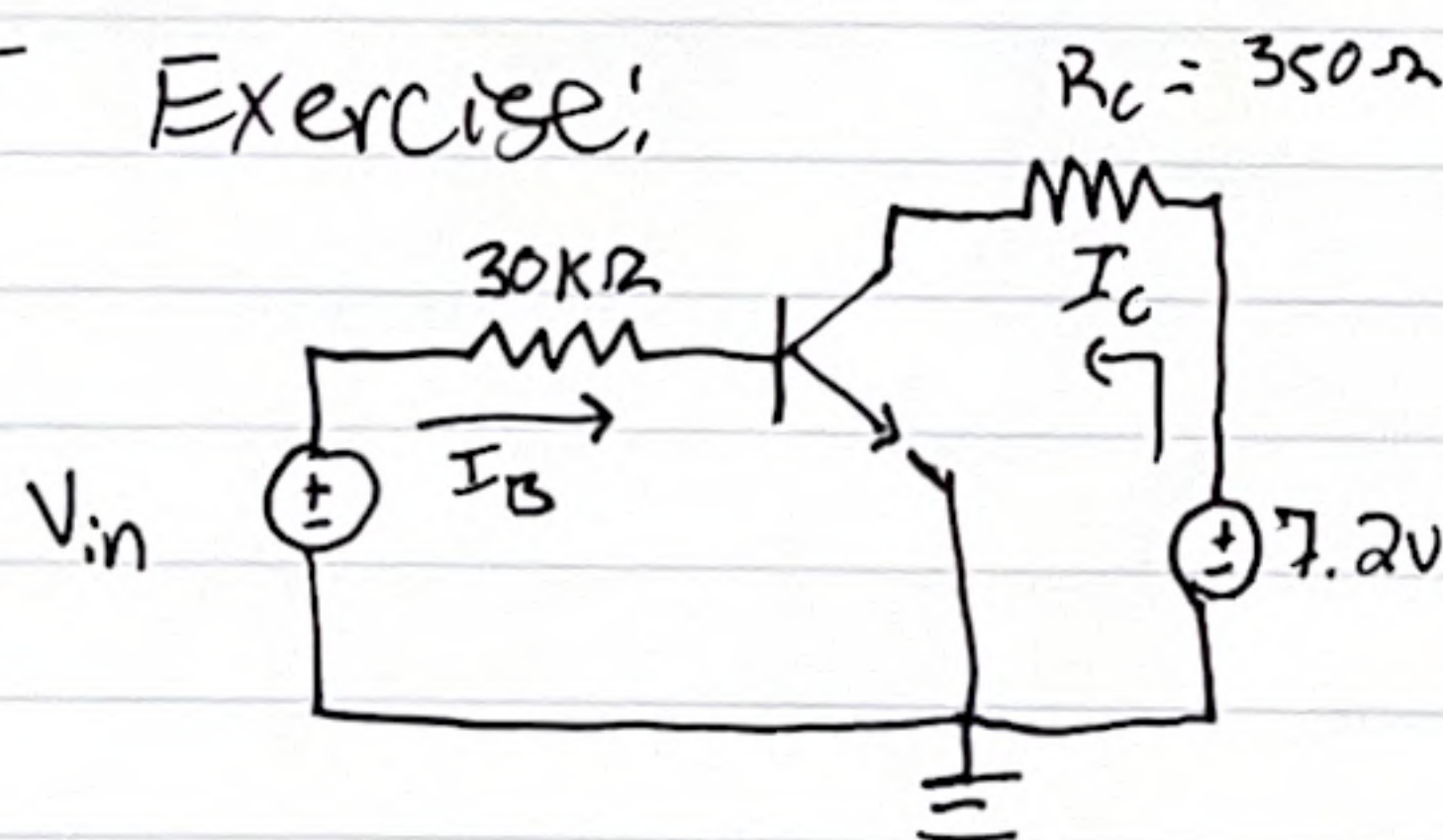

$$\begin{aligned} \beta &= 100 \\ V_{BE, on} &= 0.7V \\ V_{CE, sat} &= 0.2 \end{aligned}$$

What V_{in} would ^{drive} ~~cause~~ the trans. to the edge of saturation
 I_C


$$\beta I_B = I_{C, sat}$$

$$100 \left(\frac{V_{in@sat} - 0.7V}{30000\Omega} \right) = \frac{7.2 - 0.2V}{350}$$

$$V_{in@sat} = 6.7V$$


BJT

$$V_{out} = V_{CE} = V_{CC} - I_C R_C$$

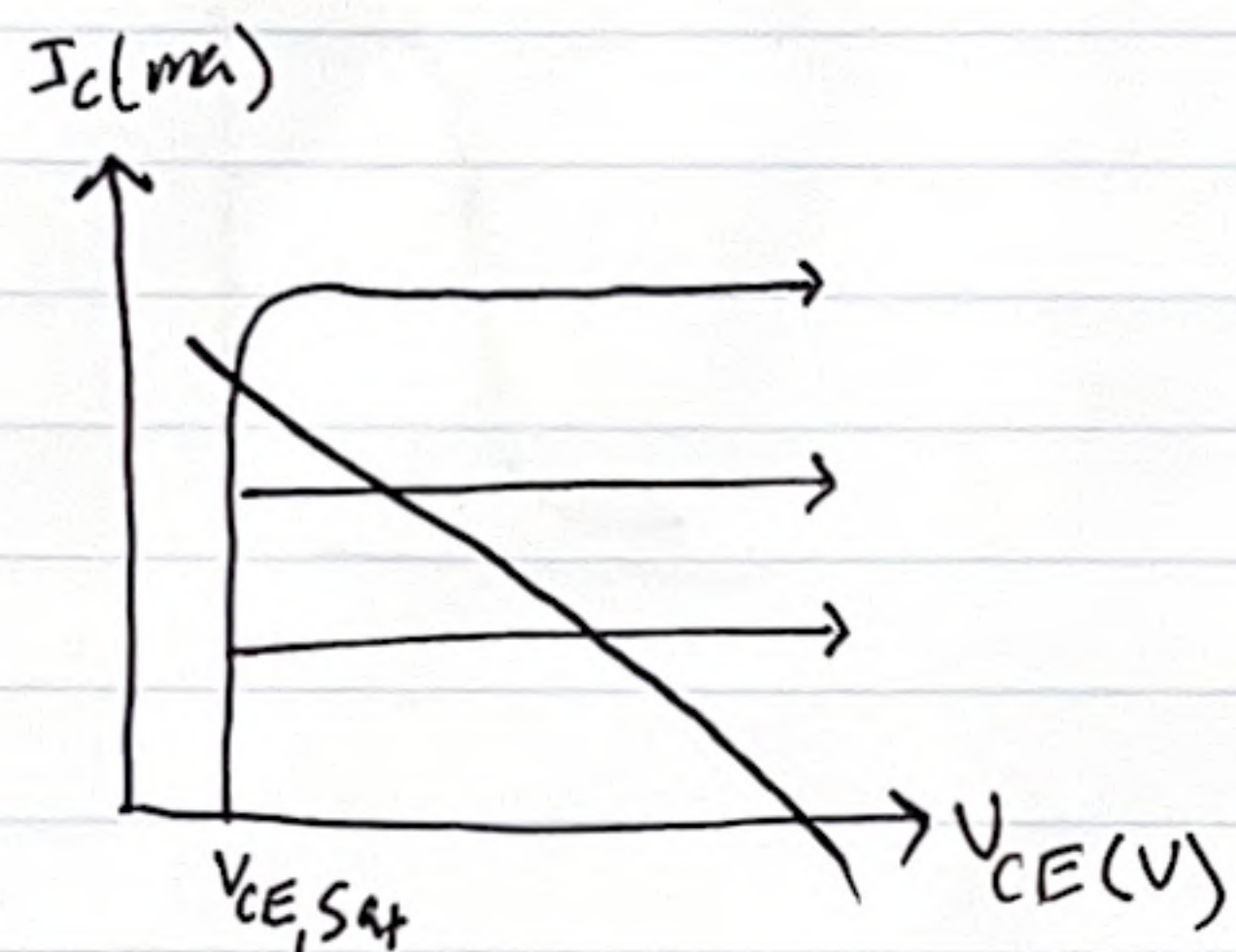


Mosfet

$$V_{out} = V_{DS} = V_{DD} - I_D R_D$$

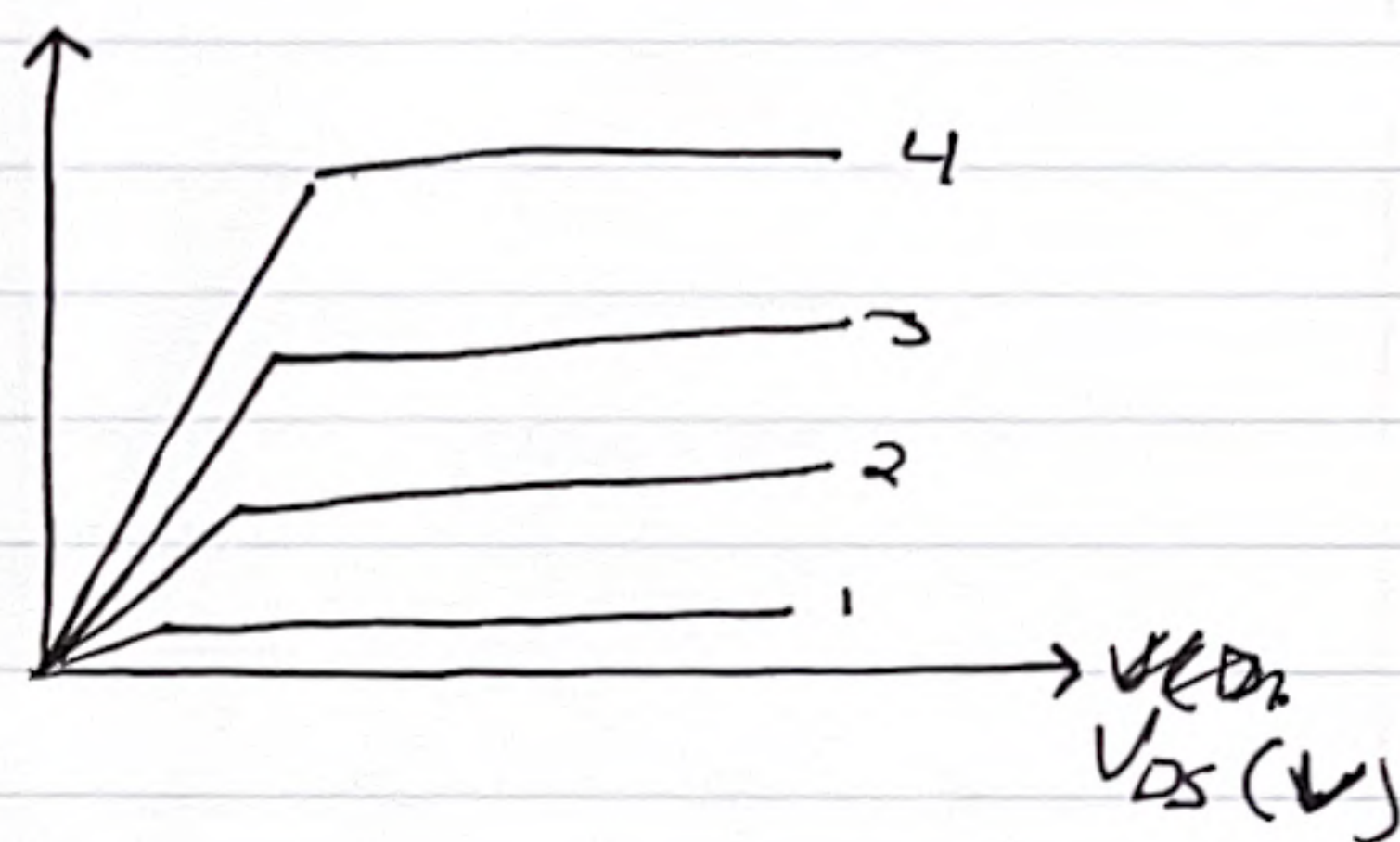


Lecture

nMOS

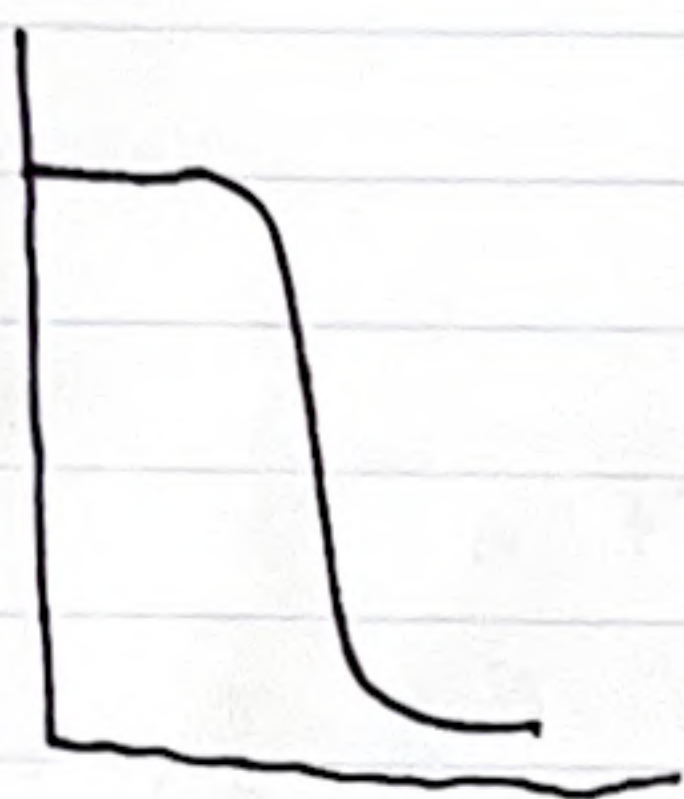


CMOS implementation of inverter

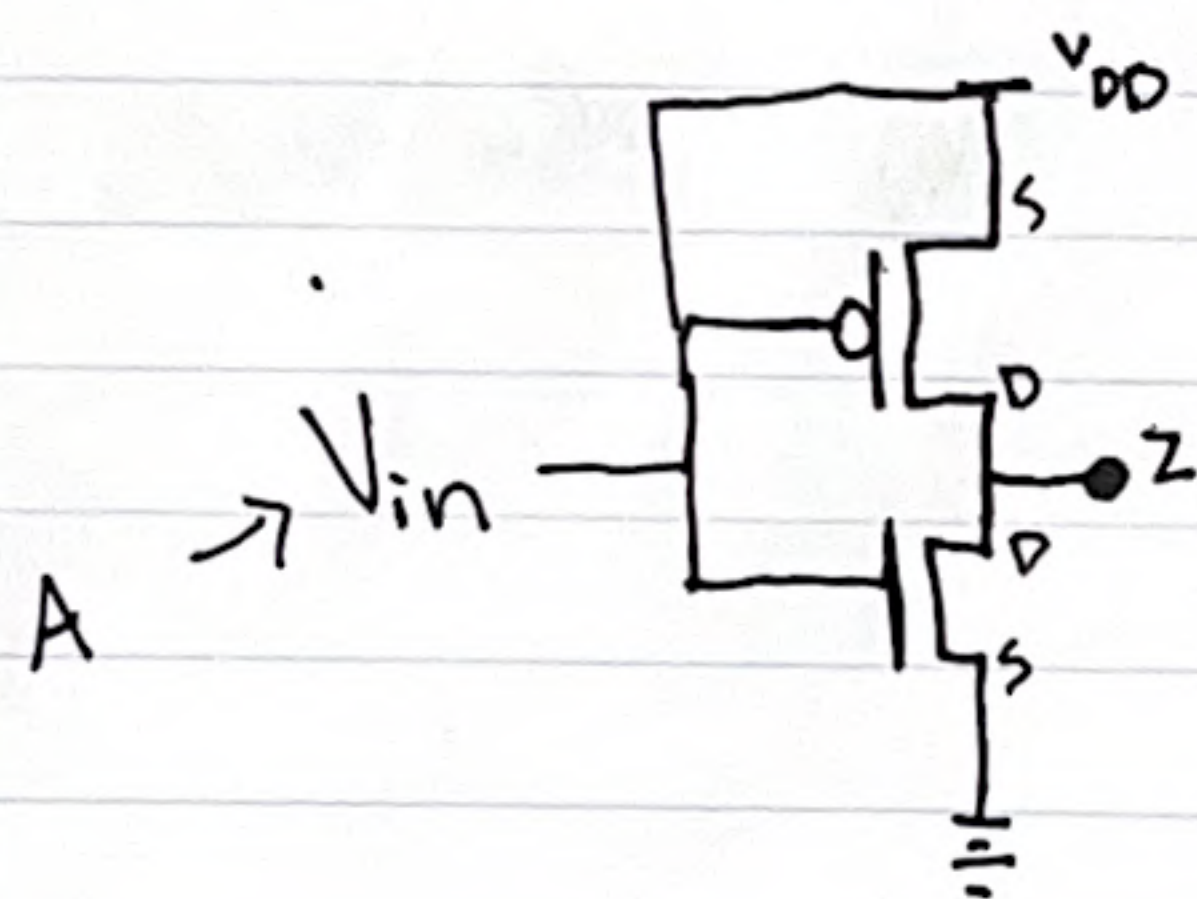

input(A)	output(Z)
0	1
1	0

When V_{in} high: nMOS ON
pMOS OFF

Two Input CMOS Circuit

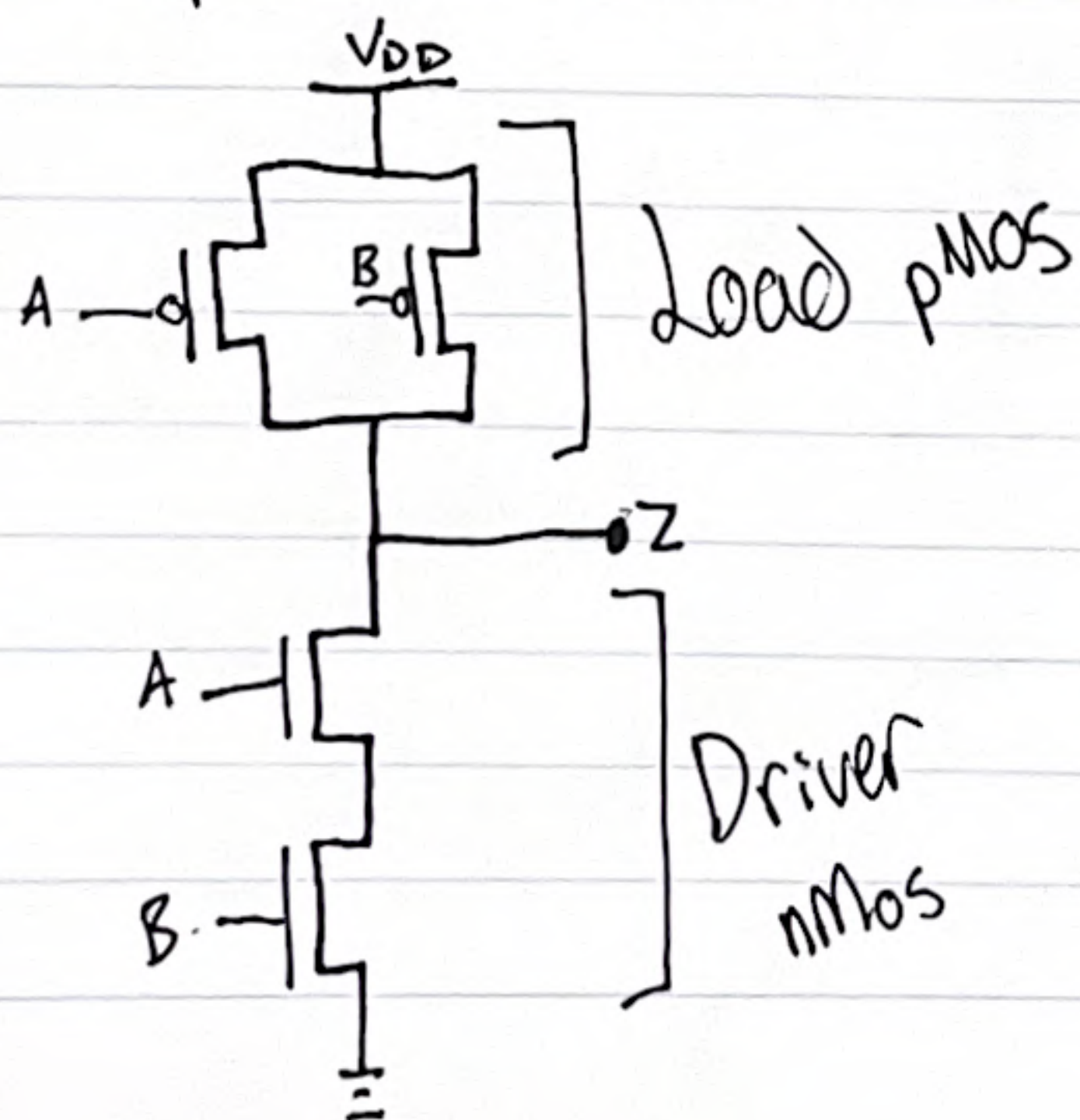

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

Lecture

CMOS Logic Pt II

Power consumed by a switching FET:

$$P = \alpha f C V^2 n$$

Where:

α - activity factor

f - switching frequency

C - load capacitance

V - switching voltages

n - number of transistors switching

Photodiodes and Solar Panels