

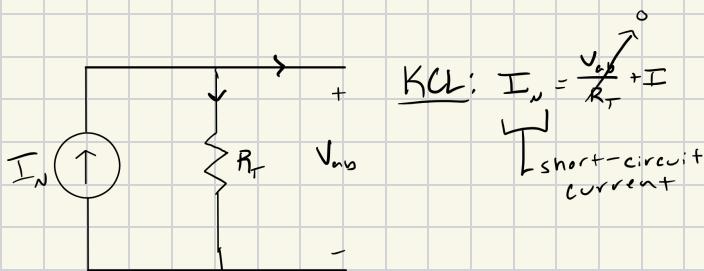


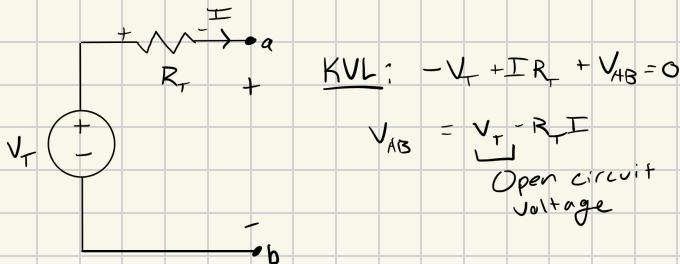

How to make Thevenin and Norton Circuits

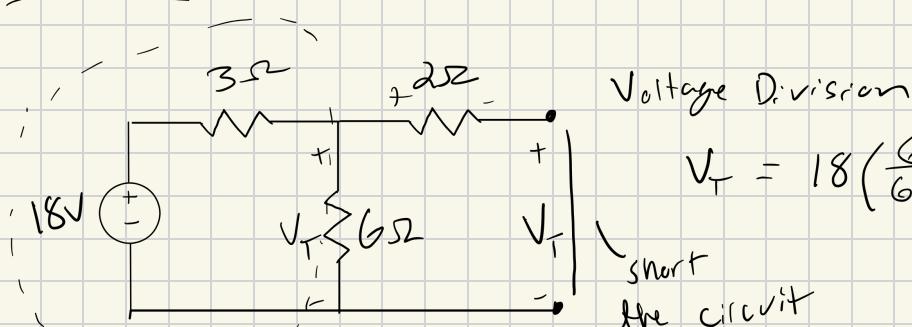


Example:



$$V_T = 18 \left(\frac{6}{6+3} \right) = 12V$$

short
circuit
for I_N

Transform

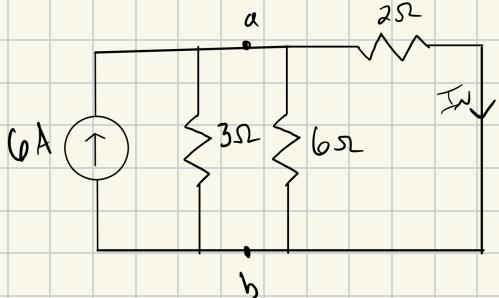


Current Division:

$$I_N = 6A \left(\frac{2\Omega}{2\Omega + 3\Omega} \right) = 6 \left(\frac{1}{2} \right) = 3A$$


$$R_T = \frac{V_T}{I_N} = \frac{12V}{3A} = 4\Omega$$

How to get R_T directly:

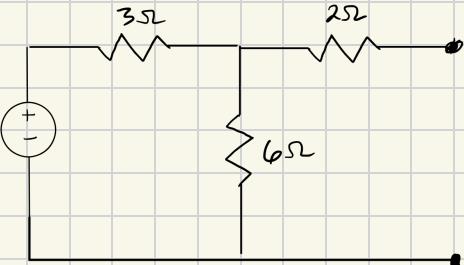


① Source suppression
- remove independent sources

② Find R_{eq} :

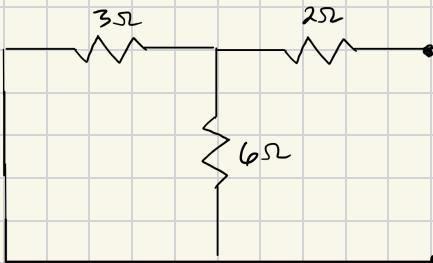

→

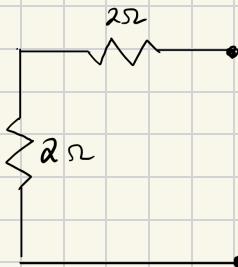


$$R_T = 4\Omega$$

• Test Signal Method

- What if you can't simplify to a single resistor?

① Source suppression

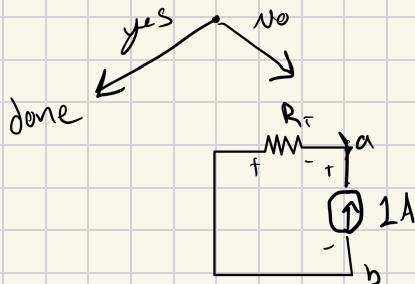② Check if we can reduce to single resistor



$$\text{KVL: } R_T I + V_{ab} = 0$$


$$R_T = \frac{-V_{ab}}{I} = \frac{-V_{ab}}{-1} = V_{ab}$$

Example: Obtain V_T , I_N , R_T for the following circuit.

V_T : No independent sources: $V_T = 0V$

I_N " $I_N = 0A$

Get R_T :

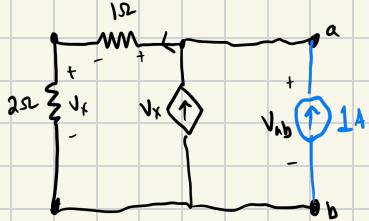

KCL:



$$I + V_x = I_{2\Omega} = \frac{V_x}{2} \Rightarrow V_x = -2V$$

KVL:


$$-V_x - 1\left(\frac{V_x}{2}\right) + V_{AB} = 0$$

$$V_{AB} = \frac{3}{2}V_x = -3V \Rightarrow R_T = -3\Omega$$

• Operational Amplifier (Op-amp)

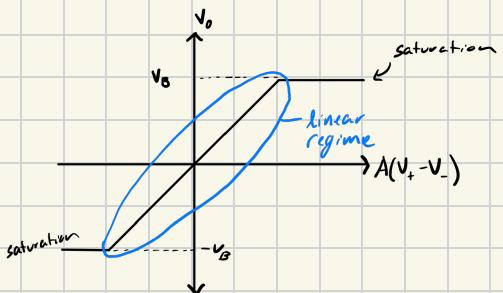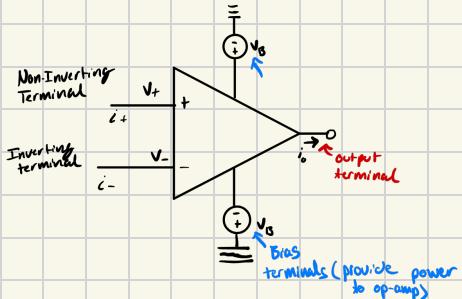

OP-Amp in linear regime:

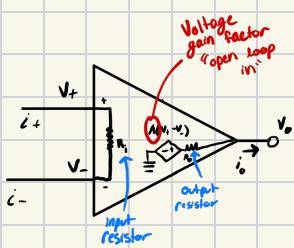

- $|V_+ - V_-| \ll (< 10 \mu V)$
- $R_i \gg (> 10^6 \Omega)$
- $R_o \ll (< 10 \Omega)$
- $A \gg (> 10^6)$

Ideal op-amp approximations


- $i_+ = i_- = 0 \rightarrow$ within pA
- $V_+ = V_- \rightarrow$ within μV

Example 1: Voltage Follower


- Obtain V_o in the following circuit assuming the ideal op-amp approx:

$$\bullet V_+ = V_-$$

$$\bullet i_+ = i_- = 0$$

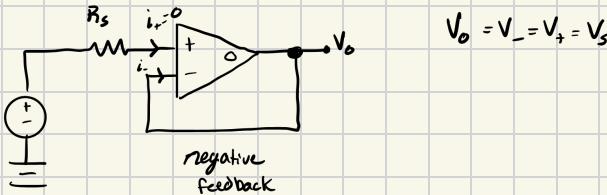

Consider attaching a load

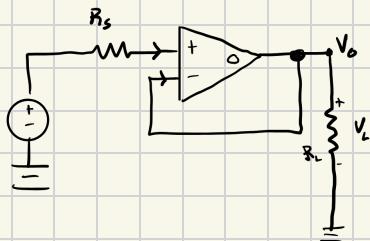


$$\bullet P_L = \frac{V_L^2}{R_L} = \frac{1}{R_L} \left(V_s \frac{R_L}{R_L + R_s} \right)^2 = \frac{V_s^2}{R_L} \left(\frac{R_L^2}{(R_L + R_s)^2} \right)$$

- Op-Amp acts as a buffer between the source and the load

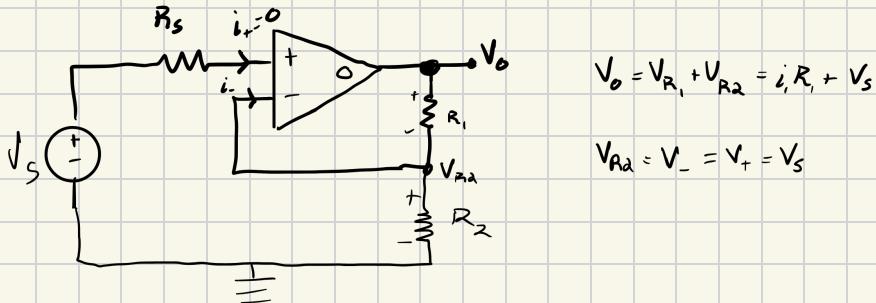Example 2: non-inverting amplifier

- Obtain V_o in the following circuit assuming the ideal op-amp approx




- Never do KCL @ ground in op-amps

- $i_o = 0$ (in general)


Example 3: Inverting Amplifier

- Obtain V_o in the following circuit

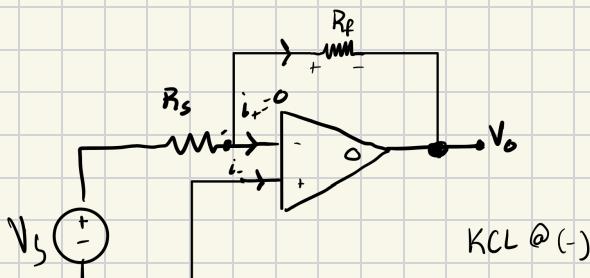

$$\frac{V_s}{R_s} = \frac{-V_o}{R_f} \Rightarrow -V_s \left(\frac{R_f}{R_s} \right) = V_o$$

Example 4: Hodoer

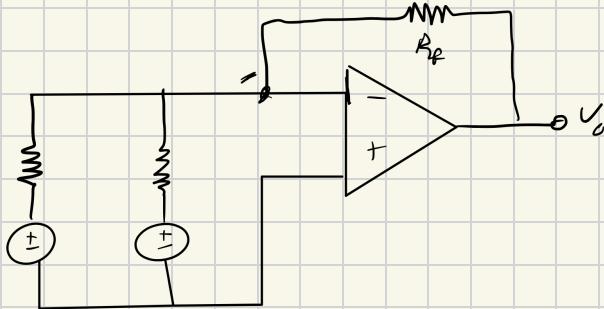

$$\frac{V_1}{R_1} + \frac{V_a}{R_2} = \frac{-V_o}{R_f}$$

Linearity, time-invariance and LTI systems

$$V_o(t) = -\frac{R}{L} \int_{-\infty}^t V_s(x) dx = \xrightarrow{\text{f}(t)} \boxed{\text{System}} \xrightarrow{y(t)}$$

$$= -\frac{R}{L} \underbrace{\int_{-\infty}^0 V_s(x) dx}_{V_o} - \frac{R}{L} \int_0^t V_s(x) dx$$

$$= V_o - \frac{R}{L} \int_0^t V_s(x) dx$$

zero input response
 (when $V_s(t)=0$) → $V_{zs}(t)$
 (no initial state)

zero-state response
 when $V_o=0$
 (no initial state)

Zero State:

- no initial state
- a weighted sum of inputs produces a similarly weighted sum of corresponding zero-state outputs, consistent with superposition principle

if

$$f_1(t) \rightarrow \boxed{\substack{\text{zero state} \\ \text{linear}}} \rightarrow y_{zs,1}(t)$$

and

$$f_2(t) \rightarrow \boxed{\substack{\text{zero state} \\ \text{linear}}} \rightarrow y_{zs,2}(t)$$

then

$$f_3(t) = K_1 f_1(t) + K_2 f_2(t) \rightarrow \boxed{\substack{\text{zero state} \\ \text{linear}}} \rightarrow y_{zs,3}$$

Example:

Consider a system with input $f(t)$, initial state $y(0) = y_0$ and input-output rule given by

$$y(t) = y_0 e^{-t} - \int_0^t f(x) dx$$

Determine if the system is linear or not

Q: Zero-state linear or not? $\Rightarrow y_0 = 0 \Rightarrow y_{2s}(t) = - \int_0^t f(x) dx$

$$f_1(t) \rightarrow \boxed{\quad} \rightarrow y_1(t) = - \int_0^t f_1(x) dx$$

$$f_2(t) \rightarrow \boxed{\quad} \rightarrow y_2(t) = - \int_0^t f_2(x) dx$$

$$\begin{aligned} K_1 f_1(t) + K_2 f_2(t) \rightarrow & \boxed{\quad} \rightarrow K_1 y_1(t) + K_2 y_2(t) \\ & = - \int_0^t (K_1 f_1(x) + K_2 f_2(x)) dx = \\ & K_1 \underbrace{\left(- \int_0^t f_1(x) dx \right)}_{y_1} + K_2 \underbrace{\left(- \int_0^t f_2(x) dx \right)}_{y_2} \end{aligned}$$

↑
IS
linear

Q: zero input linear? $\Rightarrow f(t) = 0 \Rightarrow y_{2I}(t) = y_0 e^{-t}$

$$\boxed{y_0} \rightarrow y_{2I,0}(t) = y_0 e^{-t}$$

$$\boxed{y_1} \rightarrow y_{2I,1}(t) = y_1 e^{-t}$$

$$\boxed{y_3 = K_1 y_0 + K_2 y_1} \rightarrow y_{2I,3}(t) = K_1 y_{2I,0}(t) + K_2 y_{2I,1}(t)$$

Example: $y(0) = y_0$

$$y(t) = y_0^2 + f^2(t)$$

① Zero-state linear! $\Rightarrow y_0 = 0 \Rightarrow y_{zs}(t) = f^2(t)$

LTI - Linear + Time Invariant

Time Invariance: delayed inputs cause equally delayed outputs for zero initial state and any delay t_0 . So

If

$$f_1(t) \rightarrow \boxed{\text{time-invariant}} \rightarrow y_1(t)$$

$$f_2(t) = f(t-t_0) \rightarrow \boxed{\text{time-invariant}} \rightarrow y_2(t) = y_1(t-t_0)$$

Example:

$$y(0) = y_0 \quad y(t) = y_0^2 + 2f(t)$$

$$\text{zero-state} \Rightarrow y_0 = 0 \Rightarrow y_{zs}(t) = 2f(t)$$

$$f_1(t) \rightarrow \boxed{\quad} \rightarrow y_1(t) = 2f_1(t)$$

$$f_2(t) \rightarrow \boxed{\quad} \rightarrow y_2(t) = y_1(t-t_0)$$

"

$$f_1(t-t_0)$$

$$2f_2(t) = 2f_1(t-t_0)$$

same TI system

$$y_1(t-t_0) = 2f_1(t-t_0)$$

Ex: $y(0) = y_0 \quad y(t) = y_0^2 + f(t^2)$

$$\text{zero state} \Rightarrow y_0 = 0 \Rightarrow y_{zs}(t) = f(t^2)$$

$$f_1(t) \rightarrow \boxed{\quad} \rightarrow y_1(t) = f_1(t^2)$$

$$f_2(t) \rightarrow \boxed{\quad} \rightarrow y_2(t) = y_1(t-3)$$


$$f_2(t-3)$$

$$f_2(t^2) = f_1(t^2-3)$$

$$y_1(t-3) = f_1((t-3)^2) \neq \text{TI}$$

$t_0 = 3s$
for simplicity.
Must work for
any t_0

• First Order RC and RL Circuits

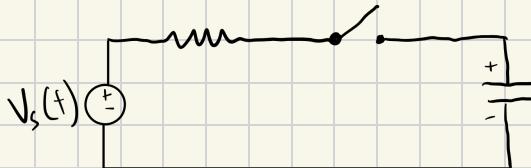

Initial Conditions:

$$V_c(0^-) = V_c(0) = V_c(0^+) - I.C.$$

$t \rightarrow 0$

KVL: $-V_s(t) + i(t) \cdot R + V_c(t) = 0$

$$i(t) = C \frac{dV_c}{dt}$$

$$RC \frac{dV_c}{dt} + V_c(t) = V_s(t)$$

$$\frac{dV_c}{dt} + \frac{1}{RC} V_c(t) = \frac{V_s(t)}{RC}$$

How to solve:

- Start with a simple case:
constant input

$$f(t) = K \Rightarrow K = \frac{dy}{dt} + ay(t) \Rightarrow K = 0 + aB \Rightarrow B = \frac{K}{a}$$

$$y(t) = B - \text{constant}$$

$$K = \frac{dy}{dt} + ay(t)$$

$$y(t) = \underbrace{\frac{K}{a}}_{\text{particular solution}} + \underbrace{y_h(t)}_{\text{homogeneous solution}}$$

$$K = \frac{d}{dt} \left(\frac{K}{a} + y_h(t) \right) + a \left(\frac{K}{a} + y_h(t) \right)$$

$$K = \frac{d}{dt} y_h(t) + K + ay_h(t)$$

$$\frac{dy_h(t)}{dt} + ay_h(t) = 0 \rightarrow -a e^{-at} + a e^{-at} = 0$$

$$\uparrow \\ y_h = A e^{-at}$$

$$y(t) = \frac{K}{a} + A e^{-at} \\ \text{when } t=0$$

$$y_p = \frac{K}{a} = V_s$$

$$y_h = (y(0) - \frac{K}{a}) e^{-at} = (V_c(0^-) - V_s) e^{-at}$$

$$V_c(t) = (V_c(0^-) - V_s) e^{-\frac{t}{RC}} + V_s$$

$t > 0$


First Order linear ordinary differential equation (ODE) with constant coefficients, which governs RC circuit for $t > 0$

Can also use $\mu(t) = e^{\frac{1}{RC}t}$

$$(e^{\frac{1}{RC}t} y(t))' = e^{\frac{1}{RC}t} \frac{1}{RC} V_s(t)$$

$$\Rightarrow \frac{V_s}{RC} = \frac{dV_c}{dt} + \frac{1}{RC} V_c(t)$$

Example

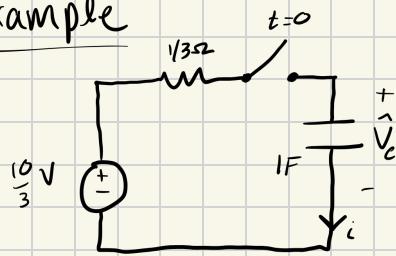

$$\textcircled{1} \quad \frac{dV_c}{dt} + \frac{1}{RC} V_c(t) = \frac{V_s}{RC} = 10$$

$\alpha = 3$

$$\textcircled{2} \quad \frac{dV_c}{dt} + 3V_c(t) = 10 \Rightarrow A + 3B = 10$$

$B = \frac{10}{3}$

$$\textcircled{3} \quad y(t) = y_p + y_h = B + Ae^{-\alpha t}$$


$$\textcircled{4} \quad V_c(t) = \frac{10}{3} + Ae^{-3t}$$

$$\textcircled{5} \quad \text{Find } A$$

$$V_c(0^-) = V_c(0^+) = 1$$

$$1 = \frac{10}{3} + A \Rightarrow A = -\frac{7}{3}$$

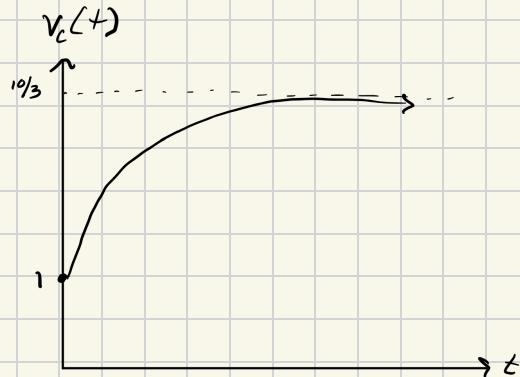
$$\textcircled{6} \quad V_c(t) = \left(\frac{10}{3} - \frac{7}{3} e^{-3t} \right) \text{ Volts}$$



$$\textcircled{7} \quad i_c(t) = C \frac{dV_c}{dt} = 7e^{-3t} \text{ Amps}$$

$$i_c(0^+) = 7A$$

$$i_c(0^-) = 0A$$

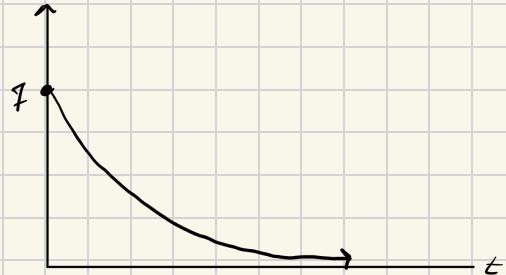

Time-Constant

• Recall

$$y(t) = \frac{k}{\alpha} + (y(0^+) - \frac{k}{\alpha}) e^{-\alpha t}$$

$$V_C(t) = \underbrace{(V_C(0^-) - V_s)}_{\text{transient response}} e^{-\frac{t}{RC}} + V_s$$

Steady state response

(a part which goes to 0 when $t \rightarrow \infty$)

(which is left after transient response has vanished)



Rate of decay is controlled by a time const.

$$\tau \uparrow \Rightarrow$$

$$\tau = RC \text{ [s]} \quad \text{unit = seconds}$$

slower decay

Simple Solution Method:

(only works for first order ODE with const coefficients and const inputs)

$$y(t) = B + Ae^{-\alpha t}$$

$$\alpha = \frac{1}{RC} = \frac{1}{\tau}$$

$$V_C(t) = B + Ae^{-\frac{t}{\tau}}$$

Need to evaluate:

$$\cdot V_C(\infty) = B + Ae^{-\frac{\infty}{\tau}} = B$$



$$i_C(t) = C \frac{dV_C}{dt}$$

at the DC steady-state ($t \rightarrow \infty$) capacitor acts as an open-circuit ($i_C = 0A$)

$$\cdot V_C(0^-) = B + A$$


$$\Delta B = V_s$$

$$A = V_c(0^-) - B = V_c(0^-) - V_s$$

$$V_c(t) = V_s + (V_c(0^-) - V_s)e^{-t/\tau}$$

Redo example w/ shortcut:
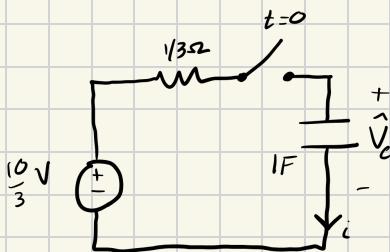
$$V_c(0^-) = 1V, \text{ determine } V_c(t) \text{ for } t > 0$$



$$\underline{t > 0}$$

$$V_c(t) = B + Ae^{-t/\tau}$$

$$V_c(\infty) = \frac{10}{3}V = B$$

$$V_c(0^-) = B + A = 1 \Rightarrow A = \left(1 - \frac{10}{3}\right) = -\frac{7}{3}$$

$$V_c(t) = \frac{10}{3} - \frac{7}{3}e^{-3t}$$

If a resistive circuit w/ a single capacitor:



Find Thevenin circuit
as seen by the
capacitor

• Zero-input (ZI), zero-state (ZS)

$$y(+)=\underbrace{\frac{K}{a}}_{\text{particular}} + \underbrace{(y(0^+) - \frac{K}{a})e^{-at}}_{\text{hom}} \xrightarrow{t \rightarrow 0}$$

$$\frac{K}{a} - \frac{K}{a} e^{-at}$$


First order circuits are when there are only one power storage device in a circuit.

Zero state is easiest to do.

Recall

$$y(t) = \frac{K}{\alpha} + (y(0^+) - \frac{K}{\alpha}) e^{-\alpha t}$$

zero state: $\frac{K}{\alpha}$

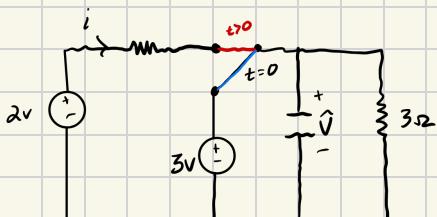

t < 0

capacitor acts as open circuit.
 $V_c(0^-) = 3V$

t > 0

$$V_c(t) = B + Ae^{-t/\tau}$$

Find τ : $\tau = R_T C \rightarrow \text{Find } R_T$
from perspective of the cap.

$$R_T = \left(\frac{3}{3+1}\right)^{-1} = \frac{3}{4}\Omega$$

Must find V_c at ∞ and initial conditions

$$V_c(\infty) = B = 2V \left(\frac{3}{3+1}\right) = \frac{3}{2}V$$


$$V_c(0^+) = V_c(0^-) = B + A \Rightarrow A = (V_c(0^-) - \frac{3}{2}V)$$

$$V_c(t) = \frac{3}{2} + \frac{3}{2}e^{-t/3}$$


$$= y_{ZS}(t) = \frac{3}{2} - \frac{3}{2}e^{-t/3}$$

$$+ y_{ZI}(t) = V_c(0^-) e^{-t/3} = 3e^{-t/3}$$
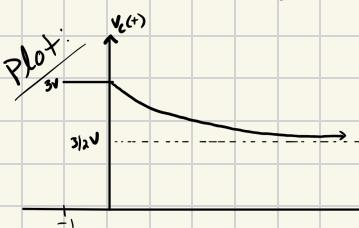
$$V_c(t) = \frac{3}{2} + \frac{3}{2}e^{-t/3}$$



Ex with inductor

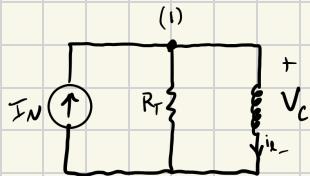

$$\text{KCL @ Node 1 : } I_{IN} = \frac{V_L}{R_T} + i_L \\ = \frac{L}{R_T} \frac{di_L}{dt} + i_L \times \frac{R_T}{L}$$

$$V_L = L \frac{di_L}{dt}$$

↳ In DC-Steady state, inductor acts as a short circuit.

$$\frac{di_L}{dt} + \frac{R_T}{L} i_L = \frac{R_T}{L} I_{IN}$$

$$T' = \frac{L}{R_T}$$

$$\alpha = \frac{1}{T'}$$


Solution should be in the form: $i_L(t) = B + A e^{-\alpha t}$

$$i_L(t) = B + A e^{-\frac{t}{T'}}$$

$$i_L(\infty) = B$$

$$i_L(0^+) = i_L(0^-) = B + A$$

Example:

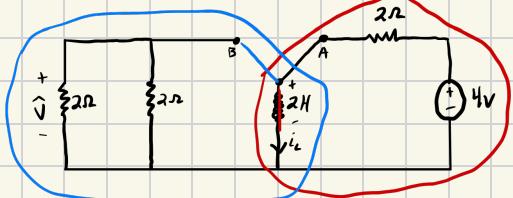

$t < 0$

$$i_L(0^-) = \frac{4V}{2\Omega} = 2A$$

$t > 0$

$$i_L(t) = B + A e^{+t/T}$$

$$T' = \frac{L}{R_T}$$

$$\text{First Find } T': T' = \frac{L}{R_T}$$

$R_T = 1\Omega$ (From perspective of the inductor)

$$T' = \frac{2H}{1\Omega} = 2s$$

$$i_L(0^+) = B = 0A \text{ (no source)}$$

$$i_L(0^-) = i_L(0^+) = 0 + A$$

$$i_L(t) = i_L(0^-) e^{-\frac{t}{T'}} \text{ Amps}$$

$$\left\{ \begin{array}{l} i_{2S}(t) = i_L(0^-) e^{-\frac{t}{T'}} \text{ Amps} \\ i_{2S}(t) = 0 \text{ (force } i_L(0^-) \text{ to be } 0) \end{array} \right.$$

$$i_{2I}(t) = i_L(0^-) e^{-\frac{t}{T'}} = 2e^{-\frac{t}{2}} \text{ Amps}$$

What if the circuit goes from A \rightarrow B \rightarrow A

$t < 0$

$$i_L(0^-) = \frac{4}{2} = 2A$$

$0 < t < 2$

$$i_L(t) = B + Ae^{-\frac{t}{T}} ; T = 2s$$

$$i_L(\infty) = B = 0$$

$$i_L(0^+) = i_L(0^-) = A = 2$$

$$i_L(t) = 2e^{-\frac{t}{2}} \text{ amps}$$

Now going
back to pos A
 \rightarrow

$t > 2$

$$i_L(t) = \hat{B} + \hat{A}e^{-\frac{t}{T}}$$

Consider the particular solution:

$$y_p(t) = \frac{1}{2}\cos(t) + \frac{1}{2}\sin(t) = H\cos(t+\gamma)$$
$$= H\cos(\gamma)\cos(t) - H\sin(\gamma)\sin(t) \Rightarrow H\cos(\gamma) = \frac{1}{2}$$
$$-H\sin(\gamma) = \frac{1}{2}$$

Determine H and γ

Get γ :

$$\frac{H\sin(\gamma)}{H\cos(\gamma)} = \frac{-\frac{1}{2}}{\frac{1}{2}} = \tan(\gamma) = -1 \Rightarrow$$
$$\gamma = -\frac{\pi}{4} \text{ or } \frac{3\pi}{4}$$

Get H

$$H\cos(\gamma) = \frac{1}{2}$$

$$H\cos(\frac{3\pi}{4}) = \frac{1}{2}$$

$$H = \frac{\sqrt{2}}{2} \text{ or } -\frac{\sqrt{2}}{2}$$

$$y_p(t) = \frac{\sqrt{2}}{2} \cos\left(t - \frac{\pi}{4}\right)$$

Transient Response vs. Steady-State Response

Transient: $y_{tr}(t) \forall$:

$t \rightarrow \infty$

$$y_{tr}(t) \rightarrow 0$$

Steady state: $y_{ss}(t)$ is what's left after $y_{tr} \rightarrow 0$

$$y(t) = y_{tr}(t) + y_{ss}(t)$$

• Recall

$$y(t) = \underbrace{Ae^{-at}}_{\text{transient}} + \underbrace{B}_{\text{ss}}$$

$$y(t) = \underbrace{Ae^{-at}}_{\text{transient}} + \underbrace{Be^{-pt}}_{\text{transient}}$$

$$y(t) = \underbrace{Ae^{-at}}_{\text{transient}} + \underbrace{H\cos(\omega t + \gamma)}_{\text{steady state}}$$

Last Week:

$$\frac{dy}{dt} + \frac{y}{t} = C_1 \Rightarrow y(t) = K_1 e^{-\frac{t}{t}} + K_2$$

Lets make a particular solution table

What if:

$$\frac{dy}{dt} + \frac{y}{t} = f(t)$$

$$(y = y_h(t) + y_p(t))$$

$$\text{st } \frac{dy_h}{dt} + \frac{y_h}{t} = 0$$

$f(t)$	$y_p(t)$
C_1	C_2
$Kt + b$	$at + b$
polynomial of degree "n"	polynomial w/ same degree "n" with all other lower terms.
$\cos(\omega t)$ or $\sin(\omega t)$	$A\cos(\omega t) + B\sin(\omega t)$
Ae^{ct}	If $\begin{cases} C \neq -\frac{1}{t}, Be^{ct} \\ C = -\frac{1}{t}, Bte^{ct} \end{cases}$

Example:

$$\frac{dy}{dt} + y = e^{-2t}$$

$$y_h = Ae^{-t/2}; \quad t=1 \\ = Ae^{-t}$$

$$y = Ae^{-t} - e^{-2t}$$

use I.C. (initial conditions)
to find A.

$$\begin{aligned}
 & y_h: C = -\frac{1}{t} \\
 & y_p = Be^{-2t} \\
 & \left. \begin{array}{l} \text{plug into original eq. where} \\ y = y_p \end{array} \right\} \frac{dy}{dt} = -2Be^{-2t} \\
 & -2Be^{-2t} + Be^{-2t} = e^{-2t} \\
 & -Be^{-2t} = e^{-2t} \\
 & B = -1 \\
 & \Delta y_p = -e^{-2t}
 \end{aligned}$$

Example:

$$\frac{dy}{dt} + y = e^{-t}$$

$$y_p = Bte^{-t}$$

$$-Bte^{-t} + Be^{-t} + Be^{-t} = e^{-t}$$

$$\frac{dy_h}{dt} + y_h = 0$$

$$\Rightarrow \frac{dy_p}{dt} = B(-te^{-t} + e^{-t})$$

$$Be^{-t} = e^{-t}$$

$$B=1$$

$$y_p = te^{-t}$$

$$y_h = Ae^{-t}$$

Particular is at the same order as homogeneous we must multiply by t.

Δy :

$$y = y_h + y_p \Rightarrow y = Ae^{-t} + te^{-t}$$

Example:

$$\frac{dy}{dt} + y = t^2$$

$$y_p = Bt^2 + Ct + D$$

plugging in

$$2Bt + C + Bt^2 + Ct + D = t^2$$

$$y_h = Ae^{-t}$$

$$\frac{dy_p}{dt} = 2Bt + C$$

$$Bt^2 + \underline{2Bt + Ct} + \underline{C + D} = t^2$$

$$\tau = 1$$

$$y_p = t^2 - 2t + 2$$

$$B = 1 \quad A + C = 0 \Rightarrow C = -A$$

$$2B + C = 0$$

$$C + D = 0 \quad D = -C \Rightarrow D = 2$$

$$y = Ae^{-t} + t^2 - 2t + 2$$

Ex w/ Sinusoidal input

$$\frac{dy}{dt} + y = \cos(t)$$

$$y_p = B\cos(t) + C\sin(t)$$

$$-B\sin(t) + C\cos(t) + B\cos(t) + C\sin(t) = \cos(t)$$

$$y_h = Ae^{-t}; \tau = 1$$

$$\frac{dy_p}{dt} = -B\sin(t) + C\cos(t)$$

$$C + B = 1 \quad C = \frac{1}{2}, B = \frac{1}{2}$$

$$C - B = 0$$

$$y = Ae^{-t} + \frac{\sqrt{2}}{2}\cos(t - \frac{\pi}{4})$$

$$y_p = \frac{1}{2}\cos(t) + \frac{1}{2}\sin(t)$$

$$C = B$$

$$C\cos(t) + D\sin(t) = K\cos(t + \theta)$$

$$K = \sqrt{\frac{1}{4} + \frac{1}{4}} = \sqrt{\frac{2}{4}} = \frac{\sqrt{2}}{2}$$

$$\theta = \tan^{-1}\left(\frac{-1}{1}\right) = \tan^{-1}(-1) = -\frac{\pi}{4}$$

$$\begin{cases} K = \sqrt{A^2 + B^2} \\ \theta = \tan^{-1}\left(\frac{-B}{A}\right) \end{cases}$$

• Dissipative Systems

- has a transient zero-state response

$$y_{zi}(t) \rightarrow 0$$


$t \rightarrow \infty$

- the ss response to a sinusoidal input applied at $t = -\infty$ will be sinusoidal independent of the initial state

$$y(t) = Ae^{-at} + \underbrace{H\cos(\omega t + \gamma)}_{y_{ss}(t)}$$

• n^{th} order LTI systems

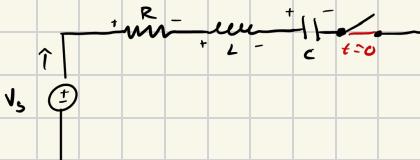- Determine the ODE governing the capacitor voltage in the following circuit:



$$-V_s + V_R + V_C + V_L = 0$$

$$-V_s + iR + L \frac{di}{dt} + V_C = 0$$

$$-V_s + R(C \frac{dV_C}{dt}) + L \frac{d}{dt}(C \frac{dV_C}{dt}) + V_C = 0$$

In general: $\frac{d^n y}{dt^n} + \alpha_1 \frac{d^{n-1} y}{dt^{n-1}} + \dots + \alpha_n y = f(t)$

Where n-number of energy storage elements (L, C)

Solution is

$$y(t) = \underbrace{y_p(t)}_{\text{same as in 1st order ODE}} + y_n(t)$$


same as in 1st order ODE

$$\text{if } P_1 = P_2 \quad A_1 e^{-P_1 t} + t A_2 e^{-P_2 t} + \dots$$

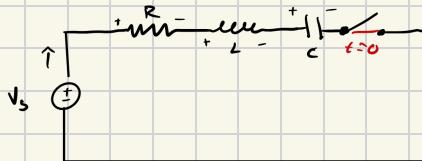Example:

For $t > 0$, obtain $V_c(t)$

$$V_s = 0 \text{ V}, R = 0 \Omega, i_c(0^-) = 0 \text{ A}, V_c(0^-) = 1 \text{ V}, L = 1 \text{ H}, C = 1 \text{ F}$$



$$\frac{V_c}{LC} = \frac{\partial^2 V_c}{\partial t^2} + \frac{R}{L} \frac{\partial V_c}{\partial t} + \frac{V_c}{LC} - 1$$

$$0 = \frac{\partial^2 V_c}{\partial t^2} + V_c$$

Now we find A_1 and A_2 :

$$V_c(0^-) = V_c(0^+) = 1 \text{ V}$$

$$i_c = A_1 + A_2 \quad \textcircled{1}$$

$$i_c(0^+) = 0 \text{ A}$$

$$i_c(t) = C \frac{\partial V_c}{\partial t} = -j A_1 e^{-jt} + j A_2 e^{jt}$$

$$i_c(0^+) = -j A_1 + j A_2 = 0 \quad \textcircled{2}$$

$$\text{Solving } \textcircled{1} \text{ and } \textcircled{2} \Rightarrow A_1 = A_2 = \frac{1}{2}$$

Solution:

$$\frac{\partial^2 V_c}{\partial t^2} + V_c = 0$$

$$y_n(t) = e^{st}$$

$$s^2 + 1 = 0$$

$$s = \pm \sqrt{-1} = \pm j$$

$$y_n = A_1 e^{-jt} + A_2 e^{jt}$$

$$y_n = \frac{1}{2} e^{-jt} + \frac{1}{2} e^{jt}$$

$= \cos(t) \rightarrow$ zero-input response

is not transient

$$i_c(t) = -\sin(t) \text{ Amps}$$

system
is non-dissipative

Friday Lecture: to Watch

Last time:

- must convert sin into cos
- phasors are cos-based objects

Phasor Superposition

- The weighted superposition
- Don't have to have same magnitude, must have same frequency

Derivative Principle

The derivative

$$g(t) = \frac{d}{dt} f(t)$$

of co-sinusoid $f(t) = \operatorname{Re}[F e^{j\omega t}]$ is also a co-sinusoid with phasor

$$G = j\omega F$$

Note: N^{th} derivative

$$\frac{d^n f}{dt^n} = (j\omega)^n F$$

Consider

$$f(t) = 3\cos(2t + \frac{\pi}{4}) \rightarrow F = 3e^{j\frac{\pi}{4}} = 3\left(\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}\right)$$

Determine $f'(t)$

$$\begin{aligned} g(t) &= \operatorname{Re}[G e^{j\omega t}] \\ G &= j\omega F = j2\left(\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}\right) \\ &= j\frac{2}{\sqrt{2}} - \frac{2}{\sqrt{2}} = \end{aligned}$$

$$A = \sqrt{\left(\frac{2}{\sqrt{2}}\right)^2 + \left(-\frac{2}{\sqrt{2}}\right)^2} = 2$$

$$\Theta = \pi + \tan^{-1}(-1) = \pi - \frac{\pi}{4} = \frac{3\pi}{4}$$

Determine the steady state solution to the following diff eq.

$$\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + y = -5 \sin(at)$$

↓
phasors

turn this to pos by shifting π
then convert to cos by subtracting $\frac{\pi}{2}$

- turn into phasor
 $= 5 \cos(at + \frac{\pi}{2})$
 $= 5e^{j\pi/2} = 5j$


$$(j\omega)^2 + 2j\omega y + y = 5j$$

$$-4y + j4y + y = j^5$$

$$y = \frac{j^5}{-3+j4} = \frac{5e^{j\pi/2}}{3e^{j(\pi/4-\tan^{-1}(4/3))}}$$

$$y_{ss} = 1 \cos\left(at + \frac{\pi}{2} - \pi - \tan^{-1}\left(\frac{4}{3}\right)\right) = \cos\left(at - \frac{\pi}{2} - \tan^{-1}\left(\frac{4}{3}\right)\right)$$

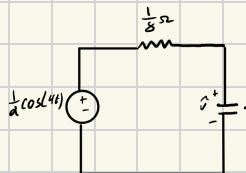Determine $\hat{V}_{ss}(t)$ using phasors



$$\text{KVL: } \frac{-1}{2} \cos(4t) + \frac{1}{4} \frac{d\hat{v}}{dt} + \hat{v} = 0$$

$$\frac{1}{4} \frac{d\hat{v}}{dt} + \hat{v} = \frac{1}{2} \cos(4t)$$

$$\frac{1}{4}(j\omega) \hat{v} + \hat{v} = \frac{1}{2} \quad \frac{1}{4} e^{j\pi} = -\frac{1}{2}$$

$$j\hat{v} + \hat{v} = \frac{1}{2}$$

• V-I relationships in phasors


• Resistor

$$V(t) = R \cdot i(t)$$

$$V = IR$$

$$|V|e^{j\theta_V} = R \cdot |I|e^{j\theta_I} \Rightarrow \theta_V = \theta_I \quad (\text{voltage and current are in-phase})$$

• Inductor

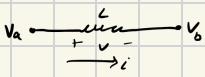

$$V(t) = L \frac{di}{dt}$$

↓ phasors

$$V = (Lj\omega) I = Z I = V$$


Z-impedance [N]

$$|V|e^{j\theta_V} = LWe^{j\frac{\pi}{2}} |I|e^{j\theta_I} = \theta_V = \theta_I + \frac{\pi}{2}$$

$\theta_I = \theta_V - \frac{\pi}{2}$

Voltage leads current by $\frac{\pi}{2}$, or current lags voltage by $\frac{\pi}{2}$

• Capacitor

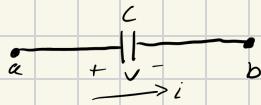

$$i = C \frac{dv}{dt}$$

↓ phasors

$$I = C j\omega V \rightarrow \frac{1}{j\omega C} I = V$$


$$Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$V = Z \cdot I$$

$$|V|e^{j\theta_V} = \frac{1}{\omega C} e^{-j\frac{\pi}{2}} |I|e^{j\theta_I}$$

$$\theta_V = \theta_I - \frac{\pi}{2}$$

$$\theta_I = \theta_V + \frac{\pi}{2}$$

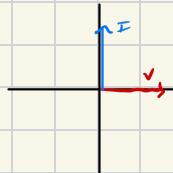


Current leads
Voltage by
 $\frac{\pi}{2}$

• V-I relationships in phasors

$$\text{Impedance, } Z = \left\{ \begin{array}{l} R \quad \text{resistor} \\ j\omega L \quad \text{inductor} \\ \frac{1}{j\omega C} = \frac{-j}{\omega C} \quad \text{capacitor} \end{array} \right\} \begin{array}{l} \leftarrow \text{purely resistive} \\ \leftarrow \text{purely reactive} \end{array}$$

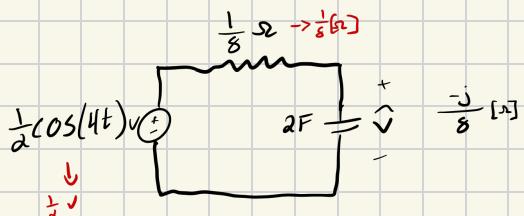• Determine $\hat{V}_{ss}(+)$ using phasors





Voltage Division

$$\hat{V} = \frac{1}{2} \left(\frac{-j/8}{-j/8 + \frac{1}{8}} \right) = \frac{1}{2} \left(\frac{-j}{-j+1} \right) = \frac{1}{2} \left(\frac{e^{-j\frac{\pi}{4}}}{j+1} \right) = \frac{1}{2\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$\hat{V}_{ss}(+) = \frac{1}{2\sqrt{2}} \cos(4t - \frac{\pi}{4}) [V]$$


Ex

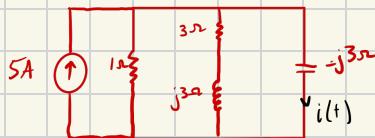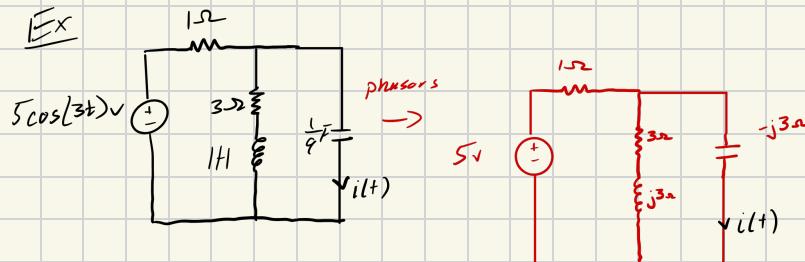

$$5A \left(\frac{Z_P}{-j^3} \right) =$$


Current division

Multiple Sources

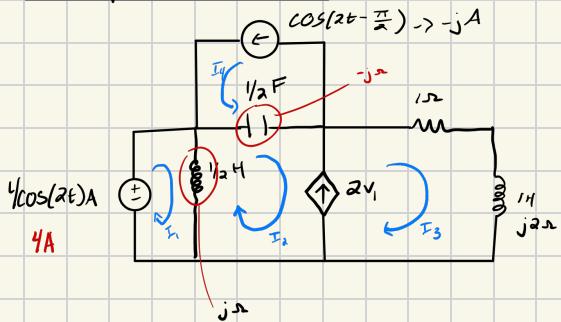


Can use node-voltage method or loop current

- We can still find Thevenin equivalents

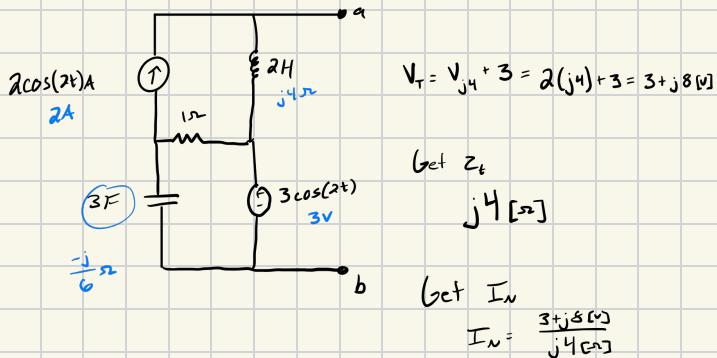

- Average power

- Recall $P = IV$

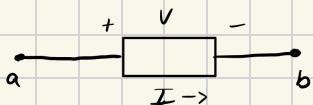

- If v and i are time varying, then the instantaneous power is

$$p(t) = v(t)i(t)$$

- For periodic signals with period T , the average power is:

$$P = \frac{1}{T} \int p(t) dt = \frac{1}{T} \int v(t)i(t) dt$$

$$\frac{1}{2} (\text{Re}\{Vi e^{j\omega t}\} + \text{Re}\{Vi^* e^{-j\omega t}\})$$

Average Power for Phasor

$$P = \frac{1}{T} \int_T P(t) dt = \frac{1}{T} \int_T V(t) I(t) dt$$

$$P = \frac{1}{T} \int_T \frac{1}{2} \left(\operatorname{Re}\{VI e^{j\omega t}\} + \operatorname{Re}\{VI^*\} \right) dt =$$


$$= \frac{1}{2T} \int_T \operatorname{Re}\{VI e^{j\omega t}\} dt + \left(\frac{1}{2T} \int_T \operatorname{Re}\{VI^*\} dt \right)$$

$$= \underbrace{\frac{1}{T} \int_T |VI| \cos(\omega t + \angle VI) dt}_{\text{Average of } \cos \text{ over } T \text{ cycles}} + \frac{1}{2} \operatorname{Re}\{VI^*\}$$

$$P = \frac{1}{2} \operatorname{Re}\{VI^*\}$$

angle of VI
Average of a \cos over a cycles
is zero


Average Absorbed Power

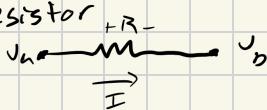Resistor 

$$P = \frac{1}{2} \operatorname{Re}\{VI^*\} = \frac{1}{2} (\operatorname{Re}\{R \cdot I \cdot I^*\})$$

$$= \frac{1}{2} R(I^2) = \frac{1}{2} \frac{|V|^2}{R}$$

Inductor


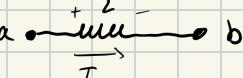


$$P = \frac{1}{2} \operatorname{Re}\{VI^*\} = \frac{1}{2} \operatorname{Re}\{j\omega L |I^2|\} = 0$$


Capacitor $\rightarrow P = 0W!$

 OW since they store energy then end up discharging it (1 cycle charge, 1 cycle discharge)

- Determine Avg Power for each element

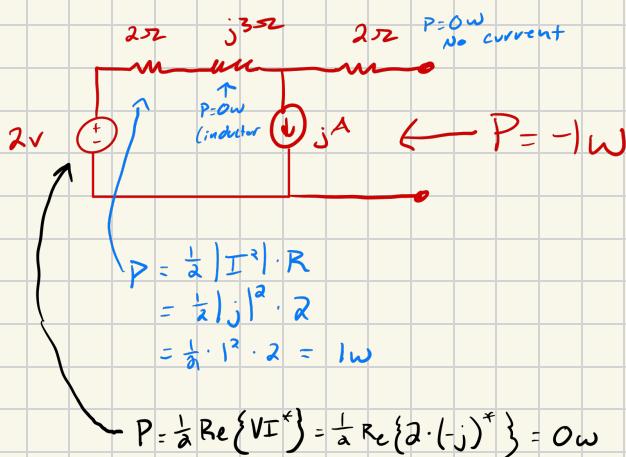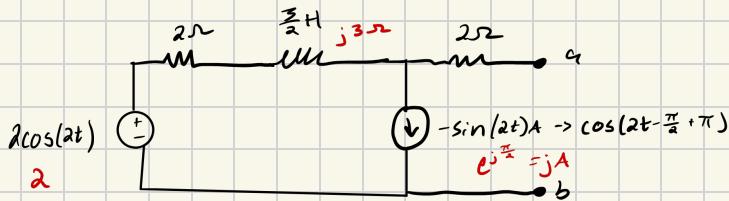

• Available Power

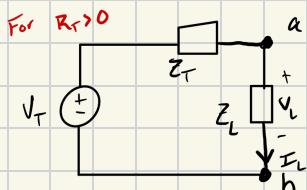

$$P_a = \frac{|V_T|^2}{8R_T} = \frac{1}{2} \frac{|V_T|^2}{|Z_T + Z_L|^2}$$

From phasors

only real part of Z_T

$$Z_T = R_T + jX_T$$

$$Z_L = R_L + jX_L$$

$$I_L = \frac{V_T}{Z_T + Z_L}$$

$$V_L = V_T \left(\frac{Z_L}{Z_T + Z_L} \right)$$

$$P_L = \frac{1}{2} \operatorname{Re}\left\{ V_L \cdot I_L^* \right\} = \frac{1}{2} \operatorname{Re}\left\{ \frac{V_T \cdot Z_L}{Z_T + Z_L} \cdot \frac{V_T^*}{Z_T + Z_L} \right\} =$$



$$= \frac{1}{2} \operatorname{Re}\left\{ \frac{|V_T|^2 \cdot Z_L}{|Z_T + Z_L|^2} \right\}$$

$$= \frac{1}{2} \frac{|V_T|^2 \cdot R_L}{|Z_T + Z_L|^2} =$$

$$= \frac{1}{2} \frac{|V_T|^2 \cdot R_L}{|(R_T + R_L) + j(X_T + X_L)|^2}$$

$$Z_L = R_L - jX_T = Z_T^* \quad \begin{cases} X_L = -X_T \\ R_L = R_T \end{cases}$$

Example:

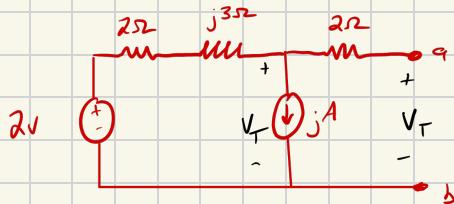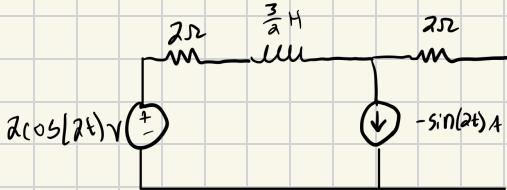

Get V_T :

$$\text{KVL: } -2 + 2j + j(3) + V_T = 0$$

$$V_T = 5 - j2V$$

Get Z_T


$$Z_T = 2 + j_3 + 2 = \boxed{4 + j3\Omega}$$

$$P_a = \frac{1}{2} \frac{|V_T|^2}{4R_T} = \frac{1}{2} \frac{\sqrt{5^2 + (-2)^2}}{4 \cdot 4}^2 = \frac{25}{32} \omega \quad \text{only if } \boxed{P_T}$$

$$Z_L = Z_T^* = 4 - j3\Omega$$

• Resonance

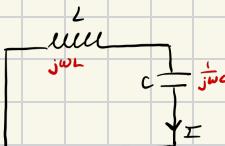- Circuit below with $v_c(0^-) = 1V$, $i_L(0^-) = 0A$, $v_c(t) = 4\cos(\omega t)$



KVL: $v_L + v_C = 0$

$$j\omega L \cdot I + \frac{1}{j\omega C} I = 0$$

$$I(j\omega L - \frac{1}{j\omega C}) = 0$$

can be satisfied by any I as long as $j\omega L - \frac{1}{j\omega C} = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

resonant frequency

What if we add a source?

$$V_c = V_i \left(\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L} \right) = \frac{V_i}{\frac{1}{j\omega C} + j\omega L + \frac{1}{j\omega C}}$$

if $\omega = \frac{1}{\sqrt{LC}}$

What if we also add a resistor?

$$V_c = V_i \left(\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L + R} \right) = \frac{V_i}{1 - \omega^2 LC + j\omega RC}$$

$$V_L = V_i \left(\frac{j\omega L}{j\omega L + \frac{1}{j\omega C} + R} \right) = j \sqrt{\frac{L}{C}} \cdot \frac{1}{R} \cdot V_i = -V_c$$

complex conjugate of one another


$$V_c + V_L = 0$$

(net zero voltage)

$$Z_s = R + j\omega L - \underbrace{\frac{j}{\omega C}}$$


$= 0$ if $\omega = \frac{1}{\sqrt{LC}}$

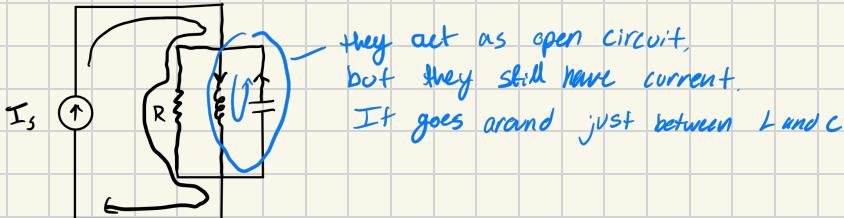- What if the elements are in parallel : Parallel Resonance



Chapter 5 Frequency Response $H(\omega)$ of LTI Systems

Example:

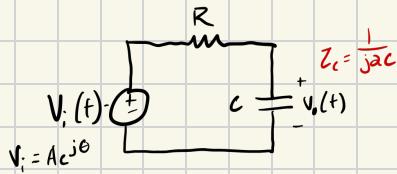

$$\text{let } V_i(t) = A \cos(\omega t + \theta)$$

Determine $V_{o,ss}(+)$

$$V_o = V_i \left(\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right) = V_i \left(\frac{1}{j\omega RC + 1} \right)$$

$$= \frac{|V_i| e^{j\angle V_i}}{\sqrt{1 + (\omega RC)^2}} e^{j\tan^{-1}(\frac{\omega RC}{1})}$$

$$V_o = \frac{|V_i|}{\sqrt{1 + (\omega RC)^2}} e^{j(\angle V_i - \tan^{-1}(\frac{\omega RC}{1}))}$$

$$H(\omega) = |H(\omega)| e^{j\angle H(\omega)}$$

$$\text{Amplitude response: } \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = |H(\omega)|$$


$$\text{Phase response: } -\tan^{-1}(\omega RC) = \angle H(\omega)$$


$$V_o = V_i H(\omega)$$

↑ ↑
output phasor input phasor

$$V_i = |V_i| e^{j(\angle V_i)}$$

$$V_o = |V_i| |H(\omega)| e^{j(\angle V_i + \angle H(\omega))}$$

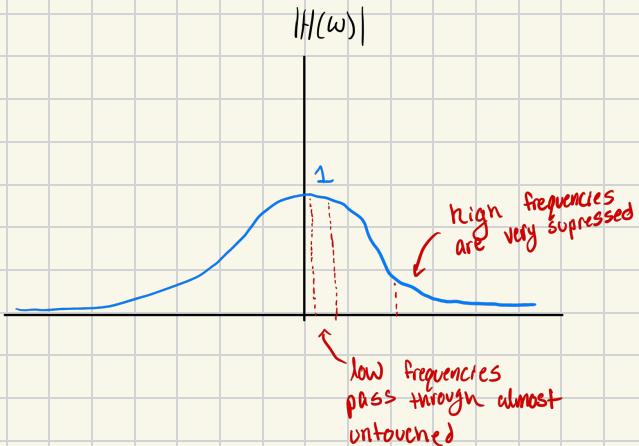

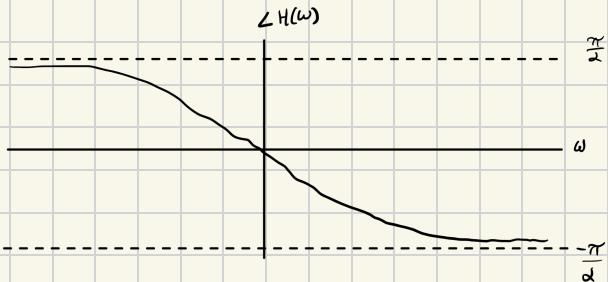

• Recall from example above:

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$

Find $V_o(t)$ if $V_i(t) = 2 \cos(3t + \frac{\pi}{3})$

$$V_o = |V_i| |H(3)| \cos(3t + \frac{\pi}{3} - \angle H(3))$$

Find $V_o(t)$ if $V_i(t) = 3 \sin(6t + \frac{\pi}{6})$
 $= 3 \cos(6t - \frac{\pi}{3})$

$$V_o(t) = 3 |H(6)| \cos(6t - \frac{\pi}{3} - \angle H(6))$$

• For LTI systems with

input $f(t) = \text{Re}\{F e^{j\omega t}\}$

output $y(t) = \text{Re}\{Y e^{j\omega t}\}$

$$f(t) \rightarrow \boxed{\text{LT\!T}} \rightarrow y(t)$$

$$F \rightarrow \boxed{H(\omega)} \rightarrow Y = F \cdot H(\omega)$$


We have:

$$Y = FH(\omega)$$

$$F = |F| e^{j\angle F}$$

$$Y = |F| |H(\omega)| e^{j(\angle F - \angle H(\omega))}$$

Example

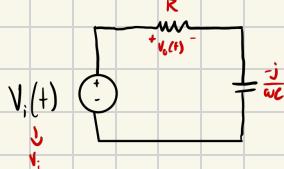


$$V_o = V_i \left(\frac{R}{R + \frac{1}{j\omega C}} \right) = V_i \frac{j\omega RC}{j\omega RC + 1} \quad H(\omega)$$

$$|H(\omega)| = \frac{|ω| RC}{\sqrt{1 + ω^2 R^2 C^2}}$$


$$\angle H(\omega) = \begin{cases} \frac{\pi}{2} - \tan^{-1}(\omega RC) & \text{if } \omega > 0 \\ -\frac{\pi}{2} - \tan^{-1}(\omega RC) & \text{if } \omega < 0 \\ 0 & \text{if } \omega = 0 \end{cases}$$

Let $V_i(t) = A \cos(\omega t + \theta)$

$$|H(\omega)|$$

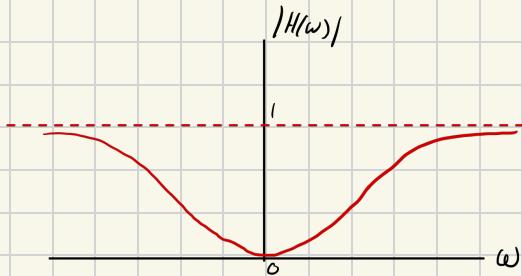

Example:

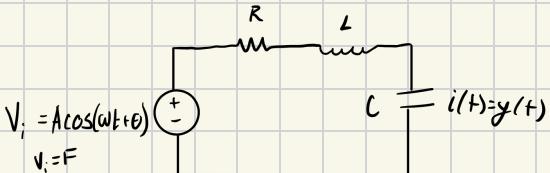

$$H(\omega) = \frac{Y}{F} = \frac{I}{V_i}$$

$$I = \frac{V_i}{R + j\omega L + \frac{1}{j\omega C}}$$

Consider the ODE

$$\frac{dy}{dt} + y = 3f(t) ; \text{ let } f(t) = A \cos(\omega t + \theta)$$

$$j\omega Y + Y = 3F \quad \rightarrow \quad Y = \frac{3F}{j\omega + 1}$$

Find $H(\omega)$, $|H(\omega)|$, and $\angle H(\omega)$

$$H(\omega) = \frac{Y}{F} ; \quad Y = F H(\omega)$$

$$|H(\omega)| = \sqrt{\frac{3}{1 + \omega^2}}$$

$$\angle H(\omega) = 0 - \tan^{-1}(\omega) = -\tan^{-1}(\omega)$$

comes from $\frac{Y}{F} \leftarrow \begin{matrix} \text{angle of } F \\ \text{minus angle of } Y \end{matrix}$

- General First Order filters and second order filters

- Low pass

$$|H(0)| = C$$

$$|H(\infty)| = 0$$

$$|H(\omega)| \approx \frac{1}{\sqrt{1+\omega^2}}$$

- High Pass

$$|H(0)| = 0$$

$$|H(\infty)| = C$$

$$|H(\omega)| \approx \frac{|w|}{\sqrt{1+w^2}}$$

- Band Pass (only for dissipative systems)

$$|H(0)| = 0$$

$$|H(\infty)| = 0$$

in between
 $H(\pm) \neq 0$

$$|H(\omega)| \approx \frac{|w|}{\sqrt{w^2 + (1-w^2)^2}}$$

Note: $\frac{H(0)}{w}$ is real number

- Properties of $H(\omega)$ for real valued LTI systems

- Conjugate Symmetry $H(\omega) = H^*(\omega)$

- Even Amplitude Response $|H(\omega)| = |H(-\omega)|$

- Odd Phase Response $\angle H(\omega) = -\angle H(-\omega)$

- Real-Valued DC Response $H(0) \in \mathbb{R}$

- Steady-State response to complex exponential

$$f(t) = A e^{j(\omega t + \theta)} \quad H(\omega) A e^{j(\omega t + \theta)}$$

$\hookrightarrow [H(\omega)]$

• What if you have multiple frequencies

Let $f(t) = \cos\left(\frac{1}{\alpha}t\right) + 3\cos\left(2t + \frac{\pi}{4}\right) + 2\sin(3t)$

↓ ↓ ↓
input ω_1 ω_2 ω_3

$$y(t) = \frac{d}{dt} f(t)$$

$$Y = j\omega F$$

Find $y_{ss}(t)$

(1) $H(w)$, $|H(w)|$, $\angle H(w)$

$$H(w) = \frac{Y}{F} = jw$$

$$|H(w)| = |w|$$


(2) $y_{ss}(t) = 1 \cdot |H(\frac{1}{\alpha})| \cos\left(\frac{1}{\alpha}t + \angle H(\frac{1}{\alpha})\right) + 3|H(2)| \cos\left(2t + \frac{\pi}{4} + \angle H(2)\right) +$

$$2|H(3)| \sin(3t + \angle H(3)) =$$

$$= \frac{1}{\alpha} \cos\left(\frac{1}{\alpha}t + \frac{\pi}{4}\right) + 3 \cdot 2 \cos\left(2t + \frac{\pi}{4} + \frac{\pi}{2}\right) + 2 \cdot 3 \sin(3t + \frac{\pi}{2})$$

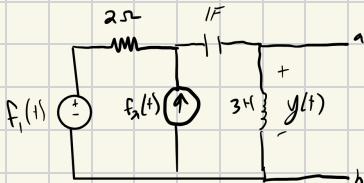
Example:

$$f_1(t) = 2\cos\left(\frac{1}{3}t\right) V \text{ and } f_2(t) = 3\sin(t) A$$




Look at each source individually
and add in time domain
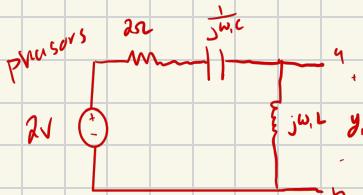
$$y_{ss}(t) = y_{ss_1}(t) + y_{ss_2}(t)$$



$$y_1 = \frac{1}{\sqrt{a}} e^{j\frac{3\pi}{4}} \xrightarrow{\text{convert to time domain}} = \frac{1}{\sqrt{a}} \cos\left(\frac{1}{3}t + \frac{3\pi}{4}\right) V$$

Only $f_2(t)$

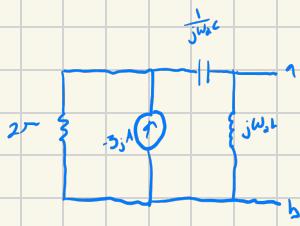

$$Y_2 = \frac{1}{j\omega_L} e^{-j\frac{\pi}{4}} \rightarrow y_{ss_2} = \frac{1}{\sqrt{2}} \cos(t - \frac{\pi}{4}) v$$

$$y_{ss} = y_{ss_1} + y_{ss_2} = \frac{1}{\sqrt{2}} \cos\left(\frac{1}{3}t + \frac{3\pi}{4}\right) + \frac{1}{\sqrt{2}} \cos(t - \frac{\pi}{4})$$

Frequency Response

$$f(t) \rightarrow \boxed{\text{system}} \rightarrow y(t)$$


$$f(t) = F_p \cos(\omega t) \longleftrightarrow \bar{F} = F_p \angle 0^\circ$$

$$F_p \angle 0^\circ \rightarrow \boxed{\text{system}} \rightarrow Y_p \angle \theta$$

$H(\omega)$ ← frequency response (complex)

$$\bar{Y} = H(\omega) \bar{F} \Rightarrow H(\omega) = \frac{\bar{Y}}{\bar{F}}$$

Ex: RC Circuit

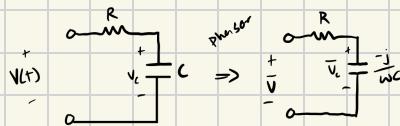

$$\bar{V}_c = \left(\frac{\frac{-j}{\omega C}}{R + j\frac{1}{\omega C}} \right) \bar{V} \Rightarrow \left(\frac{\frac{-j(R+j/\omega C)}{\omega C}}{R^2 + j(\omega C)^2} \right) \bar{V} = \left(\frac{\frac{1}{(\omega C)^2} - j \frac{R}{\omega C}}{R^2 + (\omega C)^2} \right) \bar{V}$$

$$= \left(\frac{\frac{1}{R\omega^2} - j \frac{\omega}{RC}}{\omega^2 + \frac{1}{(RC)^2}} \right) \bar{V} \quad \omega_c = \frac{1}{RC} \Rightarrow \underbrace{\left(\frac{\omega_c^2 - j \omega \omega_c}{\omega^2 + \omega_c^2} \right)}_{H(\omega)} \bar{V}$$

$$\rightarrow H(\omega) = \frac{\omega_c^2 - j \omega \omega_c}{\omega_c^2 + \omega^2}$$

$$|H(\omega)| = \sqrt{Re^2 + Im^2} = \sqrt{\left(\frac{\omega_c^2}{\omega_c^2 + \omega^2} \right)^2 + \left(\frac{-\omega \omega_c}{\omega_c^2 + \omega^2} \right)^2} = \sqrt{\frac{\omega_c^4 + \omega^2 \omega_c^2}{(\omega_c^2 + \omega^2)^2}} \sqrt{\frac{\omega_c^2 (\omega_c^2 + \omega^2)}{(\omega_c^2 + \omega^2)^2}} = \sqrt{\frac{\omega_c^2}{\omega_c^2 + \omega^2}} =$$

$$|H(\omega)| = \sqrt{\frac{1}{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\frac{\omega}{\omega_c} \rightarrow 0, |H(\omega)| \rightarrow 1$$

$$\frac{\omega}{\omega_c} \rightarrow \infty, |H(\omega)| \rightarrow 0$$



$$\Theta(\omega) = \tan^{-1}\left(\frac{Im}{Re}\right) \rightarrow \Theta(\omega) = \tan^{-1}\left(\frac{-\omega w_c}{w_c^2}\right) = \tan^{-1}\left(\frac{-\omega}{\omega_c}\right)$$


$$\frac{\omega}{\omega_c} \rightarrow 0, \theta \rightarrow 0 \quad \frac{\omega}{\omega_c} \rightarrow \infty, \theta \rightarrow -\frac{\pi}{2}$$



RL Low Pass



R-L High Pass

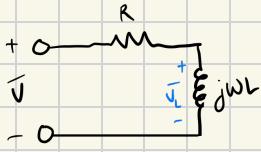

$$\begin{aligned}
 H(\omega) &= \frac{j\omega L}{R + j\omega L} \bar{V} \\
 &= \frac{j\omega L(R - j\omega L)}{R^2 + (\omega L)^2} \bar{V} = \frac{j\omega LR + \omega^2 L^2}{R^2 + \omega^2 L^2} \bar{V} = \frac{j\omega \left(\frac{L}{R}\right) + \omega^2 \left(\frac{L}{R}\right)^2}{1 + \omega^2 \left(\frac{L}{R}\right)^2} \bar{V} \\
 &= \frac{j\left(\frac{\omega}{\omega_c}\right) + \left(\frac{\omega}{\omega_c}\right)^2}{1 + \left(\frac{\omega}{\omega_c}\right)^2} \bar{V}
 \end{aligned}$$

$H(\omega)$

$$\begin{aligned}
 |H(\omega)| &= \sqrt{\left(\frac{\left(\frac{\omega}{\omega_c}\right)^2}{1 + \left(\frac{\omega}{\omega_c}\right)^2}\right)^2 + \left(\frac{\omega}{1 + \left(\frac{\omega}{\omega_c}\right)^2}\right)^2} \\
 &= \sqrt{\frac{\left(\frac{\omega}{\omega_c}\right)^2 \left(1 + \left(\frac{\omega}{\omega_c}\right)^2\right)}{\left(1 + \left(\frac{\omega}{\omega_c}\right)^2\right)^2}} = \sqrt{\frac{\left(\frac{\omega}{\omega_c}\right)^2}{1 + \left(\frac{\omega}{\omega_c}\right)^2}}
 \end{aligned}$$

$$\frac{\omega}{\omega_c} \rightarrow 0, |H(\omega)| \rightarrow 0$$


$$\frac{\omega}{\omega_c} \rightarrow \infty, |H(\omega)| \rightarrow 1$$



$$\Theta(w) = \tan^{-1}\left(\frac{Im}{Re}\right) = \tan^{-1}\left(\frac{w/w_c}{(w/w_c)^2}\right) = \tan^{-1}\left(\frac{w_c}{w}\right) \quad w \rightarrow \infty, \Theta(w) \rightarrow 0$$

$$w \rightarrow 0, \Theta(w) \rightarrow \frac{\pi}{2}$$

RLC

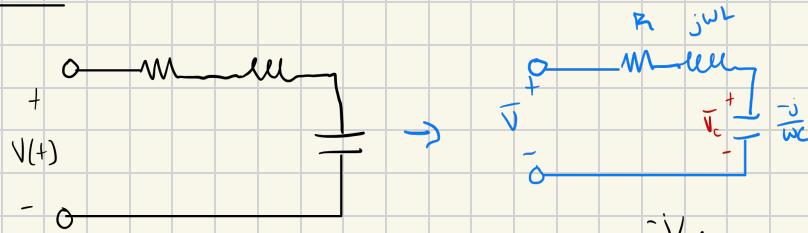

$$H(w) = \frac{-j/w_c}{R + jwL - j/w_c} \quad * \text{Band Pass Filter} *$$

More Schuh lectures:

- LTI system response to cosinusoids & Multi frequency inputs

Ex]

$$\frac{d^2y}{dt^2} + 4 \frac{dy}{dt} + 4y = \frac{df}{dt}$$

Assuming $f(t) = F_p \cos(\omega t)$

$$\bar{F} = (F_p e^{j\phi}) e^{j\omega t}$$

$$\begin{aligned}\frac{d\bar{F}}{dt} &= j\omega \underbrace{\bar{F}}_{\bar{F}} e^{j\phi} e^{j\omega t} \\ &= j\omega \bar{F}\end{aligned}$$

phasor's

$$(j\omega)^2 \bar{Y} + j4\omega \bar{Y} + 4\bar{Y} = j\omega \bar{F}$$

$$\bar{Y}(4 - \omega^2 + j4\omega) = j\omega \bar{F}$$

$$\bar{Y} = \underbrace{\left(\frac{j\omega}{4 - \omega^2 + j4\omega}\right)}_{H(\omega)} \bar{F}$$

$$H(\omega) = \frac{j\omega}{4 - \omega^2 + j4\omega}$$


$$H(\omega) = \frac{j\omega}{4 - \omega^2 + j4\omega} \cdot \frac{(4 - \omega^2 - j4\omega)}{(4 - \omega^2 - j4\omega)} = \frac{4\omega^2 + j\omega(4 - \omega^2)}{(4 - \omega^2)^2 + 16\omega^2}$$

$$|H(\omega)| = \sqrt{Re^2 \cdot Im^2} = \sqrt{\frac{(4\omega^2)^2 + \omega^2(4 - \omega^2)^2}{((4 - \omega^2)^2 + 16\omega^2)^2}} = \sqrt{\frac{16\omega^4 + \omega^2(4 - \omega^2)^2}{((4 - \omega^2)^2 + 16\omega^2)^2}} = \sqrt{\frac{\omega^2(16\omega^2 + (4 - \omega^2)^2)}{(16\omega^2 + (4 - \omega^2))^2}} = \sqrt{\frac{\omega^2}{16\omega^2 + (4 - \omega^2)^2}} = |H(\omega)|$$

$$\omega \rightarrow 0, |H(\omega)| \rightarrow 0$$

$$\omega \rightarrow \infty, |H(\omega)| \rightarrow 0$$

* Band Pass Filter *

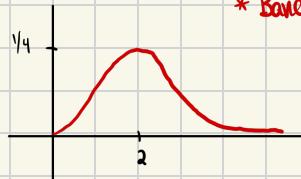

Decibels (dB)

$$|H(\omega)|_{dB} = 20 \log_{10} (|H(\omega)|)$$

$$\text{Low Pass Filter } |H(\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

$$\begin{aligned}|H(\omega)|_{dB} &= 20 \log_{10} \left([1 + \omega^2]^{-1/2} \right) \\ &= -10 \log_{10} (1 + \omega^2)\end{aligned}$$

$$\omega \rightarrow 0, |H(\omega)|_{dB} \rightarrow 0$$

$$\omega \rightarrow \infty, |H(\omega)|_{dB} \rightarrow -20 \log_{10} (\omega^2) \rightarrow -20 \log_{10} (\omega)$$

For every time ω increases by 10x

$|H(\omega)|$ decreases by 20 dB



High Pass Filter


Assume $|H(\omega)| = \sqrt{\frac{\omega^2}{1+\omega^2}}$

$$\begin{aligned} |H(\omega)|_{dB} &= 20 \log_{10} \left(\left[\frac{\omega^2}{1+\omega^2} \right]^{1/2} \right) \\ &= 10 \log_{10} \left(\frac{\omega^2}{1+\omega^2} \right) \\ &= 10 \left(\log_{10} (\omega^2) - \log_{10} (1+\omega^2) \right) \end{aligned}$$

$$\begin{aligned} \omega \rightarrow \infty, |H(\omega)|_{dB} &\rightarrow 10(\log(\omega^2) - \log(\omega^2)) \rightarrow 0 \\ \omega \rightarrow 0, |H(\omega)|_{dB} &\rightarrow 10(\log(\omega^2) - \log(1)) \rightarrow 10\log(\omega^2) \rightarrow 20\log_{10}(\omega) \end{aligned}$$



Multiple Frequencies

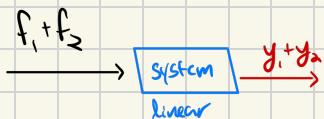

$$\tilde{F}_1 = F_{p_1} e^{j\phi} e^{j\omega_1 t}$$

$$\tilde{Y}_1 = |H(\omega)| F_{p_1} e^{j\phi} e^{j\omega_1 t} e^{j\theta(\omega)}$$

$$\tilde{F}_2 = F_{p_2} e^{j\phi} e^{j\omega_2 t}$$

$$\tilde{Y}_2 = |H(\omega)| F_{p_2} e^{j\phi} e^{j\omega_2 t} e^{j\theta(\omega)}$$

$$Y = Y_1 + Y_2$$



$$\text{Ex)} \quad H(\omega) = \frac{1}{1+j\omega} = \frac{1-j\omega}{1+\omega^2} \rightarrow |H(\omega)| = \frac{1}{\sqrt{1+\omega^2}} \rightarrow \Theta(\omega) = \tan^{-1}(-\omega)$$

Let $f(t) = 1\cos(t) + 0.1\cos(10t) + 0.01\cos(100t)$


ω	F	$ H(\omega) $	$\Theta(\omega_c)$
1	1	$\frac{\sqrt{2}}{2} \approx 0.707$	$\tan^{-1}(1) = -45^\circ = -\frac{\pi}{4}$
10	0.1	$\frac{1}{\sqrt{101}} \approx 0.1$	$\tan^{-1}(10) = -84.29^\circ$
100	0.1	$\frac{1}{\sqrt{10001}} \approx 0.03$	$\tan^{-1}(100) = -89.43^\circ$

$$y(t) = 0.7(1)\cos(t - 45^\circ) + 0.1(0.1)\cos(10t - 84.29^\circ) + 0.03(0.01)\cos(100t - 89.43^\circ)$$

Periodic Signals

$\exists f(t) = f(t-t_0)$
 $t \neq 0, f(t)$ is periodic

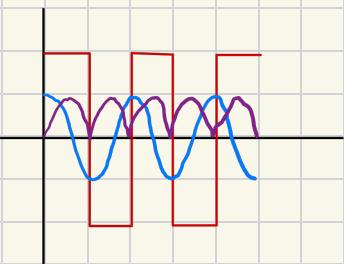KE integers *periodic functions repeat in time*
 $f(t) = f(t-kt_0)$



T : smallest t_0 for which a signal repeats

$$\text{Ex)} \cos(t) \rightarrow T = 2\pi \text{ sec}$$

$$\cos(3t) \rightarrow T = \frac{2\pi}{\omega} \rightarrow T = \frac{2\pi}{3} \text{ sec}$$

$$f(t) = \cos(2t) + \cos(3t)$$

$$T_1 = \frac{2\pi}{\omega} = \pi \text{ sec} \quad T_2 = \frac{2\pi}{3} \text{ sec}$$

Overall: LCM $T_1 + T_2$

$$T_{\text{tot}} = 2\pi$$

$$T_1(2) = 2\pi$$

$$T_2(3) = 2\pi$$

Test for if sum of periodic signals is periodic

$\frac{\omega_1}{\omega_2}$ = rational Number (Fraction) \rightarrow will be periodic

Ex) $\omega_1 = 2, \omega_2 = 3$

$$\frac{\omega_1}{\omega_2} = \frac{2}{3} \quad \text{periodic}$$

Ex) $f(t) = \cos(\omega t) + \cos(\sqrt{2}\omega t)$

$$\omega_1 = 1 \quad \omega_2 = \sqrt{2}$$

$$\frac{\omega_1}{\omega_2} = \frac{1}{\sqrt{2}} \quad \text{non periodic}$$

Fourier Series

* Periodic functions can be approximated by sums of sines + cosines *

Complex Exponential Form ($e^{j\theta} = \cos\theta + j\sin\theta$)

$$f(t) = \sum_{k=-\infty}^{\infty} F_k e^{jk\omega_0 t} \quad \begin{matrix} \text{complex #} \\ \text{fundamental frequency} \end{matrix}$$
$$F_k = \text{integers} \quad \omega_0 = \frac{2\pi}{T} \quad k\omega_0 = k^{\text{th}} \text{ harmonic}$$

$F_k \in \mathbb{C}$ ($F_k \in \text{complex #}'s$)

Trigonometric Form

$$F_k e^{jk\omega_0 t} = F_k \cos(k\omega_0 t) + j F_k \sin(k\omega_0 t)$$

$$f(t) = \sum_{k=-\infty}^{\infty} F_k \cos(k\omega_0 t) + j F_k \sin(k\omega_0 t)$$

$$k=0 : F_0 \cos(0) + j F_0 \sin(0)$$

$$= F_0$$

$$f(t) = F_0 + \sum_{k=1}^{\infty} F_k \cos(k\omega_0 t) + j F_k \sin(k\omega_0 t) + F_{-k} \cos(-k\omega_0 t) + j F_{-k} \sin(-k\omega_0 t)$$

Since cos is an even function, positives and negatives are equal
and sin functions are odd: $\sin(-t) = -\sin(t)$

$$= F_0 + \sum_{k=1}^{\infty} (F_k + F_{-k}) \cos(k\omega_0 t) + j(F_k - F_{-k}) \sin(k\omega_0 t)$$

We can define:

$$a_0 = 2F_0$$

$$a_k = F_k + F_{-k}$$

$$b_k = j(F_k - F_{-k})$$

$$f(t) = \frac{a_0}{2} + \sum_{k=1}^{\infty} a_k \cos(k\omega_0 t) + b_k \sin(k\omega_0 t)$$

Compact Form (non-complex functions only)


$$c_0 = 2|F_0|$$

$$f(t) = \frac{c_0}{2} + \sum_{k=1}^{\infty} c_k \cos(k\omega_0 t + \theta_k)$$

$$c_k = 2|F_k|$$

$$\theta_k = \tan^{-1}\left(\frac{\text{Im}(F_k)}{\text{Re}(F_k)}\right)$$


Ex] $f(t) = |\sin(t)|$

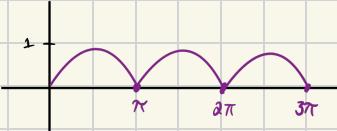

$$T = \pi$$

$$\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{\pi} = 2 \frac{\text{rad}}{\text{sec}}$$

Ex)

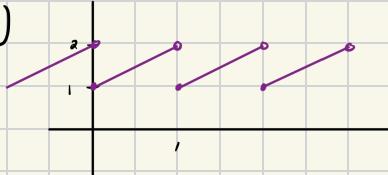

$$T = 1 \text{ sec}$$

$$\omega_0 = \frac{2\pi}{T} \Rightarrow \omega_0 = 2\pi \text{ rad/sec}$$

Fourier Series & its forms

1) Sinusoidal input (Frequency Response)


2) Multiple Sinusoidal inputs (Frequency Response + Linearity)

3) Periodic Signals

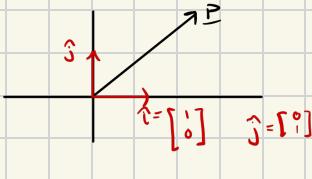4) Fourier Series - periodic signal written as sines + cosines

Linear Algebra

Basis: $[\hat{i}, \hat{j}]$ ← orthogonal (no mixing of information)



$$a = \frac{\underline{P} \cdot \hat{i}}{|\hat{i}|^2} \quad b = \frac{\underline{P} \cdot \hat{j}}{|\hat{j}|^2}$$
$$\underline{P} = a\hat{i} + b\hat{j}$$

* functions are vectors in ∞ dimensional space

Inner Product

Extension of the dot product to ∞ -dimensional spaces

$$\langle f(t), g(t) \rangle = \int_0^T f(t) g^*(t) dt$$

inner product of
f(t) and g(t)

$\langle f(t), g(t) \rangle = 0 \rightarrow$ the functions are orthogonal

Ex 1 $e^{j\omega_0 t}, e^{-j\omega_0 t} \rightarrow$ Find inner product

$$\begin{aligned} \langle e^{j\omega_0 t}, e^{-j\omega_0 t} \rangle &= \int_0^T e^{j\omega_0 t} e^{-j\omega_0 t} dt \\ &= \int_0^T 1 dt \\ &= \int_0^T \cos(\omega_0 t) - j \sin(\omega_0 t) dt \\ &= \left[\frac{1}{\omega_0} \sin(\omega_0 t) + j \frac{1}{\omega_0} \cos(\omega_0 t) \right]_0^T \end{aligned}$$

$$\begin{aligned}
 &= \frac{1}{w_0} (\sin(w_0 T) - \sin(0) + j [\cos(w_0 T) - \cos(0)]) \\
 w_0 = \frac{2\pi}{T} \\
 w_0 T = 2\pi \\
 &= \frac{1}{w_0} (0 + j(1-1)) = \frac{1}{w_0} (0 + j0) = 0
 \end{aligned}$$

Orthogonal

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

$$\langle f(t), e^{jm\omega_0 t} \rangle = \int_0^T \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} e^{jm\omega_0 t} dt$$

which ever F_n we care about

$$= \sum_{n=-\infty}^{\infty} F_n \int_0^T e^{j\omega_0(n-m)t} dt$$

$$\begin{aligned}
 &\int_0^T e^{j\omega_0(n-m)t} dt = 0 & n \neq m \\
 &\int_0^T e^{j\omega_0(n-n)t} dt = \int_0^T e^{j\omega_0 0 t} dt & n = m \\
 &= \int_0^T dt = T
 \end{aligned}$$

$$\langle f(t), e^{jm\omega_0 t} \rangle = T F_m$$

\star

$F_m = \frac{1}{T} \int_0^T f(t) e^{-jm\omega_0 t} dt$

\star

Ex) $f(t) = \cos^2(t) = \frac{1}{2}(1 + \cos(2t))$

$$= \frac{1}{2} + \frac{1}{2} \cos(2t)$$

① Start with finding F_0

$$\begin{aligned}
 F_0 &= \frac{1}{T} \int_0^T f(t) e^{j0t} dt = \frac{1}{T} \int_0^T f(t) dt \quad \text{Average value of } f(t) \\
 &= \frac{1}{\pi} \int_0^\pi \left(\frac{1}{2} + \frac{1}{2} \cos(2t) \right) dt = \frac{1}{\pi} \left[\frac{1}{2}t + \frac{1}{2} \left(\frac{1}{2} \sin(2t) \right) \right]_0^\pi \\
 &= \frac{1}{\pi} \left[\frac{1}{2}(\pi - 0) + \frac{1}{4}(\sin(2\pi) - \sin(0)) \right] \\
 &= \frac{1}{\pi} \left[\frac{\pi}{2} \right] \Rightarrow \boxed{F_0 = \frac{1}{2}}
 \end{aligned}$$

② Find F_n ($n \neq 0$)

$$F_n = \frac{1}{\pi} \int_0^{\pi} \cos^2(t) e^{jnw_0 t} dt \Rightarrow \frac{1}{\pi} \int_0^{\pi} \cos^2(t) e^{j2at} dt \Rightarrow \frac{1}{\pi} \int_0^{\pi} \left(\frac{1}{2} + \frac{1}{2} \cos(2at) \right) (\cos(2at) - j \sin(2at)) dt \\ = \frac{1}{\pi} \int_0^{\pi} \left(\frac{1}{2} \cos(2at) - j \frac{1}{2} \sin(2at) + \frac{1}{2} \cos(2at) \cos(2at) - j \frac{1}{2} \cos(2at) \sin(2at) \right) dt \\ = 0 \quad (\text{after integration})$$

$$\cos(A)\cos(B) = \frac{1}{2}(\cos(A+B) + \cos(A-B))$$

$$\cos(A)\sin(B) = \frac{1}{2}(\sin(A+B) + \sin(A-B))$$

$$= \frac{1}{\pi} \left(\int_0^{\pi} \left(\cos(a(1+n)t) + \cos(a(1-n)t) \right) + \frac{1}{2} \left(\sin(a(1+n)t) + \sin(a(1-n)t) \right) dt \right)$$

only 2 values of n where

the integral $\neq 0$

$$n=-1$$

$$n=1$$

$$\Rightarrow \frac{1}{\pi} \int_0^{\pi} \frac{1}{4}(1) dt \Rightarrow \frac{1}{\pi} \left(\frac{1}{4}t \right) \Big|_0^{\pi} = \frac{1}{4}$$

$$\Rightarrow \frac{1}{\pi} \int_0^{\pi} \frac{1}{4}(1) dt \Rightarrow \frac{1}{\pi} \left(\frac{1}{4}t \right) \Big|_0^{\pi} = \frac{1}{4}$$

In terms of complex exp.

$$F_n = \frac{1}{2} \quad F_1 = \frac{1}{4}$$

$$f(t) = \frac{1}{2} + \frac{1}{4} e^{j2at} + \frac{1}{4} e^{-j2at}$$

Craig Form:

$$a_0 = 2F_0$$

$$a_0 = 2\left(\frac{1}{2}\right) = 1$$

$$a_n = F_n + F_{-n}$$


$$a_1 = \frac{1}{4} + \frac{1}{4} = \frac{1}{2}$$

$$b_n = F_n - F_{-n}$$

$$b_1 = \frac{1}{4} - \frac{1}{4} = 0$$

$$f(t) = \frac{1}{2} + \frac{1}{2} \cos(2at) \quad \checkmark$$

Running through examples of Fourier

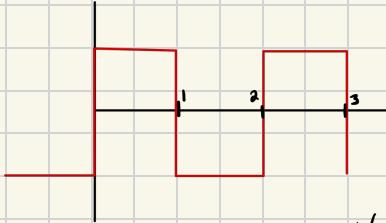

$$T = 2\pi$$

$$\omega_0 = \frac{2\pi}{T} = \pi$$

$$F_0 = \frac{1}{T} \int_0^T f(t) dt \Rightarrow$$

$$\frac{1}{2} \int_0^2 f(t) dt$$

must break this up
because values are different
at diff locations

$$= \frac{1}{2} \left(\int_0^1 1 dt + \int_1^2 -1 dt \right)$$

$$= \frac{1}{2} (1|_0^1 - 1|_1^2) = \frac{1}{2} (1 - (2-1)) = 0 \quad F_0 = 0$$

$$F_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt = \frac{1}{2} \int_0^2 f(t) e^{-jn\pi t} dt = \frac{1}{2} \left(\int_0^1 e^{jn\pi t} dt + \int_1^2 -e^{jn\pi t} dt \right) = \frac{1}{2} \left(\frac{1}{jn\pi} e^{jn\pi t} \Big|_0^1 + (-1) \frac{1}{jn\pi} e^{jn\pi t} \Big|_1^2 \right)$$

$$\frac{1}{2} \left(\frac{1}{jn\pi} (e^{-jn\pi} - 1) - \frac{1}{jn\pi} (e^{-jn\pi} - e^{-jn\pi}) \right) = \frac{1}{2} \left(\frac{1}{jn\pi} (e^{-jn\pi} - 1) + \frac{1}{jn\pi} (e^{-jn\pi} - e^{jn\pi}) \right)$$

$$\frac{1}{2} \left(\frac{1}{jn\pi} (e^{-jn\pi} - 1) + \frac{1}{jn\pi} (e^{-jn\pi} - 1) \right) = \frac{1}{jn\pi} (e^{-jn\pi} - 1)$$

$$e^{jn\pi} = \cos(n\pi) - j\sin(n\pi)$$

$$n \in \mathbb{Z}$$

$$\frac{1}{jn\pi} ((-1)^n - 1)$$

$n:$ even $\Rightarrow F_n = 0$
 $n:$ odd $\Rightarrow F_n = \frac{-2}{jn\pi} \cdot \frac{1}{j} = \frac{-2}{n\pi}$

n	$\cos(n\pi)$
1	-1
2	1
3	-1

if n is odd: $\cos(n\pi) = -1$
 if n even: $\cos(n\pi) = 1$


$$\cos(n\pi) = (-1)^n$$

$$n: \text{even}, F_n = 0$$

$$n: \text{odd}, F_n = \frac{-2}{n\pi}$$

$$f(t) = 0 + \sum_{\substack{n=-\infty \\ n \neq 0 \\ n \text{ odd}}}^{\infty} \frac{-2}{n\pi} e^{jn\pi t}$$

Ex)

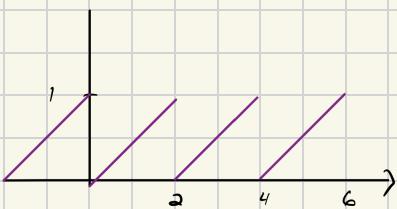

$$f(t) = \frac{t}{2} \quad 0 \leq t < 2$$

$$T = 2s$$

$$\omega_0 = \frac{2\pi}{2s} = \pi$$

① Find F_0

$$F_0 = \frac{1}{2} \int_0^2 \frac{t}{2} dt \Rightarrow \frac{1}{2} \left(\frac{t^2}{4} \right)_0^2 = \frac{1}{2} \left(\frac{4}{4} - 0 \right) = \frac{1}{2}$$

② Find F_n

$$F_n = \frac{1}{2} \int_0^2 \frac{t}{2} e^{j n \pi t} dt = \frac{1}{4} \int_0^2 t e^{j n \pi t} dt = \frac{1}{4} \left(\frac{t}{j n \pi} e^{-j n \pi t} \right)_0^2 + \underbrace{\int_0^2 \frac{1}{j n \pi} e^{-j n \pi t} dt}_0 = \frac{1}{4} \left(\frac{2}{j n \pi} e^{-j n \pi} - 0 \right) = \frac{1}{2} \left(\frac{1}{j n \pi} \right) e^{-j n \pi}$$

$\begin{aligned} \text{let } u = t & \quad v = \frac{1}{j n \pi} e^{j n \pi t} \\ du = dt & \quad dv = e^{j n \pi t} \end{aligned}$


$$\therefore \frac{1}{2} \left(\frac{1}{j n \pi} \right) = \frac{j}{2n\pi} = F_n$$

$$e^{j n \pi} = 1$$

$$f(t) = \frac{1}{2} + \sum_{n=0}^{\infty} \frac{j}{2n\pi} e^{j n \pi t}$$

Ex]

$$f(t) = |\sin(t)|$$

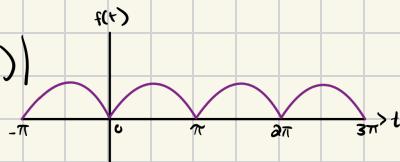

$$T = \pi s$$

$$\omega_0 = \frac{2\pi}{T} = \frac{2\pi}{\pi} = 2 \text{ rad/sec}$$

① Find F_0

$$\frac{1}{\pi} \int_0^\pi \sin(t) dt = \frac{1}{\pi} (-\cos(t)) \Big|_0^\pi = \frac{1}{\pi} (-(-1) + 1) = \frac{2}{\pi} = F_0$$

② Find F_n

$$F_n = \frac{1}{\pi} \int_0^\pi \sin(t) e^{-j n \pi t} dt = \frac{1}{\pi} \int_0^\pi \left(\frac{e^{jt} - e^{-jt}}{j} \right) e^{-j n \pi t} dt = \frac{1}{j n \pi} \int_0^\pi e^{jt} e^{-j n \pi t} - e^{-jt} e^{-j n \pi t} dt = \frac{1}{j n \pi} \int_0^\pi e^{j(1-n)t} - e^{-j(1+n)t} dt$$

$$F_n = \frac{2}{\pi} \left[\frac{1}{1-4n^2} \right]$$

$$f(t) = \frac{a}{\pi} + \sum_{\substack{n=-\infty \\ n \neq 0}}^{\infty} \frac{a}{\pi} \left(\frac{1}{1-4n^2} \right) e^{j2nt}$$

• Exponential Fourier Series

DC offset

$$\cdot \text{Let } f(t) = 1 + 2\sin(t) + \sin^2\left(\frac{\pi}{4}t\right)$$

Determine its exponential Fourier Series

Find signal must look like $\sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$

$$\sin^2(x) = \frac{1}{2}(1 - \cos(2x))$$

$$f(t) = 1 + 2\sin(t) + \frac{1}{2} - \frac{1}{2}\cos\left(\frac{\pi}{2}t\right) = \frac{3}{2} + 2\sin(t) - \frac{1}{2}\cos\left(\frac{\pi}{2}t\right)$$

$$= \frac{3}{2} + 2\left(\frac{e^{jt} - e^{-jt}}{2j}\right) - \frac{1}{2}\left(\frac{e^{j\frac{\pi}{2}t} + e^{-j\frac{\pi}{2}t}}{2}\right) =$$

$$\frac{3}{2} + \frac{1}{j}e^{jt} - \frac{1}{j}e^{-jt} - \frac{1}{4}e^{j\frac{\pi}{2}t} - \frac{1}{4}e^{-j\frac{\pi}{2}t} = f(t)$$


$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} = F_0 + F_1 e^{j\frac{\pi}{2}t} + F_{-1} e^{-j\frac{\pi}{2}t} + F_2 e^{jt} + F_{-2} e^{-jt} + F_3 e^{j\frac{\pi}{4}t} + F_{-3} e^{-j\frac{\pi}{4}t} + \dots + F_4 e^{j\frac{\pi}{2}t} + F_{-4} e^{-j\frac{\pi}{2}t} + \dots$$

• What if $f(t)$ is cosinusoidal or a complex exponential? Just match coefficients

• If not, but $f(t)$ is periodic, will use $\{e^{jn\omega_0 t}\}$ as a basis to project onto.

a is a projection of \vec{v} onto \vec{x}

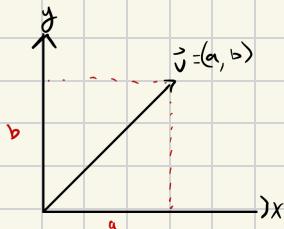b is a projection of \vec{v} onto \vec{y} .



$$F_n = \langle f(t), e^{jn\omega_0 t} \rangle = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

or $0 \rightarrow T$
or $-\frac{T}{2} \rightarrow \frac{T}{2}$

• $\{e^{jn\omega_0 t}\}$ is an orthonormal basis.

$$\langle e^{jn\omega_0 t}, e^{jm\omega_0 t} \rangle = \begin{cases} 1 & n=m \\ 0 & \text{else} \end{cases}$$

$$\begin{aligned} \langle e^{jn\omega_0 t}, e^{jm\omega_0 t} \rangle &= \frac{1}{T} \int_T e^{jn\omega_0 t} \cdot e^{-jm\omega_0 t} dt = \frac{1}{T} \int_T e^{j(n-m)\omega_0 t} dt = \\ &\stackrel{!}{=} \frac{e^{j(n-m)\omega_0 t}}{j(n-m)\omega_0} \Big|_0^T = \frac{1}{T} \frac{(e^{j(n-m)\omega_0 T} - 1)}{j(n-m)\omega_0} = \frac{1}{T} \left(\frac{(e^{j(n-m)2\pi} - 1)}{j(n-m)\omega_0} \right) = 0 \end{aligned}$$

if $n \neq m$:


if $n = m$:

$$\langle e^{jn\omega_0 t}, e^{jn\omega_0 t} \rangle = \frac{1}{T} \int_T e^{jn\omega_0 t} \cdot e^{jn\omega_0 t} dt = \frac{1}{T} \int_T dt = 1$$

Ex:

$$\text{Let } f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases}$$

have period = 2s

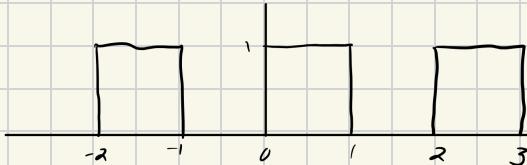

Determine exponential Fourier Series

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$


$$\begin{aligned} F_n &= \frac{1}{T} \int_T f(t) e^{-jn\omega_0 t} dt = \frac{1}{2} \left[\int_0^1 (1) e^{-jn\omega_0 t} dt + \int_1^2 (0) e^{-jn\omega_0 t} dt \right] \quad (n \text{ is an integer}) \\ &= \frac{1}{2} \left. \frac{e^{-jn\omega_0 t}}{-jn\omega_0} \right|_0^1 = \frac{-1}{2j\pi n} (e^{-jn\pi} - 1) \end{aligned}$$



$n \neq 0$

$$F_0 = \frac{1}{T} \int_T f(t) e^{-j0\omega_0 t} dt = \frac{1}{2} \int_T f(t) dt = \frac{1}{2} \leftarrow \text{average of } f(t)$$

DC term

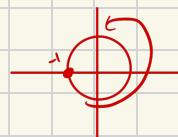

$$F_n = \begin{cases} \frac{-1}{j n 2\pi} (-1 - 1) = 0 & n \text{ even} \\ \frac{-1}{j n 2\pi} (-1 + 1) = \frac{1}{j n \pi} & n \text{ is odd} \\ \frac{1}{2} & n = 0 \end{cases}$$

$$f(t) = \frac{1}{2} + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \frac{1}{j n \pi} e^{j n \pi t}$$

Terminology:

F_0 is the DC component

F_1 corresponds to the fundamental frequency term


F_n corresponds to the n^{th} harmonic

- Existence of Fourier Series representation


$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

$$f(t) = F_0 + F_1 e^{j\omega_0 t} + F_1 e^{-j\omega_0 t} + \dots$$

① $f(t) = |\sin(t)|$

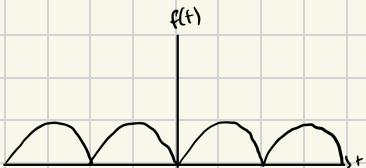

②

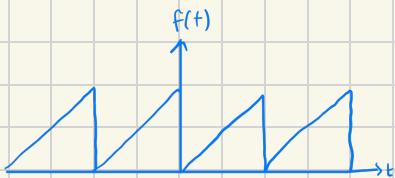

Note: With Fourier transform, the transform does not know where discontinuities exist. This is known as Gibbs phenomenon.

- For existence of the Fourier series, we need:

① Absolute integrability of $f(t)$ over period T

$$\int_T |f(t)| dt < \infty \text{ has to be finite}$$

② Plotability

- over one period*
- {
 - Finite # of maxima and minima
 - Finite number of finite discontinuities
(series converges to midpoint at discontinuity)

• Fourier Series Forms

- Exponential Fourier Series

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

- Trigonometric

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

$$a_0 = 2F_0 \quad a_n = F_n + E_n \quad b_n = j(F_n - E_n)$$

$$F_0 = \frac{a_0}{2} \quad F_n = \frac{a_n + jb_n}{2} \quad E_n = \frac{a_n - jb_n}{2}$$

- Compact Fourier Series, for real valued functions only

$$f(t) = \frac{c_0}{2} + \sum_{n=1}^{\infty} c_n (\cos(n\omega_0 t + \theta_n))$$

$$C_0 = 2F_0 \quad C_n = 2|F_n| \quad \Theta_n = \angle F_n$$

$$F_0 = \frac{c_0}{2} \quad F_n = \frac{c_n}{2}$$

$$f(t) = \frac{1}{2} + \sum_{n=1}^{\infty} \frac{1}{jn\pi} e^{jn\pi t} \rightarrow \text{trig FS of } f(t)$$

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

$$= \frac{1}{2} + \sum_{n=1}^{\infty} \left(\frac{1}{jn\pi} e^{jn\pi t} + \frac{1}{j(n\pi)} e^{-jn\pi t} \right) =$$

$$= \frac{1}{2} + \sum_{n=1}^{\infty} \frac{1}{n\pi} \left(\frac{e^{jn\pi t} - e^{-jn\pi t}}{j} \right) =$$

$$= \frac{1}{2} + \sum_{n=1}^{\infty} \frac{a}{n\pi} \left(\frac{e^{jn\pi t} - e^{-jn\pi t}}{j2} \right) =$$

$$= \frac{1}{2} + \sum_{n=1}^{\infty} \frac{a}{n\pi} \sin(n\pi t) \quad \longrightarrow \quad a_n = \begin{cases} 1 & n=0 \\ 0 & \text{else} \end{cases}$$

$$b_n = \begin{cases} 0 & n=\text{even} \\ \frac{a}{n\pi} & n=\text{odd} \end{cases}$$

Exponential F.S. \rightarrow compact F.S.

$$F_n = \begin{cases} \frac{1}{2} & n=0 \\ \frac{1}{jn\pi} & n \text{ odd} \\ 0 & \text{else} \end{cases}$$

$$C_0 = 2F_0 = 1$$
$$C_n = 2|F_n| = 2\left|\frac{1}{jn\pi}\right|$$

$$= \begin{cases} \frac{2}{n\pi} & n \text{ odd} \\ 0 & \text{even, } n \neq 0 \end{cases}$$

$$\Theta_n = LF_n = \begin{cases} -\pi/2 & n \text{ odd} \\ 0 & \text{else} \end{cases}$$

$$f(t) = \frac{1}{2} + \sum_{\substack{n=1 \\ n \text{ odd}}}^{\infty} \frac{2}{n\pi} \cos(n\pi t - \frac{\pi}{2})$$

- Properties of Exp. F.S.

Consider

$$g(t) = \begin{cases} 2 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases} \quad \text{With period 2s, and } f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases} = \frac{1}{2} + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \frac{1}{jn\pi} e^{jn\pi t}$$

What are the exponential Fourier series coefficients G_n

$$g(t) = 2f(t)$$

$$2(f(t)) = 2\left(\frac{1}{2} + \sum_{n=-\infty}^{\infty} \frac{1}{jn\pi} e^{jn\pi t}\right)$$

(Amplitude Scaling property)
only the amplitude is affected

Consider:

$$f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases} = \frac{1}{2} + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \frac{1}{jn\pi} e^{jn\pi t}$$

and

$$h(t) = \begin{cases} 0 & t \in [0, 1) \\ 1 & t \in [1, 2) \end{cases}$$

$$h(t) = f(t-1) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0(t-1)} = \sum_{n=-\infty}^{\infty} F_n e^{-jn\omega_0} \cdot e^{jn\omega_0 t}$$

$$h(t) = \sum_{n=-\infty}^{\infty} H_n e^{jn\omega_0 t}$$

$$h(t) = \sum_{n=-\infty}^{\infty} H_n e^{jn\omega_0 t} [v]$$

$$H_n = F_n e^{-jn\omega_0 t_0}$$

$$h(t) = f(t-1) \Rightarrow H_n = F_n e^{-jn\omega_0} = F_n e^{-jn\pi}$$

• Time shift property:

$$h(t) = f(t-t_0)$$

$$H_n = F_n e^{-jn\omega_0 t_0}$$

$$F_n = \begin{cases} \frac{1}{jn\pi} & n \text{ odd} \\ \frac{1}{2} & n=0 \\ 0 & n \text{ even} \\ n \neq 0 \end{cases}$$


$$H_n = \begin{cases} \frac{1}{jn\pi} (-1) = \frac{-1}{jn\pi} & n \text{ odd} \\ \frac{1}{2} (1) & n=0 \\ 0 & n \text{ even} \\ n \neq 0 \end{cases}$$

• Addition Property: If $f(t)$ and $h(t)$ have same w_0 , then

$$X(t) = f(t) + h(t) ; X_n = F_n + H_n$$

Let:
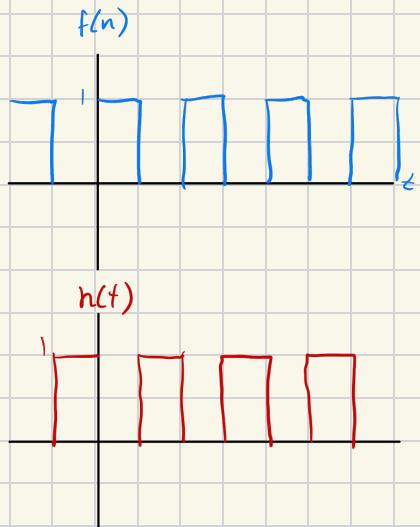
$$x(t) = \begin{cases} 1 & t \in [0, 1) \\ -1 & t \in [1, 2) \end{cases} \quad T=2s$$



Recall:

$$g(t) = \begin{cases} 2 & t \in [0, 1) \\ 0 & t \in [1, 2) \end{cases}$$

$$G_n = \begin{cases} \frac{2}{j n \pi} & n \text{ odd} \\ 1 & n = 0 \\ 0 & n \text{ even} \neq 0 \end{cases}$$

$$X(t) = \begin{cases} 1 & t \in [0, 1) \\ -1 & t \in [1, 2) \end{cases} \quad T=2s$$

• Recall that in an LTI system

$$e^{j\omega t} \rightarrow \boxed{\text{LTI}} \rightarrow H(\omega) e^{j\omega t}$$

$$\cos(\omega t + \theta) \rightarrow \boxed{\text{LTI}}_{H(\omega)} \rightarrow |H(\omega)| \cos(\omega t + \theta + \angle H(\omega))$$

so that

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} \rightarrow \boxed{\text{LTI}} \rightarrow y(t) = \sum_{n=-\infty}^{\infty} H(n\omega_0) F_n e^{jn\omega_0 t}$$

or

$$f(t) = \frac{C_0}{2} + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \theta_n) \rightarrow \boxed{\text{LTI}} \rightarrow y(t) = H(0) \frac{C_0}{2} + \sum_{n=1}^{\infty} |H(n\omega_0)| C_n \cos(n\omega_0 t + \theta_n + \angle H(n\omega_0))$$

Ex:

$$f(t) = \begin{cases} 1 & t \in [0, 1) \\ 0 & t \in [1, 2] \end{cases} = \frac{1}{2} + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \frac{1}{jn\pi} e^{jn\pi t} \quad \omega_0 = \pi \text{ rad}$$

Let

$$H(\omega) = \frac{1}{2+j\omega} \quad |H(\omega)| = \sqrt{4+\omega^2} \quad \angle H(\omega) = -\tan^{-1}\left(\frac{\omega}{2}\right)$$

Determine the steady state output, $y(t)$

$$y(t) = \underbrace{\frac{1}{2} H(0)}_{= \frac{1}{2}} + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} H(n\omega_0) \frac{1}{jn\pi} e^{jn\pi t} =$$


$$\frac{1}{2} \left(\frac{1}{2} \right) + \sum_{\substack{n=-\infty \\ n \text{ odd}}}^{\infty} \left(\frac{1}{2+jn\pi} \right) \frac{1}{jn\pi} e^{jn\pi t}$$

Chapter 7

Fourier Transform and LTI System Response to Energy Signals

Recall that in an LTI system, the output to a periodic input is also periodic.

What if $f(t)$ is not periodic
aperiodic

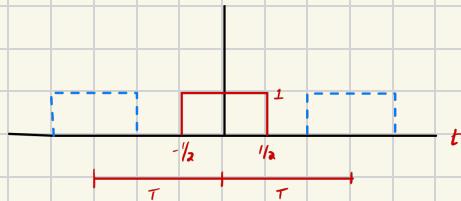

Fourier Transform

$$\begin{aligned}
 f_T(t) &= \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} \left(\frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(s) e^{-jnw_0 s} ds \right) e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} \frac{\omega_0}{2\pi} \int_{-\pi/\omega_0}^{\pi/\omega_0} f(s) e^{-jnw_0 s} ds \cdot e^{jn\omega_0 t} = \\
 &= \frac{1}{2\pi} \sum_{n=-\infty}^{\infty} \left(\int_{-\pi/\omega_0}^{\pi/\omega_0} f(s) e^{-jnw_0 s} ds \right) e^{jn\omega_0 t} \cdot \omega_0 = \\
 &\quad \text{define as } F(n\omega_0) \\
 &= \frac{1}{2\pi} \sum_{n=-\infty}^{\infty} F(n\omega_0) e^{jn\omega_0 t} \cdot \omega_0 \xrightarrow{\omega_0 \rightarrow 0} \\
 &\rightarrow \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega = f(t)
 \end{aligned}$$

Fourier Transform Pairs

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad \in \mathcal{C} \quad \text{Fourier Transform}$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega \quad \text{inverse Fourier Transform}$$

time domain

$$f(t) \leftrightarrow F(\omega)$$

Unique transform pair

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega \rightarrow \boxed{H(\omega)}$$

$$y(t) = \frac{1}{2\pi} \dots$$


We can represent any function in terms of a Fourier Transform if $f(t)$ is absolutely integrable

i.e.

$$\int_{-\infty}^{\infty} |f(t)| dt < \infty$$





Ex)

$$f(t) = \begin{cases} 1 & |t| < \frac{1}{2} \\ 0 & \text{else} \end{cases} = \text{rect}(t)$$

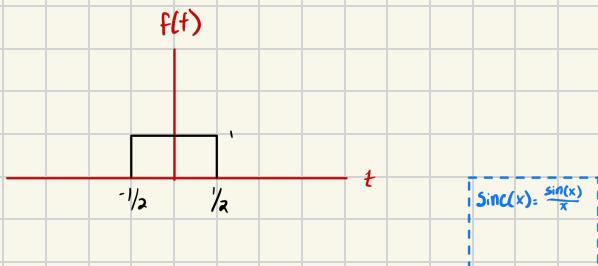

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt = \int_{-1/2}^{1/2} (1) e^{-j\omega t} dt =$$

$$= \frac{e^{-j\omega t}}{-j\omega} \Big|_{-1/2}^{1/2} = \frac{e^{-j\omega(1/2)}}{-j\omega} - \frac{e^{-j\omega(-1/2)}}{-j\omega} = \left(\frac{e^{j\frac{\omega}{2}} - e^{-j\frac{\omega}{2}}}{j\omega} \right) \frac{1}{2} = \frac{2\sin(\frac{\omega}{2})}{\omega} = \frac{\sin(\frac{\omega}{2})}{\frac{\omega}{2}} = \text{sinc}(\frac{\omega}{2})$$

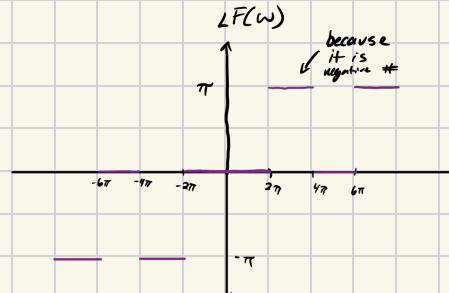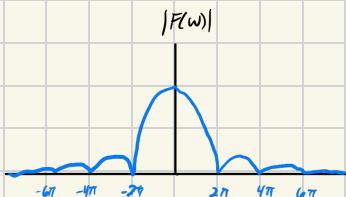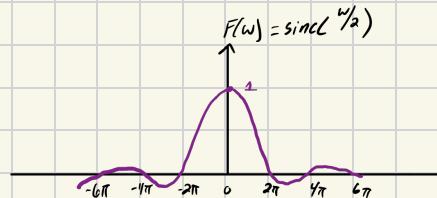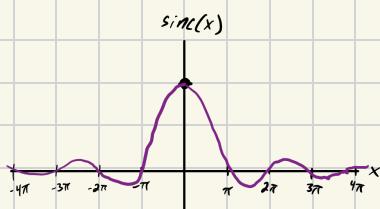

Doing Prof Schuh's lectures

$$P_{avg} = \frac{1}{T} \int_0^T |f(t)|^2 dt \quad \text{st. } |f(t)|^2 = f(t) * f^*(t)$$

$$= \left(\sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} \right) \left(\sum_{m=-\infty}^{\infty} F_m^* e^{-jm\omega_0 t} \right)$$

$$= \sum_{n=-\infty}^{\infty} \sum_{m=-\infty}^{\infty} F_n F_m^* e^{j(n-m)\omega_0 t}$$

$$P_{avg} = \frac{1}{T} \int_0^T \sum_{n=-\infty}^{\infty} \sum_{m=-\infty}^{\infty} F_n F_m^* e^{j(n-m)\omega_0 t} dt$$

$$= \frac{1}{T} \sum_{n=-\infty}^{\infty} \sum_{m=-\infty}^{\infty} F_n F_m^* \int_0^T e^{j(n-m)\omega_0 t} dt \quad \leftarrow n \text{ must }= m, \text{ because otherwise you're integrating over sines + cosines which would be zero.}$$

$$= \frac{1}{T} \sum_{n=-\infty}^{\infty} F_n F_n^*$$

$$= \sum_{n=-\infty}^{\infty} |F_n|^2$$

Real Valued $f(t)$

$$C_0 = 2|F_0| \Rightarrow |F_0| = \frac{C_0}{2}$$

$$C_n = 2|F_n| \Rightarrow |F_n| = \frac{C_n}{2}$$

\downarrow changing bounds

$$P_{avg} = |F_0|^2 + \sum_{n=1}^{\infty} |F_n|^2 + |F_n|^2$$

$$= |F_0|^2 + 2 \sum_{n=1}^{\infty} |F_n|^2$$

$$= \left(\frac{C_0}{2}\right)^2 + 2 \sum_{n=1}^{\infty} \left(\frac{C_n}{2}\right)^2$$

$$P_{avg} = \frac{C_0^2}{4} + \sum_{n=1}^{\infty} \frac{C_n^2}{2}$$

\uparrow DC power \nwarrow similar to $P_{ac} = \frac{1}{2} V_p^2$

Distortion

$$\text{Non-linear system: } y(t) = A f(t) + E f(t)^2 \quad E \ll 1$$

Let's say $f(t) = \cos(\omega t)$

$$y(t) = A \cos(\omega t) + E \cos^2(\omega t)$$

$$= A \cos(\omega t) + E \left(\frac{1}{2} + \frac{1}{2} \cos(2\omega t) \right)$$

$$= \frac{1}{2} + A \cos(\omega t) + \frac{E}{2} \cos(2\omega t)$$


1st harmonic power: $\frac{1}{2} A^2$

and Harmonic Distortion: $\frac{\frac{E}{2}}{\frac{1}{2} A^2} = \frac{E^2}{A^2}$

2nd harmonic power: $\frac{E^2}{8}$

Total Harmonic Distortion
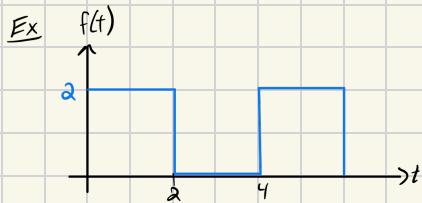
$$THD = \frac{\sum_{n=2}^{\infty} \frac{1}{2} C_n^2}{\frac{1}{2} C_1^2} = \frac{\sum_{n=2}^{\infty} C_n^2}{C_1^2}$$



$$\begin{aligned} P_{avg} &= \frac{1}{4} \int_0^4 f(t)^2 dt = \frac{1}{4} \left(\int_0^2 a^2 dt + \int_2^4 0^2 dt \right) \\ &= \frac{1}{4} \int_0^2 a^2 dt \\ &= t \Big|_0^2 \\ &= 2a^2 \end{aligned}$$

$$f(t) = 1 + \sum_{n=1}^{\infty} \frac{4}{n\pi} \sin\left(\frac{n\pi t}{2}\right)$$

$$P_1 = \frac{1}{2} C_1^2 = \frac{1}{2} \left(\frac{4}{\pi}\right)^2 = \frac{16}{a^2 \pi^2} = \frac{8}{\pi^2} = 0.8106W$$

$$P_{2-a} = \sum_{n=2}^{\infty} \frac{1}{2} C_n^2 \approx 0.1878W$$

$$THD = \frac{P_{2-a}}{P_1} = \frac{0.1878}{0.8106} = 23.17\%$$

$$H(j\omega) = \frac{1}{1+j\omega} \Rightarrow |H(j\omega)| = \frac{1}{\sqrt{1+\omega^2}}$$

$$y(t) = \underbrace{|H(j\omega)|}_{Y_0} \underbrace{(1 + \sum_{n=1}^{\infty} |H(j\frac{n\pi}{2})| \frac{4}{n\pi} \sin(\frac{n\pi t}{2} + \phi))}_{Y_n}$$

$$Y_n = \frac{4}{n\pi} \left(\frac{1}{\sqrt{1+(\frac{n\pi}{2})^2}} \right) \rightarrow Y_0 = 2$$

$$P_{avg} = \frac{Y_0^2}{4} + \sum_{n=1}^{\infty} \frac{1}{2} Y_n^2 = 1.238W$$

$$P_1 = \frac{1}{2} Y_0^2 \approx 0.2538W$$

$$P_{2-a} = \sum_{n=2}^{\infty} \frac{1}{2} Y_n^2 = 0.00468W$$

$$THD = \frac{P_{2-a}}{P_1} \Rightarrow 1.84\%$$

Review of periodic signals

$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t}$$

$$\omega_0 = \frac{2\pi}{T}$$

$$F_n \rightarrow H(\omega) \rightarrow Y_n = H(n\omega_0) F_n$$

* What if we are no longer periodic *

* Fourier Transform *

Assume $f(t) = \sum_{n=-\infty}^{\infty} F_n e^{jn\omega_0 t} \Rightarrow F_n = F(n\omega_0)$ $\hat{F}(n\omega_0) = F(n\omega_0)$

$$\begin{aligned} f(t) &= \sum_{n=-\infty}^{\infty} \frac{\omega_0}{2\pi} \hat{F}(n\omega_0) e^{jn\omega_0 t} \\ \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) e^{-j\omega_0 t} dt &= \sum_{n=-\infty}^{\infty} \frac{\omega_0}{2\pi} \hat{F}(n\omega_0) \int_{-\frac{T}{2}}^{\frac{T}{2}} e^{j(n-m)\omega_0 t} dt \\ &= \frac{\omega_0}{2\pi} \hat{F}(n\omega_0) T \quad \text{since it's like } \int_{-\infty}^{\infty} e^{j(n-m)\omega_0 t} dt = 0 \\ \hat{F}(n\omega_0) &= \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) e^{-j\omega_0 t} dt \end{aligned}$$

For nonperiodic signals, $T \rightarrow \infty$, $\omega_0 \rightarrow 0$

$$m\omega_0 \Rightarrow m \dots -2, -1, 0, 1, 2, \dots$$

$$-\infty \leq m \leq \infty$$

$$\hat{F}(w) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad \text{Fourier Transform} \star$$

$m\omega_0 \rightarrow \omega$
discrete \uparrow continuous

standard notation:


$$F(w) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt = \text{forward Fourier Transform}$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j\omega t} dw = \text{inverse Fourier Transform}$$

Fourier Transform


is essentially converting from time domain to frequency domain

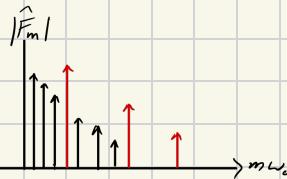Fourier Transform is the combination of sines and cosines of all possible frequencies for aperiodic signals



Ex] Unit step function
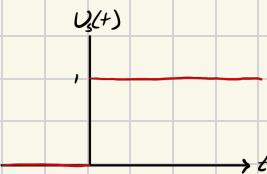
$$U_s(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



$$f(t) = e^{-t} U_s(t)$$

$$\begin{aligned} F(\omega) &= \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt = \int_{-\infty}^0 f(t) e^{-j\omega t} dt + \int_0^{\infty} f(t) e^{-j\omega t} dt \\ &= \int_0^{\infty} e^{-t} e^{-j\omega t} dt \\ &= \int_0^{\infty} e^{-(1+j\omega)t} dt \\ &= \left[\frac{e^{-(1+j\omega)t}}{-1-j\omega} \right]_0^{\infty} \\ &= \boxed{F(\omega) = \frac{1}{1+j\omega}} \end{aligned}$$


Ex] $f(t) = e^{-|t|}$



$$\begin{aligned} F(\omega) &= \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^0 f(t) e^{-j\omega t} dt + \int_0^{\infty} f(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^0 e^t e^{-j\omega t} dt + \int_0^{\infty} e^{-t} e^{-j\omega t} dt \\ &= \left[\frac{e^{(1-j\omega)t}}{1-j\omega} \right]_{-\infty}^0 + \left[\frac{e^{-(1+j\omega)t}}{1+j\omega} \right]_0^{\infty} \\ &= \frac{1}{1-j\omega} + \frac{1}{1+j\omega} \\ &= \frac{1+j\omega+1-j\omega}{1+\omega^2} \\ &= \boxed{F(\omega) = \frac{2}{1+\omega^2}} \end{aligned}$$



$$\text{Ex} \boxed{\text{rect}(t)} \rightarrow \begin{cases} 0 & |t| > \frac{1}{2} \\ 1 & |t| \leq \frac{1}{2} \end{cases}$$

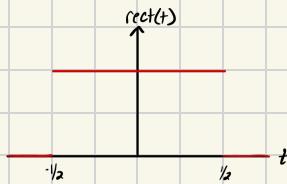

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$


$$= \int_{-1/2}^{1/2} e^{-j\omega t} dt$$

$$\sin(x) = \frac{e^{ix} - e^{-ix}}{2j} \Rightarrow j\sin(x) = e^{ix} - e^{-ix}$$

$$F(\omega) = \left. \frac{e^{-j\omega t}}{-j\omega} \right|_{-1/2}^{1/2} = \frac{1}{j\omega} \left(e^{-j\frac{\omega}{2}} - e^{j\frac{\omega}{2}} \right) = \frac{1}{j\omega} (-j2\sin(\frac{\omega}{2})) = \frac{2}{\omega} \sin(\frac{\omega}{2}) = \text{sinc}(\frac{\omega}{2})$$

$$\text{rect}(t) \longleftrightarrow \text{sinc}(\frac{\omega}{2})$$

$$\text{Ex} \boxed{\Delta(t) = \begin{cases} 1 & |t| < 1/2 \\ 0 & |t| > 1/2 \end{cases}}$$

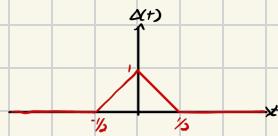

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-1/2}^{1/2} (1-|t|) e^{-j\omega t} dt + \int_{1/2}^{\infty} (1-|t|) e^{-j\omega t} dt$$

$$= \frac{2}{(-j\omega)^2} \left[2\cos(\frac{\omega}{2}) - \omega \right]$$

$$= \frac{4}{\omega^2} (\cos(\frac{\omega}{2}) - 1)$$

$$= \frac{4}{\omega^2} (1 - \cos(\frac{\omega}{2}))$$

$$= \frac{8}{\omega^3} \sin^2(\frac{\omega}{4})$$

$$= \frac{1}{\omega} \left(\frac{16}{\omega^2} \right) \sin^2(\frac{\omega}{4})$$


$$= \frac{1}{\omega} \left(\frac{\sin^2(\frac{\omega}{4})}{(\frac{\omega}{4})^2} \right)$$

$$= \frac{1}{\omega} \text{sinc}^2(\frac{\omega}{4})$$

$$\Delta(t) \longleftrightarrow \frac{1}{\omega} \text{sinc}^2(\frac{\omega}{4})$$

Ex] $\delta(t)$ (Dirac Delta function)
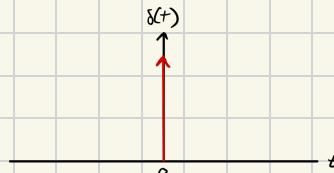
$$\delta(t) = \begin{cases} \infty & t=0 \\ 0 & \text{otherwise} \end{cases}$$



Properties

- 1) Linearity $f_1 + f_2 \longleftrightarrow F_1(\omega) + F_2(\omega)$
- 2) time-shift $f(t-t_0) \longleftrightarrow e^{j\omega t_0} F(\omega)$
- 3) Frequency shift $F(\omega + \omega_0) \longleftrightarrow e^{j\omega_0 t} f(t)$
- 4) Time scaling $f(ct) \longleftrightarrow \frac{1}{|c|} F\left(\frac{\omega}{c}\right)$
- 5) Time derivative $\frac{df}{dt} \longleftrightarrow j\omega F(\omega)$

Ex] $f(t) = \Delta(t - \frac{1}{\alpha})$

$$\Delta(t) \longleftrightarrow \frac{1}{\pi} \operatorname{sinc}^2\left(\frac{\omega}{4}\right)$$

$$f(t) = \Delta(t - \frac{1}{\alpha}) \longleftrightarrow F(\omega) = \frac{1}{\alpha} \operatorname{sinc}\left(\frac{\omega}{4}\right) e^{-j\omega/\alpha}$$

Ex] $f(t) = \cos(\omega_0 t)$

use inverse

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$$

$$\cos(\omega_0 t) = \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$$

$$e^{j\omega_0 t} + e^{-j\omega_0 t} = \frac{1}{\pi} \int F(\omega) e^{j\omega t} d\omega$$

$$F(\omega) = \pi \delta(\omega - \omega_0) + \pi \delta(\omega + \omega_0)$$

Fourier Series

Periodic Signals $\Rightarrow f(t) \longleftrightarrow F_n$ used to describe a signal in Fourier domain
Discrete frequencies, two.

Aperiodic Signals $\Rightarrow g(t) \longleftrightarrow G(w)$ Fourier Transform

All frequencies

How do we determine what freq. is important in Fourier Transform?

$$W = \int_{-\infty}^{\infty} |f(t)|^2 dt = \int_{-\infty}^{\infty} f(t)f^*(t) dt$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{jw t} dw \quad f^*(t) = \left(\frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{-jw t} dw \right)^* = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{-jw t} dw$$

$$W = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(w)|^2 dw \quad \text{Rayleigh's Theorem}$$


$$P = \sum_{n=-\infty}^{\infty} |F_n|^2 \quad \leftarrow \text{Parseval's Theorem}$$

$|F(w)|^2$ = energy spectrum

Signal has finite $|F(w)|^2$, "energy signal"

Ex]

$\text{rect}(t)$

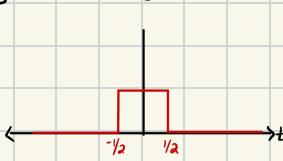

$$f(t) = \text{rect}(t) \xrightarrow{F} \text{sinc}\left(\frac{w}{2}\right) \cdot F(w)$$


Since integrating $\text{sinc}\left(\frac{w}{2}\right)$ may be difficult, we will use time domain

$$W = \int_{-\infty}^{\infty} |\text{rect}(t)|^2 dt = \int_{-\infty}^{\infty} \text{rect}^2(t) dt = \int_{-1/2}^{1/2} 1^2 dt = t \Big|_{-1/2}^{1/2} = \boxed{1J}$$

Signal Classification

* $|F(\omega)|^2$ is concentrated around low frequencies
 \Rightarrow low pass signal


* $|F(\omega)|^2$ is concentrated around a band of frequencies
= band pass signal

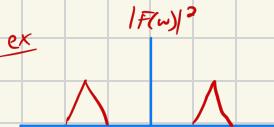

Signal Bandwidth - width of the energy spectrum

$$\xrightarrow{\text{low pass bandwidth}} \omega = 2\pi B \quad \text{Hz, Bandwidth}$$

3dB Bandwidth: $\frac{|F(\omega)|^2}{|F(0)|^2} = \frac{1}{2}$

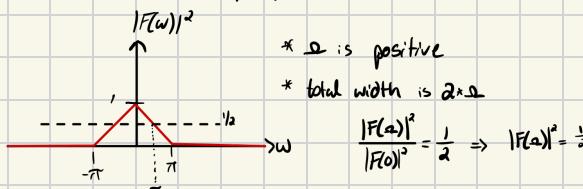

$$\omega = \frac{\pi}{2} \text{ rad/s} \Rightarrow \frac{\pi}{2} = 2\pi B \Rightarrow B = \frac{1}{4} \text{ Hz}$$

Percentage Bandwidth


$$r\omega = \frac{1}{2} \int_{-\infty}^{\infty} |F(\omega)|^2 d\omega$$

$$r \in [0, 1]$$

Ex] $f(t) = \text{rect}\left(\frac{t}{\tau}\right)$

$$\begin{aligned} \frac{t}{\tau} &= \frac{-1}{2} & \frac{t}{\tau} &= \frac{1}{2} \\ t &= -\frac{\tau}{2} & t &= \frac{\tau}{2} \end{aligned}$$
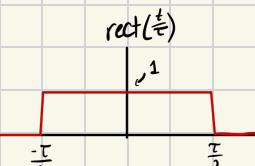
$$\omega = \int_{-\infty}^{\infty} f^2(t) dt = \int_{-\frac{\tau}{2}}^{\frac{\tau}{2}} (1)^2 dt = \omega_0 = \frac{\pi}{\tau}$$



Let's say our bandwidth is $\omega_0 = \frac{\pi}{\tau}$

$$\text{rect}\left(\frac{t}{\tau}\right) \leftarrow \tau \text{sinc}\left(\frac{\omega_0 t}{\pi}\right) = \tau \left(\frac{\sin\left(\frac{\pi t}{\tau}\right)}{\frac{\pi t}{\tau}} \right)$$

$$r(\omega) = \frac{1}{2\pi} \int_{-\pi}^{\pi} \tau^2 \sin^2\left(\frac{\omega\tau}{2}\right) d\omega$$

$$\tau = \frac{1}{2\pi} \int_{-\pi}^{\pi} \tau^2 \sin^2(x) dx =$$

$$\text{let } x = \frac{\omega\tau}{2}$$

$$\frac{d}{dx} = \frac{1}{2\tau}$$


$$r(\tau) = \frac{1}{\pi} \int_{-\pi}^{\pi} \sin^2(x) dx$$

$$r(\tau) = 0.903$$

$\Omega = \frac{\pi\tau}{2}$ is the 90.3% bandwidth

$$\Omega = \frac{\pi\tau}{2} \Rightarrow (\Omega = \frac{1}{2} \text{ Hz})$$

Bandpass Bandwidth

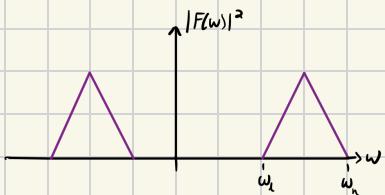


$$\Delta = \omega_{\text{upper}} - \omega_{\text{lower}} \quad (\text{positive values})$$

if $f(t)$ is real:

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} 2|F(\omega)| \cos(\omega t + \theta) d\omega$$

Ex)

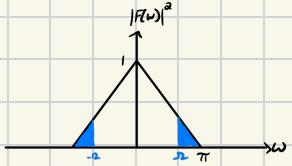

Δ is the 95% bandwidth

$$W = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(\omega)|^2 d\omega = \frac{1}{2\pi} \left(\frac{1}{2}(2\pi)(1) \right) \Rightarrow [W = \frac{1}{2}]$$

We need the area of our triangles to be 5% of W


$$\frac{1}{2\pi} \left(\frac{1}{2} \left(\pi - \Delta \right) \left[\frac{\pi - \Delta}{\pi} \right] \right) = 0.025 \left(\frac{1}{2} \right)$$

$$\frac{1}{4\pi} (\pi - \Delta)^2 = 0.025 \left(\frac{1}{2} \right)$$

$$(\pi - \Delta)^2 = 0.05 \pi^2$$

$$\Delta = \pi (1 - \sqrt{0.05}) \text{ rad/sec}$$

Let's say now:

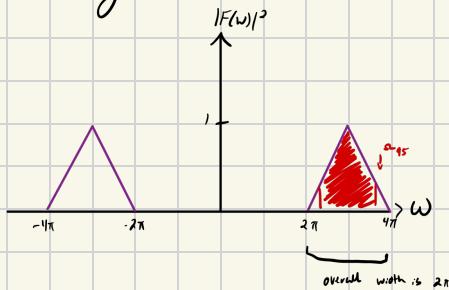


We want to find 95% bandwidth

We only shifted our bandwidth by 2,
so our 95% bandwidth is twice our
previous, i.e.

$$\sigma_{95,\text{new}} = 2(\sigma_{95}) \\ = 2\pi(1 - \sqrt{0.05})$$

$Y(w) = H(w)F(w)$ is the entire 0 state response
not just steady state

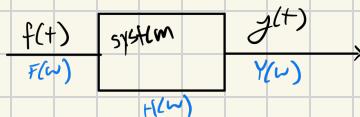Ex) $\frac{d^2y}{dt^2} + 4\frac{dy}{dt} + 3y = u_s(t)$



$$(jw)^2 Y(w) + 4jwY + 3Y = \frac{1}{jw} + \pi\delta(w)$$

$$(3w^2 + j4w)Y(w) = \frac{1}{jw} [1 + jw\pi\delta(w)]$$

$$3j4w - w^2 = (jw)(3jw)$$

$$\frac{dy}{dt} \leftrightarrow jwG(w)$$

$$Y(w) = \frac{1+jw\pi\delta(w)}{jw(3w^2+j4w)} \Rightarrow Y(w) = \frac{1+jw\pi\delta(w)}{jw(1+jw)(3jw)} = \frac{A}{jw} + \frac{B}{1+jw} + \frac{C}{3jw} = \frac{1}{jw} + \frac{\frac{\pi}{2}\delta(w) - \frac{1}{2}}{1+jw} + \frac{\frac{1}{2}\pi\delta(w)}{3jw}$$

$$Y(w) = \frac{\frac{1}{jw}}{\frac{1}{jw}} + \frac{\frac{\pi}{2}\delta(w)}{\frac{1}{jw}} - \frac{\frac{1}{2}}{\frac{1}{jw}} + \frac{\frac{1}{2}\pi\delta(w)}{\frac{1}{jw}}$$


$$\frac{1}{6}\text{sign}(+) + \frac{1}{6}e^{-t}u_3(t) + \frac{1}{6}e^{-3t}u_3(t)$$

$$y(t) = \frac{1}{6}\text{sign}(+) - \frac{1}{2}e^{-t}u_3(t) + \frac{1}{6}e^{-3t}u_3(t) + \frac{1}{6} \int_{-\infty}^t \left(\frac{\pi}{2}\delta(u) - \frac{\pi}{2}\delta(u) \right) e^{j\omega u} du$$

$$+ \frac{1}{2\pi} \left(\frac{\pi}{2} \left(\frac{1}{2} \right) e^{j0} - \frac{\pi}{2} \left(\frac{1}{2} \right) e^{j0} \right) + \frac{1}{2\pi} \left(\frac{\pi}{2} \left(\frac{\pi}{2} \right) e^{j0} - \frac{\pi}{2} \left(\frac{\pi}{2} \right) e^{j0} \right)$$

$$y(t) = \frac{1}{3}u_3(t) + \frac{1}{6}e^{-t}u_3(t) - \frac{1}{2}e^{-t}u_3(t) + \frac{1}{6}$$

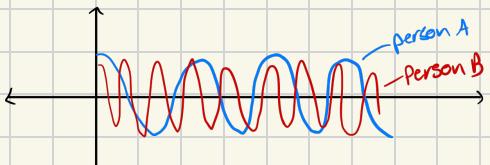Modulation property, AM signal, coherent demodulation



How do we get the information?

-occupy same frequency band + can't get information


Ampititude Modulation

$$y = f(t) \cos(\omega_c t)$$

carrier wave
 info
 carrier frequency

In the United States, AM radio stations use 590-1600 kHz for f_c at 10 kHz intervals

Ex) $y(t) = \cos(f_t t) \cos(10t)$

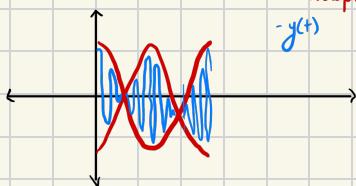

-Envelope

$$-y(t)$$


$$\begin{aligned} y(t) &= f(t) \cos(\omega_c t) = \frac{1}{2} f(t) [e^{j\omega_c t} + e^{-j\omega_c t}] \\ y(t) &= \frac{1}{2} (f(t) e^{j\omega_c t} + f(t) e^{-j\omega_c t}) \end{aligned}$$

$$Y(\omega) = \frac{1}{2} (F(\omega - \omega_c) + F(\omega + \omega_c))$$

* Modulation is not LTI *

Ex) $f(t) = \cos(4\pi t)$

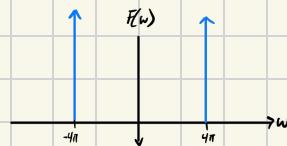
$$F(\omega) = \pi [\delta(\omega - 4\pi) + \delta(\omega + 4\pi)]$$




$$y(t) = f(t) \cos(500\pi t)$$

$$\uparrow \quad \omega_c = 500\pi$$
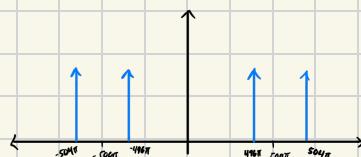
$$Y(\omega) = \frac{1}{2} [F(\omega - 500\pi) + F(\omega + 500\pi)]$$




Ex)

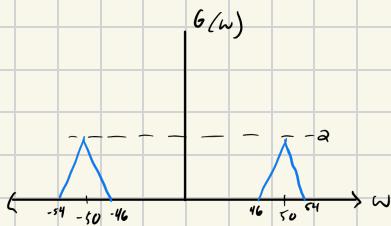

$$y(t) = g(t) \cos(100t)$$
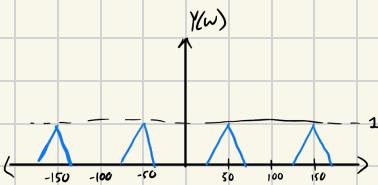
$$Y(w) = \frac{1}{2} [G(w-100) + G(w+100)]$$




How to reconstruct a signal and get the information?

• Coherent Demodulation

* Receiving Many Signals at once *

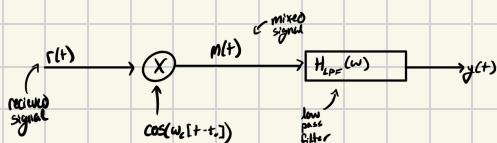* An adjustable band-pass filter to "tune in" the correct station *



$$\begin{aligned} f(t) &\xleftrightarrow{F} F(w) \\ f(t)\cos(\omega_c t) &\xleftarrow[\text{Freq. modulation}]{F} \frac{1}{2}[F(w-\omega_c) + F(w+\omega_c)] \\ r(t) &\xleftrightarrow[\text{time delay}]{F} \frac{1}{2}(F(w-\omega_c)e^{j\omega_c t} + F(w+\omega_c)e^{-j\omega_c t}) \\ r(t) &= f(t-t_0)\cos(\omega_c(t-t_0)) \end{aligned}$$



$$\begin{aligned} M(t) &= f(t-t_0)\cos^2(\omega_c(t-t_0)) \\ M(t) &= f(t-t_0) \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega_c(t-t_0)) \right] \end{aligned} \quad \longleftrightarrow \quad M(w) = \frac{1}{2} F(w) e^{j\omega_c t_0} + \frac{1}{4} [F(w-\omega_c) e^{j\omega_c t_0} + F(w+\omega_c) e^{-j\omega_c t_0}]$$

$$\begin{aligned} H(w) &= M(w) H(w) \\ &= \frac{1}{2} F(w) e^{j\omega_c t_0} \\ y(t) &= \frac{1}{2} f(t-t_0) \end{aligned}$$

* When implementing this, must know we AND at the receiving end to use this *


Envelope DetectionDesired: $f(t)$ dc biasat send: $f(t) + \alpha > 0 \quad \forall t$ Modulation: $s(t) = (f(t) + \alpha) \cos(\omega_c t)$ carrier frequencyReceiving End: $r(t) = (f(t) + \alpha) \cos(\omega_c t)$ * there will be t -delay, but we are ignoring it for simplicity *Envelope: $|f(t) + \alpha| = f(t) + \alpha$ because of init. cond.

Envelope Detector

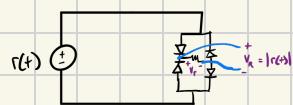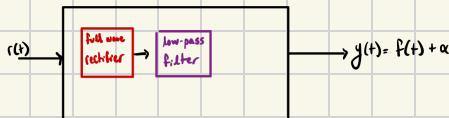

$$\begin{aligned}
 |r(t)| &= |(f(t) + \alpha) \cos(\omega_c t)| = |f(t) + \alpha| |\cos(\omega_c t)| \\
 &= (f(t) + \alpha) \underbrace{|\cos(\omega_c t)|}_{T = \frac{1}{\omega_c} T_0 = \frac{2\pi}{\omega_c}} = \frac{\pi}{\omega_c} = \frac{\pi}{\omega_c} \rightarrow \omega_0 = \frac{2\pi}{\lambda} = 2\omega_c \rightarrow |\cos(\omega_c t)| = \\
 &= (f(t) + \alpha) \left(\frac{\pi}{\pi} + \sum_{n=1}^{\infty} \frac{4}{(n\pi)^2 - 1} \cos(2n\omega_c t) \right)
 \end{aligned}$$


Design a filter that looks like this:

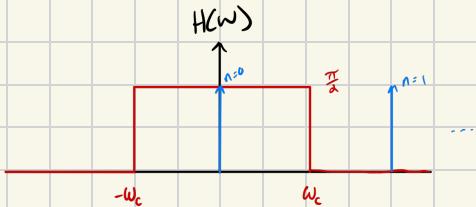

By designing the filter like this, we eliminate all higher frequencies of α

$$\begin{aligned}
 y(t) &= H(\omega) |r(t)| \\
 &= \left[\frac{2}{\pi} (f(t) + \alpha) \right] \left(\frac{\pi}{2} \right)
 \end{aligned}$$

$$y(t) = f(t) + \alpha$$

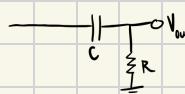

* This requires a tunable low pass filter *

Superheterodyne

1) Mix $r(t) = (f(t)+\alpha) \cos(\omega_c t)$ with $\cos(\omega_{lo} t)$
 Local oscillator

$$m(t) = (f(t)+\alpha) \cos(\omega_c t) \cos(\omega_{lo} t)$$


$$m(t) = \frac{(f(t)+\alpha)}{2} [\cos((\omega_c - \omega_{lo})t) + \cos((\omega_c + \omega_{lo})t)]$$

$$\omega_{lo} = \omega_c + \omega_{if}$$

center frequency f_{if} is fixed. f_{if} tends to be = 455 kHz

$$m(t) = \frac{f(t)+\alpha}{2} [\cos(-\omega_{if}t) + \cos(2\omega_c + \omega_{if}t)]$$

a) Send through a fixed BPF

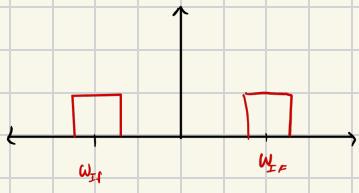


$$y(t) = \frac{f(t)+\alpha}{2} \cos(\omega_{if} t)$$

Send through envelope detector
 $\frac{f(t)+\alpha}{2}$ = output

ω_{lo} : Local LC Circuit that we tune by adjusting the capacitance of the capacitor

$$\omega_{lo} = \frac{1}{\sqrt{LC}}$$

Image Station Problem

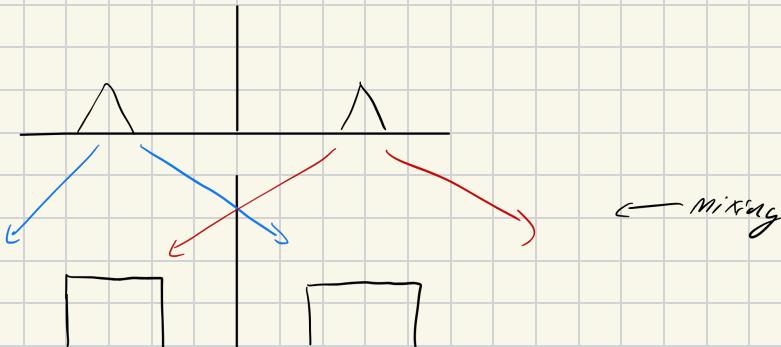



$$\omega_{c2} = \omega_{c1} + 2\omega_{IF}$$

Image
Station

$$m(t) = \frac{f(t) + \alpha}{2} (\cos((\omega_c - \omega_{IF})t) + \cos(\omega_c + \omega_{IF})t))$$

$$\omega_{LO} = \omega_{c1} + \omega_{IF}$$

$$= \omega_{c2} - \omega_{LO}$$

$$= (\omega_{c1} + 2\omega_{IF}) - (\omega_{c1} + \omega_{IF})$$


$$= \omega_{IF}$$

\leftarrow Will interfere w actual desired freq.

We can use pre-selector p. 276 in textbook

Convolution & FT convolution properties

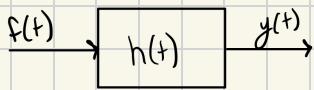Convolution: how the shape of one function is modified by another



Convolution is commutative


$$y(t) = f(t) * h(t)$$

\uparrow convolved with


$$y(t) = \int_{-\infty}^{\infty} h(\tau) f(t-\tau) d\tau$$

\uparrow dummy variable

Ex)

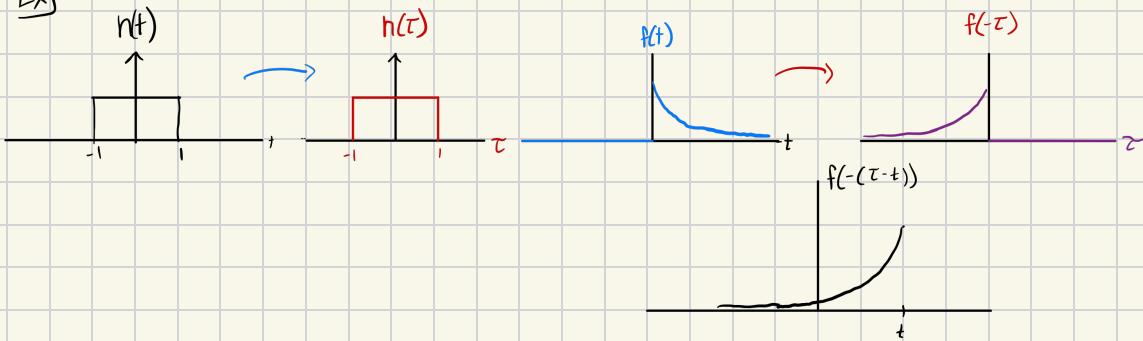

Ex) $h(t) = u_s(t)$

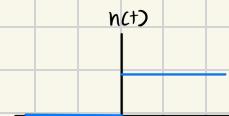

$$f(t) = e^{-t} u_s(t)$$

$f(t)$



t

$$f(-\tau) = e^{-(-\tau)} u_s(-\tau)$$

$$= e^{\tau} u_s(-\tau)$$

$f(-\tau)$




$$f(t-\tau) = e^{-(t-\tau)} u_s(t-\tau) = e^{\tau-t} u_s(-(t-\tau))$$

$f(t-\tau)$

τ

$$y(t) = \int_{-\infty}^{\infty} h(\tau) f(t-\tau) d\tau$$

look when the functions overlap
→

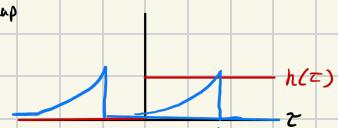


t can be any value.
For what value of t do we see the functions begin to overlap?

$t-\tau = 0$: overlap

$$y(t) = \int_0^t (1) e^{-(t-\tau)} d\tau = \int_0^t e^{\tau-t} d\tau = \int_0^t e^{\tau} e^{-t} d\tau = e^{-t} \left[\int_0^t e^{\tau} d\tau \right] = e^{-t} (e^t - 1) = (1 - e^{-t}) u_s(t)$$

Ex)

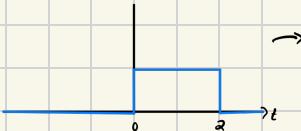
$$h(t) = \text{rect}\left(\frac{t-1}{2}\right)$$



$$h(t) = \text{rect}\left(\frac{t-1}{2}\right)$$




$$f(t) = e^{-t} u_s(t)$$

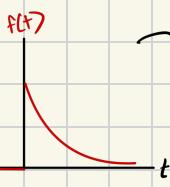


$$f(-\tau) = e^{-t\tau} u_s(-\tau)$$

$$= e^{\tau} u_s(\tau)$$

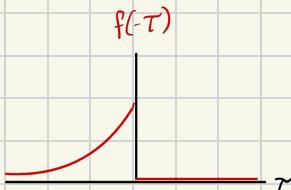

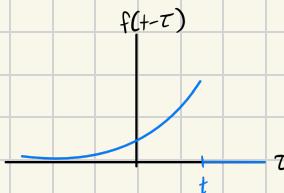
$$f(t-\tau) = e^{-(t-\tau)} u_s(t-\tau) = e^{\tau-t} u_s(\tau-t)$$




Again, t is arbitrary

$0 \leq t \leq a$

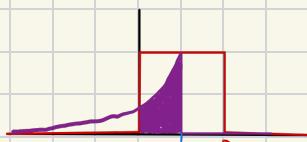

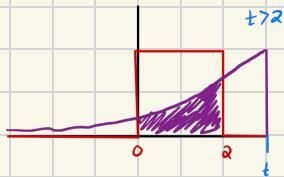
$$\int_0^t e^{-(t-\tau)} h(\tau) d\tau = (1-e^{-t}) u_s(t)$$



$$y(t) = \int_0^t e^{-(t-\tau)} h(\tau) d\tau = e^t (e^{\tau}]_0^t) = e^t (e^a - 1) \Rightarrow (e^{(t-a)} - e^{-t}) u(t-a)$$
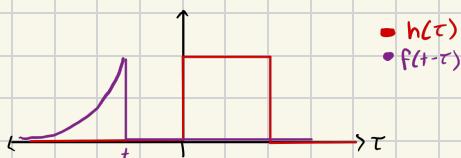
$$y(t) = \begin{cases} 0 & t < 0 \\ (1-e^{-t}) u_s(t) & 0 \leq t < a \\ (e^{(t-a)} - e^{-t}) u_s(t-a) & a \leq t \end{cases}$$



$t=0$: overlap

$t=a$: other considerations

Properties of Convolution

$$1) y(t) = f(t) * h(t) = h(t) * f(t)$$

$$4) y(t-(t_1+t_2)) = h(t-t_1) * f(t-t_2)$$

$$2) y(t) = f(t) * h(t)$$

$$y(t-t_0) = f(t-t_0) * h(t) = f(t) * h(t-t_0)$$

$$5) (f_1 + f_2) * h(t) = f_1 * h(t) + f_2 * h(t)$$

$$3) y(t) = h(t) * f(t)$$

$$\frac{dy}{dt} = \frac{dh}{dt} * f(t)$$


Graphical Convolution

Ex $\text{rect}\left(\frac{t-1}{2}\right)$ $f(t) = e^{-t} u_s(t)$


$$\text{rect}\left(\frac{t-1}{2}\right) = u_s(t) - u_s(t-2)$$

$$\begin{aligned} y(t) &= \text{rect}\left(\frac{t-1}{2}\right) * e^{-t} u_s(t) \\ &= (u_s(t) - u_s(t-2)) * e^{-t} u_s(t) \\ &= u_s(t) * e^{-t} u_s(t) - u_s(t-2) * e^{-t} u_s(t) \\ &= u_s(t) * e^{-t} u_s(t) - u_s(t) * e^{-(t-2)} u_s(t-2) \\ &= (1 - e^{-t}) u_s(t) - (1 - e^{-(t-2)}) u_s(t-2) \end{aligned}$$

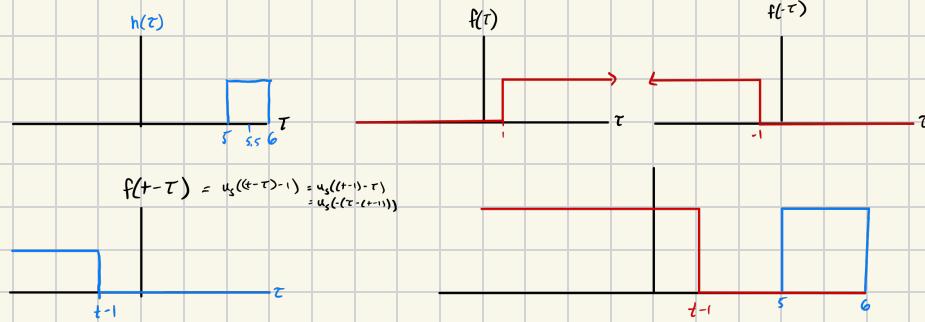Ex $y(t) = \underbrace{\text{rect}(t-5.5)}_{h(t)} * u_s(t-1)$




$$6 \leq t \leq 7$$

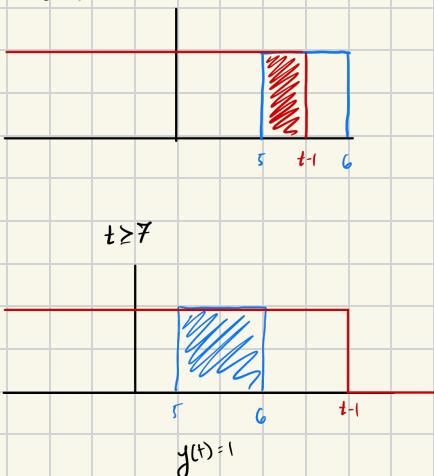

$$6 \leq t \leq 7$$

$$y(t) = \int_5^{t-1} (1)(1) d\tau = \int_5^{t-1} d\tau = \tau \Big|_5^{t-1} = t-1-5 = \boxed{t-6 = y(t)}$$



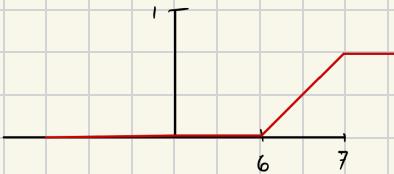
$$y(t) = \begin{cases} 0 & t < 6 \\ \frac{t-6}{1} & 6 \leq t \leq 7 \\ 1 & t > 7 \end{cases}$$



Convolution gives the zero-state solution
so does solving a system in frequency domain.

Convolution Examples

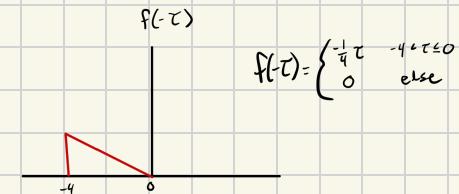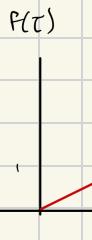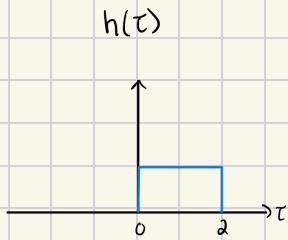
Ex) $\text{rect}\left(\frac{t-1}{2}\right) * f(t)$ st $f(t) = \begin{cases} \frac{1}{4}t & 0 \leq t \leq 4 \\ 0 & \text{otherwise} \end{cases}$




$$f(t-\tau) = \begin{cases} \frac{1}{4}(t-\tau) & 0 \leq t-\tau \leq 4 \\ 0 & \text{else} \end{cases}$$

$$= \begin{cases} \frac{1}{4}(\tau-t) & -t \leq \tau \leq 4-t \\ 0 & \text{else} \end{cases}$$
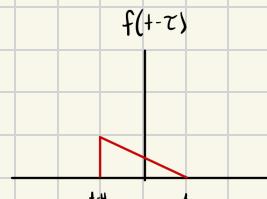
$$= \begin{cases} \frac{1}{4}(T-t) & t \geq \tau > t-4 \\ 0 & \text{else} \end{cases}$$



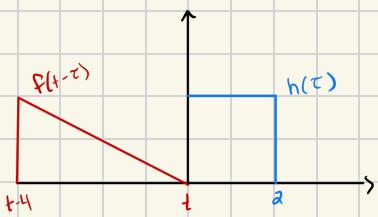

$t < 0$

$$y(t) = 0$$

$t=0$: overlap

$t=\alpha$: overlap 2

$t=4=\alpha$
 $t=6$: end of overlap

$0 \leq t \leq 2$

$$y(t) = \int_0^t (1) \left(\frac{1}{4}(\tau-t) \right) d\tau \Rightarrow \frac{1}{4} \left(\frac{1}{2}\tau^2 - \tau t \right) \Big|_0^t = \frac{t^2}{8}$$

$2 \leq t \leq 4$

$$y(t) = \int_0^2 (1) \left(\frac{1}{4}(\tau-t) \right) d\tau \Rightarrow \frac{1}{4} \left(\frac{1}{2}\tau^2 - \tau t \right) \Big|_0^2 = \frac{1}{2}(t-1)$$

$4 \leq t \leq 6$


$$y(t) = \int_{t-4}^4 (1) \left(\frac{1}{4}(\tau-t) \right) d\tau = \frac{1}{4} \left(\frac{1}{2}\tau^2 - \tau t \right) \Big|_{t-4}^4 \Rightarrow y(t) = \frac{1}{8}(t+3)(6-t)$$

$$y(t) = \begin{cases} \frac{1}{8}t^2 & 0 \leq t < 2 \\ \frac{1}{2}(t-1) & 2 \leq t < 4 \\ \frac{1}{8}(t+3)(6-t) & 4 \leq t < 6 \\ 0 & \text{else} \end{cases}$$

Ex

$$\underline{\text{rect}}\left(\frac{t}{\alpha}\right) * \underline{\text{rect}}\left(\frac{t}{\alpha}\right)$$

$$h(\tau) = \text{rect}(\tau)$$

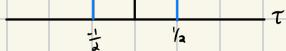

$$f(t-\tau)$$



$$f(\tau) = \text{rect}\left(\frac{\tau}{\alpha}\right)$$

$$f(t-\tau) = \text{rect}\left(\frac{t-\tau}{\alpha}\right)$$


$$= \text{rect}\left(-\left(\frac{\tau-t}{\alpha}\right)\right)$$

$$= \text{rect}\left(\frac{\tau-t}{\alpha}\right)$$

$$\frac{\tau-t}{\alpha} = \frac{1}{\alpha} \Rightarrow \tau-t=1$$

$$\tau=t+1$$

$$\tau=t-1$$

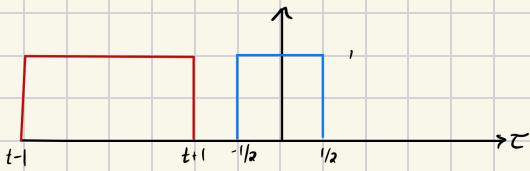

$$t+1 = \frac{-1}{2} \Rightarrow t = \frac{-3}{2} \quad (\text{Start of overlap})$$

$$t-1 = \frac{1}{2} \Rightarrow t = \frac{3}{2} \quad (\text{end of overlap})$$

$$t+1 = \frac{1}{2} \Rightarrow t = \frac{-1}{2} \quad (\text{blue fully enclosed by red})$$

$$t-1 = \frac{1}{2} \Rightarrow t = \frac{1}{2} \quad (\text{blue no longer fully enclosed by red})$$

$$-\frac{3}{2} \leq t < \frac{-1}{2}$$

$$y(t) = \int_{-1/2}^{t+1} 1 \cdot 1 dt = t \Big|_{-1/2}^{t+1} = t + 1 + \frac{1}{2} = t + \frac{3}{2}$$

$$\frac{-1}{2} \leq t < \frac{1}{2}$$

$$y(t) = \int_{-1/2}^{1/2} 1 dt = t \Big|_{-1/2}^{1/2} = \frac{1}{2} + \frac{1}{2} = 1$$

$$\frac{1}{2} \leq t < \frac{3}{2}$$

$$y(t) = \int_{1/2}^{t+1} 1 \cdot 1 dt = t \Big|_{1/2}^{t+1} = \frac{1}{2} - t + 1 = \frac{3}{2} - t$$

$$y(t) = \begin{cases} t + \frac{3}{2} & -\frac{3}{2} \leq t < -\frac{1}{2} \\ 1 & -\frac{1}{2} \leq t < \frac{1}{2} \\ \frac{3}{2} - t & \frac{1}{2} \leq t < \frac{3}{2} \\ 0 & \text{else} \end{cases}$$

Properties

$$y(t) = \text{rect}\left(\frac{t}{2}\right) * \text{rect}(t) \Rightarrow \left(\text{rect}\left(t + \frac{1}{2}\right) + \text{rect}\left(t - \frac{1}{2}\right) \right) * \text{rect}(t)$$

$$= \text{rect}\left(t + \frac{1}{2}\right) * \text{rect}(t) + \text{rect}\left(t - \frac{1}{2}\right) * \text{rect}(t)$$

$$y(t-t_0) = f(t-t_0) * h(t)$$

$$\text{rect}(t) * \text{rect}(t) = \Delta\left(\frac{t}{2}\right)$$

$$= \Delta\left(\frac{t + \frac{1}{2}}{2}\right) + \Delta\left(\frac{t - \frac{1}{2}}{2}\right)$$

$$\text{rect}\left(\frac{t}{B}\right) * \text{rect}\left(\frac{t}{B}\right) = B \cdot \Delta\left(\frac{t}{2B}\right)$$

Impulse and its properties


* $a(1) = a \leftarrow \text{scalar multiplication}$

* $M I = M \leftarrow \text{matrix multiplication}$

* $f(t) * g(t) = f(t)$

Approximate Function
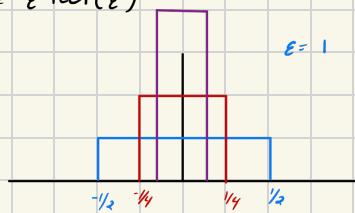
$$P_\epsilon(t) = \frac{1}{\epsilon} \text{rect}\left(\frac{t}{\epsilon}\right)$$



$$\epsilon = 1$$

$$y(t) = f(t) * P_\epsilon(t)$$

$$\begin{aligned} &= \int_{-\infty}^{\infty} \frac{1}{\epsilon} \text{rect}\left(\frac{t-\tau}{\epsilon}\right) f(t-\tau) d\tau \\ &= \frac{1}{\epsilon} \int_{-\infty}^{\infty} f(t-\tau) d\tau \quad \text{for } \epsilon \ll 1 \end{aligned}$$

$$= \frac{1}{\epsilon} \int_{-1/2}^{1/2} f(t-\tau) d\tau$$

$$\lim_{\epsilon \rightarrow 0} \frac{1}{\epsilon} \int_{-1/2}^{1/2} f(t-\tau) d\tau \Rightarrow f(t)$$

Identity for convolution

$$f(t) * \delta(t) = f(t)$$

Properties of $\delta(t)$


$$1) \delta(t-t_0) * f(t) = f(t-t_0)$$

$$2) \delta(t) = \frac{du}{dt}$$

$$u(t) = \int_{-\infty}^t \delta(x) dx$$

$$3) \frac{d}{dt}(\delta(t)) * f(t) = \frac{df}{dt}$$

$$4) \delta(t) \xrightarrow{F} 1$$

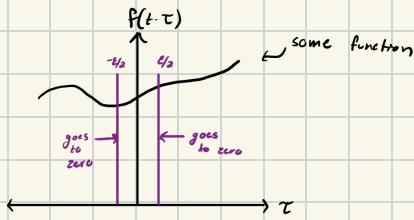

* Convolution in the time domain is the same as multiplication in the frequency domain *


$$5) \int_{-\infty}^{\infty} \delta(t - t_0) f(t) dt = f(t_0)$$

$$6) \int_{-\infty}^{\infty} \delta(t) dt = 1$$


Ex] $f(t) = \text{rect}(t - \frac{1}{2})$ $h(t) = \delta(t-1) - \delta(t-3)$

$$\begin{aligned} y(t) &= \text{rect}(t - \frac{1}{2}) * (\delta(t-1) - \delta(t-3)) \\ &= \text{rect}(t - \frac{1}{2}) * \delta(t-1) - \text{rect}(t - \frac{1}{2}) * \delta(t-3) \\ &= \text{rect}(t - 1.5) - \text{rect}(t - 3.5) \end{aligned}$$



Ex]

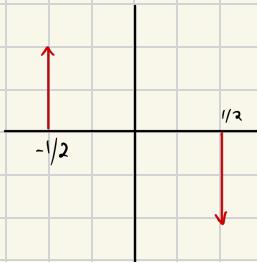

*

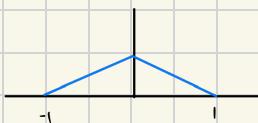

=

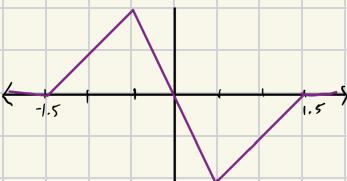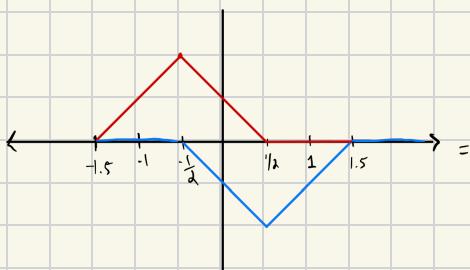

$$\boxed{\text{Ex}} \quad H(\omega) = \frac{j\omega}{1+j\omega}$$

$$f(t) = \text{rect}(t)$$

$f \uparrow$

$$F(\omega) = \text{sinc}(\frac{\omega}{\alpha})$$

$$Y(\omega) = \frac{j\omega}{1+j\omega} \left(\text{sinc}(\frac{\omega}{\alpha}) \right) \quad \begin{matrix} \leftarrow & \text{Not useful} \\ & \text{Not helpful} \end{matrix}$$

$$f(t) = \text{rect}(t)$$

$$H(\omega) = \frac{j\omega}{1+j\omega} = \frac{j\omega + 1 - 1}{1+j\omega} = \frac{1+j\omega}{1+j\omega} - \frac{1}{1+j\omega} = 1 - \frac{1}{1+j\omega}$$

$$h(t) = \delta(t) - e^{-t} u_s(t)$$

$$\begin{aligned} y(t) &= (\delta(t) - e^{-t} u_s(t)) * (u_s(t+\frac{1}{2}) - u_s(t-\frac{1}{2})) \\ &= \delta(t) * u_s(t+\frac{1}{2}) - \delta(t) * u_s(t-\frac{1}{2}) - e^{-t} u_s(t) * u_s(t+\frac{1}{2}) + e^{-t} u_s(t) * u_s(t-\frac{1}{2}) \\ &= u_s(t+\frac{1}{2}) - u_s(t-\frac{1}{2}) - (1 - e^{-(t+1/2)}) u_s(t+1/2) + (1 - e^{-(t-1/2)}) u_s(t-1/2) \\ &= \text{rect}(t) - (1 - e^{-(t+1/2)}) u_s(t+\frac{1}{2}) + (1 - e^{-(t-1/2)}) u_s(t-\frac{1}{2}) \end{aligned}$$

FT of power signals

What is a power signal?

Energy Signals : $W = \int_{-\infty}^{\infty} |f(t)|^2 dt < \infty$

What about signals s.t.

$$\underbrace{|f(t)|^2}_{\text{instantaneous power}} < \infty, \quad W = \int_{-\infty}^{\infty} |f(t)|^2 dt \rightarrow \infty$$

* Power Signal : $|f(t)|^2 < \infty, W \rightarrow \infty$

Ex, $\cos(\omega_0 t), \sin(\omega_0 t), u_s(t)$

Fourier Transform of Power Signals

$$f(t) = \cos(\omega_0 t)$$

$$F(w) = \int_{-\infty}^{\infty} \cos(\omega_0 t) e^{-j\omega t} dt = \frac{1}{2} \int_{-\infty}^{\infty} (e^{j\omega_0 t} + e^{-j\omega_0 t}) e^{-j\omega t} dt = \frac{1}{2} \int_{-\infty}^{\infty} e^{j(\omega_0 - \omega)t} + e^{-j(\omega_0 + \omega)t} dt$$

Value is unhelpful since
 $\lim_{t \rightarrow \infty} e^{j\omega_0 t} = \infty$

Solve the inverse problem instead.

We know we want $f(t) = \cos(\omega_0 t) = \frac{1}{2}(e^{j\omega_0 t} + e^{-j\omega_0 t})$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$$\frac{1}{2}[e^{j\omega_0 t} + e^{-j\omega_0 t}] = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$$\pi[e^{j\omega_0 t} + e^{-j\omega_0 t}] = \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

← By analyzing this, we see only two frequency values survive:
 ω_0 and $-\omega_0$.

$$F(w) = \pi[\delta(w - \omega_0) + \delta(w + \omega_0)]$$

$$\underline{\text{Ex}} \quad f(t) = \sin(\omega_0 t) = \frac{j}{2} (e^{j\omega_0 t} - e^{-j\omega_0 t})$$

$$f(t) = \frac{-j}{2} (e^{j\omega_0 t} - e^{-j\omega_0 t}) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$$j\pi (e^{j\omega_0 t} - e^{-j\omega_0 t}) = \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$$F(w) = j\pi [\delta(w+w_0) - \delta(w-w_0)]$$

$$\underline{\text{Ex}} \quad f(t) = 1$$


$$1 = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$$2\pi = \int_{-\infty}^{\infty} F(w) e^{j\omega_0 t} dw$$

$\leftarrow w=0 \text{ sec}$

$$F(w) = 2\pi \delta(w)$$
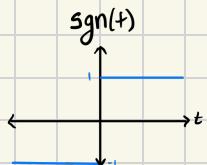
$$\underline{\text{Ex}} \quad f(t) = u_s(t) = \frac{1}{2} (\text{sgn}(t) + 1)$$



$$1 \xleftrightarrow{F} 2\pi \delta(w)$$

$$\text{sgn}(t) \xleftrightarrow{F} \frac{a}{jw}$$

$$f(t) = u_s(t) = \frac{1}{2} (1 + \text{sgn}(t)) \xleftrightarrow{} \pi \delta(w) + \frac{1}{jw}$$

Ex Modulation

$$f(t)g(t) \xleftrightarrow{F} \frac{1}{2\pi} F(w) * G(w)$$

$$f(t) * g(t) \xleftrightarrow{} F(w) \cdot G(w)$$

$$\text{let } g(t) = \cos(\omega_c t)$$

$$f(t)\cos(\omega_c t) \xleftrightarrow{F} \frac{1}{2\pi} (F(w) * \pi[\delta(w-\omega_c) + \delta(w+\omega_c)])$$

$$\xleftrightarrow{} \frac{1}{2} (F(w) * \delta(w-\omega_c) + F(w) * \delta(w+\omega_c))$$

$$\xleftrightarrow{} \frac{1}{2} (F(w-\omega_c) + F(w+\omega_c))$$

Let's now try the Fourier Transform of a generic periodic function

periodic Signal


$$f(t) = \sum_{n=-\infty}^{\infty} F_n e^{j n \omega_0 t}$$

$$\omega_0 = \frac{2\pi}{T}$$



$$\sum_{n=-\infty}^{\infty} F_n e^{j n \omega_0 t} = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(w) e^{j w t} dw$$

Integer
multiples of
some base ω
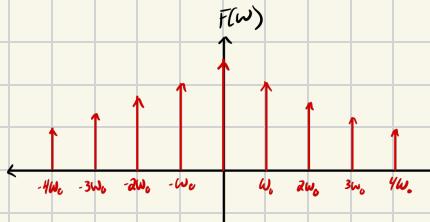
$$F(w) = \sum_{n=-\infty}^{\infty} 2\pi F_n \delta(w - n\omega_0)$$



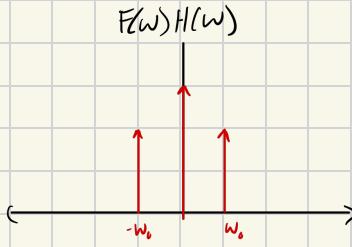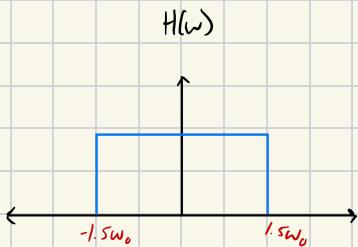
* Impulse Train: sum of delta functions
a fixed interval apart *



Sampling and analog signal reconstruction

$$f(t) = \cos(2\pi f t) \quad \leftarrow f \text{ is a frequency in Hz}$$

$f = \frac{1}{T}$

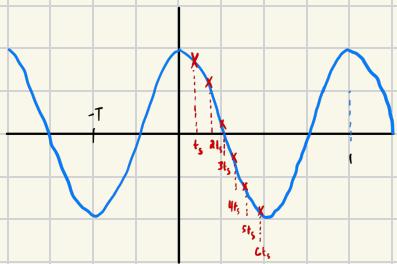

$f_s = \text{sampling rate}$
 $t_s = \text{sampling time}$

$$t = \frac{1}{f_s}$$

$$F[n] = f(nt_s) = \cos(2\pi f n t_s) = [f(0), f(t_s), f(2t_s), \dots]$$

↑
some integer

Reconstruction:

$$f_r(t) = \sum_n F[n] \phi_n(t)$$


basis function

In this class, $\phi_n(t)$ will be $= \text{sinc}\left(\frac{\pi}{t_s}[t-nt_s]\right)$

$$\Rightarrow \sum_n F[n] \text{sinc}\left(\frac{\pi}{t_s}[t-nt_s]\right)$$

$$\text{sinc}(x) = \frac{\sin(x)}{x}$$
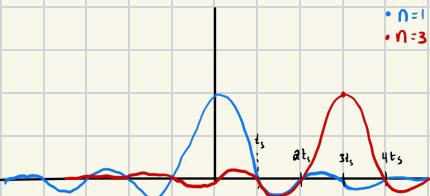
$$\phi_n = \begin{cases} 1 & t=nt_s \\ 0 & \text{all other vals of } t_s \end{cases}$$



Now from continuous to discrete

$$F[n] = \sum f(t) \delta(t-nt_s)$$




We can also take the Fourier Transform of a discrete signal

$$\begin{aligned}
 \sum_n f(t) \delta(t - nt_s) &\xleftarrow{\mathcal{F}} \frac{1}{2\pi} \left(F(\omega) * \sum_{n=-\infty}^{\infty} \frac{a\pi}{t_s} \delta(\omega - n \frac{a\pi}{t_s}) \right) \\
 &= \frac{1}{2\pi} \sum_{n=-\infty}^{\infty} F(\omega) * \frac{a\pi}{t_s} \delta(\omega - n \frac{a\pi}{t_s}) \\
 &= \frac{1}{t_s} \sum_{n=-\infty}^{\infty} F(\omega - n \frac{a\pi}{t_s}) \\
 &= f_s \sum_{n=-\infty}^{\infty} F(\omega - n 2\pi f_s)
 \end{aligned}$$

Let's say $f(t) \rightarrow$ Bandwidth B

$$\omega_c = 2\pi B$$

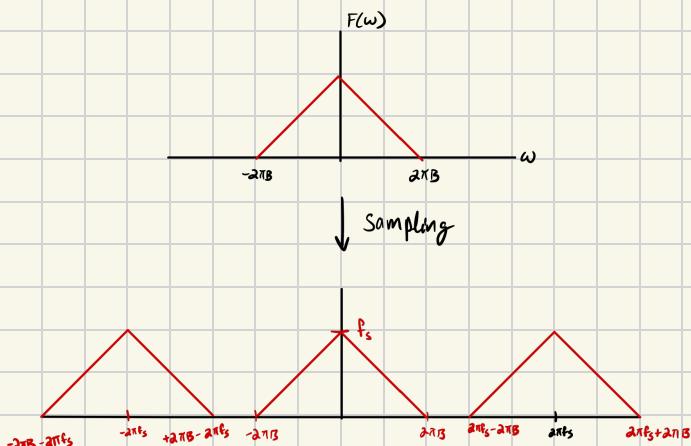


for some sampling rate:



$$\therefore \text{the minimum: } 2\pi f_s - 2\pi B = 2\pi B$$

\downarrow
what this means

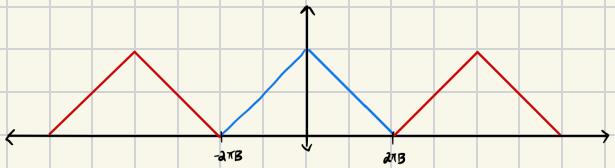

$$f_s = 2B$$

Nyquist Frequency

Nyquist's Sampling Theorem:

$f_s > 2B$ to reconstruct $f(t)$ from sampled signal

If $f_s < 2B$: aliasing (projecting higher frequency signal onto a lower frequency)

DAC: Digital to analog converter

$$f(nt_s) \xrightarrow{\sum_n p(t-nt_s)} m(t) \quad \rightarrow \quad p(t-nt_s) = \text{rect}\left(\frac{t-nt_s}{t_s}\right)$$

