

(Chapter 7)(Alternating Current)

Additional Exercises

Question 7.12:

An LC circuit contains a 20 mH inductor and a 50 μ F capacitor with an initial charge of 10 mC. The resistance of the circuit is negligible. Let the instant the circuit is closed be t=0.

- (a) What is the total energy stored initially? Is it conserved during LC oscillations?
- **(b)** What is the natural frequency of the circuit?
- (c) At what time is the energy stored (i) completely electrical (i.e., stored in the capacitor)? (ii) completely magnetic (i.e., stored in the inductor)?
- (d) At what times is the total energy shared equally between the inductor and the capacitor?
- (e) If a resistor is inserted in the circuit, how much energy is eventually dissipated as heat?

Answer 7.12:

Inductance of the inductor, L=20 mH = 20×10^{-3} H Capacitance of the capacitor, C=50 $\mu F=50\times 10^{-6}$ F Initial charge on the capacitor, Q=10 mC = 10×10^{-3} C

(a) Total energy stored initially in the circuit is given as:

$$E = \frac{1}{2} \frac{Q^2}{C}$$
$$= \frac{\left(10 \times 10^{-3}\right)^2}{2 \times 50 \times 10^{-6}} = 1 \text{ J}$$

Hence, the total energy stored in the LC circuit will be conserved because there is no resistor connected in the circuit.



(b) Natural frequency of the circuit is given by the relation,

$$v = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{20 \times 10^{-3} \times 50 \times 10^{-6}}}$$

$$= \frac{10^{3}}{2\pi} = 159.24 \text{ Hz}$$

Natural angular frequency,

$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{20 \times 10^{-3} \times 50 \times 10^{-6}}} = \frac{1}{\sqrt{10^{-6}}} = 10^3 \text{ rad/s}$$

Hence, the natural frequency of the circuit is 10^3 rad/s.

(c) (i) For time period (T = $\frac{1}{v}$ = $\frac{1}{159.24}$ = 6.28 ms), total charge on the capacitor at time t, $Q' = Q \cos \frac{2\pi}{T} t$

For energy stored is electrical, we can write Q' = Q.

Hence, it can be inferred that the energy stored in the capacitor is completely

electrical at time,
$$t = 0, \frac{T}{2}, T, \frac{3T}{2}, \dots$$

(ii) Magnetic energy is the maximum when electrical energy, Q' is equal to Hence, it can be inferred that the energy stored in the capacitor is completely magnetic at time, $t = \frac{T}{4}, \frac{3T}{4}, \frac{5T}{4}$

(d) Q¹ = Charge on the capacitor when total

magnetic at time,
$$t = \frac{T}{4}, \frac{3T}{4}, \frac{5T}{4}...$$

magnetic at time, $t = \frac{T}{4}, \frac{3T}{4}, \frac{5T}{4}$

(d) Q¹ = Charge on the capacitor when total energy is equally shared aly sh between the capacitor and the inductor at time t.



When total energy is equally shared between the inductor and capacitor, the energy stored in the capacitor = $\frac{1}{2}$ (maximum energy)

$$\Rightarrow \frac{1}{2} \frac{\left(Q^{1}\right)^{2}}{C} = \frac{1}{2} \left(\frac{1}{2} \frac{Q^{2}}{C}\right) = \frac{1}{4} \frac{Q^{2}}{C}$$

$$Q^{1} = \frac{Q}{\sqrt{2}}$$
But $Q^{1} = Q \cos \frac{2\pi}{T} t$.
$$\frac{Q}{\sqrt{2}} = Q \cos \frac{2\pi}{T} t$$

$$\cos \frac{2\pi}{T} t = \frac{1}{\sqrt{2}} = \cos(2n+1) \frac{\pi}{4};$$
 where $n = 0, 1, 2, ...$

$$t = (2n+1) \frac{T}{8}$$

Hence, total energy is equally shared between the inductor and the capacity at time,

$$t = \frac{T}{8}, \frac{3T}{8}, \frac{5T}{8}....$$

If a resistor is inserted in the circuit, then total initial energy is (e) dissipated as heat energy in the circuit. The resistance damps out the LC oscillation.

Question 7.13:

A coil of inductance 0.50 H and resistance 100 Ω is connected to a 240 V, (b) What is the time lag between the voltage maximum and the current maximum?



Answer 7.13:

Inductance of the inductor, L = 0.50 H

Resistance of the resistor, $R = 100 \Omega$

Potential of the supply voltage, V = 240 V

Frequency of the supply, v = 50 Hz

(a) Peak voltage is given as:

$$V_0 = \sqrt{2}V$$

= $\sqrt{2} \times 240 = 339.41 \text{ V}$

Angular frequency of the supply, $\omega = 2 \pi v$

$$= 2\pi \times 50 = 100 \,\pi \,\text{rad/s}$$

Maximum current in the circuit is given as:

$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

$$= \frac{339.41}{\sqrt{(100)^2 + (100\pi)^2 (0.50)^2}} = 1.82 \text{ A}$$

(b) Equation for voltage is given as:

 $V=V_0\;cos\;\omega t$

Equation for current is given as:

$$I = I_0 \cos (\omega t - \Phi)$$

Where,

 Φ = Phase difference between voltage and current At time, t = 0.

 $V = V_0$ (voltage is maximum)

For
$$\omega t - \Phi = 0$$
 i.e., at time $t = \frac{\phi}{\omega}$, $I = I_0$ (current is maximum)

Stars Pracing Hence, the time lag between maximum voltage and maximum current is

Million Stars & Practice

Williams and Start Sta



https://millionstar.godaddysites.com/

Now, phase angle Φ is given by the relation,

$$\tan \phi = \frac{\omega L}{R}$$

$$= \frac{2\pi \times 50 \times 0.5}{100} = 1.57$$

$$\phi = 57.5^{\circ} = \frac{57.5\pi}{180} \text{ rad}$$

$$\omega t = \frac{57.5\pi}{180}$$

$$t = \frac{57.5}{180 \times 2\pi \times 50}$$

$$= 3.19 \times 10^{-3} \text{ s}$$

$$= 3.2 \text{ ms}$$

Hence, the time lag between maximum voltage and maximum current is 3.2 ms.

Question 7.14:

Obtain the answers (a) to (b) in Exercise 7.13 if the circuit is connected to a high frequency supply (240 V, 10 kHz). Hence, explain the statement that at very high frequency, an inductor in a circuit nearly amounts to an open circuit. How does an inductor behave in a dc circuit after the steady state?

Answer 7.14:

Inductance of the inductor, L = 0.5 Hz

Resistance of the resistor, $R = 100 \Omega$

Potential of the supply voltages, V = 240 V

Frequency of the supply, $v = 10 \text{ kHz} = 10^4 \text{ Hz}$

Angular frequency, $\omega = 2\pi v = 2\pi \times 10^4 \text{ rad/s}$





(a) Peak voltage,
$$V_0 = \sqrt{2} \times V = 240\sqrt{2} \text{ V}$$

Maximum current,
$$I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

$$= \frac{240\sqrt{2}}{\sqrt{(100)^2 + (2\pi \times 10^4)^2 \times (0.50)^2}} = 1.1 \times 10^{-2} \text{ A}$$

(b) For phase difference Φ , we have the relation:

$$\tan \phi = \frac{\omega L}{R}$$

$$= \frac{2\pi \times 10^{4} \times 0.5}{100} = 100\pi$$

$$\phi = 89.82^{\circ} = \frac{89.82\pi}{180} \text{ rad}$$

$$\omega t = \frac{89.82\pi}{180}$$

$$t = \frac{89.82\pi}{180 \times 2\pi \times 10^{4}} = 25\mu \text{s}$$

It can be observed that I₀ is very small in this case. Hence, at high frequencies, the inductor amounts to an open circuit.

In a dc circuit, after a steady state is achieved, $\omega = 0$. Hence, inductor L behaves like a pure conducting object.

Question 7.15:

A 100 μ F capacitor in series with a 40 Ω resistance is connected to a 110 V, 60 Hz supply.

- (a) What is the maximum current in the circuit?
- (b) What is the time lag between the current maximum and the voltage maximum?

Wondershare

<u>PDFelement</u>



Answer 7.15:

Capacitance of the capacitor, $C=100~\mu F=100\times 10^{-6}~F$

Resistance of the resistor, $R = 40 \Omega$

Supply voltage, V = 110 V

(a) Frequency of oscillations, v=60 Hz

Angular frequency, $\omega = 2\pi v = 2\pi \times 60 \text{ rad/s}$

For a RC circuit, we have the relation for impedance as:

$$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$110\sqrt{2}$$
as:

Peak voltage, $V_0 = V\sqrt{2} = 110\sqrt{2}$

Maximum current is given as:

$$I_{0} = \frac{V_{0}}{Z}$$

$$= \frac{V_{0}}{\sqrt{R^{2} + \frac{1}{\omega^{2}C^{2}}}}$$

$$= \frac{110\sqrt{2}}{\sqrt{(40)^{2} + \frac{1}{(120\pi)^{2} \times (10^{-4})^{2}}}}$$

$$= \frac{110\sqrt{2}}{\sqrt{1600 + \frac{10^{8}}{(120\pi)^{2}}}} = 3.24 \text{ A}$$

(b) In a capacitor circuit, the voltage lags behind the current by a phase angle of Φ . This angle is given by the relation:





Hence, the time lag between maximum current and maximum voltage is 1.55 ms.

Question 7.16:

Obtain the answers to (a) and (b) in Exercise 7.15 if the circuit is connected to a 110 V, 12 kHz supply? Hence, explain the statement that a capacitor is a conductor at very high frequencies. Compare this behaviour with that of a capacitor in a dc circuit after the steady state.

Answer 7.16:

Millions are advactice Capacitance of the capacitor, $C = 100 \mu F = 100 \times 10^{-6} F$

Resistance of the resistor, $R = 40 \Omega$

Supply voltage, V = 110 V

Frequency of the supply, $v = 12 \text{ kHz} = 12 \times 10^3 \text{ Hz}$

Angular Frequency, $\omega = 2 \pi v = 2 \times \pi \times 12 \times 10^3 03$

$$= 24\pi \times 10^3 \text{ rad/s}$$





Peak voltage,
$$V_0 = V\sqrt{2} = 110\sqrt{2} \text{ V}$$

Maximum current,
$$I_0 = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

$$= \frac{110\sqrt{2}}{\sqrt{(40)^2 + \frac{1}{(24\pi \times 10^3 \times 100 \times 10^{-6})^2}}}$$

$$= \frac{110\sqrt{2}}{\sqrt{24\pi \times 10^3 \times 100 \times 10^{-6}}}$$

For an RC circuit, the voltage lags behind the current by a phase angle of Φ given as:

$$\tan \phi = \frac{\frac{1}{\omega C}}{R} = \frac{1}{\omega CR}$$

$$= \frac{1}{24\pi \times 10^3 \times 100 \times 10^{-6} \times 40}$$

$$\tan \phi = \frac{1}{96\pi}$$

$$\therefore \phi \approx 0.2^\circ$$

$$= \frac{0.2\pi}{180} \text{ rad}$$
∴ Time lag = $\frac{\phi}{\omega}$

$$= \frac{0.2\pi}{180 \times 24\pi \times 10^3} = 1.55 \times 10^{-3} \text{ s} = 0.04 \mu \text{s}$$

 $=\frac{3.2\pi}{180\times24\pi\times10^3}=1.55\times10^{-3}\,\text{s}=0.04\mu\text{s}$ Hence, Φ tends to become zero at high frequencies. At a high frequency, capacitor C acts as a conductor. In a dc circuit, after the steady state is achieved, $\omega=0$. Hence, capacitor C amounts to an open circuit.



Question 7.17:

Keeping the source frequency equal to the resonating frequency of the series LCR circuit, if the three elements, L, C and R are arranged in parallel, show that the total current in the parallel LCR circuit is minimum at this frequency. Obtain the current rms value in each branch of the circuit for the elements and source specified in Exercise 7.11 for this frequency.

https://millionstar.godaddysites.com/

Answer 7.17:

An inductor (L), a capacitor (C), and a resistor (R) is connected in parallel with each other in a circuit where,

$$L = 5.0 H$$

$$C = 80 \; \mu F = 80 \times 10^{-6} \, F$$

$$R = 40 \Omega$$

Potential of the voltage source, V = 230 V

Impedance (Z) of the given parallel LCR circuit is given as:

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$$

Where, $\omega = \text{Angular frequency}$

At resonance,
$$\frac{1}{\omega L} - \omega C = 0$$

$$\therefore \omega = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{5 \times 80 \times 10^{-6}}} = 50 \text{ rad/s}$$

Hence, the magnitude of Z is the maximum at 50 rad/s. As a result, the total current is minimum. rms current flowing through inductor \mathbf{I} is \mathbf{I}





$$I_L = \frac{V}{\omega L}$$
$$= \frac{230}{50 \times 5} = 0.92 \text{ A}$$

rms current flowing through capacitor C is given as:

$$I_C = \frac{V}{\frac{1}{\omega C}} = \omega CV$$
$$= 50 \times 80 \times 10^{-6} \times 230 = 0.92 \text{ A}$$

rms current flowing through resistor R is given as:

$$I_R = \frac{V}{R}$$

$$= \frac{230}{40} = 5.75 \text{ A}$$

Question 7.18:

A circuit containing a 80 mH inductor and a 60 µF capacitor in series is connected to a 230 V, 50 Hz supply. The resistance of the circuit is negligible.

- (a) Obtain the current amplitude and rms values.
- (b) Obtain the rms values of potential drops across each element.
- (c) What is the average power transferred to the inductor?
- (d) What is the average power transferred to the capacitor?
- Willion Stars Practice (e) What is the total average power absorbed by the circuit? ['Average' implies 'averaged over one cycle'.]

Answer 7.18:

Inductance,
$$L = 80 \text{ mH} = 80 \times 10^{-3} \text{ H}$$

Capacitance,
$$C = 60 \mu F = 60 \times 10^{-6} F$$

Million Stars Practice





https://millionstar.godaddysites.com/

Supply voltage, V = 230 V

Frequency, v = 50 Hz

Angular frequency, $\omega = 2\pi v = 100 \pi \text{ rad/s}$

Peak voltage, $V_0 = v\sqrt{2} = 230\sqrt{2} \text{ V}$

(a) Maximum current is given as:

Hence, rms value of current,

$$\begin{split} I_0 &= \frac{V_0}{\left(\omega L - \frac{1}{\omega C}\right)} \\ &= \frac{230\sqrt{3}}{\left(100\pi \times 80 \times 10^{-3} - \frac{1}{100\pi \times 60 \times 10^{-6}}\right)} \\ &= \frac{230\sqrt{2}}{\left(8\pi - \frac{1000}{6\pi}\right)} = -11.63 \text{ A} \end{split}$$

The negative sign appears because

$$\omega L < \frac{1}{\omega C}$$

Amplitude of maximum current, $I_0 = 11.63 \text{ A}$

$$I = \frac{I_0}{\sqrt{2}} = \frac{-11.63}{\sqrt{2}} = -8.22 \text{ A}$$

(b) Potential difference across the inductor,

$$V_L \!\! = I \times \omega L$$

$$= 8.22 \times 100 \; \pi \times 80 \times 10^{-3}$$

Potential difference across the capacitor,

$$V_{\rm c} = I \times \frac{1}{\omega C}$$

= $8.22 \times \frac{1}{100\pi \times 60 \times 10^{-6}} = 436.3 \text{ V}$



- (c) Average power consumed by the inductor is zero as actual voltage leads the current by $\frac{\pi}{2}$.
- (d) Average power consumed by the capacitor is zero as voltage lags current by $\frac{\pi}{2}$.
- (e) The total power absorbed (averaged over one cycle) is zero.

Question 7.19:

Suppose the circuit in Exercise 7.18 has a resistance of 15 Ω . Obtain the average power transferred to each element of the circuit, and the total power absorbed.

Answer 7.19:

Average power transferred to the resistor = 788.44 W

Average power transferred to the capacitor = 0 W

Total power absorbed by the circuit = 788.44 W

Inductance of inductor, $L = 80 \text{ mH} = 80 \times 10^{-3} \text{ H}$

Capacitance of capacitor, $C = 60 \mu F = 60 \times 10^{-6} F$

Resistance of resistor, $R = 15 \Omega$

Potential of voltage supply, V = 230 V

Frequency of signal, v = 50 Hz

The elements are connected in series to each other. Hence, impedance of the circuit is given as:



Current flowing in the circuit,

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= \sqrt{\left(15\right)^2 + \left(100\pi \left(80 \times 10^{-3}\right) - \frac{1}{\left(100\pi \times 60 \times 10^{-6}\right)}\right)^2}$$

$$= \sqrt{\left(15\right)^2 + \left(25.12 - 53.08\right)^2} = 31.728 \Omega$$

$$I = \frac{V}{Z} = \frac{230}{31.728} = 7.25 \text{ A}$$

Average power transferred to resistance is given as:

$$P_R = I^2 R$$

= $(7.25)^2 \times 15 = 788.44 W$

Average power transferred to capacitor, P_C = Average power transferred to inductor, $P_L = 0$

Total power absorbed by the circuit:

$$= P_R + P_C + P_L$$

= 788.44 + 0 + 0 = 788.44 W

Hence, the total power absorbed by the circuit is 788.44 W.

Question 7.20:

A series LCR circuit with L = 0.12 H, C = 480 nF, R = 23 Ω is connected to

- (a) What is the source frequency for which current amplitude is maximum?

 Obtain this maximum value.

 (b) What is the source frequency for the last of the last of the source frequency for the last of th
- (b) What is the source frequency for which average power absorbed by the circuit is maximum? Obtain the value of this maximum power.

Willion Stars & Practice



https://millionstar.godaddysites.com/

- (c) For which frequencies of the source is the power transferred to the circuit half the power at resonant frequency? What is the current amplitude at these frequencies?
- (d) What is the Q-factor of the given circuit?

Answer 7.20:

Inductance, L = 0.12 H

Capacitance, $C = 480 \text{ nF} = 480 \times 10^{-9} \text{ F}$

Resistance, $R = 23 \Omega$

Supply voltage, V = 230 V

Peak voltage is given as:

$$V_0 = \sqrt{2} \times 230 = 325.22 \text{ V}$$

(a) Current flowing in the circuit is given by the relation,

$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

Where,

 $I_0 = maximum$ at resonance

At resonance, we have

$$\omega_R L - \frac{1}{\omega_R C} = 0$$

Where,

 $\omega_R\!=Resonance\ angular\ frequency$





$$\therefore \omega_R = \frac{1}{\sqrt{LC}}$$
=\frac{1}{\sqrt{0.12 \times 480 \times 10^{-9}}} = 4166.67 \text{ rad/s}

:.Resonant frequency,
$$v_R = \frac{\omega_R}{2\pi} = \frac{4166.67}{2 \times 3.14} = 663.48 \text{ Hz}$$

And, maximum current $(I_0)_{\text{Max}} = \frac{V_0}{R} = \frac{325.22}{23} = 14.14 \text{ A}$

(b) Maximum average power absorbed by the circuit is given as:

$$(P_{\text{av}})_{\text{Max}} = \frac{1}{2} (I_0)_{\text{Max}}^2 R$$

= $\frac{1}{2} \times (14.14)^2 \times 23 = 2299.3 \text{ W}$

Hence, resonant frequency (V_R) is 663.48 Hz

(c) The power transferred to the circuit is half the power at resonant frequency.

Frequencies at which power transferred is half, $= \omega_R \pm \Delta \omega$ $=2\pi(v_R \pm \Delta v)$ Million Stars Practice

Where,

$$\Delta\omega = \frac{R}{2L}$$
$$= \frac{23}{2 \times 0.12} = 95.83 \text{ rad/s}$$

Hence, change in frequency, $\Delta v = \frac{1}{2\pi} \Delta \omega = \frac{95.83}{2\pi} = 15.26 \text{ Hz}$

$$v_R + \Delta v = 663.48 + 15.26 = 678.74 \text{ Hz}$$





And,

Hence, at 648.22 Hz and 678.74 Hz frequencies, the power transferred is half.

At these frequencies, current amplitude can be given as:

(d) Q-factor of the given circuit can be obtained using the relation,

Hence, the Q-factor of the given circuit is 21.74.

Question 7.21:

Obtain the resonant frequency and Q-factor of a series LCR circuit with L = Ÿ ,W LV GHVLUHG —) DQG 5 &

WKH UHVRQDQFH RI WKH FLUFXLW E\ UHGXFLQJ a factor of 2. Suggest a suitable way.

Answer 7.21:

Inductance, L = 3.0 H

Capacitance, $C = 27 \mu F = 27 \times {}^{6} \Phi$

5 H V L V W D Q F H

At resonance, angular frequency of the source for the given LCR series circuit is given as:



Q-factor of the series:

$$Q = \frac{\omega_r L}{R}$$
=\frac{111.11 \times 3}{7.4} = 45.0446

To improve the sharpness of the resonance by reducing its 'full width at half maximum' by a factor of 2 without changing ω_r , we need to reduce R to half i.e., Resistance = $\frac{R}{2} = \frac{7.4}{2} = 3.7 \Omega$

Question 7.22:

Answer the following questions:

- (a) In any ac circuit, is the applied instantaneous voltage equal to the algebraic sum of the instantaneous voltages across the series elements of the circuit? Is the same true for rms voltage?
- (b) A capacitor is used in the primary circuit of an induction coil.
- (c) An applied voltage signal consists of a superposition of a dc voltage and an ac voltage of high frequency. The circuit consists of an inductor and a capacitor in series.

Show that the dc signal will appear across C and the ac signal across L.

- (d) A choke coil in series with a lamp is connected to a dc line. The lamp is seen to shine brightly. Insertion of an iron core in the choke causes no change in the lamp's brightness. Predict the corresponding observations if the connection is to an ac line.
- (e) Why is choke coil needed in the use of fluorescent tubes with ac mains? e coil? Why can we not use an ordinary resistor instead of the choke coil?

Remove Watermark



Answer 7.22:

- (a) As:th statement is not true for rms wag I is true that in any ac circuit, thated viag is equal to thaverag sum of th instantaneous vlags across th series elements of th circuit. Hwever, the is not true for rms what because what across different elements may not be in place.
- (b) Hinduced viag is used to care the carcitor. A capcitor is used in the pimary circuit of an induction coil is because who the circuit is broken, a Hainduced what is used to chre the capcitor to avid sprk.
- sigalwilapar across capcitor Gecause for dc sigal, th (c) **Tdc** impdance of an inductor (L is nelibe with the impdance of a capcitor (Cis vry lifamost infinite). Hece,a de signalapars across Of an ac signififequency, the impdance of is thand that of Gs ery bw. Hence, an ac signal of the general agars across L
- fan iron core is inserted in the chk coil (whelis in series with (d) hmpconnected to the ac lne), then the hmpwill be dimby. It is because the chk coil and the iron core increase the impedance of the
- se offiorescent tubes withac mains

 secause it reduces th was across th tube withut wastingnuclpwer.

 An ordinary resistor cannot be used instead of achk coil of the propose because it wastes pwer in th firm of that.



Question 7.23:

A power transmission line feeds input power at 2300 V to a stepdown transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary in order to get output power at 230 V?

Answer 7.23:

Input voltage, $V_1 = 2300$

Number of turns in primary coil, $n_1 = 4000$

Output voltage, $V_2 = 230 \text{ V}$

Number of turns in secondary $coil = n_2$

Voltage is related to the number of turns as:

$$\frac{V_1}{V_2} = \frac{n_1}{n_2}$$

$$\frac{2300}{230} = \frac{4000}{n_2}$$

$$n_2 = \frac{4000 \times 230}{2300} = 400$$

Hence, there are 400 turns in the second winding.

Question 7.24:

At a hydroelectric power plant, the water pressure head is at a height of 300 m and the water flow available is $100 \text{ m}^3 \text{ s}^{-1}$. If the turbine generator efficiency is 60%, estimate the electric power available from the plant (g = 9.8 m s^{-2}).

£Answer 7.24:

Height of water pressure head, h = 300 m

Volume of water flow per second, $V = 100 \text{ m}^3/\text{s}$





Efficiency of turbine generator, n = 60% = 0.6

Acceleration due to gravity, $g = 9.8 \text{ m/s}^2$

Density of water, $\rho = 10^3 \text{ kg/m}^3$

Electric power available from the plant = $\eta \times h\rho gV$

$$=0.6\times300\times10^3\times9.8\times100$$

- $= 176.4 \times 10^6 \text{ W}$
- $= 176.4 \, MW$

Ouestion 7.25:

A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is 0.5Ω per km. The town gets power from the line through a 4000220 V step-down transformer at a sub-station in the town.

- (a) Estimate the line power loss in the form of heat.
- (b) How much power must the plant supply, assuming there is negligible power loss due to leakage?
- (c) Characterise the step up transformer at the plant.

Answer 7.25:

voltage at which electric plant is generating power, V' = 440 V
Distance between the town and power generating station, d=15~km
Resistance of the two wire lines carrying power = $0.5~\Omega/\text{km}$



XII

Total resistance of the wires, $R = (15 + 15)0.5 = 15 \Omega$

A step-down transformer of rating 4000 - 220 V is used in the sub-station.

Input voltage, $V_1 = 4000 \text{ V}$

Output voltage, $V_2 = 220 \text{ V}$

rms current in the wire lines is given as:

$$I = \frac{P}{V_1}$$

$$= \frac{800 \times 10^3}{4000} = 200 \text{ A}$$

- (a) Line power loss = I^2R
- $=(200)^2 \times 15$
- $= 600 \times 10^3 \text{ W}$
- = 600 kW
- (b) Assuming that the power loss is negligible due to the leakage of the current:

Total power supplied by the plant = 800 kW + 600 kW

- = 1400 kW
- (c) Voltage drop in the power line = $IR = 200 \times 15 = 3000 \text{ V}$

Hence, total voltage transmitted from the plant = 3000 + 4000

= 7000 V

Also, the power generated is 440 V.

Millions and Statistics of the College of the Colle Hence, the rating of the step-up transformer situated at the power plant is 440 V - 7000 V.



Question 7.26:

Do the same exercise as above with the replacement of the earlier transformer by a 40,000-220 V step-down transformer (Neglect, as before, leakage losses though this may not be a good assumption any longer because of the very high voltage transmission involved). Hence, explain why high voltage transmission is preferred?

Answer 7.26:

The rating of a step-down transformer is 40000 V-220 V.

Input voltage, $V_1 = 40000 \text{ V}$

Output voltage, $V_2 = 220 \text{ V}$

Total electric power required, $P = 800 \text{ kW} = 800 \times 10^3 \text{ W}$

Source potential, V = 220 V

Voltage at which the electric plant generates power, V' = 440 V

Distance between the town and power generating station, d = 15 km

Resistance of the two wire lines carrying power = $0.5 \Omega/\text{km}$

Total resistance of the wire lines, $R = (15 + 15)0.5 = 15 \Omega$

$$P=V_1I$$

Millions are advactice Rms current in the wire line is given as:

$$=\frac{800\times10^3}{40000}=20\,\mathrm{A}$$

- (a) Line power loss = I^2R
- $=(20)^2 \times 15$
- = 6 kW

Million Stars Practice



https://millionstar.godaddysites.com/

(b) Assuming that the power loss is negligible due to the leakage of current.

Hence, power supplied by the plant = 800 kW + 6 kW = 806 kW

(c) Voltage drop in the power line = $IR = 20 \times 15 = 300 \text{ V}$

Hence, voltage that is transmitted by the power plant

$$=300 + 40000 = 40300 \text{ V}$$

The power is being generated in the plant at 440 V.

Hence, the rating of the step-up transformer needed at the

plant is 440 V - 40300 V.

Hence, power loss during transmission = $\frac{600}{1400} \times 100 = 42.8\%$

In the previous exercise, the power loss due to the same reason is

$$\frac{6}{806} \times 100 = 0.744\%$$

Since the power loss is less for a high voltage transmission, high voltage transmissions are preferred for this purpose.