

# "Alarm Circuit"

Independent Security

P. ~~Box 411BB, Rt. 1~~  
Pevely, Missouri 63070


2156 Second St.

Bill these are super simple circuits  
Very cheap but they work you can  
lay out an extensive perimeter very  
cheaply - once set off they latch and must  
be reset manually, but if one is always  
gone - so this should be no problem

Use Decent Switches NO Radio Shack Junk

use George Risk on Sentrakol Type  
Also micro switches

IN914 Diode Stops RF Falsing

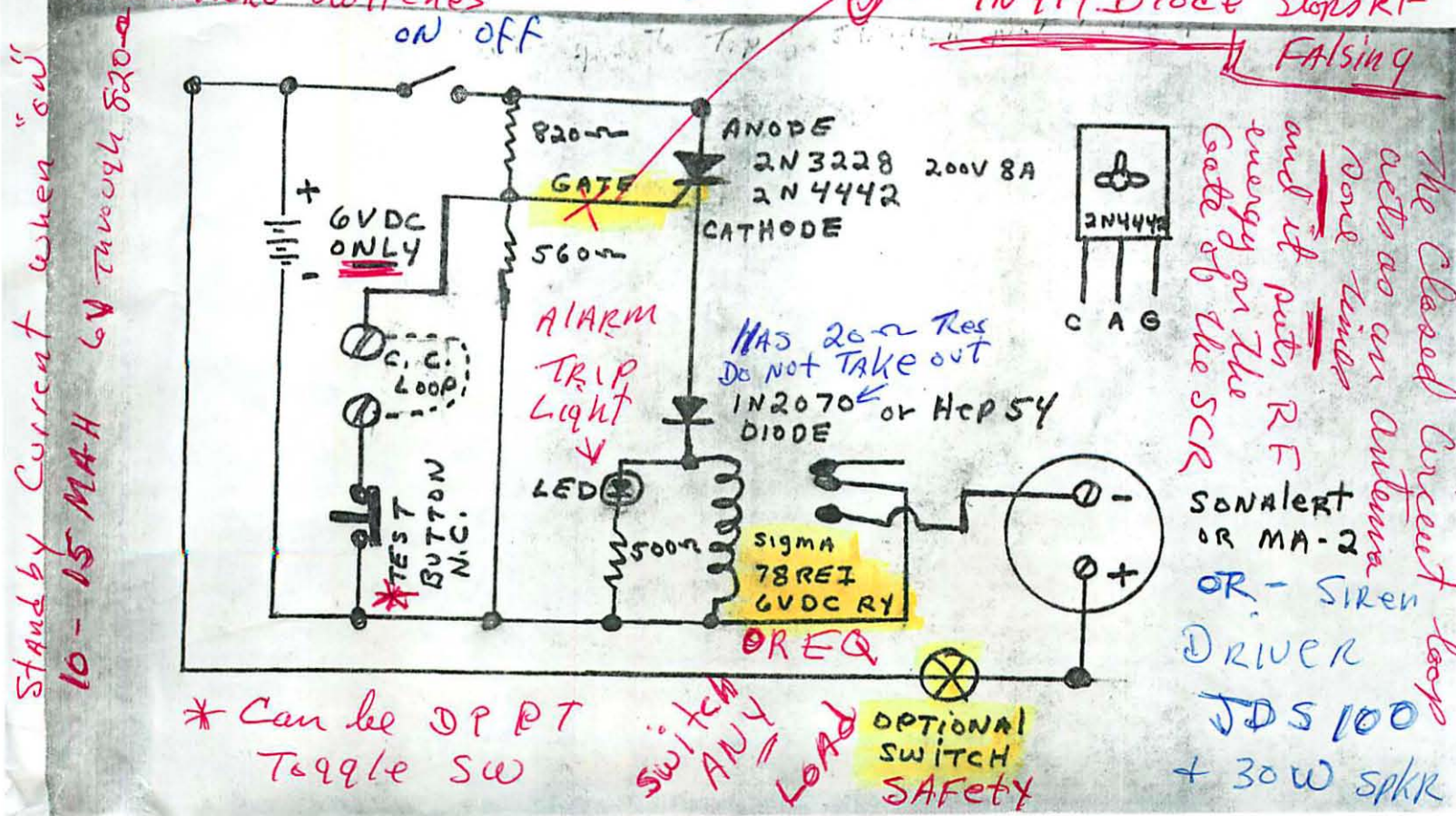

\* Can be DPDT Toggle SW

switch ANY LOAD

OPTIONAL SWITCH SAFETY

The Closed Current Loop acts as an antenna  
None times and it puts RF energy on the Gate of the SCR  
SONALERT OR MA-2  
OR - Siken DRIVER  
JDS 100 + 30W SPKR

