
Yellow 3 [HL only] [68 marks]

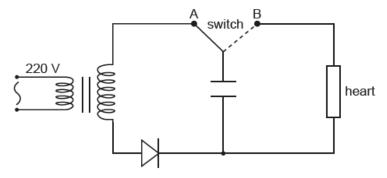A device sends an impulse of electrical energy to maintain a regular heartbeat in a person. The device is powered by an alternating current (ac) supply connected to a step-up transformer that charges a capacitor of capacitance 30 µF.



Expla A.	 10 1	OIC	 	 	 	 	11C V	VIIC	 10	J V V	icci	1 1	, u	- p	 -	<i>,</i> ,,,	L 2	 110


	primary coil.
1b.	Show that the maximum energy stored by the capacitor is about 160 J. [2 marks]
1c.	Calculate the maximum charge Q_0 stored in the capacitor. [1 mark]
1d.	Identify, using the label + on the diagram, the polarity of the capacitor. [1 mark]

The voltage across the primary coil of the transformer is 220 V. The number of turns on the secondary coil is 15 times greater than the number of turns on the


The	switch	is	moved	to	position	В.
	0111011				0001011	_

1e.	Describe what happens to the energy stored in the capacitor when the	[1 mark]
	switch is moved to position B	

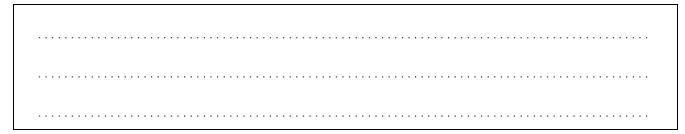
1f. Show that the charge remaining in the capacitor after a time equal to one [1 mark] time constant τ of the circuit will be 0.37 Q₀.



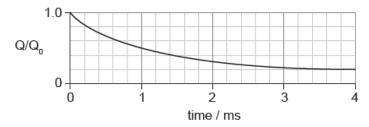1g. The graph shows the variation with time of the charge in the capacitor as[2 marks] it is being discharged through the heart.



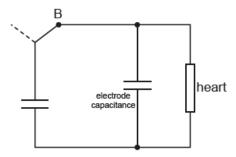
Determine the electrical resistance of the closed circuit with the switch in position B.



Explain the effect of the electrode capacitance on the discharge time.

A student makes a parallel-plate capacitor of capacitance 68 nF from aluminium foil and plastic film by inserting one sheet of plastic film between two sheets of aluminium foil.

diagram not to scale

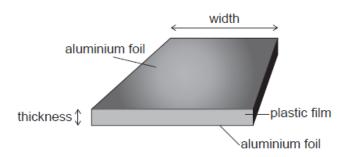


The aluminium foil and the plastic film are 450 mm wide.

The plastic film has a thickness of 55 μm and a permittivity of 2.5 \times 10^{-11} C^2 N^{-1} $m^{-2}.$

2a. Calculate the total length of aluminium foil that the student will require. [3 marks]

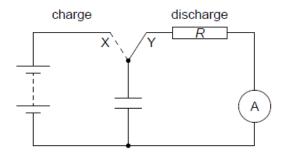The student uses a switch to charge and discharge the capacitor using the circuit shown. The ammeter is ideal.




The emf of the battery is 12 $\rm V.$

2c.	The resistor R in the circuit has a resistance of 1.2 k Ω . Calculate the time [3 marks]
	taken for the charge on the capacitor to fall to 50 % of its fully charged
	value.

ugge oil, tl	est one change to the discharge circuit, apart from changes to the [2 m hat will increase the maximum induced emf in the coil.

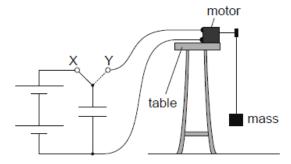A small electric motor is used with a 12 mF capacitor and a battery in a school experiment.



When the switch is connected to X, the capacitor is charged using the battery. When the switch is connected to Y, the capacitor fully discharges through the electric motor that raises a small mass.

	electric motor that raises a small mass.
3a.	The battery has an emf of $7.5\mathrm{V}$. Determine the charge that flows through $[1\ mark]$ the motor when the mass is raised.
h	The motor can transfer one-third of the electrical energy stored in the 12 marks
	The motor can transfer one-third of the electrical energy stored in the [2 marks] capacitor into gravitational potential energy of the mass. Determine the maximum height through which a mass of 45 g can be raised.
	capacitor into gravitational potential energy of the mass. Determine the
	capacitor into gravitational potential energy of the mass. Determine the
	capacitor into gravitational potential energy of the mass. Determine the
	capacitor into gravitational potential energy of the mass. Determine the
	capacitor into gravitational potential energy of the mass. Determine the
	maximum height through which a mass of 45 g can be raised.

A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm × 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm × 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm \times 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm \times 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm \times 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm \times 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
A capacitor consists of two parallel square plates separated by a vacuum. The plates are 2.5 cm \times 2.5 cm squares. The capacitance of the capacitor is 4.3 pF.
. Calculate the distance between the plates. [1 ma


4b. The capacitor is connected to a 16 V cell as shown.
diagram not to scale

[2	marks]
----	--------

	diagram not to scale
	pacitor 16V
	alculate the magnitude and the sign of the charge on plate A when the capacitor fully charged.
fil Ex	the capacitor is fully charged and the space between the plates is then [2 marks] led with a dielectric of permittivity $\varepsilon=3.0\varepsilon_0$. Explain whether the magnitude of the charge on plate A increases, decreases or easys constant.

4d. In a different circuit, a transformer is connected to an alternating current[3 marks] (ac) supply.
ac supply output voltage primary coil secondary coil
The transformer has 100 turns in the primary coil and 1200 turns in the secondary coil. The peak value of the voltage of the ac supply is 220 V. Determine the root
mean square (rms) value of the output voltage.
4e. Describe the use of transformers in electrical power distribution. [3 marks]

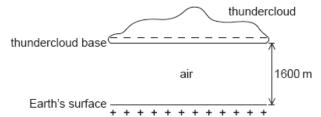A negatively charged thundercloud above the Earth's surface may be modelled by a parallel plate capacitor.



The lower plate of the capacitor is the Earth's surface and the upper plate is the base of the thundercloud.

The following data are available.

Area of thundercloud base	=	$1.2 imes 10^8 \mathrm{m}^3$
---------------------------	---	-------------------------------

Charge on thundercloud base = -25C

Distance of thundercloud base from Earth's surface = 1600m

Permittivity of air $= 8.8 \times 10^{-12} \text{Fm}^{-1}$

5a. Sho	w that	the ca	pacita	nce o	f this	arrang	gemen	nt is C	= 6.6	× 10	⁻⁷ F.	[.	1 mark]

5b. Calculate in V, the potential difference between the thundercloud and [2 marks] the Earth's surface.


. Calculate in J, the energy stored in the system.	[2 marks]
Lightning takes place when the capacitor discharges through th thundercloud and the Earth's surface. The time constant of the lightning strike lasts for 18 ms.	ne air between the system is 32 ms. A
l. Show that about -11 C of charge is delivered to the Earth's surf	ace. [3 marks]
e. Calculate, in A, the average current during the discharge.	[1 mark

5f. State one assumption that needs to be made so that the Earththundercloud system may be modelled by a parallel plate capacitor.
The electrical circuit shown is used to investigate the temperature change in a wire that is wrapped around a mercury-in-glass thermometer.
24 V
A power supply of emf (electromotive force) 24 V and of negligible internal resistance is connected to a capacitor and to a coil of resistance wire using an arrangement of two switches. Switch S_1 is closed and, a few seconds later, opened. Then switch S_2 is closed.
6a. The capacitance of the capacitor is 22 mF. Calculate the energy stored in [1 mark the capacitor when it is fully charged.


......

	pacitor to discharge through the resistance wire. Assume that the pacitor is completely discharged when the potential difference across it has len to 0.24 V.
is	e mass of the resistance wire is 0.61 g and its observed temperature [2 mage is 28 K. Estimate the specific heat capacity of the wire. Include an propriate unit for your answer.
is	e is 28 K. Estimate the specific heat capacity of the wire. Include an
is	e is 28 K. Estimate the specific heat capacity of the wire. Include an
is	e is 28 K. Estimate the specific heat capacity of the wire. Include an
is	e is 28 K. Estimate the specific heat capacity of the wire. Include an

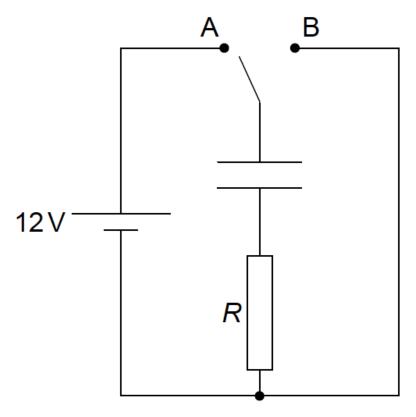An uncharged capacitor in a vacuum is connected to a cell of emf 12V and negligible internal resistance. A resistor of resistance R is also connected.



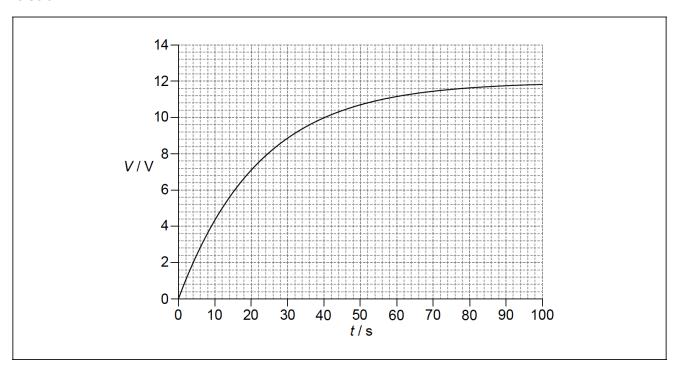At t=0 the switch is placed at position A. The graph shows the variation with time t of the voltage V across the capacitor. The capacitor has capacitance 4.5 μ F in a vacuum.



7a. On the axes, draw a graph to show the variation with time of the voltage [2 marks] across the resistor.

c. A dielectric material is now inserted between the plates of the fully charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.	ſ	(ii) Calculate the resistance <i>R</i> .
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
charged capacitor. State the effect, if any, on (i) the potential difference across the capacitor. (ii) the charge on one of the capacitor plates.		
(ii) the potential difference across the capacitor. (iii) the charge on one of the capacitor plates.		
(ii) the charge on one of the capacitor plates.		(i) the potential difference across the capacitor.
	ſ	
	_	

d.	(i) The permittivity of the dielectric material in (c) is twice that of a vacuum. Calculate the energy stored in the capacitor when it is fully charged.	[3 marks]
	(ii) The switch in the circuit is now moved to position B and the fully character discharges. Describe what happens to the energy in (d)(i).	arged

7d. (i) The permittivity of the dielectric material in (c) is twice that of a

© International Baccalaureate Organization 2022 International Baccalaureate® - Baccalauréat International® - Bachillerato Internacional®



Printed for CONCORDIAN INTL SCH THAILAND