



ACADEMIA SINICA
Institute of Astronomy and
Astrophysics

HARVARD-SMITHSONIAN
Center for Astrophysics





SMA Interferometry School

Basics of Analog Signal Processing & Transmission


March 15-19, 2021

Derek Kubo - ASIAA

What is an analog signal?

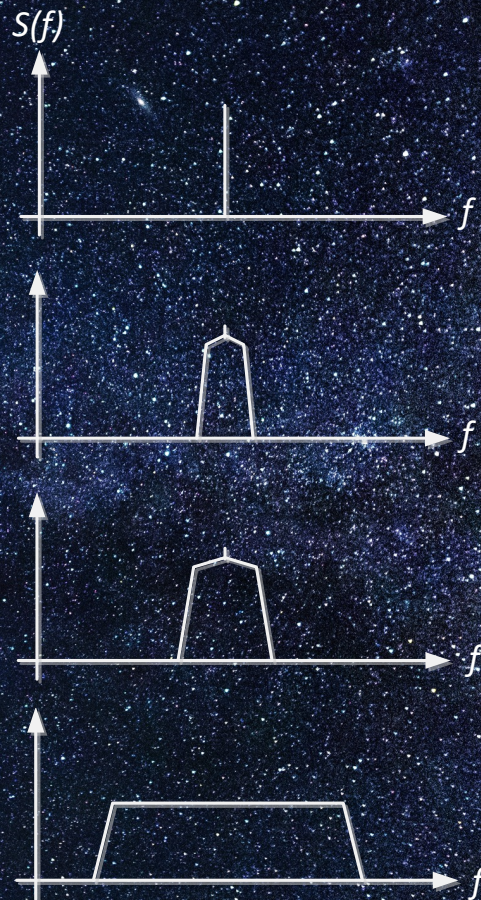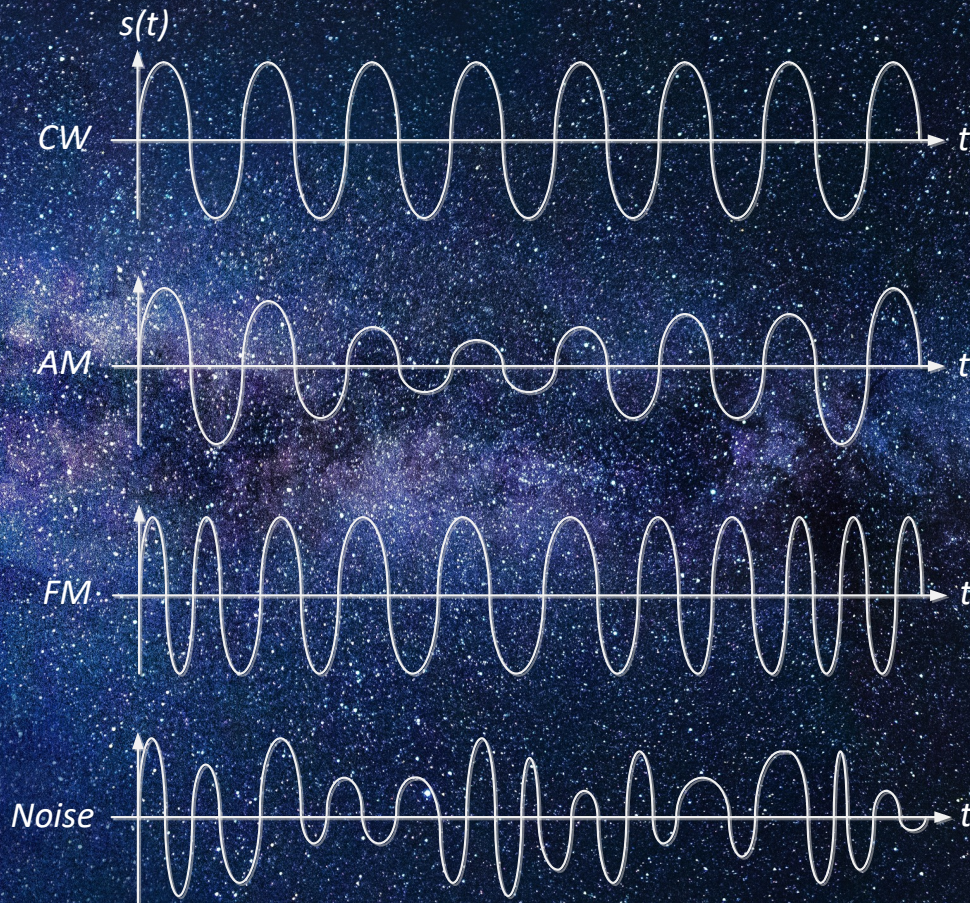

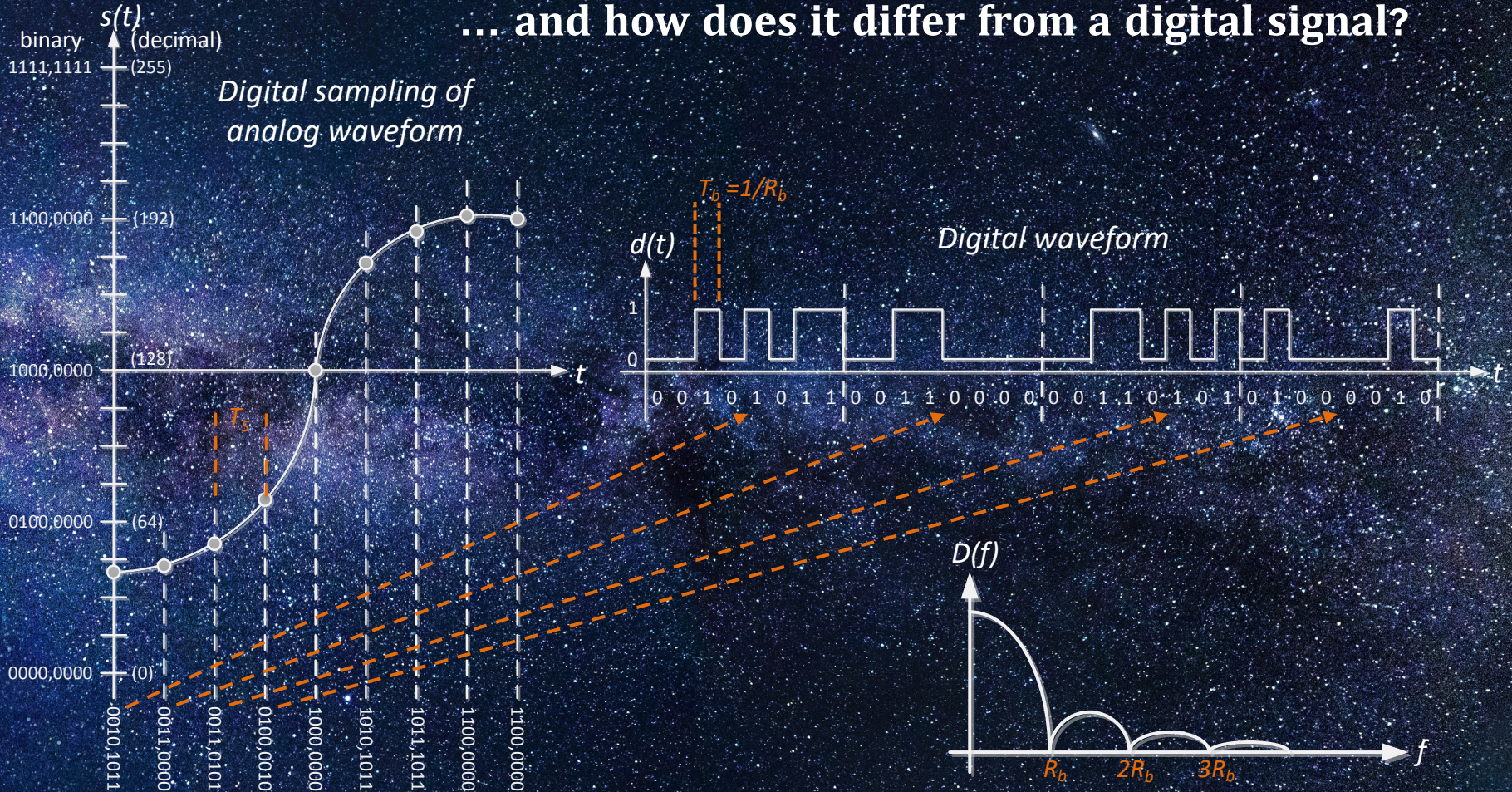... and how does it differ from a digital signal?





Why do we still use analog signal processing?

- The front-end of radio receivers utilize analog signal processing
 - Receiving antenna is usually followed by a combination of Low Noise Amplifier (LNA) and/or detector
 - Analog filtering and heterodyne frequency conversion to a common Intermediate Frequency (IF)
- Digitization is generally implemented as early as possible
 - Typically performed at IF but sometimes it is performed at RF for low frequency applications
- Radio Interferometer telescopes require the generation and distribution of a pure Local Oscillator (LO) from a central location to all of the antennas


Basic analog building blocks

- **Transmission line**

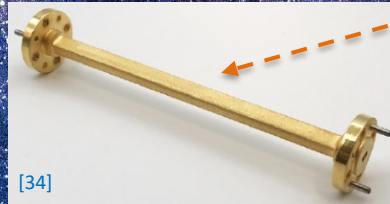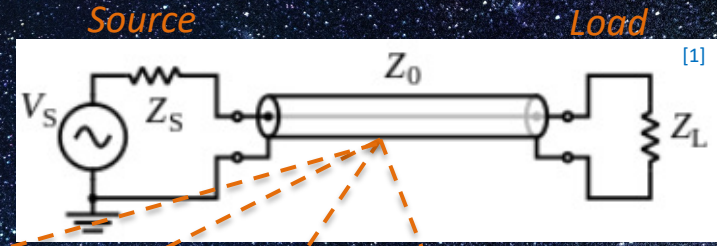- Characteristic impedance standardized to 50 Ohms
- Waveguide
- Coaxial cables




Straight waveguide
(75-110 GHz)

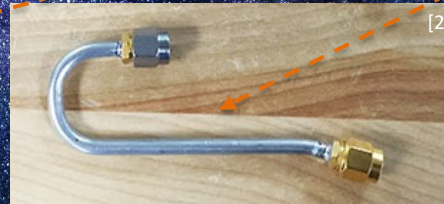

Semirigid coaxial cable
(0-18 GHz)





Flexible coaxial cable
(0-18 GHz)

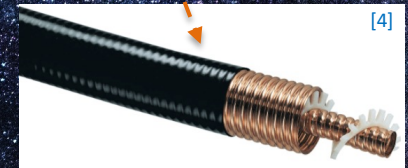


Heliax coaxial cable
(0-1 GHz)

Basic analog building blocks

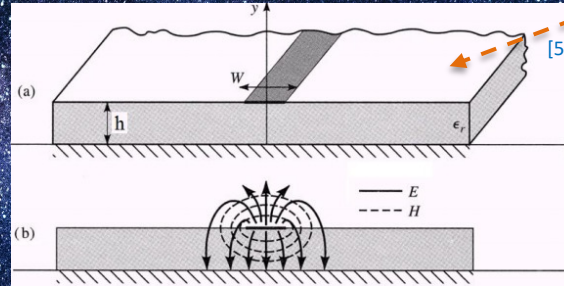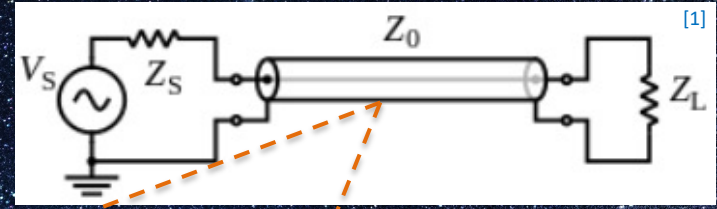- **Transmission line**
 - Circuit board transmission lines



Microstrip

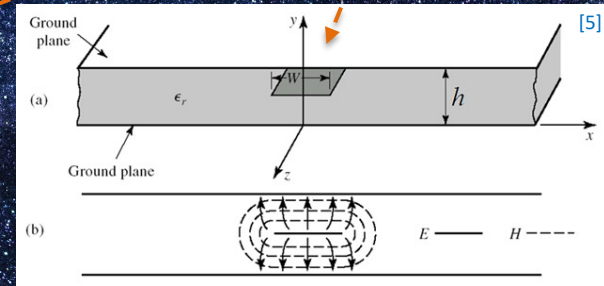


Stripline



Basic analog building blocks



- Transmission line and VSWR**

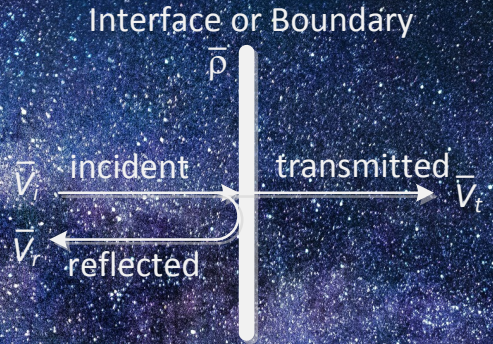

Voltage reflection coefficient $\rho = \bar{V}_r / \bar{V}_i$

Return Loss in dB = $20 * \text{Log}_{10}(\rho)$

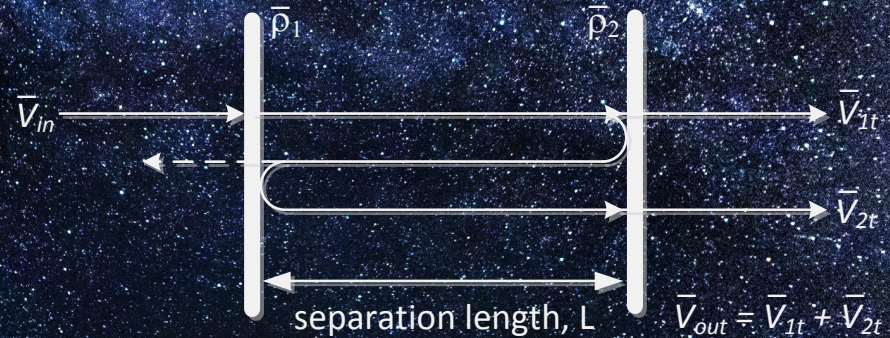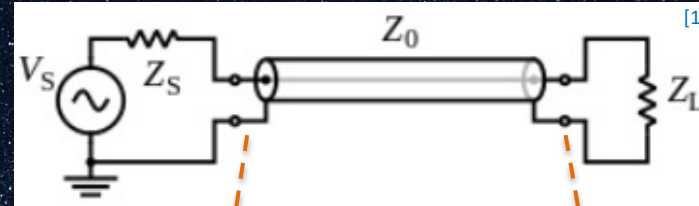Voltage Standing Wave Ratio = $(1 + \rho) / (1 - \rho)$





Basic analog building blocks

- **Transmission line and VSWR**

Interference pattern $f_{\text{ripple}} = \frac{c/\sqrt{\epsilon_r}}{2L}$

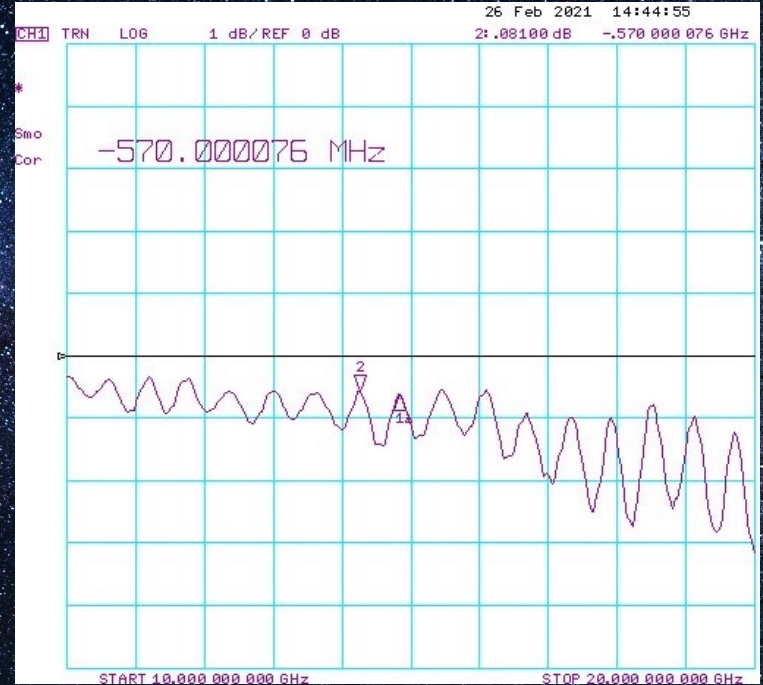
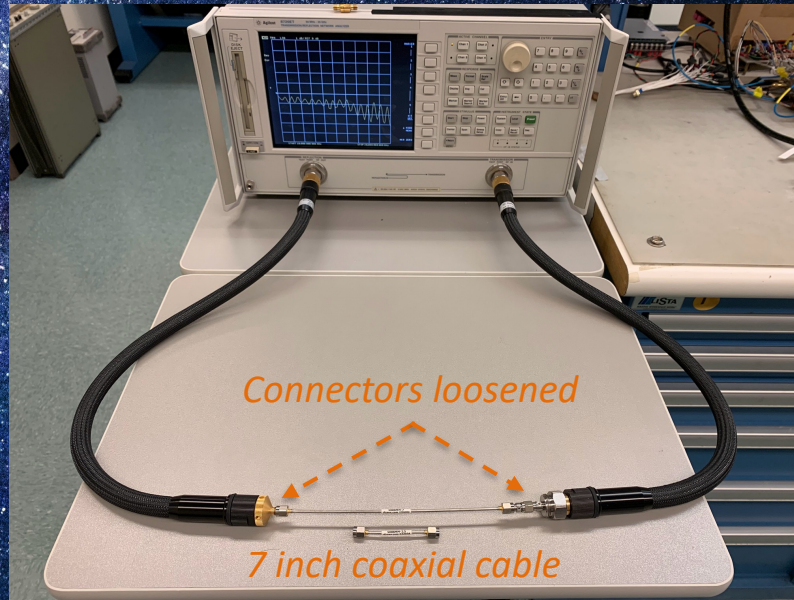
$$F_{\text{ripple}} = \frac{(3e8\text{m/s})(0.674)}{2*(0.178\text{m})} = 568 \text{ MHz}$$




Basic analog building blocks

- **Directional coupler**

- Sample fractional portion of a signal

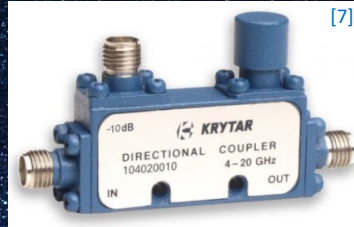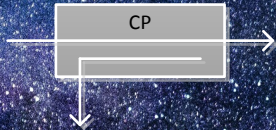


10 dB coupler
(4 - 20 GHz)

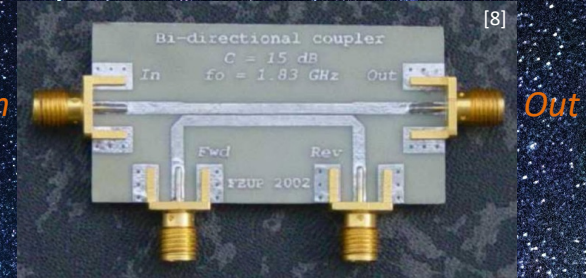


Forward coupled
Reverse coupled

- **Power divider**

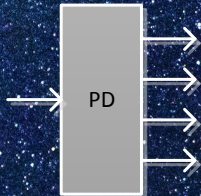- Divide signal N-ways
- Input to output loss $10 \cdot \log(N)$



2-way power divider
(1.7 - 9 GHz)



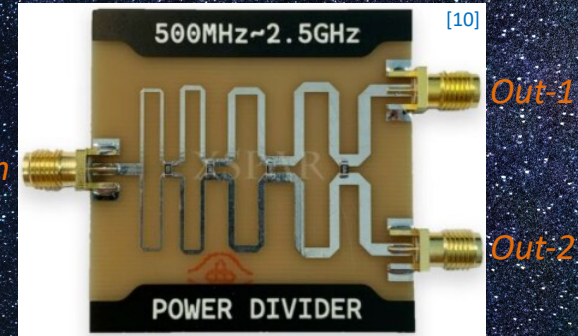


2-way power divider

Basic analog building blocks


• **90° hybrid coupler**

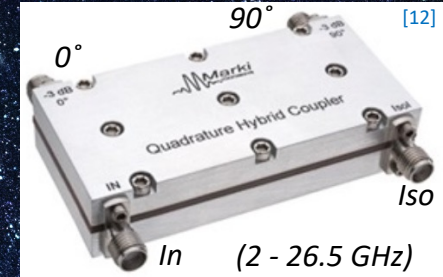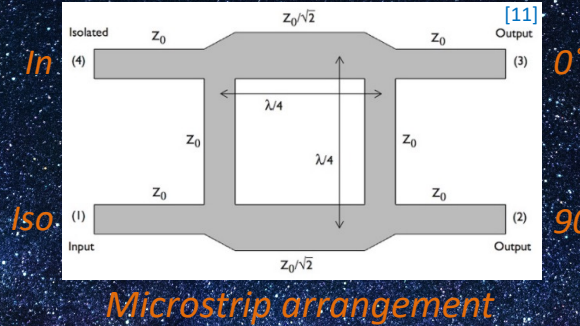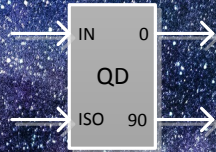- Divide signal into 0° and 90°
- I/Q modulator/demodulator
- I/Q down converter



• **Fixed attenuator**

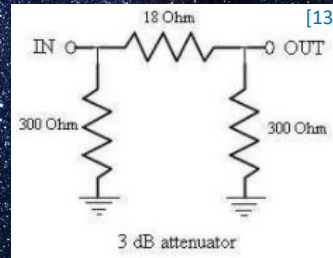- Signal level control
- Impedance matching



Resistive Pi circuit


(0 – 18 GHz)



(0 – 18 GHz)



Chip 3.12 x 3.73 mm

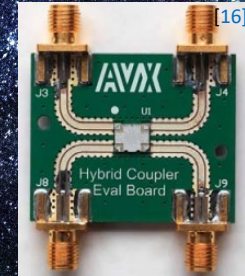


Chip mounted on Evaluation board (1.5 – 2.1 GHz)



Basic analog building blocks

• **Variable attenuator**

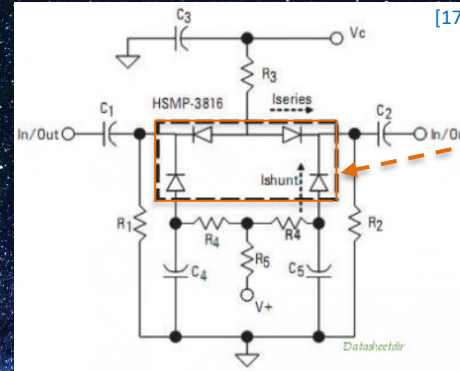- Variable signal power control
- Automatic level control (ALC)
- Amplitude/pulse modulation




PIN diodes (0 – 4 GHz)


PIN diode attenuator



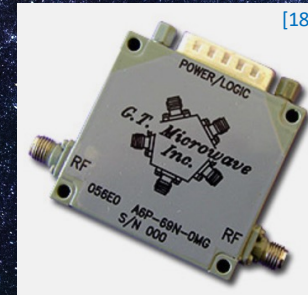*Manually controlled
W/G attenuator
(50-75 GHz)*



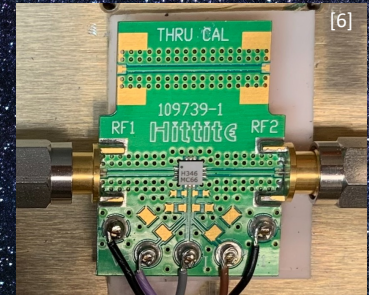*Digitally controlled
attenuator (2 - 18 GHz)*




*GaAs MMIC (0 – 18 GHz)
chip attenuator*



Basic analog building blocks

• Power detector

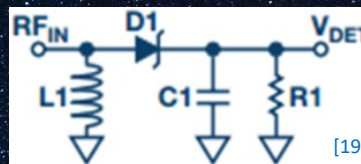
- Convert power to voltage for signal level measurement
- AM/pulse detector



Zero bias Schottky




DC Out
RF In (0.01 – 26.5 GHz)

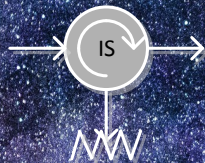

• Circulator

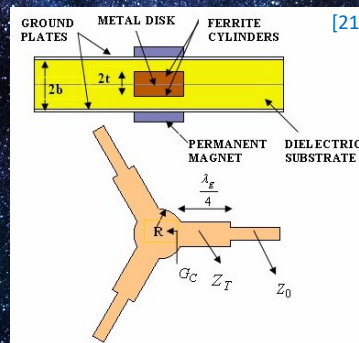- Port-1 → Port-2, Port-2 → Port-3, Port-3 → Port-1
- Low loss & high reverse isolation
- Isolate mismatches between components
- Separation of bidirectional signals



Internal configuration



Surface mount




(6 – 18 GHz)

Basic analog building blocks




• Filter

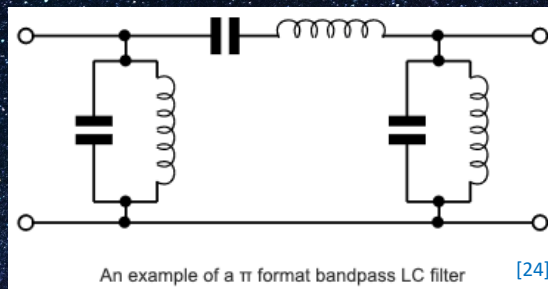
- Low-pass, high-pass, band-pass
- Band-stop, notch




Schematic of 3rd order BPF

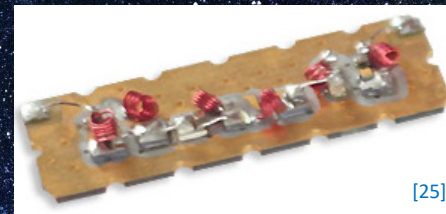


Lumped Element

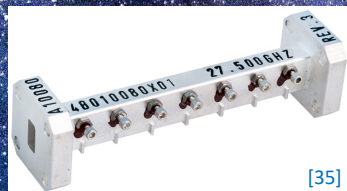


*W/G cavity
(27.325 – 27.675 GHz)*

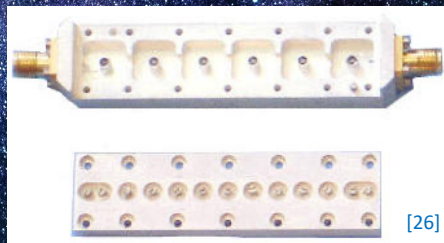

Cavity

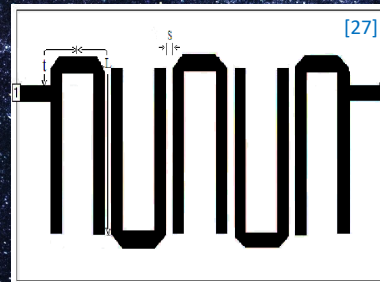

Coupled line hairpin

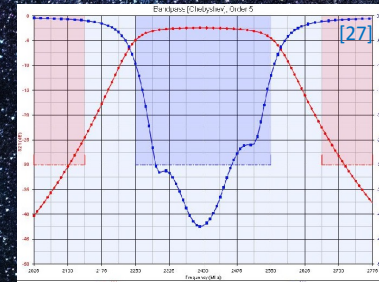


*Filter response
(-3 dB at 2250 and 2550)*

Basic analog building blocks




• Mixer

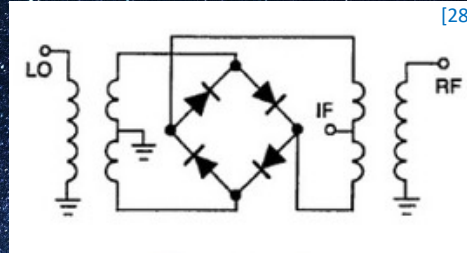- Frequency translation, up or down conversion
- Data modulation, demodulation
- Frequency multiplication



Schematic of double balanced mixer

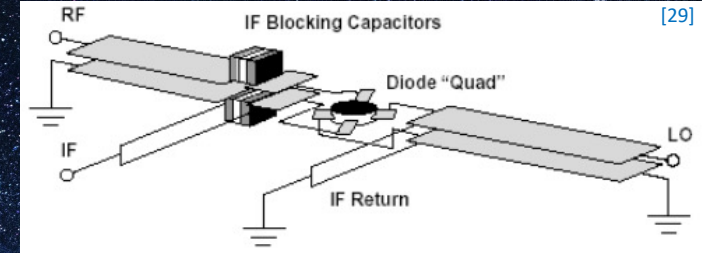


Typical layout of double balanced mixer



*W/G mixer
(RF/LO 75 – 110 GHz,
IF 0.1 – 35 GHz)*



Packaged mixer

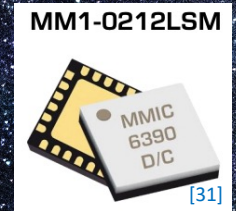

*Active GaAs
MMIC mixer
(RF/LO 2 – 12 GHz,
IF 0 – 3 GHz)*

Basic analog building blocks




• Amplifier

- Frequency
- Gain and flatness
- Noise figure
- Linearity
- Match




[38]

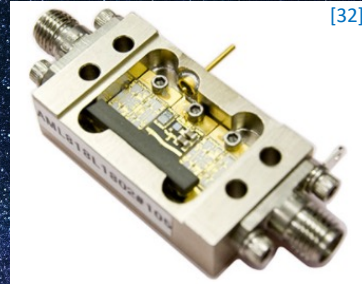65 – 115 GHz
gain 23 dB
flatness +/- 3 dB
NF 0.4 dB
P1dBc - dBm
VSWR 3.6:1, 2.5:1




[32]

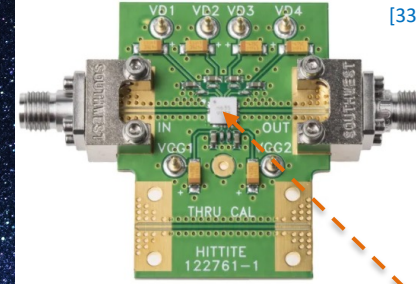1 – 8 GHz
gain 30 dB
flatness +/- 2 dB
NF 1.8 dB
P1dBc +13 dBm
VSWR 1.8:1



[33]

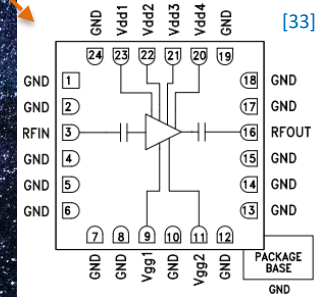18 - 36 GHz
gain 18 dB
flatness +/- 1 dB
NF 7 dB
P1dBc +22 dBm
VSWR 1.6:1, 1.9:1




[33]


Basic analog building blocks

- **Local Oscillator**

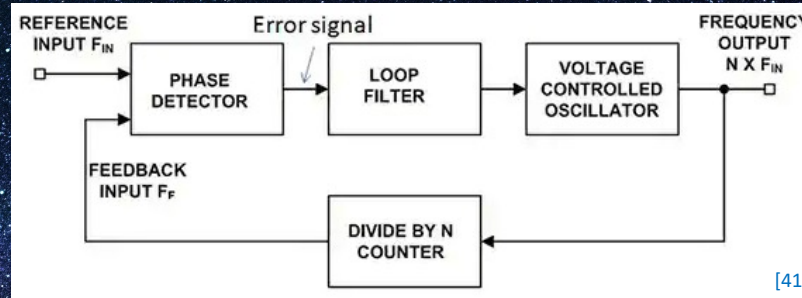- Synthesize sinusoid waveform
- Phase lock loop (PLL)




[41]

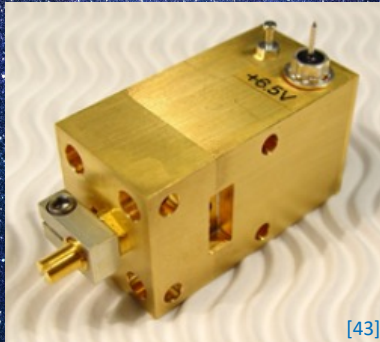


[43]



[42]

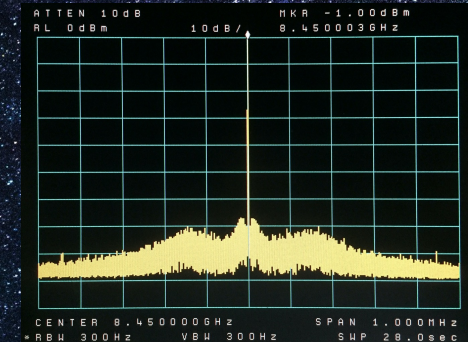


Basic analog building blocks

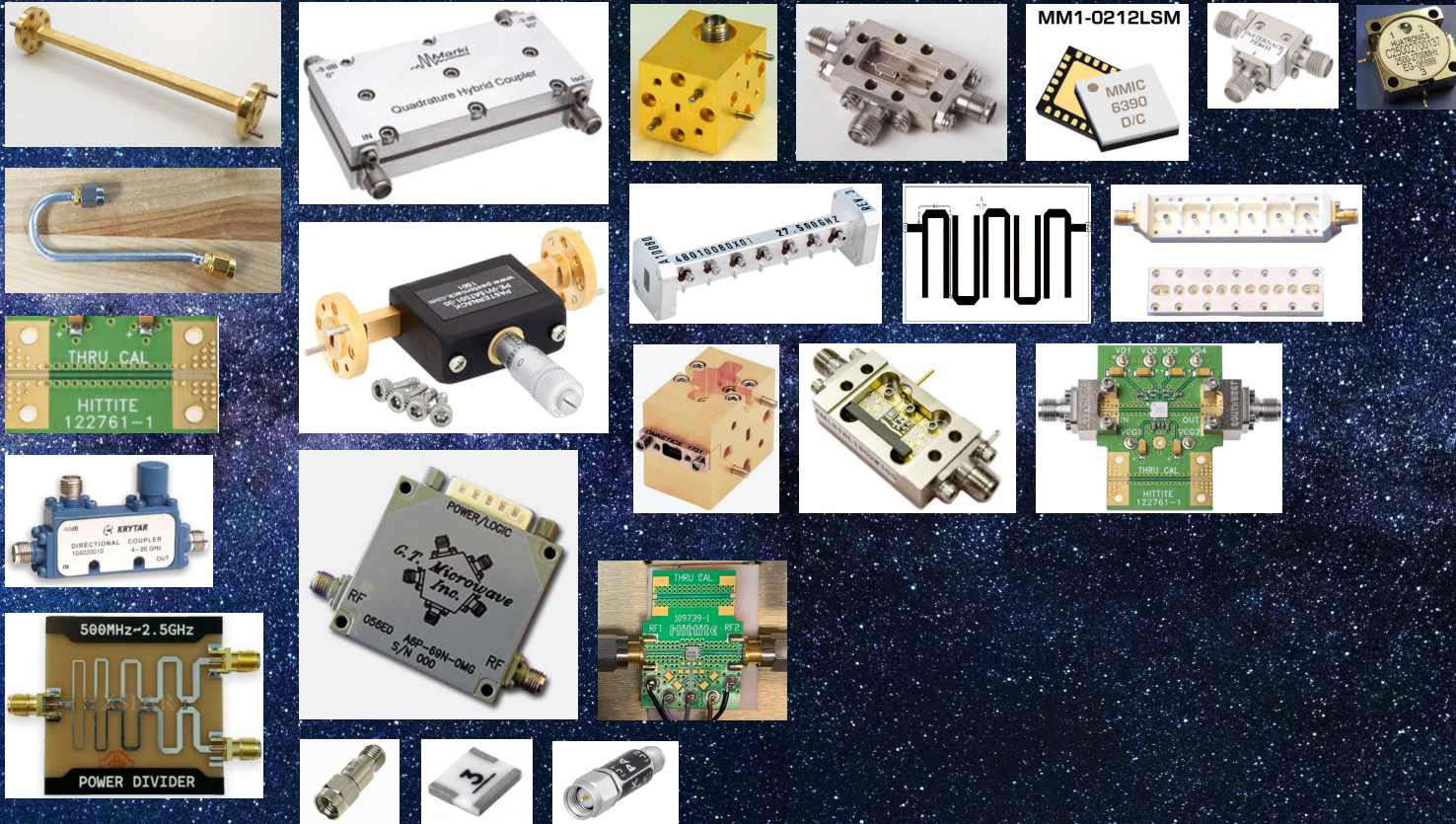



Cryogenic receiver

- 86 – 102 GHz receiver for YTLA project

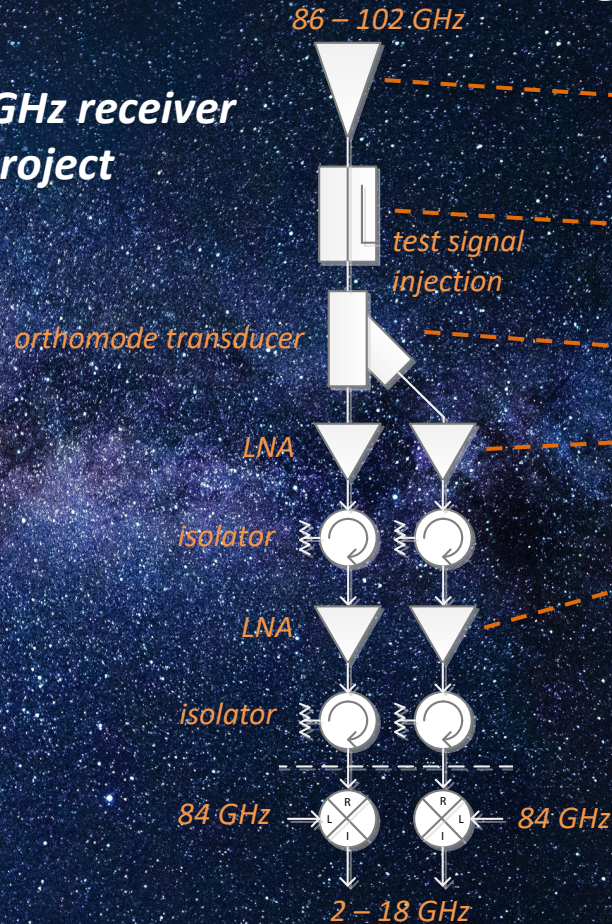

Transmission of IF signal from antenna



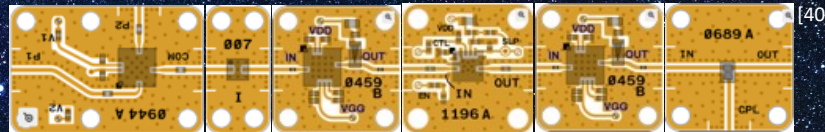
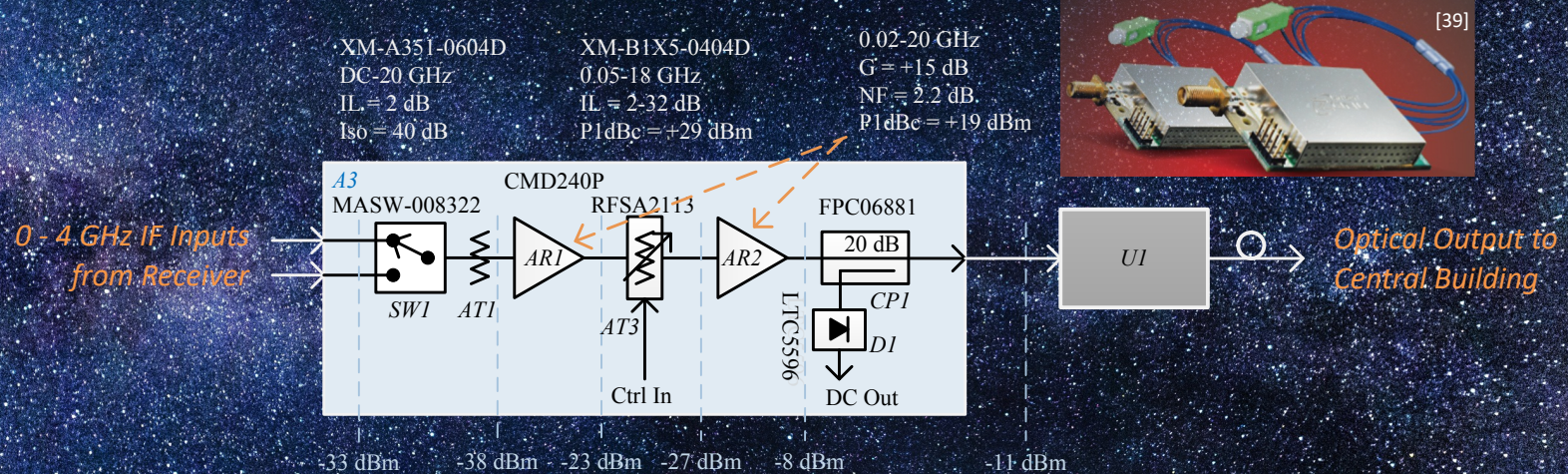
- SMA design concept for transmission of 0 – 4 GHz IF Signal from antenna to central building**



Individual microwave drop-in components




Frequency translation from IF to baseband

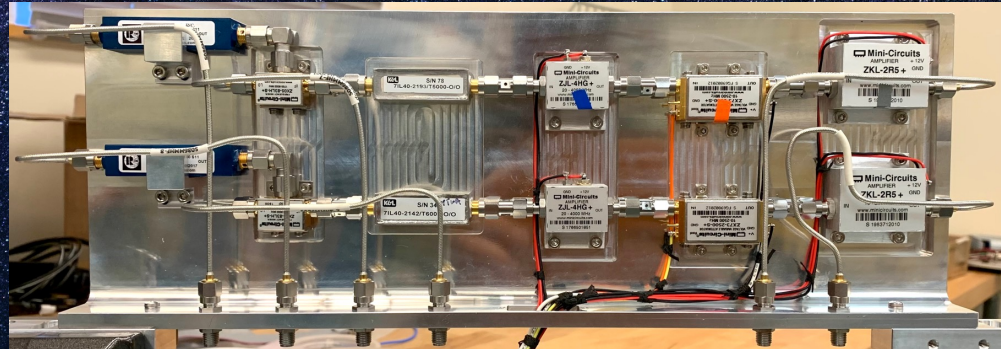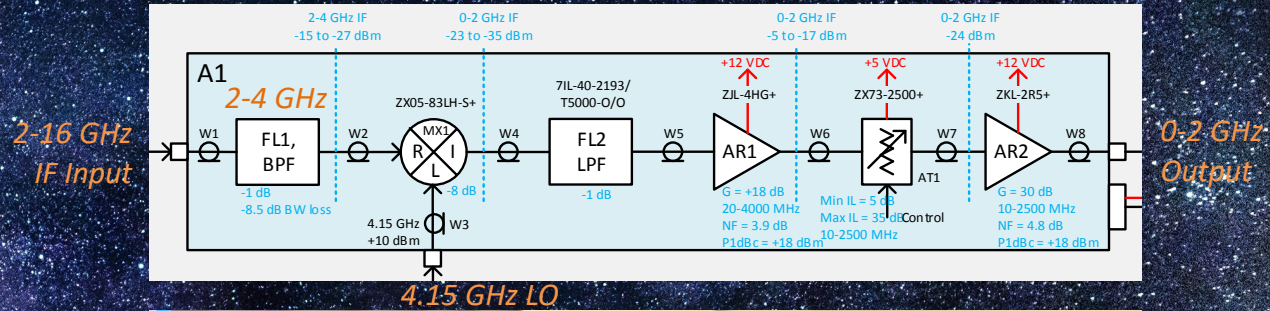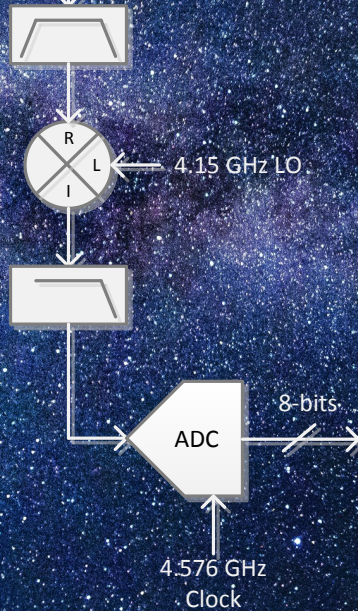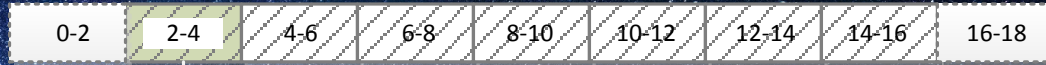- **Block Down Converter for SMA project**



Frequency translation from IF to baseband

- Block Down Converter**

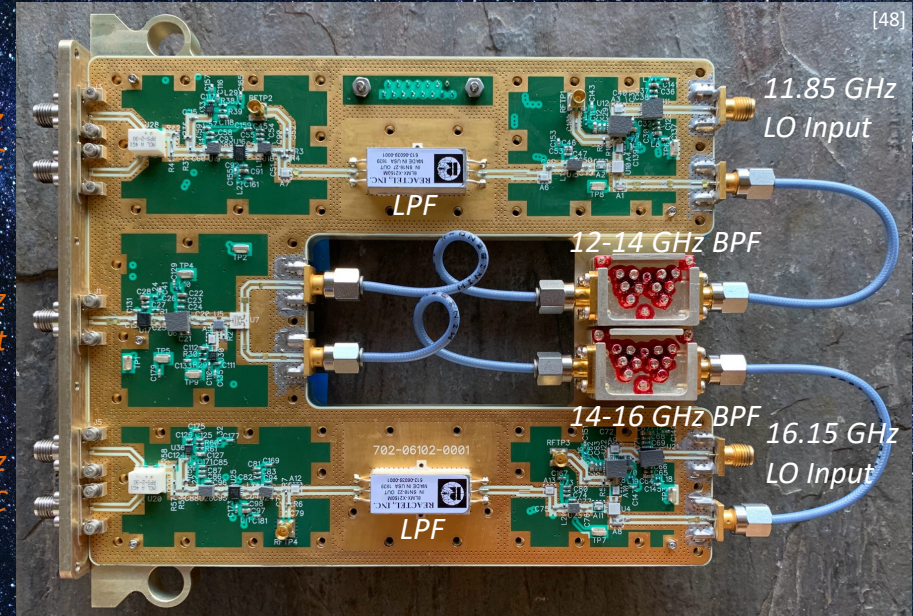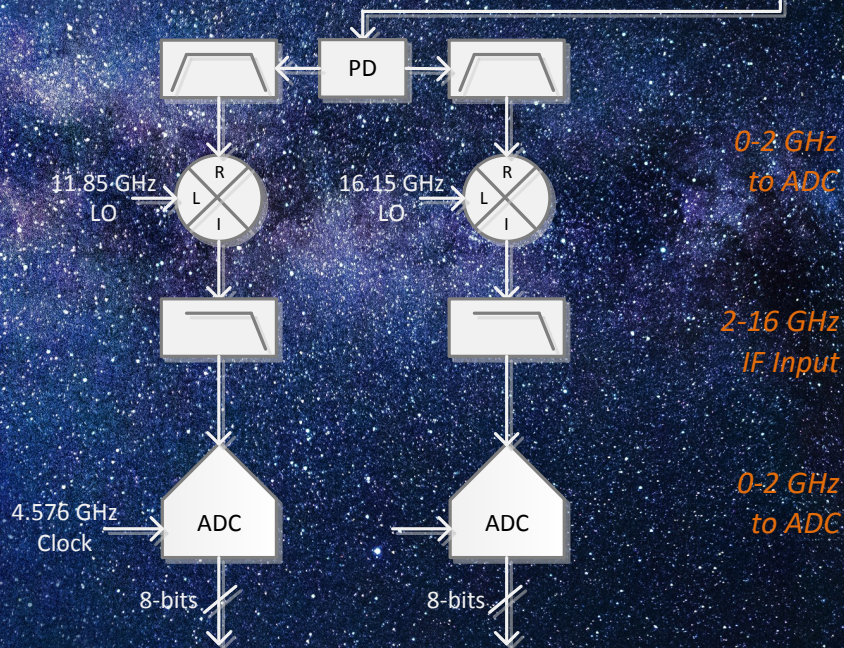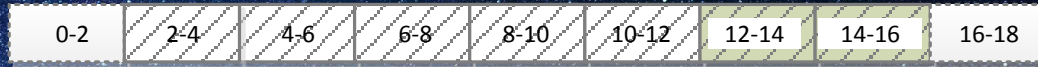


Transmission of LO to antenna

- **Transmission of 18 – 32 GHz LO Signal from central building to antenna, GLT project**

Fiber optics to antenna — — — — — →





Optical LO transmitter — — — — — →

Low phase noise synthesizer — — — — — →

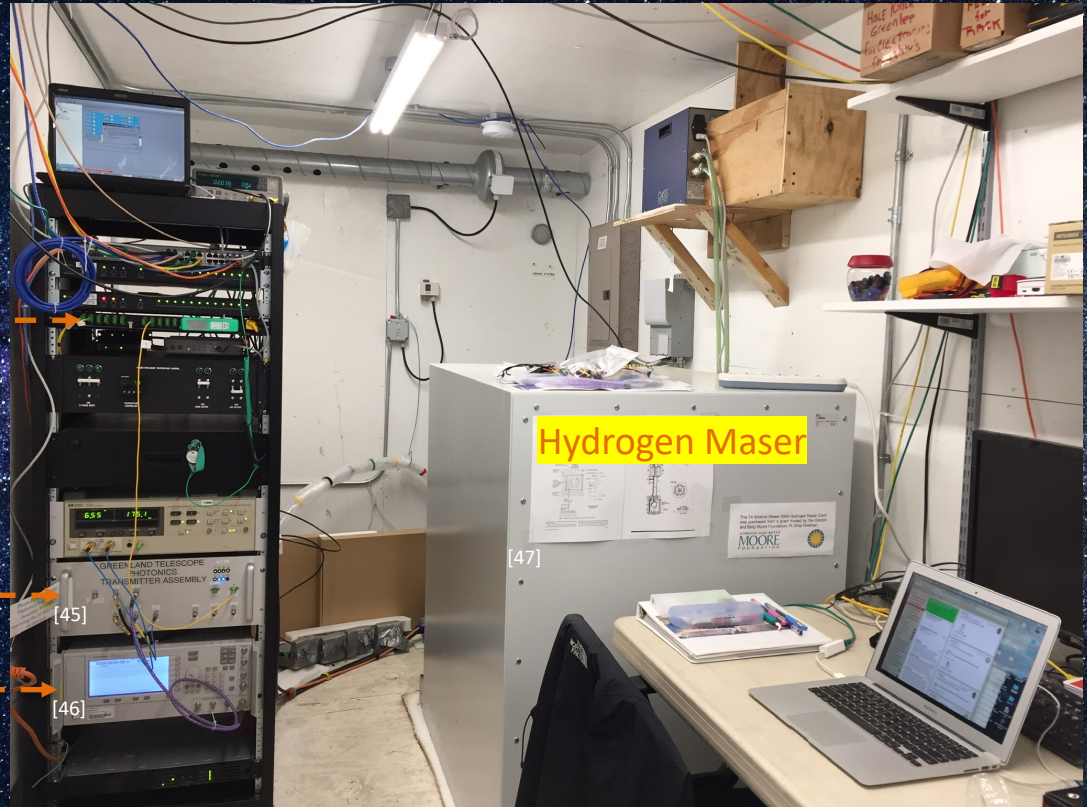

Reception of L0 in antenna

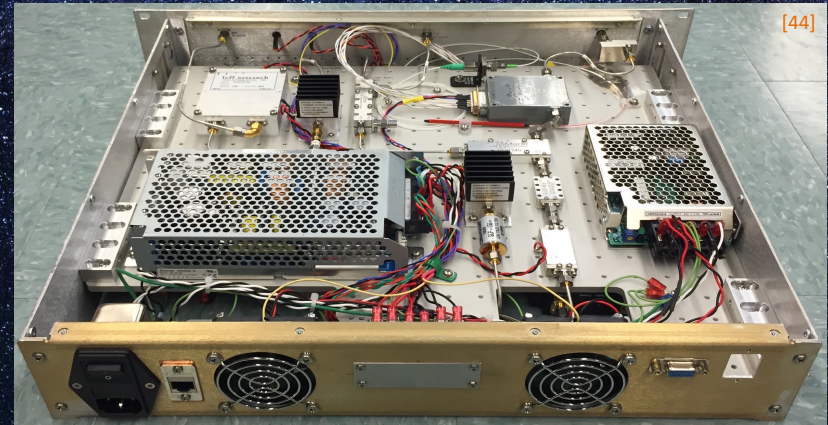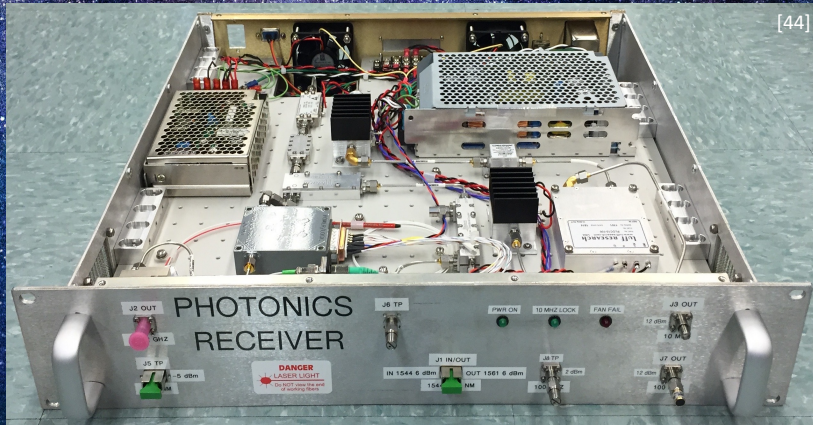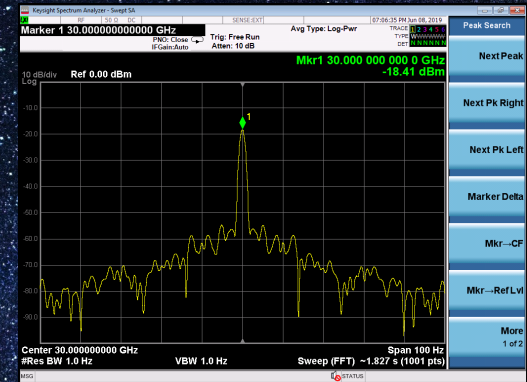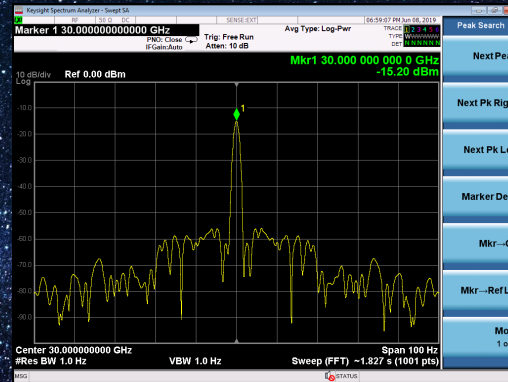- **Reception of 18 – 32 GHz LO signal in antenna, GLT project**



References

Image sources and references:

- [1] <https://www.pngegg.com/en/png-pb1lr>
- [2] <https://www.santron.com/blog/index.cfm/2015/3/26/SemiRigid-Cable-Assemblies-Still-Alive-and-Well>
- [3] <https://www.centricrf.com/cable-assemblies/sma-cable-assemblies/>
- [4] <https://www.dielectric.com/trans-lines/hj9-50/>
- [5] Skaik, Talal, EELE 3332 lecture, 2013, <http://site.iugaza.edu.ps/tskaik/files/Microstrip.pdf>
- [6] <https://www.analog.com/media/en/technical-documentation/data-sheets/hmc346lc3b.pdf>
- [7] <https://krytar.com/products/couplers/directional-couplers/directional-coupler-104020010/>
- [8] <http://www.ittc.ku.edu/~jstiles/723/handouts/The%20Directional%20Coupler.pdf>
- [9] <https://www.bsbaytech.com/product-catagory/power-splitter-divider/>
- [10] <https://www.ebay.com/itm/283986682223>
- [11] <https://www.comsol.com/blogs/modeling-branch-line-coupler/>
- [12] <https://www.markimicrowave.com/hybrids/qh-0226.aspx>
- [13] <https://www.rfwireless-world.com/Vendors/rf-attenuator.html>
- [14] <https://www.everythingrf.com/browse/rf-attenuators>
- [15] <https://www.everythingrf.com/product-datasheet/29-194-ts0300w3>
- [16] <https://www.modelithics.com/models/Vendor/AVX/PC2025A2100.pdf>
- [17] <https://www.mwrf.com/technologies/semiconductors/article/21846368/diode-quad-is-foundation-for-pin-diode-attenuator>
- [18] http://www.gtmicrowave.com/Index.php?option=com_content&view=article&id=23:digitally-controlled-attenuators&catid=12&Itemid=111
- [19] <https://www.analog.com/en/technical-articles/integrated-diode-based-rf-detectors.html>
- [20] <https://www.pasternack.com/images/ProductPDF/PE8014.pdf>
- [21] https://www.scrip.org/html/3-9801086_2766.htm
- [22] <http://www.globalmarket.com/product-info/gull-wing-tab-smt-circulator-for-td-lte-wimax-2795891.html>
- [23] <https://www.pasternack.com/50-ohm-sma-isolator-8000-mhz-18000-mhz-20-watts-16-db-pe8304-p.aspx>
- [24] http://www.pro-line.co.kr/default/LC_Filters/ST_Band_Pass.php?sub=23
- [25] http://www.orionmicrowave.com/filter_cavity.htm
- [26] http://www.orionmicrowave.com/filter_cavity.htm
- [27] <https://www.semanticscholar.org/paper/Design-of-microstrip-tapped-hairpin-dual-band-pass-Yang-Xiong/bb0e2b7b5197c86974b767382e0913de639e1437>
- [28] <https://www.rfwireless-world.com/Terminology/single-balanced-mixer-vs-double-balanced-mixer-vs-triple-balanced-mixer.html>

References

Image sources and references:

- [29] <https://www.edn.com/harmonic-balance-simulation-speeds-rf-mixer-design-2/>
- [30] <https://www.conet.in/index.php/r-f-microwave-accessories>
- [31] <https://www.markimicrowave.com/Assets/datasheets/MM1-0212LSM.pdf?v=051820>
- [32] <https://www.mrcy.com/products/rf-and-mixed-signal/rf-amplifiers/low-noise-amplifiers>
- [33] <https://docs.rs-online.com/bff1/0900766b8152ac6c.pdf>
- [34] <https://quantummicrowave.com/wp-content/uploads/2020/10/Quantum-Microwave-QMC-WGS10-0400AU.pdf>
- [35] <https://www.surplussales.com/rf/RFWaveG-14.html>
- [36] <https://www.smithsinterconnect.com/products/multi-fuction-rf-systems/mixers-and-detectors/>
- [37] <https://www.pasternack.com/images/ProductPDF/PE-W15AT001-30.pdf>
- [38] https://www.lownoisefactory.com/files/8315/3624/7640/LNF-LNC65_115WB.pdf
- [39] <https://www.opticalzonu.com/modules/oz516/>
- [40] <https://www.xmicrowave.com/product-category/x-mwblocks/>
- [41] <https://www.digikey.ch/en/articles/integrated-phase-locked-loops-offer-higher-frequency-performance-enhanced-user-benefits>
- [42] [https://www.pasternack.com/pages/rf-microwave-and-millimeter-wave-products/phase-locked-oscillators-\(plo\)-with-external-references.html?utm_source=everythingRF](https://www.pasternack.com/pages/rf-microwave-and-millimeter-wave-products/phase-locked-oscillators-(plo)-with-external-references.html?utm_source=everythingRF)
- [43] <https://www.spaceklabs.com/categories/millimeter-wave-gunn-oscillators>
- [44] <https://www.asiaa.sinica.edu.tw/gallery/show.php?i=9bc513515828624144d267ed0cbee5e8>
- [45] <https://www.asiaa.sinica.edu.tw/gallery/show.php?i=48711039449b9de38c76d1438c8846f0>
- [46] <https://www.keysight.com/en/pdx-x202237-pn-E8257D/psg-analog-signal-generator-100-khz-to-67-ghz?nid=32488.1150403&cc=US&lc=eng>
- [47] <https://www.t4science.com/products/imaser3000/>
- [48] <https://nordengroup.com/>