

Exam questions:

1. A system is monitored using sensors. The sensors output binary values corresponding to physical conditions, as shown in the table:

Parameter	Description of parameter	Binary value	Description of condition
P	oil pressure	1	pressure $\geq$ 3 bar
		0	pressure $<$ 3 bar
T	temperature	1	temperature $\geq$ 200°C
		0	temperature $<$ 200°C
R	rotation	1	rotation $\leq$ 1000 revs per minute (rpm)
		0	rotation $>$ 1000 revs per minute (rpm)

The outputs of the sensors form the inputs to a logic circuit. The output from the circuit, X, is 1 if any of the following three conditions occur:

either oil pressure $\geq$ 3 bar **and** temperature $\geq$ 200°C
or oil pressure $<$ 3 bar **and** rotation $>$ 1000 rpm
or temperature $\geq$ 200°C **and** rotation $>$ 1000 rpm

(a) Draw a logic circuit to represent the above system.



[5]

(b) Complete the truth table for this system.

P	T	R	Workspace	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

9608/13/M/J/18


2 A student needs to design a logic circuit to model the requirements for membership of a snooker club. Membership (X) depends on four criteria, as shown in the table:

Parameter	Description of parameter	Binary value	Condition
A	Over 18	1	True
		0	False
B	Recommended	1	True
		0	False
C	Full-time	1	True
		0	False
D	Retired	1	True
		0	False

Membership is approved ($X = 1$) if the person:

- is over the age of 18 and has been recommended by a pre-existing member and
- either is working full-time or is retired, but not both.

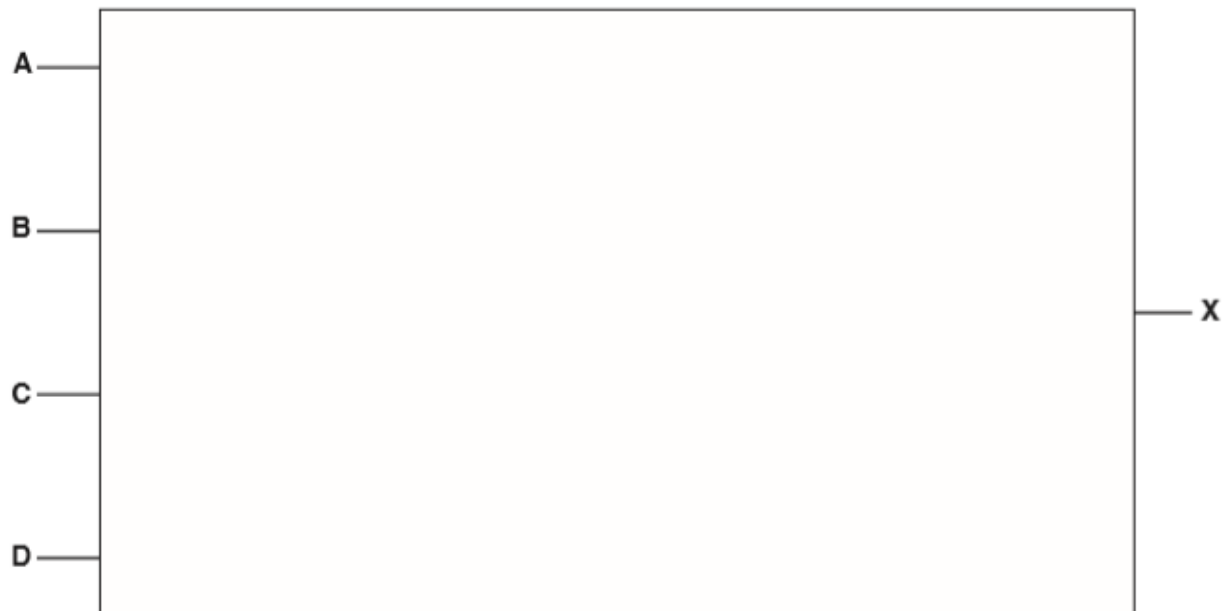Draw a logic circuit to represent the membership requirements.



[3]

9608/11/M/J/18

3 An alarm system (X) is enabled and disabled using either a switch (A) or a remote control (B). There are two infra-red sensors (C, D) and one door pressure sensor (E).

Parameter	Description of parameter	Binary value	Condition
A	Switch	1	Switch enabled
		0	Switch disabled
B	Remote control	1	Remote enabled
		0	Remote disabled
C	Infra-red sensor	1	Activated
		0	Not activated
D	Infra-red sensor	1	Activated
		0	Not activated
E	Door pressure sensor	1	Activated
		0	Not activated

The alarm sounds ($X = 1$) if the alarm is enabled and any one or more of the sensors is activated. Draw a logic circuit to represent the alarm system.



[3]

- 4 A safety monitoring system uses three inputs S, T and G. These inputs are used in a logic circuit which produces an output value, X.

The description of each input is shown in the table.

Parameter	Description	Binary value	Conditions
S	sound level	1	sound level ≥ 90 dB
		0	sound level < 90 dB
T	temperature	1	temperature $\geq 35^{\circ}\text{C}$
		0	temperature $< 35^{\circ}\text{C}$
G	oxygen level	1	oxygen level $\geq 75\%$
		0	oxygen level $< 75\%$

X has the value 1, if:

either sound level ≥ 90 dB **and** temperature $\geq 35^{\circ}\text{C}$

or temperature $\geq 35^{\circ}\text{C}$ **and** oxygen level $< 75\%$

or sound level < 90 dB **and** oxygen level $\geq 75\%$

(a) Draw a logic circuit to represent the above safety system.




[7]

(b) Complete the truth table for this safety system

Inputs			Working space	Output
S	T	G		X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[4]

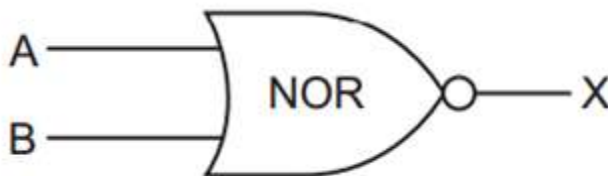
5 (a) Complete the truth table to show the output from the logic gate shown



A	B	X
0	0	
0	1	
1	0	
1	1	

[2]

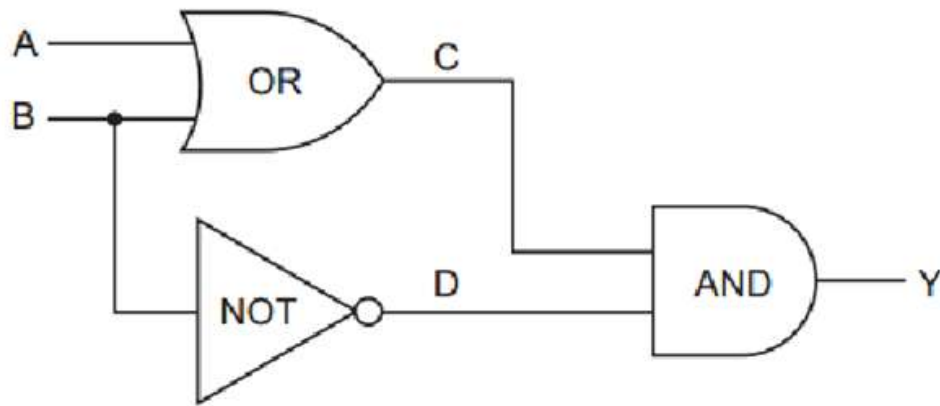(b) Complete the truth table to show the outputs from the logic circuit shown.




A	B	C	D	Y
0	0			
0	1			
1	0			
1	1			

[4]

6(a)

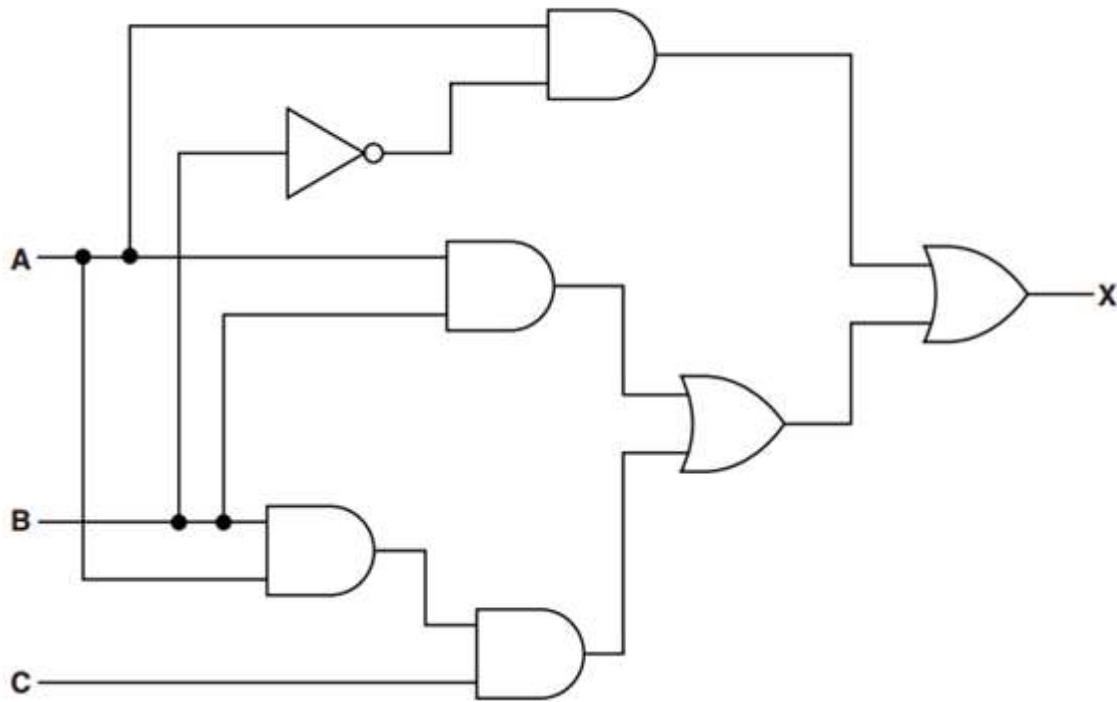
(a) A student, in an electronics lesson, built the following circuit.



Inputs			Working space	Output
A	B	C		X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


[4]

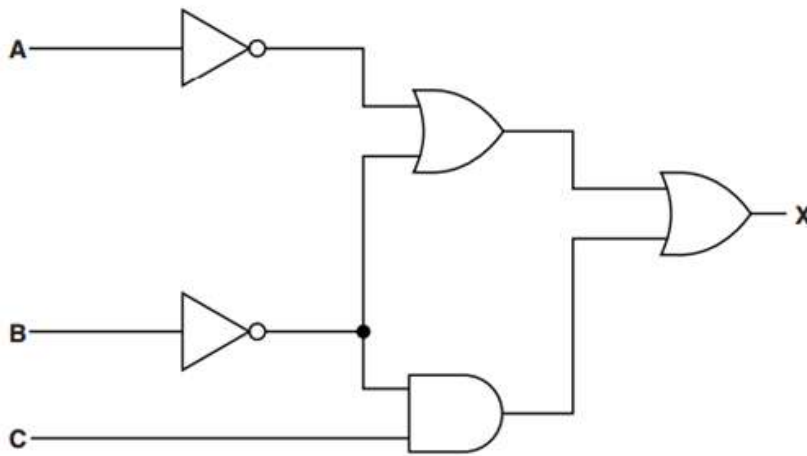(b) Write a logic expression to represent the following logic circuit.



.....
.....
..... [3]

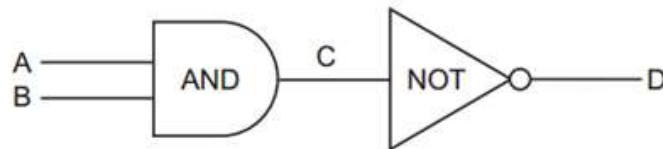(c) Complete the truth table for logic circuit.




A	B	C	D
0	0		
0	1		
1	0		
1	1		

[1]

(d) State a single logic gate to replace the above circuit in part (c)

..... [1]

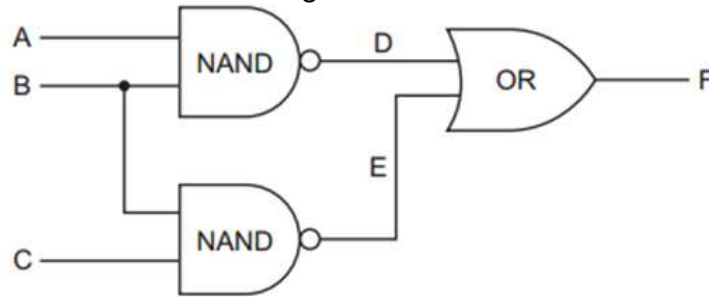7. (a) Complete the truth table for this logic circuit



A	B	C	D	E	F
0	0	0			
0	0	1			
0	1	0			
0	1	1			

[4]

(b) The following logic statements define the light sequence



$R = 1$ IF (A is NOT 1)




$G = 1$ IF (B is 1 AND C is 1)



$Y = 1$ IF (A is 1 AND NOT(B is 1 AND C is 1))

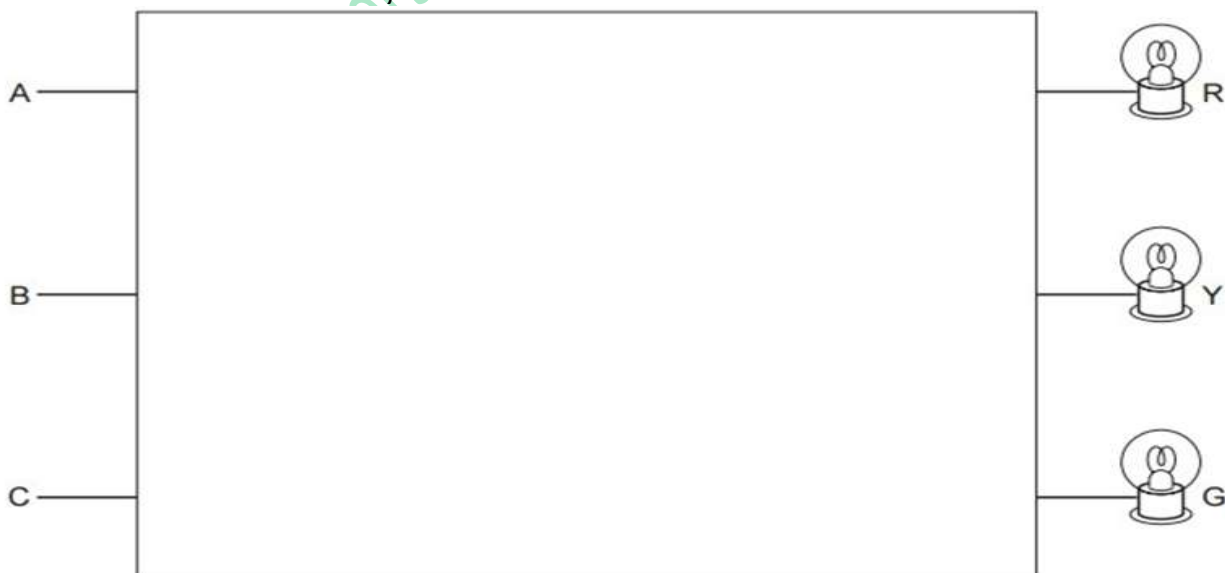Draw the logic circuit and directly combine ALL three of these logic statements and produce **three** OUTPUTS **R, G and Y**




[5]

9618/12/M/J/23

8 (a) Draw the logic circuit for this logic expression:
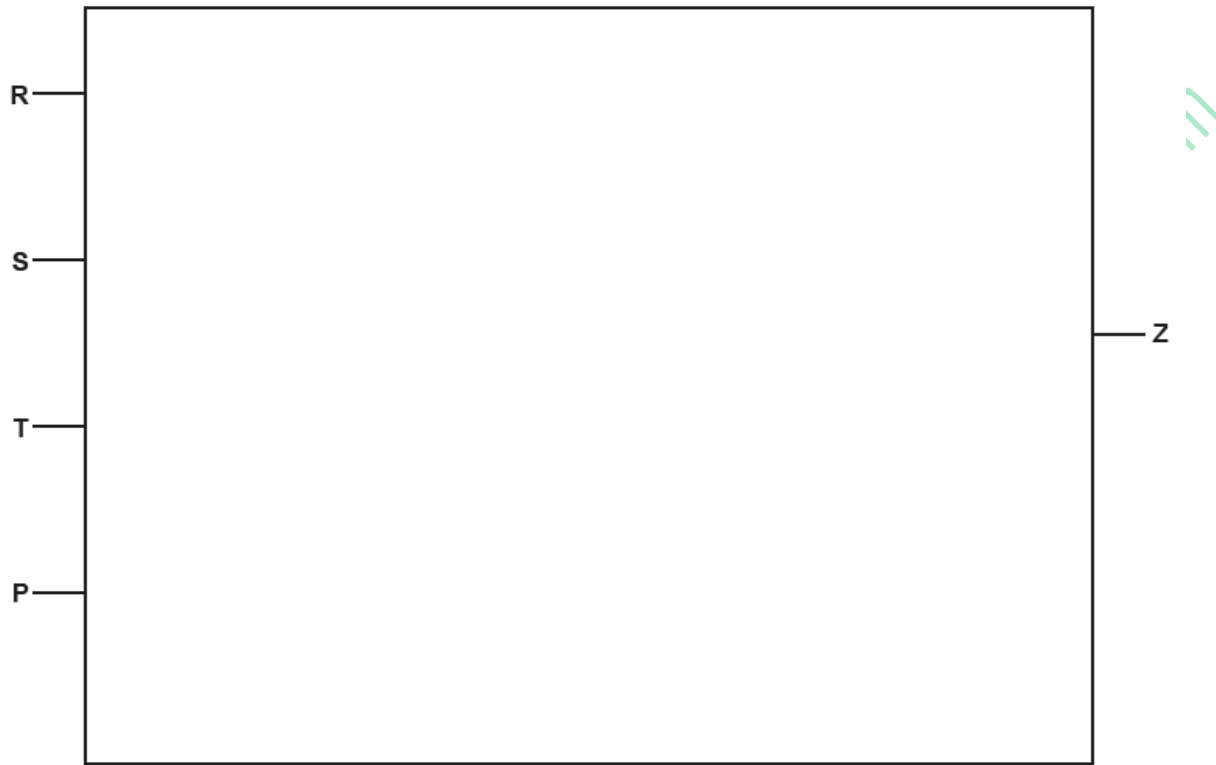
$$Z = (R \text{ XOR } S) \text{ AND } (\text{NOT } T \text{ NOR } P)$$



[2]

(b) Complete the truth table for this logic expression: $Z = (\text{NOT } P \text{ OR } Q) \text{ XOR } (R \text{ NOR } Q)$

Inputs			Working space	Output
P	Q	R		Z
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]


9618/13/M/J/2

9 (a) Write the logic expression for this truth table:

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

[1]

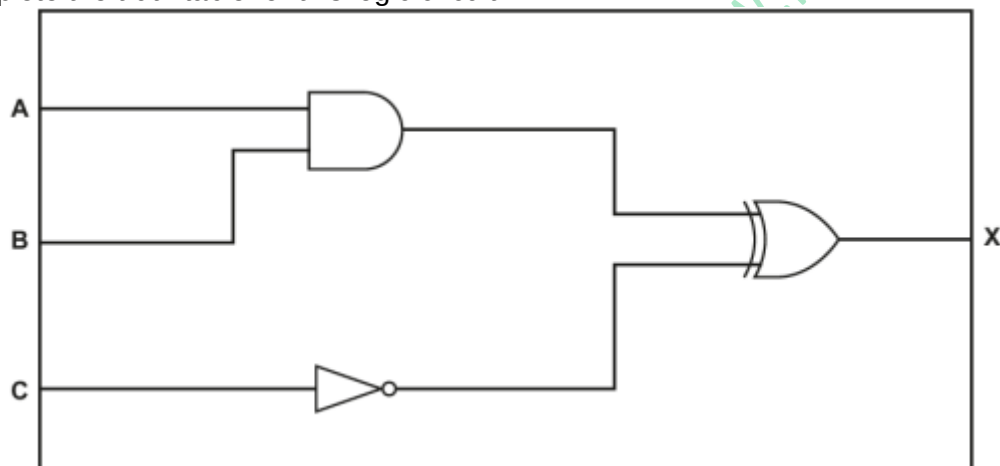9(b) Complete the truth table for this logic circuit:



Inputs			Working space	Output
A	B	C		X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

9618/12/M/J/22

10 Complete the truth table for the following logic expression:

$$X = (A \text{ XOR } B) \text{ AND NOT } C$$

Inputs			Working space	Output
A	B	C		X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

(9618/12/M/J/21)

11 A logic expression is given:

$$S = (A \text{ AND } B \text{ AND } C) \text{ OR } (B \text{ XOR } C)$$

(a) Draw the logic circuit for the given expression.



[4]

11 (b) Complete the truth table for the logic expression:


$$S = (A \text{ AND } B \text{ AND } C) \text{ OR } (B \text{ XOR } C)$$

Inputs			Working space	Output
A	B	C		S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

Answers

1 (a)

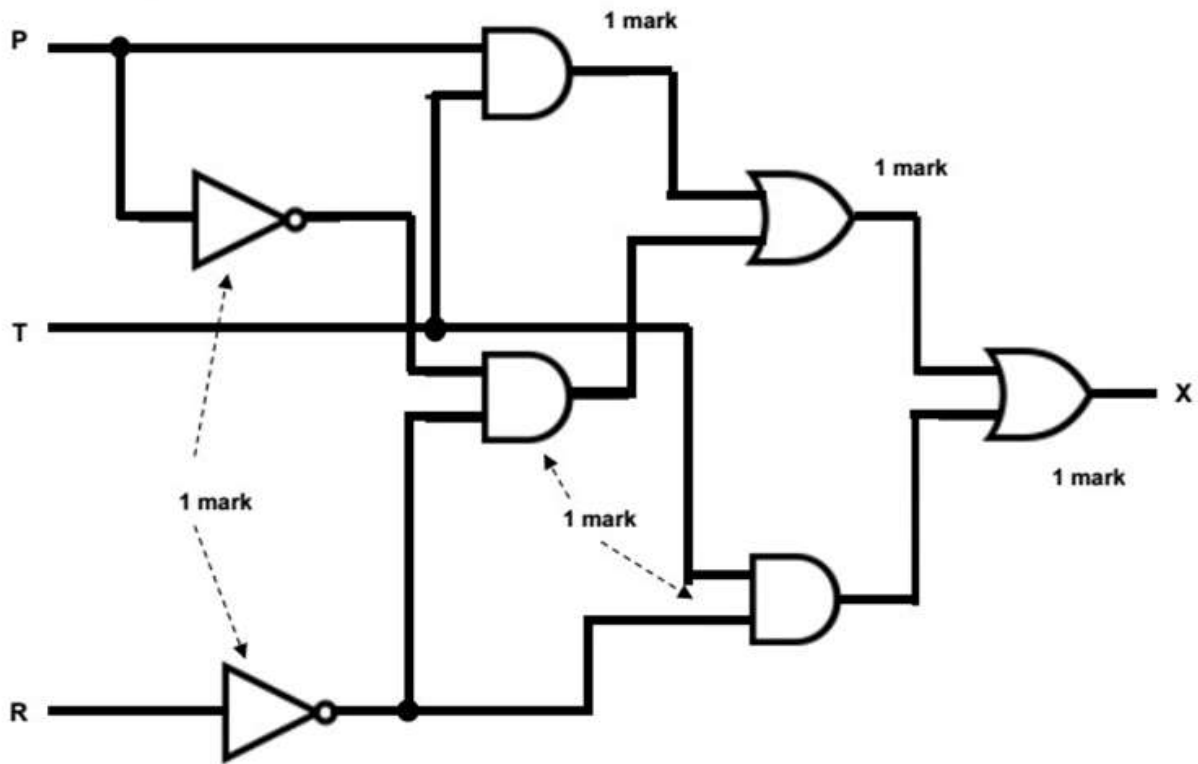

(b)

P	T	R	Workspace	X
0	0	0		1
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

} 1 mark


} 1 mark

} 1 mark


} 1 mark

[4]

Alternative solution 1:

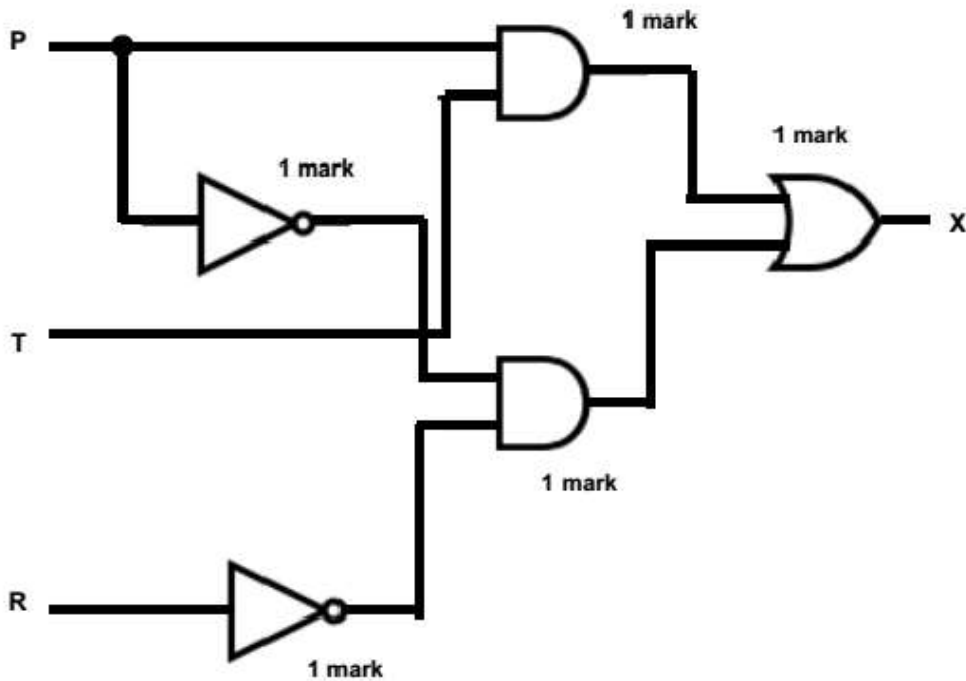

Alternative solution 2:

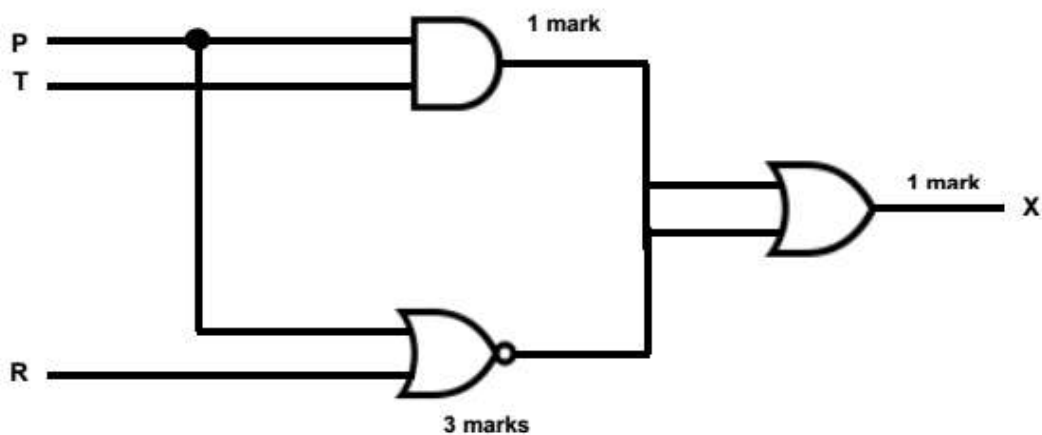

[5]


Note: other solutions may be possible depending on how simplification of the original statement is done



9608/13/M/J/18

2

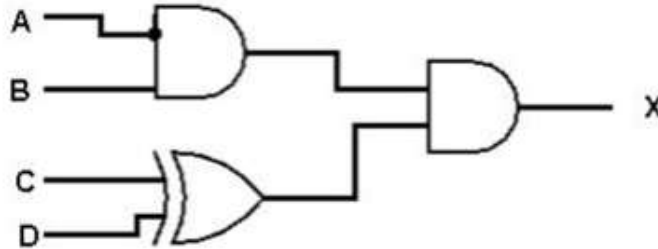1 mark per correct gate with correct inputs




3

3

1 mark per bullet:


- ☐ A OR B
- ☐ C OR D OR E
- ☐ Final AND

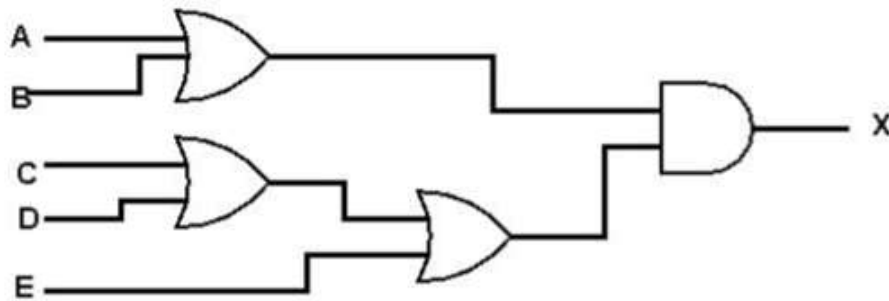

3

4

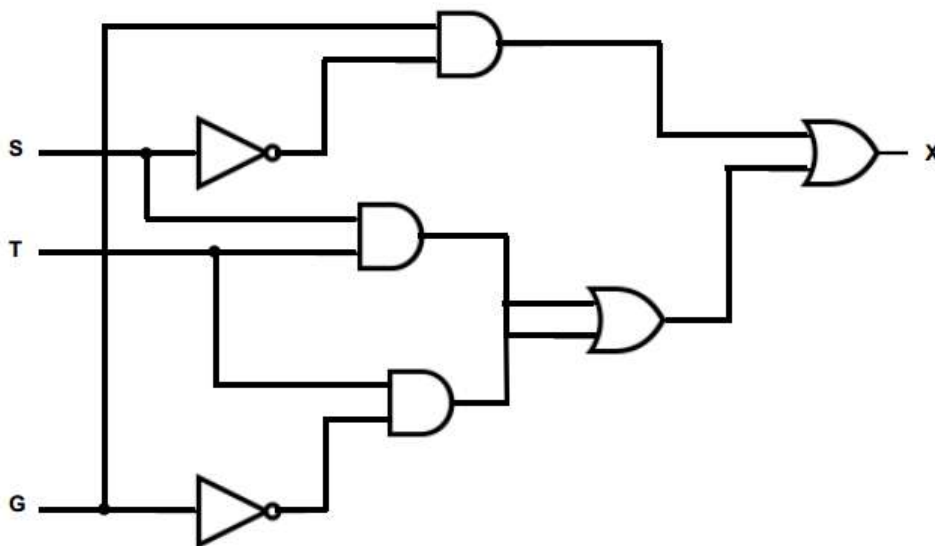4 (a) 1 mark for each correct gate (look out for alternative answers that work)



Allow a single triple input OR gate at the right hand side

[7]

4

(b) 1 mark for each pair of outputs – shown highlighted in table

Inputs			Workspace	Output
S	T	G		X
0	0	0		0
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

[4]

5 (a)

(a)

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

(1 mark for the 1,0 and 1 mark for 0, 0)

[2]

5 (b)

(b)

A	B	C	D	Y
0	0	0	1	0
0	1	1	0	0
1	0	1	1	1
1	1	1	0	0

(1 mark for each row).

[4]

6(a)

(a) (i) 1 mark for each pair of rows

Inputs			Working space	Output
A	B	C		X
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		1

[4]

6

(b) (A is NOT 1 OR B is NOT 1) OR (B is NOT 1 AND C is 1) //

(NOT A OR NOT B) OR (NOT B AND C) //

$(A + \bar{B})$ $+$ $(\bar{B}.C)$ //

IF (A = 0) OR (B = 0) OR (B = 0 AND C = 1)

[3]

<----- 1 mark -----><1 mark><----- 1 mark ----->

(c)

A	B	C	D
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

1 mark for both columns correct

[1]

(d) NAND Gate [1]


7 (a)

A	B	C	D	E	F
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	1	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	1	0	0	0

(1 for each bold box) no follow through


[4]

7(b)

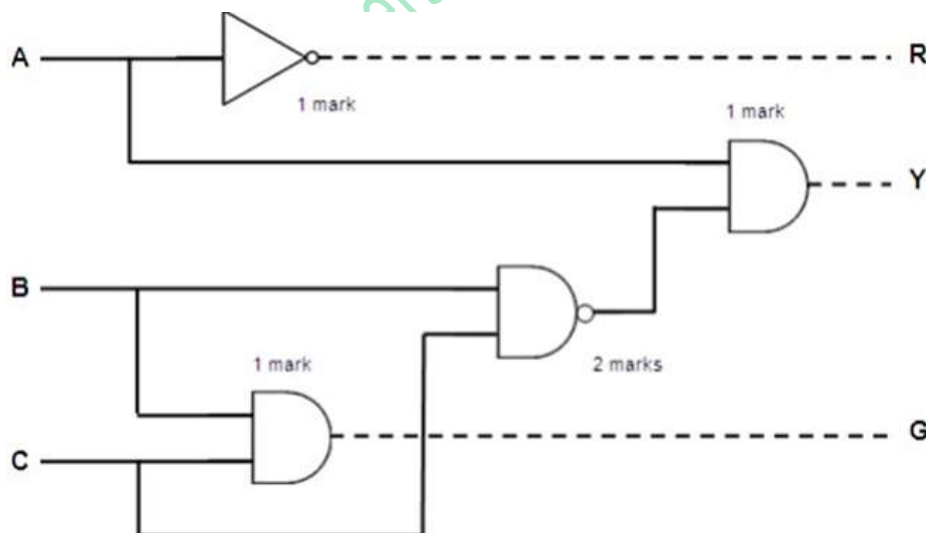

[5]


Or

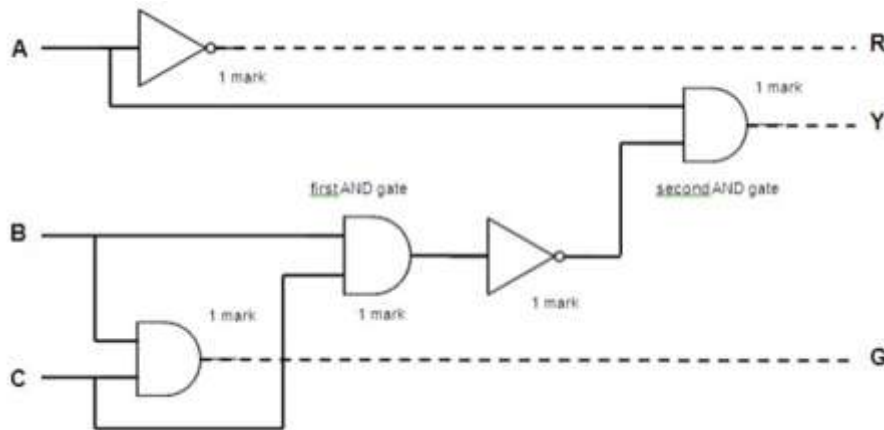

[5]

8 (a)

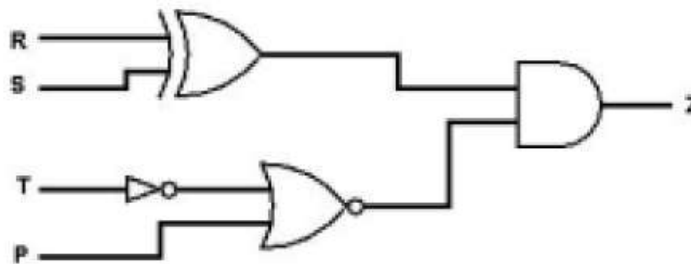1 mark for correct XOR and AND gates, with correct inputs
1 mark for correct NOT and NOR gates with correct inputs



[2]

(b)

1 mark for first 4 rows
1 mark for last 4 rows

P	Q	R	Working space	Z
0	0	0		0
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		0
1	1	0		1
1	1	1		1

[2]

9618/13/M/J/2

Answer

9(a) NOT B 1

9(b) 1 mark for first 4 rows correct; 1 mark for second 4 rows correct

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

1 marks

1 mark

[2]

9618/12/M/J/22

10. 1 mark for first 4 rows, 1 mark for second 4 rows

A	B	C	Working space	X
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		0
1	1	0		0
1	1	1		0


1 mark

1 mark

Answer (9618/12/M/J/21)

11 (a) 1 mark for each correct gate, with correct inputs

[4]

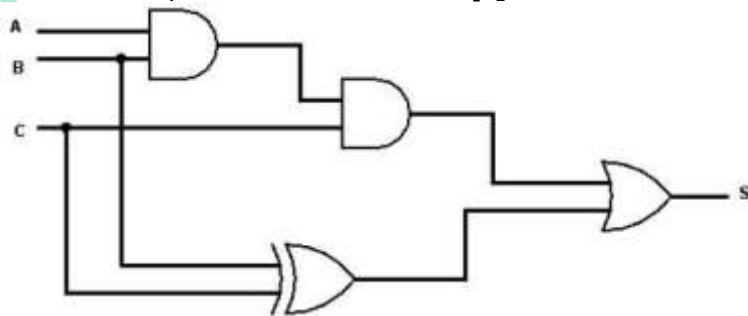

11(b)

1 mark for each half

A	B	C	Working space	S
0	0	0		0
0	0	1		1
0	1	0		1
0	1	1		0
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		1

1 mark

1 mark