

NCERT Solutions for Class 12 Physics

Chapter 7 Alternating Current

Question 1.

A 100 Ω resistor is connected to a 220 V, 50 Hz ac supply.

- (a) What is the rms value of current in the circuit?
 (b) What is the net power consumed over a full cycle?

Answer:

$$(a) \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{220}{100} = 2.20 \text{ A}$$

$$(b) \quad \text{Net power} = V_{\text{rms}} \times I_{\text{rms}} = 220 \times 2.20 \\ = 484 \text{ W}$$

Question 2.

- (a) The peak voltage of an a.c. supply is 300 V. What is the rms voltage?
 (b) The rms value of current in an ac circuit is 10 A. What is the peak current?

Answer:

$$(a) \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{300}{\sqrt{2}} = 212.1 \text{ V}$$

$$(b) \quad I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \text{ or } I_0 = I_{\text{rms}} \sqrt{2}$$

$$\text{i.e. } I_0 = 10 \times \sqrt{2} = 14.1 \text{ A.}$$

Question 3.

A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.

Answer:

Here, reactance $X_L = 2\pi\nu L = 2\pi \times 50 \times 44 \times 10^{-3}$

$$\therefore I_{\text{rms}} = \frac{V_{\text{rms}}}{X_L} = \frac{220}{2\pi \times 50 \times 44 \times 10^{-3}} \\ = 15.91 \text{ A}$$

Question 4.

A 60 μF capacitor is connected to a 110 V, 60 Hz ac supply. Determine the RMS value of the current in the circuit.

Answer:

Here, reactance $X_C = \frac{1}{2\pi\nu C} = \frac{1}{2\pi \times 60 \times 60 \times 10^{-6}}$

$$\begin{aligned} \therefore I_{\text{rms}} &= \frac{V_{\text{rms}}}{X_C} = \frac{110}{1/(2\pi \times 60 \times 60 \times 10^{-6})} \\ &= 110 (2\pi \times 60 \times 60 \times 10^{-6}) \\ &= 2.49 \text{ A} \end{aligned}$$

Question 5.

In Exercise 7.3 and 7.4, what is the net power absorbed by each circuit over a complete cycle? Explain your answer.

Answer:

In the case of an ideal inductor or capacitor, there is no power loss.

Question 6.

Obtain the resonant frequency ω_r of a series LCR circuit with $L = 2.0 \text{ H}$, $C = 32 \mu\text{F}$ and $R = 10 \Omega$. What is the Q-value of this circuit?

Answer:

Using $\omega_r = \frac{1}{\sqrt{LC}}$, we get

$$\begin{aligned} \omega_r &= \frac{1}{\sqrt{2 \times 32 \times 10^{-6}}} = \frac{1}{8 \times 10^{-3}} \\ &= 125 \text{ s}^{-1} \end{aligned}$$

Then, $Q = \frac{X_L}{R} = \frac{\omega_r L}{R} = \frac{125 \times 2}{10} = 25$

Question 7.

A charged $30 \mu\text{F}$ capacitor is connected to a 27 mH inductor. What is the angular frequency of free oscillations of the circuit?

Answer:

Using $\omega_r = \frac{1}{\sqrt{LC}}$, we get

$$\begin{aligned} \omega_r &= \frac{1}{\sqrt{27 \times 10^{-3} \times 30 \times 10^{-6}}} \\ &= 1111 = 1.1 \times 10^3 \text{ s}^{-1} \end{aligned}$$

Question 8.

Suppose the initial charge on the capacitor in Exercise 7.7 is 6 mC . What is the total energy stored in the circuit initially? What is the total energy at later time?

Answer:

Using $U = \frac{1}{2} \frac{Q^2}{C}$, we get

$$U = \frac{1}{2} \times \frac{6 \times 10^{-3} \times 6 \times 10^{-3}}{30 \times 10^{-6}} = 0.6 \text{ J}$$

At a later time, energy is shared between capacitor and inductor, However, the total energy remains the same, provided there is no loss of energy.

Question 9.

A series LCR circuit with $R = 20 \Omega$, $L = 1.5 \text{ H}$ and $C = 35 \mu\text{F}$ is connected to a variable-frequency 200 V ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?

Answer:

At natural frequency

$$X_L = X_C \therefore Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\begin{aligned} \text{Using } P &= \frac{V^2}{R}, \text{ we get } P = \frac{200 \times 200}{20} \\ &= 2000 \text{ W} \end{aligned}$$

Question 10.

A radio can tune over the frequency range of a portion of the MW broadcast band : (800 kHz to 1200 kHz). If its LC circuit has an effective inductance of 200 pH, what must be the range of its variable capacitor?

[Hint. For tuning, the natural frequency i.e., the frequency of free oscillations for the LC circuit should be equal to the frequency of the radio wave.]

Answer:

$$\text{Using } \nu = \frac{1}{2\pi\sqrt{LC}}, \text{ we get } C = \frac{1}{4\pi^2\nu^2L}$$

$$(i) \text{ For } \nu = 800 \text{ kHz} = 800 \times 10^3 \text{ Hz}$$

$$\begin{aligned} C &= \frac{1}{4\pi^2(200 \times 10^{-6})(800 \times 10^3)^2} \\ &= 197.8 \text{ pF} \approx 198 \text{ pF} \end{aligned}$$


$$(ii) \text{ For } \nu = 1200 \text{ kHz} = 1200 \times 10^3 \text{ Hz, we get}$$

$$\begin{aligned} C &= \frac{1}{(4\pi^2 \times 200 \times 10^{-6})(1200 \times 10^3)^2} \\ &= 87.9 \text{ pF} \approx 88 \text{ pF} \end{aligned}$$

Thus, the range of the variable capacitor must be 88 pF to 198 pF.

Question 11.

Figure shows a series LCR circuit connected to a variable frequency 230 V source. $L = 5.0 \text{ H}$, $C = 80 \mu\text{F}$, $R = 40 \Omega$.

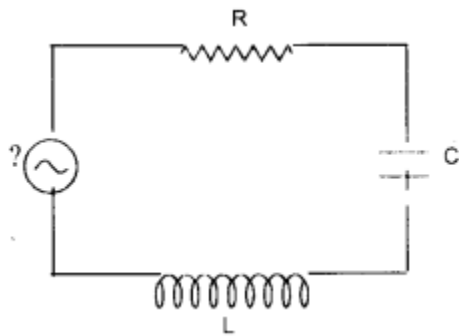

- (a) Determine the source frequency which drives the circuit in resonance.
- (b) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- (c) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency. **(C.B.S.E. 1994, 1998, 2006)**

Answer:

- (a) Resonant angular frequency,

$$\begin{aligned} \omega &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 80 \times 10^{-6}}} \\ &= 50 \text{ rad s}^{-1} \end{aligned}$$

- (b) At resonance

$$Z = R = 40 \Omega$$

$$\therefore I_0 = \frac{V_0}{R} = \frac{\sqrt{2} V_{\text{rms}}}{R} = \frac{\sqrt{2} \times 230}{40} = 8.1 \text{ A}$$

- (c) Pot. drop across inductance

$$\begin{aligned} V_L &= I_{\text{rms}} X_L = \frac{V_{\text{rms}}}{R} \omega L = \frac{230}{40} \times 50 \times 5 \\ &= 1437.5 \text{ V} \end{aligned}$$

- Pot. drop across capacitance

$$\begin{aligned} V_C &= I_{\text{rms}} X_C = \frac{V_{\text{rms}}}{R \omega C} = \frac{230}{40 \times 50 \times 80 \times 10^{-6}} \\ &= 1437.5 \text{ V} \end{aligned}$$

- Potential drop across LC combination

$$\begin{aligned} &= V_L - V_C \\ &= 1437.5 - 1437.5 = 0 \end{aligned}$$

$$\text{Pot. drop across R, } V_R = I_{\text{rms}} R = \frac{230}{40} \times 40 = 230 \text{ V}$$

Question 12.

An LC circuit contains a 20 mH inductor and a 50 μF capacitor with an initial charge of 10 mC. The resistance of the circuit is negligible. Let the instant the circuit is closed be $t = 0$.

- (a) What is the total energy stored initially? Is it conserved during LC oscillations?
- (b) What is the natural frequency of the circuit?

- (c) At what time is the energy stored:
 (i) completely electrical (i.e., stored in the capacitor)?
 (ii) completely magnetic (i.e., stored in the inductor)?
 (d) At what times is the total energy shared equally between the inductor and the capacitor?
 (e) If a resistor is inserted in the circuit, how much energy is eventually dissipated as heat? **(C.B.S.E. Sample Paper 1998)**

Answer:

- (a) Total initial energy
 (a) Total initial energy

$$= \frac{Q^2}{2C} = \frac{10^{-4}}{2 \times 50 \times 10^{-6}} = 1\text{J}$$

Yes, total energy is conserved in LC oscillations as resistance of L - C circuit is negligible.

- (b) Using $\omega = \frac{1}{\sqrt{LC}}$, we get

$$\omega = \frac{1}{\sqrt{(20 \times 10^{-3})(50 \times 10^{-6})}} = 10^3 \text{ rad s}^{-1}$$

$$\text{and } \omega = 2\pi\nu \text{ or } \nu = \frac{\omega}{2\pi} = \frac{10^3}{2\pi} = 159 \text{ Hz}$$

- (c) Let the charge on the capacitor at any instant during L - C oscillations is $q = q_0 \cos \omega t$
 (i) The energy stored will be completely electrical if $q = \pm q_0$ (max.)
 or $\cos \omega t = \pm 1$ or $\omega t = n\pi$, when $n = 0, 1, 2, 3, \dots$

$$\begin{aligned} \text{or } t &= \frac{n\pi}{\omega} = \frac{n\pi}{2\pi} T & (\because \omega &= \frac{2\pi}{T}) \\ &= \frac{nT}{2} \end{aligned}$$

or energy stored will be completely electrical at

$$t = 0, \frac{T}{2}, T, \frac{3T}{2}, 2T, \dots$$

(ii) The energy stored will be completely magnetic if electrical energy is zero.

$$\text{or } q = 0 \text{ or } \cos \omega t = 0 \text{ or } \omega t = (2n + 1) \frac{\pi}{2},$$

$$n = 0, 1, 2, \dots$$

$$t = \frac{(2n+1)\pi}{2\omega} = \frac{(2n+1)\pi T}{2 \times 2\pi} = \frac{(2n+1)T}{4}$$

Thus, energy stored will be completely magnetic at

$$t = \frac{T}{4}, \frac{3T}{4}, \frac{5T}{4}, \frac{7T}{4}, \dots$$

(d) Total energy stored = $\frac{q_0^2}{2C}$. Let q be the charge on the capacitor, when energy stored in the capacitor is equal to $\frac{1}{2}$ the total energy stored *i.e.*

$$\frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \left(\frac{q_0^2}{2C} \right) \text{ or } q = \pm \frac{q_0}{\sqrt{2}}$$

Since $q = q_0 \cos \omega t \therefore \pm \frac{q_0}{\sqrt{2}} = q_0 \cos \omega t$

or $\cos \omega t = \pm \frac{1}{\sqrt{2}}$

or $\omega t = (n\pi + \frac{\pi}{4}) = (n + \frac{1}{4})\pi$

or $t = \frac{(n + \frac{1}{4})\pi}{\omega} = \frac{(4 + \frac{1}{4})\pi T}{2\pi}$

$= (n + \frac{1}{4})\frac{T}{2}$

or $\omega t = n\pi + \frac{3\pi}{4} = (n + \frac{3}{4})T$

or $t = \frac{(n + \frac{3}{4})\pi T}{2\pi} = (n + \frac{3}{4})\frac{T}{2}$

Thus, total energy is shared equally between the inductor

and the capacitor at $t = \frac{T}{8}, \frac{3T}{8}, \frac{5T}{8}, \frac{7T}{8}, \frac{9T}{8},$

$\frac{11T}{8}, \dots$

(e) Total initial energy of 1 J will be lost as heat due to Joule's heating effect in the resistor.

Question 13.

A coil of inductance 0.50 H and resistance 100 Ω is connected to a 240 V, 50 Hz ac supply.

(a) What is the maximum current in the coil?

(b) What is the time lag between the voltage maximum and the current maximum?

Answer:

$$\begin{aligned}
 \text{(a) Maximum current } I_0 &= \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} = \frac{\sqrt{2}V_{\text{rms}}}{\sqrt{R^2 + \omega^2 L^2}} \\
 &= \frac{240 \times \sqrt{2}}{\sqrt{100^2 + 0.5^2 \times 4\pi^2 \times 2500}} \\
 & \qquad \qquad \qquad (\because \omega = 2\pi\nu) \\
 &= 1.82 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b) } \tan \phi &= \frac{X_L}{R} = \frac{2\pi\nu L}{R} \\
 &= \frac{2\pi \times 50 \times 0.5}{100} = 1.571
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow \phi &= \tan^{-1} 1.571 = 57.5^\circ \\
 &= \frac{57.5 \times \pi}{180} \text{ rad}
 \end{aligned}$$

$$\begin{aligned}
 \text{Time lag} &= \frac{\phi}{\omega} = \frac{\phi}{2\pi\nu} \\
 &= \frac{57.5\pi}{180 \times 2\pi \times 50} = 3.2 \text{ ms}
 \end{aligned}$$

Question 14.

Obtain the answers (a) to (b) in Exercise 7.13 if the circuit is connected to a high-frequency supply (240 V, 10 kHz). Hence, explain the statement that at very high frequency, an inductor in a circuit nearly amounts to an open circuit. How does an inductor behave in a dc circuit after the steady-state?

Answer:

For the given high frequency, $\omega = 2\pi\nu = 2\pi \times 10^4 \text{ rad s}^{-1}$

I_0 , in this case, is too small, so it can be concluded that at high frequencies an inductor behaves as on an open circuit.

In a steady d.c. circuit $\nu = 0$, so the inductor acts as a simple conductor.

Question 15.

A 100 μF capacitor in series with a 40 Ω resistance is connected to a 110 V, 60 Hz supply.

(a) What is the maximum current in the circuit?

(b) What is the time lag between the current maximum and the voltage maximum?

Answer:

$$\begin{aligned}
 I_0 &= \frac{V_0}{\sqrt{R^2 + X_C^2}} = \frac{\sqrt{2} V_{\text{rms}}}{\sqrt{R^2 + \frac{1}{C^2 \times 4\pi^2 \nu^2}}} \\
 &= \frac{110\sqrt{2}}{\sqrt{1600 + \frac{1}{4\pi^2 \times 3600 \times 10^{-8}}}} \\
 &= 3.23 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 (b) \tan \phi &= -\frac{X_C}{R} = -\frac{1}{\omega CR} \\
 &= -\frac{1}{2\pi \times 60 \times 10^{-4} \times 40} \\
 &= -0.6631
 \end{aligned}$$

$$\therefore |\phi| = 33.5^\circ = \frac{33.5 \times \pi}{180} \text{ rad}$$

$$\text{Time lag} = \frac{\phi}{\omega} = \frac{33.5 \pi}{180 \times 2\pi \times 60} = 1.55 \text{ ms}$$

Question 16.

Obtain the answers to (a) and (b) in Exercise 7.15 if the circuit is connected to a 110 V, 12 kHz supply. Hence, explain the statement that a capacitor is a conductor at very high frequencies. Compare this behavior with that of a capacitor in a dc circuit after the steady-state.

Answer

$$\begin{aligned}
 I_0 &= \frac{V_0}{\sqrt{R^2 + X_C^2}} = \frac{\sqrt{2} V_{\text{rms}}}{\sqrt{R^2 + \frac{1}{C^2 \times 4\pi^2 \nu^2}}} \\
 &= \frac{110\sqrt{2}}{\sqrt{1600 + \frac{1}{4\pi^2 \times 3600 \times 10^{-8}}}} \\
 &= 3.23 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 (b) \tan \phi &= -\frac{X_C}{R} = -\frac{1}{\omega CR} \\
 &= -\frac{1}{2\pi \times 60 \times 10^{-4} \times 40} \\
 &= -0.6631
 \end{aligned}$$

$$\therefore |\phi| = 33.5^\circ = \frac{33.5 \times \pi}{180} \text{ rad}$$

embed="true">or n is nearly zero at high frequency. In part (a) C term is negligible at a high frequency so it acts like a resistor. For a steady d. c. we have v like

Question 17.

Keeping the source frequency equal to the resonating frequency of the series LCR circuit, if the three elements. L, C, and R are arranged in parallel, show that the total current in the parallel LCR circuit is minimum at this frequency. Obtain the current rms value in each branch of the circuit for the elements and source specified in Exercise 7.11 for this frequency.

Answer:

In the case of parallel LCR circuit, impedance is given by,

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

At resonance frequency $\frac{1}{Z}$ is minimum *i.e.* Z is maximum (=R) and current is minimum.

In resistor $I_R = \frac{V_{rms}}{R} = \frac{230}{40} = 5.75 \text{ A}$

In inductor $I_L = \frac{V_{rms}}{X_L} = \frac{V_{rms}}{\omega L} = \frac{230}{50 \times 5} = 0.92 \text{ A}$

In capacitor $I_C = \frac{V_{rms}}{X_C} = V_{rms} \omega C = 230 \times 50 \times 80 \times 10^{-6} = 0.92 \text{ A}$

Total current = 5.75 A

(∵ I_L and I_C are 180° out of phase at every instant, so they add up to zero)

Question 18.

A circuit containing an 80 mF inductor and a 60 μF capacitor in series is connected to a 230 V, 50 Hz supply. The resistance of the circuit is negligible.

- (a) Obtain the current amplitude and rms values.
- (b) Obtain the rms values of potential drops across each element.
- (c) What is the average power transferred to the inductor?
- (d) What is the average power transferred to the capacitor?
- (e) What is the total average power absorbed by the circuit? [‘Average’ implies ‘averaged over one cycle’.]

Answer:

$$(a) \quad I_0 = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Here $R = 0$, $\omega = 2\pi \times 50$
 $= 100\pi \text{ rad s}^{-1}$,

$$V_0 \sqrt{2} = 230 \times \sqrt{2} \text{ V}$$

$$V_{\text{rms}} = 80 \times 10^{-3} \text{ V}, \quad C = 60 \times 10^{-6} \text{ F}$$

$$\therefore X_L = \omega L = 100\pi \times 80 \times 10^{-3}$$

$$= 25.14 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times 60 \times 10^{-6}}$$

$$= 53.03 \Omega$$

Using these values

$$I_0 = 11.6 \text{ A}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} = \frac{11.6}{\sqrt{2}} = 8.24 \text{ A}$$

$$(b) \quad V_L = I_{\text{rms}} \times \omega L$$

$$= 8.24 \times 100\pi \times 80 \times 10^{-3}$$

$$= 207 \text{ V}$$

$$V_C = I_{\text{rms}} \times \frac{1}{\omega C}$$

$$= 8.24 \times \frac{1}{100\pi \times 60 \times 10^{-6}}$$

$$= 437 \text{ V}$$

(c) Here $\phi = \pi/2$, because current lags voltage by 90° in the case of an inductor

$$\therefore P_L = VI \cos \pi/2 = 0$$

(d) Here $\phi = \pi/2$, because current lags voltage by 90° in the case of a capacitor

$$\therefore P_C = VI \cos \pi/2 = 0$$

(e) Total average power absorbed = 0

Question 19.

Suppose the circuit in Exercise 7.18 has a resistance of 15Ω . Obtain the average power transferred to each element of the circuit, and the total power absorbed.

Answer:

Using $I_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}}$ and given worked

out values

$$I_{\text{rms}} = \frac{230}{\sqrt{(15)^2 + (53 \cdot 03 - 25 \cdot 14)^2}}$$

$$= 7.26 \text{ A}$$

Average power to inductance as well as to capacitor is zero.

$$\text{Average power to resistance} = I_{\text{rms}}^2 R$$

$$= (7.26)^2 \times 15 = 791 \text{ W}$$

Thus total power consumed = 791 W

Question 20.

A series LCR circuit with $L = 0.12 \text{ H}$, $C = 480 \text{ nF}$, $R = 23 \Omega$ is connected to a 230 V variable frequency supply.

- (a) What is the source frequency for which current amplitude is maximum. Obtain this maximum value.
- (b) What is the source frequency for which the average power absorbed by the circuit is maximum. Obtain the value of this maximum power.
- (c) For which frequencies of the source are the power transferred to the circuit half the power at resonant frequency? What is the current amplitude at these frequencies?
- (d) What is the Q-factor of the given circuit? **(C.B.S.E. 1992)**

Answer:

$$(a) \omega_{\text{resonance}} = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{0.12 \times 480 \times 10^{-9}}}$$

$$= 4167 \text{ rad s}^{-1}$$

$$v_{\text{resonance}} = \frac{\omega_{\text{resonance}}}{2\pi} = 663 \text{ Hz}$$

$$I_0 = \frac{V_0}{R} = \frac{\sqrt{2}V_{\text{rms}}}{R} = \frac{230\sqrt{2}}{23}$$

$$= 14.14 \text{ A}$$

$$(b) P_{av} = \frac{1}{2} I_0^2 R$$

$$= \frac{1}{2} (14 \cdot 1)^2 \times 23 = 2300 \text{ W}$$

(c) Two angular frequencies at which the power transferred to the circuit is half the power at resonant frequency are

$$\omega = \omega_0 \pm \Delta\omega = \omega_0 \pm \frac{R}{2L}$$

$$\text{or } 2\pi v = 2\pi v_0 \pm \frac{R}{2L} \text{ or } v = v_0 \pm \frac{1}{2\pi} \frac{R}{2L}$$

$$\begin{aligned} \text{or } v &= 633 \pm \frac{1}{2 \times 3 \cdot 14} \times \frac{23}{2 \times 0 \cdot 12} \\ &= 633 \pm 15 \text{ Hz} = 648 \text{ Hz and } 678 \text{ Hz} \end{aligned}$$

Thus, the power transferred to the circuit is half the power at resonant frequency at 648 Hz and 678 Hz.

$$\begin{aligned} \text{Current amplitude} &= \frac{I_0}{\sqrt{2}} = \frac{14 \cdot 1}{\sqrt{2}} \\ &= 10 \text{ A} \end{aligned}$$

$$(d) Q = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{4167 \times 0 \cdot 12}{23} = 21 \cdot 7$$

Question 21.

Obtain the resonant frequency and Q-factor of a series LCR circuit with $L = 3.0 \text{ H}$, $C = 27 \mu\text{F}$, and $R = 7.4 \Omega$. It is desired to improve the sharpness of the resonance of the circuit by reducing its 'full width at half maximum' by a factor of 2. Suggest a suitable way.

Answer:

$$\begin{aligned} \omega_{\text{resonance}} &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \times 27 \times 10^{-6}}} \\ &= 111 \text{ rad s}^{-1} \end{aligned}$$

$$\begin{aligned} Q &= \frac{X_L}{R} = \frac{\omega_{\text{resonance}} \times L}{R} = \frac{111 \times 3}{7 \cdot 4} \\ &= 45 \end{aligned}$$

For doubling Q for same $\omega_{\text{resonance}}$, R should be reduced

$$\text{to half i.e. } \frac{7 \cdot 4}{2} = 3 \cdot 7 \Omega$$

Question 22.

Answer the following questions :

(a) In any ac circuit, is then applied instantaneous voltage equal to the algebraic sum of the instantaneous voltages across the series elements of the circuit? Is the same true for rms voltage?

(b) A capacitor is used in the primary circuit of an induction coil.

(c) An applied voltage signal consists of a superposition of a dc voltage and an ac voltage of high frequency. The circuit consists of an inductor and a capacitor in series. Show that the dc signal will appear across C and the ac signal across L.

(d) A choke coil in series with a lamp is connected to a dc line. The lamp is seen to shine brightly. Insertion of an iron core in the choke causes no change in the lamp's brightness. Predict the corresponding observations if the connection is to an ac line.

(e) Why is choke coil needed in the use of fluorescent tubes with ac mains? Why can we not use an ordinary resistor instead of the choke coil?

Answer:

(a) Yes, the applied instantaneous voltage is equal to the algebraic sum of the instantaneous voltages across the series elements of the circuit. It is because voltages across different elements are not in phase.

It is not true for rms voltages. It is because rms voltages across different elements are not in phase with each other.

(b) At the break, a large induced emf is produced. In case the capacitor is not connected, sparking will take place. But when the capacitor is used, the large induced emf produced at break is used up in charging the capacitor and no sparking takes place.

(c)

Inductive reactance, $X_L = \omega L = 2\pi \nu L$

Capacitive reactance, $X_C = \frac{1}{C\omega} = \frac{1}{2\pi \nu C}$

For d.c., $X_L = 0$, therefore, $X_L = 0$ and $X_C = \infty$. Hence, d.c. signal appears across capacitor. For high frequency a.c., $X_L \rightarrow \text{High}$ and $X_C \rightarrow 0$. Hence, a.c. signal appears across inductor.

(d) When a choke coil in series with a lamp is connected to a d.c. line, L has no effect on the steady value of the current. Therefore, the brightness of the lamp is not affected by the insertion of the iron core in the choke. On a.c. line, the lamp will shine dimly due to the impedance of the choke coil. The brightness of the lamp will further go dim on the insertion of an iron core, which increases the impedance of the choke coil.

(e) The choke coil is used to reduce the current. As its power factor is zero, it reduces the current without wasting the power. If an ordinary resistor is used instead of a choke coil, it will waste power in the form of heat.

Question 23.

A power transmission line feeds input power at 2300 V to a step-down transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary in order to get output power at 230 V? (C.B.S.E. 1997)

Answer:

Using $\frac{E_1}{E_2} = \frac{N_1}{N_2}$, we get

$$N_2 = \frac{N_1 E_2}{E_1} = \frac{4000 \times 230}{2300} \\ = 400 \text{ turns.}$$

Question 24.

At a hydroelectric power plant, the water pressure head is at a height of 300 m and the water flow available is $100 \text{ m}^3\text{s}^{-1}$. If the turbine generator efficiency is 60%, estimate the electric power available from the plant ($g = 9.8 \text{ ms}^{-2}$).

Answer:

$$\begin{aligned} \text{Hydroelectric power} &= \frac{\text{Work}}{\text{time}} = \frac{\text{Force} \times \text{distance}}{\text{time}} \\ &= \text{Column pressure} \times \text{Volume of water flowing per} \\ &\quad \text{second across a cross-section.} \\ &= h\rho g (Av) \\ &= 300 \times 9.8 \times 10^3 (100) \\ \text{Electric power} &= 60\% \text{ of hydroelectric power} \\ &= 0.6 \times 300 \times 9.8 \times 10^3 \times (100) \\ &= 176 \text{ MW} \end{aligned}$$

Question 25.

A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wirelines carrying power is 0.5 Ω per km. The town gets power from the line through a 4000-220 V step-down transformer at a sub-station in the town.

- (a) Estimate the line power loss in the form of heat.
- (b) How much power must the plant supply, assuming there is negligible power loss due to leakage?
- (c) Characterise the step-up transformer at the plant. **(C.B.S.E. Sample Paper 2003)**

Answer:

Total resistance of line = $0.5 \times 30 = 15 \Omega$

Power supplied to town sub-station = 800 kW
 $= 800 \times 10^3 \text{ W}$

Voltage at which power is sent through line = 4000 V

RMS value of current in line, $I_{\text{rms}} = \frac{\text{Power}}{\text{Voltage}}$

$$= \frac{800 \times 10^3 \text{ W}}{4000 \text{ V}} = 200 \text{ A}$$

(a) Line power loss, $P = I_{\text{rms}}^2 R = (200)^2 \times 15 = 600 \text{ kW}$

(b) Power supplied by plant = Power received + Line power loss = $800 + 600 = 1400 \text{ kW}$

(c) Voltage drop on line, $V = I_{\text{rms}} R = 200 \times 15 = 3000 \text{ V}$.

Voltage output of the step-up transformer at the plant = $4000 + 3000 = 7000 \text{ V}$

Therefore, the step-up transformer at the plant is $440 \text{ V} - 7000 \text{ W}$.

Question 26.

Do the same exercise as above with the replacement of the earlier transformer by a $40,000 - 220 \text{ V}$ step-down transformer (Neglect, as before, leakage losses though this may not be a good assumption any longer because of the very high voltage transmission involved). Hence, explain why high voltage transmission is preferred.

Answer:

In this case I_{rms} on line

$$= \frac{\text{Power}}{\text{Voltage}} = \frac{800 \times 1000}{40000} = 20 \text{ A}$$

(a) Line power loss = $I^2 R = (20)^2 \times 15 = 6 \text{ kW}$

(b) Power supplied = $800 + 6 = 806 \text{ kW}$

(c) Voltage dropped = $IR = 20 \times 15 = 300 \text{ V}$

(d) Step up transformer should be of $440 \text{ V} - 40300 \text{ V}$
 Power loss in Ex. 7.25

$$= \frac{600}{1400} \times 100 = 43 \%$$

$$\text{Power loss} = \frac{6}{806} \times 100 = 0.74 \%$$

Thus, Power losses reduce a lot if power is transmitted at high voltage.