

NEW DUAL LOUD SPEAKER

Combining the Best Qualities of Electrostatic and Moving-coil Units.


By H. A. HARTLEY.



been put into production (see *The Wireless World*, June 1st, 1932, p. 585) which has many interesting points. It may be considered a pure capacity, and its reactance will be determined by the well-known formula

$$X = \frac{1}{2\pi fC}$$

When connected in the anode circuit of a valve whose resistance is R ohms, the impedance of the circuit is $Z = \sqrt{R^2 + X^2}$, and it follows that the impedance goes down with increasing frequency, so that there will be good top response; this is further aided by the fact that the diaphragm has small radiation resistance. On the other hand, the impedance increases as we come down the frequency scale, so there is bound to be a bass cut-off. It would seem, therefore, to be logical to use the electrostatic and electrodynamic loud speakers in combination, each making good the deficiencies of the other.

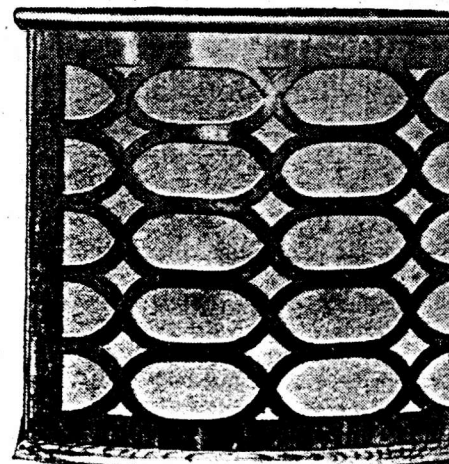

The "primustatic" electrostatic speaker forms one member of the dual unit.

THE moving-coil loud speaker as usually sold may be said to be deficient in the reproduction of the higher audio-frequencies, and now at the importance of good "top" is beginning to be realised, many readers of *The Wireless World* are wanting to know how this may be done.

Without going into the mathematics of loud speaker operation it may be said that the moving-coil loud speaker has constant power output at all frequencies, but this holds good only up to a certain frequency, determined by the size of the cone, at which point the power begins to fall off rapidly. Usually this frequency is between 2,000 and 3,000 cycles per second, and unless the cone is specially designed to give a series of controlled resonances there will be a top cut-off.

PRACTICAL details are here given of dual speaker equipment combining the excellent high-note response of the electrostatic speaker with full-bass reproduction of the moving-coil type. The combination ensures that each speaker makes good the deficiencies of the other. This article should prove a useful contribution towards the achievement of realistic reproduction.

apparent input impedance of this circuit low compared with that of the electrostatic speaker that all power will be diverted to the latter. The arrangement is shown in Fig. 1 where V is the output valve, T₁ the output transformer of the moving-coil speaker, L₁ the high frequency "stop choke," and E.S. the electrostatic speaker.

Output Transformer Ratio.

In some cases it will not be possible to choose a transformer ratio to achieve the desired result, as many loud speakers have non-variable transformers built into them. In such cases it will be necessary to connect a choke across the electrostatic speaker designed that the circuit formed has a resonant frequency at which it is desired that the electrostatic takes up the work which will be necessary simultaneously to its condenser in series with this circuit.

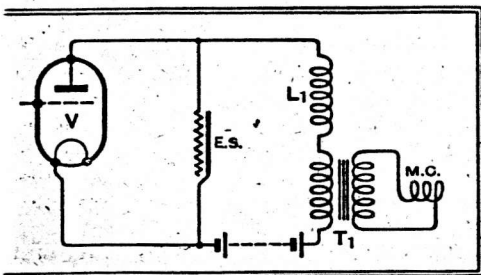


Fig. 1.—A suitable circuit where the transformation ratio of T₁ can be altered at will.

the size of the cone is reduced the frequency at which this cut-off takes place will be raised, but, unfortunately, the bass will suffer. The smaller the cone the greater is the required displacement at the lower end of the scale, and while a cone of, say, two inches diameter would give excellent top, it would have to be mounted in such a way that the amplitude of vibration at 50 cycles would be several inches. This, of course, is impracticable, so the cone is usually made about seven inches in diameter as a compromise.

An electrostatic loud speaker has recently

This, as it happens, is a method of getting quite good reproduction, but the application of the idea is not so simple as would appear on first thoughts.

To render the combination effective, two things must be done. First, we have seen that the electrostatic loud speaker will have a bass cut-off owing to its high impedance at low frequencies, but, owing to the small clearances in the design, the loud speaker will rattle unless the lower frequencies are prevented from reaching it. Secondly, the moving-coil loud speaker, having constant impedance, will act as a short circuit across the electrostatic at high frequencies unless the capacity of the electrostatic is so high that it acts as a short across the moving coil. In practice this is not so, and we must prevent the high-frequencies from reaching the moving-coil unit. To take the latter problem first, the desired result can be attained by inserting a choke in series with the moving-coil speaker; this will raise the impedance at high frequencies and so the electrostatic will take up the work at this end of the scale. At the same time we must choose a transformation ratio for the moving coil unit so that, at low frequencies, the

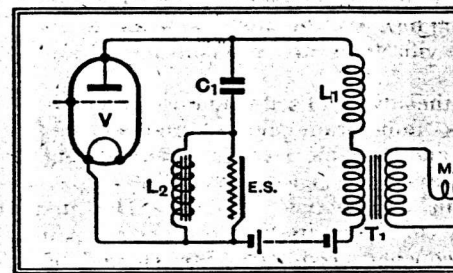


Fig. 2.—When the ratio of T₁ cannot be altered a resonant circuit L₂ E.S. prevents the low audio-frequencies from rattling the electrostatic loud speaker.

reactance at low frequencies is substantially greater than that of the choke. In Fig. 2 the resonant circuit is formed by E.S. and the choke L₂. This is insulated from

few Dual Loud Speaker.—

steady anode voltage by the condenser C_1 , so much for the theoretical considerations of the separation of the audio-frequency output into the two desired channels; we must now put this into practice.

The electrostatic loud speaker requires a polarising voltage of 200 to 250 volts, and in Fig. 1 it will be seen that the potential difference between the anode of V and H.T. — can be used for this purpose. If the circuit of Fig. 2 has to be adopted, then this source of polarising voltage is removed; some other means must also be found in cases where the voltage on the anode of the output valve is in excess of 250 volts, as the electrostatic loud speaker is not designed for such voltages.

Polarising Voltage.

If the moving-coil speaker has a D.C. excited field of appropriate voltage then this will form a suitable source of supply, otherwise the polarising voltage must be derived from the eliminator in some way. If the maximum H.T. is 250 volts and the output valve is directly heated, no special precautions are necessary, but in the case of an indirectly heated cathode type of output valve it is advisable that the rectifier, if the eliminator is of the A.C. type, be also an indirectly heated valve, to prevent excessive voltages being applied to the electrostatic speaker before the output valve warms up. If the output valve calls for 400 or more volts on the anode, a potentiometer must be added to break down the voltage to the desired figure. These various arrangements are shown in Fig. 3, which also shows a filter system in the supply. The choke L_3 , as well as reducing mains hum, is essential to prevent audio-frequency energy being diverted

from the electrostatic loud speaker into the supply system. The resistance R is also required in order to pass a small D.C. current through the choke, otherwise there will be no smoothing of mains hum.

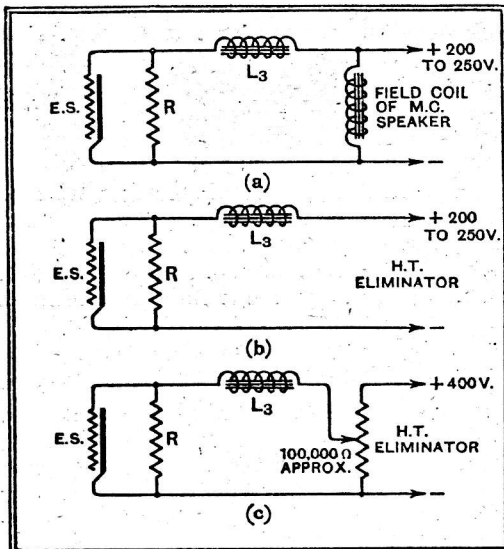


Fig. 3.—Various methods of obtaining the polarising voltage. The potentiometer in (c) should be adjusted so that the voltage applied to E.S. is about 220.

All the foregoing has been based on the assumption that the impedance relation between the electrostatic speaker and valve is such that the speaker forms an efficient load towards the upper limit of the frequency required. Where this is not the case, and, on the whole it will be exceptional, it will be necessary to feed the electrostatic speaker through a step-up or step-down transformer, according to the type of valve used. A step-down ratio will be required for valves of

very high impedance, and a step-up for power valves of unusually low impedance especially when such valves are used in parallel. For experimental purposes, a quality audio-frequency transformer of 3½ to 1 ratio, and of low self capacitance will be quite suitable. Fig. 4 shows the connections.

Compensating Unit.

We are now in a position to construct a compensating unit for the two loud speakers. Fig. 5 gives all values and connections; the reader is advised to study it closely. It will be seen that a choke of one henry inductance, L_1 is connected in series with the electrostatic speaker and the moving-coil output transformer. The function of which, as we have seen, is to prevent the higher frequencies from passing through this unit. The electrostatic loud speaker is in parallel with this; it is insulated from the steady anode voltage by C_1 of one farad capacity. The inductance L_2 of one henry and the electrostatic loud speaker together form a resonant circuit which is tuned to the desired cut-off frequency by means of the tapping on L_2 . The polarising voltage $E.S.$ is obtained from any convenient source and is fed through the filter system L_3 , L_3 being of 100 henries inductance and 250,000 ohms.


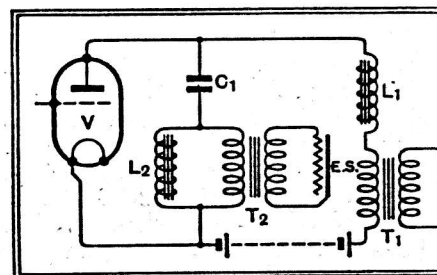


Fig. 4.—Where the impedance of E.S. is too high or too low to act as an efficient load on the valve, the transformer T_2 is used to match the impedances at high frequencies.


First of all, it is necessary to balance the two loud speakers for sensitivity. Fig. 5 shows the connections of both speakers. For this test, diagrams being shown for both direct output transformer feed, or through a compensating unit. Arrangements should be made so that the circuits can be broken at the point X. Tune in a station with E.S. connected and M.C. broken at X (one of the leads from the secondary of the output transformer), then as quickly as possible, break the lead between E.S. and H.T.—and connect in M.C. The volume of sound, making allowance for the different character of the reproduction, appears to be about the same on both speakers, nothing more need be done, the moving-coil loud speaker seems to be louder of the two an attempt should be made to reduce its sensitivity by adding a resistance to the field coil. This method, although not the best which can be used in ordinary cases, is forced on one here, the usual procedure, by adding a resistance to the output circuit, will affect the performance of the electrostatic. If of the permanent magnet type the sensitivity will probably be approximately equal to that of the electrostatic. On the other hand, the moving-coil unit may be one of the inexpensive type so popular, when the sensitivity will decrease; in this case nothing very much

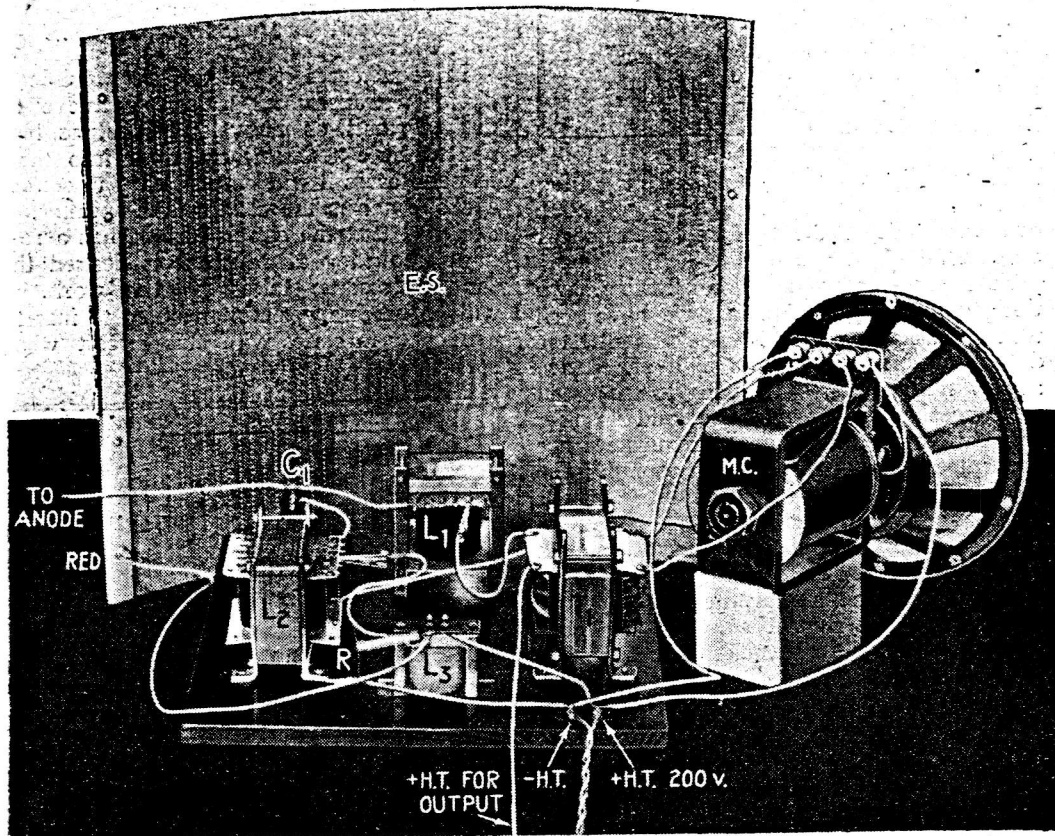

Experimental layout showing connections of electrostatic and moving-coil units together with filter components.


Dual Loud Speaker.

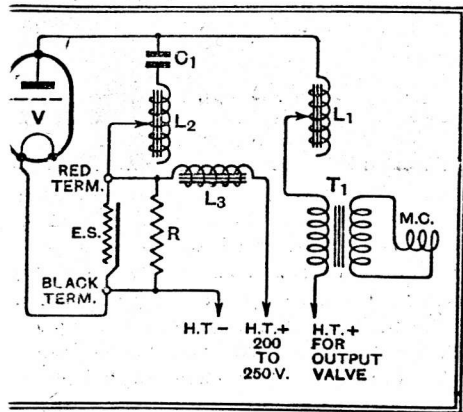one, as it is difficult to "desensitise" the inductive without impairing its performance.



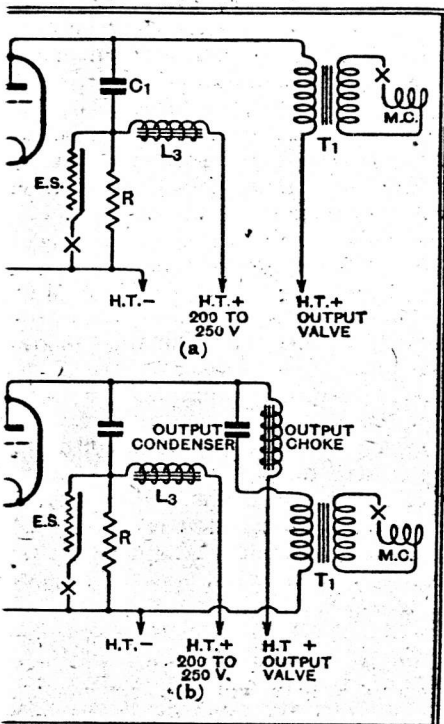5.—The complete schematic diagram. L_1 , 1 henry (tapped); L_2 , 0.2 henry (tapped); L_3 , 100 henrys; C_1 , 1 mfd.; R , 250,000 ohms; T_1 , moving-coil output transformer; T_2 , moving-coil loud speaker; E.S., "Primustatic" loud speaker; V , output valve. If matching transformer T_2 of Fig. 4 is used, one winding replaces E.S. in the above diagram, and E.S., R and L_3 are connected to the other winding.

assuming now that we have the two loud speakers of approximately equal sensitivity, that the complete unit has been assembled, a local station should be tuned in the lead removed from the red terminal of the "Primustatic" loud speaker. The tuning on the choke L_1 must now be varied until there is a marked cut-off at 2,000 cycles on the moving-coil speaker. The listener may well ask how he will know when this cut-off is at this figure. It can be said that speech and music should sound very "flat" and, if the loud speaker normally "grunts" at about 2,000 cycles (a common fault), all trace of brightness or shrillness should be removed. Now, reconnect the "Primustatic" loud speaker and remove the



6.—Connecting the two loud speakers for matching sensitivity. (a) Straight transformer output; (b) Choke output.

field supply from the moving-coil unit; if of the permanent magnet type disconnect one of the leads from the output transformer secondary winding. Adjust the tapping on the choke L_2 until all trace of lower frequencies has disappeared and the reproduction is so shrill as to be irritating. We can assume, somewhat casually, no doubt, that frequencies up to about 1,000 cycles have been removed. Returning the moving-coil speaker to its normal condition will result in a combination which ought to sound very pleasant indeed, but if the higher frequencies sound weak, it will be advisable to experiment with a suitable transformer feeding the electrostatic loud speaker as suggested earlier in this article and illustrated diagrammatically in Fig. 4.

It should be borne in mind that the dual unit has no better bass performance than the moving coil alone, and if this latter "grunts" at low frequencies, the combination will grunt also. The high-frequency response will, however, be so greatly improved as to commend the dual loud speaker to all discriminating listeners. The moving-coil loud speaker shown in the illustration has

been chosen as one not hitherto on the market, and it is hoped thus to avoid criticism from the maker of any particular brand of loud speaker who might object to any public attempt to alter the performance of his product, or from competitive makers who might equally strongly object to any one make being singled out for rejuvenation treatment. The device will work with a moving-coil speaker, and the excellence otherwise of the original bass response will be a measure of the total excellence of the whole. The normal power-handling capacity of the "Primustatic" loud speaker is rather less than one watt, but the combination will handle 5 watts A.C. without distress, and readers with output valves of the L.S.6a type need have no hesitation in making up the arrangement as described. If the two loud speakers are not to be built into one cabinet they should be as close together as possible to avoid hearing separately the complementary halves of the frequency response of the two loud speakers. As there is only slight focusing of the high frequencies from the electrostatic speaker, the general diffusion of sound will be found very pleasing.

NEWS BY TELEVISION

A New Marconi System.

APPARATUS has now been evolved by the Marconi Company for the commercial transmission of news by television. This is one of the applications of television which do not necessarily involve the use of wide frequency bands; the new instrument can be operated satisfactorily on a medium long wave of 1,000 metres.


It is designed to transmit images of a moving tape on which characters are printed by a special typewriter. The light source is a 1,000-watt gas-filled metal-filament projector lamp mounted vertically with a reflector behind it. The light passes through a spherical condenser lens system, on to a reflecting mirror and an aperture, and thence through a system of lenses mounted in a spiral on a lens drum. There are fifteen such lenses on the drum, and the picture repetition frequency corresponding to the speed of the drum is twenty per second.

The Photo Cell Amplifier.

A sharp image of the aperture is projected by each lens on the tape, and is swept over it by the lens drum motion. The tape is carried vertically between two rollers, the bottom one of which is driven through suitable gearing by the same motor that drives the lens drum, and the tape can be given a speed of either 60 or 120 w.p.m. Behind the tape is mounted the photo cell and photo cell amplifier, both of which are contained in a single shielded unit. The lens drum driving motor is maintained at constant speed by means of a synchronous motor controlled by a tuning fork mounted in the bottom of the frame under the lamp house. Above the tuning fork is the fork amplifier unit, and above that is the control unit for the whole system. The frame which supports the lens wheel and tape drive carries two panels, the lower one being the line amplifier and the other the synchronising circuit, which sends out a special signal with the picture signal for the purpose of keeping the receiver scanning motor in step.

In this type of transmitter the frequency band necessary depends on the number of letters shown at the same time in the picture,

and a convenient method of adapting the television transmission to any width of band available is therefore to alter the length of the picture, which alters the number of letters shown accordingly. Thus, the frequency band required by the apparatus described is 13 k/c but by reducing the distance between the lenses on the drum which shortens the picture length and reduces the number of letters shown this band width can be reduced to any convenient value.

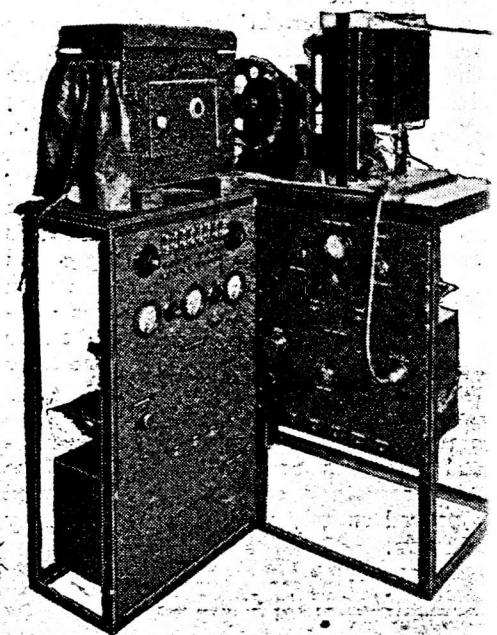

The new Marconi television transmitter designed for operation on the long waveband. The visual transmission of typed news bulletins is suggested.

The receiver shows a long, narrow picture having a size dependent on the power of the modulated light source, and with existing facilities pictures can be obtained from a few inches in length up to several feet.