

## ID STRVILL INSHHHHHHHHH OLD HENGELING FOR

proved by AICTE New Delhi & Govt. of Maharashtra, Affiliated to University of Mumbai (Religious Jain Minority)

### **Chapter 1: DC Circuits**

- 1. What is Resistance, Inductance and capacitance?
- 2. State ohms law. Where it is not applicable?
- 3. Define voltage, current
- 4. What are dependent and independent sources
- 5. What is source transformation
- 6. State kirchoffs laws.
- 7. Identify series and parallel circuits
- 8. What is star and delta connection? state formulas for transformations
- 9. Identify Star and delta networks and do conversion
- 10. Statements of Superposition, thevenins, nortons, max power theorem
- 11. What are internal resistances of ideal voltage source and current source?
- 12. What is the condition for max power transfer from source to load in any circuit?

### **Chapter 2: AC Circuits**

- 13. What is DC and AC supply? Difference between them
- 14. Generation of DC and AC voltages with emf equations
- 15. What is period, frequency, average, rms, peak amplitude, phase difference, leading, lagging waveform
- 16. Define amplitude factor and form factor
- 17. What is rms and average value of pure sinusoidal waveform
- 18. What is power factor? Should be high or low. Explain
- 19. Add and subtract following signals and find resultant:
  - $V_1 = 10 \sin (wt+30)$ ,  $V_2 = 20 \cos (wt+70)$
- 20. If AC supply is given to Resistor, draw phasor diagram. What will be power factor
- 21. If pf is unity, circuit contains which component?
- 22. If total impedance angle is negative, pf is lagging or leading?
- 23. If AC supply is given to pure Inductor, draw phasor diagram. What will be power factor
- 24. If AC supply is given to pure Capacitor, draw phasor diagram. What will be power factor
- 25. If AC supply is given to choke coil, draw phasor diagram. What will be power factor
- 26. If AC supply is given to Resistor- capacitor circuit, draw phasor diagram. What will be power factor
- 27. Draw impedance, power and voltage triangle for RL and RC circuit
- 28. How many powers are involved in AC circuits. Which are they? Explain each one
- 29. What are concepts of susceptance, conductance, admittance for parallel circuits
- 30. What is Resonance? Difference between series and parallel resonance.
- 31. What is dynamic impedance?
- 32. What is concept of 3 dB bandwidth in resonance graph
- 33. What is Quality factor? Justify it should be high or low



# (Approved by AICTE New Delhi & Govt. of Maharashtra, Affiliated to University of Mumbai) (Religious Jain Minority)

#### **Chapter 3: Three phase Circuits**

- 34. What is difference between single phase and polyphase system
- 35. What is phase sequence for three phase system. What is phase difference between each phase? And why?
- 36. Explain three phase supply generation
- 37. Draw phasor diagram and waveform for three phase supply
- 38. What are advantages and applications of three phase system
- 39. What is concept of phase voltage, phase current, line voltage, line current
- 40. Explain Balanced load and balanced supply system
- 41. What is relation between phase voltage and line voltage for star and delta connection
- 42. What is relation between phase current and line current for star and delta connection
- 43. What is impedance and power relation between star and delta connections
- 44. Phasor diagram for star and delta connection
- 45. What are methods of power measurement in three phase system? Which method is more preferable and why?
- 46. Explain advantages of three phase system

### **Chapter 4: Single phase transformers**

- 47. Explain working of transformer with emf equation
- 48. What is transformation ratio
- 49. Explain constructional details and types of transformer
- 50. What is kva rating of transformer? What is full load current? No load current?
- 51. What are losses in transformer
- 52. What is practical transformer? Draw and explain
- 53. Draw phasor diagram for ideal transformer with no load
- 54. Draw phasor diagram for practical transformer with no load
- 55. What are two components of no load current
- 56. Draw equivalent circuit of transformer
- 57. Define voltage regulation with formula
- 58. Define efficiency with formula
- 59. What is oc test and sc test and where it is used
- 60. In a transformer primary and secondary voltages are \_\_\_\_\_\_0 out of phase

### **Chapter 5: Electrical Machines**

- 61. Explain principle of operation of Three-phase induction motor.
- 62. What are the different parts used in three phase induction machine.