




SHRI BALAJI STATIONERS © 8949469034

M. B. M. UNIVERSITY
JODHPUR

Date Experiment No. P. No.
Name V.I. KRAM SOLANKI Faculty No. Class BE-1st year Batch H-4

INDEX

S.No	EXPERIMENT	Page/s	Remark
1.	Convert galvanometer to ammeter	1-5	} May 13/19/20
2.	Convert galvanometer to Voltmeter	6-10	
3.	Study of RC circuit	11-12	
4.	Study of LCR circuit	13-14	} May 5/19
5.	determine refractive index and dispersive power of prism	15-16	
6.	To study characteristics of charging and discharging of Capacitor	21-24	} May 23/19
7.	To determine the wavelength of light by plane diffraction grating	17-20	
8.	To find wavelength of light by Newton's Ring method.	25-27	

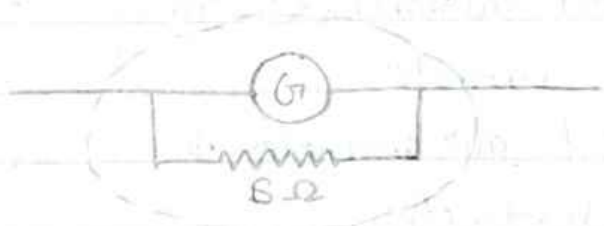

Ammeter of Range
 $I = 3 \text{ Amp}$



M. B. M. UNIVERSITY JODHPUR

Date 22/09/23 Experiment No. 1 P. No. 1
Name Vikram Solanki Faculty No. Class BE 1st year Batch H-9

Object- To convert a galvanometer into an ammeter of given range & to calibrate it.

Apparatus required- Galvanometer, Battery accumulator, ammeter of range as required for conversion, high & low resistance box, rheostat, plug key, connecting wires & screw gauge.

Theory- A galvanometer can be converted to an ammeter by putting a low resistance shunt in parallel to its coil. whose value is given by

$$S = \frac{I_g \times G}{I - I_g}$$

Here, I = Range of ammeter (given 3 amp)

G = Resistance of galvanometer

I_g = Current required for full scale deflection in galvanometer scale (Here $N=30$)

$$\text{Also } I_g = N \times C_s$$

where N = Total no. of divisions on galvanometer (30)

C_s = Current sensitivity / Figure of merit

is defined as minimum amount of current required for unit division deflection in galvanometer scale



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 2
Name Vikram Solanki Faculty No. Class Batch

Here, the value of shunt (S) comes out to be very small (less than 1Ω) therefore the length of a Copper wire required for the resistance of the amount of shunt S calculated in above formula

$$l = \frac{S \times A}{\rho}$$

Here, $S = 0.031\Omega$

$\rho = 1.7 \times 10^{-6} \Omega \text{ cm}$

$A = \pi r^2$ (area of cross-section)

$r = 0.055 \text{ cm}$


Step 1: Determine the resistance of galvanometer (G) by half deflection method.

Step 2: Determine the current sensitivity (C_s) of given galvanometer.

Resistance of galvanometer, G and Current sensitivity (C_s) can be determined by circuit of half deflection method.

The procedure is as follows:-

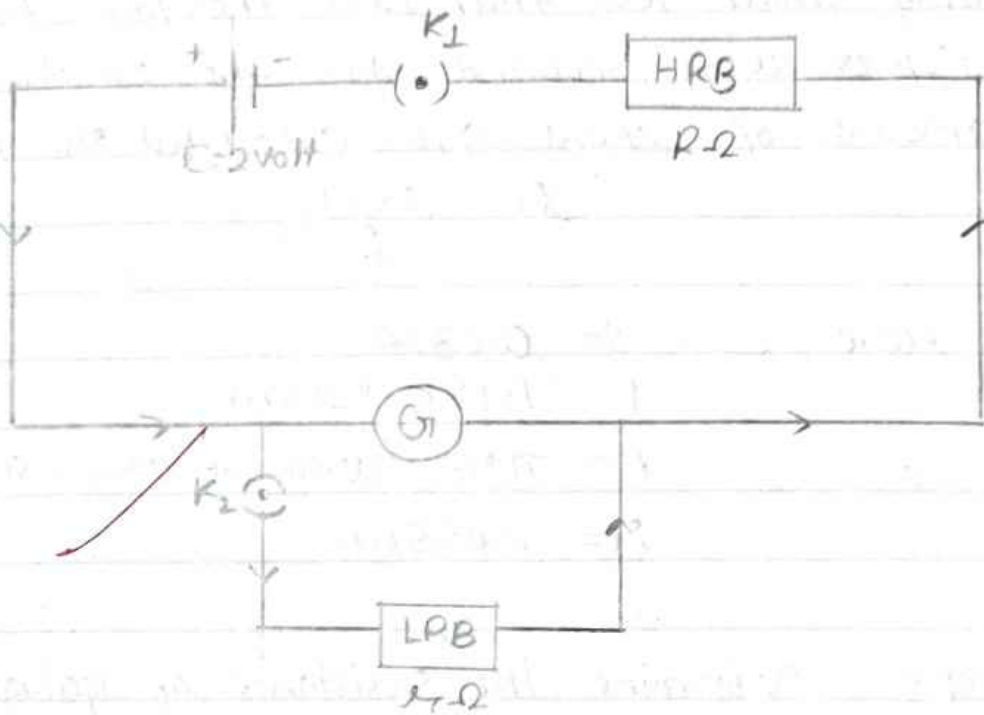1. Keep the key K_2 open & close key K_1 , apply load resistance R_2 from high resistance box. Due to this





M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 3
Name Nikesam Sulanki Faculty No. Class Batch

load current will flow in the circuit & the deflection is produced in galvanometer.

2. Note down the value of load resistance as R_L & the deflection in galvanometer as n (0-30)
3. Now without changing the value of load resistance (R_L) close the key K_2 also. the shunt resistance = r is now connected with galvanometer (LRB). Due to this the deflection in the galvanometer will decrease as some current flow through this LRB.
4. Now keep on changing the LRB value such that the deflection in galvanometer reduces to half i.e. $n/2$. Note down the value of load resistance (r) which is required to make half deflection in galvanometer
$$r = R_L$$

Observation

- (a.) For determining the resistance of the galvanometer.
- (b.) To determine the current sensitivity



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 4
 Name Vikram Solanki Faculty No. Class Batch

S.No	Resistance	Deflection in galvanometer	IRB required for half deflection	$n =$ R/R	Mean G	$C_s = \frac{E}{(R+n)G}$ (amp/div)	mean C_s
	HRB R/R	(m)	R/R				
1	10100	12	200	200		1.51×10^{-5}	1.48×10^{-5}
2	8610	16	200	200	200	1.41×10^{-5}	
3	7610	18	200	200		1.42×10^{-5}	

$$\text{Mean } G = 200$$

$$\text{Mean } C_s = 1.48 \times 10^{-5}$$

Step 3: To calculate $I_g = C_s \times N = 44.4 \times 10^{-5}$


Step 4: For conversion of galvanometer into ammeter of range $I = 3\text{amp}$, calculate the value of required shunt using the formula.

$$S = \frac{I_g \times G}{I - I_g} = \frac{44.4 \times 10^{-5} \times 200}{3 - 44.4 \times 10^{-5}} = 0.029$$

$$S = 0.029$$

Here, the S is very small (less than 1Ω), so the length of wire used as shunt is given by
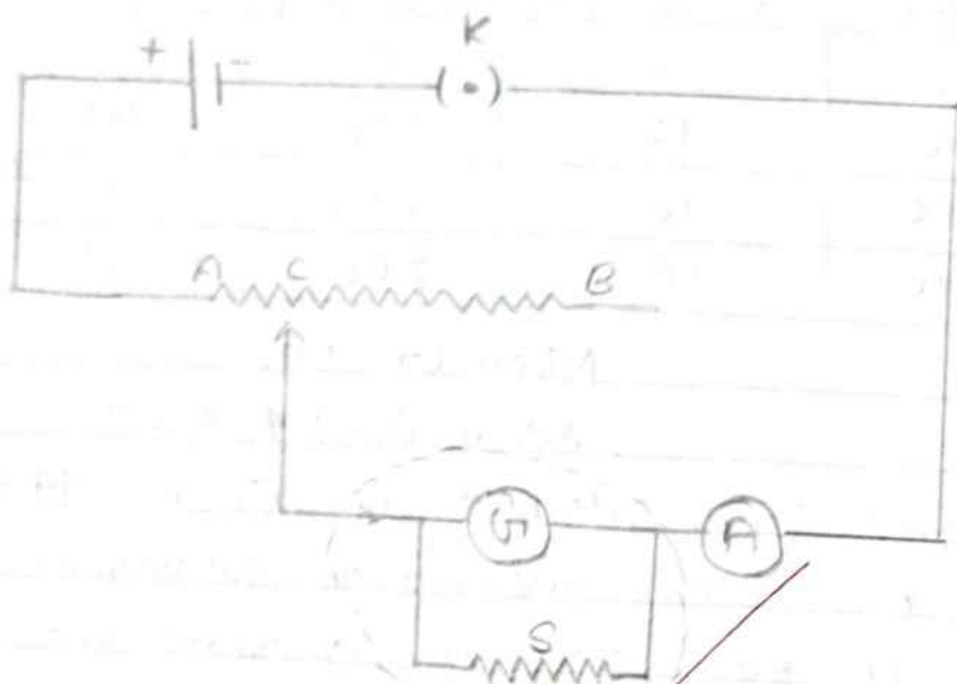
$$L = \frac{S \times A}{\rho} = \frac{0.029 \times \pi \times (0.055)^2 \times 10^{-4}}{1.7 \times 10^{-8}} = 162.03 \text{ cm}$$



CALIBRATION OF CONVERTED GALVANOMETER



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 5
Name Vikram Solanki Faculty No. Class Batch

Step 5: Calibration

The galvanometer is converted into ammeter by connecting the shunt wire of length as calculated
least count of shunted = $\frac{\text{Range}}{N} = \frac{3}{30} = 0.1 \text{ amp}$

galvanometer (converted ammeter)

Least count of actual ammeter-

S.No	Reading of shunted galvanometer		Actual ammeter	Error
	In division	In amp. (I) (div x LC) amp	reading I' amp	$\Delta I = I - I'$
1.	5	0.5	0.5	0
2.	7	0.7	0.75	0.05
3.	12	1.2	1.25	0.05

Result To convert given galvanometer of $U_n = 200$ into ammeter of range 3A, shunt required $S = 0.029$ & length of shunt wire connected is $l = 162.03 \text{ cm}$

13/10

Precautions (1) All connections should be tight.

(2) The accumulator should be charged & there should be no error in galvanometer reading (point to zero)

(3) The emf of battery should be greater than range of converted galvanometer.

M. B. M. UNIVERSITY
JOLAPUR



Voltmeter of Range 3V



M. B. M. UNIVERSITY JODHPUR

Date 22/09/23 Experiment No. 2 P. No. 6
Name Vikram Solanki Faculty No. Class BE 1st year Batch 11-4

Object - To convert galvanometer into a voltmeter of range 3 volt & calibrate it.

Apparatus required - Galvanometer, accumulator, ammeter, high resistance box, rheostat, plug key, screw gauge, connecting wires.

Theory & Principle - To convert galvanometer into a voltmeter of specific range (say $V=3V$) The required value of series resistance to be connected to galvanometer is calculated by the formula.

$$R = \frac{V}{I_g} - G$$

Where V = Range of voltmeter (given 3V)


G = Resistance of galvanometer

I_g = current required for full scale deflection in galvanometer scale

$$\text{Also } I_g = N \times C_s$$

N = Total no. of divisions on galvanometer scale $N=30$

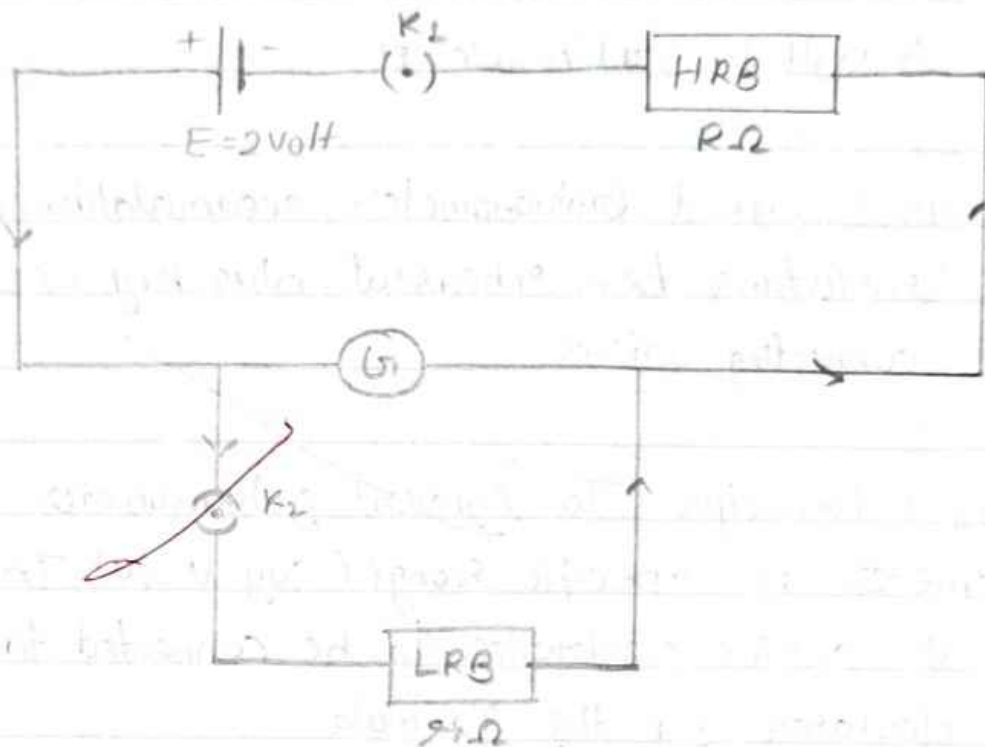C_s = current sensitivity is defined as minimum amount of current required for unit division deflection in galvanometer scale.



CIRCUIT OF HALF DEFLECTION METHOD



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 7
Name Vikram Solanki Faculty No. Class Batch

Step(I): Determine the resistance of galvanometer (G) by half deflection method

Step(II): Determine the current sensitivity (C_s) of given galvanometer

Resistance of galvanometer (G) & Current sensitivity (C_s) can be determined by one common circuit used in half deflection method.

The procedure is as follows:-

4. Keep the key K_2 open & close key K_1 . apply load resistance R_L by high resistance box (HRB). Due to this load resistance current will flow in circuit & a deflection is produced in galvanometer.
5. Note down the value of load resistance as R_L & the deflection in galvanometer as n (lies 0-30)
6. Now without changing the value of load resistance (R_L) close key K_2 also. The shunt resistance (S) from LRB is now connected with galvanometer. Due to this the deflection in galvanometer will decrease as some current will also flow through LRB.
7. Now keep on changing the LRB value such the deflection



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 8
Name Vikram Solanki Faculty No. Class Batch

In galvanometer reduces to half i.e. $n/2$. Note down the value of r_n which is required to make half deflection in galvanometer

$$G = r_n$$

Repeat the procedure for 3 observations.

- for determining the resistance of galvanometer.
- for calculation of current sensitivity.

Observation table


S.No	Resistance from HRB (R_n)	Deflection in Galvanometer	1 RB for half deflection $n/2$	$G = r_n$	Mean $G = r_n$	$C_s = \frac{E}{(R_n) \theta}$ Amp/Div	Mean C_s
1	10,100	12	200	200		1.61×10^{-5}	
2	8610	16	200	200	200	1.41×10^{-5}	1.48×10^{-5}
3	7610	18	200	200		1.42×10^{-5}	10^{-5}

$$\text{Mean } G = 200$$

$$\text{Mean } C_s = 1.48 \times 10^{-5}$$

Step 3 : Calculate $I_g = C_s \times N = 44.4 \times 10^{-5}$

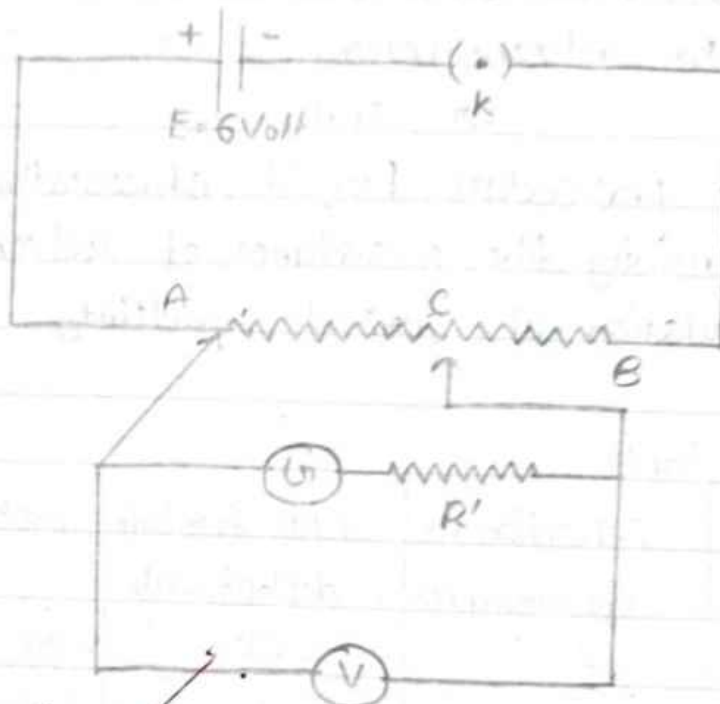Step 4 : For the conversion of galvanometer into voltmeter of range $V = 3 \text{ volt}$. Calculate the value of series resistance required to connect with the galvanometer using the formula.



CIRCUIT OF CALIBRATION OF
CONVERTED GALVANOMETER



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 9
Name Vikram Silanki Faculty No. Class Batch

$$R' = \frac{V}{I_g} - G = \frac{3}{49.4 \times 10^{-5}} - 200$$

$$R' = 6556.75$$

$$\text{Least Count of converted Voltmeter} = \frac{\text{Range}}{N} = \frac{3}{30} = 0.1 \text{ V}$$

Step(5) : Calibration of converted galvanometer.

(B) Observation table for calibration of converted galvanometer after conversion-

$$\text{Least Count of convert galv.} = \frac{3}{30} = 0.1 \text{ V}$$

$$\text{Least Count of actual Voltmeter} = 0.05 \text{ V}$$

$$\text{Series Resistance } R \text{ to be connected} = 6556.75 \Omega$$

S.No Reading of converted galvanometer

	In division	In volts (division $\times$ L.C.) (V Volts)	Actual Voltmeter Reading	Error $\Delta V = V' - V$
1.	2	$2 \times 0.1 = 0.2$	$6 \times 0.05 = 0.3$	0.1
2.	2.5	$2.5 \times 0.1 = 0.25$	$12 \times 0.05 = 0.6$	0.35
3.	4	$4 \times 0.1 = 0.4$	$18 \times 0.05 = 0.9$	0.5



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 10
Name Vikram Solanki Faculty No. Class Batch

Result- For conversion of given galvanometer of resistance $G = 200$ into a voltmeter of range $3V$, the required value of series resistance is $R' = 6556.75 \Omega$

Precautions-


- (1) The accumulator should be fully charged.
- (2) In the beginning of galvanometer needle should read zero scale division, otherwise there will be some error.
- (3) The emf of battery should be greater than the range of converted galvanometer to voltmeter.

Mey
06/10/2023

YTIENHVIU . M . S . M

PHYSICS

CIRCUIT DIAGRAM

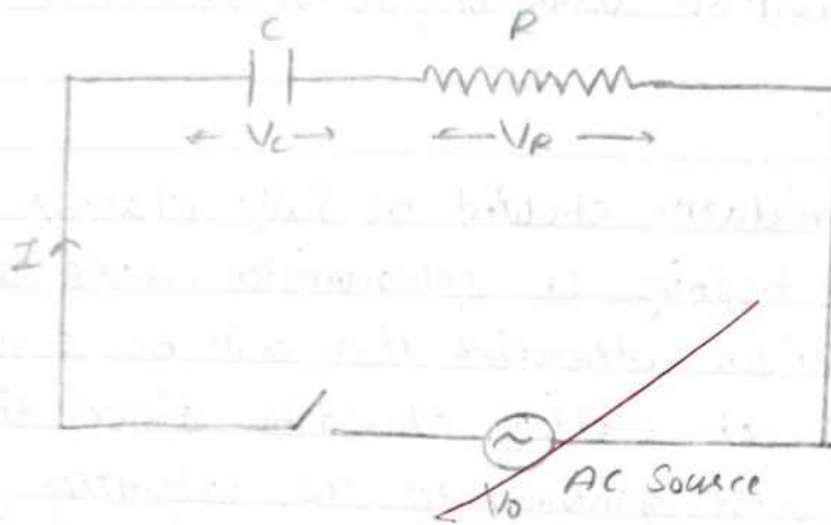



M. B. M. UNIVERSITY JODHPUR

Date 6/10/23 Experiment No. 03 P. No. 11
Name Vikram Salanki Faculty No. Class BE 1st year Batch H-9

Object- To study the phase relationship between voltage and current in RC circuit with AC Voltage.

Apparatus required- CR(AC) Circuit board, multimeter and connecting wires.

Theory- When an AC voltage is applied across a capacitor resistor combination, the voltage across capacitor & resistor add according to

$$\vec{V}_0 = \vec{V}_R + \vec{V}_C$$

where, $\vec{V}_0$, $\vec{V}_R$ and $\vec{V}_C$ are applied voltage, voltage across R & C respectively. As voltage across capacitor lag behind the voltage across the resistor by 90° (Phase difference $\pi/2$)

$$V_0 = \sqrt{V_R^2 + V_C^2}$$

Here

V_R is in phase component as the current is always in phase with V_R

The phase difference ' θ ' b/w current I and V_0 (applied voltage) is given by-

$$\tan \theta = \frac{1}{\omega RC} = \frac{1}{2\pi f RC} \quad f = 50 \text{ Hz}$$

Calculations

(9) $V_c = 21.8 \text{ V}$; $V_R = 15.5 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$

$$= \sqrt{(21.8)^2 + (15.5)^2} = 26.75$$

(10) $V_c = 23.5 \text{ V}$; $V_R = 12.5 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$

$$= \sqrt{(23.5)^2 + (12.5)^2} = 26.62$$

(11) $V_c = 25.9 \text{ V}$; $V_R = 6.1 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$

$$= \sqrt{(25.9)^2 + (6.1)^2} = 26.60$$

(12) $V_c = 26.3 \text{ V}$; $V_R = 3.9 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$

$$= \sqrt{(26.3)^2 + (3.9)^2} = 26.58$$

(13) $V_c = 21.5 \text{ V}$; $V_R = 15.6 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$

$$= \sqrt{(21.5)^2 + (15.6)^2} = 26.56$$


(14) $V_c = 14.8 \text{ V}$; $V_R = 22.4 \text{ V}$

$$V_o = \sqrt{V_c^2 + V_R^2}$$


$$= \sqrt{(14.8)^2 + (22.4)^2} = 26.84$$

Scale

On x-axis 1 unit = 5 Volt

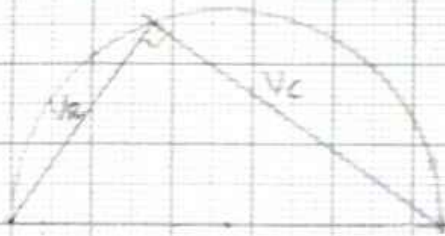

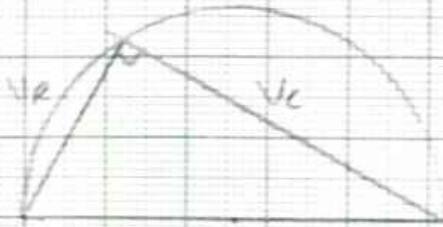
$$\begin{aligned} V_0 &= 26.75 \\ V_R &= 15.5 \\ V_C &= 22 \end{aligned}$$




$$\begin{aligned} V_0 &= 25.62 \\ V_R &= 12.5 \\ V_C &= 24 \end{aligned}$$



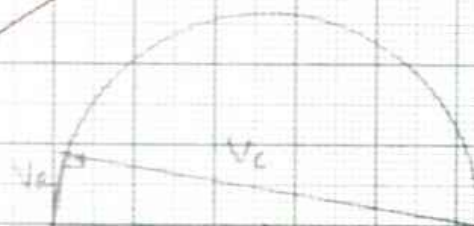
$$\begin{aligned} V_0 &= 25.50 \\ V_R &= 5.1 \\ V_C &= 25.5 \end{aligned}$$


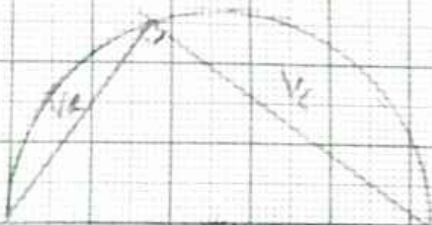
$$\begin{aligned} V_0 &= 25.58 \\ V_R &= 3.9 \\ V_C &= 26 \end{aligned}$$


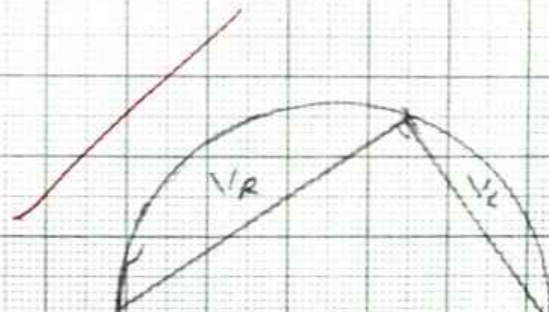
$$\begin{aligned} V_0 &= 26.56 \\ V_R &= 15.6 \\ V_C &= 21.5 \end{aligned}$$



$$\begin{aligned} V_0 &= 26.84 \\ V_R &= 22.4 \\ V_C &= 15 \end{aligned}$$



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. 03 P. No. 12
Name Vikram Solanki Faculty No. Class Batch


OBSERVATION TABLE-

SNo	C (μF)	R ($k\Omega$)	V_C (V _{OH})	V_R (V _{OH})	$V_0 = \sqrt{V_R^2 + V_C^2}$	V_C (graph)	θ	θ (graph)
1.	0.47	4.7k	21.8	15.5	26.75	22	54.58	55
2	0.33	4.7k	23.5	12.5	26.62	24	61.99	61
3.	0.33	2.2k	25.9	6.1	26.60	25.5	76.74	75
4.	0.22	2.2k	26.3	3.9	26.58	26	81.56	80
5.	0.22	1.0k	21.5	15.6	26.56	21.5	59.03	54
6	0.47	1.0k	14.8	22.4	26.84	15	33.45	34

Result:

- (1) It is clear and verified from table that addition of V_R and V_C follows vector addition law.
- (2) Measured value of V_0 match with found from figure.
- (3) The values of phase difference θ from formula match with those found from vector diagram.

CIRCUIT DIAGRAM -

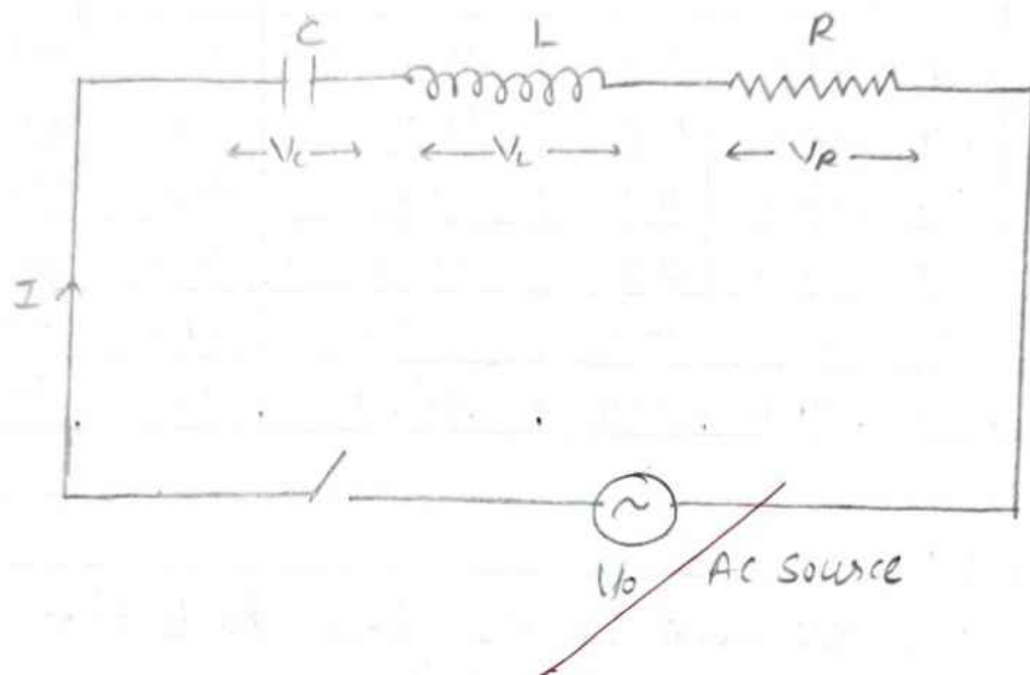



M. B. M. UNIVERSITY JODHPUR

Date 6/10/2023 Experiment No. 04 P. No. 13
Name Vikram Salunki Faculty No. Class BE 17 Jan Batch H-4

Object To study voltage and phase relationship between a series LCR (AC) circuit.

Apparatus required- LCR circuit board, multimeter and connecting wires.

Theory- IF an AC Voltage is applied across LCR component connected in series, the addition of voltage is governed by vector addition law as

$$\vec{V}_0 = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

Here, $\vec{V}_R$, $\vec{V}_L$, $\vec{V}_C$ are voltage across R, L, C respectively and $\vec{V}_0$ is applied voltage.

The current flowing in the circuit always remains in the phase with V_R where as voltage across 'L' leads the current phase by ' $\pi/2$ ' and across 'C' lags behind by ' $\pi/2$ '

Hence

$$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\text{i.e. } V_0^2 = I^2 (R^2 + (\omega L - 1/\omega C)^2)$$

Phase difference between current I & applied voltage is given as

$$\tan \theta = \frac{V_L - V_C}{V_R} = \frac{I(\omega L - 1/\omega C)}{IR} = \frac{(\omega L - 1/\omega C)}{R}$$

Calculations &

(i) $V_L = 7.1V$, $V_C = 19.5V$, $V_R = 19.2V$


$$\begin{aligned} V_0 &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{(19.2)^2 + (7.1 - 19.5)^2} \\ &= \sqrt{(19.2)^2 + (-12.4)^2} = 22.85 \end{aligned}$$

(ii) $V_L = 8.4V$, $V_C = 14.1V$, $V_R = 21.3$

$$\begin{aligned} V_0 &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{(21.3)^2 + (8.4 - 14.1)^2} = \\ &= \sqrt{(21.3)^2 + (-5.7)^2} = 22.04 \end{aligned}$$

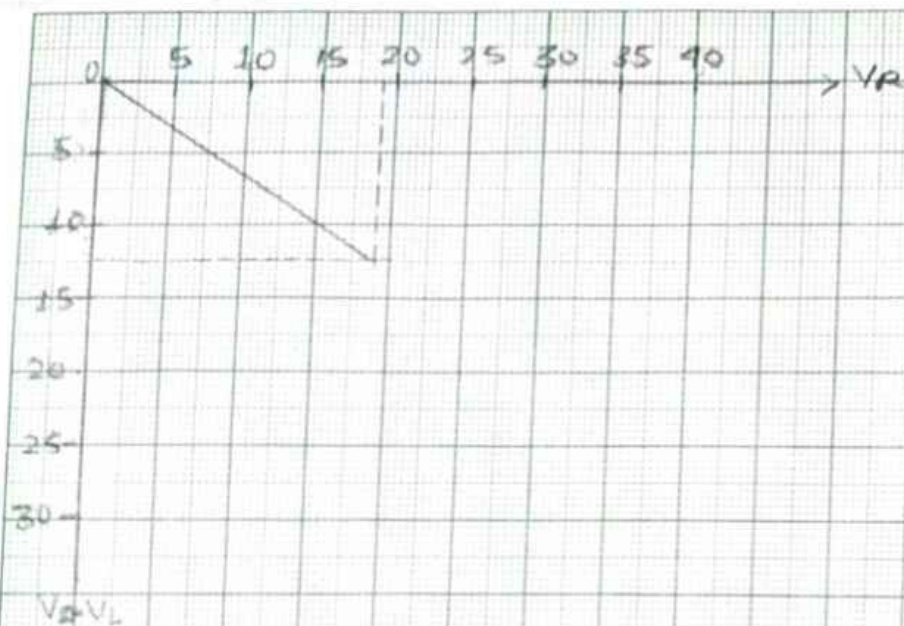(iii) $V_L = 8.7$, $V_C = 11.3$, $V_R = 21.8$


$$\begin{aligned} V_0 &= \sqrt{V_R^2 + (V_L - V_C)^2} \\ &= \sqrt{(21.8)^2 + (8.7 - 11.3)^2} \\ &= \sqrt{(21.8)^2 + (-2.6)^2} = 21.99 \end{aligned}$$



$$C = 0.22 \mu F$$

$$V_C - V_L = 12.4 V$$


$$V_R = 19.2$$

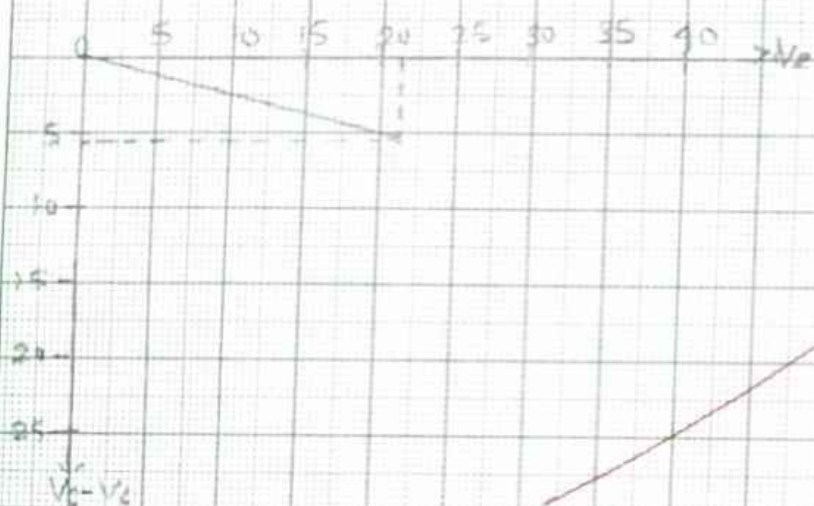

$$C = 0.33 \mu F$$

$$V_C - V_L = 5.7 V$$

$$V_R = 21.3 V$$

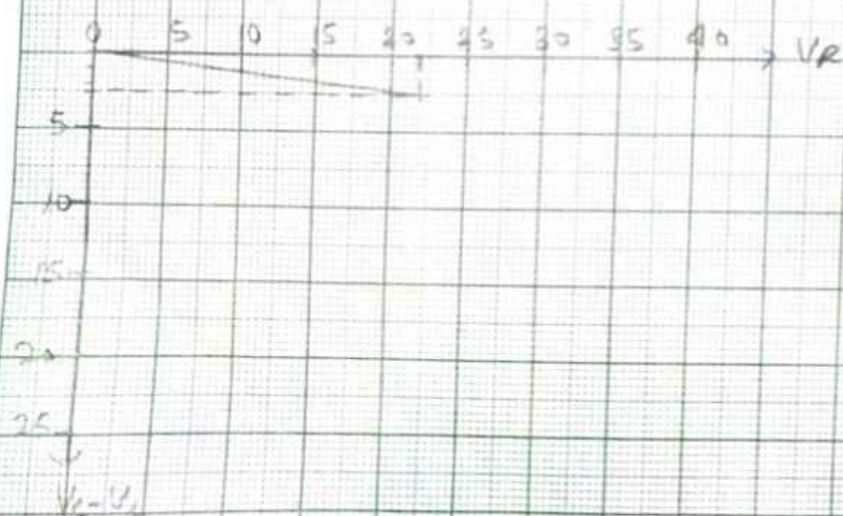

$$C = 0.47 \mu F$$

$$V_C - V_L = 2.6 V$$

$$V_R = 21.8 V$$



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. 04 P. No. 14
Name Vikram Solanki Faculty No. Class Batch

V_R is a phase component as the current is always in phase with V_R

OBSERVATION TABLE


SNo	C (UF)	V_L (V)	V_C (V)	V_R (V)	$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$ (V)	V_0 (graph)	$\theta = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$	θ (graph)
1.	0.22	7.1	19.5	19.2	22.85	24	-32.85	-33°
2.	0.33	8.4	14.1	21.3	22.04	22	-14.98	-14.5°
3.	0.47	8.7	11.3	21.8	21.99	22	-6.80	-6.5°

Result


- (i) It has been verified that V_R , V_L and V_C adds by the law of vector addition.
- (ii) Value of V_0 obtained from the graph will be matched with applied voltage.
- (iii) Value of phase difference ' θ ' obtained from graph matches with calculated value.

Muy
13/10/2023

UNIVERSITY OF JALPAIGURI RUPNAGAR

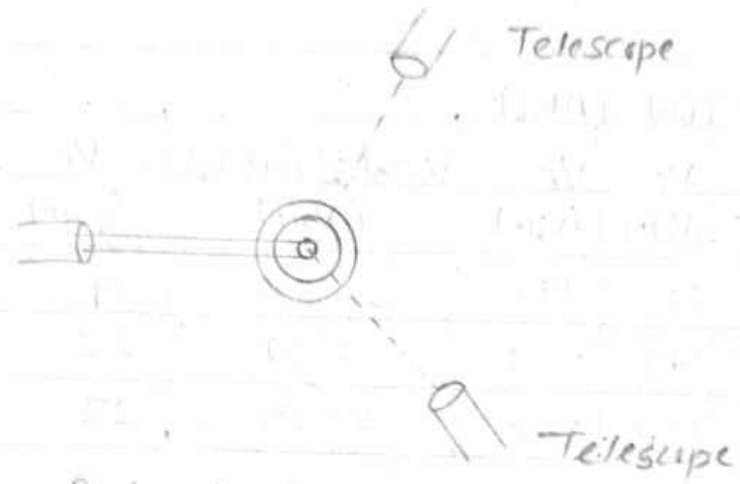

Determination of angle from prism

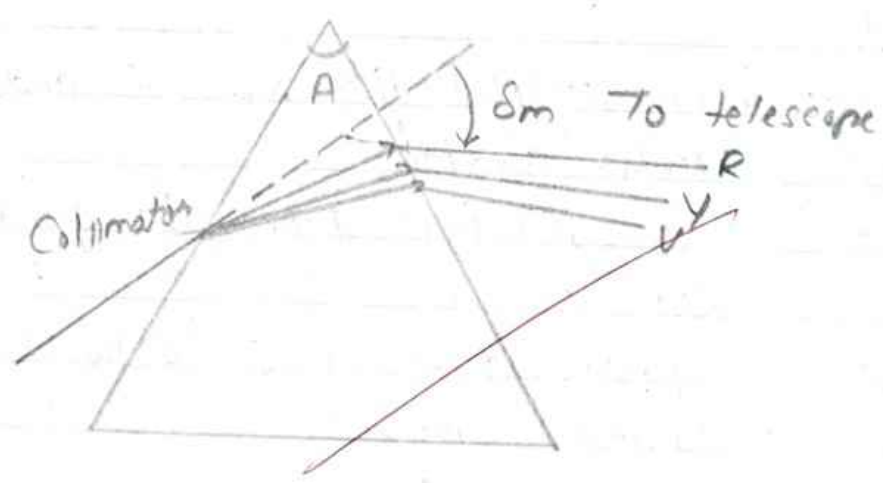



M. B. M. UNIVERSITY JODHPUR

Date 13/10/2023.. Experiment No. 05..... P. No. 15.....

Name VIKRAM SOLANKI.. Faculty No. Class BE 1st year Batch H-4...

Object- To determine refractive index & dispersive power of material of prism by using spectrometer.

Apparatus required- Spectrometer, reading lens, lamp, spirit level prism.

Theory- The refractive index of the material of prism is given by

$$\mu = \frac{\sin(A + \delta_m)}{2}$$

$$\sin(A/2)$$

Here, A = angle of prism

δ_m = angle of minimum deviation

$$\text{Dispersive power } (\omega) = \frac{\mu_y - \mu_r}{\mu_y - 1}$$

Observation.

The observations noted using the apparatus is-

(i) Angle of prism (given) = 60°

(ii) Value of 1 division on main scale = $(1/2)^\circ$ total divisions on circular scale

L.C of circular scale = $(\frac{1}{120})^\circ$

Calculations &

given angle of prism = 60°

(i) Angle of min^m deviation for extreme violet colour

$$S_v = 24^\circ 6' 0''$$

Refractive Index of violet colour

$$\mu_v = \frac{\sin\left(\frac{60 + 24.0}{2}\right)}{\sin\left(\frac{60}{2}\right)}$$

$$= 1.36$$

(ii) Angle of min^m deviation for extreme red colour

$$S_r = 24^\circ 7' 12''$$

Refractive Index of Red colour

$$\mu_r = \frac{\sin\left(\frac{60 + 24.12}{2}\right)}{\sin\left(\frac{60}{2}\right)}$$

$$= 1.34$$

(iii) Angle of min^m deviation for extreme yellow colour

$$S_y = 23^\circ 58' 12''$$

Refractive Index of yellow colour

$$\mu_y = \frac{\sin\left(\frac{60 + 23.97}{2}\right)}{\sin\left(\frac{60}{2}\right)}$$

$$= 1.38$$

$$\text{So } W = \frac{\mu_v - \mu_r}{\mu_y - 1} = \frac{1.36 - 1.34}{1.38 - 1}$$

$$= 0.052$$



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. 05 P. No. 16
Name Vikram Salanki Faculty No. Class Batch

(11.) For minimum deviation (Sm)

Least count of spectrometer = $\left(\frac{1}{2}\right)' - 30''$

Spectral line	Circular line	Reading of circular scale for min ^m deviation			Direct Image position			Sm (a-b)
		MS	VS	Total (a)	MS	VS	Total (b)	
Red	V ₁	122.1	40	61°22'48"	74	32	37°15'36"	24°7'12"
Yellow	V ₁	122.2	16	61°13'48"	74	32	37°15'36"	23°58'12"
Violet	V ₂	122.3	25	61°21'36"	74	32	37°15'36"	24°6'0"

Result- The dispersive power of material of a given prism $w = 0.052$


Precautions: (i.) Prism should be clean.

(ii.) The edge of slit & prism should be perfectly vertical.

(iii.) All the adjustments should be made perfectly to obtain accurate angle.

(iv.) The Ramp illuminated should be saved from all jerks & movements.

May 20/10/2023

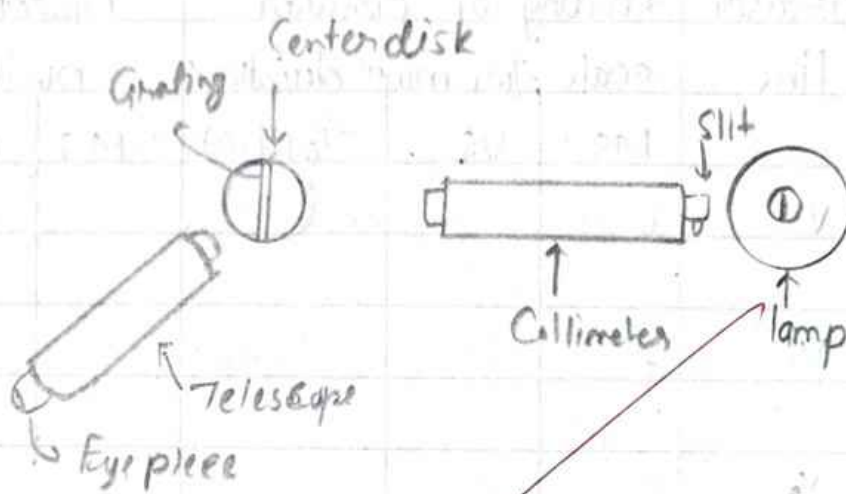



M.B.M. UNIVERSITY

JODHPUR

Date..... Experiment No. Q.6 P.No. 17

Name Vikram Solanki Faculty No..... Class BE 1st year H-4

Object - To determine the wavelengths of prominent lines of mercury by plane diffraction grating.

Apparatus required - A plane diffraction grating, spectrometer, mercury lamp, spirit level, reading lens.

Theory - The wavelength λ of a particular spectral line is calculated by the grating equation

$$(a+b) \sin \theta = n\lambda$$

$$\lambda = \frac{(a+b) \sin \theta}{n}$$

Where,

$(a+b)$ = Grating element

θ = Angle of diffraction and

n = The order of spectrum

Diffraction Grating - A diffraction grating is an arrangement of large number of parallel slits of same width and separated by equal opaque spaces is known as diffraction Grating.





M.B.M. UNIVERSITY

JODHPUR

Date..... Experiment No..... P.No. 18

Name Vikram Solanki Faculty No..... Class.....

Procedure :-

1. Note the least count of spectrometer.
2. The telescope from the position of direct image of slit is rotated left till the first order spectrum is seen in the field of view. Then the telescope is clamp near the red end of the spectrum. The telescope is then gradually rotated with the help of its tangential screw and its vertical cross wire is made to coincide the red, yellow, green and violet spectral lines one by one and each time reading of main scale and vernier are noted.
3. Now the telescope is turned on the right side of the direct image of slit and again the reading of the main scale and vernier are noted.
4. Then for the spectral lines of each color, find the difference of reading either side of slit for the same vernier. Take the mean find the half of it, which will give the angle of diffraction θ for the spectral lines of that color.

Observation :-

Value of 1 division on main scale = $(\frac{1}{2})^\circ$ total divisions on circular scale.

Calculations

(1) for violet colour.

$$\lambda = \frac{2.54}{15000} \times \sin(15^\circ 25' 48'')$$

$$= 1.69 \times 10^{-4} \times 0.264$$

$$= 4839.9 \text{ \AA}$$

(2) for green colour

$$\lambda = \frac{2.54}{15000} \times \sin(19^\circ 30')$$

$$= 1.69 \times 10^{-4} \times 0.333$$

$$= 5476.5 \text{ \AA}$$

(3) for yellow colour

$$\lambda = \frac{2.54}{15000} \times \sin(20^\circ 45' 36'')$$

$$= 1.69 \times 10^{-4} \times 0.354$$

$$= 5805.8 \text{ \AA}$$



M.B.M. UNIVERSITY

JODHPUR

Date..... Experiment No..... P.No. 19

Name Vikram Salanki Faculty No..... Class.....

L.C. of circular scale = $(\frac{1}{120})^{\circ}$

L.C. of spectrometer = $(\frac{1}{2})' = 30''$

Colour of light	Spectrum on left			Spectrum on Right			$\theta = \frac{(O-B)}{2}$	Mean θ	
	Reading of telescope			Reading of telescope					
	M.S.	V.S.	Total (b)	MS	V.S.	Total (b)			
Violet	V ₁	65	26	65°12'36"	96	8	96°4'11"	15.42	15°25'48"
	V ₂	246	18	246°9'10"	277	7	277°3'	15.45	
Green	V ₁	61	26	61°12'57"	100	9	100°4'12"	19.43	19°30'
	V ₂	242	6	242°3'	281	25	281°12'	19.57	
Yellow	V ₁	60	15	60°7'12"	102	10	102°4'48"	20.98	20°45'36"
	V ₂	241	12	241°13"	282	13	282°5'28"	20.55	

Result: Wavelength of various lines are given below

Colour	Standard wavelength, Å	observed (Å) n	error
Violet	3667.3 Å	4339.9 Å	
Green	4739.6 Å	5476.5 Å	
Yellow	5222.1 Å	5805.8 Å	

Precautions - (1) Spectrometer leveling and adjustments should be properly done.



M.B.M. UNIVERSITY

JODHPUR

Date..... Experiment No..... P.No. 20

Name Vikram Solanki..... Faculty No..... Class.....

- (ii) Setting up the collimator and telescope for parallel rays is essential.
- (iii) The formula used is for normal incidence of light on grating, hence this adjustment should be accurately done.
- (iv) The slit should be sharp and vertical, i.e. parallel to the rulings on the grating.



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. 06 P. No. 24
Name Vikram Salanki Faculty No. Class BE 1st year Batch H-4

OBJECT To study characteristics of charging and discharging of capacitor through a resistor.

APPARATUS REQUIRED-

CR circuit board (D-C), power supply (DC), digital voltmeter and connecting wires

THEORY When a capacitor and a resistance are connected in series and applied with a DC voltage of V_0 voltage, the capacitor begins to store the charge. During the charging of a capacitor, the voltage across the capacitor (V_c) is given as

$$V_c = V_0 (1 - e^{-t/RC})$$

And the voltage across the resistance (V_R), during charging is given as

$$V_R = V_0 e^{-t/RC}$$


The value of current is given as

$$I_R = \frac{V_0}{R} e^{-t/RC} = I_0 e^{-t/RC}$$


Where V_0 = Voltage applied through power supply

V_c = Voltage across Capacitor

V_R = Voltage across R.

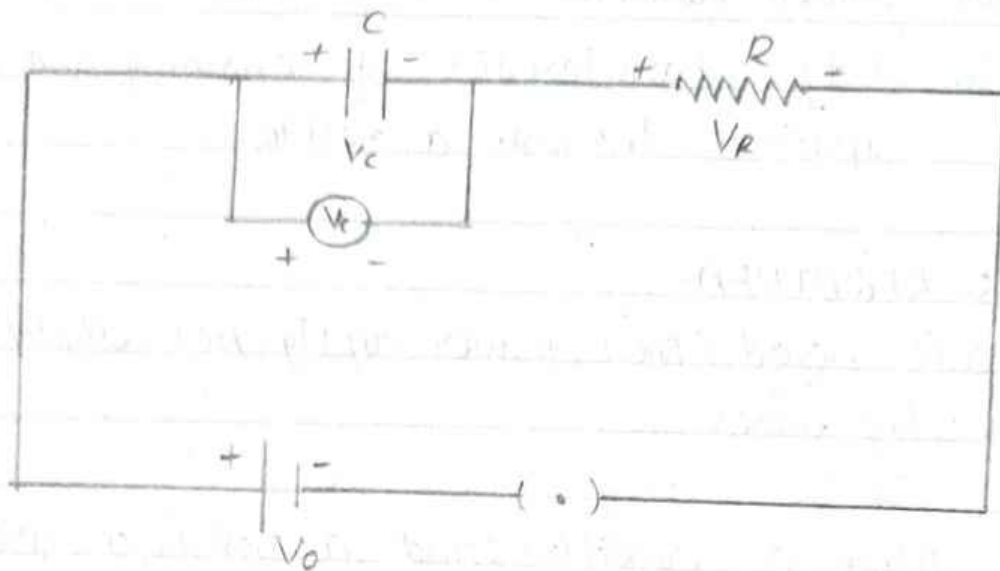

CHARGING CIRCUIT

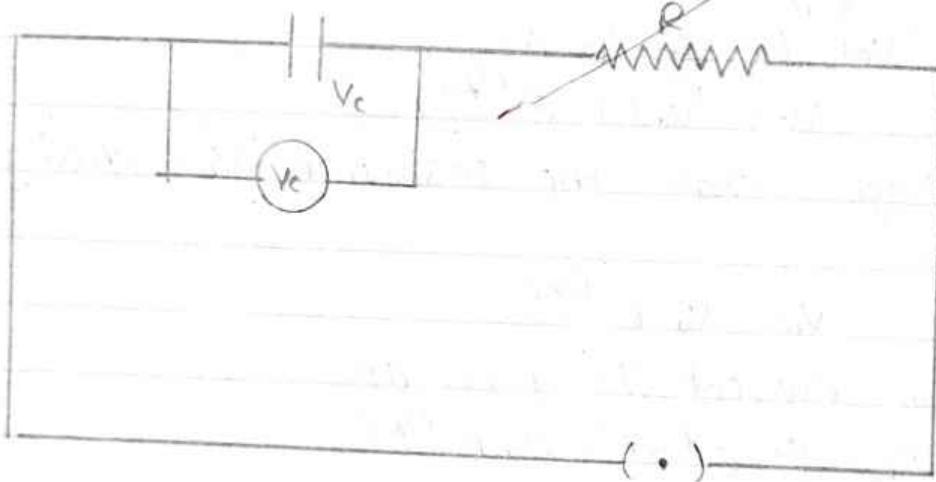

DISCHARGING CIRCUIT



M. B. M. UNIVERSITY JODHPUR

SHRI BALAJI STATIONERS © 8949469034

Date Experiment No. P. No. 22
Name Faculty No. Class Batch

For CR circuit the time constant is given as
 $\tau = CR$ ($\tau = \text{Time constant}$)

During discharging, $V_c = V_0 e^{-t/\tau}$

Time constant (τ) can be calculated from graph plotted b/w V_c and time (t)

⇒ During charging -

The time constant is that time by which the voltage V_c across the capacitor becomes 63% of the applied voltage

$$V_c(\tau) = 0.63 V_0$$

⇒ During discharging

The time constant is that time by which the voltage V_c across the capacitor discharges to 37% of the applied voltage


$$V_c(\tau) = 0.37 V_0$$

where $\tau = \text{time constant}$

Scale:

on x-axis $\rightarrow 1 \text{ unit} = 20 \text{ sec}$

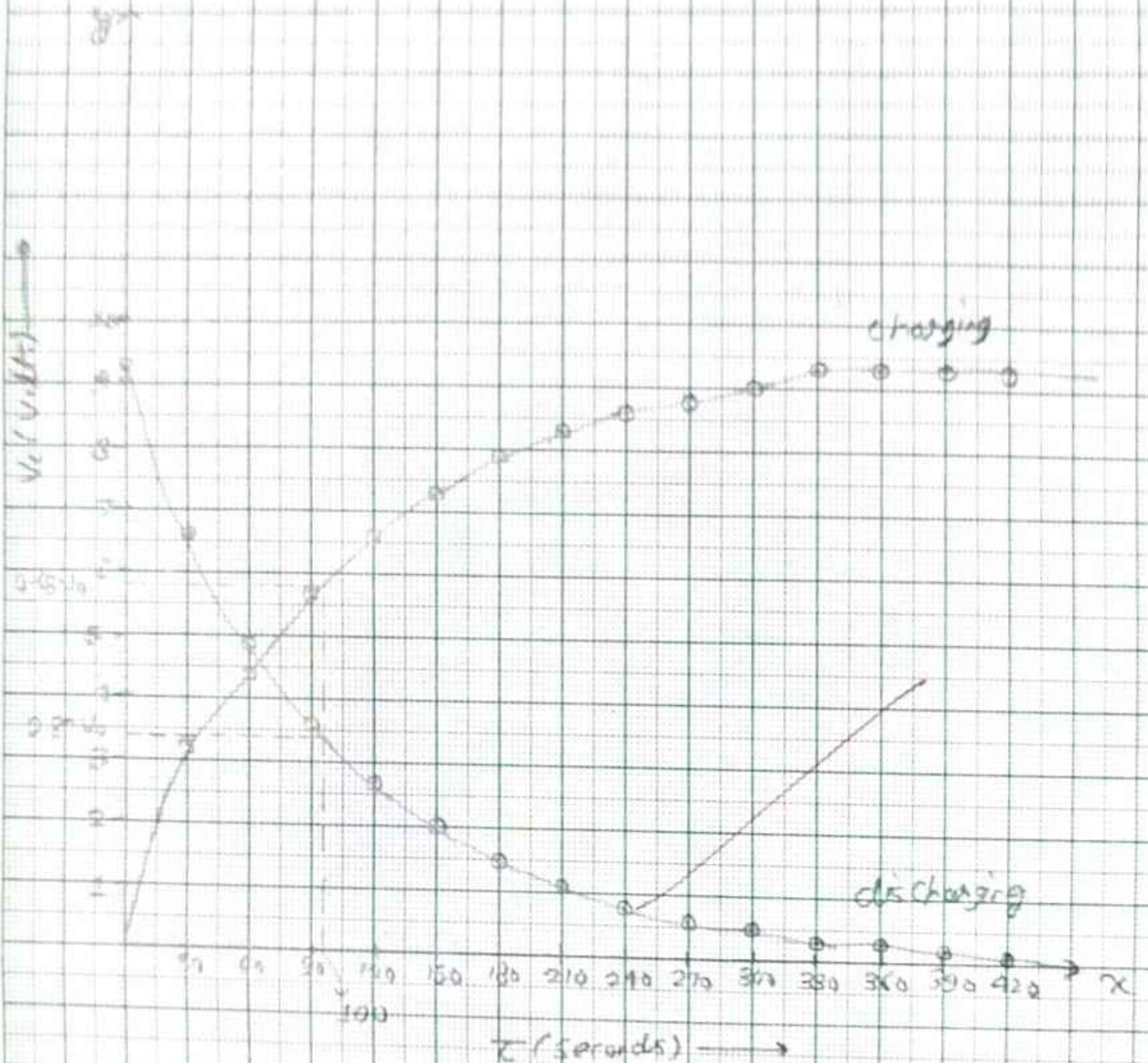on y-axis $\rightarrow 1 \text{ unit} = 1 \text{ Volt}$





M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 23
Name Faculty No. Class Batch

OBSERVATION TABLE - $C = 1000 \mu F$ $R = 100 k\Omega$

During charging						During discharging					
S.No	Time(s)	Vc(Volt)	S.No	Time(s)	Vc(Volt)	S.No	Time(s)	Vc(Volt)	S.No	Time(s)	Vc(Volt)
1	0	0	21	200	8.1	1	0	9.3	22	210	1.1
2	10	1.0	22	210	8.3	2	10	8.1	23	220	1.0
3	20	1.8	23	220	8.4	3	20	7.4	24	230	0.9
4	30	2.6	24	230	8.5	4	30	6.6	25	240	0.8
5	40	3.2	25	240	8.6	5	40	6.0	26	250	0.8
6	50	3.9	26	250	8.7	6	50	5.4	27	260	0.7
7	60	4.4	27	260	8.7	7	60	4.9	28	270	0.6
8	70	4.9	28	270	8.8	8	70	4.4	29	280	0.6
9	80	5.3	29	280	8.9	9	80	4.0	30	290	0.5
10	90	5.7	30	290	8.9	10	90	3.6	31	300	0.5
11	100	6.0	31	300	9.0	11	100	3.3	32	310	0.4
12	110	6.3	32	310	9.0	12	110	3.0	33	320	0.4
13	120	6.6	33	320	9.1	13	120	2.7	34	330	0.3
14	130	6.9	34	330	9.1	14	130	2.4	35	340	0.3
15	140	7.1	35	340	9.1	15	140	2.2	36	350	0.3
16	150	7.3	36	350	9.2	16	150	2.0	37	360	0.3
17	160	7.5	37	360	9.2	17	160	1.8	38	370	0.2
18	170	7.7	38	370	9.2	18	170	1.6	39	380	0.2
19	180	7.9	39	380	9.3	19	180	1.5	40	390	0.2
20	190	8.0	40	390	9.3	20	190	1.4	41	400	0.2
						21	200	1.2	42	410	0.1

Calculations:

(1) During charging

Total voltage across capacitor, $V_0 = 9.3V$

$$V_1(z) = 0.63V_0$$

$$= 0.63 \times 9.3$$

$$= 5.859V$$

Time corresponding to V_1 is 100 sec

$$\tau = 100 \text{ sec}$$

(2) During ~~discharging~~

~~Initial voltage across capacitor = $V_0 = 9.3V$~~

~~$$V_2(z) = 0.37V_0$$~~

~~$$= 0.37 \times 9.3$$~~

~~$$= 3.441V$$~~

~~Time corresponding to $V_2 = 100 \text{ sec}$~~

~~$$\tau = 100 \text{ sec}$$~~



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 24
Name Faculty No. Class Batch

43	420	0.1	49	480	0.1
44	430	0.1	50	490	0.1
45	440	0.1	51	500	0.1
46	450	0.1	52	510	0
47	460	0.1	53	520	0
48	470	0.1	54	530	0

⇒ Comparison of the value of Time constant (τ) -

Theoretical value of $\tau = RC$




$$= 100 \times 10^3 \times 1000 \times 10^{-6}$$

$$= 100 \text{ sec}$$

Value of τ from V_c vs t graph = 100 sec

RESULT

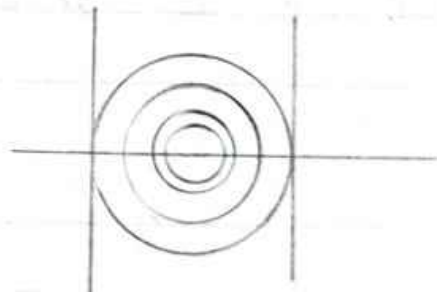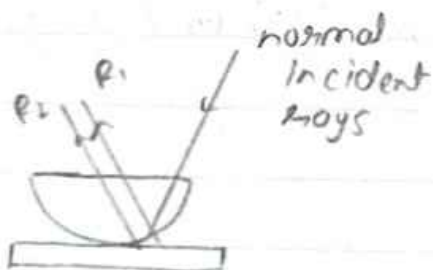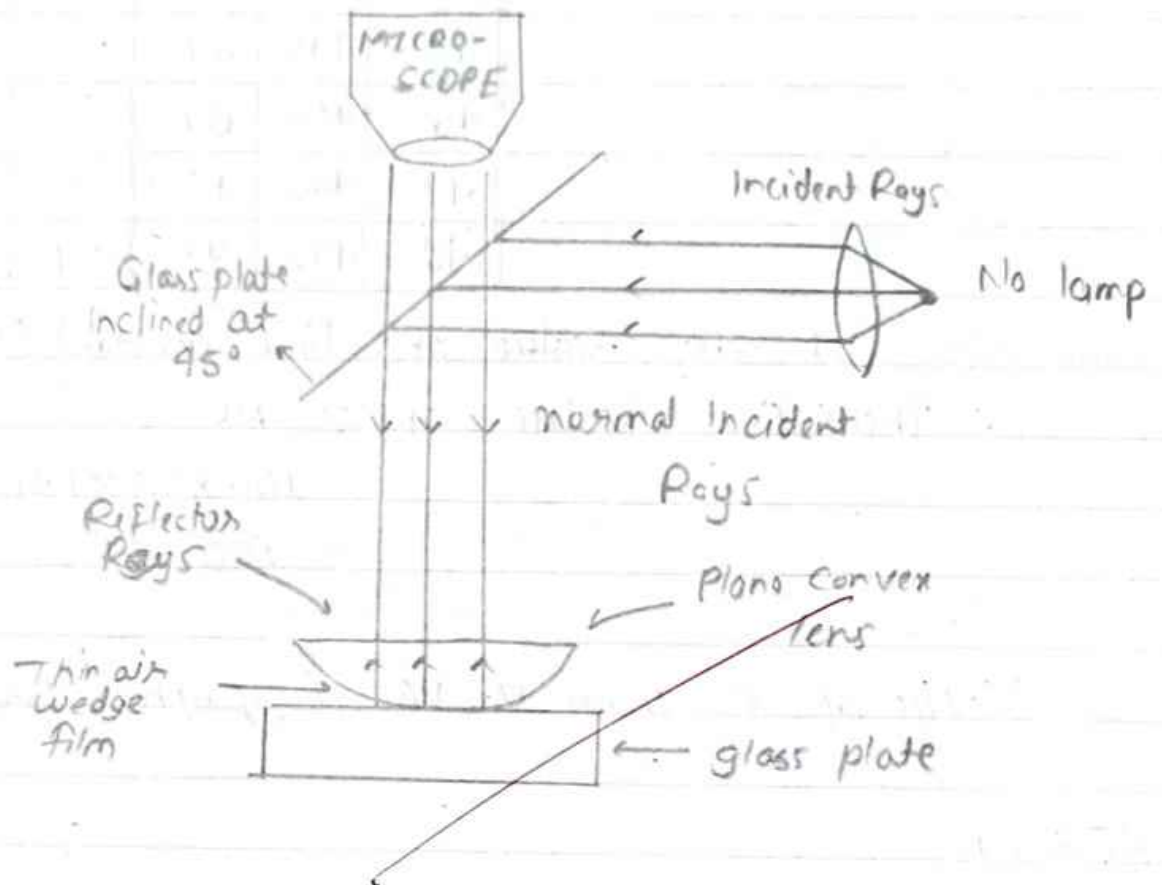The theoretical value of τ is almost same as the value of τ obtained from $(V_c \text{ vs } t)$ graph



L-20 R-20
18
16
14
12
10



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. 08 P. No. 25
Name Vikram Salanki Faculty No. Class BE 1st year Batch H-4

Object: To find wave length of light by Newton's Ring method.

Apparatus: A plane-concave lens of large radius of curvature (about 100cm), travelling microscope, optical arrangement for Newton's ring, sodium lamp & a spectrometer

Formula: The mean wave length of D_1 & D_2 lines of sodium light is given by

$$\lambda = \frac{D_{n+p}^2 - D_n^2}{4pR\mu} \quad (n \text{ \& } p \text{ are integers})$$

Here, D_{n+p} = Diameter of $(n+p)^{\text{th}}$ ring.

D_n = Diameter of n^{th} ring.

R = Radius of curvature, $\mu = 1$ (air)

Theory: When a parallel beam of monochromatic light is incident normally on a combination of plano-convex lens L & a glass plate on a part of each incident ray is reflected from the lower surface of the lens & a part after refraction through the air film between the lens & the plate is reflected back from the plate surface. These two reflected rays are Coherent. Hence they interfere & produce a



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 26
Name Faculty No. Class Batch

system of alternate dark & bright rings with the point of contact between the lens & the plate as the centre. These rings are known as Newton's rings.

Observations

$$R = 65 \text{ cm (given)}$$

Least count of microscope = $\frac{\text{one division of main scale (n)}}{\text{Total division on vernier scale (n)}}$

$$\text{One division of main scale (n)} = 0.1 \text{ cm}$$

$$\text{Total no. of divisions on vernier scale (n)} = 100$$

$$\text{Least count of microscope} = \frac{n}{n} = \frac{0.1 \text{ cm}}{100}$$

$$= 0.001 \text{ cm}$$



Experiment No. _____
 Faculty No. _____

Calculations:

$$\lambda = \frac{D_{n+p}^2 - D_n^2}{4pR}$$

$$= \frac{0.1130345 \text{ cm}^2}{4 \times 8 \times 65 \text{ cm}}$$

$$= \frac{1130345}{208} \times 10^{-10} \text{ m}$$

$$= 5434.35 \text{ \AA}$$



M. B. M. UNIVERSITY JODHPUR

Date Experiment No. P. No. 27
Name Faculty No. Class Batch

No of Rings n	MICROSCOPE READING						Diameter		mean
	Left hand side			Right hand side			$D_n = a-b$	$(D_n)^2$	
	MS	CSXLC	Total (a)	MS	CSXLC	Total (b)		$D_n^2 - D_n^2$	
20	2.5	0.027	2.527	1.9	0.052	1.952	0.575	0.330625	
18	2.5	0.000	2.500	1.9	0.087	1.987	0.513	0.263169	
16	2.4	0.054	2.454	2.0	0.012	2.012	0.442	0.195364	
14	2.4	0.033	2.433	2.0	0.039	2.039	0.305	0.093025	
12	2.4	0.021	2.421	2.0	0.057	2.057	0.364	0.132496	0.198129
10	2.3	0.097	2.397	2.0	0.076	2.076	0.321	0.103041	0.160155
8	2.3	0.083	2.383	2.0	0.096	2.096	0.287	0.082369	0.112595
6	2.3	0.067	2.367	2.1	0.016	2.116	0.251	0.063001	0.030024
4	2.3	0.045	2.345	2.1	0.042	2.142	0.203	0.041209	0.091287
2	2.3	0.010	2.310	2.1	0.078	2.178	0.132	0.017424	0.085617

RESULT-

The wavelength (λ) of sodium light (monochromatic light).

$$\lambda = 5434.35 \text{ \AA}$$

$$\text{Percentage Error} = \frac{\text{Actual} - \text{Calculated}}{\text{Actual}} \times 100 = \frac{5893 - 5434}{5893} \times 100$$

$$= 7.78\%$$