
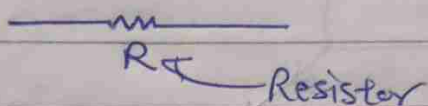


Basic Laws :-

Resistance :- The property or ability of physical material to resist the flow of current.

$$R = \frac{\rho l}{A} \Omega$$

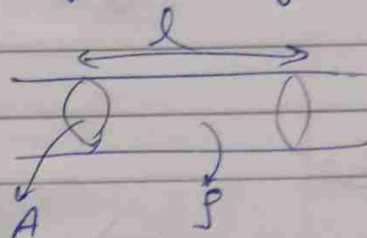


Ohm's Law (Georg Simon Ohm)

$$V \propto I$$

$$V = RI$$

$$R \rightarrow \text{Range} \Rightarrow [0, \infty)$$

↑ short circuit

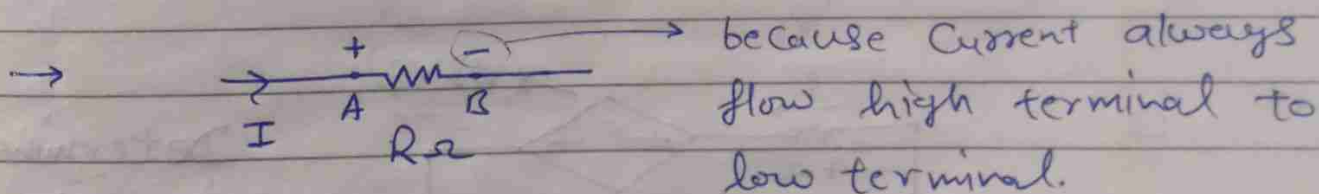


(Gustav Robert)

Kirchhoff's Laws :- (Law of con. charge)


(1) KCL :- The algebraic sum of current at a junction or closed boundary is zero.

Ex!

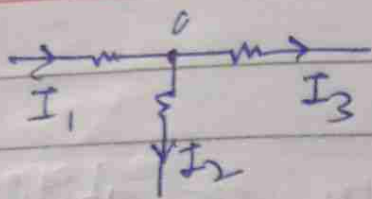


$\sum I = 0 \quad I_1 - I_2 - I_3 = 0$

Ex!

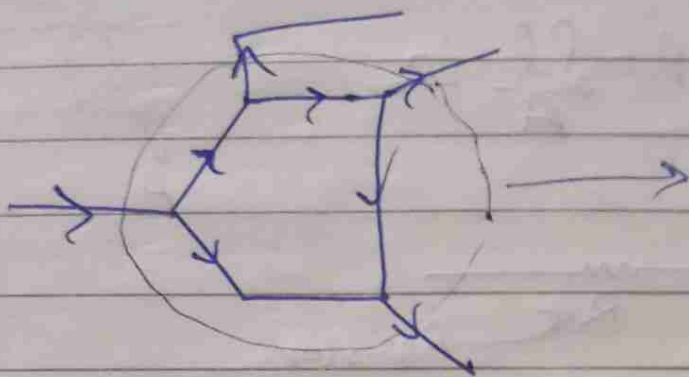


(2) KVL:- (Based on Law of Conservation Energy)
The algebraic sum of voltage in a loop or closed path of a circuit is zero.

Ex!

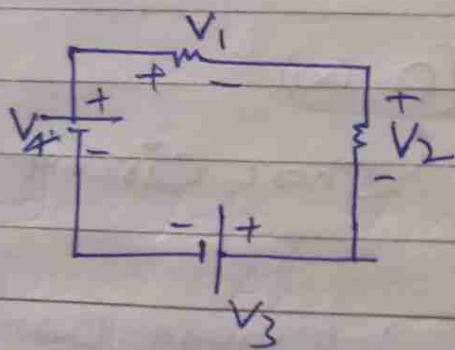

$V_1 + V_2 + V_3 - V_4$

Q

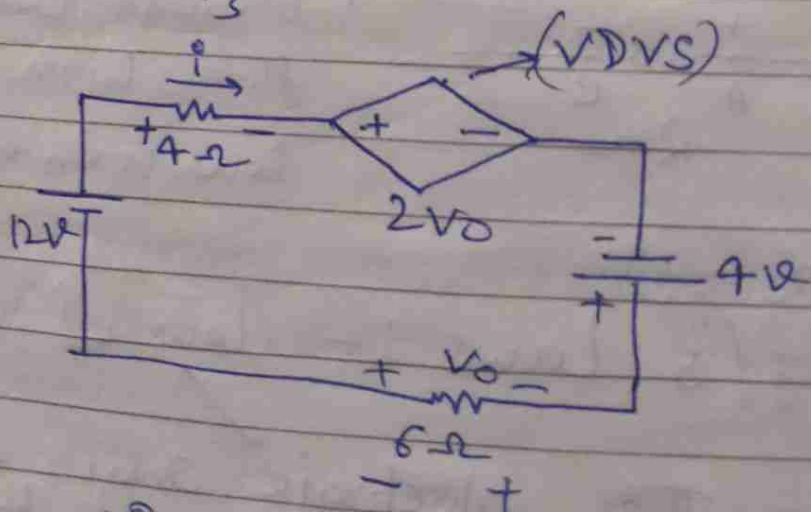

Determine V_0 & i in the circuit shown below.

Soln

$4i + 2V_0 + 4 - V_0 - 12 = 0$
 $4i + V_0 - 16 = 0$

$$V_0 = -61$$



$$I = 1.6 A$$

$$V_0 = 9.6 V$$

$$I = -8 A$$

$$V_0 = 48 V$$

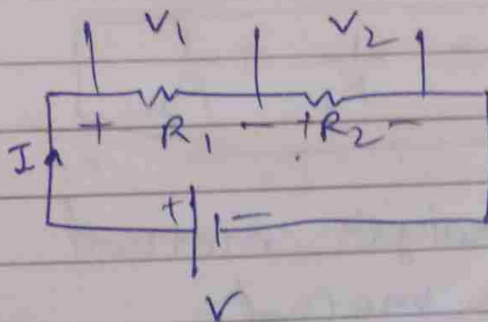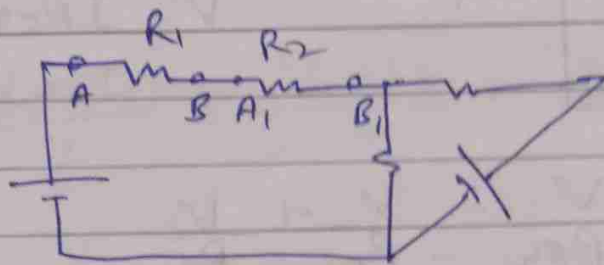
Element in Series/Voltage division in Series Elements.



$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V = V_1 + V_2$$

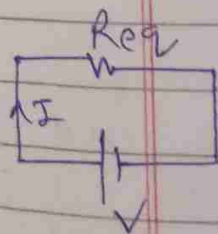

$$V = IR_{eq}$$


$$IR_{eq} = IR_1 + IR_2$$

$$R_{eq} = R_1 + R_2$$

$$V_1 = \left(\frac{V}{R_1 + R_2} \right) R_1$$

$$V_2 = \left(\frac{V}{R_1 + R_2} \right) R_2$$

Parallel

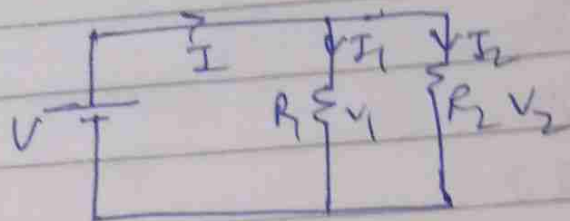


$$V = V_1 = V_2$$

$$V_1 = I_1 R_1$$

$$V_2 = I_2 R_2$$

$$I = I_1 + I_2$$

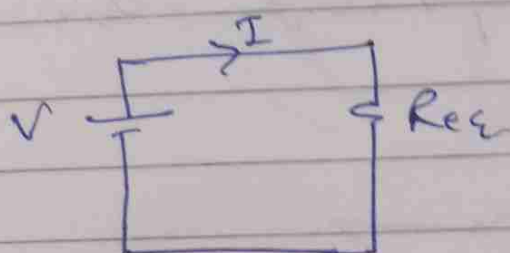

$$V = I R_{eq}$$


$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$$

Node Volt Analysis method

Nodal Analysis method

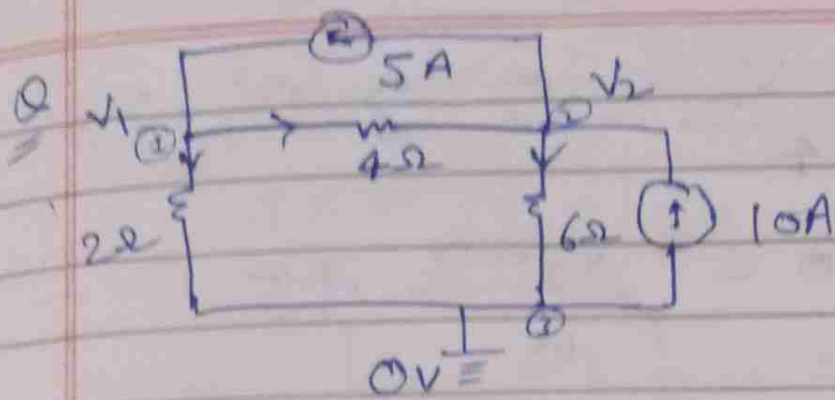1. Identify the number of nodes in a circuit.
2. Out of n nodes mark one node as reference node.
3. Assume voltages for remaining $(n-1)$ nodes.
4. Apply KCL at all non reference node.
5. Solve the Eq. obtained by (4)



~~let ($V_2 > 0 > V_1$)~~

we apply KCL at Node ①

let ($V_2 > V_1 > 0$)

~~$$2A \left(\frac{V_1 - 0}{2} \right) + \frac{V_2 - V_1}{4} = 5 \times 4$$~~

~~$$\frac{V_2 - V_1}{4} + 10 = \frac{V_2 - 0}{6} + 5$$~~

~~$$2V_1 + V_2 - V_1 = 20$$~~

~~$$V_1 + V_2 = 20 \quad \text{--- ①}$$~~

~~$$3V_2 - 3V_1 + 120 = 2V_2 + 60$$~~

~~$$60 = 3V_1 - V_2 \quad \text{--- ②}$$~~

~~$$80 = 4V_1$$~~

~~$$V_1 = 20$$~~

~~$$V_2 \neq 0$$~~

Node ①

$$\frac{V_1 - 0}{2} + \frac{V_1 - V_2}{4} = 5 \Rightarrow 3V_1 - V_2 = 20 \quad \text{--- (1)}$$

Node ②

$$\frac{V_2 - V_2}{4} + 10 = \frac{V_2 - 0}{6} + 5$$

$$3V_1 - 3V_2 + 120 = 2V_2 + 60 \Rightarrow 5V_2 - 3V_1 = 60 \quad \text{--- (2)}$$

$$V_2 = 20$$

$$V_1 = \frac{40}{3}$$

Cramers Rule:-

$$a_{11}x_1 + a_{12}x_2 + \dots + a_{1n}x_n = b_1$$

$$a_{21}x_1 + a_{22}x_2 + \dots + a_{2n}x_n = b_2$$

⋮

$$a_{n1}x_1 + a_{n2}x_2 + \dots + a_{nn}x_n = b_n$$

$$x_1 = \frac{\Delta_1}{\Delta}, \quad x_2 = \frac{\Delta_2}{\Delta}, \quad \dots \quad x_n = \frac{\Delta_n}{\Delta}$$

$$\Delta = \begin{vmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{vmatrix}$$

$$3V_1 - V_2 = 20$$


$$5V_2 - 3V_1 = 60$$

$$\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix}$$

$$\Delta = +2$$

$$\Delta_1 = \begin{vmatrix} 20 & -1 \\ 60 & 5 \end{vmatrix} = 10$$
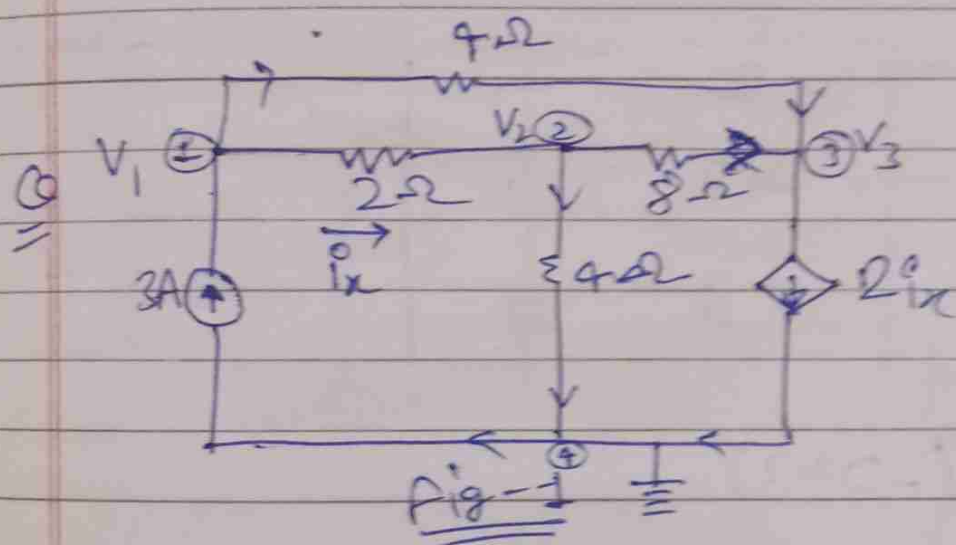
$$\Delta_2 = \begin{vmatrix} 3 & 20 \\ -3 & 60 \end{vmatrix} = -240$$



By Apply Kcl at all node

at Node ① $\frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 3$

$$2V_1 - 2V_2 + V_1 - V_3 = 12$$

$$3V_1 - 2V_2 - V_3 = 12 \quad \text{--- ①}$$

③ $\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = 2 \left(\frac{V_1 - V_2}{2} \right)$

$$2V_1 - V_2 + V_3 = 0$$

② $\frac{V_2 - V_3}{8} + \frac{V_2}{4} + \frac{V_2 - V_1}{2} = 0$

$$4V_1 - 7V_2 + V_3 = 0$$

$$A = \begin{vmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ 2 & -3 & 1 \end{vmatrix}$$

$$3(-7+3) + 2(4-2) - 1(-12+4)$$

$$-12 + 4 = -8$$

$$A = -10$$

$$A_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & -7 & 1 \\ 0 & -3 & 1 \end{vmatrix}$$

$$= 12(-7+3)$$

$$= -48$$

$$A_2 = \begin{vmatrix} 3 & 12 & -1 \\ 4 & 0 & 1 \\ 2 & 0 & 1 \end{vmatrix}$$

$$= 12(4-2)$$

$$= 24$$





$$A_3 = \begin{vmatrix} 3 & -2 & 12 \\ 4 & -7 & 0 \\ 2 & -3 & 0 \end{vmatrix} = 12(-12+4) = -96$$

$$V_1 = 4.8 \quad V_2 = -2.4 \quad V_3 = -2.4$$

Special Cases:-

- (1) Voltage Source: connected b/w a reference and non-reference node.
- (2) When we have voltage source b/w two non-reference nodes

Ex (3)

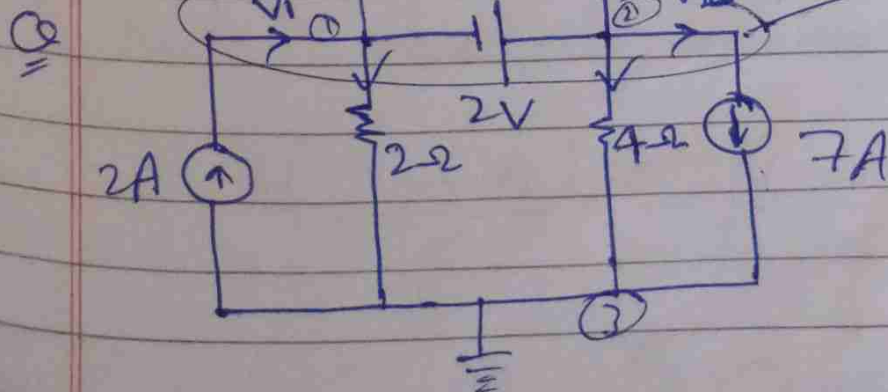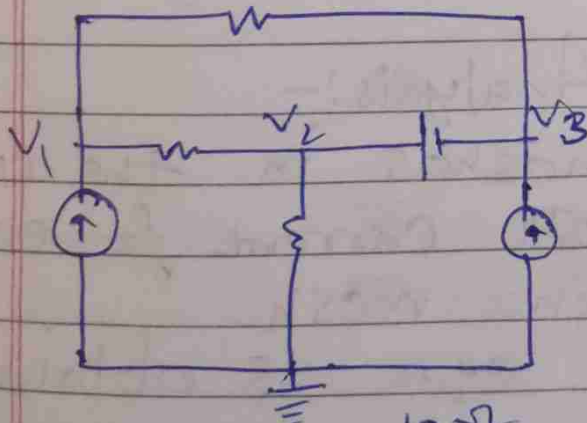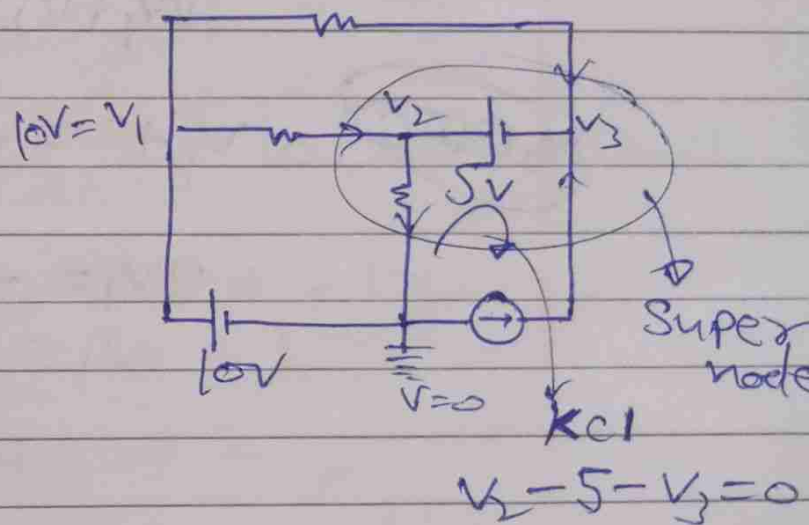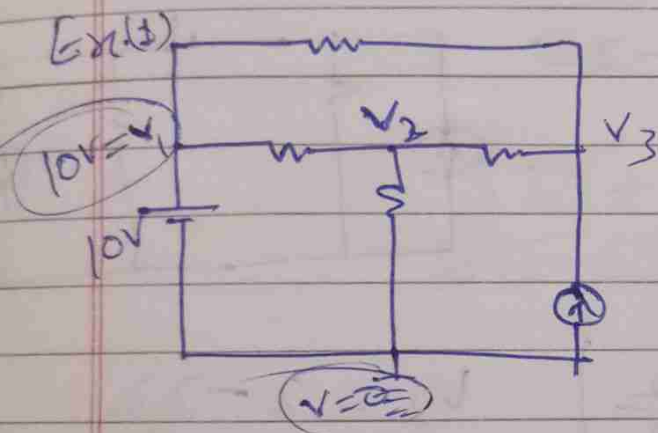

By applying KCL at Super node we get

$$2 + \frac{V_2 - V_1}{10} = \frac{V_1}{2} + \frac{V_2}{4} + 7 + \frac{V_2 - V_1}{10}$$

(यदि voltage source के parallel में resistances हों तो उसे हटा देंगे उसका कोई मतलब नहीं होगा)


$$2V_1 + V_2 = -20$$

or (1) (2) (3)

$$V_1 + 2 = V_2$$

$$3V_1 = -22$$

$$V_1 = -\frac{22}{3}$$

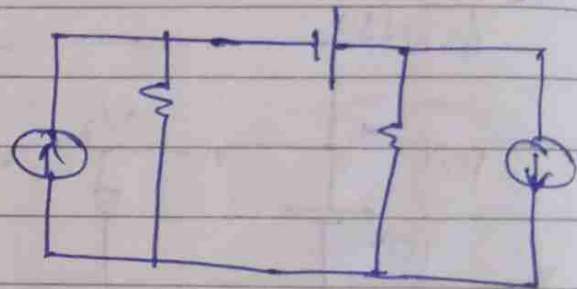

$$V_2 = 2 - \frac{22}{3}$$


$$V_2 = -\frac{16}{3}$$

Mesh Current Analysis:-

- (1) Identify the meshes in the circuit and assign mesh current for each mesh
- (2) Apply KVL in each mesh
- (3) ~~Solve~~ Solve the eq. as obtained by using Step (2)

I_A I_B

Date _____
Page _____

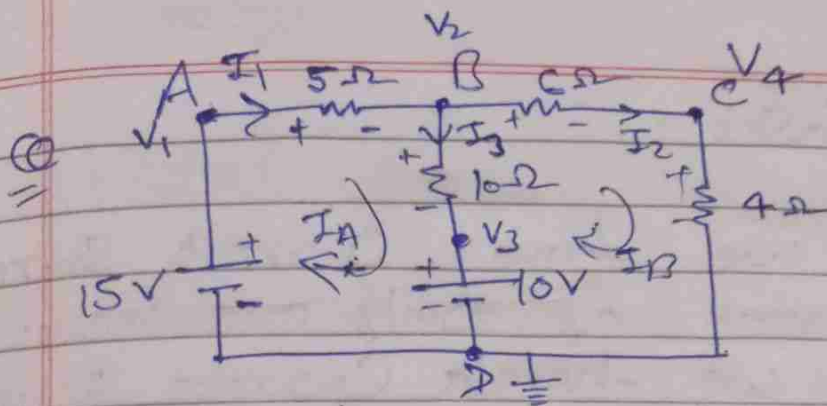

$$\begin{aligned} V_1 &= 15V \\ V_2 &= 10V \\ V_3 &= ? \\ V_4 &= ? \end{aligned}$$

Applying KVL in mesh ABDA we get

(for I_A & I_B)

$$5I_A + 10(I_A - I_B) + 10 - 15 = 0$$

$$15I_A - 10I_B - 5 = 0$$

$$3I_A - 2I_B = 1 \quad \text{--- (1)}$$

$$6I_B + 4I_B - 10 - 10(I_A - I_B) = 0$$

$$16I_B - 10I_A = 10$$

$$20I_B - 10I_A = 10$$

$$2I_B - I_A = 1$$

$$2I_A = 0 \quad 2$$

$$I_A = 1$$

$$I_B = 1$$

$$I_1 = I_A = 1$$

$$I_B = I_2 = 1$$

$$I_3 = I_A - I_B = 0$$

Nodal Analysis method


$$2(15 - V_2) = \frac{V_2 - 10}{10} + \frac{V_2}{10}$$

$$\frac{V_2}{2} \quad 20 - 2V_2 = \frac{2V_2 - 10}{10} \quad 40 = 4V_2 \Rightarrow V_2 = 10$$

Special Cases

- (1) when we have Current Source in branch of only one mesh.
- (2) when we have a Current Source in a branch common to two meshes

Case-I

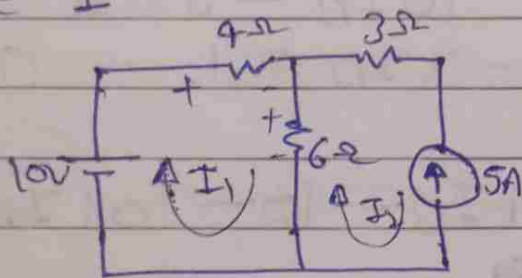

let $I_1 > I_2$

$$I_2 = -5A$$

let $(I_1 > I_2)$


$$4I_1 + 6(I_1 - I_2) = 10$$

$$10I_1 = -20$$

$$I_1 = -2$$

$$I_{AB} = 3A$$

Case-II

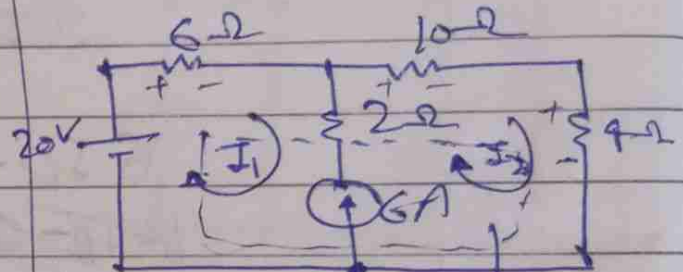

Super mesh

By Apply KVL in Super mesh

$$6I_1 + 10I_2 + 4I_2 - 20 = 0$$

$$6I_1 + 14I_2 = 20$$

$$3I_1 + 7I_2 = 10$$

$$3I_1 + 4I_2 + 7I_1 = 10$$


$$10I_1 = -32$$

$$I_1 = -3.2$$

$$I_2 = 2.8$$

at (P) $I_2 = 6 + I_1$

Nodal Analysis method

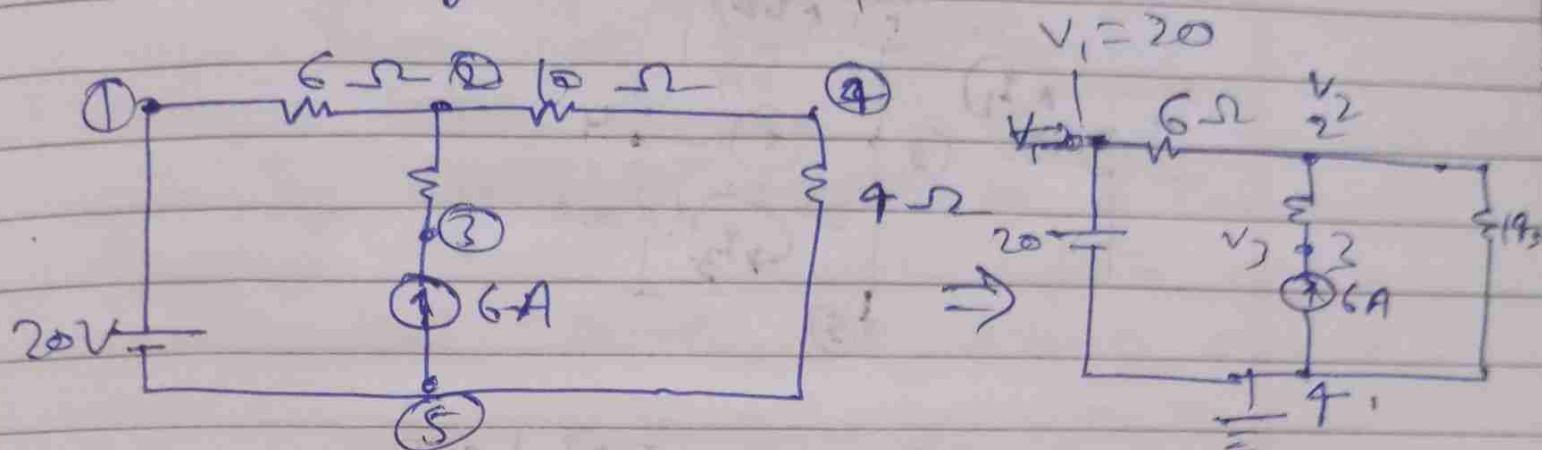

$$\frac{20 - V_2}{6} + 6 = \frac{V_2}{14}$$

$$\frac{20}{6} + 6 = \frac{V_2}{6} + \frac{V_2}{14}$$

$$\frac{56}{6} = \frac{20V_2}{6 \times 14}$$

$$\boxed{39.2 = V_2}$$


$$V_2 = I \times 6$$

$$\frac{39.2}{6} = I$$

$$I = 6$$

$$\frac{39.2 - 20}{6} = I$$

$$3.2 = \frac{19.2}{6} = I$$

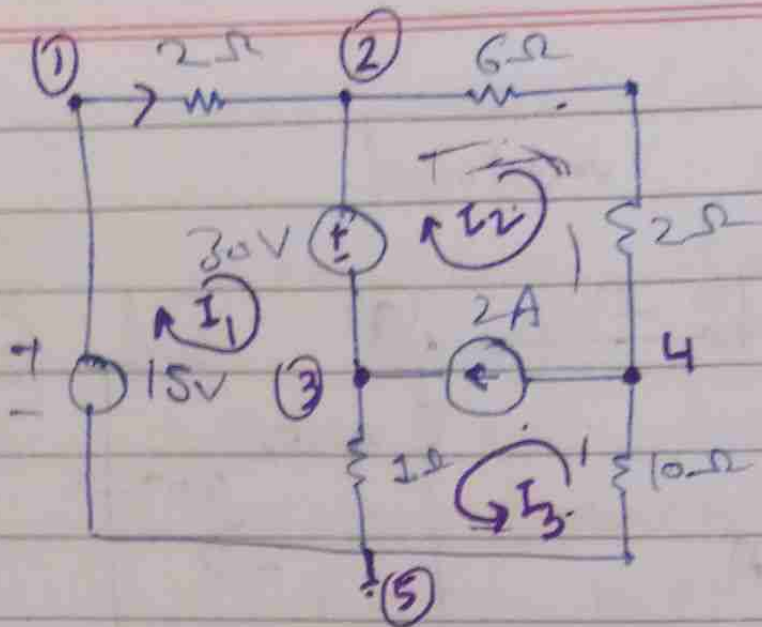

$$-15 + 2I_1 + 30 + (I_1 + I_3) = 0$$


$$6I_2 + 2I_2 - 10I_3 + (I_3 + I_1) = 0$$

$$I_2 + I_3 = 2A$$

Superposition Theorem :-

in linear circuit

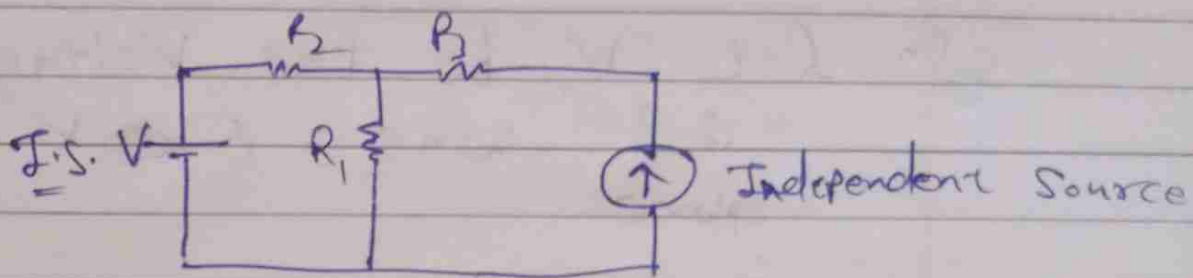States that the Voltage across or Current through any element is equal to algebraic sum of voltages across or currents through that element when each independent source is acting alone.



Linear Element :-

- (i) Homogeneity (scaling)
- (ii) additivity

Ex 1 - (i) $y = 2x$

$x_1 \rightarrow y_1$

$Kx_1 \rightarrow Ky_1$



(ii) $V = IR$

$\begin{matrix} 0 \\ 1 \end{matrix} \rightarrow V_1$
 $K \begin{matrix} 0 \\ 1 \end{matrix} \rightarrow KV_1$


(iv) $y = mx + c$



it is not linear system

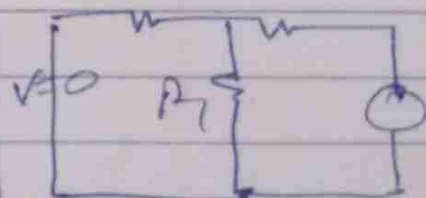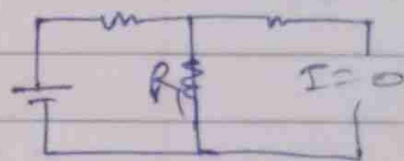


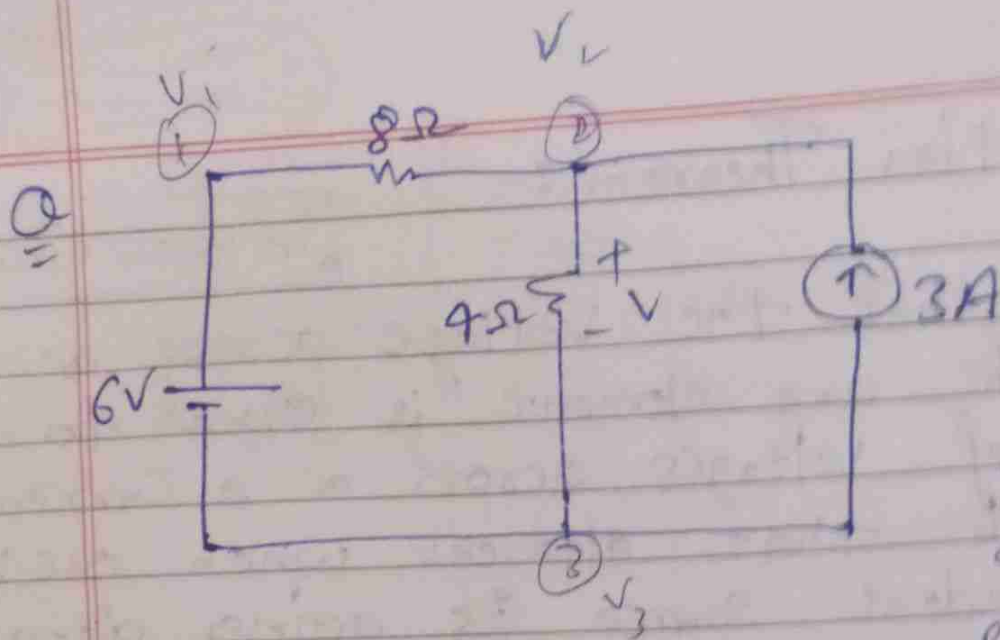(iii) $y = 2x^2$
 $x_1 \rightarrow y_1^2$
 $Kx_1 \rightarrow Ky_1^2$
 Not satisfied




using Super Theorem
find voltage
across 4Ω
Res.

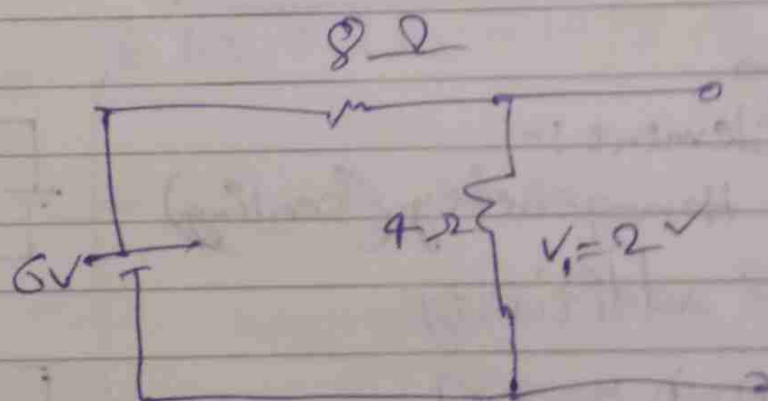Soln let V_1 be the voltage across 4Ω when $6V$ is acting alone



$$V_1 = \frac{6 \times 4}{12} = \frac{V \times R_1}{R_1 + R_2}$$

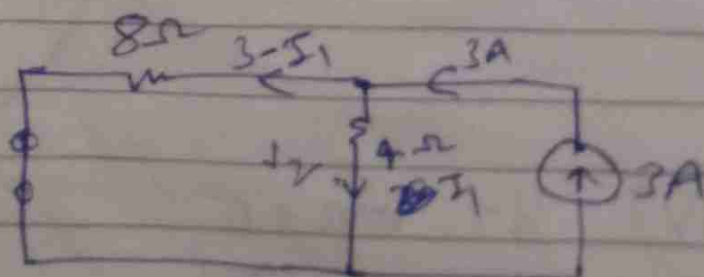to let V_2 be the voltage across 4Ω when $3A$ is acting alone




$$I_1 = \frac{3 \times 8}{12} = 2A$$

$$V_2 = 4 \times 2 = 8$$

There for using Super. The the voltage across 4Ω resistes

$$V = V_1 + V_2 = 10V$$

Method


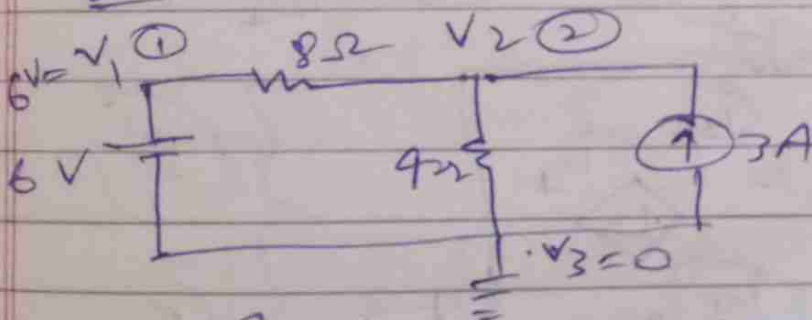


$$\frac{6 - V_2}{8} + 3 = \frac{V_2}{4}$$


$$6 - V_2 + 24 = 2V_2$$

$$30 = 3V_2$$

$$V_2 = 10$$

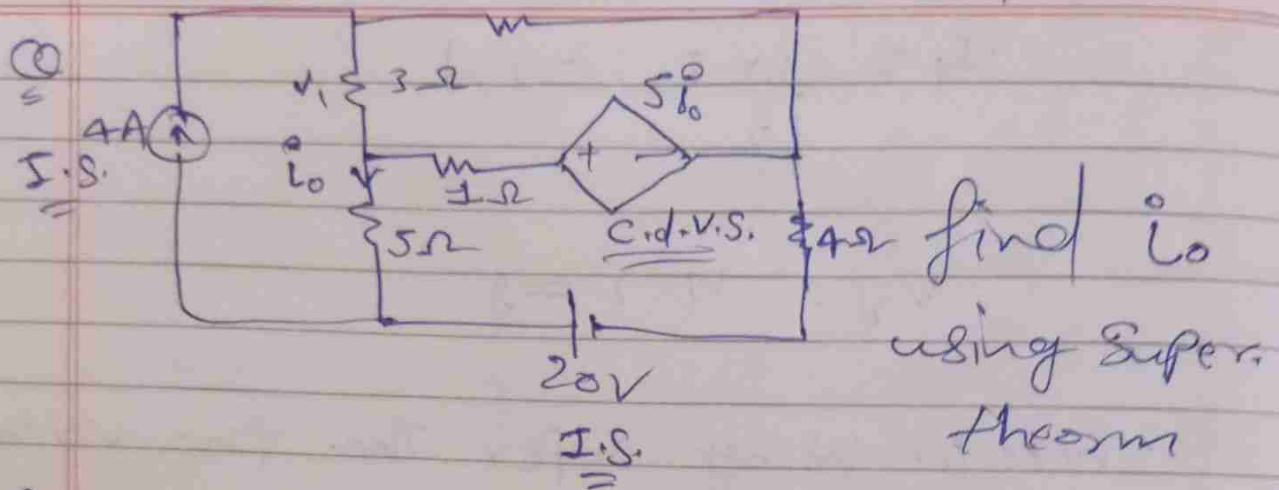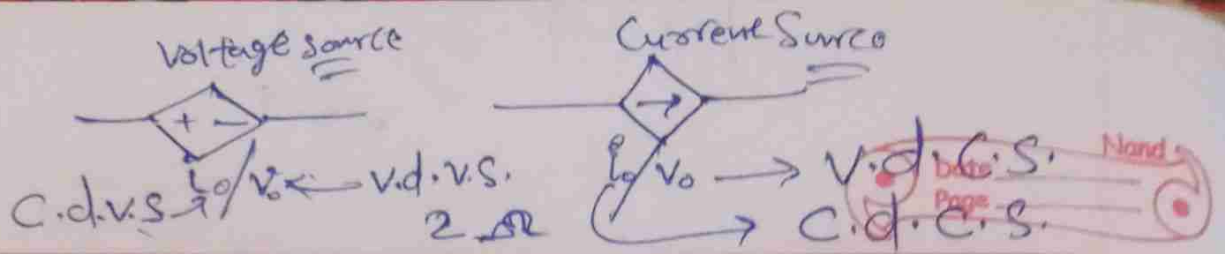

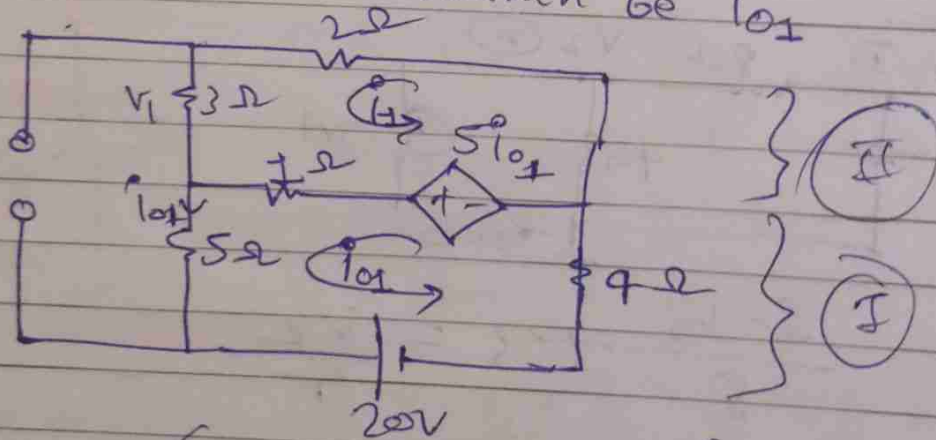Solu Step-I The circuit is as shown below when 4A source is turned off i.e. in the circuit there is only one 20V I.S. let now the current in 5Ω branch be i_{o1}



$$+5i_{o1} + 20 + 4i_{o1} - 8i_{o1} + i_{o1} - i_{o1} = 0$$

$$5i_{o1} - i_{o1} = -20 \quad \text{--- (A)}$$

$$+2i_1 + 3i_1 + 5i_{o1} + 1(i_{o1} - i_1) = 0$$

$$6i_1 + 4i_{o1} = 0$$

$$3i_1 + 2i_{o1} = 0$$

$$i_1 = -\frac{2}{3} i_{o1}$$


$$5i_{o1} + \frac{2}{3} i_{o1} = -20$$

$$17i_{o1} = -60$$

$$i_{o1} = -\frac{60}{17}$$

Step-II

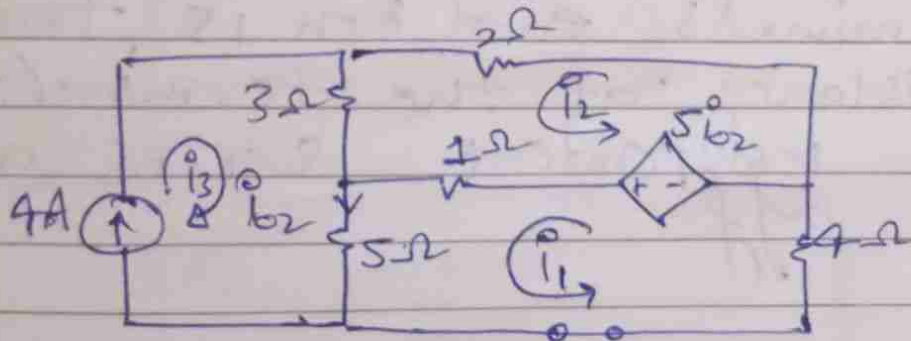The circuit is as shown below when 20V source is turned off i.e. in the circuit there is only one 4A D.S., let now the current in 5Ω branch be i_{o2}



$$i_3 = 4A$$

$$i_1 = i_{o2} + 4$$

$$i_{o2} = i_1 + 4$$

$$5(i_1 + 4) + 4(i_1) - 5i_{o2} + 1(i_1 - i_2) = 0$$

$$5i_1 - i_2 = 0 \Rightarrow 30i_1 - 6i_2 = 0$$

$$+2i_2 + 3(i_2 + 4) + 1(i_2 - i_1) + 5(i_1 + 4) = 0$$

$$4i_1 + 6i_2 = -32 \Rightarrow 34i_1 = -32 \Rightarrow i_1 = -\frac{16}{17}A$$


$$i_{o2} = i_1 + 4 = -\frac{16}{17} + 4 = \frac{52}{17}$$

$$\begin{aligned}
 I_0 &= I_{01} + I_{02} \\
 &= \frac{-60}{17} + \frac{52}{17} \\
 &= \frac{-8}{17} \text{ A}
 \end{aligned}$$



2017
(BE-2018)

Thevenin's Theorem:-

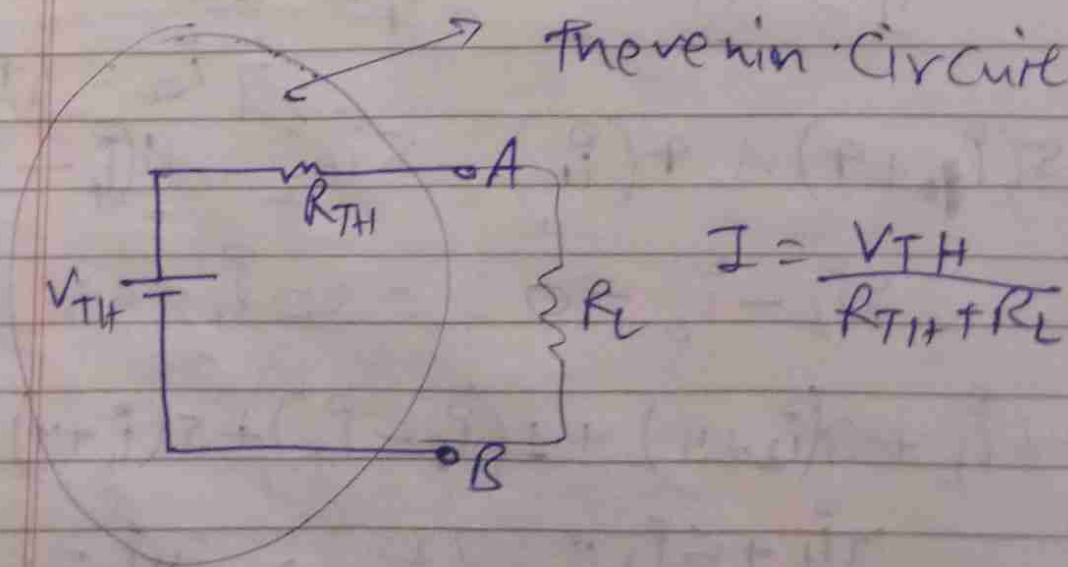
States that any linear two terminal network (circuit) can be replaced by an equivalent circuit consisting of a voltage source (V_{TH}) in series with a resistance (R_{TH}), where V_{TH} is the open circuit voltage across the terminals and R_{TH} is the equivalent resistance at the terminals when all independent sources are turned off.




Linear two terminal circuit

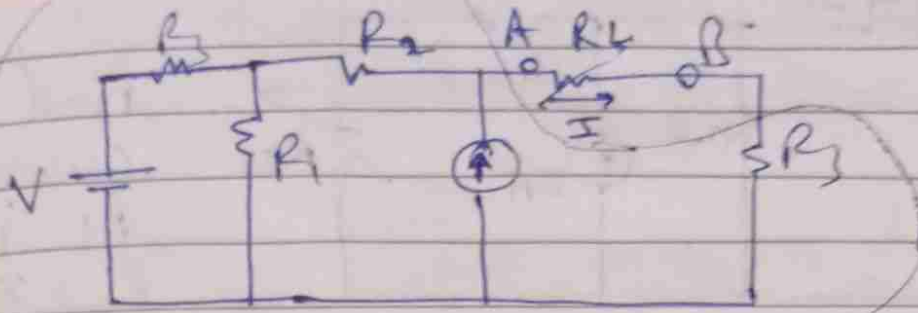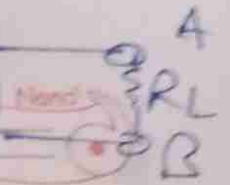

Represented by

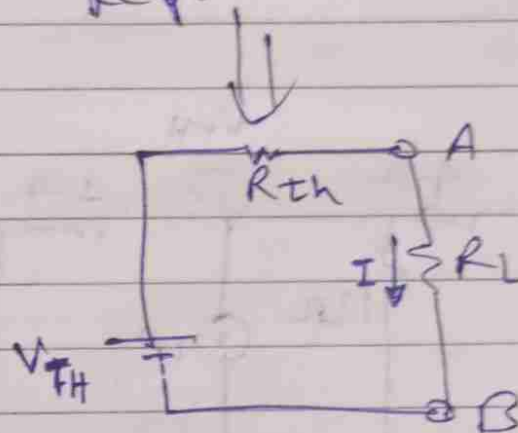

How to find R_{TH} ?

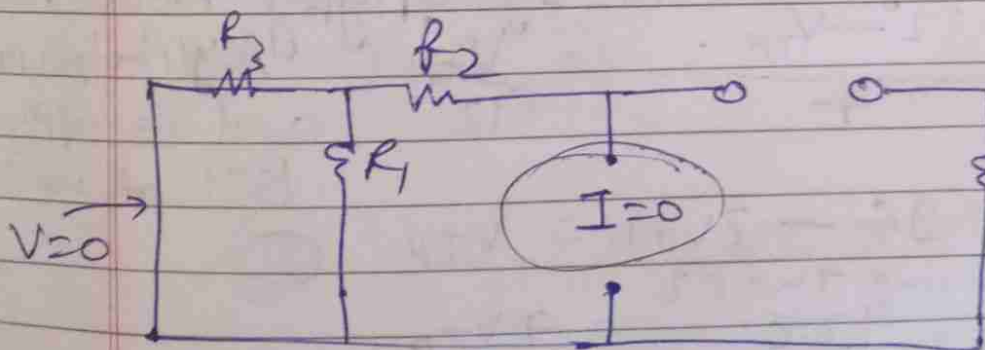


and find R_{TH}

$$R_{TH} = \frac{R_1 R_3}{R_1 + R_3} + R_2 \text{ (in this circuit)}$$


$$P = VI = I^2 R = \frac{V^2}{R}$$

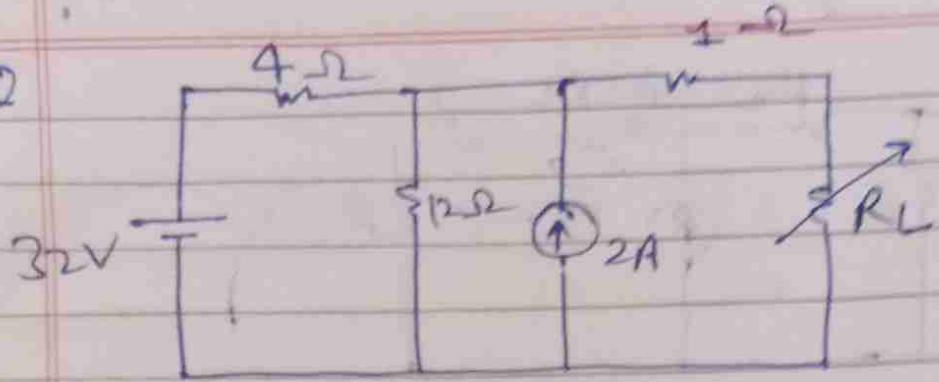Q. Find current in R_L if $R_L = 6, 16 \Omega$ respectively.



Find current in R_L if $R_L = 6, 16 \Omega$ respectively.

Soln

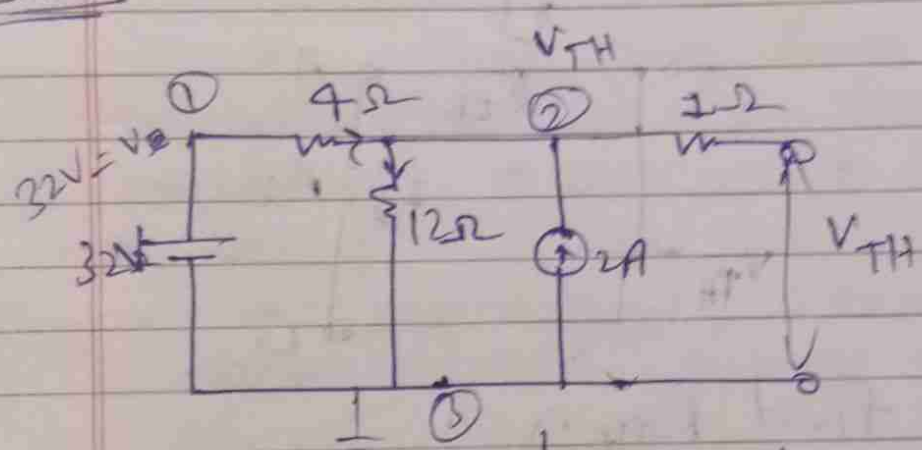

First we find V_{TH} by applying Nodal voltage analysis and apply KCL at node ②

$$2 + \frac{32 - V_{TH}}{4} = \frac{V_{TH}}{12}$$

$$24 + 96 - 3V_{TH} = V_{TH}$$

Solving the eq

$$120 = 4V_{TH}$$

$$\boxed{30 = V_{TH}}$$


Now for finding R_{TH} we turn off all Independent Sources

$$\frac{10 \times 4}{12+4}$$


$$\frac{1}{12} + \frac{1}{4}$$



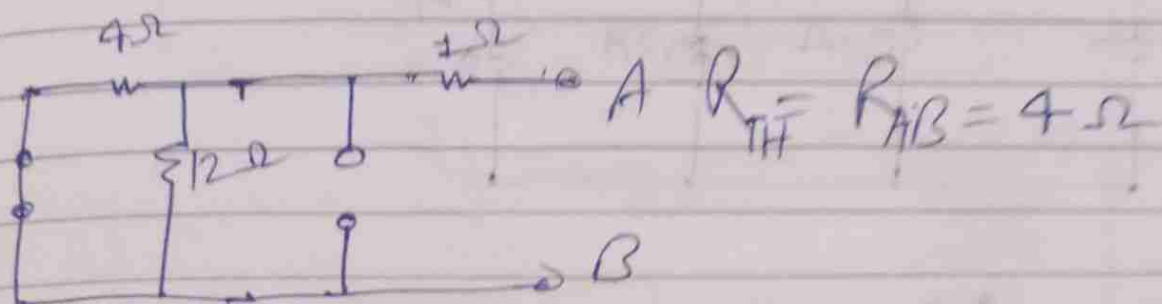By turning off independent sources the ckt is as shown b/w



Therefore, The thevenin eq. circuit

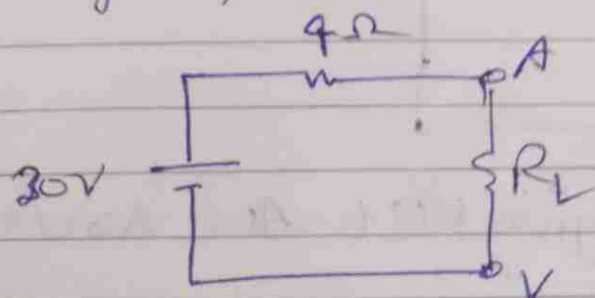

$$I = \frac{30}{4 + R_L}$$

(I) when $R_L = 6\Omega$

$$I = \frac{30}{4+6} = 3A$$



$$R_L = 16$$

$$I = \frac{30}{4+16} = \frac{3}{2}$$

$$R_L = 36$$

$$I = \frac{30}{36+4} = \frac{3}{4}$$

Check the Ans

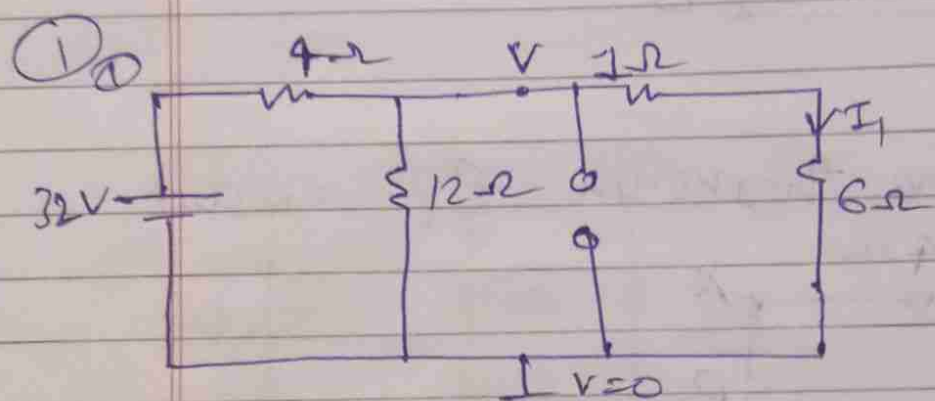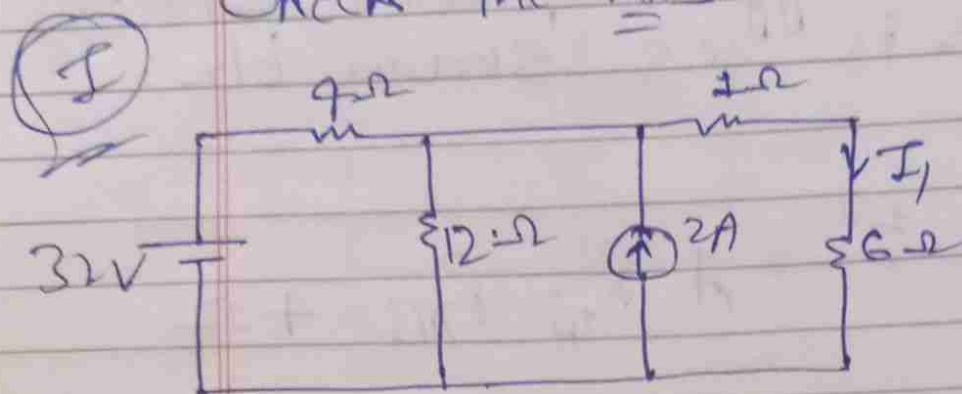

Now Applying KCL at node ②


$$\frac{32 - V}{9} = \frac{V}{12} + \frac{V}{7}$$

$$8 = \frac{V}{12} + \frac{V}{9} + \frac{V}{7}$$

$$8 = V \left(\frac{1}{12} + \frac{1}{9} + \frac{1}{7} \right)$$

$$V = \frac{168}{10}$$

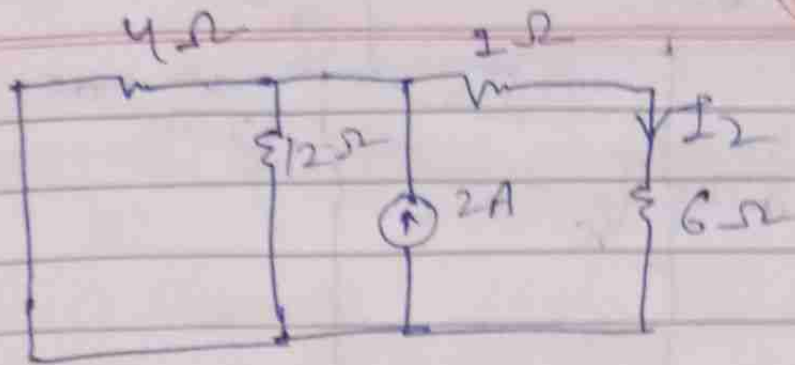
$$I_1 = 2.4 \text{ A} = \frac{168 \times 1}{10 \times 7}$$



$$I_2 = \frac{2 \times 3}{10} = 0.6 A$$

$$I = I_1 + I_2$$

$$= 2.4 + 0.6 = \underline{3 A}$$

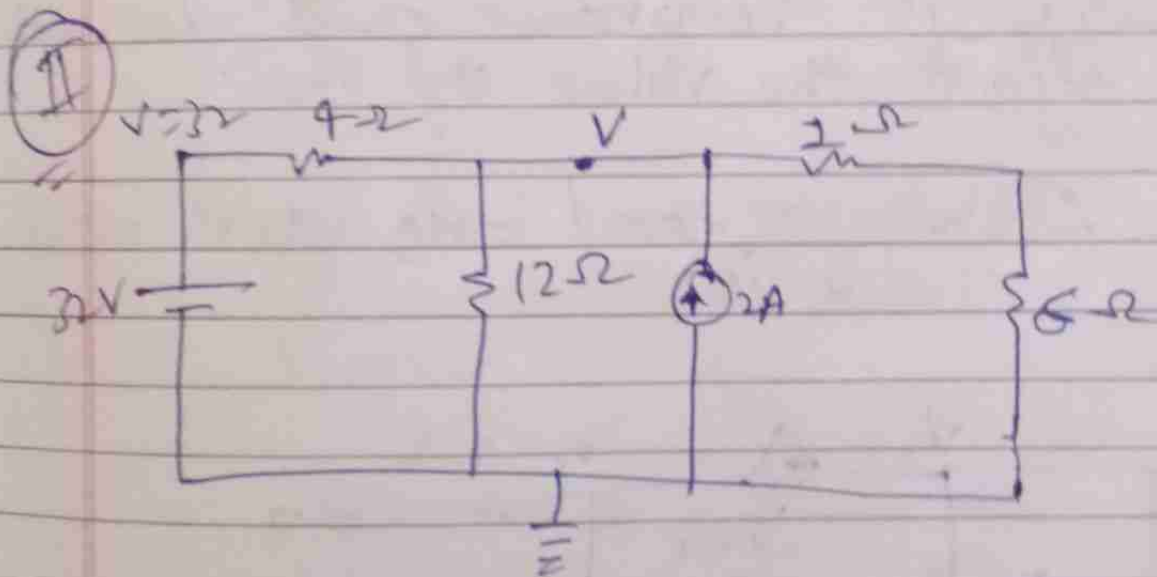


$$2 + \frac{32 - V}{4} = \frac{V}{12} + \frac{V}{7}$$

$$10 = V \left(\frac{1}{12} + \frac{1}{4} + \frac{1}{7} \right)$$

$$V = 21 V$$


$$I = \frac{21}{7} = 3 A$$

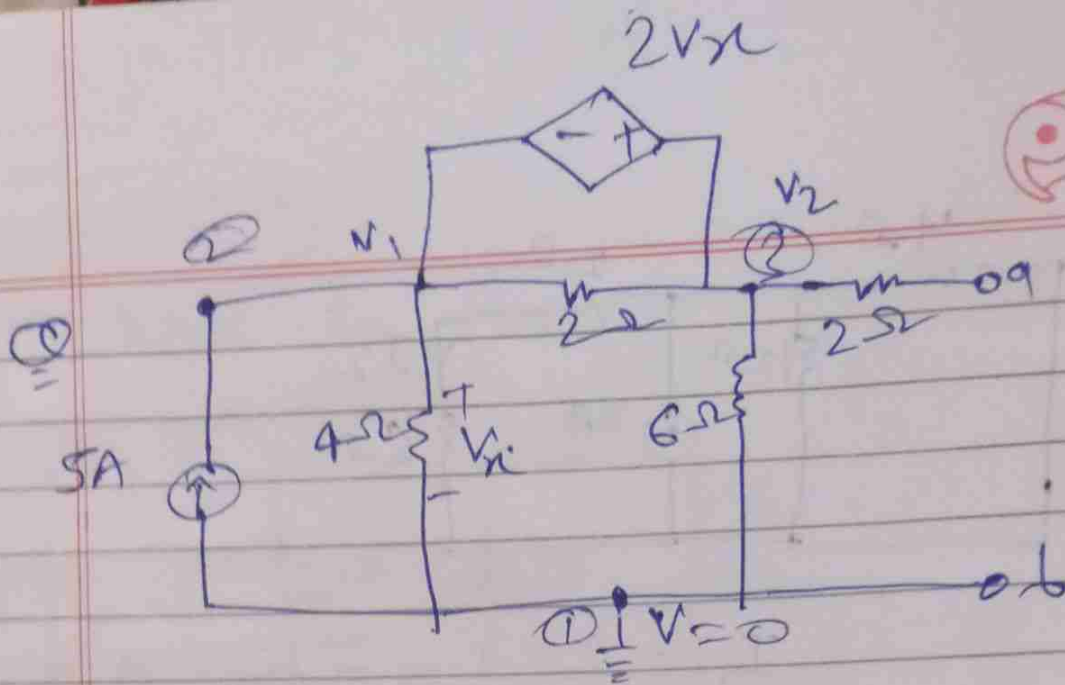

First we determine V_{TH} or V_{ab} by using Nodal Analysis method

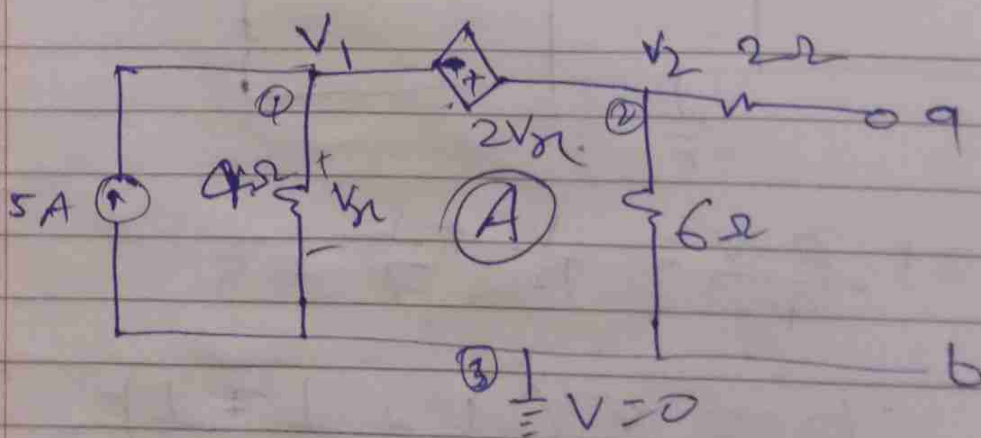- (i) Since 2Ω is connected in parallel with a dependent voltage source it is redundant and does not effect the value of V_{TH} .

$\therefore$ We removed this and new circuit is.



Now as shown in circuit there are three nodes ① ② ③ respectively let node ③ be

reference node and voltage of node ① & ② be V_1 & V_2 respectively

By assuming Node ① & Node ② as one node called as supernode

because there is a voltage source b/w them. Now we apply KCL at

this supernode.
we get.

$$5 = \frac{V_1}{4} + \frac{V_2}{6}$$

Apply KVL at mesh ① we get.

$$V_1 + 2V_1 = V_2$$

$$3V_1 = V_2$$

$$5 = \frac{V_1}{4} + \frac{3V_1}{6}$$


$$\frac{3V_1}{4} = 5$$

$$V_2 = 20$$

$$V_1 = \frac{20}{3}$$

$$V_{TH} = 20V$$

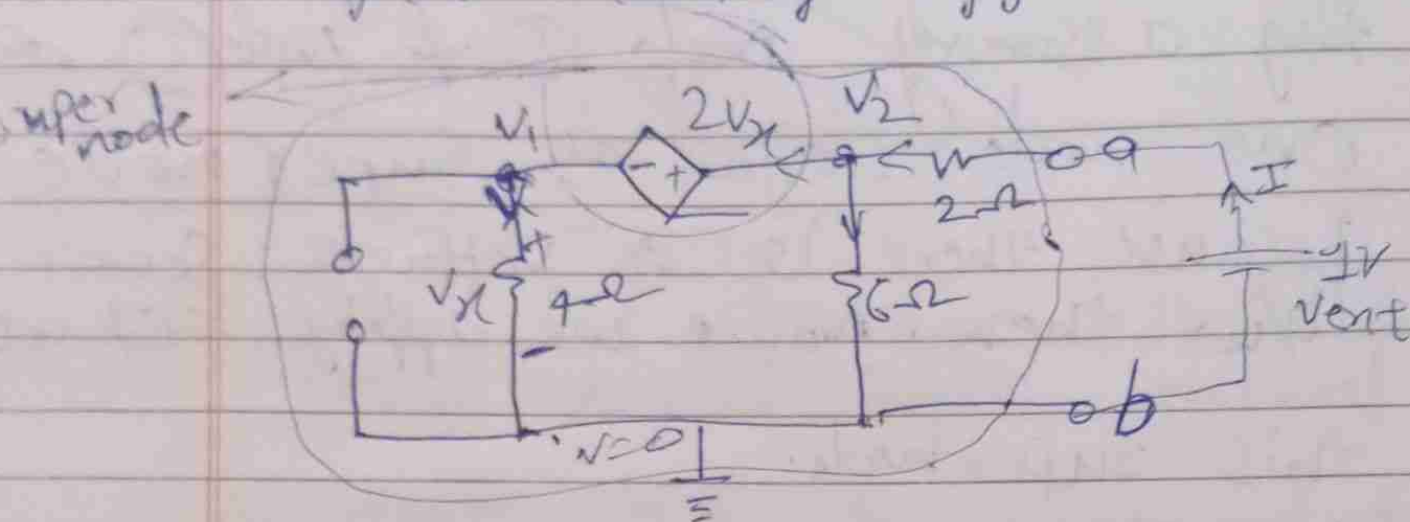For finding R_{TH} we turn off all independent sources. The circuit after turning off I.S.



Because the circuit has dependent source therefore we apply external voltage $V_{ext} = 1V$ and find I in the circuit which will give

$$R_{TH} = \frac{V_{ext}}{I}$$

By applying KCL at Super node we get

$$\frac{V_1}{4} + \frac{V_2}{6} = \frac{1 - V_2}{2}$$

$$\begin{aligned} V_1 + 2V_2 &= V_2 \\ 3V_1 &= V_2 \end{aligned}$$

$$\frac{1}{2} = \frac{V_1}{4} + \frac{V_2}{6} + \frac{V_2}{2}$$


$$V_2 = \frac{2}{3}V$$

$$\frac{1}{2} = \frac{V_1}{4} + \frac{V_1}{2} + \frac{3V_1}{2}$$


$$\begin{aligned} \frac{9V_1}{4} &= \frac{1}{2} \\ V_1 &= \frac{2}{9}V \end{aligned}$$

$$I = \frac{1 - \frac{2}{3}}{2} = \frac{1}{6} \text{ A}; R_{TH} = 6 \Omega$$

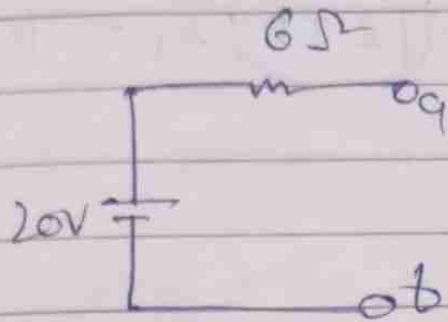
$\therefore$ Therefore Thevenin Eq. Ckt is



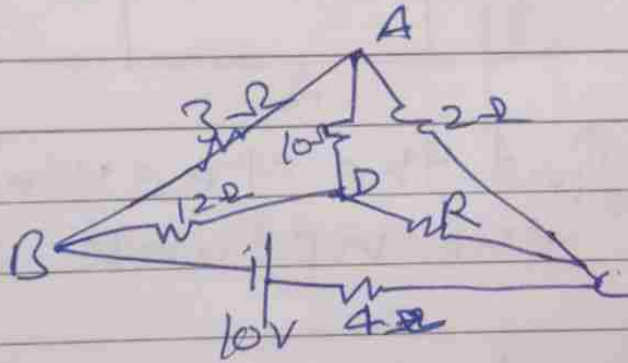Q Find the value of R and Current through in the circuit shown in fig. when branch AD carries no current (BE-2018)



Soln

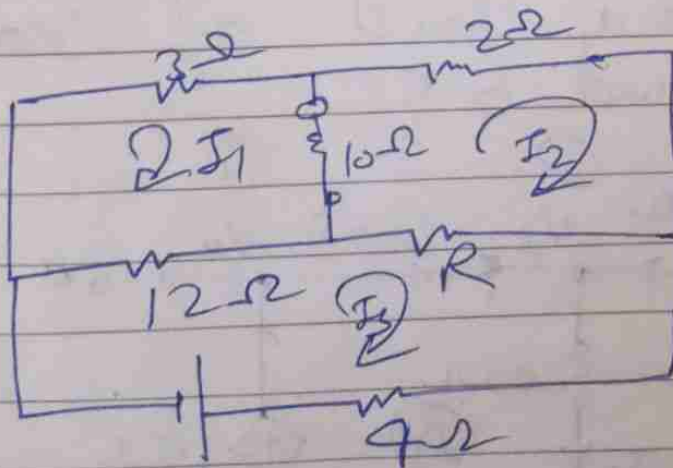

$$I_1 - I_2 = 0$$

$$I_1 = I_2$$

$$3I_1 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0$$

①

$$2I_2 + R(I_2 - I_3) + 10(I_2 - I_1) = 0$$

②


$$4I_3 - 10 + 12(I_3 - I_1) + R(I_3 - I_1) = 0$$

$$15I_1 - 12I_3 = 0$$

$$5I_1 - 4I_3 = 0 \quad \text{--- (1)}$$


$$(2+R)I_1 - RI_3 = 0 \quad \text{--- (2)}$$
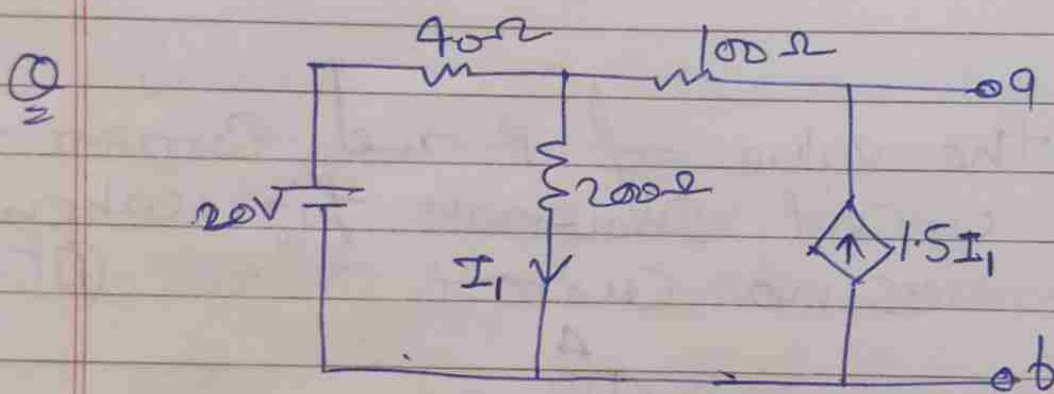
$$(16+R)I_3 - (12+R)I_1 = 10 \quad \text{--- (3)}$$



① find the thevenin equivalent of the network shown in fig.

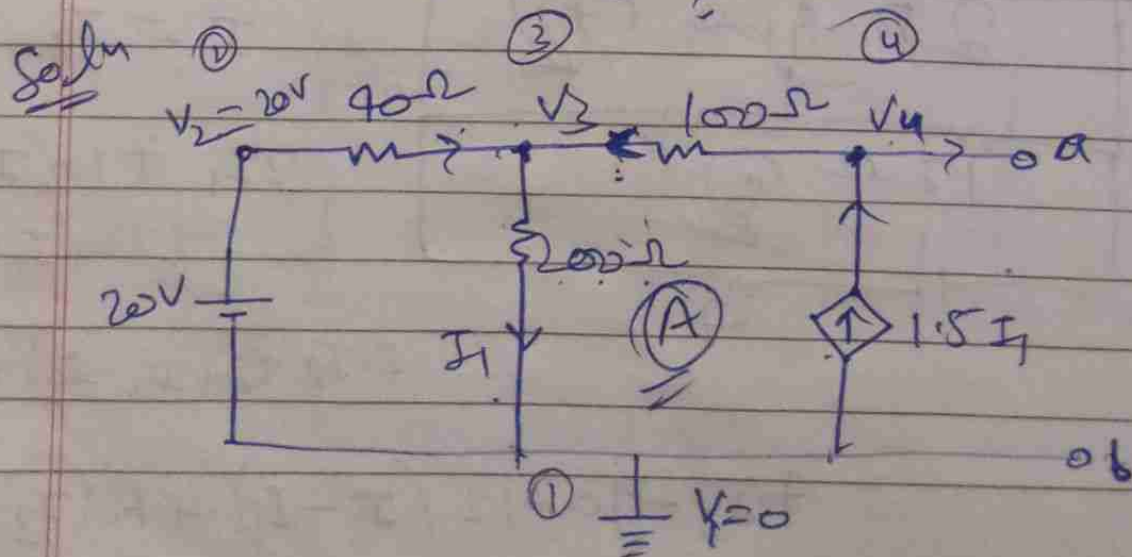② what power will be delivered to a load of 100Ω at a and b?



Apply KCL at (3) node

$$V_A - 3 \times 9 = 12$$

Date: ~~22/11~~ 22/11
Page: ~~7~~ 7

$$\frac{20 - V_3}{40} + \frac{V_4 - V_3}{100} = \frac{V_3}{200}$$

Apply KVL at mesh (A)

~~$$V_3 \cdot 200 I_1 + 1.5 + 100 V_4 - V_3$$~~

~~$$-V_3 + V_4 + V_4 - V_3$$~~

~~$$0 + V_3 + V_4 + 0 = 0$$~~


~~$$200 I_1 + 1.5 I_1 \times 40 + 20 = 0$$~~

~~$$I_1 = \frac{-20}{180}$$~~

~~$$I_1 = -\frac{1}{9}$$~~


~~$$\frac{V_3 - 0}{200} = I_1$$~~

~~$$V_3 = -\frac{1}{9} \times 200$$~~

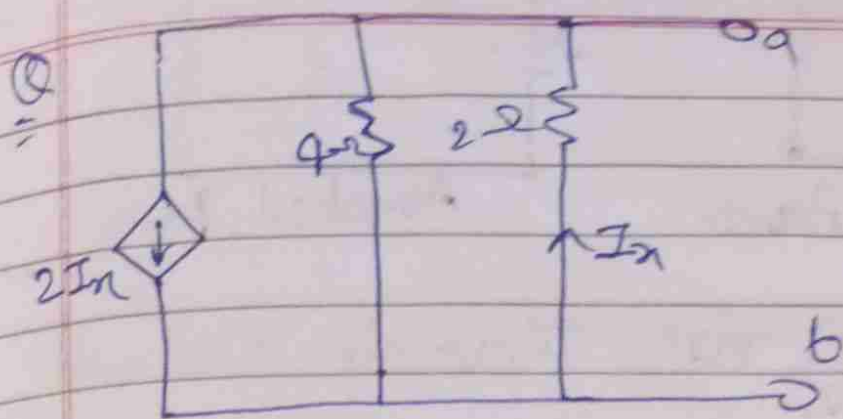

find Thevenin eq. Circuit.

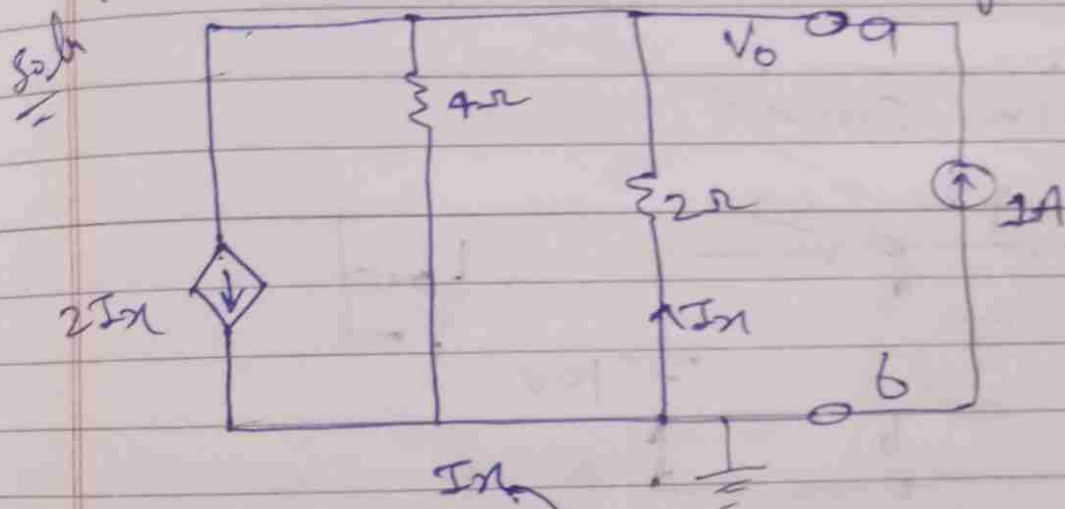in this circuit does not have any I_n s. ^{current} So in this circuit will be zero



$$2 \left(\frac{-V_o}{2} \right) + \frac{V_o}{4} + \frac{V_o}{2} = 1$$

$I_o = 1A$

$$\frac{V_o}{4} + \frac{V_o}{4} - \frac{4V_o}{4} = 1$$

$$-\frac{V_o}{4} = 1$$

$$V_o = -4$$



$$\frac{V_o}{I_o} = \frac{-4}{1} = -4\Omega$$

if circuit has d.s.

In this circuit has d.s. So it is resistance of total circuit


This circuit delivers power

⇒ Thevenin

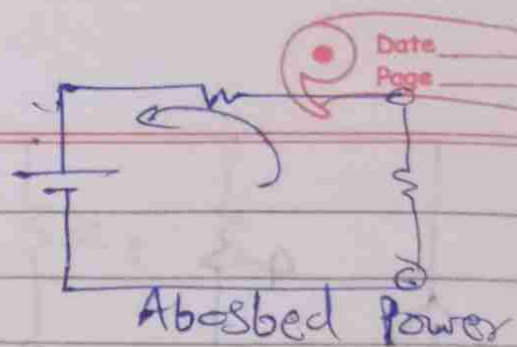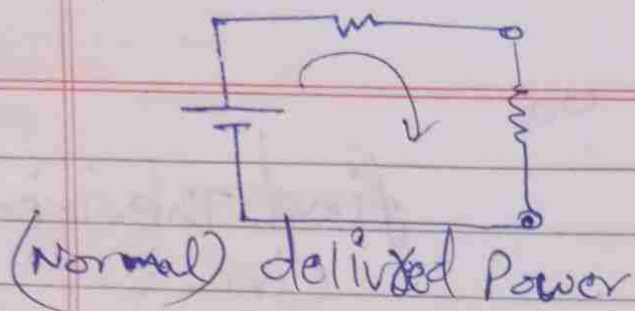


⇒ R_{Th} -ve की होना Thevenin R_{Th} -ve हो सकता है।

Thevenin circuit.

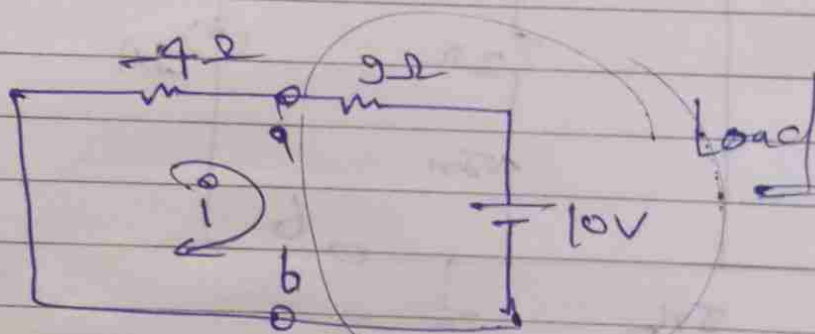

$$-4i + 9i + 10 = 0$$


$$i = 2A$$

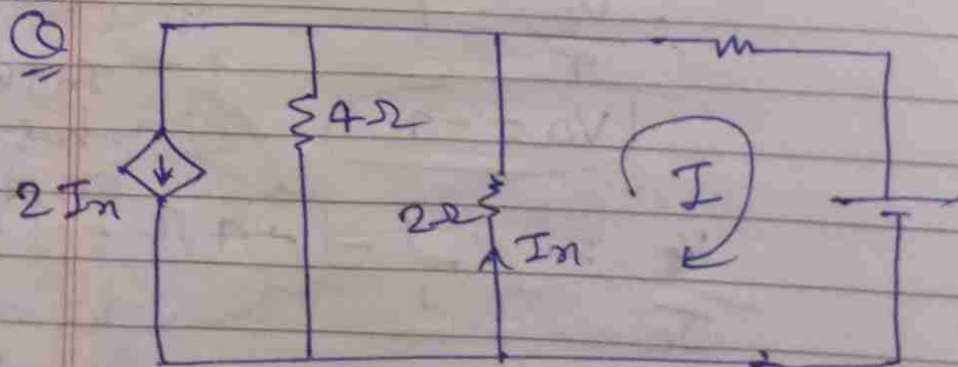

find (I) from nodal Analysis

for find dual circuit

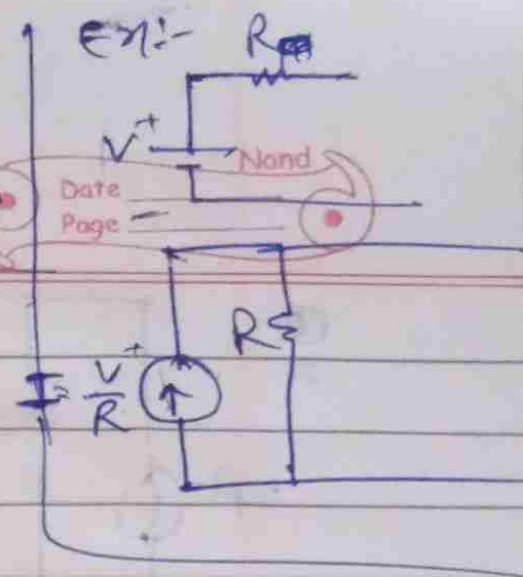
- ① Current Source $\longleftrightarrow$ Voltage Source
- ② Resis. Series $\longleftrightarrow$ Resis. Parallel



→ NORTON'S THEOREM



dual of Thevenin theorem

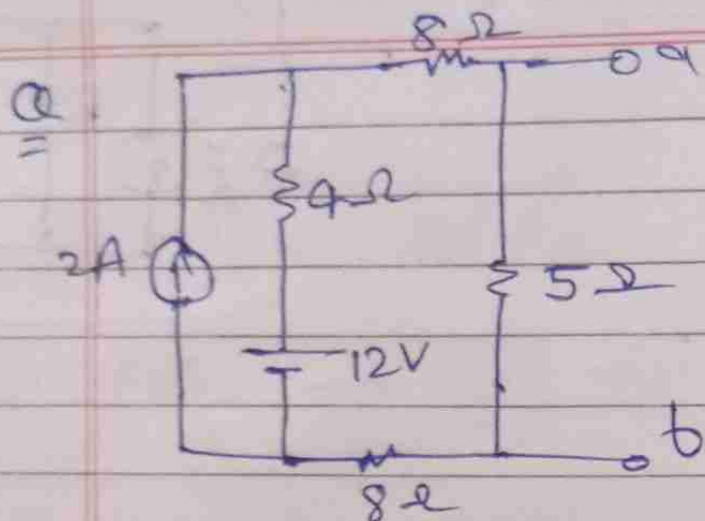States that any linear two terminal circuit can be replaced by an equivalent circuit consisting of a Current Source (I_N) in parallel with a resistance (R_N) where I_N is the short circuit current is through the two terminal and R_N is the eq. resistance when all I. S. are turned off.



find the Norton eq.
on given circuit.

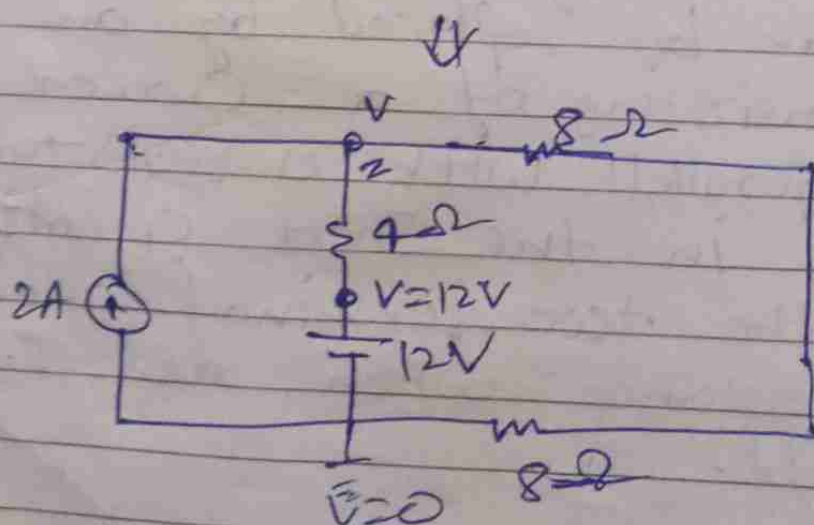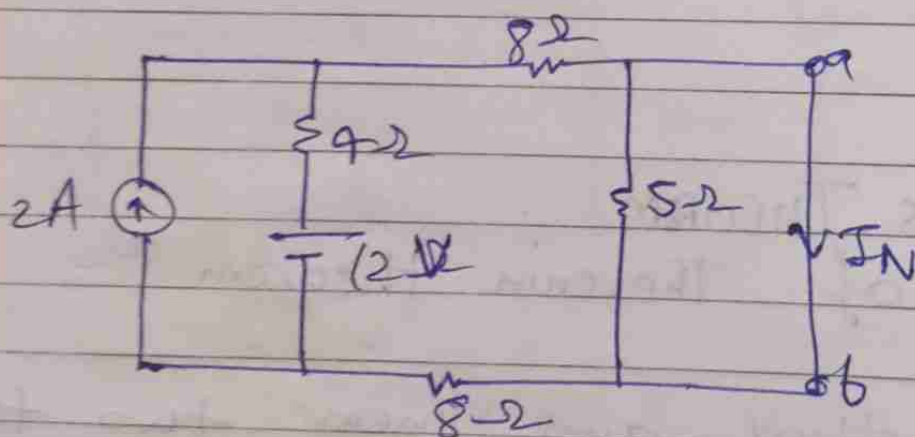Soln we first determined I_N and for that we short the terminal a & b i.e. now the circuit is



Applying KCL at Node ② we get

$$2 + \frac{12 \cdot V}{4} = \frac{V}{16}$$


$$5 = \frac{V}{16} + \frac{4V}{16}$$

$$I_N = \frac{V}{16} = 1A$$

$$\frac{5V}{16} = 5$$


$$V = 16$$

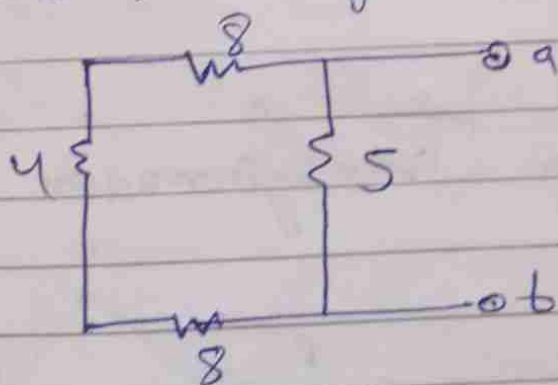Now for finding R_N we turned off all I.S., thereafter the new circuit is




$$\therefore R_N = 4\Omega$$

Norton eq. circuit

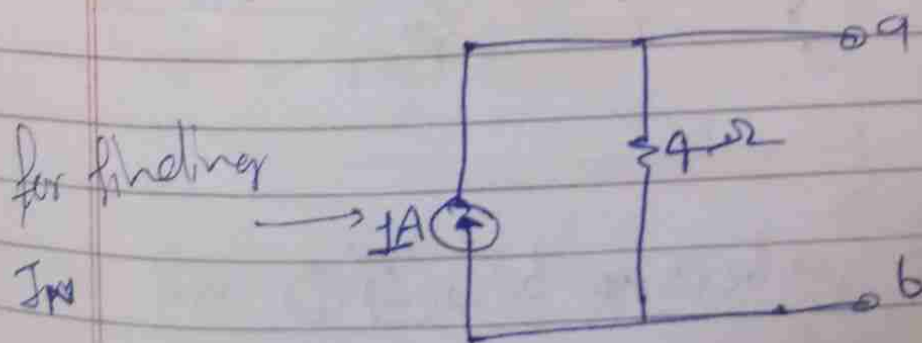

for finding

I_{sc}

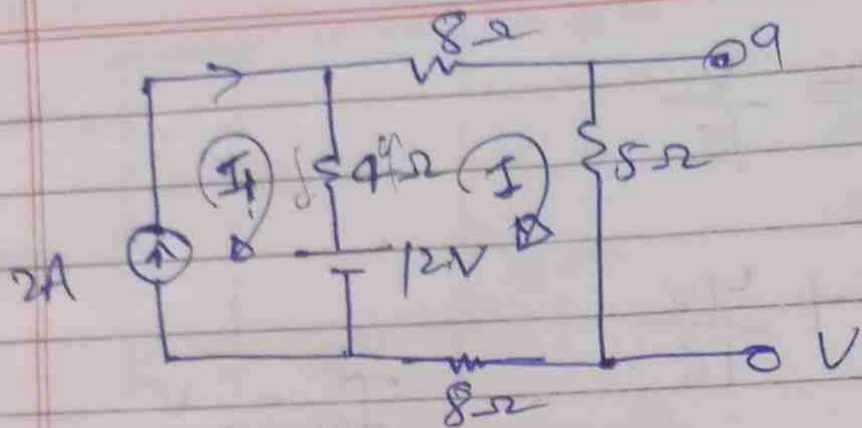

$$V_{ab} = 5I = 4V$$

$$= \frac{5 \times 4}{5}$$

$$8I + 5I + 8I + 12 + 4(I - I_1) = 0$$



$$I_1 = 2A$$

$$8I + 5I + 8I$$

$$25I = 20$$

$$I = \frac{4}{5}$$

Star - Delta Transformation :-

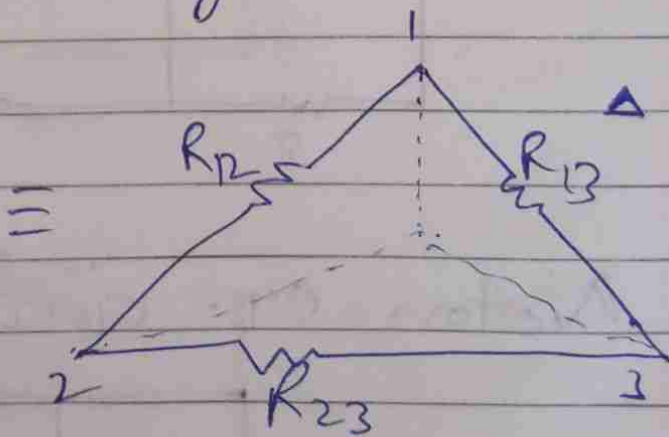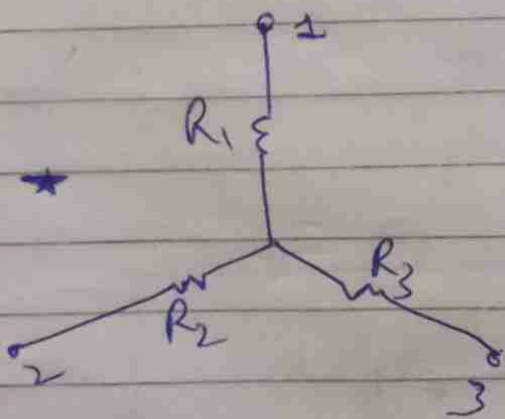

~~Resistor~~

Connect a battery b/w (1/2) and

$$R_1 + R_2 = \frac{R_{12}(R_{13} + R_{23})}{R_{12} + R_{13} + R_{23}} \quad (1)$$

Simplify

$$R_2 + R_3 = \frac{R_{23} \times (R_{12} + R_{13})}{R_{12} + R_{23} + R_{13}} \quad \text{--- (B)}$$

$$R_1 + R_3 = \frac{R_{13} \times (R_{23} + R_{12})}{R_{12} + R_{13} + R_{23}} \quad \text{--- (C)}$$

(A) - (B)

$$R_1 - R_3 = \frac{R_{12} \times R_{13} - R_{13} R_{23}}{R_{12} + R_{13} + R_{23}} \quad \text{--- (D)}$$

(C) + (D)

$$2R_1 = \frac{2R_{12} R_{13} - R_{13} R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{12} \times R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_3 = \frac{R_{13} R_{23}}{R_{12} + R_{13} + R_{23}} \quad \text{--- (f)}$$

$$\Rightarrow R_1 R_2 + R_1 R_3 + R_2 R_3 = \frac{R_{12}^2 R_{13} R_{23} + R_{13}^2 R_{12} R_{23} + R_{23}^2 R_{12} R_{13}}{(R_{12} + R_{13} + R_{23})^2}$$

$$= \frac{R_{12} \cdot R_{12} R_{13} R_{23}}{R_{12} + R_{13} + R_{23}} \quad \text{--- (e)}$$

10/11/15

10/11/15

212

10/11/15

10/11/15

10/11/15

C/P

10/11/15

10/11/15


$$\frac{R_1 R_2 + R_1 + R_2}{R_3} = R_{12}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$


$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$



Q





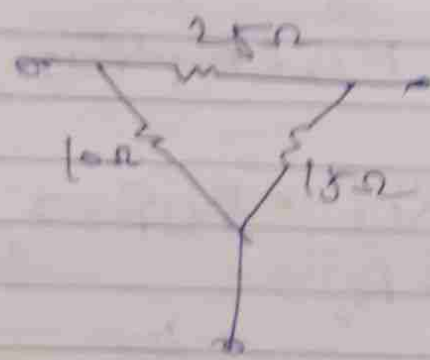


⇒

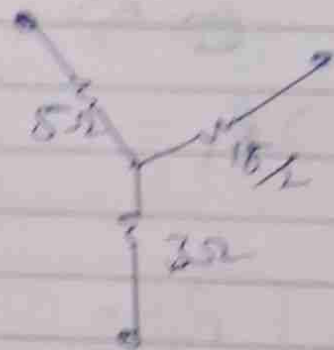

Q

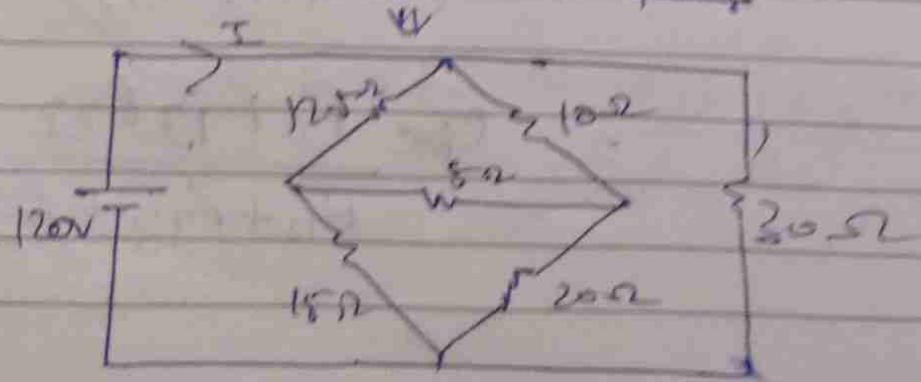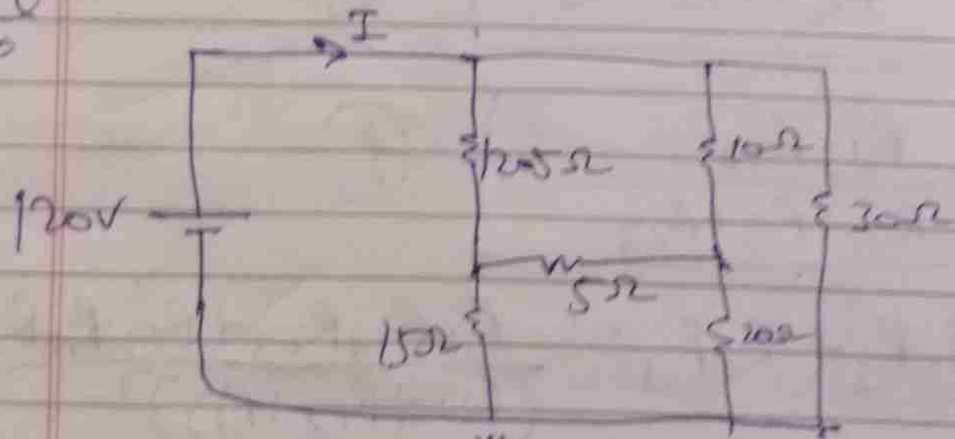


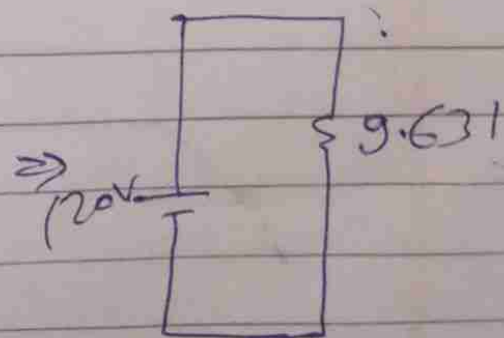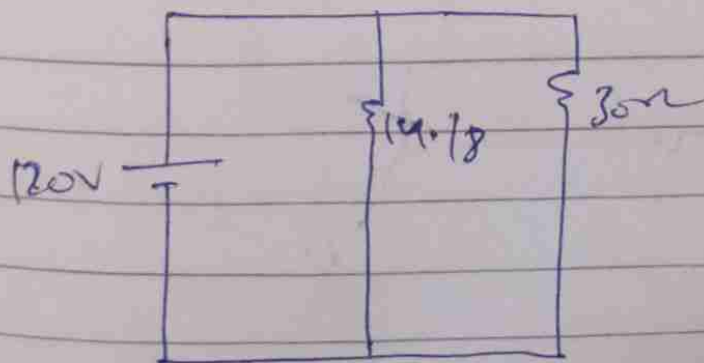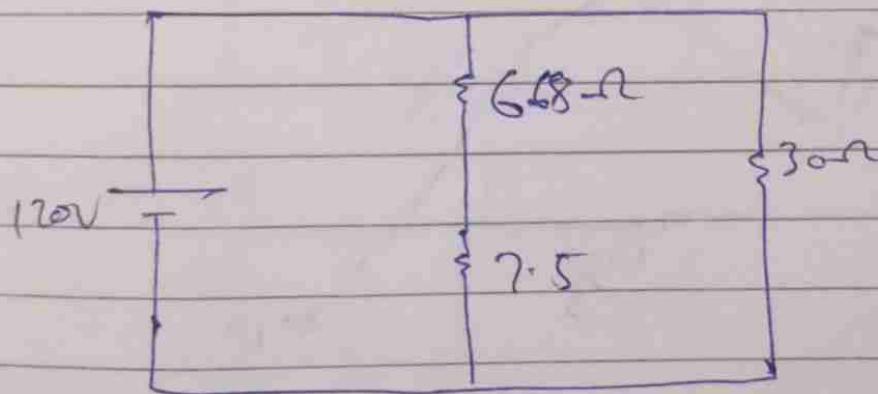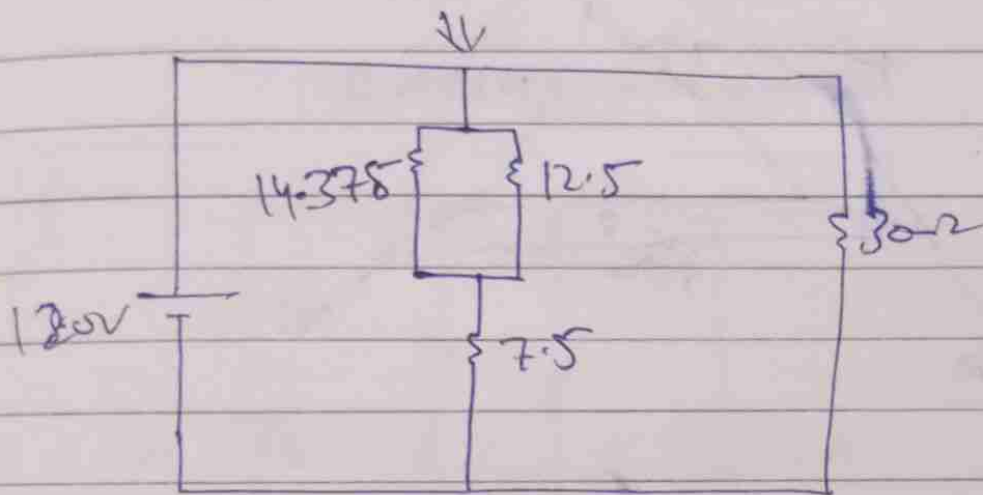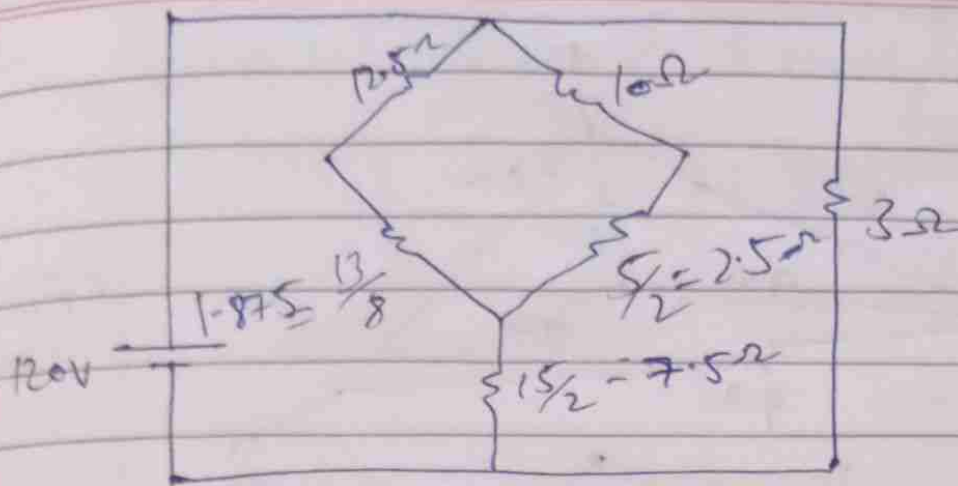




$$I = \frac{120}{9.631}$$

$$12.459A$$


Q

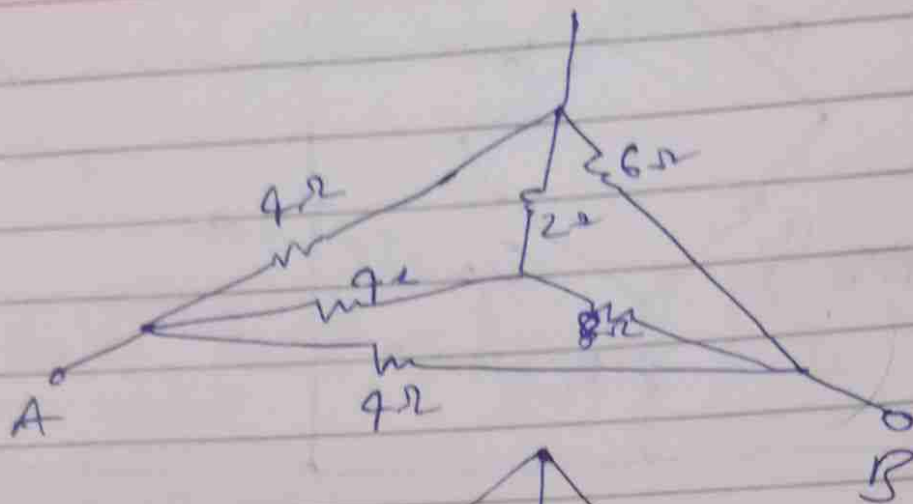


$$R_{AB} = ?$$

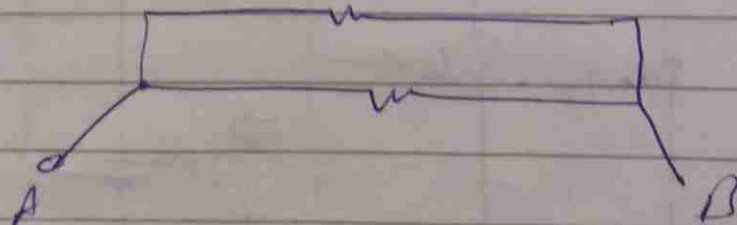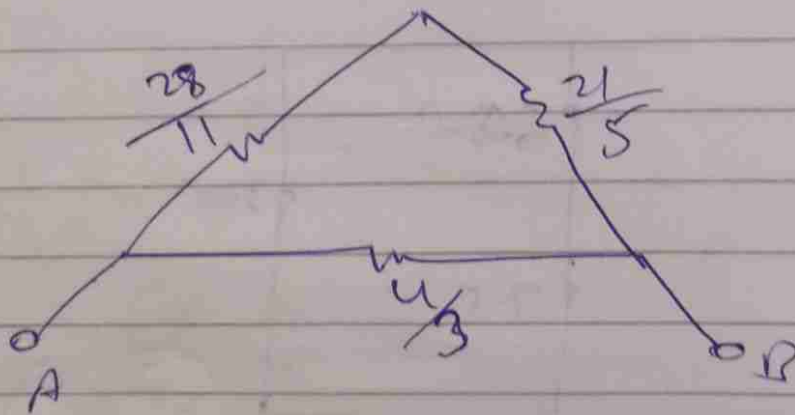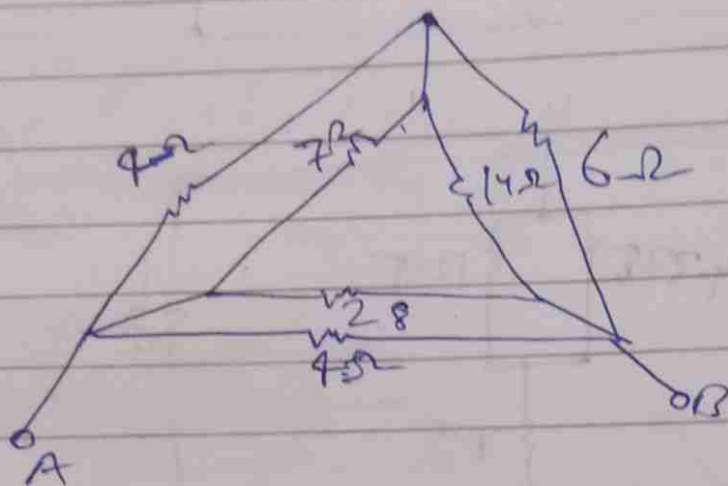

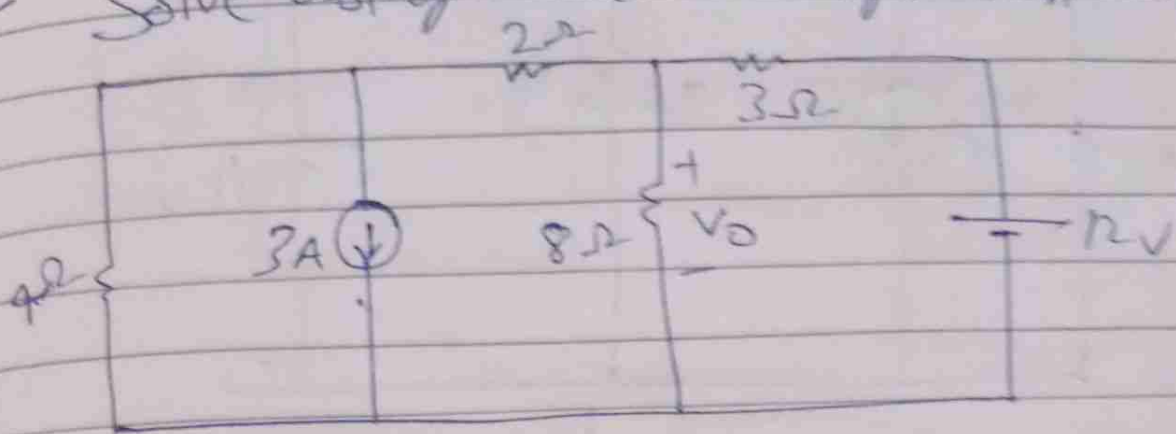
Solve using Source transformation and find V_0








Note if

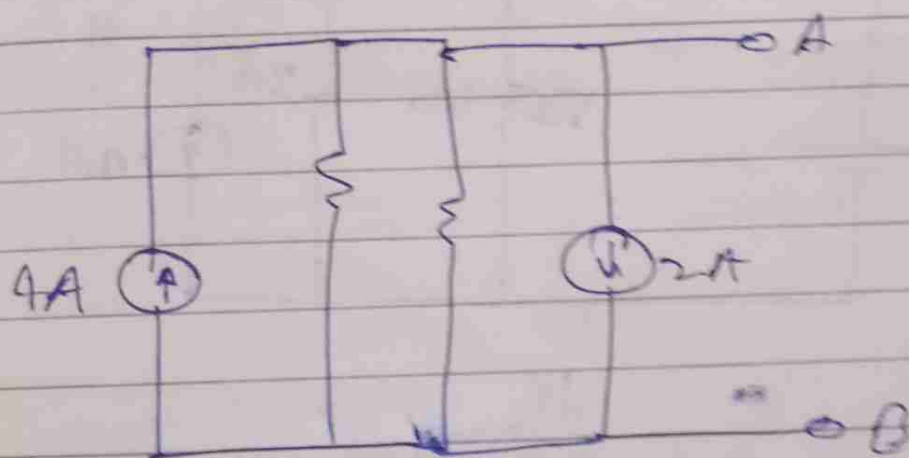

$$4A - 2A = 2A$$


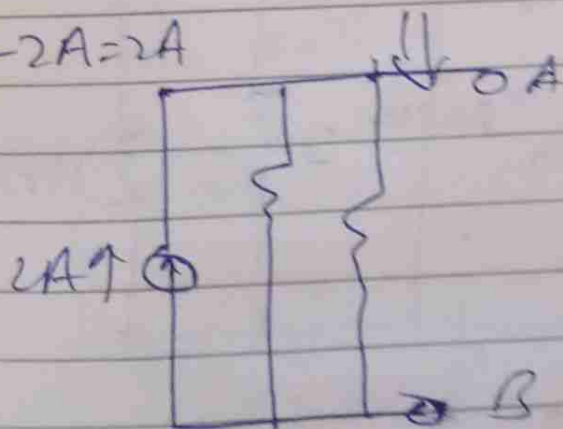


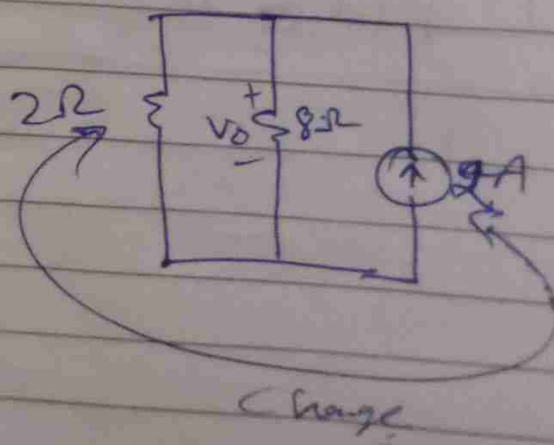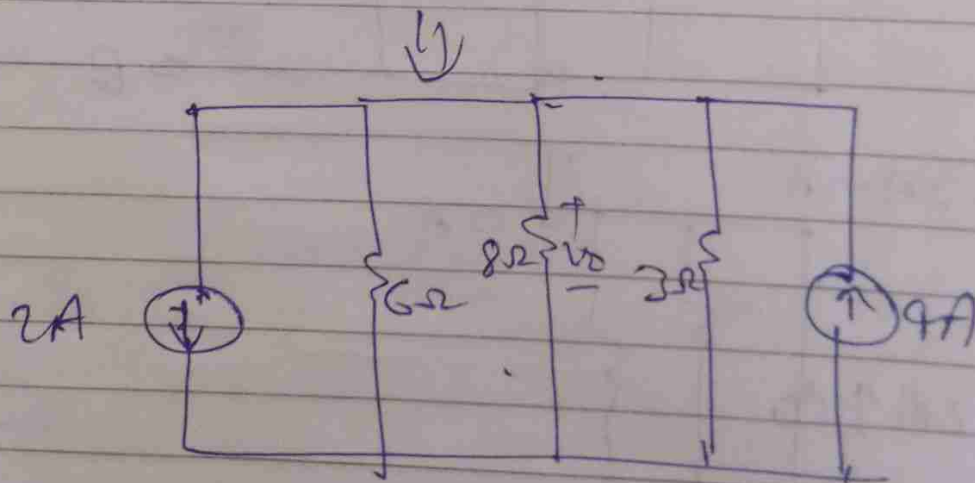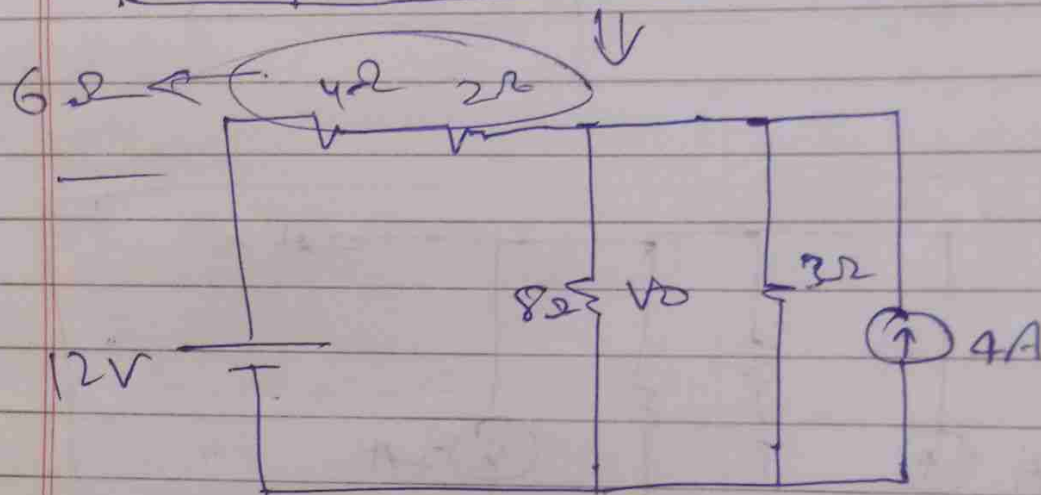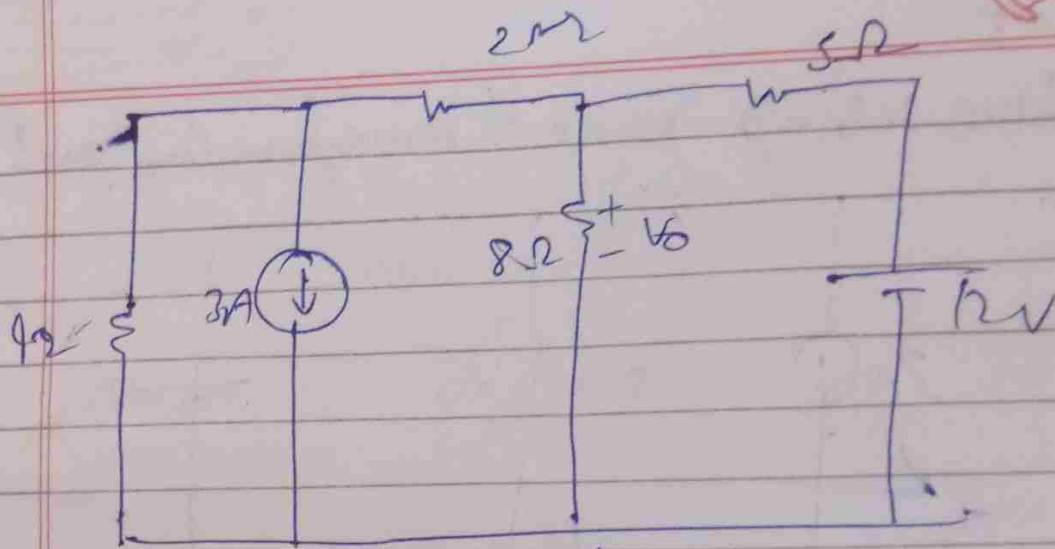

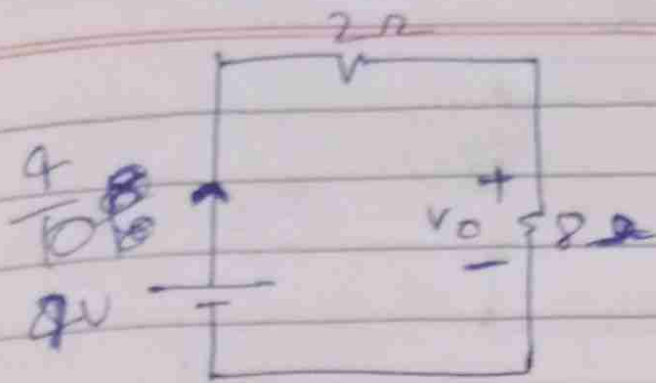

$$V_0 = 3.2 \text{ V}$$
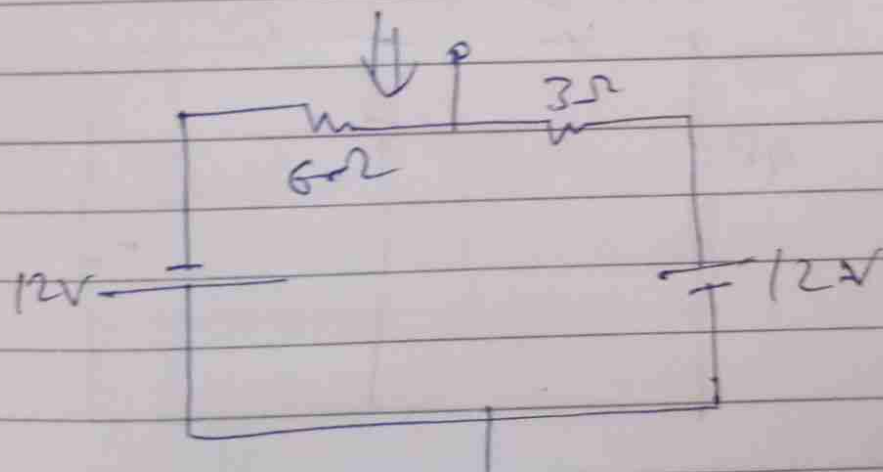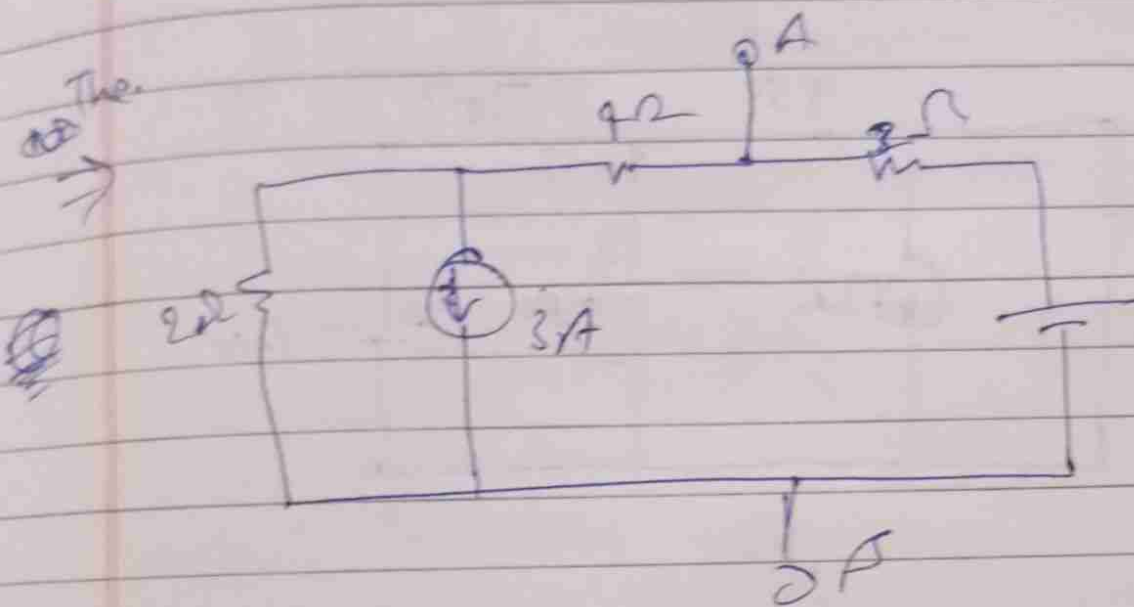
$$V_0 = \frac{8 \times 8}{10} = \frac{4 \times 8}{10}$$




$$12 + 6I + 3I + 12 = 0$$

$$9I = -24$$




$$I = \frac{-24}{9} = -\frac{8}{3}$$

$$-8 \times 8 + 12 = V_{AB} = 0 \quad V_{AB} = 4\text{V}$$

~~$V_{AB} = 4\text{V}$~~

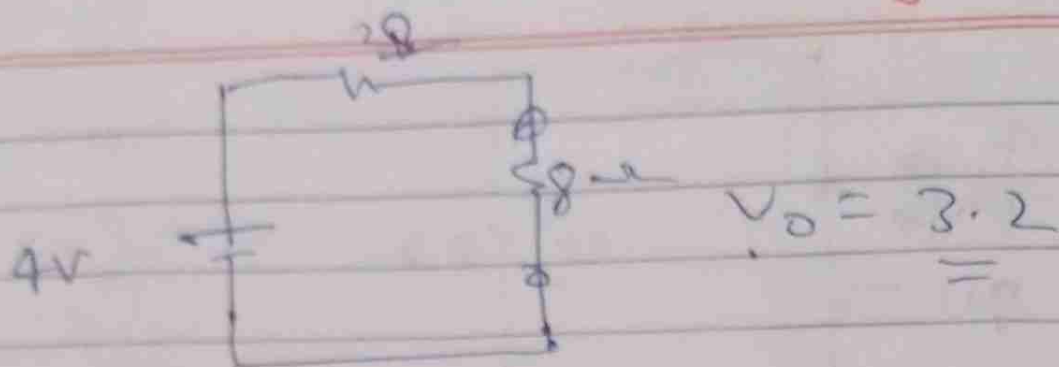

Super

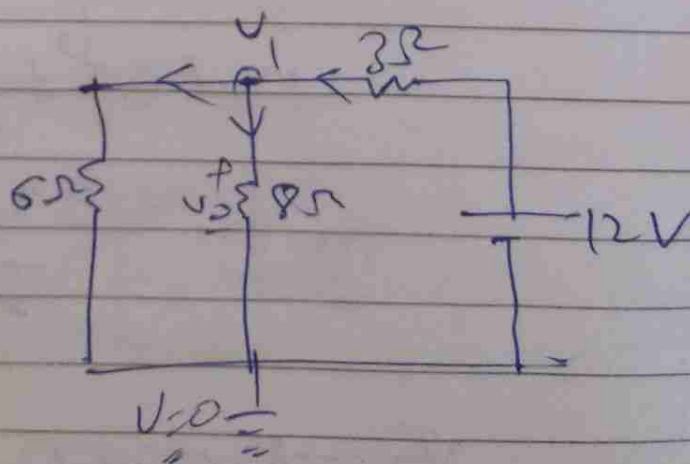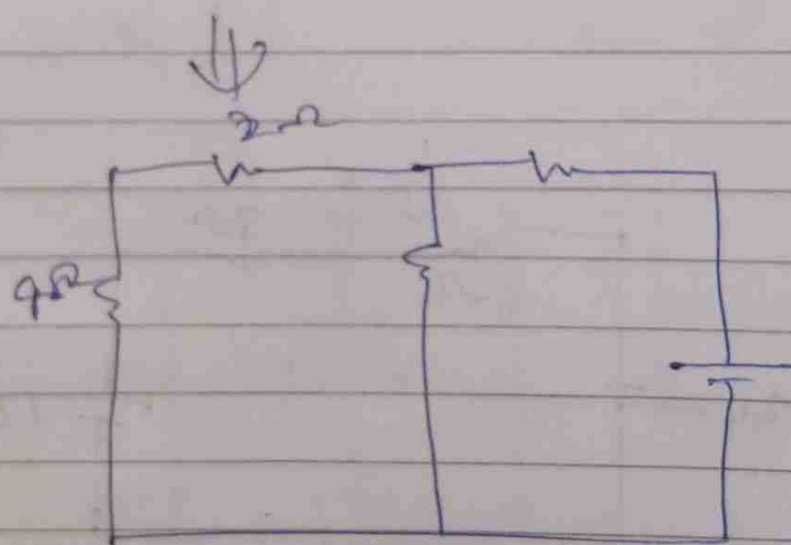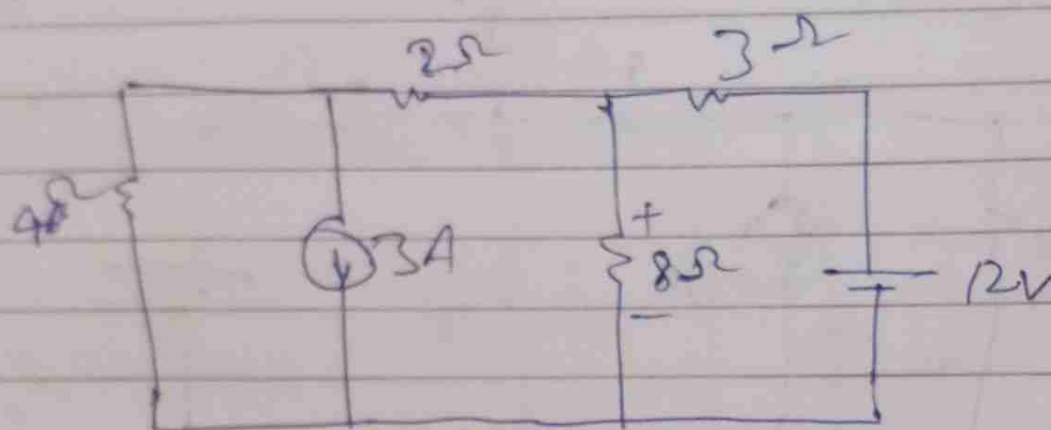

$$\frac{V_1}{6} + \frac{V_1}{8} = \frac{12 - V_1}{3}$$


$$\frac{21V_1}{24} = \frac{12 - V_1}{3}$$

$$\frac{7V_1}{8} + \frac{3V_1}{8} = 4$$

$$\frac{10V_1}{8} = 4$$

$$V_1 = \frac{32}{10} = 3.2$$

$$I_1 = 0.8 \text{ A}$$

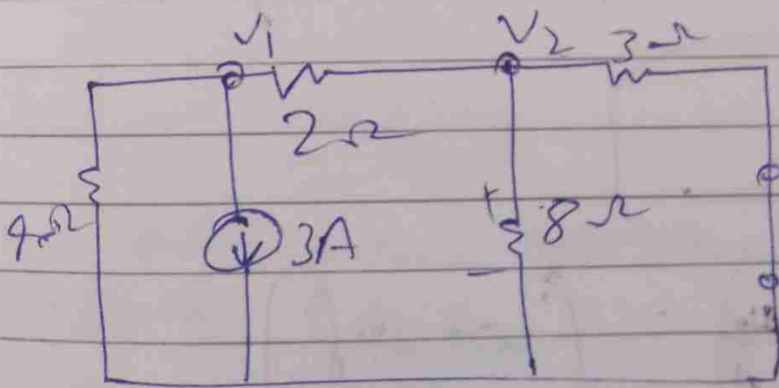

$$\underline{V_1}$$

A.C. Circuit


Date _____
Page _____
Time _____

#

↓ Sinusoid ⇒

↓
sin (Periodic fⁿ)

Fourier series

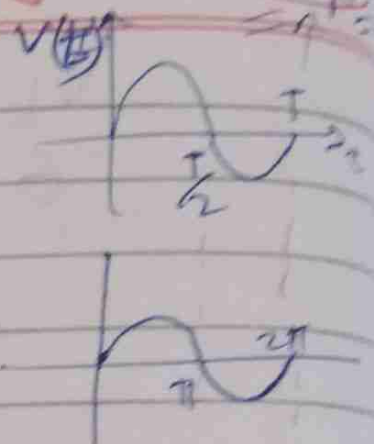

Sinusoid:- $\begin{cases} V(t) = V_m \cos \omega t \\ V(t) = V_m \sin(\omega t) \end{cases}$

Angular frequency (rad/s) → ω
Argument (rad) → ωt
Amplitude of sinusoid
or Peak value of sinusoid
or Max. value of sinusoid

$$\rightarrow T = \frac{2\pi}{\omega}$$

$$f = \frac{1}{T} \text{ Hz}$$


Hertz

$$\omega = 2\pi f$$

→ $V(t) = V_m \sin(\omega t + \phi)$ → Phase diff.

→ Periodic fⁿ:- $f(t) = f(t + nT)$

Phase:-

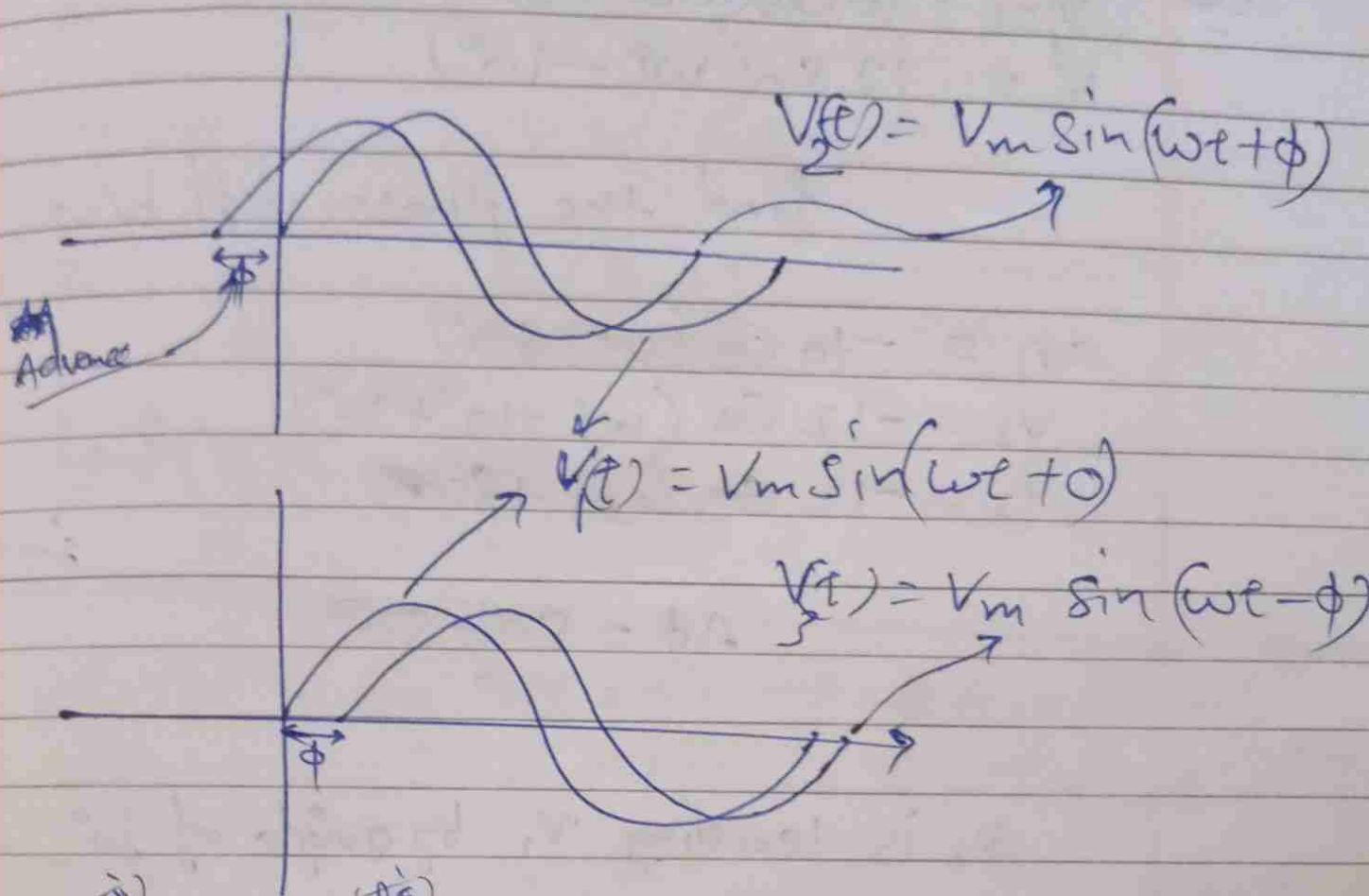


(पुर्वा) (पश्चा)

leading lagging

V_2 is leading V_1 by ϕ from	V_1 is lagging V_2 by ϕ
---	-------------------------------------
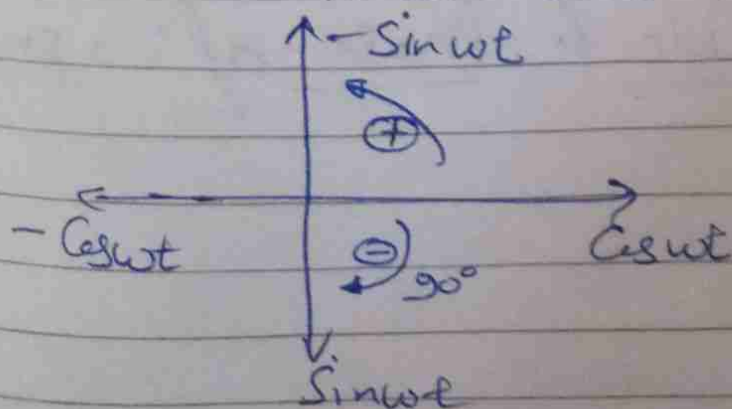
$$\Rightarrow V(t) = 10 \cos(\omega t + 10^\circ) \Rightarrow$$
$$= 10 \sin(\omega t + 10 + 90^\circ)$$
$$= -10 \sin(\omega t + 10 - 90^\circ)$$
$$\uparrow -\sin \omega t \quad = -10 \cos(\omega t + 10 + 180^\circ)$$
$$\quad \quad \quad = -10 \cos(\omega t + 10 - 180^\circ)$$



Q

$$V_1 = -10 \cos(\omega t + 50^\circ)$$


$$V_2 = 12 \sin(\omega t - 10^\circ)$$

find the phase diff. b/w V_1 & V_2

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$V_2 = -12 \cos(\omega t - 10^\circ + 90^\circ)$$

$$V_2 = -12 \cos(\omega t + 80^\circ)$$

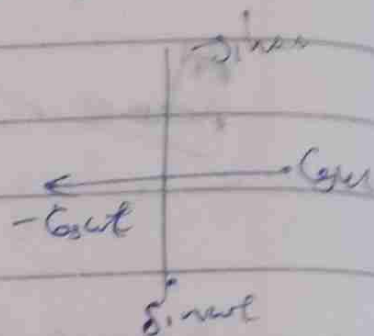

$$\Delta\phi = 80^\circ - 50^\circ$$

$$= 30^\circ$$

V_2 is leading V_1 by angle of 30°

or

$$V_1 = 10 \sin(\omega t + 50^\circ - 90^\circ) = 10 \sin(\omega t - 40^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

$$\Delta\phi = 30^\circ$$

Phasor! - ← Steinhmetz

It is a complex ^{number} no. which contains the amplitude & phase of a sinusoid

$$Z = x + jy \quad \underline{r = \sqrt{-1}}$$

Cartesian

Polar form $Z = r \angle \phi = \sqrt{x^2 + y^2} \angle \tan^{-1}(y/x)$

$$Z = r e^{j\phi} = r(\cos\phi + j\sin\phi)$$


$$\rightarrow Z = Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\rightarrow Z = Z_1 Z_2 = r_1 r_2 \angle (\phi_1 + \phi_2)$$

$$\rightarrow Z = \frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle (\phi_1 - \phi_2)$$

$$\Rightarrow Z = (Z_1)^{1/2} = (r_1)^{1/2} \angle (\phi_1/2)$$

$$\Rightarrow v(t) = V_m \cos(\omega t + \phi) \rightarrow v(t) = \text{Re}[V_m e^{j(\omega t + \phi)}]$$

$$v(t) = V_m \sin(\omega t + \phi) \rightarrow v(t) = \text{Im}[V_m e^{j(\omega t + \phi)}]$$

Time domain representation



$$\text{Re}\left[\bar{V} e^{j\omega t}\right]$$

Phasor Sine wave

Phase domain representation $\rightarrow \bar{V} = V_m e^{j\phi} = V_m \angle \phi$

→ for adding and subtracting any two voltage equations they have same angular frequency.

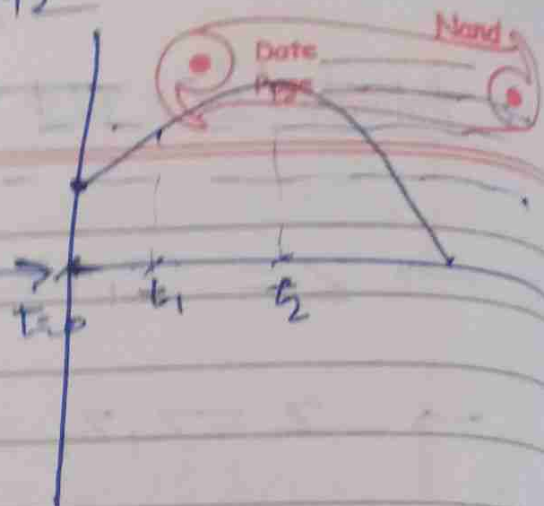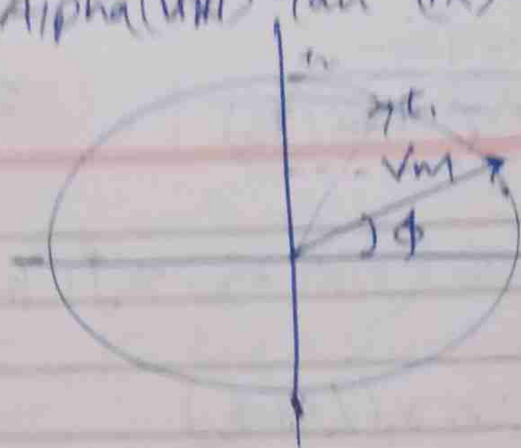Step (i) ON (ii) Shift (iii) Rec (iv) Rec (25.711, 45.51) (v) enter (vi) 13
 (vii) Alpha (viii) tan (ix) 22.742



Evaluate

$$= \left(40 \angle 50^\circ + 20 \angle -20^\circ \right)^{1/2}$$

$$= \left(25.711 + j 30.64 + 17.32 - j 10 \right)^{1/2}$$

$$= \left(43.031 + j 20.64 \right)^{1/2}$$

$$= \left(47.72 \angle 25.62^\circ \right)^{1/2}$$

$$= 6.90 \angle 12.81^\circ$$

Transform these sinusoids into phasors



$$i = 6 \cos(50t - 40^\circ) A = 6 \angle -40^\circ A$$

$$v = -4 \sin(30t + 50^\circ) V$$

$$= 4 \cos(30t + 140^\circ) = 4 \angle 140^\circ V$$
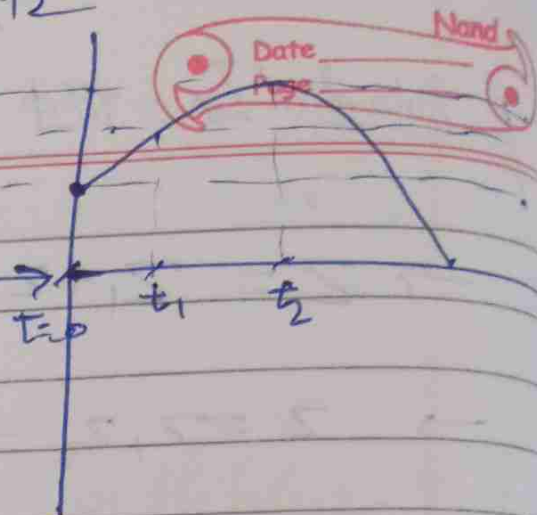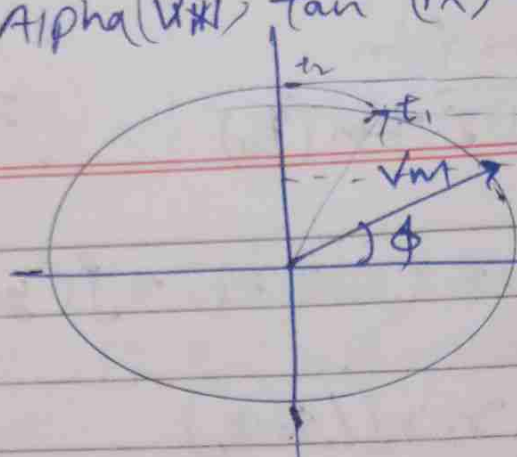
#2 Type

Step (i) ON (ii) Shift (iii) Rec (iv) Rec (v) Rec (vi) Alpha (vii) tan (ix) 22.742



Evaluate

$$= \left(40 \angle 50^\circ + 20 \angle -20^\circ \right)^{1/2}$$

$$\left(25.711 + j 30.64 + 17.32 - j 10 \right)^{1/2}$$

$$\left(43.031 + j 20.64 \right)^{1/2}$$

$$\left(47.72 \angle 25.62^\circ \right)^{1/2}$$


$$= 6.90 \angle 12.81^\circ$$

Transform these sinusoids into phasors

$$i = 6 \cos(50t - 40^\circ) \text{ A} = 6 \angle -40^\circ \text{ A}$$

$$v = -4 \sin(30t + 50^\circ) \text{ V}$$
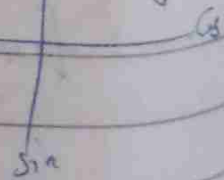
$$= 4 \cos(30t + 140^\circ) = 4 \angle 140^\circ \text{ V}$$



Step: (i) ON (ii) Shift (iii) Pol (iv) Pol (13.14, 22.742) (v) Enter (vi) Value
for angle (vii) Alpha (viii) tan (ix) Enter

→ If $V_1 = -10 \sin(\omega t - 30^\circ) \text{ V} = 10 \angle 150^\circ$

$V_2 = 20 \cos(\omega t + 45^\circ) \text{ V} = 20 \angle 45^\circ$

find $V_1 + V_2$

$V_1 = 5 + j8.6$

$V_2 = 14.14 + j14.142$

$V_1 + V_2 = 19.14 + j22.742$

$= 29.724 \angle 49.91$

$= 29.72 \cos(\omega t + 49.91)$

$V(t) = V_m \cos(\omega t + \phi)$

$\frac{dv}{dt} = -\omega V_m \sin(\omega t + \phi)$

$= \omega V_m \cos(\omega t + \phi + 90^\circ)$

$= \text{Re} [j\omega V_m e^{j\phi} e^{j90^\circ} e^{j\omega t}]$

$= \text{Re} [j\omega V_m e^{j\phi} \cdot e^{j\omega t}]$

Phase of $\frac{dv}{dt} = j\omega V$

$$\Rightarrow \int v dt$$

$$\int V_m \cos(\omega t + \phi)$$

$$\frac{V_m}{\omega} \sin(\omega t + \phi)$$

$$\frac{V_m}{\omega} \cos(\omega t + \phi - 90^\circ) = \text{Re} \left[\frac{V_m}{\omega} e^{j\phi} e^{-j90^\circ} \right]$$

$$= \frac{j V_m}{\omega} \angle \phi$$

$$= \frac{V}{j\omega}$$

$$\cos(-90^\circ)$$

$$= \sin(-90^\circ)$$

Q. Solve using phasor algebra
find $i(t)$ if

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$4\bar{I} + 8 \frac{\bar{I}}{j\omega} - 3 \times 2j\bar{I} = 50 \angle 75^\circ$$

Integrate
phasor
differentiate
or


$$\vec{I}(4 - 10j) = 50 \angle 75^\circ$$

$$\vec{I} = \frac{50 \angle 75^\circ}{(4 - j10)} = \frac{50 \angle 75^\circ}{10.7703 \angle -68.198^\circ}$$

$$= \frac{46.4239 \angle 143.1^\circ}{10.7703}$$

$$= 4.64 \angle 143.1^\circ$$

Phasor relationship for elements:-

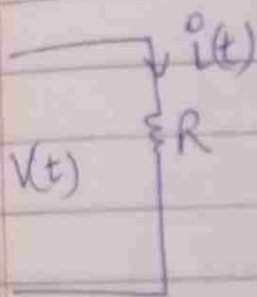

$$i(t) = I_m \cos(\omega t + \phi) \Rightarrow \vec{I} = I_m \angle \phi$$


$$V = IR$$

$$V(t) = R I_m \cos(\omega t + \phi)$$

$$\vec{V} = R \vec{I} \angle \phi$$

$$\vec{V} = R \vec{I}$$

Inductor :-

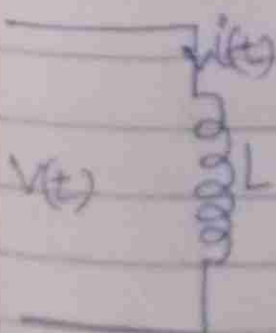

$$i(t) = I_m \cos(\omega t + \phi)$$

$$V_i = L \frac{di}{dt}$$

$$V(t) = -L \omega I_m \sin(\omega t + \phi) = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$


Date _____
Page _____
Nand

$$V(t) = \text{Re} \left[\omega L I_m e^{j\phi} e^{j90^\circ} e^{j\omega t} \right]$$

$$\bar{V} = j\omega L I_m \angle \phi$$

$$\bar{V} = j\omega L \bar{I}$$

Capacitor :-

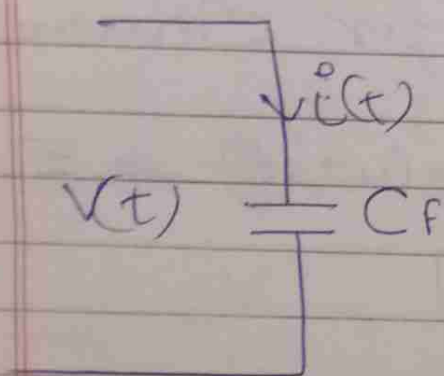

$$V(t) = V_m \cos(\omega t + \phi)$$

$$i(t) = C \frac{dv}{dt}$$

$$\bar{I} = j\omega C \bar{V}$$

Impedance :-

$$Z = \frac{\bar{V}}{\bar{I}}$$

↓

This is the property of appse
the Sinusoids

→ $Z = R$ (for pure Resistive element circuit)

→ $Z = j\omega L$ (for pure inductive circuit)


→ $Z = \frac{1}{j\omega C} = -\frac{j}{\omega C}$ (for pure Capacitor element circuit)

$$Z = R + jX$$


$$R = \operatorname{Re}(Z)$$

$$X = \operatorname{Im}(Z)$$


↑
Reactance

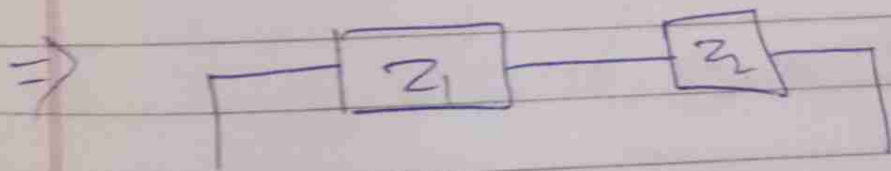

$$Z = Z_1 + Z_2$$

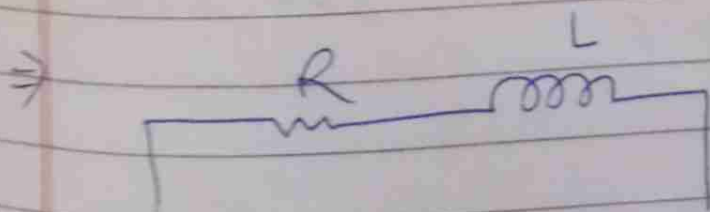


$$Z = R + j\omega L$$

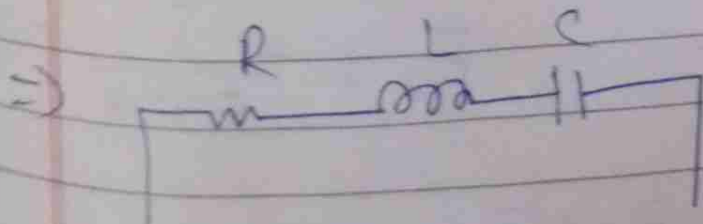

$$Z = R + j\omega L - \frac{j}{\omega C}$$
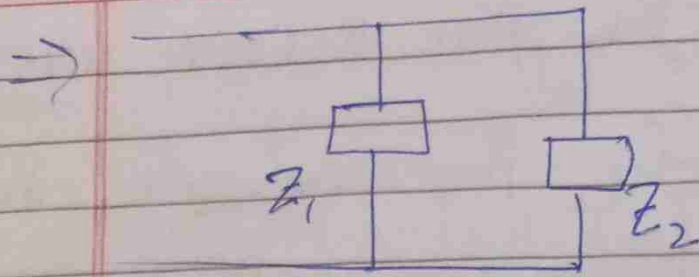
$$Z = R + j\left(\omega L + \frac{1}{\omega C}\right)$$




$$Z = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y = Y_1 + Y_2 + \dots + Y_N$$

$$Y = \frac{1}{Z}$$

Admittance

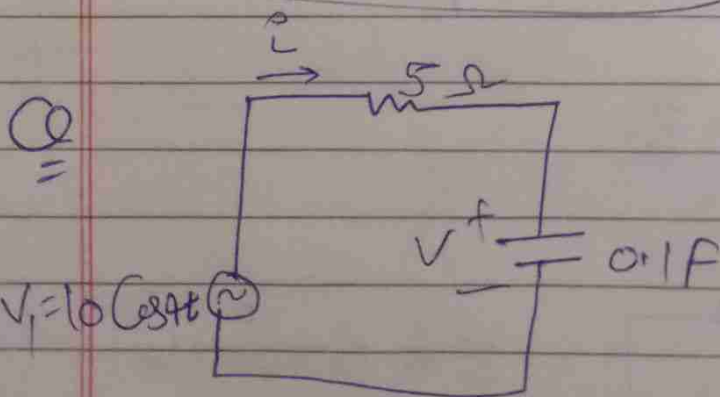

find i, v

Sol.

$$Z_1 = 5 \Omega$$

$$Z_2 = -\frac{j}{0.1 \times 4} = -j2.5$$

$$Z = Z_1 + Z_2$$

$$= (5 - j2.5) \Omega$$

$$\bar{V} = 10 \angle 0^\circ$$

$$Z\bar{I} = \bar{V}$$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{10 \angle 0^\circ}{5 - j2.5}$$

$$= \frac{10 \angle 0^\circ}{5.59 \angle -26.56^\circ}$$

$$= 1.78 \angle 26.56^\circ$$


$$i(t) = 1.788 \cos(4t + 26.56^\circ)$$

$$V = \bar{I} \times Z_2$$

$$Z_2 = 0.4 \angle 90^\circ \quad V = (1.788 \cos 4t + 26.56^\circ) \times (0.4 \angle 90^\circ)$$

$$V = (1.788 \angle 26.56^\circ) \times \left(\frac{1}{0.4 \angle 90^\circ} \right)$$

$$V = 4.47 \angle -63.44^\circ$$

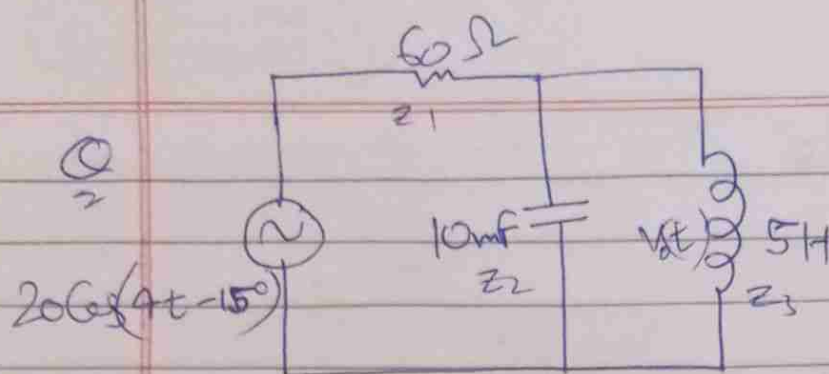

$$V_o = \frac{\bar{V}_s \times Z_{eq}}{Z_1 + Z_{eq}}$$

$$Z_{eq} = \frac{Z_2 \times Z_3}{Z_2 + Z_3} = \frac{-j20 \times j25}{j20 - j25}$$

$$Z_1 = 60\Omega \quad Z_3 = j20$$

$$Z_2 = \frac{-j}{10 \times 10^{-3} \times 4}$$

$$= j25$$

$$= \frac{25 \times 20}{-j5}$$

$$Z_{eq} = j100\Omega$$

$$V_o = \frac{20 \angle -15^\circ \times 100 \angle 90^\circ}{60 + j100}$$


$$= \frac{2000 \angle 75^\circ}{116.61 \angle 59.036^\circ}$$

$$= 17.15 \angle 15.964^\circ$$

$$= 17.15 \angle 15.964^\circ$$

Page _____

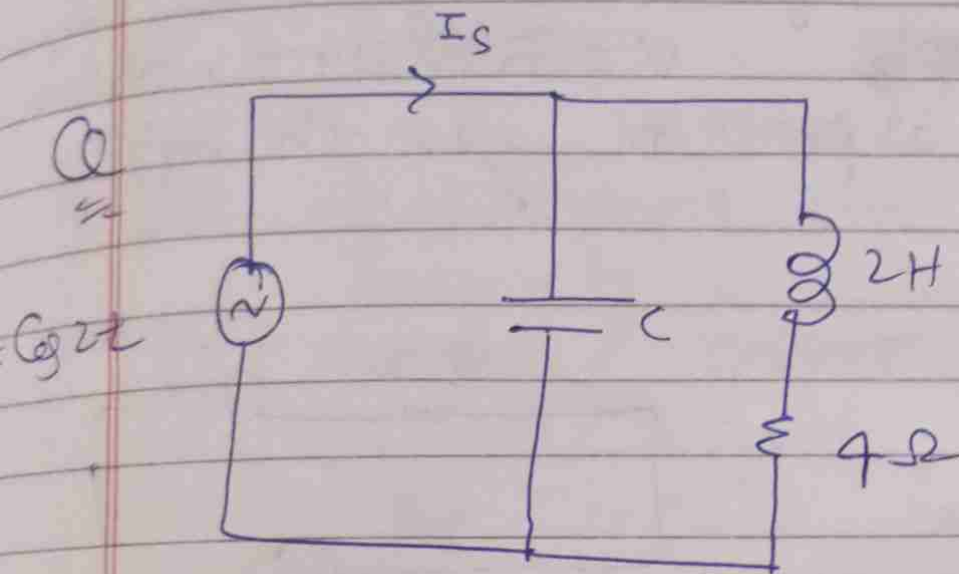
$$V_o(t) = 17.15 \cos(4t + 15.96^\circ)$$



$$C = ?$$

Q A Coil has an inductor of 20mH and a resistance of 5Ω . If it is connected across a supply $V = 50 \sin 314t$. Obtain a similar expression for the supply current.

Soln

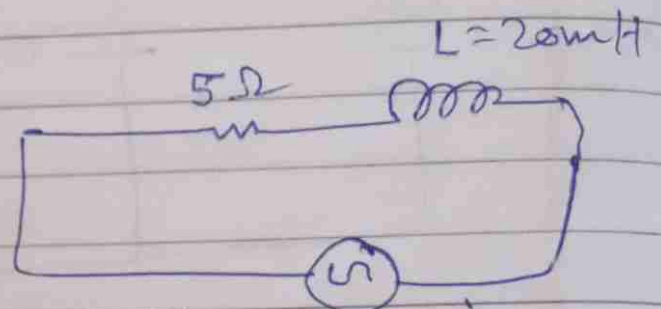

$$Z = (5 + (6.28)j) \Omega$$

$$V = 50 \sin 314t$$

$$\bar{V} = 50 \angle 0^\circ$$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{50 \angle 0^\circ}{5 + (6.28)j}$$


$$\bar{I} = \frac{50 \angle 0^\circ}{8.027 \angle 51.47^\circ}$$

$$\bar{I} = 6.228 \angle -51.47^\circ$$

$$\bar{I} = 6.228 \sin(314t - 51.47^\circ) \text{ A}$$

Q A parallel circuit of two branches, one containing a coil of resistance 5Ω and inductance 38.2mH , the other a non-inductive resistance 16Ω in series with a capacitor of $300\mu\text{F}$.

#

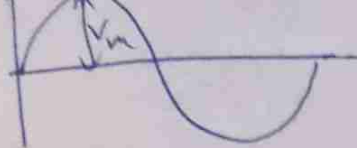

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$


$$V = V_m \angle \phi$$

$$\left\{ \begin{array}{l} V = V_{rms} \angle \phi \\ I = I_{rms} \angle \phi \end{array} \right\}$$

Capacitance. The circuit is connected in ~~com~~ to a 240V, 50Hz supply

- (i) determine (i) the current in each branch
 (ii) The total current
 (iii) The circuit phase angle.
 (iv) The circuit impedance.
 (v) The components of equivalent circuit consisting of resistance and reactance

Solⁿ

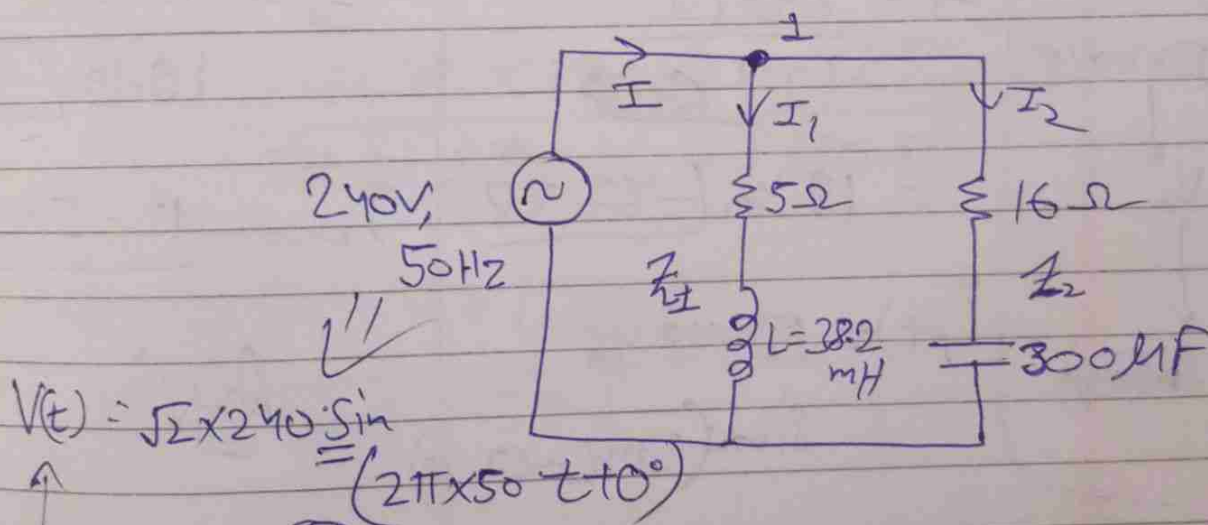

$$V(t) = \sqrt{2} \times 240 \sin(2\pi \times 50 t + 0^\circ)$$

any one
choose

$$V(t) = \sqrt{2} \times 240 \sin(2\pi \times 50 t + 0^\circ)$$

$$Z_1 = 5 + j \times 314 \times 38.2 \times 10^{-3}$$

$$Z_1 = 5 + j(11.9948)$$

$$Z_1 = 5 + j(12) = 13 \angle 67.38^\circ$$

5m

$$\omega = 314$$

$$\frac{100000}{314 \times 300}$$


DATE _____

PAGE _____

$$Z_2 = 16 - \frac{j}{\omega C}$$

$$= 16 - j(10.61)$$

$$= 19.19 \angle -33.54$$

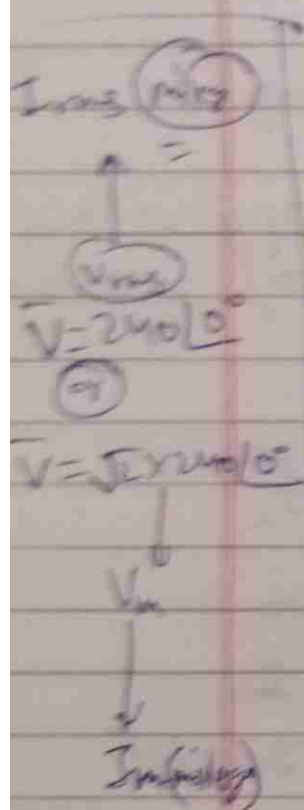

$$\bar{I}_1 = \frac{\bar{V}}{Z_1}$$

$$\bar{I}_1 = \frac{240 \angle 0^\circ}{13 \angle 67.38}$$

$$= 18.46 \angle -67.38$$

$$i(t) = \sqrt{2} \times 18.46 \sin(314t - 67.38)$$

$$\bar{I}_2 = \frac{\bar{V}}{Z_2}$$

$$\bar{I}_2 = \frac{240 \angle 0^\circ}{19.19 \angle -33.54}$$

$$\bar{I}_2 = 12.50 \angle 33.54$$

$$\underline{\underline{\text{Ans (i)}}$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

Apply Kcl at point (1)

$$\bar{I} = 18.46 \angle -67.38$$

$$+ 12.50 \angle 33.54$$

$$= 7.1 + j(17.03) + 10.41 + j(6.9)$$

$$Z = R + jX \rightarrow \text{Inductive}$$

$$Z = R - jX \rightarrow \text{Capacitive}$$

$$\bar{I} = 17.51 - 10.13(j)$$

$$\bar{I} = 20.22 \angle -30.05^\circ$$

$$\text{Ans (ii)} \quad \bar{I} = \sqrt{2} \times 20.22 \sin(314t - 30.05^\circ)$$

$$\text{Ans (iii)} = 30.05^\circ$$

$$Z = \frac{Z_1 \times Z_2}{Z_1 + Z_2} = \frac{\bar{V}}{\bar{I}}$$

$$Z = \frac{13 \angle 67.38^\circ \times 19 \angle -32.51^\circ}{5 + j(16) + 16 - j(10.61)}$$

$$Z = \frac{249.47 \angle 33.84^\circ}{21 + 1.39j}$$

$$Z = \frac{249.47 \angle 33.84^\circ}{21.04 \angle 3.78^\circ}$$

$$Z = \frac{\bar{V}}{\bar{I}}$$

$$= \frac{240 \angle 0^\circ}{20.22 \angle -30.05^\circ}$$

$$\text{Ans (iv)} \quad Z = 11.85 \angle 30.06^\circ$$


$$= 11.86 \angle 30.05^\circ$$

(iv)

$$Z = \frac{10.25 \angle 5.93^\circ}{10.25 + (5.93j)}$$



$$\underline{\underline{Ans = 11.85 \angle 30.06^\circ}} \quad (\text{Angle ko na likhe})$$

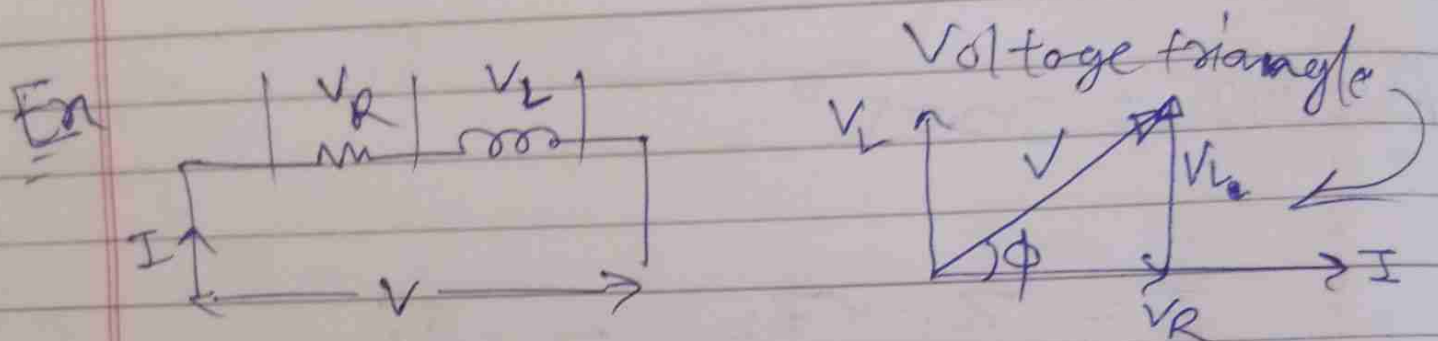Phasor Diagram (Voltage & Impedance Triangle)




$$V = V_R + jV_L \quad V = \sqrt{V_L^2 + V_R^2}$$

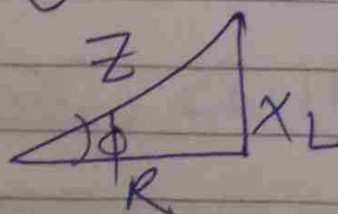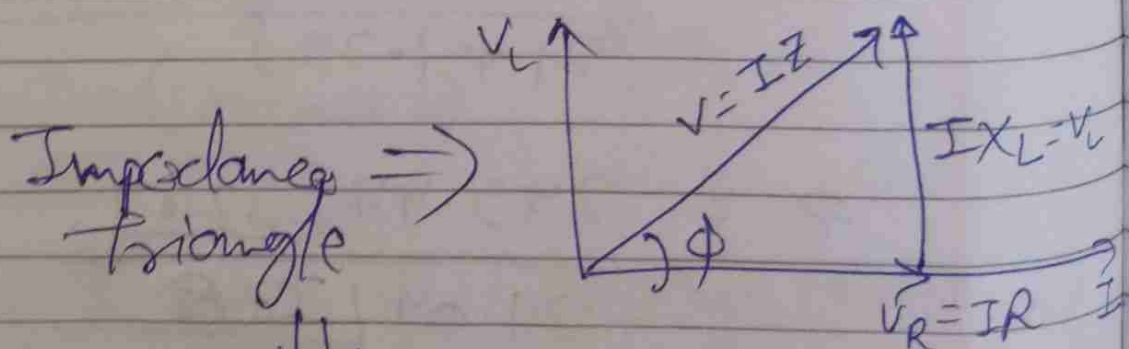
$$\tan \phi = \frac{V_L}{V_R} \quad \cos \phi = \frac{V_R}{V}$$



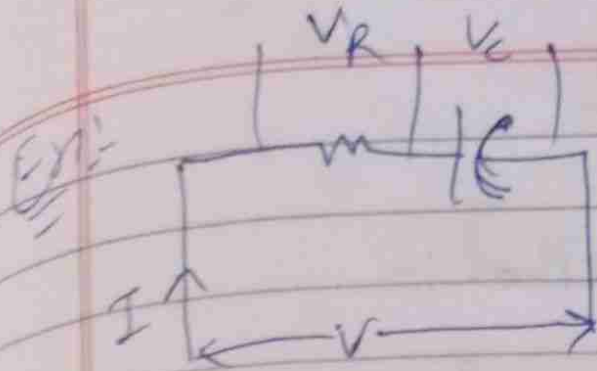(Power factor) $\Rightarrow \cos \phi = \frac{R}{Z}$



Voltage triangle

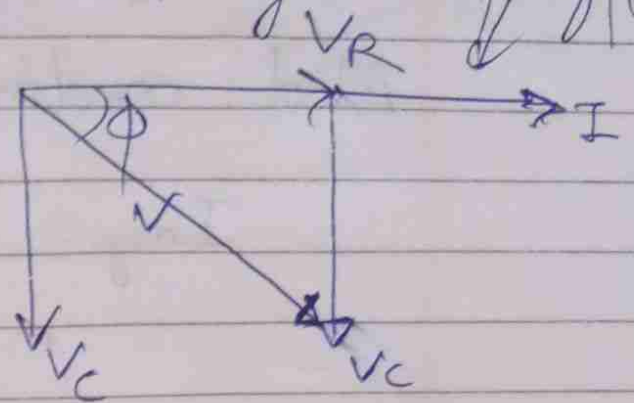


$$V = V_R - jV_C$$


$$V = \sqrt{V_R^2 + V_C^2}$$

$$\cos \phi = \frac{V_R}{V}$$

Impedance triangle

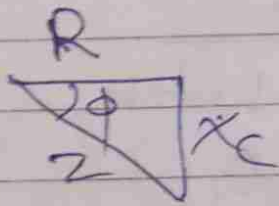

$$\cos \phi = \frac{R}{Z}$$

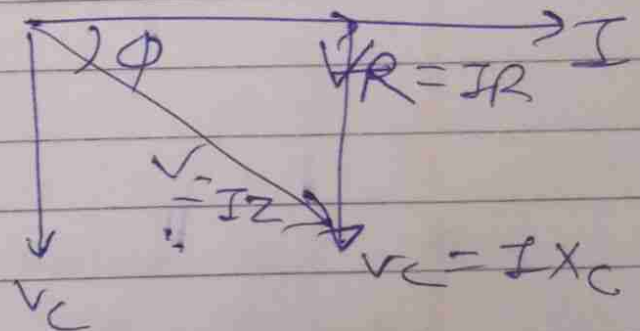

Average Value:-


Mid ordinate method:-

$$I_{avg} = \frac{i_1 + i_2 + \dots + i_n}{n}$$

Integration Method:-


$$dA = i d\theta$$

$$A = \int_0^{\theta_1} i d\theta$$

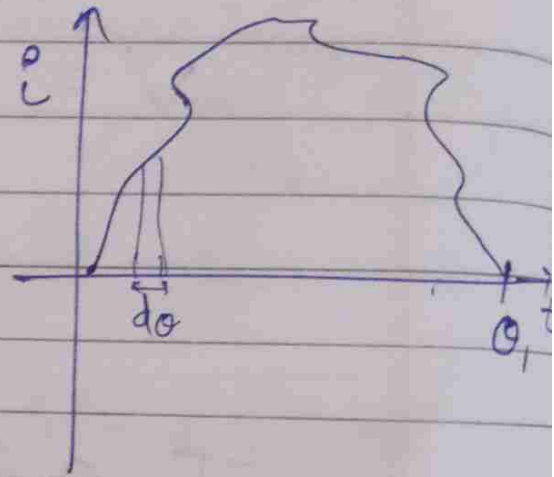


$$\text{Avg. Value} = \frac{\text{Area}}{\text{Base Width}}$$
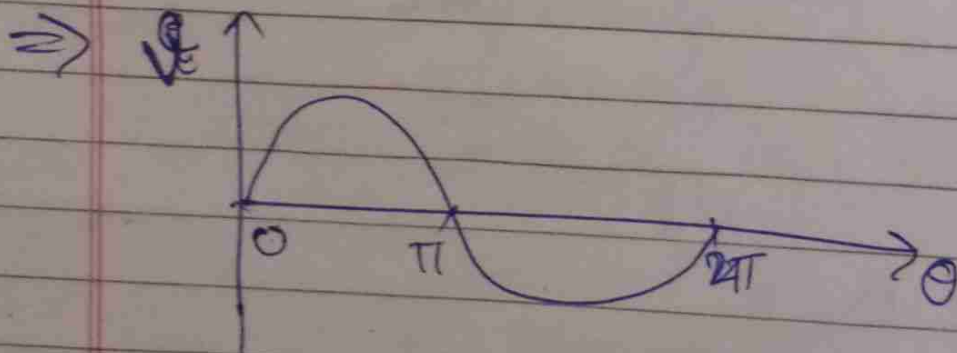
$$= \frac{1}{\theta_1} \int_0^{\theta_1} i d\theta$$



$$I_{\text{sin}} = \cos 0 + i1$$

$$I_{\text{cos}} = -\sin 0$$

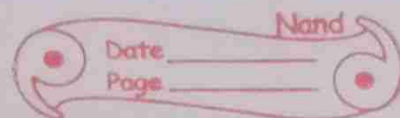

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t d\omega = \frac{1}{2\pi} V_m [\cos \omega]_0^{2\pi}$$

Avg. of Half Cycle

$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d\omega$$


$$= \frac{1}{\pi} V_m [\cos \omega]_0^{\pi}$$

$$= \frac{2}{\pi} V_m$$

RMS Value

RMS or Effective value of an alternating current is equal to that DC current which when flowing through a given resistive network delivers same amount of power to the circuit as is delivered by alternating current flowing through the same circuit.

$$G_{s2\theta} = 1 - 2\sin^2\theta$$

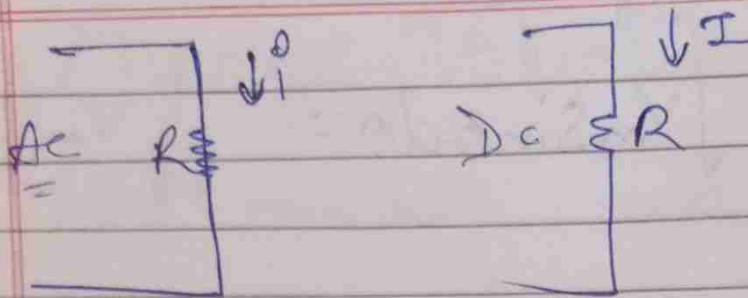

$$I_{eff}^2 R = \frac{1}{T} \int_0^T i^2 R dt$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$\left\{ \begin{array}{l} \text{Form Factor}(k_f) = \frac{\text{RMS Value}}{\text{Average Value}} \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{Peak Factor}(k_p) = \frac{\text{Peak Value}}{\text{RMS Value}} \end{array} \right.$$

Ex1.

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin\theta)^2 d\theta}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi \times 2} \int_0^{2\pi} (1 - G_{s2\theta}) d\theta}$$

$$(1,0) \quad (2, -4V) \quad y = \frac{-4}{-1} (x-1)$$


$$y = \frac{-4}{-1} (x-1)$$

Date: 9/11/19
Page: _____

$$V_{rms} = \sqrt{\frac{V_m^2}{4\pi} \left[\theta + \frac{\sin 2\theta}{2} \right]_0^{2\pi}}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{4\pi} (2\pi)}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

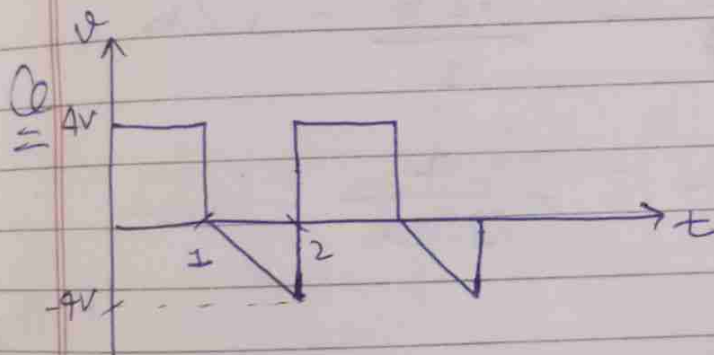

find avg, RMS, FF, PF.

Solu

avg:

$$V = 4 \quad 0 < t < 1$$

$$V = -4t + 4 \quad 1 < t < 2$$

$$\text{avg} = \frac{1}{2} \left\{ \int_0^1 4 dt + \int_1^2 (-4t + 4) dt \right\}$$

$$= \frac{1}{2} \left\{ [4t]_0^1 + \left[-\frac{4t^2}{2} + 4t \right]_1^2 \right\}$$

$$= \frac{1}{2} [4 - 2] = 1$$

$$\int_0^{\pi} \sin \theta d\theta = [-\cos \theta]_0^{\pi}$$





$$V_{rms} = \sqrt{\frac{1}{2} \left\{ \int_0^1 16 dt + \int_1^2 (-4t+4)^2 dt \right\}}$$

$$= \sqrt{\frac{1}{2} \left\{ 16 + 42.6 + 32 - 64 - 5.3 - 16 + 16 \right\}}$$

$$= 3.26$$

$$k_F = \frac{F \cdot F}{\text{Avg.}} = \frac{326}{1} = 3.26$$
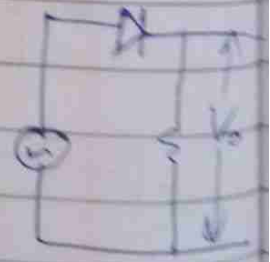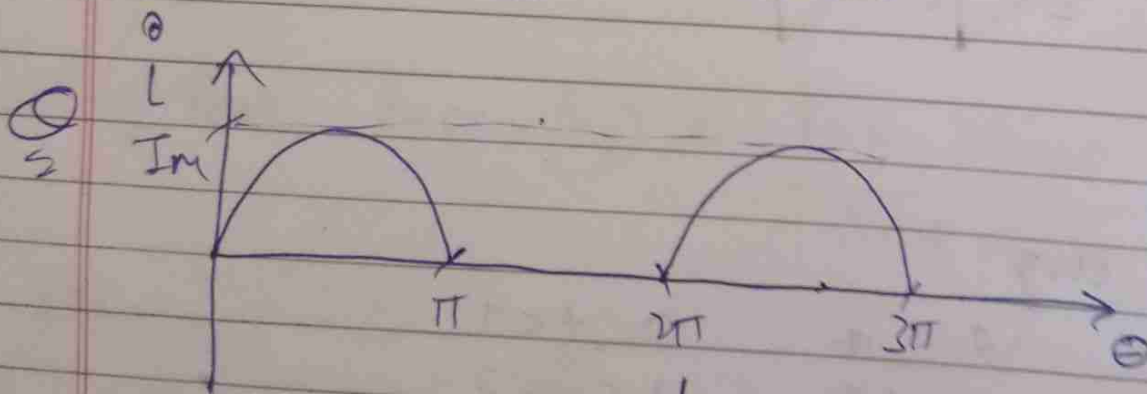
$$k_p = \frac{P \cdot F}{R_{ms}} = \frac{4}{3.26} = 1.22$$



find Avg. Rms, PF, PF

$$I_{avg} = \frac{1}{T} \int_0^T i dt$$

$$16t^2 + 16 - 32t \quad \left(\frac{16t^2}{4} + 16 - 16t \right)^2$$

$$= \frac{1}{2\pi} \left\{ \int_0^{\pi} I_m \sin^2 \omega t d\omega + \int_{\pi}^{2\pi} 0 d\omega \right\}$$

$$= \frac{I_m}{\pi}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \sin^2 \omega t d\omega}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} (1 - \cos 2\omega t) d\omega}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left(\omega + \frac{\sin 2\omega t}{2} \right) \Big|_0^{\pi}}$$


$$= \sqrt{\frac{I_m^2}{4\pi} (\pi)}$$

$$= \frac{I_m}{2}$$

$$F.F. = \frac{I_m/2}{I_m/\pi}$$

$$= \pi/2$$

$$PF = \frac{I_m}{I_m/2} = 2$$

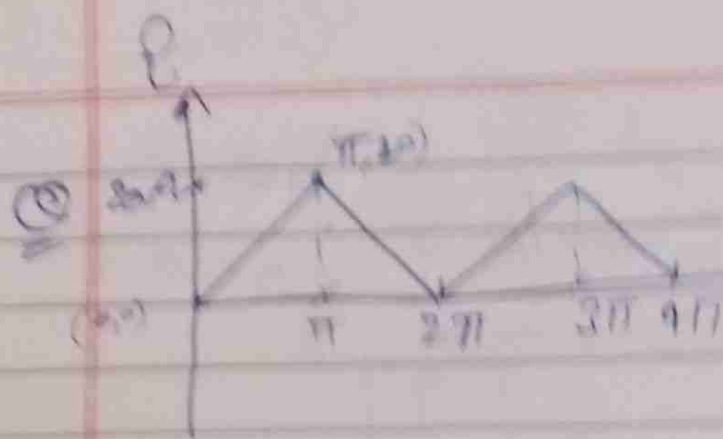

find Avg
of RMS

$$I_{avg} = \frac{1}{\pi} \int_0^{\pi} f \, d\omega$$

$$I_{avg} = \frac{1}{\pi} \int_0^{\pi} \frac{20}{\pi} \omega \, d\omega$$

$$= \int_0^{\pi} \frac{1}{\pi} \times \frac{20}{\pi} [\omega^2]_0^{\pi}$$

$$= \frac{1}{\pi} \times \frac{20}{\pi} [\pi^2]$$

$$= \frac{1}{\pi} \times 20\pi = 20$$

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} f^2 \, d\omega}$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} \frac{400}{\pi^2} \omega^2 \, d\omega}$$

Power

$$P = A + B$$

Real
power/
active power

$$V = V_m \cos(\omega t + \theta_v)$$

$$i = I_m \cos(\omega t + \theta_i)$$

$$P = V_i$$

$$P = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

$$P = \frac{1}{2} \operatorname{Re}[v i^*]$$

$$P = \operatorname{Re}[\bar{V}_{rms} \bar{I}_{rms}^*]$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P = S \cos(\theta_v - \theta_i)$$

↑
APPARENT POWER

POWER FACTOR

$$\begin{cases} v = V_m \angle \theta_v \\ i^* = I_m \angle -\theta_i \\ V_{rms} = \frac{V_m}{\sqrt{2}} \\ I_{rms} = \frac{I_m}{\sqrt{2}} \end{cases}$$

$$V = IZ$$

↑ ↑
Phase Voltage Phase Current

$$\cos(\theta_v - \theta_i) = \frac{P}{S} = \text{P.F. Angle} = \text{P.F.}$$

$$\rightarrow Z = |Z| \cdot \angle(\theta_v - \theta_i)$$

↑
Impedance angle = P.F. angle

→ Power factor depending on circuit load.
→ Power factor leading and lagging

→ If load is pure resistive load then

$$\text{P.F.} = 1$$

$$S = \frac{1}{2} V I^*$$

↑

Complex Power

$$S = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

Real Power

Reactive Power

$$S = P + jQ$$

↑
Avg Imp


↑
Watt

↑
Vol Amp Reactive


$$S = \underbrace{\frac{1}{2} VI^*}_{\text{Reactive}} = \underbrace{VI^*}_{\text{RMS}} = \underbrace{V \cdot I^*}_{V=IZ} = I^2 Z$$

Name _____
 Date _____
 Page _____




Power triangle

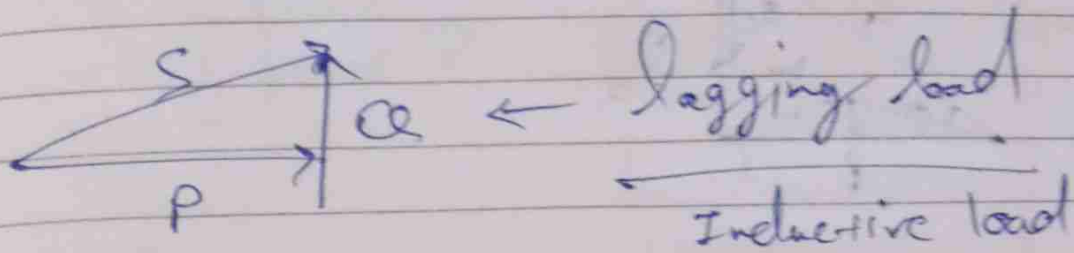

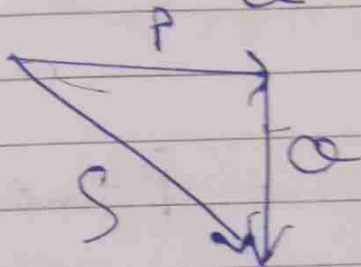
$$Z = \frac{j}{\omega C} \iff \begin{matrix} Q > 0 & \text{Inductive} \\ Q < 0 & \text{Capacitive} \\ Q = 0 & \text{pure Resistive} \end{matrix}$$



Power factor Correction

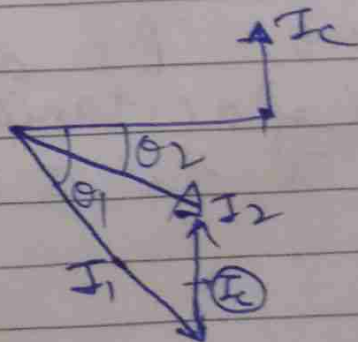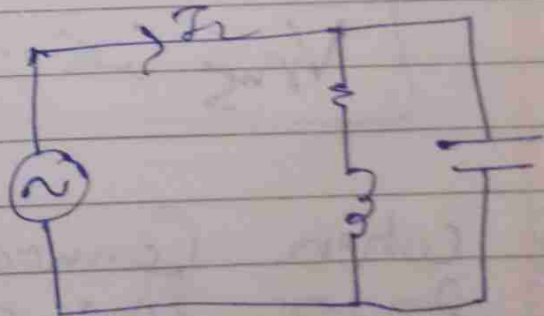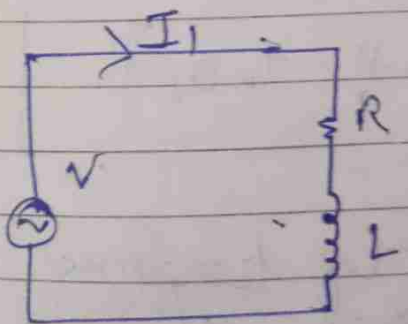

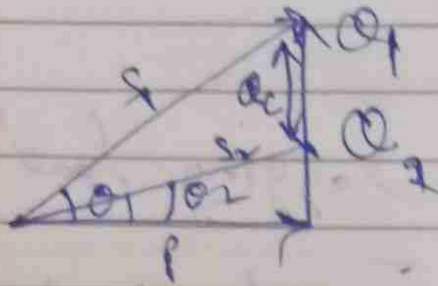

$$Q_c = \phi_1 - \phi_2 = P(\tan \theta_1 - \tan \theta_2)$$

$$P = S_1 \cos \theta_1$$

$$Q_1 = S_1 \sin \theta_1 = P \tan \theta_1$$

$$P = S_2 \cos \theta_2$$

$$Q_2 = S_2 \sin \theta_2 = P \tan \theta_2$$

$$\boxed{V_{rms} \omega C = P(\tan \theta_1 - \tan \theta_2)}$$


Q. When connected to (transformer) 60 Hz power line a load absorbs 9 kW at a lagging p.f. of 0.8. Find the value of capacitance necessary to raise the p.f. to 0.95

120

t_u 36.88

0.95 → 0.32

0.8

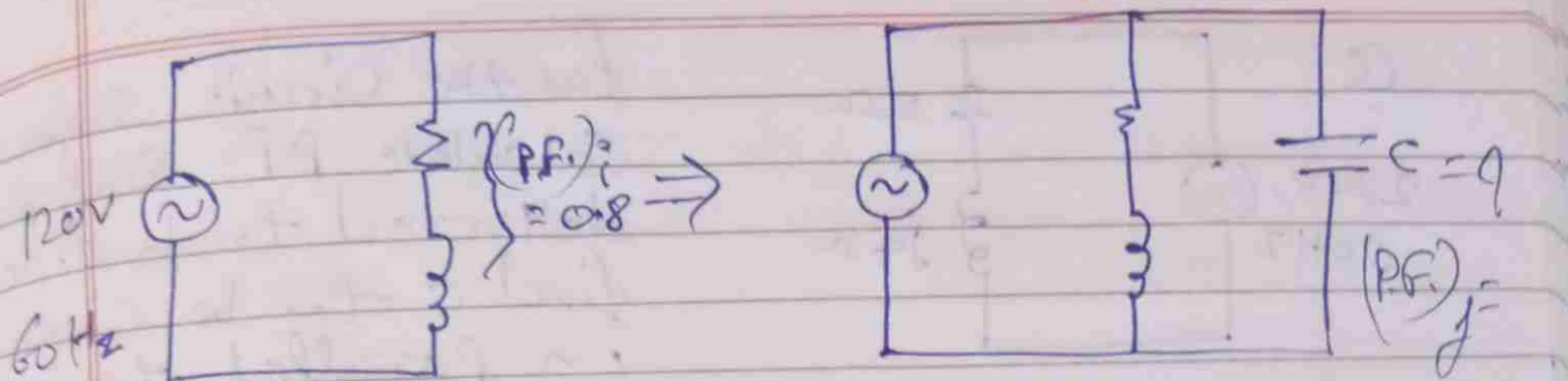


$$V_{rms}^2 \cdot \omega C = P (\tan \theta_1 - \tan \theta_2)$$

$$(120)^2 \times 2 \times \pi \times 60 \times C = 4000 (0.7897 - 0.328682706)$$

$$C = \frac{1684.4}{1728000 \times 3.14}$$

$$= \frac{1684.4}{542.5920}$$

$$= 3.104 \times 10^{-6}$$

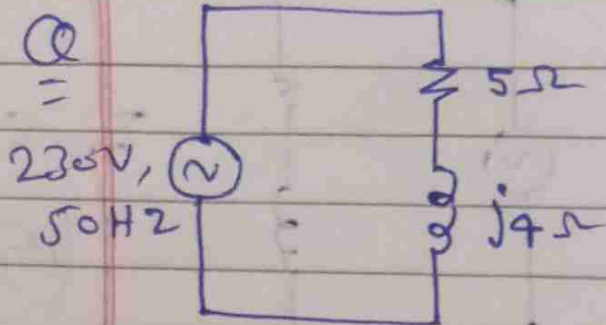

for the circuit shown above
Calculate P.F., Real power
delivered to load. Then
find C-to be connected
in parallel to improve
P.F. to 0.93

$$Z = 5 + j4$$

$$Z = 6.403 \angle 38.65^\circ \rightarrow \text{P.F. angle}$$

$$I = \frac{V}{Z} = \frac{230}{6.403 \angle 38.65^\circ}$$

$$I = 35.92 \angle -38.65^\circ$$

$$\cos 38.65^\circ = 0.7809$$

$$V_{rms}^2 \omega C = P (\tan \theta_1 - \tan \theta_2)$$

$$P = VI \cos \theta$$

$$P = 230 \times 35.92 \times 0.7809$$

$$P = 6451.1 \text{ W}$$


$$P_{\text{real}} = I_{\text{rms}}^2 \times R = (35.92)^2 \times 5$$

$$= 6451.232$$

$$P_{\text{apparent}} = S_{\text{app}} = V_{\text{rms}} \times I_{\text{rms}} = 82.61.6$$

Complex power = $S = P + jQ$
 $= 6451.232 + j5160.98$

$\Downarrow$
Volt amp reactive

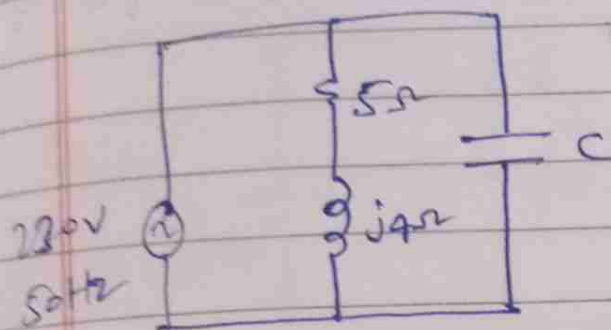

$$V_{rms}^2 \omega C = P(-\tan \phi_1 - \tan \phi_2)$$

$$(230)^2 \times 2 \times \pi \times 50 \times C = 6451.1 (0.7997 - 0.3957)$$

$$= 2610.76017$$

$$\frac{16618600}{}$$

$$= \frac{(1.571)}{}$$

$$= 157.12 \mu F$$



$$Z = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

$$= \frac{(5 + j4)(-j20)}{(5 + j4) + (-j20)} = \frac{20 \angle 90^\circ \times 6.4031 \angle -88.6^\circ}{(5 - j16)}$$


$$\frac{128.062 \angle -50.19^\circ}{(5 - j16)} = \frac{128.062 \angle -50.19^\circ}{16.396 \angle -1.16^\circ} = 7.8102 \angle -50.19^\circ$$

Three Phase System

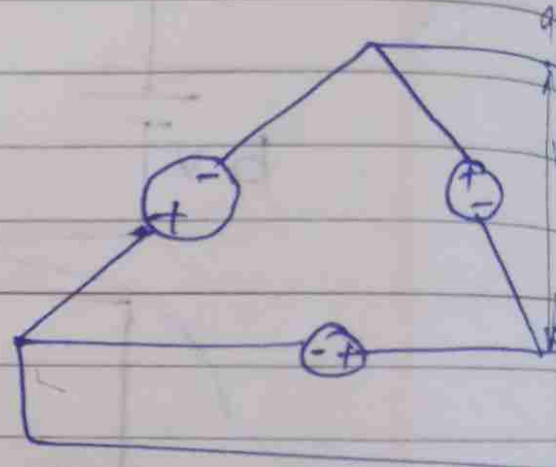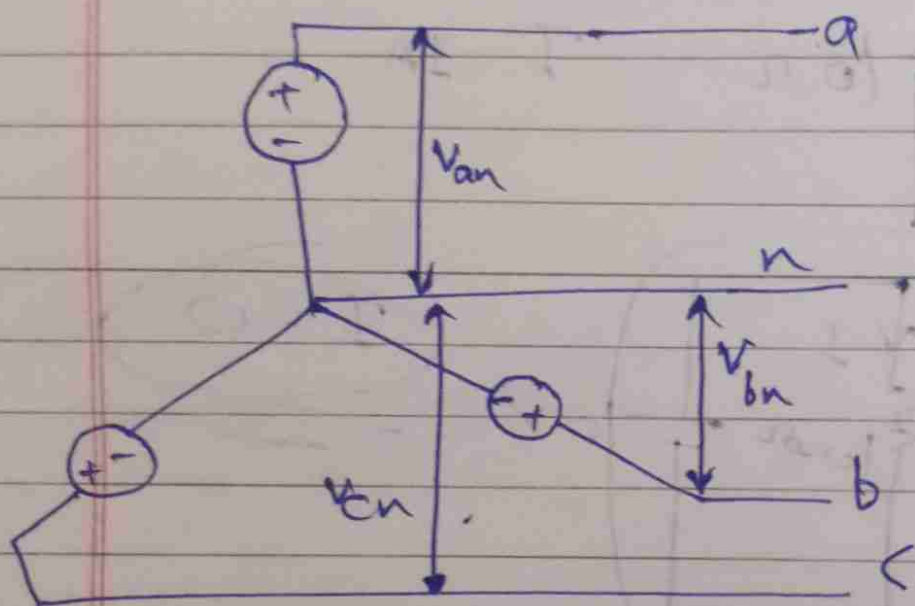
→ Three Sources Connected to load by three or four wires




Balanced System

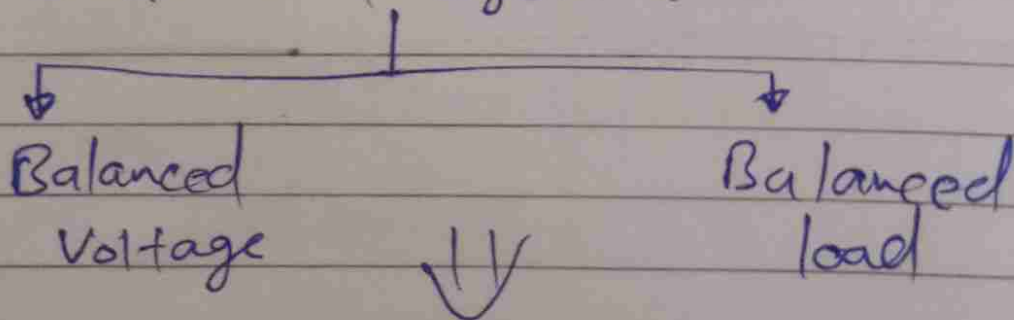

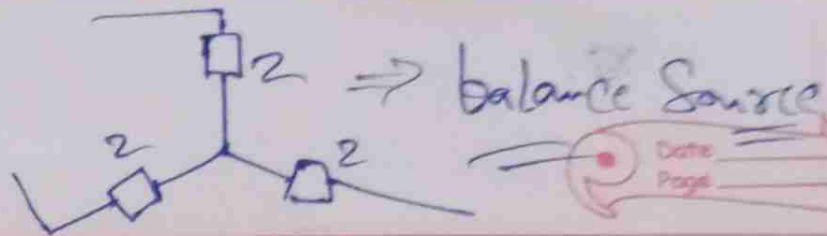amplitude & angular frequency are same
& 120° out of phase



Date _____
Page _____

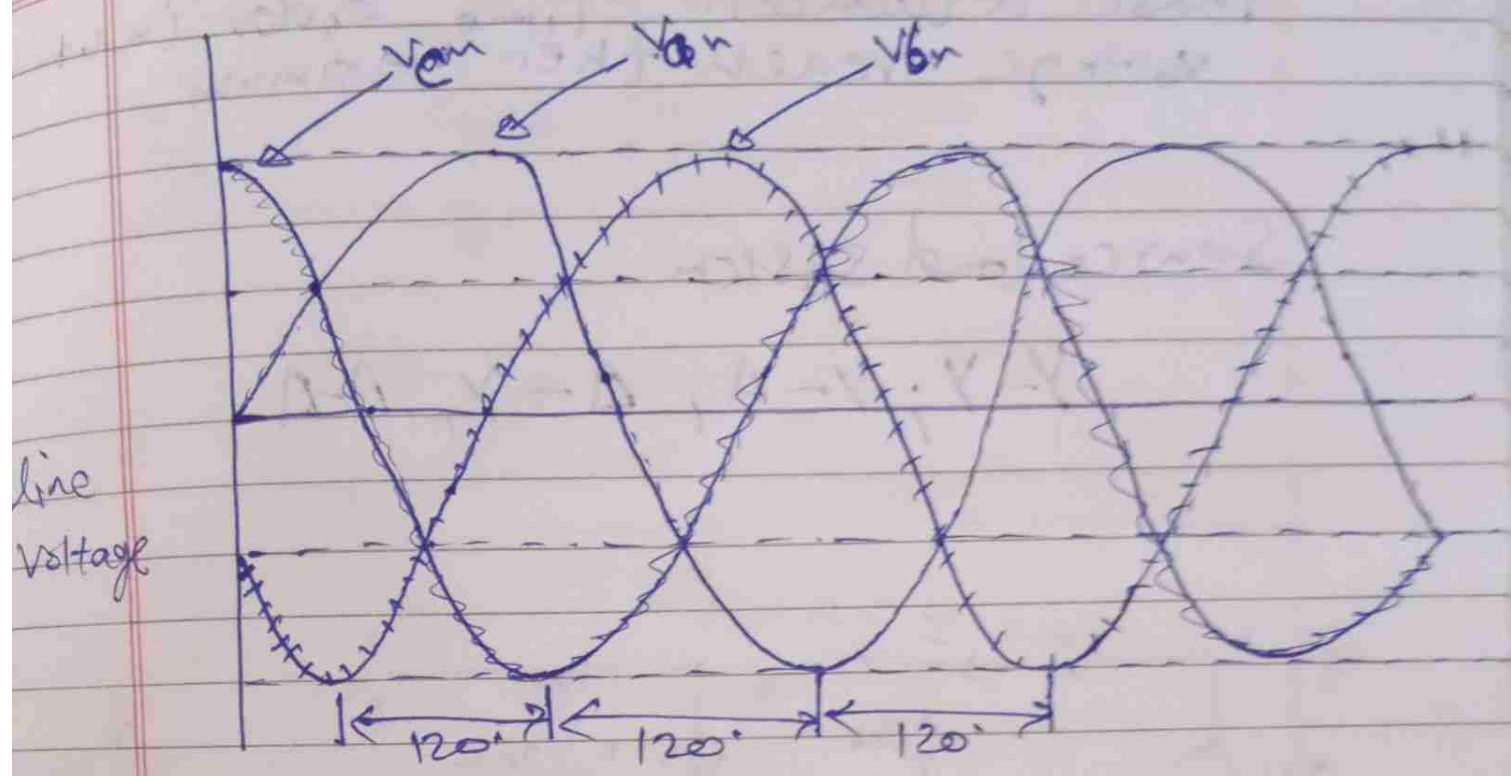


$$V_{an} = V \angle 0^\circ$$

$$V_{bn} = V \angle -120^\circ$$


$$V_{cn} = V \angle -240^\circ = V \angle 120^\circ$$

Phase sequence
abcabc...

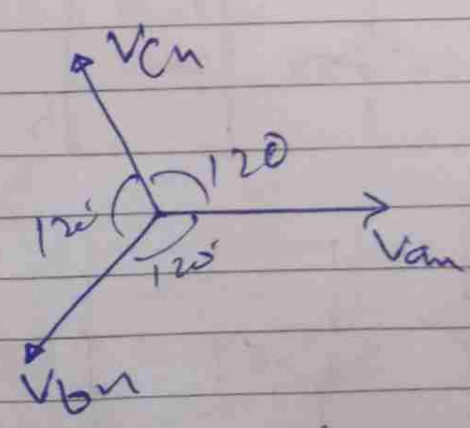

$$V_{an} + V_{bn} + V_{cn} = 0$$


for balance Source

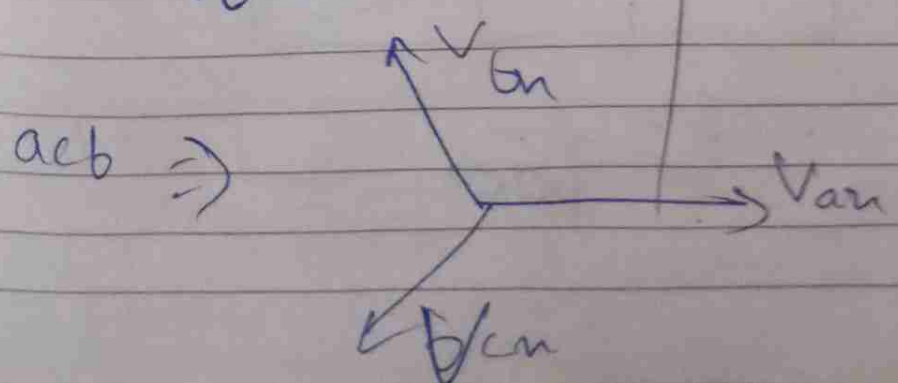



Phase Sequence - Time order in which voltage reach their maximum

Source load system

Y-Y, Y-A, A-Y, A-A

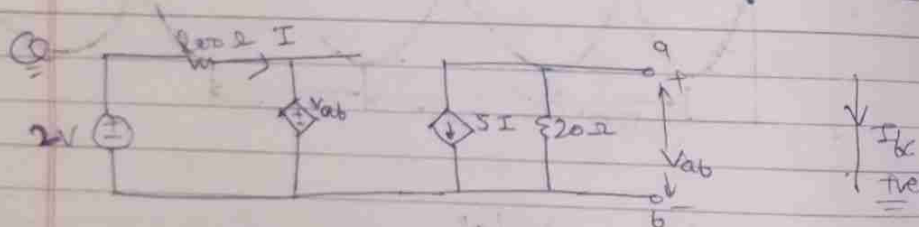



Current always choose low resistor path

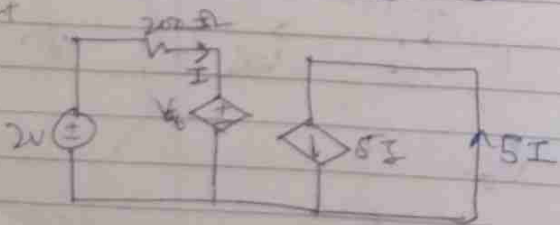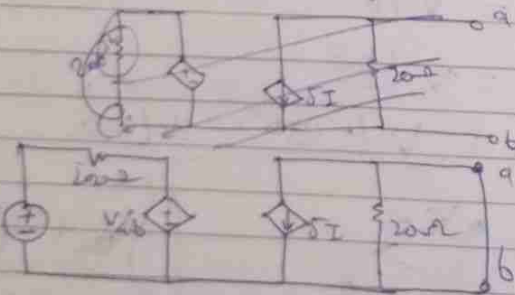

$$I = \frac{1}{100}$$

$$I_N = 5 \times I = \frac{5}{100} = \frac{1}{20}$$

In Norton Short circuit

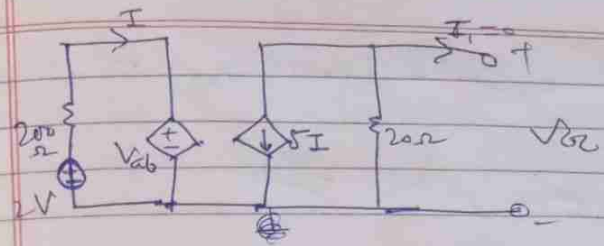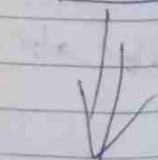

$$I_N = \frac{1}{20}$$



$$R_N = 40\Omega$$

$$V_{ab} = V_{oc} \Rightarrow 2 - 20I - V_{oc} = 0$$



$$V_{oc} = 2 - 20I$$

$$V_{oc} + 5I(20) = 0$$

$$V_{oc} = -2V$$

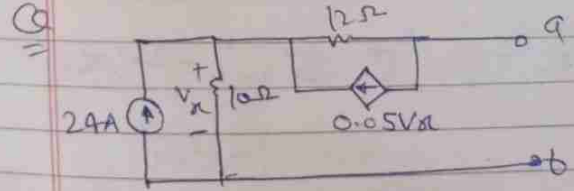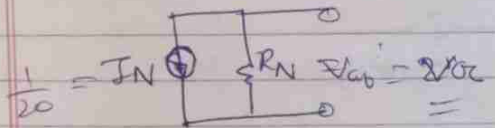

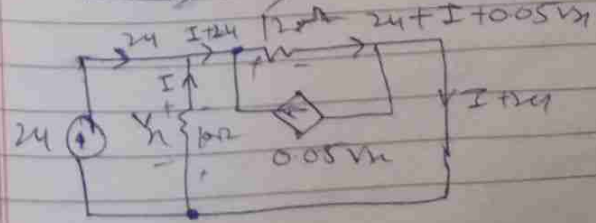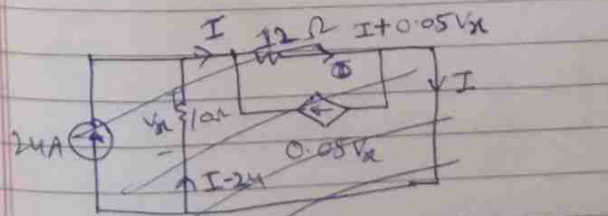Resistance -ve
 $\frac{24 \times 10}{24 + 10} = \frac{240}{34}$




$$+10I + 12(24 + I + 0.05V_1) = 0$$

$$V_1 = -I \cdot 10$$


$$24 + I_3 = I_1 + I_2$$
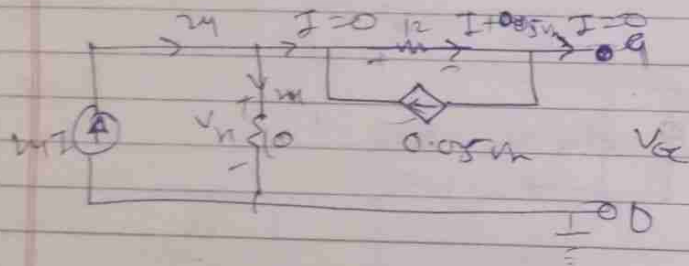
$$24 + 0.05V_1 = \frac{V_1}{12} + \frac{V_1}{10}$$




$$V_1 + 12(0.05V_1) - 24 \times 10 = 0$$

$$V_1 = 10 \times 24$$

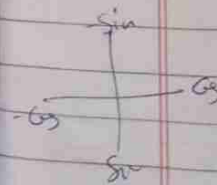

Transformer

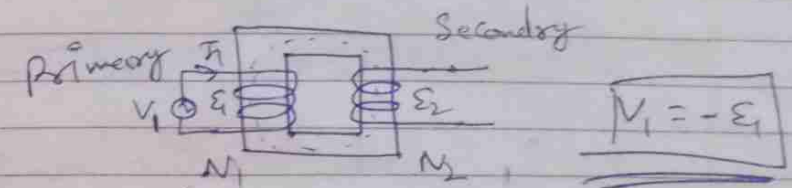→ It is a electrical who transfer electric electricity from one circuit to another circuit



$$\phi = \frac{Mmf}{R_L} = \frac{N_1 I}{R_L}$$

↓
Reluctance

if $N_1 > N_2$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$V_1 > V_2$$

Then
High voltage
Binding

Low Voltage
Binding

$$\phi = \phi_m \sin \omega t$$

$$\frac{d\phi}{dt} = \omega \phi_m \cos \omega t = \omega \phi_m \sin(\omega t - \frac{\pi}{2})$$

$$e = - \frac{d\phi}{dt}$$

$$e = - N_1 \frac{d\phi}{dt} = - \omega \phi_m N_1 \sin\left(\frac{\pi}{2} - \omega t\right)$$

$$e_1 = \omega \phi_m N_1 \sin\left(\omega t - \frac{\pi}{2}\right) \quad \text{--- (6)}$$

$$E_{\max} = 2\pi f \phi_m N_1$$

$$E_{\text{rms}} = \frac{E_{\max}}{\sqrt{2}} = \frac{2\pi f \phi_m N_1}{\sqrt{2}} = 4.44 f \phi_m N_1$$



$$E_{\text{rms}} = 4.44 f \phi_m N_2 \quad \text{--- (7)}$$

Transformation Ratio $K = \frac{N_2}{N_1}$


$$\frac{E_1}{N_1} = \frac{E_2}{N_2} \quad \text{--- (8)}$$

$$E_1 I_1 = E_2 I_2$$

⑧ & ⑦

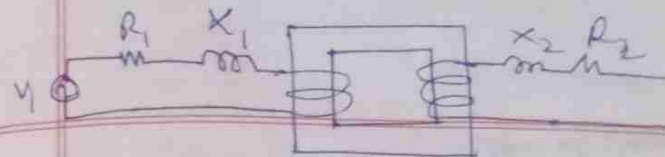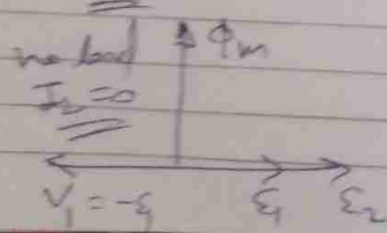


Equivalent Circuit

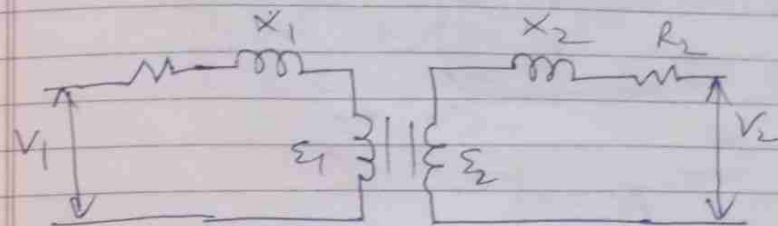

Add primary side refer

$R_0 = \text{eq. Resistance seen from primary side}$

$X_0 = \text{Inductance}$

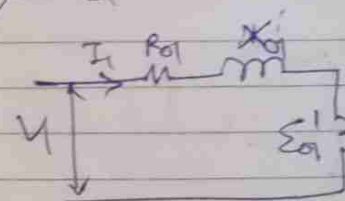

$$R_0 = R_1 + \left(\frac{N_1}{N_2}\right)^2 R_2 = R_1 + R'_1$$

$$X_0 = X_1 + \left(\frac{N_1}{N_2}\right)^2 X_2 = X_1 + X'_1$$


$$E'_1 = E_1 + \left(\frac{N_1}{N_2}\right) E_2$$

→ for secondary refer

$$R_{02} = R_2 + \left(\frac{N_2}{N_1}\right)^2 R_1 \quad E'_{02} = E_2 + \left(\frac{N_2}{N_1}\right) E_1$$


$$X_{02} = X_2 + \left(\frac{N_2}{N_1}\right)^2 X_1$$

Auto Transformer

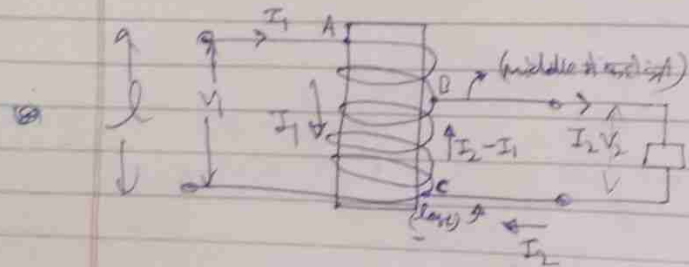

$$AC = N_1$$

$$BC = N_2$$

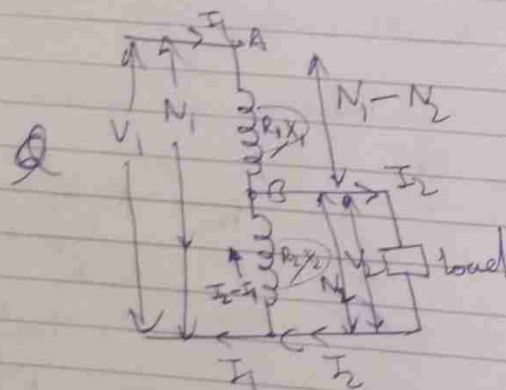

$$I_{CB} = I_2 - I_1$$

(P) In simple Transfr

$$\frac{E_1}{E_2} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

$$I_1 N_1 = I_2 N_2$$

Cu loss = $I^2 R$
Core loss $\rightarrow$ hysteresis loss $\rightarrow P_h = k_f f B_m$
eddy current loss $\rightarrow P_e = k_e f^2 B_m^2$

for Prove $I_1(N_1 - N_2) = (I_2 - I_1)N_2$

$$\begin{aligned} \text{mmf}_{AB} &= I_1(N_1 - N_2) = I_1 N_1 - I_1 N_2 \\ &= I_2 N_2 - I_1 N_2 \\ &= N_2(I_2 - I_1) \\ &= \text{mmf}_{CB} \end{aligned}$$

$$P = VI \cos \phi$$

$$P_1 = V_1 I_1 \cos \phi_1$$

$$P_2 = V_2 I_2 \cos \phi_2$$

No loss

$$V_1 I_1 = V_2 I_2$$

$\cos \phi_1 = 1$
 $\cos \phi_2 = 1$ } only Resistive load
2=1

$$\text{Wt.} = DX \text{ vol}$$

Wire same $\frac{h}{a}$ wire cross section area

$$V = AXl \rightarrow \text{wire length}$$

$$l \propto N \rightarrow \text{no of loops}$$

$$A \propto I \rightarrow \text{current (I=heavy)}$$


$$\text{Wt. of } AB \propto (N_1 - N_2) I$$




$$\text{Wt. of } BC \propto (I_2 - I_1) N$$

$$\text{Wt. of Auto} = 1 - K$$

$$\text{Wt. of Simple}$$

DC Motor Animation

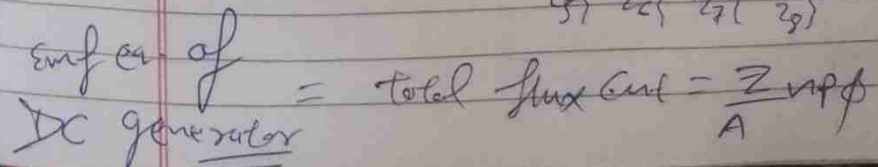

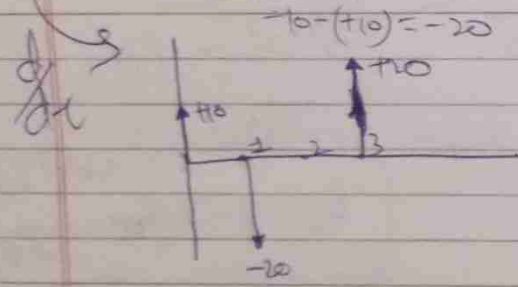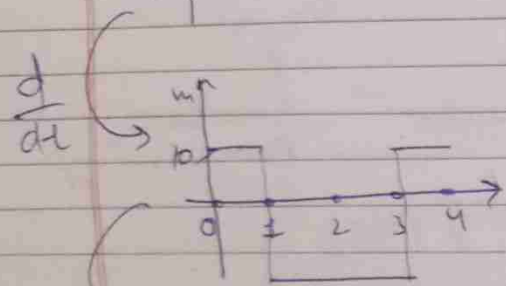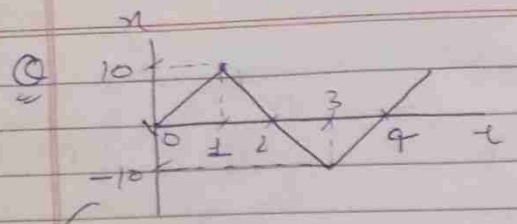


Impulse

given: impels
 find: step

soln :- Area at an Instant
 is equal to the change
 in step at that Instant

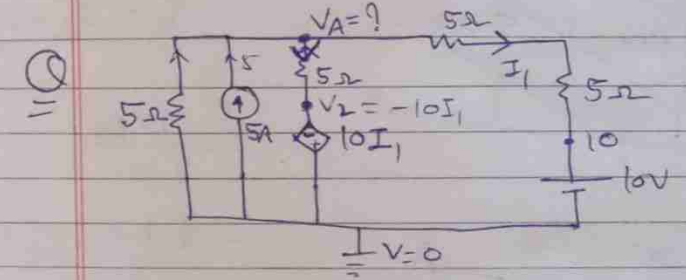Change in step at a instant
 is equal to the change in slope
 at that Particular Instant



$$\frac{-V_A}{5} + 5 + \frac{V_2}{5} = \frac{V_A}{5} = \frac{10 - V_A}{10}$$

$$\frac{V_2 - V_A}{5} = 10I_1$$



$$5 + I_1 = 3 + I_1$$

$$5 + \frac{-V_A}{5} = \frac{V_A + 10I_1}{5} + \frac{V_A - 10}{10}$$

$$V_A + 4I_1 = 10$$

$$V_A - 10I_1 - 10 = 0$$

$$V_A - 10I_1 = 10$$

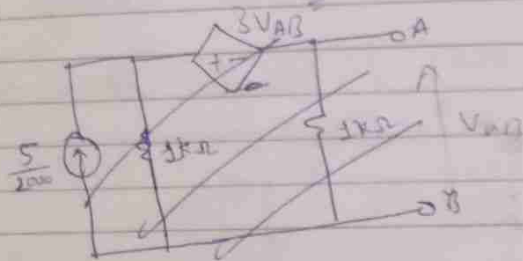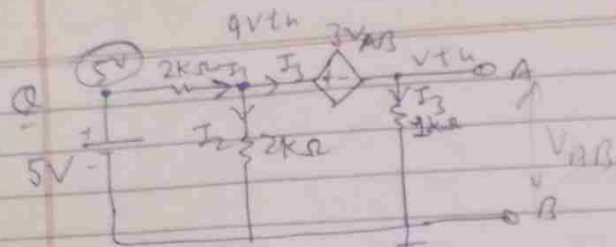

$$I_1 = I_2 + I_3$$

$$\frac{5 - 9V_{th}}{2k} = \frac{9V_{th}}{2k} + \frac{V_{th}}{1k}$$

$$V_{th} = \frac{1}{2}$$



$$\frac{5}{2} + 1000I + 3V_{AB} + 1000I = 0$$

$$V_{AB} = 1000I$$

$$\frac{5}{2} + \cancel{1000I} V_{AB} + 3V_{AB} + V_{AB} = 0$$


$$4V_{AB} = -\frac{5}{2}$$

$$V_{AB} = -\frac{5}{8}$$

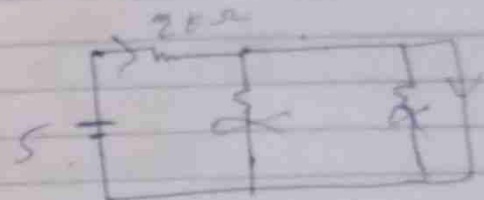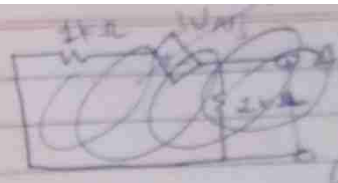

$$I_{AC} = \frac{5}{2k} = 2.5 \text{ mA}$$
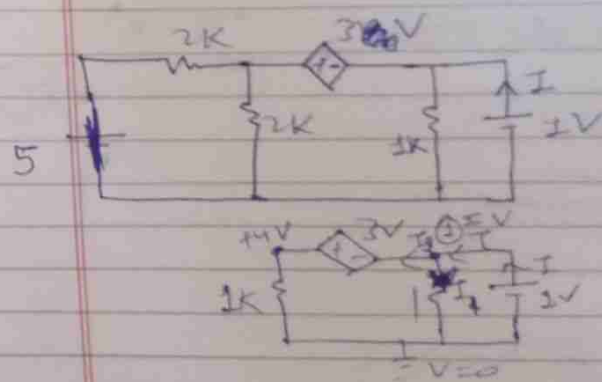
$$R_{th} = \frac{1}{\frac{1}{2k} + \frac{1}{3k}} = 1.2 \text{ k}\Omega$$




$$I = I_1 + I_2$$

$$I = \frac{1 - 0}{1k} + \frac{4}{1k}$$


$$I = \frac{1}{k} + \frac{4}{k} = \frac{5}{k} = \frac{5}{1000}$$

Balanced Three Phase System

→ Three loads

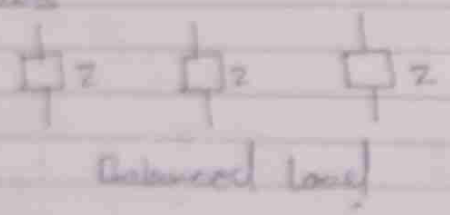


→ Phase Sequence

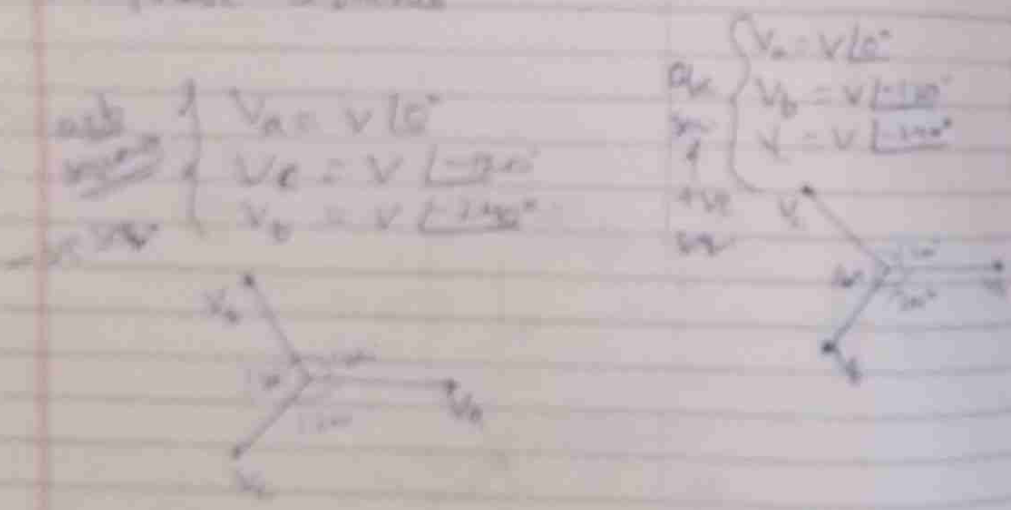

Source load System

① Y-Y Combination

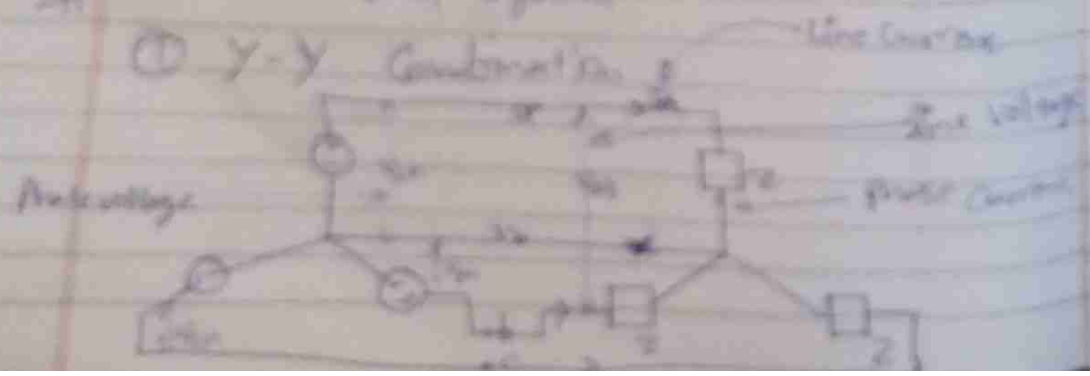

→ For Star Connected load Line Current = Phase Current

Let


$$\begin{aligned} V_{an} &= V \angle 0^\circ \\ V_{bn} &= V \angle -120^\circ \\ V_{cn} &= V \angle -240^\circ \end{aligned}$$

In ab

$$-V_{an} + V_{bn} + V_{ab} = 0$$


$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} \\ &= V \angle 0^\circ - V \angle -120^\circ \\ &= V (1 \angle 0^\circ - 1 \angle -120^\circ) \\ &= V (1 + j0 + 0.5 + j0.866) \\ &= V (1.5 + j0.866) \\ &= V (1.732 \angle 30^\circ) \\ &= \sqrt{3} V \angle 30^\circ \end{aligned}$$

$$V_{ab} = \sqrt{3} V \angle 30^\circ$$

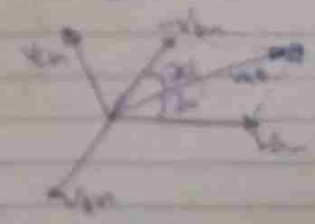

Balanced Three Phase System

→ Three loads

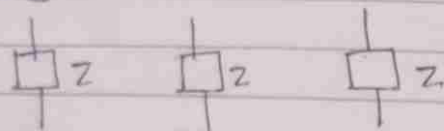


Balanced load

→ Phase Sequence

abc sequence


$$\begin{cases} V_a = V \angle 0^\circ \\ V_c = V \angle -120^\circ \\ V_b = V \angle -240^\circ \end{cases}$$

-ve seq.

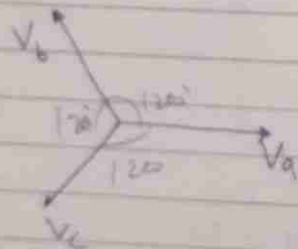


abc sequence +ve seq.
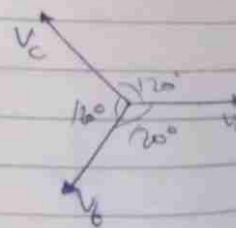
$$\begin{cases} V_a = V \angle 0^\circ \\ V_b = V \angle -120^\circ \\ V_c = V \angle -240^\circ \end{cases}$$



Source load System

① Y-Y Combination

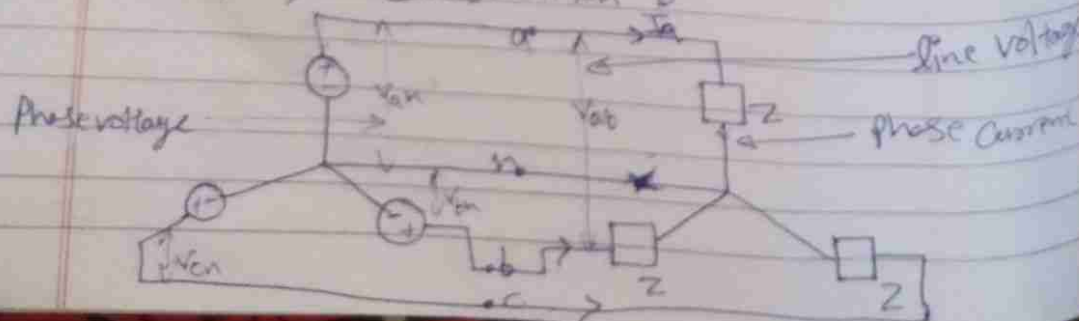

→ For star connected load line current = phase current

let


$$\begin{aligned} V_{an} &= V \angle 0^\circ \\ V_{bn} &= V \angle -120^\circ \\ V_{cn} &= V \angle -240^\circ \end{aligned}$$

$\sum_{ab} = 0$

$$-V_{an} + V_{bn} + V_{cb} = 0$$

$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} \\ &= V \angle 0^\circ - V \angle -120^\circ \\ &= V (\angle 0^\circ - \angle -120^\circ) \\ &= V (1 + j0 + 0.5 + j0.866) \\ &= V (1.5 + j0.866) \\ &= V (1.732 \angle 29.99^\circ) \\ &= V\sqrt{3} \angle 30^\circ \end{aligned}$$

$$V_{ab} = V\sqrt{3} \angle 30^\circ$$

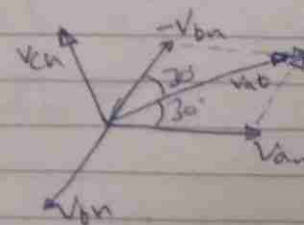

for bc

$$-V_{bn} + V_{cn} + V_{bc} = 0$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$= V \angle -120^\circ - V \angle -240^\circ$$

$$= V (1 \angle -120^\circ - 1 \angle -240^\circ)$$

$$= V (-0.5 - j0.866 + 0.5 + j0.866)$$

$$V_{bc} = V (-j1.732)$$

$$V_{bc} = \sqrt{3} V \angle -90^\circ$$

for ca

$$V_{ca} = V_{cn} - V_{an}$$

$$= V \angle -240^\circ - V \angle 0^\circ$$

$$= V (-1.5 + j0.866)$$

$$= \sqrt{3} V \angle 150^\circ$$

$$= \sqrt{3} V \angle -210^\circ$$

$$I_a = \frac{V_{an}}{Z} = \frac{V}{Z} \angle 0^\circ$$

$$I_a = I \angle 0^\circ$$

$$I_b = I \angle -120^\circ$$

$$I_c = I \angle -240^\circ$$

$$I_n = I_a + I_b + I_c$$

$$= I (1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle -240^\circ)$$


$$= I (1 + 0j + (-0.5 - j0.866) + (-0.5 + j0.866))$$

$$I_n = 0$$

Same potential

In balanced system $I_n = 0$

Q

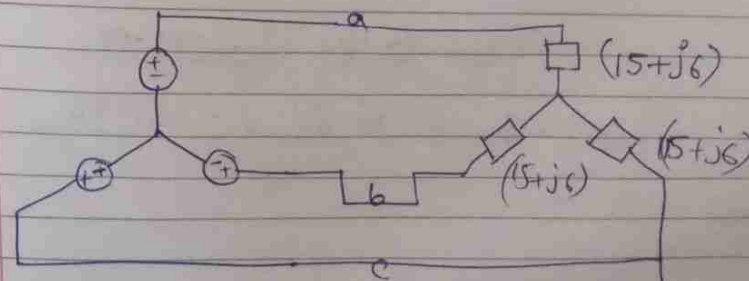

Given for the circuit phase seq abc find line voltage & line current. $V_{an} = 110 \angle 0^\circ$

Given $V_{an} = V \angle 0^\circ$

$$\left. \begin{aligned} V_{an} &= V \angle 120^\circ \\ V_{cn} &= V \angle -240^\circ \end{aligned} \right\} \text{ because system is balanced}$$

$V_{ab} = V_{an} - V_{bn}$

$= \sqrt{3} \cdot V \angle 30^\circ$

$V_{bc} = \sqrt{3} V \angle -90^\circ$

$V_{ca} = \sqrt{3} V \angle -210^\circ = \sqrt{3} V \angle 150^\circ$

$$I_a = \frac{V \angle 0^\circ}{Z} = \frac{V \angle 0^\circ}{15 + j6} = \frac{V \angle 0^\circ}{16.15 \angle 21.8^\circ}$$

$V(0.0619) \angle -21.8^\circ$

$$V = 110 \quad V(0.0574 - j0.02233)$$

$I_a = 6.81 \angle -21.8^\circ$


$I_b = 6.81 \angle -141.86^\circ$

$I_c = 6.81 \angle -261.86^\circ$

$$W_1 - W_2 = W_1^0 + 2^L W_{Cu}$$

$\uparrow$ Iron loss $\uparrow$ Copper loss

~~9~~ Δ Combination

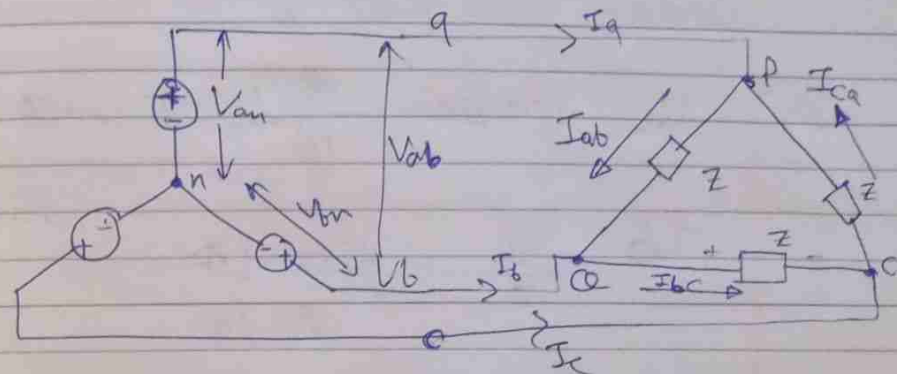

$V_{ab} = V \angle 0^\circ$

$V_{bc} = V \angle -120^\circ$

$V_{ca} = V \angle -240^\circ = V \angle 120^\circ$

$$I_{ab} = \frac{V_{ab}}{Z} = \frac{V \angle 0^\circ}{Z} = I \angle 0^\circ$$

$$I_{bc} = \frac{V \angle -120^\circ}{Z} = I \angle -120^\circ$$

$$I_{ca} = \frac{V \angle 120^\circ}{Z} = I \angle 240^\circ$$

at P
 $I_a = I_{ab} - I_{ca}$

$= I(1 \angle 0^\circ - 1 \angle -240^\circ)$

$= I(1 + j0 + 0.5 + j0.866)$

$= I(1.5 + j0.866)$

$= \sqrt{3} I \angle -30^\circ$

at Q

$I_b = I_{bc} - I_{ab}$

$= I(1 \angle -120^\circ - 1 \angle 0^\circ)$

$= \sqrt{3} I \angle -150^\circ$

$I_c = \sqrt{3} I \angle 270^\circ$

$= \sqrt{3} I \angle 90^\circ$

- Q A balanced abc sequence Δ -Connected source with $V_{an} = 100 \angle 10^\circ$ V is connected to Δ Connected balanced load $Z = 8 + j9 \Omega$. Calculate the phase & line current.

Soln

$$V_{an} = 100 \angle 10^\circ$$

$$V_{ab} = \sqrt{3} 100 \angle 40^\circ$$

$$I_{ab} = \frac{V_{ab}}{Z} = \frac{\sqrt{3} 100 \angle 40^\circ}{8 + j9}$$

$$= \frac{\sqrt{3} 100 \angle 40^\circ}{8.944 \angle 26.57^\circ}$$

$$= 19.3649 \angle 13.43^\circ \text{ A}$$

$$I_{bc} = 19.3649 \angle -106.57^\circ$$

$$I_{ca} = 19.3649 \angle -226.57^\circ$$


$$I_a = \sqrt{3} \times 19.3649 \angle [13.43 - 30^\circ]$$

$$= 33.53 \angle -16.57^\circ$$

abc $\rightarrow$ +ve Seq.

aeb $\rightarrow$ -ve Seq.

- Q Δ -Y Connected system

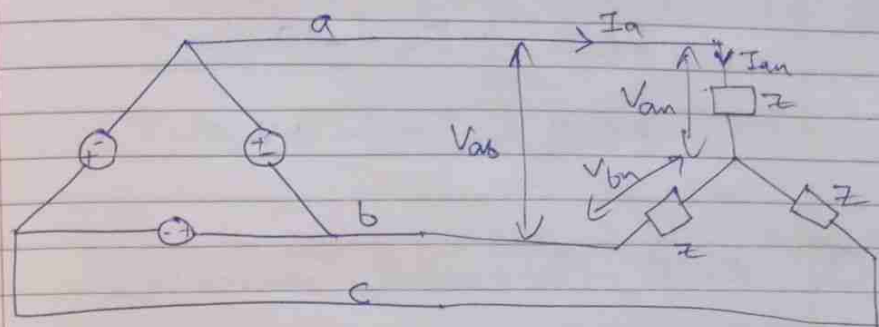

$$V_{ab} = V \angle 0^\circ \text{ then } V_{an} = \frac{V}{\sqrt{3}} \angle -30^\circ$$

$$I_a = I_{an} = \frac{V_{an}}{Z}$$

- Q A balanced Δ -Connected load having an impedance of $(40 + j25) \Omega$ per phase is applied by balanced, positive sequence Δ Connected source with line voltage of 210 V. Calculate phase current.

Soln

$$Z = 40 + j25 \Omega$$

$$V_{ab} = 210 \angle 0^\circ$$

$$V_{bc} = 210 \angle -120^\circ$$

$$V_{ca} = 210 \angle 120^\circ$$

$$V_{an} = \frac{210}{\sqrt{3}} \angle -30^\circ$$

$$I_a = \frac{210 \angle -30^\circ}{\sqrt{3} \times (40 + j25)}$$


$$= \frac{210 \angle -30^\circ}{\sqrt{3} \times 47.16 \angle 32.01^\circ}$$

$$I_a = 2.56 \angle 62.005^\circ$$

$$I_b = 2.56 \angle -182.005^\circ$$

$$I_c = 2.56 \angle -302.005^\circ$$

Q) A-A Connected Source:-

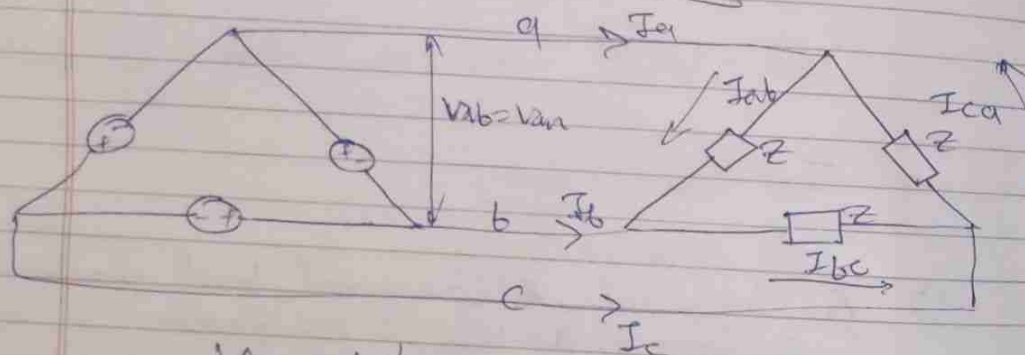

$$V_{ab} = V \angle 0^\circ$$

$$\begin{cases} I_a = \sqrt{3} I \angle -30^\circ \\ I_b = I \angle 0^\circ \end{cases}$$

Q) a balanced Δ connected load with phase impedance of $20 - j15 \Omega$ is connected to a Δ connected +ve sequence generator having calculate the phase current of load & line current.

R Y B, P L R B Y

$V_{ab} - V_{ay} \quad V_{bn}, V_{yn}, V_{bn}$

Soln

$$Z = 20 - j15$$

$$V_{ab} = 330 \angle 0^\circ$$

$$V_a = \frac{330}{\sqrt{3}} \angle 0^\circ$$

$$I_{ab} = \frac{330 \angle 0^\circ}{25 \angle (20 - j15)}$$

$$= \frac{33 \angle 0^\circ}{25}$$

$$I_{ab} = 13.2 \angle 36.86^\circ \text{ A}$$

$$I_{bc} = 13.2 \angle -83.14^\circ$$

$$I_{ca} = 13.2 \angle -203.15^\circ$$


Power in Balanced 3 ϕ system

$$\text{rms value} = \underline{V_p}$$

$$V_{an} = \sqrt{2} V_p \cos(\omega t)$$

$$V_{bn} = \sqrt{2} V_p \cos(\omega t - 120^\circ)$$
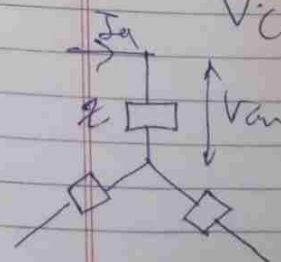
$$V_{cn} = \sqrt{2} V_p \cos(\omega t - 240^\circ)$$



$$I_a = \sqrt{3} I_p \cos(\omega t - \theta)$$

$$I_b = \sqrt{3} I_p \cos(\omega t - \theta - 120^\circ)$$

$$I_c = \sqrt{3} I_p \cos(\omega t - \theta + 120^\circ)$$

$$P = P_1 + P_2 + P_3$$

$$P_1 = \sqrt{2} V_p \times \sqrt{2} I_p (\cos \omega t) \times (\cos \omega t - 0)$$

$$P = 2 V_p I_p \left\{ \cos(\omega t) \cos(\omega t - 0) + \cos(\omega t - 120^\circ) \right. \\ \left. + \cos(\omega t + 120^\circ) \cos(\omega t + 120^\circ - 0) \right\}$$

$$P = 2 V_p I_p \left\{ \cos^2 \theta + \cos(2\omega t - 0) \right. \\ \left. + \cos \theta + \cos(2\omega t - 240^\circ - 0) \right. \\ \left. + \cos \theta + \cos(2\omega t + 240^\circ - 0) \right\}$$


if $\alpha = 2\omega t - 0$

$$P = V_p I_p (3 \cos \alpha + \cos \alpha + \cos(\alpha - 240^\circ) + \cos(\alpha + 240^\circ))$$

$$P = V_p I_p (3 \cos \alpha + \cos \alpha + 2 \cos \alpha \cdot \cos 120^\circ)$$


$$P = 3 V_p I_p \cos \theta$$

Combination	V_{an}	V_{bn}	V_{cn}	V_{an}	V_{bn}	V_{cn}	I_a	I_b	I_c
$Y-Y$	$\frac{V}{\sqrt{3}}$	$\frac{V}{\sqrt{3}} \angle -120^\circ$	$\frac{V}{\sqrt{3}} \angle -240^\circ$	$\frac{V}{\sqrt{3}} \angle 0^\circ$	$\frac{V}{\sqrt{3}} \angle -120^\circ$	$\frac{V}{\sqrt{3}} \angle -240^\circ$	I_L	I_L	I_L
$Y-\Delta$	$\frac{V}{\sqrt{3}} \angle -30^\circ$	$\frac{V}{\sqrt{3}} \angle -150^\circ$	$\frac{V}{\sqrt{3}} \angle -270^\circ$	$V \angle 0^\circ$	$V \angle -120^\circ$	$V \angle -240^\circ$	I_L	I_L	I_L
$\Delta-Y$	$\frac{V}{\sqrt{3}} \angle -30^\circ$	$\frac{V}{\sqrt{3}} \angle -150^\circ$	$\frac{V}{\sqrt{3}} \angle -270^\circ$	$V \angle 0^\circ$	$V \angle -120^\circ$	$V \angle -240^\circ$	I_L	I_L	I_L
$\Delta-\Delta$	$V \angle 0^\circ$	$V \angle -120^\circ$	$V \angle -240^\circ$	V_{an}	V_{bn}	V_{cn}	I_L	I_L	I_L


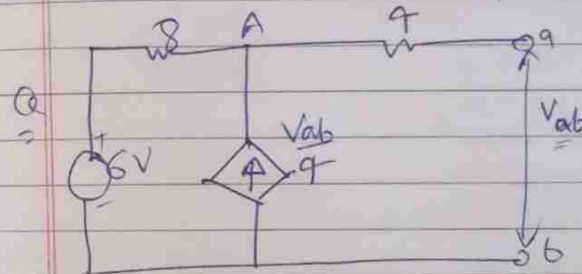


Thevenin eq.
Circuit

(ii) Resistance effect

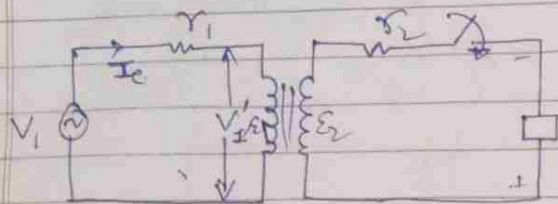

(iii) Leakage flux (ϕ_l)

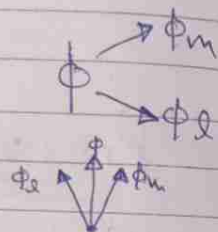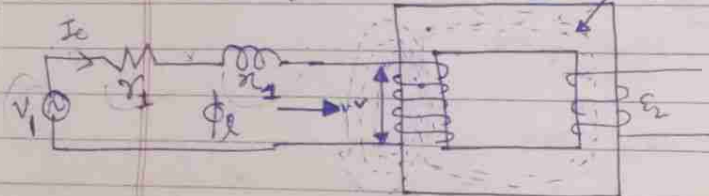

$E_2 \Rightarrow \phi_l$ at generated emf.

$$E_2 = -j I_e x_1$$


Fictitious Reactance

$$V_1 = V_1' + I_e r_1 + j I_e x_1$$


$$= V_1' + I_e (r_1 + j x_1)$$

$$= E_1 + I_e (r_1 + j x_1)$$


~~The~~ Electrical
Equivalent Circuit

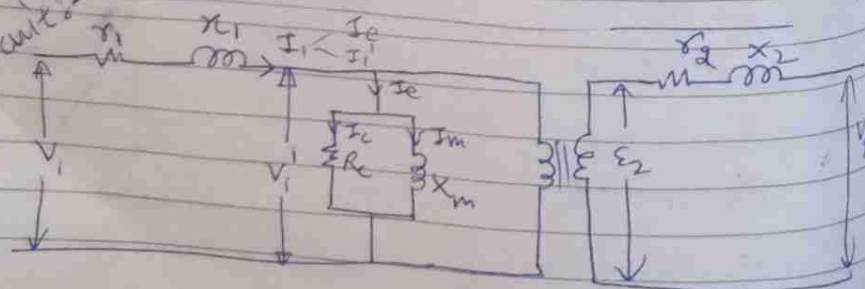

phagor diagram. Practical T/F at load

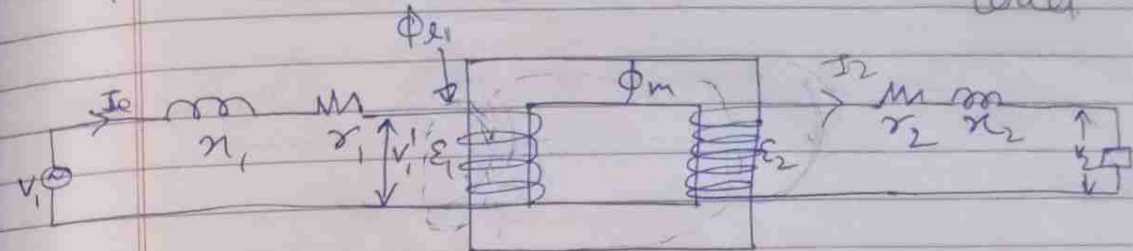

$r_1 r_2 = \text{winding resistance}$

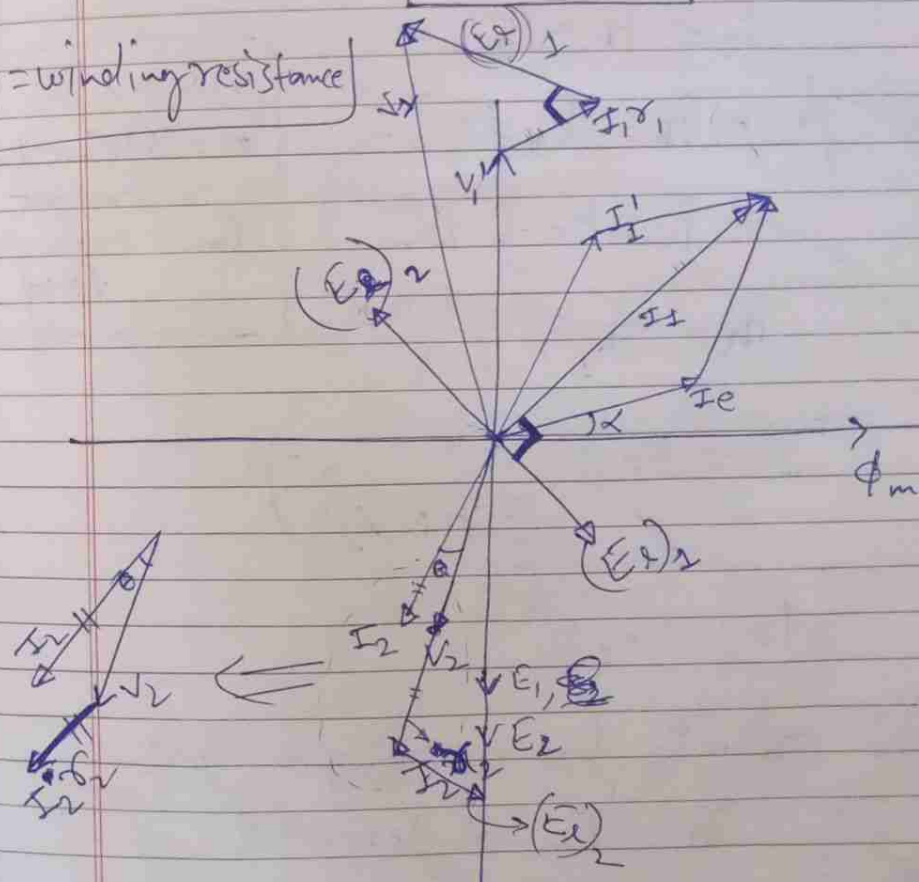

$$E_2 = V_2 + I_2 (r_2 + j x_2)$$

Below

$$\rightarrow \phi_m = B_m A$$

$$V_1 \approx E_1 = \sqrt{2} \pi f N_1 \phi_m \Rightarrow B_m = \frac{V_1}{\sqrt{2} \pi f N_1 A}$$

Losses of Transformer

(Constant loss) 1. Hysteresis & Eddy Current loss
Core loss

$$P_c = P_h + P_e$$

$$K_h f \cdot \frac{V_1}{\sqrt{2} \pi f N_1 A}^n = P_h = K_h f B_m^n$$

$$P_e = K_e f^2 B_m^2$$

$$P_h = K_{h1} V_1^n f^{1-n}$$

$$P_e = K_e f^2 \frac{V_1^2}{(\sqrt{2} \pi f N_1 A)^2} \times \frac{1}{f}$$

$$P_c = K_{c1} V_1^2$$

$n \approx 1.2$
 n = Steinmetz Constant
 B_m = magnetic field

(Variable loss) 2. Ohmic loss or Copper loss.
 r_1, r_2 are generated

$$P_{cu} = P_w = I_1^2 r_1 + I_2^2 r_2$$

$$= I_1^2 r_1 = I_2^2 r_2$$

$$= I_1^2 r_1 + I_1^2 \left(\frac{N_1}{N_2} \right)^2 r_2$$

$$= I_1^2 \left(r_1 + \left(\frac{N_1}{N_2} \right)^2 r_2 \right)$$

$$= I_1^2 r_{e1}$$

$\because \frac{I_2}{I_1} = \frac{N_1}{N_2}$

3) Stray loss

4) Dielectric loss

Efficiency of Transformer

$$\eta = \frac{\text{Output Power}}{\text{Input Power}}$$

$$\eta = \frac{V_2 I_2 \cos \theta_2}{V_2 I_2 \cos \theta_2 + P_c + P_w}$$

$$\eta = \frac{V_2 I_2 \cos \theta_2}{V_2 I_2 \cos \theta_2 + P_c + I_2^2 r_{e2}}$$

$\Rightarrow$ Condition for maximum efficiency

$$\frac{d\eta}{dI_2} = \frac{(V_2 I_2 \cos \theta_2 + P_c + I_2^2 r_{e2}) V_2 \cos \theta_2 - (V_2 I_2 \cos \theta_2) (V_2 \cos \theta_2 + 2 I_2 r_{e2})}{(V_2 I_2 \cos \theta_2 + P_c + I_2^2 r_{e2})^2}$$

$$\frac{d\eta}{dI_2} = 0$$

$$V_1 I_2 G_{S0} + R_2 I_2^2 r_{e2} = V_1 I_2 G_{S0} + 2 I_2^2 r_{e2}$$

$$P_c = I_2^2 r_{e2}$$

$$\text{if } P_c = P_w$$

then maximum efficiency of trans.

$$I_2 = \sqrt{\frac{P_c}{r_{e2}}}$$

$$I_2 = I_{fl} \sqrt{\frac{P_c}{I_{fl}^2 r_{e2}}}$$

In lab
2 KVA, 230V, 1:1
 $I_{fl} = \frac{2000}{230} = 8.69$

$$= I_{fl} \sqrt{\frac{P_c}{P_{\text{full load copper loss}}}}$$

$$I_{fl} = \frac{\text{Rated KVA}}{V_2}$$

$$\eta = \frac{P_{\text{actual}}}{P_{\text{fl}}} = \frac{I_2}{I_{fl}}$$

if $\eta = \frac{1}{2}$ then eff. $\eta = \frac{1}{2}$


$$\eta = \frac{\eta_{\text{Rated KVA}} \times G_{S0}}{\eta_{\text{Rated KVA}} G_{S0} + P_c + \eta^2 P_{wc}}$$

$$P_w = I_{\text{Actual}}^2 r_{e2}$$


$$P_{wc} = I_{fl}^2 r_{e2}$$

full load copper loss
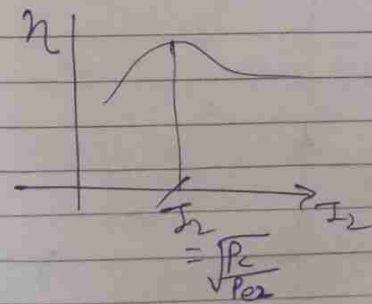
$$\frac{P_w}{P_{wc}} = \left(\frac{I_{\text{Actual}}}{I_{fl}} \right)^2 = \eta^2$$



Practical Lab

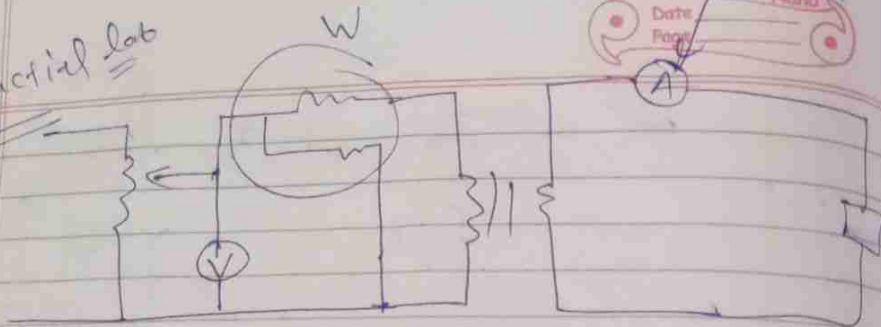

Date _____
Page _____


$I_{fl} = 8.69$

$\eta = \frac{I_{actual}}{I_{fl}}$

$W_1 = P_{iron} + \eta^2 P_w$

$W_2 = P_{iron} + \eta^2 P_w$


Phasor diagram of practical transformer

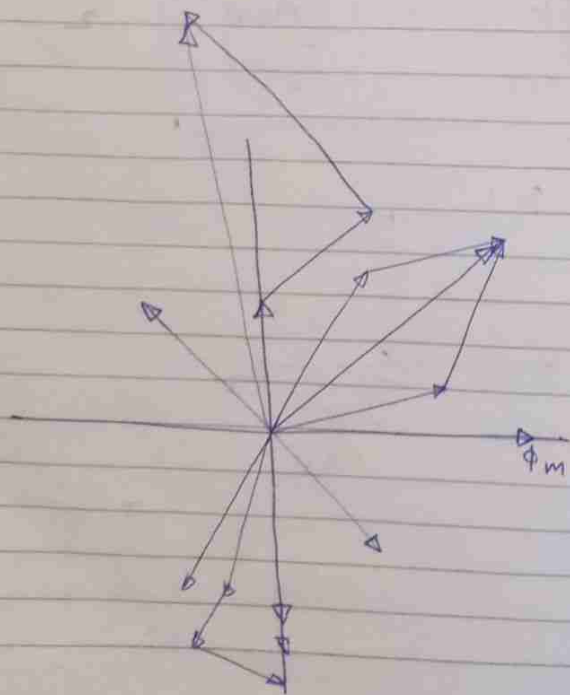

Test:

- ① open ckt test
- ② short ckt test

① open ckt test

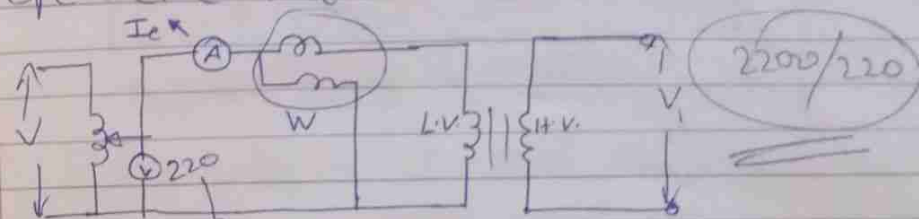

rated voltage applied on low voltage

$I_e = 2 \text{ to } 5\% \text{ of Full Load Current } (I_{fl})$

→ Watt meter reading giving only core loss b/c I_e is very less then Cu loss is neglect.

$W = V_1' I_e \cos \theta_1$

$R_c = \frac{V_1'}{I_e} = \frac{V_1'}{I_e \cos \theta_1}$

$X_m = \frac{V_1'}{I_m} = \frac{V_1'}{I_e \sin \theta_1}$

when I_e is very less then in ckt then

$V_1 = E_1 + I_e R_c \cos \theta_1$

→ neglected

if $I_e \ll I_{fl}$

then

$V_1 \approx E_1$

→


Core loss is only

→

T/F show only CORE LOSS

② Short CKT test

4KVA, 2200/220

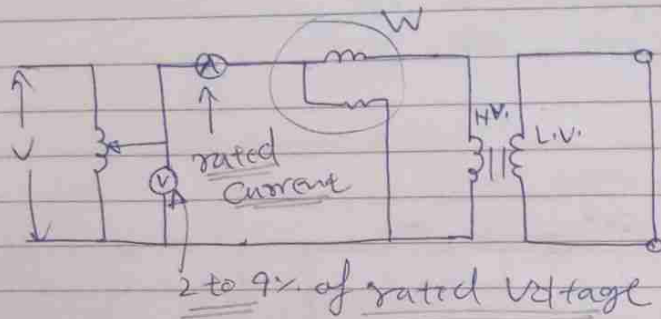

Core loss is neglected

Cu loss

When I current flows in ckt

$$V = E_1 + I(r_{1e})$$

$$P_c = P_h - P_e$$

$$P_h = K_h V^2 f^{-n}$$

$$P_e = K_e V^2$$

$V \propto$

then P_h & P_e is neglected

$$W = I^2 R_{eq}$$

$$R_{eq} = r_1 + r_2'$$

$$r_2' = R_2 + \left(\frac{N_2}{N_1}\right)^2 R_1$$

$$R_{eqH} = \frac{W}{I^2}$$

$$Z_{eqH} = \frac{V_{sc}}{I}$$

$$X_{eqH} = \sqrt{Z_{eqH}^2 - R_{eqH}^2}$$

then T/F show

only Cu loss (from resistance & Inductance)

- ③ The emf per turn for a single phase 2310/220V, 50Hz transformer is approximately 13 volts/turn. Calculate
- the number of primary & secondary turns
 - net gross sectional area of the core for a max. flux density of 1.47T

Soln Ideal trans (b/c no react.)

$$E_1 = V_1$$

$$E_2 = V_2$$

$$E_1 = \sqrt{2} \pi f N_1 \Phi_m$$

$$\frac{E_1}{N_1} = \text{emf/turns}$$

$$\frac{E_1}{N_1} = 13 = \frac{2310}{N_1} \Rightarrow N_1 = 178.5$$

$$\frac{E_2}{N_2} = 13 = \frac{220}{N_2} \Rightarrow N_2 = 16.9230$$

$$N_2 \approx 17 \text{ turns}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{2310}{220} = \frac{N_1}{17} \Rightarrow 178.5 = N_1$$

$$N_2 \approx 17 \Rightarrow \text{inc. } \textcircled{18}$$

$$\frac{2310}{220} = \frac{N_1}{18} \Rightarrow \boxed{N_1 = 189}$$

$$\phi_m = B_m \times A$$

$$E_1 = \sqrt{2} \pi N_1 f \phi_m$$

$$E_1 = \sqrt{2} \pi N_1 f B_m A$$

$$2310 = \sqrt{2} \pi \times 183 \times 50 \times 1.47 \times A$$

$$A = 0.037428115 \text{ m}^2$$

rated voltage

① A 10KVA 2500/250V, Single phase T/F gave the following test result open CKT test 250V, 0.8A, 50W
Short CKT test 60V, 3A, 45W

- ② Calculate the efficiency at $\frac{1}{4}$ FL at 0.8 p.f.
③ Calculate the load kVA at which max. efficiency occurs.

Soln $P_{\text{core loss}} = 50 \text{ W}$, $P_{\text{copper}} = 45 \text{ W}$

$$\eta = \frac{x \times \text{Rated KVA} \times \text{pf}}{x \times \text{Rated KVA} \times \text{pf} + P_{\text{core}} + x^2 W_c}$$

We will check P_{copper} is real

$$I_{fl} = \frac{10,000}{2500} = 4 \text{ A}$$

$$\frac{I_{\text{actual}}^2 R_{eq}}{I_{fl}^2 R_{eq}} = \frac{W_{\text{actual}}}{W_{\text{copper}}}$$

$I_{\text{actual}} = 3 \text{ A}$ $I_{fl} = 4 \text{ A}$

$$W_{\text{copper}} = \left(\frac{I_{fl}}{I_{\text{actual}}} \right)^2 \times W_{\text{actual}}$$

$$= \left(\frac{4}{3} \right)^2 \times 45$$

$$= 80 \text{ W}$$

$$\eta = \frac{\frac{1}{4} \times 10,000 \times 0.8}{\frac{1}{4} \times 10,000 \times 0.8 + 50 + \left(\frac{1}{4} \right)^2 \times 80}$$

$$I_2 = \sqrt{\frac{P_c}{R_{eq}}} \quad (P_c = I^2 R_{eq})$$

$$I_2 = I_{fl} \sqrt{\frac{P_c}{I_{fl}^2 R_{eq}}} = I_{fl} \sqrt{\frac{P_c}{W_c}}$$

Full load Cu

Rated 5 VA


$$E_2 \times I_2 \times 1000 = E_2 \cdot I_2 \times 1000 \sqrt{\frac{P_c}{W_c}}$$

$$= 10 \times 1000 \sqrt{\frac{50}{80}}$$

$$\text{Max. } \underline{V \cdot A} = 7905.69 \text{ V} \cdot \text{A}$$

$$\text{max. } \eta = \frac{7905}{2500} = 3.162$$

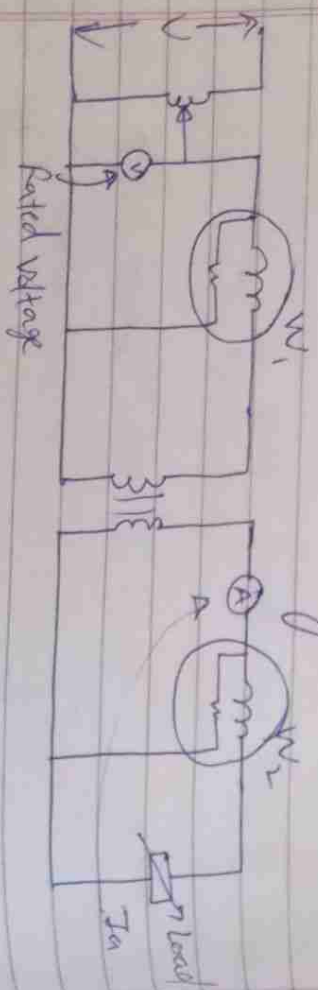Determining the losses in a T/F using direct loading:-



$$I_{\text{rated}} = I_{\text{full}} = \frac{2000}{230} \left\{ \begin{array}{l} 25 \text{ VA} \\ 230 \text{ V} \\ \text{T/F} \end{array} \right.$$

$$\rightarrow W_1 - W_2 = P_c + x W_c$$

$$\eta = \frac{\text{Actual}}{\text{Rated}}$$

→ Predetermine η at $\pm FL$, $\pm FL$, 1.25 FL at 0.8 pf lagging

$$\rightarrow \eta = \frac{x \cdot \text{Rated } \text{VA} \times \text{load} \times \text{pf}}{x \cdot \text{Rated } \text{VA} \times \text{load} \times \text{pf} + P_c + x W_c}$$

find hysteresis loss and eddy current loss
 $P_c = P_h + P_e$ Experimentally

Separation of Core losses

$$P_h = K_h f B_m^2$$


$$P_e = K_e f^2 B_m^2$$

$$P_c = K_h f B_m^2 + K_e f^2 B_m^2 = K_1 f + K_2 f^2$$

$$P_{\text{core}} = \sqrt{2} \pi N f \Phi_m \sin \alpha$$

$$\frac{P_c}{f} = K_1 + K_2 f$$

in open ckt.

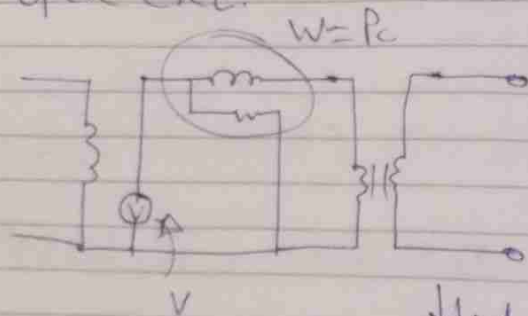


↓ determine reading.

P_{c1}	P_{c2}
f_1	f_2

$$\begin{cases} P_{c1} = k_1 f_1 + k_2 f_1^2 \\ P_{c2} = k_1 f_2 + k_2 f_2^2 \end{cases}$$

Solve find

k_1 & k_2

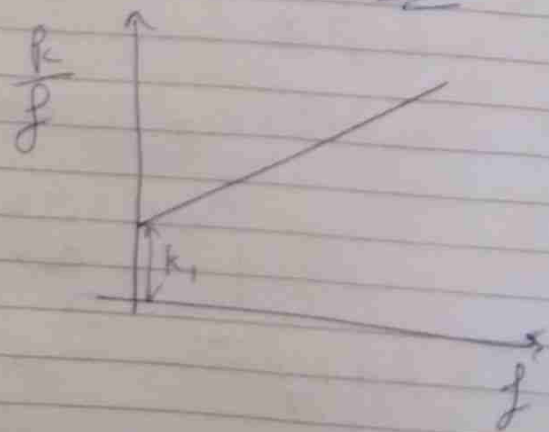

Q In a transformer the core loss is 100 W at 40 Hz and 72 W at 30 Hz. Find the hysteresis and eddy current losses at 50 Hz. Assume V/f was constant.

Soln

$$\frac{P_c}{f} = k_1 + k_2 f$$

$$\frac{100}{40} = k_1 + k_2 (40)$$

$$\frac{72}{30} = k_1 + k_2 (30)$$

$$\left(\frac{100}{40} - \frac{72}{30} \right) = k_2 \Rightarrow \frac{2.5 - 2.4}{10}$$

$$= \frac{0.1}{10}$$

$$= 0.01 = k_2$$

$$k_1 = 2.1$$

$$P_h = k_1 \times f$$

$$P_h = 2.1 \times 50$$

$$P_e = k_2 f^2$$




$$= 0.01 \times 50 \times 50$$

$$= 25$$

Construction of Transformer

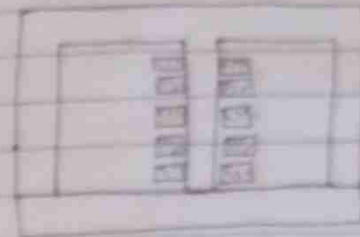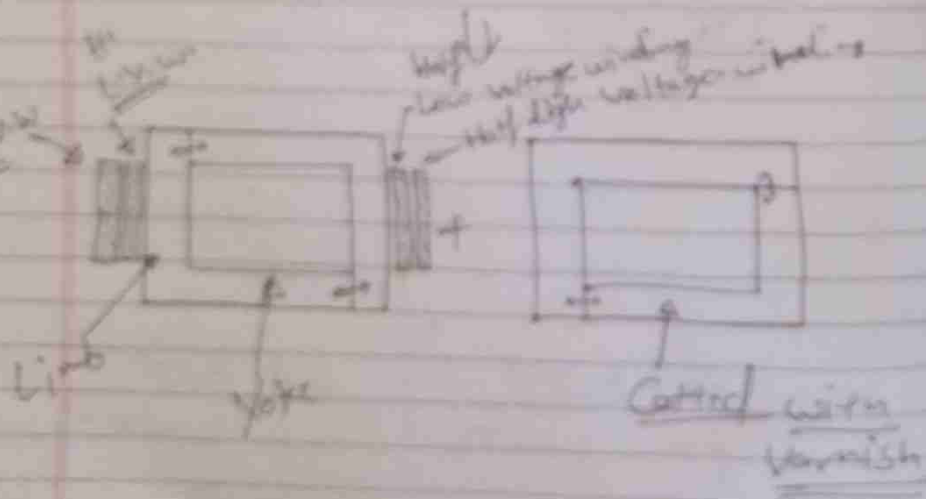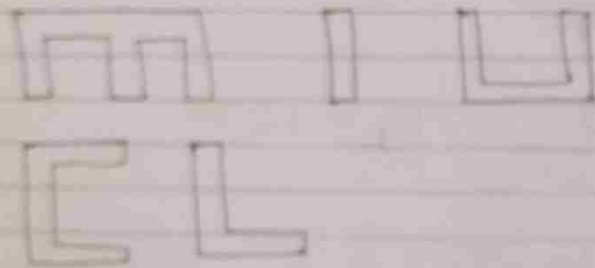- (i) Core type $\rightarrow$ winding surrounding the core
- (ii) Shell type $\rightarrow$ Core surrounds the winding

$\rightarrow$ Stamping (thin sheet of iron)
Material: CHGO (Cold rolled grain oriented)



The following results were obtained on 50kVA 2400/240V transformer after the test


Wattmeter reading 396W
Ammeter reading 3.65 A
Voltmeter reading 110V
Short circuit test

Wattmeter reading 810W
Ammeter reading 20.8 A
Voltmeter reading 92V

- (a) determine circuit constant
- (b) η at full load 0.8 pf lagging

Soln (a) $P_c = 396$ $W_c = 810W$


$I_{full} = 20.8A$

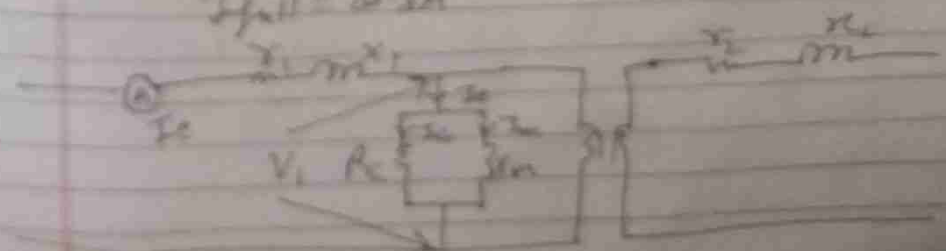

$$P_c = V_1 I_c \cos \theta$$

$$396 = 120 \times 9.65 \cos \theta$$

$$\theta = 70.123$$

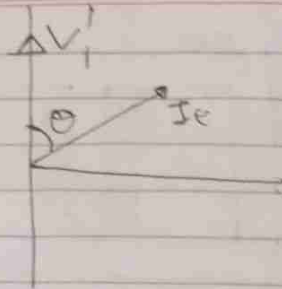

$$3.28 = I_c = I_c \cos \theta = 9.65 \cos \theta$$

$$9.07 = I_m = I_c \sin \theta = 9.65 \sin \theta$$

$$R_c = \frac{V_1}{I_c} = \frac{120}{3.28} = 36.58$$

$$X_m = \frac{V_1}{I_m} = \frac{120}{9.07} = 13.23$$

$$W_c = I_c^2 R_{eqH}$$

$$(Z_{eqH}) = \frac{V_{sc}}{I_{sc}}$$

$$(X_{eqH}) = \sqrt{Z_{eqH}^2 - R_{eqH}^2}$$

$$R_{eq} = 1.87 \Omega$$

$$Z_{eq} = 4.42 \Omega$$

$$X_{eq} = 4 \Omega$$

at full load $\eta = 1$

$$\eta = \frac{1 \times 50 \times 1000 \times 0.8}{1 \times 50 \times 1000 \times 0.8 + 396 + (1)^2 \cdot 810} \times 100$$

$$\eta =$$

###

2200/220V, 50Hz single phase T/F has exciting current of 0.6A and core loss of 361 W when its h.v. energized at rated voltage. (high voltage)

(a) Calculate the two components of exciting current


(b) If the T/F of part (a) supply a load current of 60A at 0.8 p.f. lag on its l.v. side then

Calculate the primary current and its p.f.

Soln

$$\frac{N_1}{N_2} = \frac{E_1}{E_2} = \frac{I_2}{I_1} \Rightarrow$$
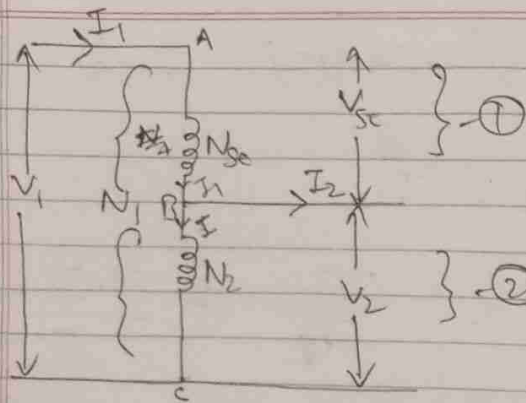
$$\frac{2200}{220} = \frac{60}{I_1} \Rightarrow I_1 = 6A$$



$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{V_{se}}{V_2} = \frac{N_{se}}{N_2}$$

$$N_1 = N_{se} + N_2$$

$$V_1 = V_{se} + V_2$$

$$V_1 = V_2 \frac{N_{se}}{N_2} + V_2$$

$$V_1 = V_2 \left(\frac{N_{se} + N_2}{N_2} \right)$$

$$V_1 = V_2 \frac{N_1}{N_2}$$

When A.T/F has no loss

$$V_1 I_1 \cos \theta_1 = V_2 I_2 \cos \theta_2$$

$$V_1 I_1 = V_2 I_2$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\text{Ratio} = \frac{N_2}{N_1} = K \quad (\text{Transformation Ratio})$$

for T/F Action:-

mmf winding ① = mmf of winding ②

$$(N_1 - N_2) I_1 = (I_2 - I_1) N_2$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\Rightarrow N_1 I_1 - N_2 I_1$$

$$N_2 I_2 - N_2 I_1$$

$$N_2 (I_2 - I_1)$$

$$\# \quad \frac{\text{Transformed V.A.}}{\text{Input V.A.}} = \frac{(V_1 - V_2) I_1}{V_1 I_1}$$

$$= 1 - K$$

$$\begin{aligned} \# \text{ Conduction V.A.} &= \text{Input V.A.} - \text{Transformed V.A.} \\ &= V_1 I_1 - (V_1 - V_2) I_1 \\ &= V_2 I_1 \end{aligned}$$

$\frac{\text{Conduction V.A.}}{\text{Input V.A.}} = k$

2 winding transformer $\textcircled{m} \text{KVA}$
Auto T/f $\textcircled{m} \text{KVA}$

Weight $\propto N \cdot I$

$\textcircled{I = n e A V_d}$

$\Rightarrow$ Weight of Auto T/F
 $\propto \cancel{N_1 I_1} (N_1 - N_2) I_1 + N_2 (I_2 - I_1)$
 $(\because N_1 I_1 = N_2 I_2)$
 $\propto 2 N_1 I_1 - 2 N_2 I_1$

$\Rightarrow$ Weight of 2 winding T/F $\propto$
 $\propto N_1 I_1 + N_2 I_2$
 $\propto 2 N_1 I_1$

$\frac{\text{Weight of AT/F}}{\text{Weight of 2W.T/F}} = \cancel{2 \frac{N_1 I_1}{N_2 I_2}} (1 - k)$

Saving:-

Wt. of 2wdg. T/F - Wt. of A.T/F
 $= K \cdot \text{Wt. of 2wdg T/F}$

Three phase Induction Motor


Generalized transformer

① Stator


Stator frame
which houses the
stator wdg.
mounted core

↓
laminated
(High grade
alloy steel)

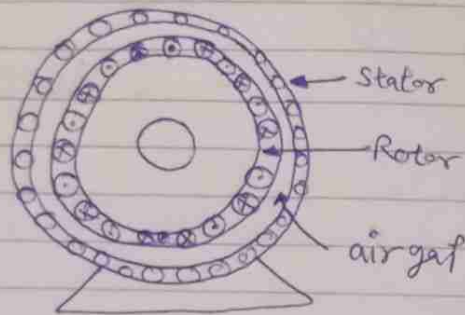↳ responsible for
producing
rotating
magnetic
field







② Rotor

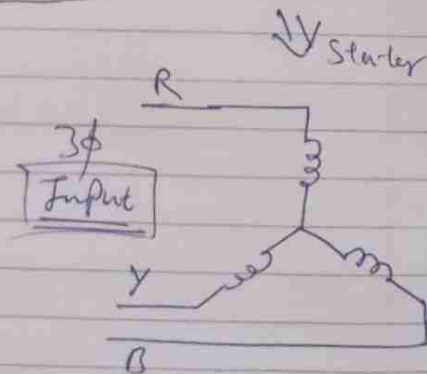

② Rotor

(a) Cage Rotor


(b) Wound Rotor

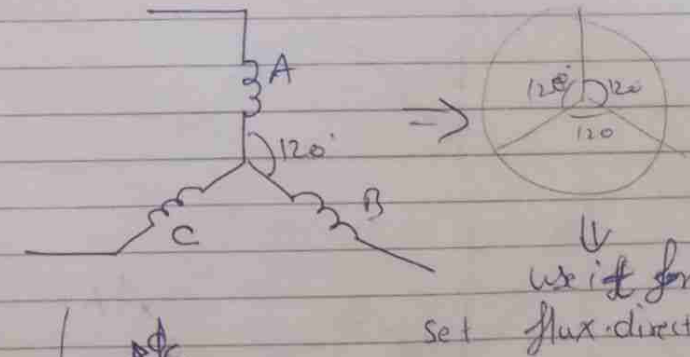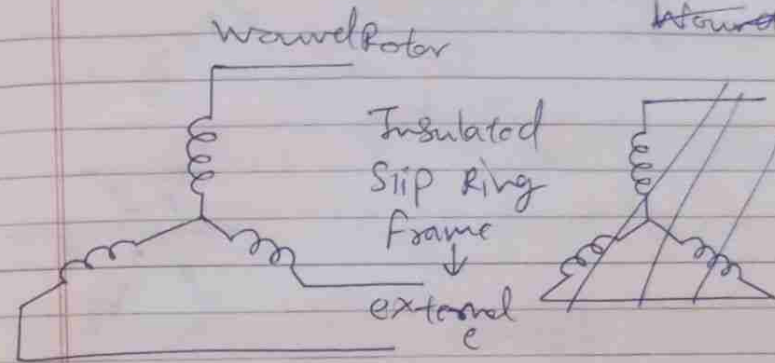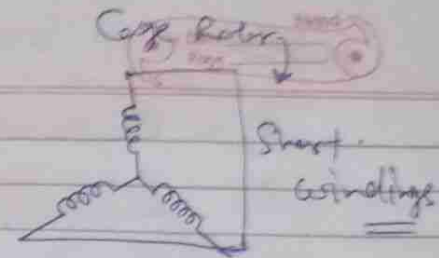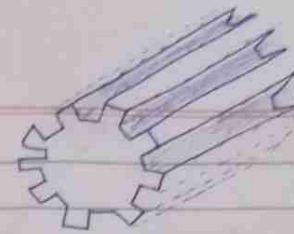

$$V_1 = V_m \sin \omega t$$

$$V_2 = V_m \sin(\omega t - 120^\circ)$$

$$V_3 = V_m \sin(\omega t - 240^\circ)$$




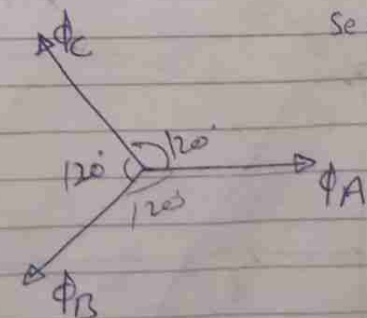


Rotating Flux:


$$\phi_A = \phi_m \sin \omega t$$

$$\phi_B = \phi_m \sin(\omega t - 120^\circ)$$
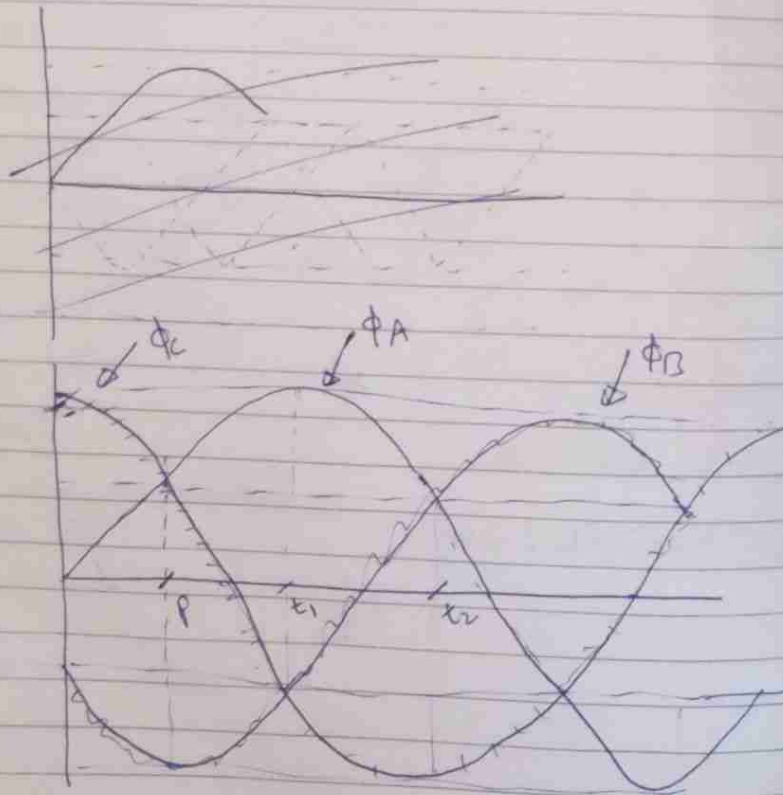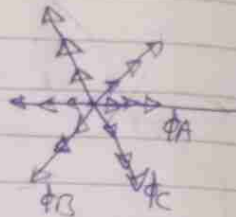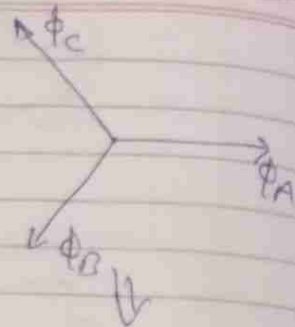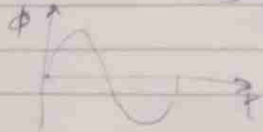
$$\phi_C = \phi_m \sin(\omega t - 240^\circ)$$



at P

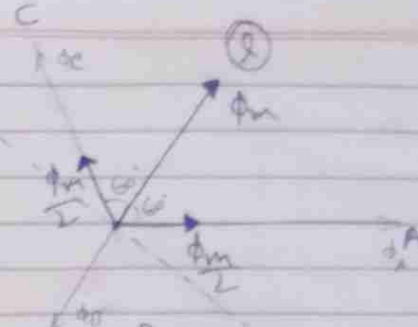


total flux in direction of ϕ_A

$$\phi_{Resultant} = \phi_m + \phi_m \times \frac{1}{2} + \phi_m \times \frac{1}{2}$$

$$\phi_{Resultant} = \frac{3\phi_m}{2}$$

at T₁

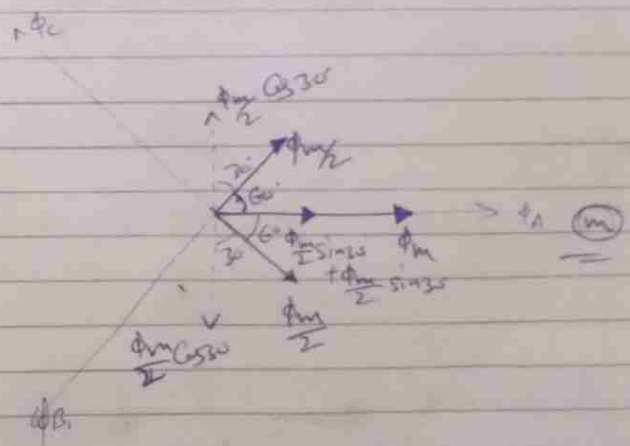


total flux in direction of ϕ_A

$$\phi_R = \phi_m + \phi_m \times \frac{1}{2} + \phi_m \times \frac{1}{2}$$

$$= \frac{3\phi_m}{2}$$

at t_2

$n\phi_c$

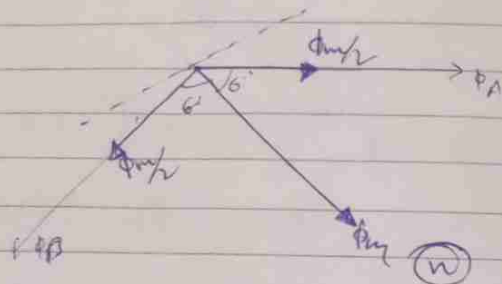

total flux resultant in $\odot$ direction.

$$\phi_R = \phi_m + \frac{\phi_m}{2} \times \frac{1}{2} + \frac{\phi_m}{2} \times \frac{1}{2}$$

$$= \frac{3}{2} \phi_m$$

Rotating flux

Reason

- ① 120° space in winding
- ② 3 ϕ voltage in 120° phase

→ Resultant sum of ϕ_A, ϕ_B, ϕ_C is $\frac{3}{2}\phi_m$ at any time in mathematical

$$(\phi_R)_{30^\circ} = |\phi_A| + |\phi_B| + |\phi_C|$$

$$= |\phi_m \sin 30^\circ| + |\phi_m \sin(30^\circ - 120^\circ)| + |\phi_m \sin(30^\circ - 240^\circ)|$$

$$= \frac{3}{2} \phi_m$$

Flux Rotating Speed/Synchronous speed

$$N_s = \frac{120f}{P} \text{ rpm}$$

No. of poles

Synchronous Speed

$$n_s = \frac{2f}{P} \text{ rps}$$

Supply Frequency

Rotor speed is less than synchronous speed
↓
Caught flux speed
Synchronous & asynchronous
↓
Rotor caught flux speed

$$\Rightarrow \text{Slip speed (S)} = n_s - n_r$$

Synchronous speed of magnetic flux

Speed of rotor

Slip/unit slip (or) fractional slip

$$s = \frac{n_s - n_r}{n_s}$$

$$\% s = \frac{n_s - n_r}{n_s} \times 100$$

$$\begin{aligned} n_s &= \text{rps} \\ N_s &= \text{rpm} \end{aligned}$$

rotor freq. $f_r = \frac{(n_s - n_r)p}{2}$ } it is freq. of rotor emf.

$$f_1 = \frac{(n_s - n_r)p n_s}{2 n_s}$$

$$f_1 = sf$$

Q A 3 ϕ , 6 pole, 50 Hz induction motor has a slip 1% at no load and 3% at full load. Determine

- Synchronous speed
- no load speed
- full load speed
- frequency of rotor current at stand still
- frequency of rotor current at full load

Soln (a) $N_s = \frac{120f}{p}$ rpm
 $= \frac{120 \times 50}{6} = 1000 \text{ rpm}$

(b) %S = $\frac{n_s - n_r}{n_s} \times 100$

%S = $\frac{N_s - N_r}{N_s} \times 100 = 1$

$\frac{1000 - N_r}{1000} = \frac{1}{100}$

990 = N_r
 $N_r = 990 \text{ rpm}$

(c) %S = 3 = $\frac{N_s - N_r}{N_s} \times 100$

3 = $\frac{1000 - N_r}{1000} \times 100$

$N_r = 970 \text{ rpm}$

(d) 50 Hz

(e) $f_r = \frac{3}{100} \times 50 = 1.5 \text{ Hz}$

3φ Induction Motor

↳ Generalized T/F

T/F	3φ IM
① Primary	① Stator
② Concentrated	② Distributed
③ Stationary flux	③ Rotating flux (N_s)
④ $E_1 = \sqrt{2} \pi f N_1 \phi_m$	④ $E_s = \sqrt{2} \pi f N_1 K_w \phi_m$
⑤ Low Reluctance path for mutual flux	⑤ High reluctance path for mutual flux
⑥ 0% to 5% of full load current	⑥ 10% to 50% of full load current
⑦ Rotating $E_2 = \sqrt{2} \pi f N_2 \phi_m$	⑦ $E_r = \sqrt{2} \pi (f - s) N_2 K_w \phi_m$ if $s = sf$

$S = 1$ (stand still)
 $S = 0$ (when rotor synchronous speed of rotor)
 $S = -ve$ (when rotor rotate in opposite direction)

E_2 (at stand still rotor)

$$E_r = sE_2$$


X_2 (at stand still)
 X_{2r} (rotor rotating)

$$X_{2r} = sX_2$$


④

20/11

Circuit at stand still

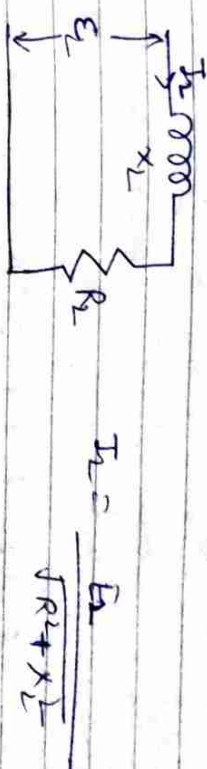

at Rotating

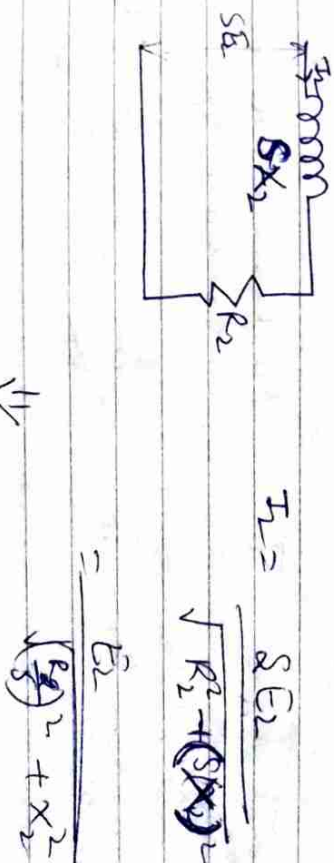

⇒ Power transfer to rotor $P_g = 6 I_2 \cos \theta$

$$\cos \theta = \frac{R_2}{Z_2}$$

$$P_g = E_2 I_2 \cdot \frac{R_2/s}{Z_2} = \frac{I_2^2 R_2}{s}$$

$$\sqrt{(R_2/s)^2 + X_2^2}$$

$$P_g = \underbrace{I_1^2 R_1}_{\text{loss in rotor}} + \underbrace{I_2^2 R_2}_{\text{Mechanical Power of rotor}} - I_2^2 R_2$$

$$P_g = \frac{I_1^2 R_1}{s} + \frac{I_2^2 R_2}{s} (1-s)$$

$$P_g = s P_g + (1-s) P_g$$

∴ Torque $T_e = \frac{\text{Mechanical Power}}{\text{angular speed}}$

$$T_e = \frac{P_m}{\omega_r} = \frac{(1-s) P_g}{\omega_r}$$

$$s = \left(\frac{N_s - N_r}{N_s} \right) = \frac{2\pi N_s - 2\pi N_r}{2\pi N_s}$$

$$s = \frac{\omega_s - \omega_r}{\omega_s}$$

$$\omega_r = (1-s) \omega_s$$

$$T_e = \frac{P_g}{\omega_r}$$

Angular speed of

Stator
 I_e

$$T_e = \frac{I_1^2 R_2}{s (2\pi N_s)} \text{ rpm}$$

$$\therefore \frac{N_s}{60} = n_s$$

$$T_e = \frac{I_1^2 R_2}{s (2\pi n_s)}$$

Starting of Induction motor:-

- 1) depend on:-
- 2) Size & design of motor
- 3) Capacity of Transmission line
- 4) Driven load

Start:-

- (a) Rated voltage (when size is low)
- (b) Reduced voltage (size is big)

(A) DOL (Direct online Starting):-



Starting torque = $\frac{I_{2s}^2 R_2}{s} \left(\frac{1}{2\pi N_s} \right)$
 $\frac{T_{st}}{T_{fl}} = \frac{\text{Starting torque}}{\text{Full load torque}} = \frac{I_{2s}^2 R_2}{s} \left(\frac{1}{2\pi N_s} \right) \div \frac{I_{2fl}^2 R_2}{s} \left(\frac{1}{2\pi N_s} \right)$

(s=1 at starting)
 $\frac{T_{st}}{T_{fl}} = \left(\frac{I_{2s}}{I_{2fl}} \right)^2 \cdot \frac{1}{s_{fl}}$

⑥ $\frac{T_{st}}{T_{fl}} = \left(\frac{I_{2s}}{I_{2fl}} \right)^2 \cdot \frac{1}{s_{fl}}$

I_{se} x Effective no. of turns in stator

= I_{2se} x Effective No. of turns in Rotor

$I_1 \times N_1 = I_2 \times N_2$

I_{se} x Eff. No of turns in stator = I_{2se} x Eff. No of turns in Rotor

$\frac{I_{1st}}{I_{fl}} = \frac{I_{2st}}{I_{fl}}$

$Z_1 \rightarrow$ Total per phase impedance of motor

$I_{sc} = \frac{V}{Z_1}$


Rotor in short

$I_1 = I_{sc}$

sc = short current


③ Series Reactor:- Reduce starting current

$x < 1$ we use series reactor

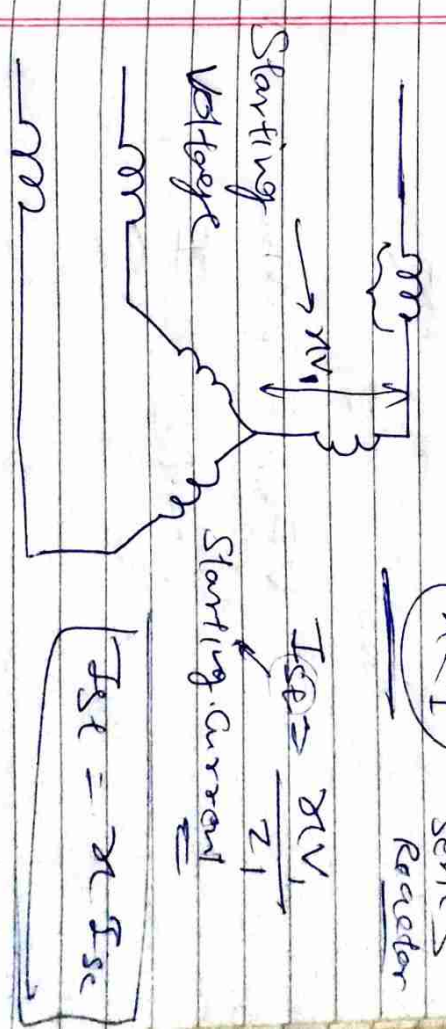

$$\frac{I_{sc}}{I_{fl}} = n^2 \left(\frac{I_{sc}}{I_{fl}} \right)^2 \cdot S_{fl}$$

(C) Auto transformer:-

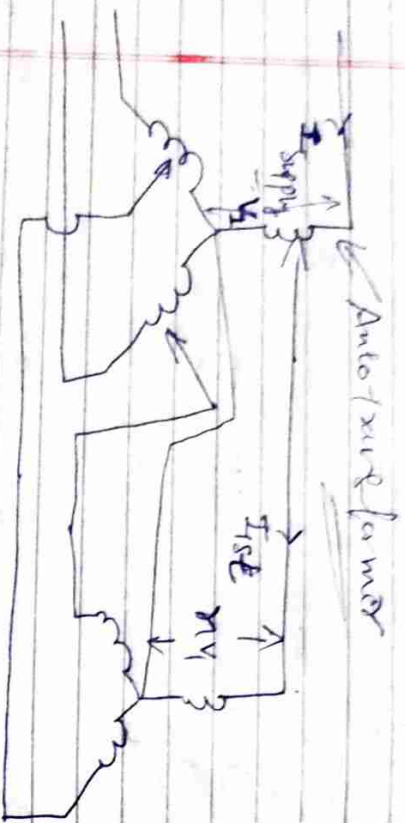

$$I_{sc} = \frac{nV_1}{Z_1} \cdot I_{sc}$$


$$V I_{supply} = n V_1 I_{sc} = n V_1 \cdot I_{sc}$$

$$I_{supply} = n^2 I_{sc}$$


$$\frac{I_{sc}}{I_{fl}} = \left(\frac{n I_{sc}}{I_{fl}} \right)^2 \cdot S_{fl}$$



$$= \frac{1}{n^2} \left(\frac{I_{supply}}{I_{fl}} \right)^2 S_{fl}$$

(d) Star Delta Starting:-

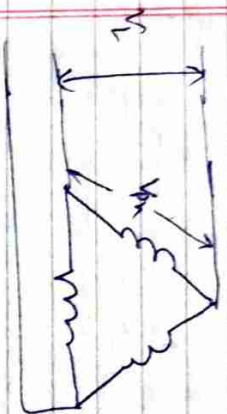

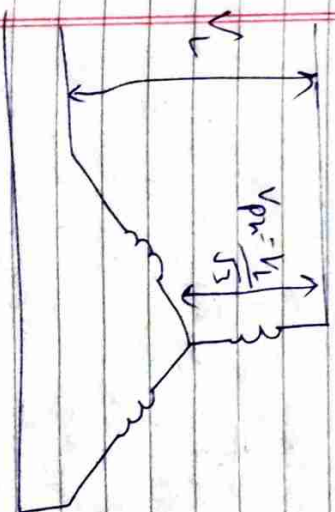When motor is large size then his ~~star~~ winding connected in Δ use if for starting motor



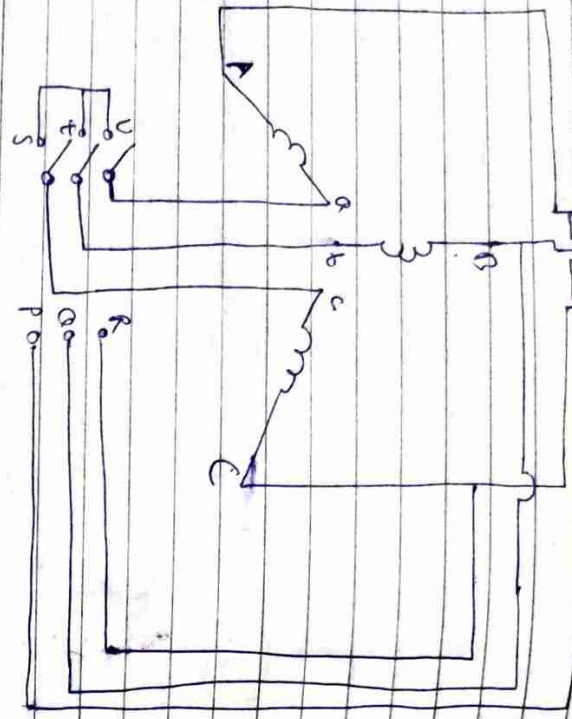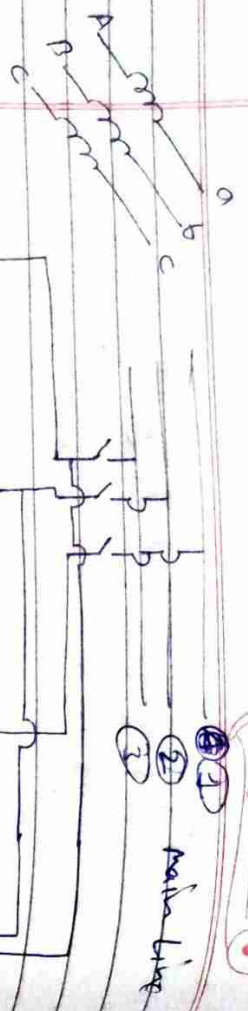

In Star

$$I_L = \frac{V_L}{\sqrt{3}} \times \frac{1}{Z_1}$$

$$I_{sc} = \frac{V_L}{Z_1}$$

$$I_L = \frac{I_{sc}}{\sqrt{3}}$$

In delta


$$I_{sc} = \frac{V_L}{Z_1} = I_{sc}$$

$$I_A = \sqrt{3} I_{sc}$$

$$\frac{I_L}{I_A} = \frac{1}{3}$$

Q A Shunt generator delivers 50kw at 250v when running at 1000rpm. The armature and field resistance are 0.02Ω and 50Ω respectively. Calculate the speed of machine when running as a Shunt motor and taking 50kw input at 250v allow 1v per brush for contact drop.


Soln

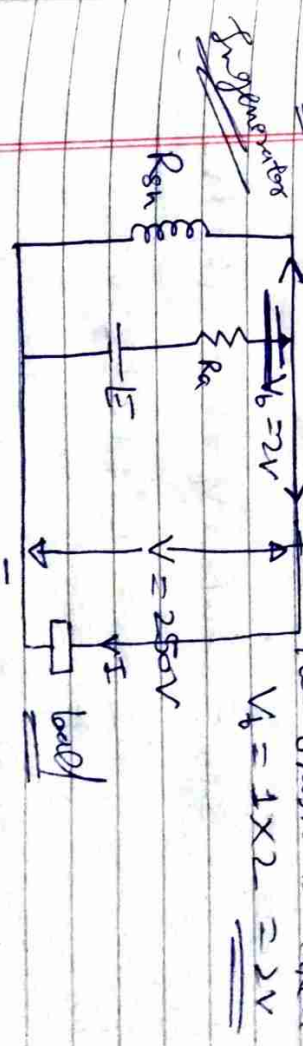

$$V_b = 1 \times 2 = 2V$$

$$P = VI$$

$$I = \frac{50000}{250} = 200A$$

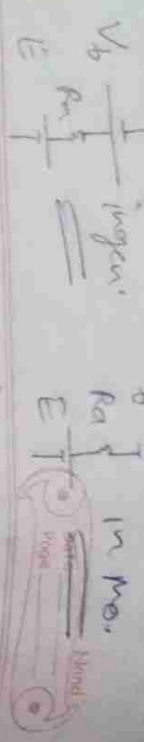

Speed $N = 400 = \frac{120f}{p}$

$R_a = 0.02 \Omega$

$R_{sn} = 50 \Omega$

$I_{sn} = \frac{250}{50} = 5$

$I_a = 200 + 5 = 205 A$

$E_g = \phi \cdot n \cdot \frac{p}{A}$

$E_g = \phi \cdot n \cdot \frac{p}{A}$


$\frac{E_g}{E_m} = \frac{\phi_g}{\phi_m} \times \frac{n_g}{n_m}$

$E_{gm} = I_a R_a + V + \text{(by kV)} \cdot 1000$

$= 205 \times 0.02 + 2 + 250$

$= 256.1 V$

if generator working as shunt motor

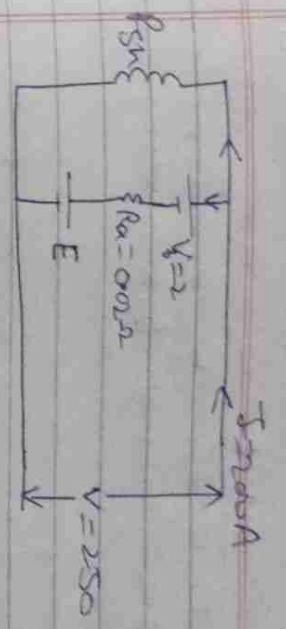

$R_{sn} = 50 \Omega$

$I_{sn} = \frac{250}{50} = 5 A$

$I_a = 200 + 5 = 205 A$

$E_m = V - I_a R_a - V_b$

$= 250 - 195 \times 0.02 - 2$

$= 244.1 V$

$\frac{E_g}{E_m} = \frac{\phi_g}{\phi_m} \times \frac{n_g}{n_m}$

$\frac{E_g}{E_m} = \frac{n_g}{n_m}$


$\frac{256.1}{244.1} = \frac{400}{N_m} = \frac{400}{N_m}$

$N_m = \frac{400 \times 244.1}{256.1} = 381.25 \text{ rpm}$



Q₂. A 4 pole 500V d.c. shunt motor has 700 Wave Connected conductors in its armature. The full load armature current is 60A and flux per pole is 30mWb. Calculate the full load speed if the motor armature resistance is 0.2Ω and brush drop is 2V.

Soln

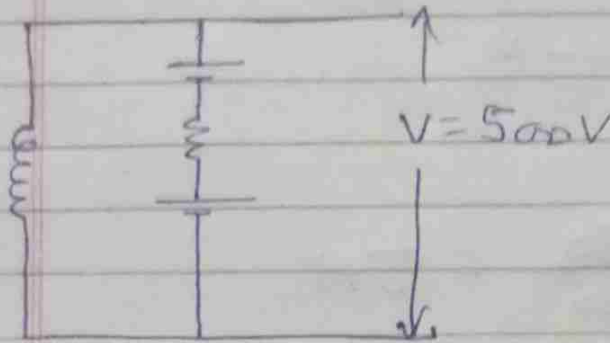

$$P = 4$$

$$Z = 700$$

$$I_a = 60A$$

$$\phi = 30mWb$$

$$R_a = 0.2\Omega$$

$$\eta = ?$$

$$A = 2 \text{ (Wave Connected)}$$

$$V_b = 2V$$

$$E = V - I_a R_a - V_b$$

$$= 500 - 60 \times 0.2 - 2$$

$$= 486V$$

$$\begin{array}{r} 12 \\ 500 \\ \hline 486 \end{array}$$

$$E = \frac{\phi Z n p}{A}$$

$$E = 486 = \frac{30 \times 10^{-3} \times 700 \times 4 \times n}{2}$$


$$n = 11$$

$$N = n \times 60$$

$$= 694.2857143$$

Construction of DC Machines :-

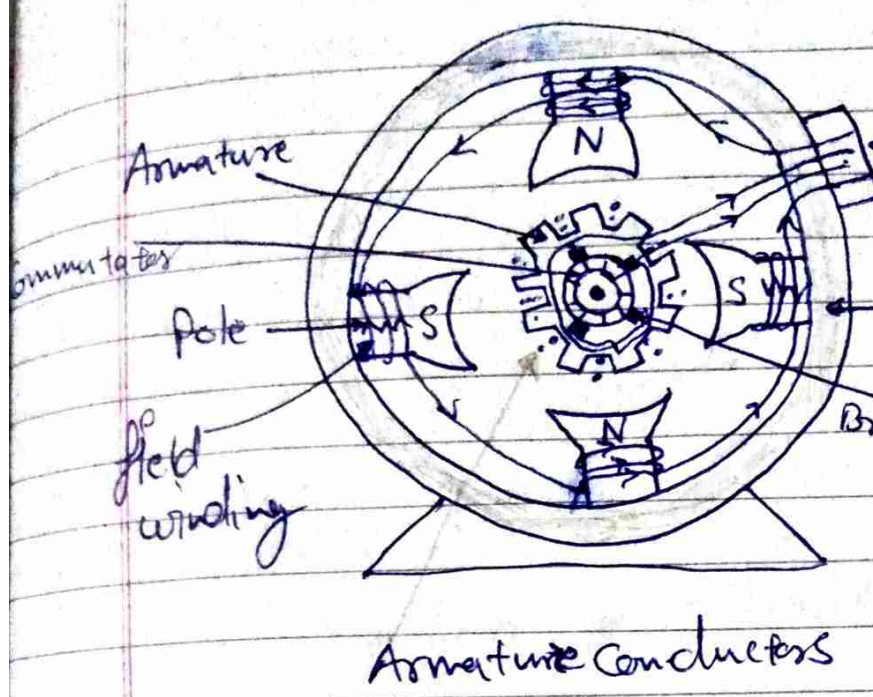Field Winding
Dynamo
Pump
Initial current
AC/DC




- Protective Cover
- protect all components
- It's give mechanical support to the poles
- it's make from Cast iron


Pole! - two parts -

- ① Pole Core
- ② Pole shoe

Best iron/
Best Steel

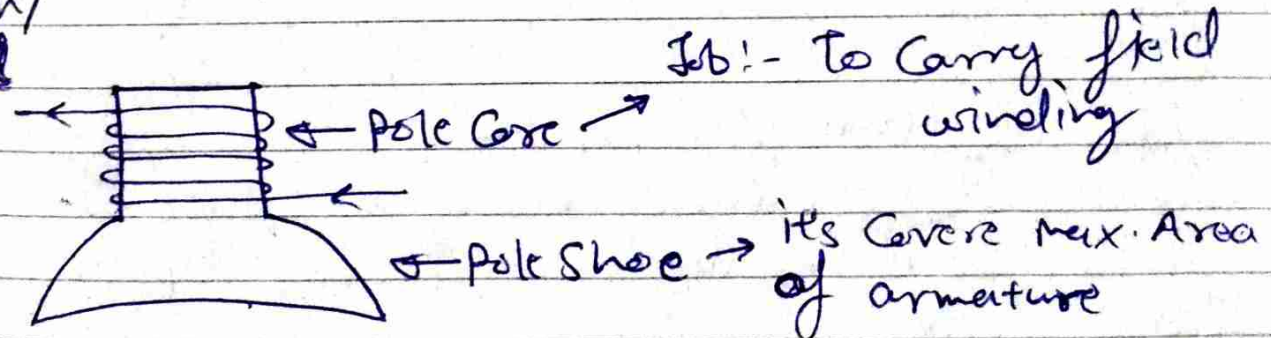


direction of flux in DC machine

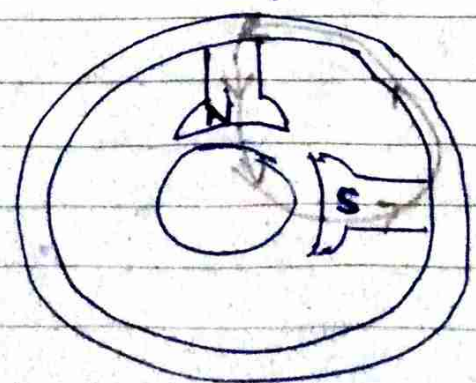


→ Pole make by thin sheets

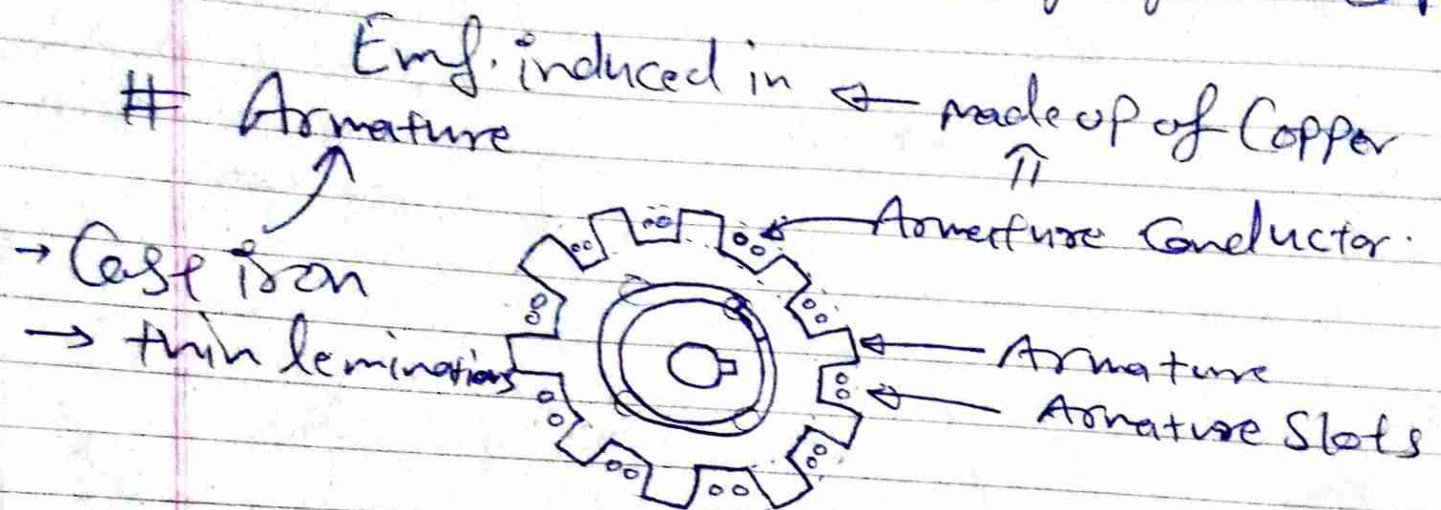field winding:- It is a coil wire
→ it's responsible for flux
→ all windings are connecting in series
→ it's making from Copper



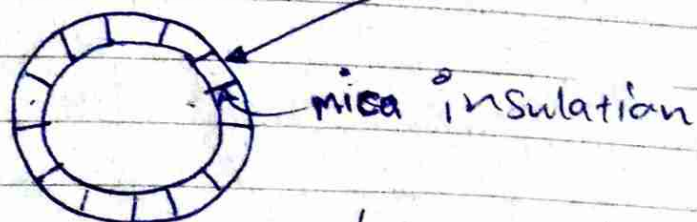Commutator:-
→ it is mechanical rectifier
→ it is made up from Copper segments



Work:- Take Voltage and current from one side and give it to armature

Brushes! -

→ it is made up from Carbon

→

DC Generator Principle:-

Principle of operation of DC generator is Faraday's law of electromagnetic induction.

→ Dynamically induced emf $e = \frac{d\phi}{dt}$

→ Relative motion b/w conductor and flux.

ways:-

① Flux is stationary, conductor is moving.

② Conductor is stationary, flux is moving.

(in DC generator)

(in AC generator)

→ Conductor can be rotated with the help of prime mover


↓

ex:- Diesel Engine, steam turbine, Diesel turbine etc.


→ Fleming's right hand rule is use to check direction of induced emf. in coil

→ Direction of induced EMF.

→ Current Coming out

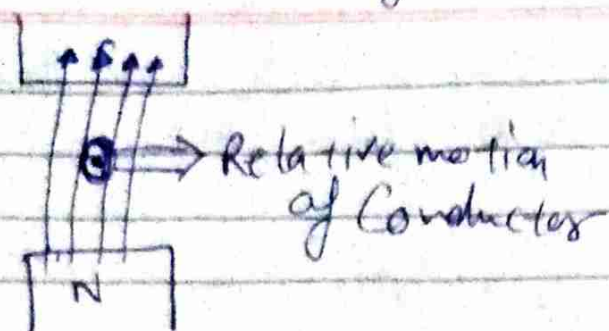

→ Current going inside plane.

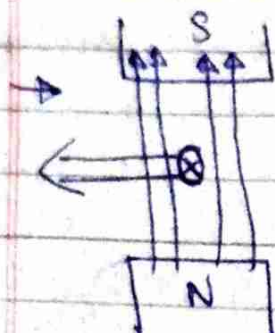

⇒ Magnitude of induced EMF.

$$e = Blv \sin \theta = E_m \sin \theta \text{ Volts}$$

B = flux density (wb/m^2)



l = active length of Conductor (m)

v = relative velocity of Conductor w.r.t. Magnetic flux (m/s)

θ = angle b/w two planes
(Plane of Rotation &

Plane of magnetic flux
measured from axis of
plane of flux)

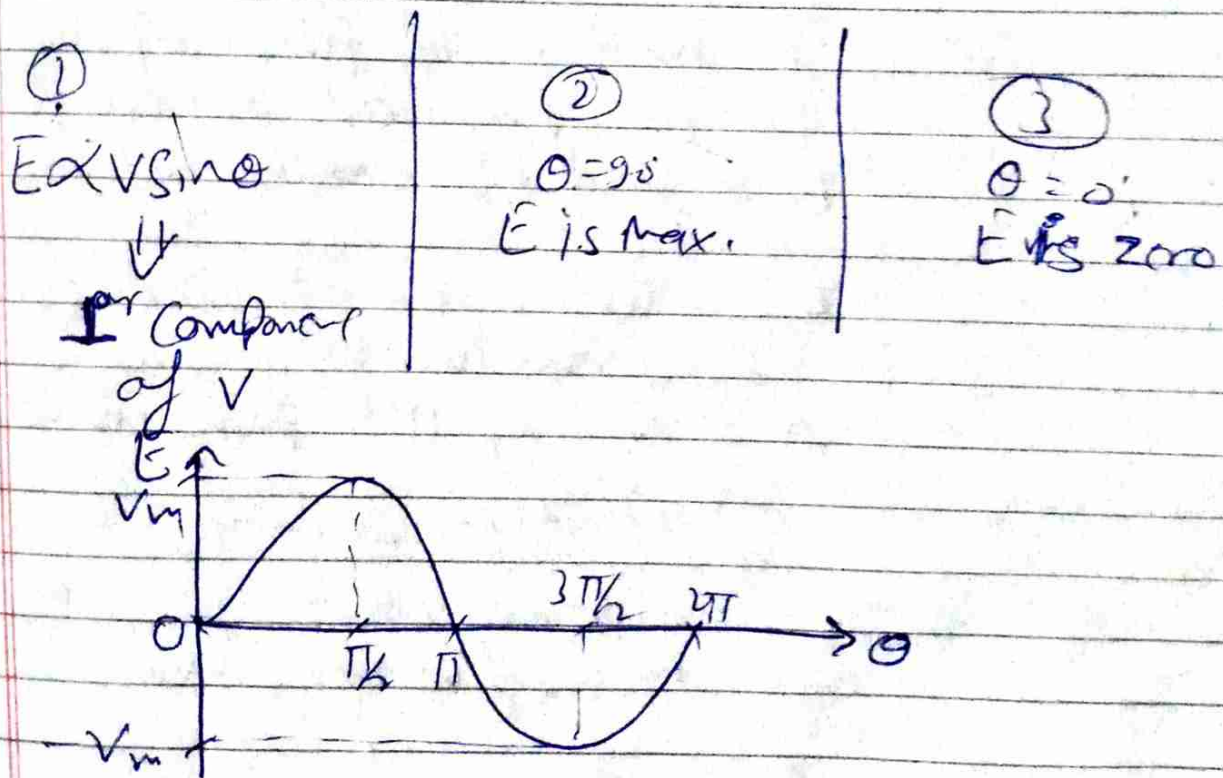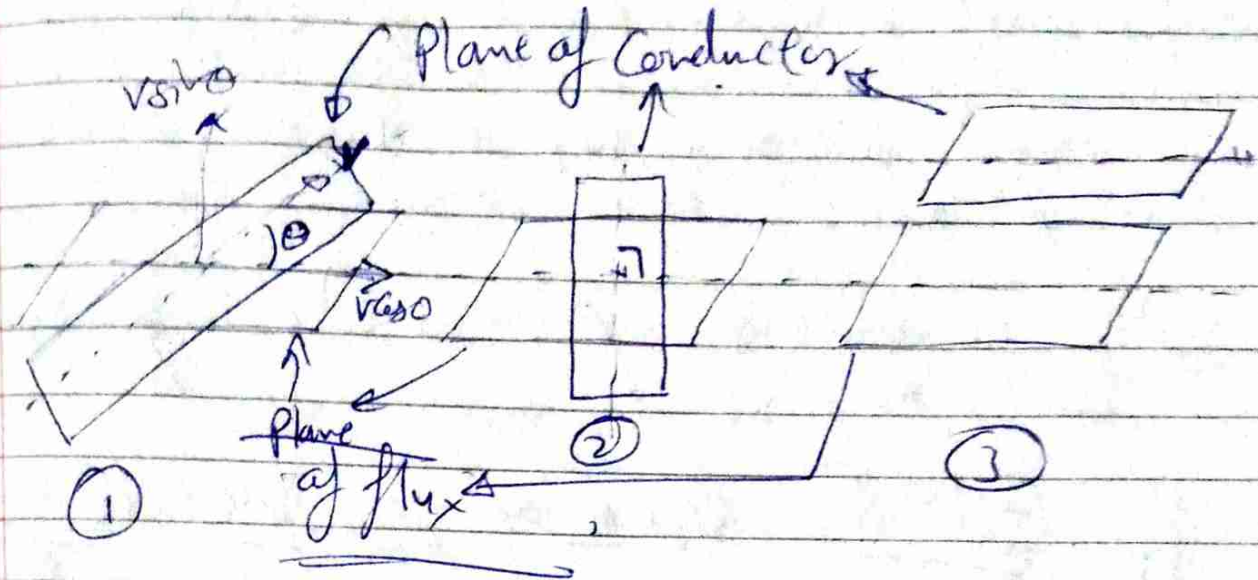→ magnitude of emf. depends on 1st Component of relative velocity of Conductor



⇒ Commutator :- a device is used in dc generator to convert ~~ac~~ alternating induced emf. to unidirectional dc. emf. (Mechanical Rectifier)

→ The Commutator is the essential part of a dc. machine used for reversing the direction of current. It is made up of wedge-shaped hard drawn copper wires.

→ It converts AC $\rightarrow$ dc in dc machine.

E.M.F. equation for D.C. Generator

Let, P = Number of poles of the generator
 ϕ = flux produced by each pole (wb)
 N = Speed of armature of generator (rpm)

Z = total no. of conductors in armature.

A = No. of path in which armature conductors are distributed.

$\mathcal{E}$ = Rate of cutting flux.

$$\mathcal{E} = \frac{d\phi}{dt} \quad \text{--- (1)}$$

as per Faraday's law of Electromagnetic Induction


Total flux = flux produced by each pole $\times$ No. of poles

$$\Rightarrow \text{total } (\phi) = \phi \times P$$

$\Rightarrow$ Time required for a conductor to complete 1 revolution.

$$T = \frac{60}{N} \text{ (sec)}$$
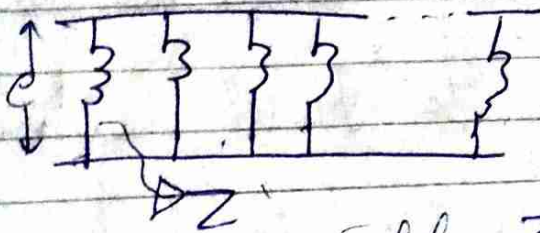
$$e = \frac{\phi P}{\left(\frac{60}{N}\right)} = \frac{\phi P N}{60} \text{ (only for one Conductor)}$$




Eff. $\frac{Z}{A}$ Conductor need to multiplied with emf induced in one Conductor

$$E = e \times \frac{Z}{A} = \frac{\phi P N Z}{A 60}$$

DC machine :-

⇒ Electromechanical Conversion

①

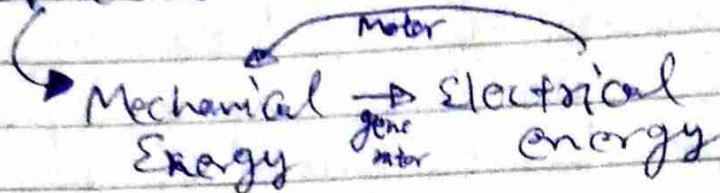

⇒ Type

① AC machine :- works on A.C. Current

② DC machine :- works on DC. Current



Types of D.C. generator :-

→ types depend on Connection on field winding.

→ Excitation to field winding

Type :- ① Separately Excited



② Self Excited

(a) Shunt generator

(b) Series generator

① Separately Excited generator :-

Circuit diag :-

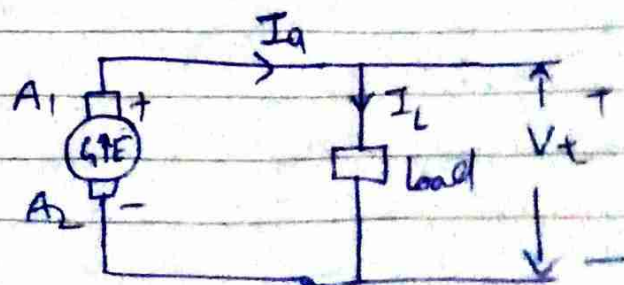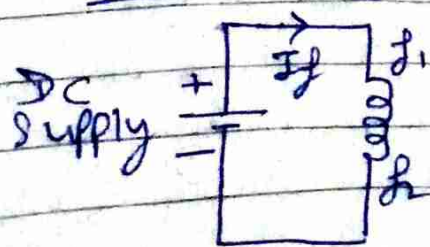

Voltage & Current Relation

$$I_a = I_l$$


I_a = Armature Curr.

$$E = V_t + I_a R_a + V_{\text{brush}}$$

R_a = Armature Resis

Brushes se have
bala drope

② (a) Shunt Generator:-

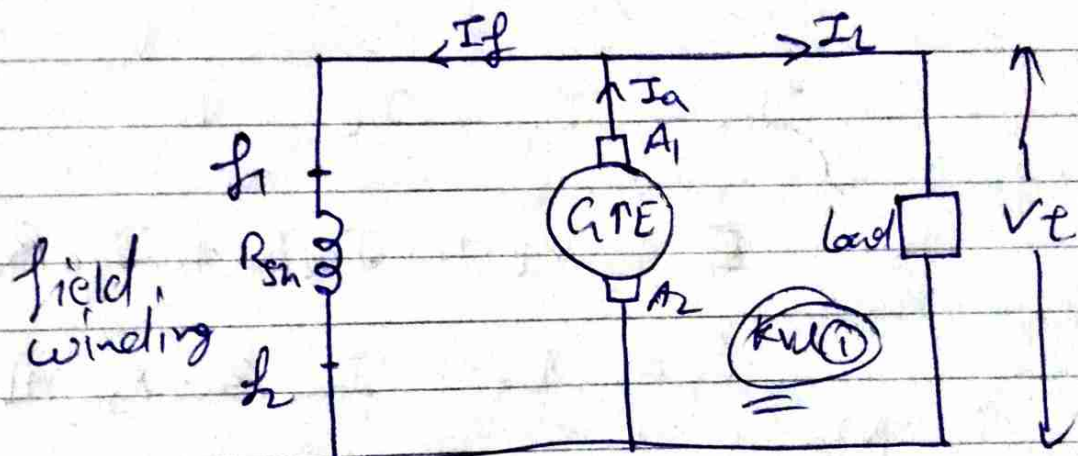

field winding share with
armature so it's called
Shunt generator.


Voltage vs Current

$$I_a = I_f + I_l$$

$$I_f = \frac{V_t}{R_{sh}}$$

KVL ① $E = V_t + I_a R_a + V_{\text{brush}}$

③ Series Generator:-

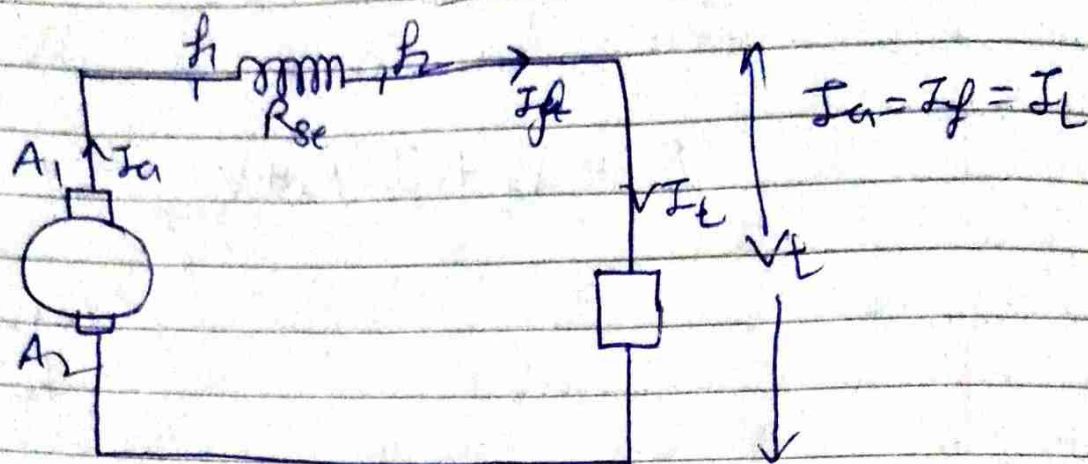

Voltage $\forall$ s Current

$$I_a = I_f = I_L$$

$$E = V_t + I_a R_a + I_a R_{se} + V_{brush}$$

$$E = V_t + I_a (R_a + R_{se}) + V_{brush}$$

② D.C. Motor:-


Working principle of D.C. Motor

When a current carrying conductor is placed in a magnetic field, it experiences a mechanical force.

→ Convert its Electrical energy to mechanical energy

Parts: -

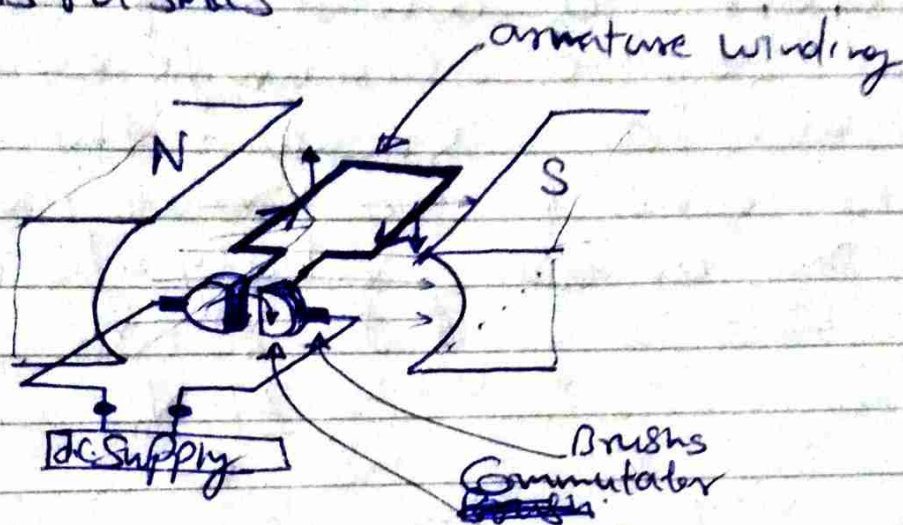- ① Stator
- ② Rotor
- ③ field winding
- ④ Armature winding
- ⑤ Commutator
- ⑥ Brushes



Torque Equation for d.c. motor

$$f = \frac{N}{60} = n$$


$$\omega = \frac{2\pi N}{60}$$

$$\text{Torque (T)} = F \times r \quad N \cdot m$$

$$\frac{W}{t} = F \times \text{distance moved}$$

$$\frac{W}{t} = F \times 2\pi r$$
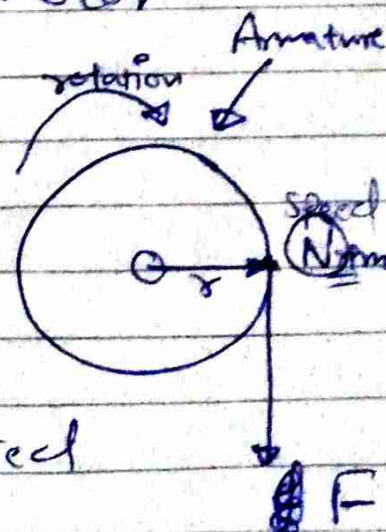
$$\text{Power} = \frac{W}{t} = \frac{2\pi r \times F}{(60/N)}$$



Name _____
Date _____
Page _____

$$P = (F \times r) \frac{2\pi N}{60}$$

$$P = T \times \frac{2\pi N}{60}$$

Consider a wheel of radius r (m) acted on by a circumferential force F (Newton) as shown. The force F causes the wheel to rotate at N rpm. The angular velocity of wheel is

$$\omega = \frac{2\pi N}{60}$$

Torque $T = F \times r$

~~W~~ = $F \times \text{distance moved}$
 $W = F \times 2\pi r$ Joules

Power developed $P_1 = \frac{\text{work done}}{\text{time}}$

$$= \frac{F \times 2\pi r}{60/N}$$

($\because \text{rpm} = 60, \text{ rps} = \frac{N}{60} \therefore \text{1 rev } \frac{60}{N}$)

$$P_1 = (F \times r) \cdot \frac{2\pi N}{60}$$

$$= T \times \frac{2\pi N}{60}$$

The torque developed by a d.c. motor is obtained by looking at the electrical power supply to it and mechanical power produced by it. It's also called armature torque. The gross mechanical power developed is $E_b \cdot I_a$, then.

$$\text{Power developed in armature} = \text{Power at output}$$

$$E_b \times I_a = T \times \frac{2\pi N}{60}$$

$$\text{When } E_b = \frac{\phi Z N P}{A 60}$$

$$\frac{\phi Z N P}{60 A} \times I_a = T \times \frac{2\pi N}{60}$$



$$T = \frac{P Z \phi I_a}{2\pi A} \text{ (N.m)}$$

$$T = 0.159 \cdot \phi \cdot I_a \cdot Z \left(\frac{P}{A} \right) \text{ Nm}$$

Hence the torque developed by a d.c. motor is directly proportional to the flux per pole and armature current.

$$T \propto I_a \phi$$

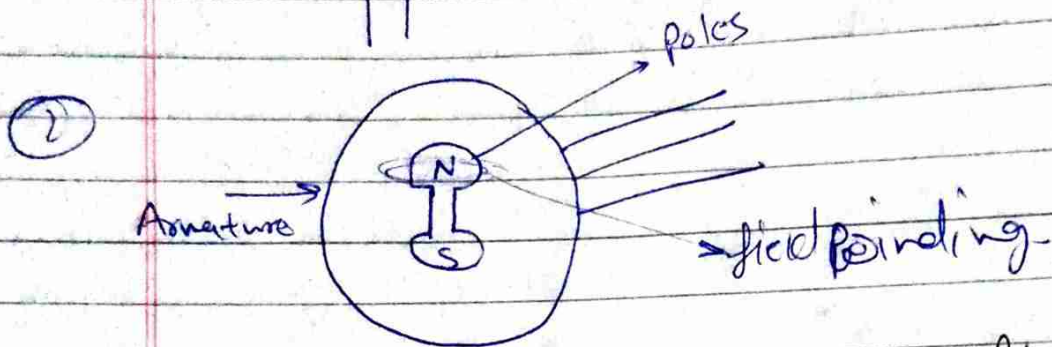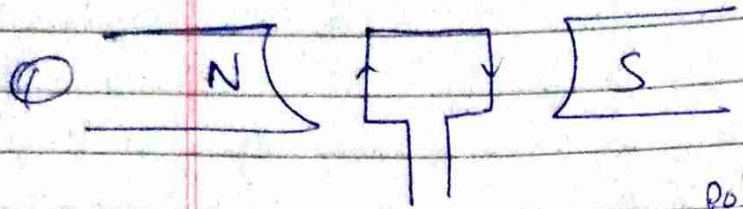Alternator (Synchronous Generator) (A.C. Generator)




- Advantages of Rotating field Alternator
- Insulation Easy on armature winding
 - No vibration & other disturbances
 - O/p, No Slip Rings and brushes in armature
 - Two Slip Rings are Required for dc input
 - Size of machine is reduced (arm. winding)
 - High speed rotation (dependent on weight) (field winding in machines)
 - Cooling is Easy (Arm. heat)

⇒ Use prime mover in rotating field winding
 ↓
 hydro turbines, steam turbines


⇒ Excitation System is use to give E in AC generator. It gives current from field winding.

⇒ Arm winding:-

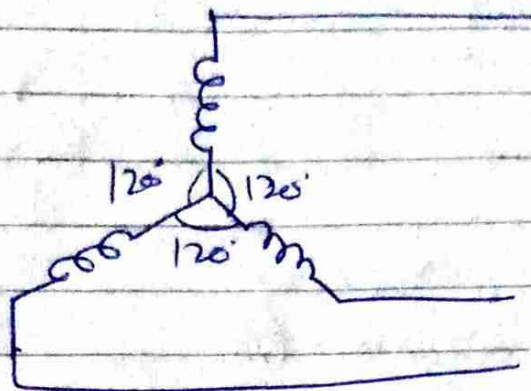


Excitation System type:-

① DC Excitation:-

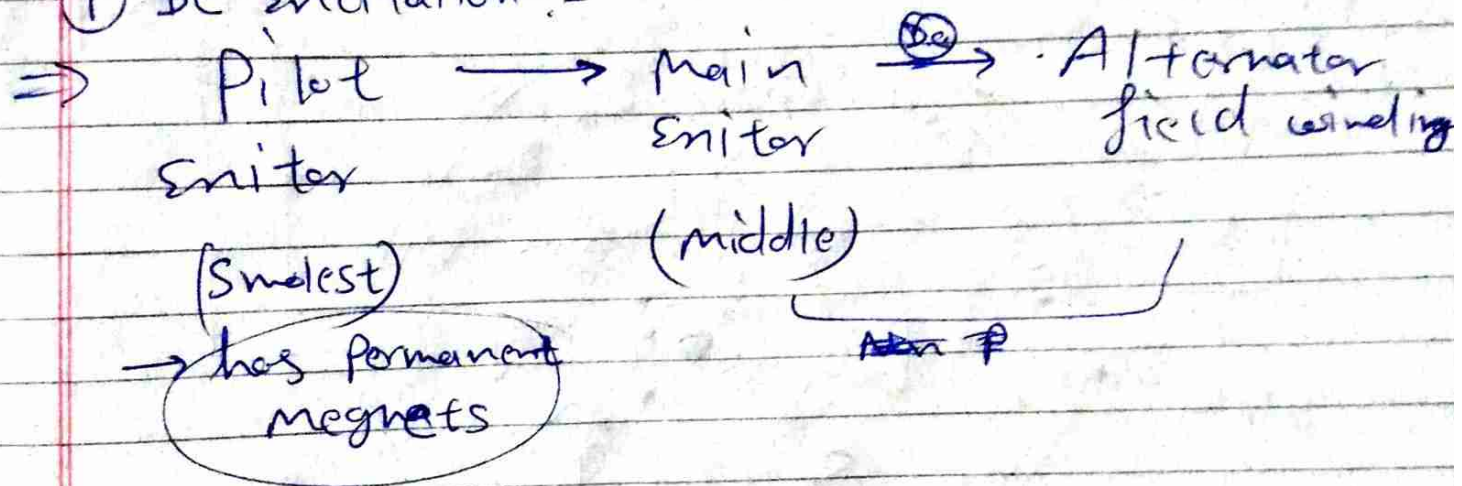


② AC-Excitation:-

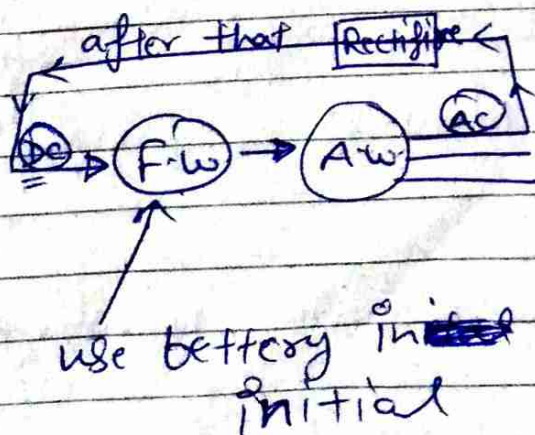

③ Brush less excitation system use in big generators

Parts of generator :-

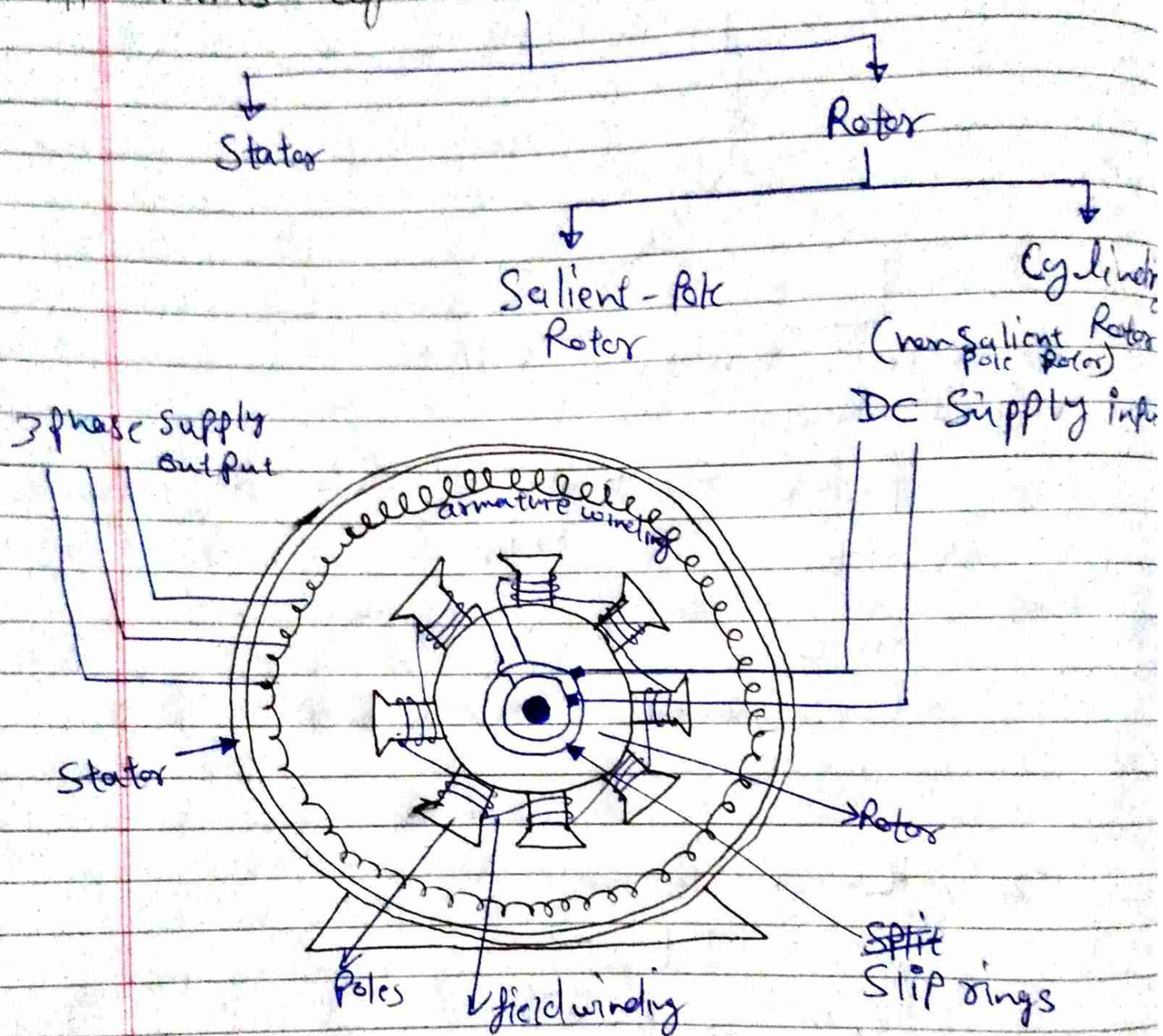

① Stator :-

Parts :- Frame, Core, windings, Cooling arrangement


Frame :- Small size machine $\rightarrow$ Cast Iron

large size machine $\rightarrow$ welded steel type

turns series $\rightarrow$ $\odot$ $\parallel$ $\rightarrow$ series winding

$\rightarrow$ Armature winding are Connected in Star

① Salient-pole Rotor:-

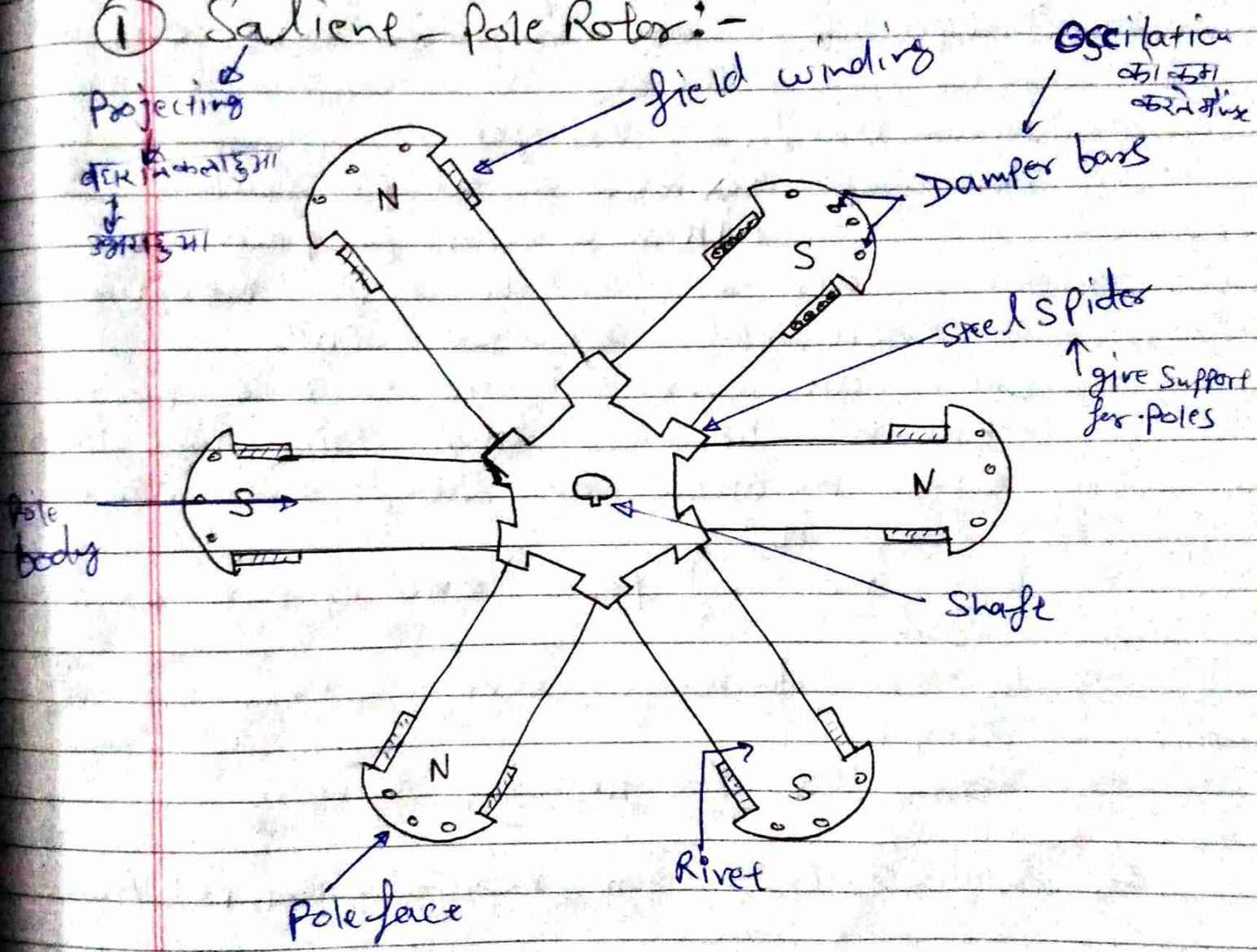

- $\rightarrow$ Max. Poles use
- $\rightarrow$ it do not gives high speed
- $\rightarrow$ No. of Poles $\uparrow$ speed $\downarrow$



$$N_s = \frac{120 f}{P}$$

$\downarrow$ $\uparrow$

$\rightarrow$ use hydro turbine in Salien-pole Rotor

- To Reduce eddy currents, thin steel laminations are used
- Concentrated winding are used
- Dampor bars are used to damp out the rotor oscillations
- Non-uniform air-gap
- Air gap maximum - at pole centres
minimum - at pole faces
- Radial air gap length helps machine to generate sinusoidal emf
- Ends are connected to a D.C. Source through brushes and slip rings (metal rings mounted on shaft and insulated from it)
- large no. of poles and operate at low speed
- larger diameter and short axial length
- ~~use~~ use concentrated winding

Cylindrical or non-Salient Pole Rotor

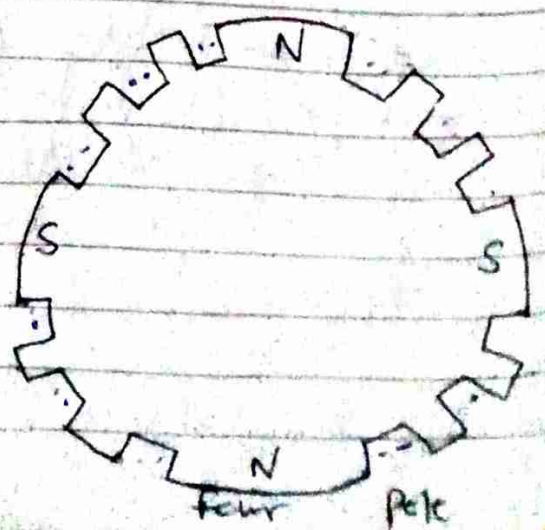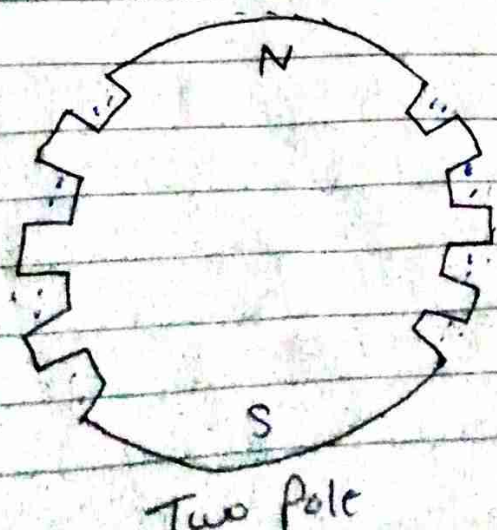

- use distributed winding.
- high grade nickel - Chrome Molybdenum
- used in high speed machine.
- Greater mechanical strength and more accurate dynamic balancing.

→ Steam turbines used

E.M.F. Equation of an Alternator

ϕ = useful flux per pole

P = total No. of poles

f = frequency of generated voltage (Hz)

n = speed of rotor in (rps)

Z_p = Total No. of conductors per phase

T_p = Total No. of coils

$Z_p = 2T_p$ in A.C. generator

E_{av} : avg. emf. in per conductor

$$\Rightarrow \begin{aligned} \text{total flux} &= P\phi, & \text{time taken in 1 rev.} &= \frac{1}{n} \text{ sec} \\ E_{av/\text{conductor}} &= \frac{P\phi}{T_n} \frac{d\phi}{dt} \end{aligned}$$

$$= Pn\phi$$

$$f = \frac{PN}{120} = \frac{Pn}{2}$$

$$Pn = 2f$$

$$E_{av/\text{conductor}} = 2f\phi$$

$$n = \frac{N}{60}$$

$$N = \frac{120f}{P}$$

$$E_{av}/\text{phase} = 2fz_p\phi$$

$$z_p = 2T_p$$

$$E_{av}/\text{phase} = 4\phi f T_p$$

$$\text{form factor} = k_f = \frac{\text{r.m.s value}}{\text{average value}}$$

$$\text{value of } k_f \text{ for } \underline{\text{sine wave}} = \underline{1.11}$$

$$E_{rms} = k_f \times E_{av}/\text{phase}$$

$$\begin{aligned} E_{rms} &= 1.11 \times 4\phi f T_p \\ &= 4.44 f T_p \phi \end{aligned}$$

Voltage Regulation:-

The voltage regulation of a synchronous generator is the rise in voltage at the terminals when the load is reduced from full-load rated value to zero, speed and field current remaining constant.

Per unit voltage Regulation

$$\underline{\underline{\Delta}} \quad \frac{|E_a| - |V|}{|V|}$$

E_a = No loaded voltage

V = terminal voltage (full load voltage)

Percento voltage Regulation

$$\underline{\underline{\Delta}} \quad \frac{|E_a| - |V|}{|V|} \times 100$$

→ it is a one type of disadvantage