

Simulating `_single_component_and_exporting_s_pars`


September 20, 2023

```
[1]: # This notebook uses scikit-rf, an open-source Python package for RF and  
      ↪ Microwave applications.  
      # Home Page https://scikit-rf.org  
      # The following is a Jupyter notebook highlighting the use of scikit-rf to  
      ↪ simulate and export s-parameters of  
      # an inductor
```


```
[2]: import skrf as rf
```

```
[3]: freq = rf.Frequency(start=0.1, stop=10, unit='GHz', npoints=1001) # the  
      ↪ necessary Frequency description
```

```
[4]: # Circuit 1 : Inductor with 50 ohm terminations on both ports.  
  
tl_media = rf.DefinedGammaZ0(freq, z0=50) # Transmission Line Properties  
gnd = rf.Circuit.Ground(freq, name='gnd')  
port1 = rf.Circuit.Port(freq, name='port1', z0=50)  
port2 = rf.Circuit.Port(freq, name='port2', z0=50)  
L = tl_media.inductor(2.5e-9, name='L')  
  
# Connection List  
  
cnx = [  
    [(port1, 0), (L, 0)],  
    [(L, 1), (port2, 0)],  
    ]  
  
cir = rf.Circuit(cnx) # Build the circuit  
ntw = cir.network     # getting the resulting Network from the 'network'  
                    ↪ parameter:  
  
# Check if netlist is correct  
cir.plot_graph(network_labels=True, network_fontsize=15,  
               port_labels=True, port_fontsize=15,  
               edge_labels=True, edge_fontsize=10)
```

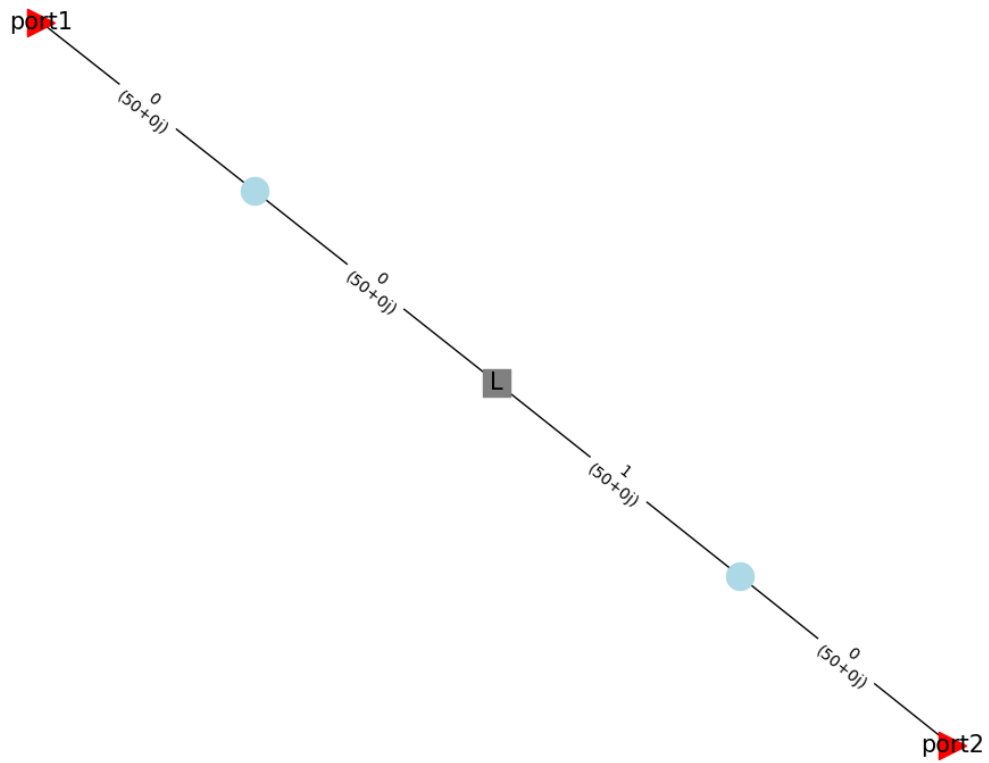
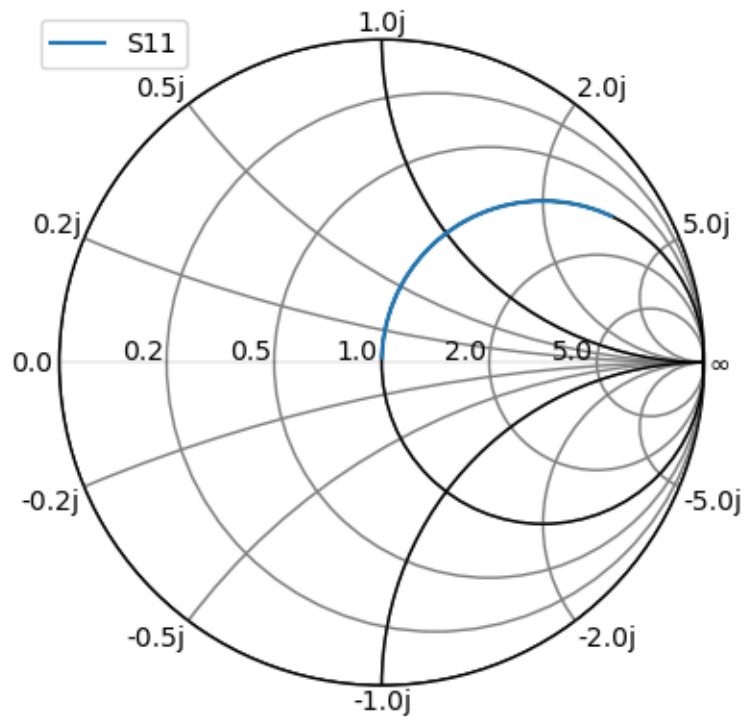
```
[5]: # Circuit 1 Plot S11  
ntw.plot_s_smith(m=0,n=0,draw_labels=True) # Plot S11 on Smith Chart
```



```
[6]: # Circuit 1 Export s2p file  
ntw.write_touchstone('inductor.s2p')
```