

04-Electric Power

ECEGR 452
Renewable Energy Systems



Overview


- Review of Electric Circuits
- Phasor Representation
- Electrical Power
- Power Factor



Introduction

- Majority of the electrical energy produced by renewable resources is ultimately transmitted and consumed within the interconnected power system
- Integration of renewable resources into the power system is a challenge
- We need to understand basics of electric power

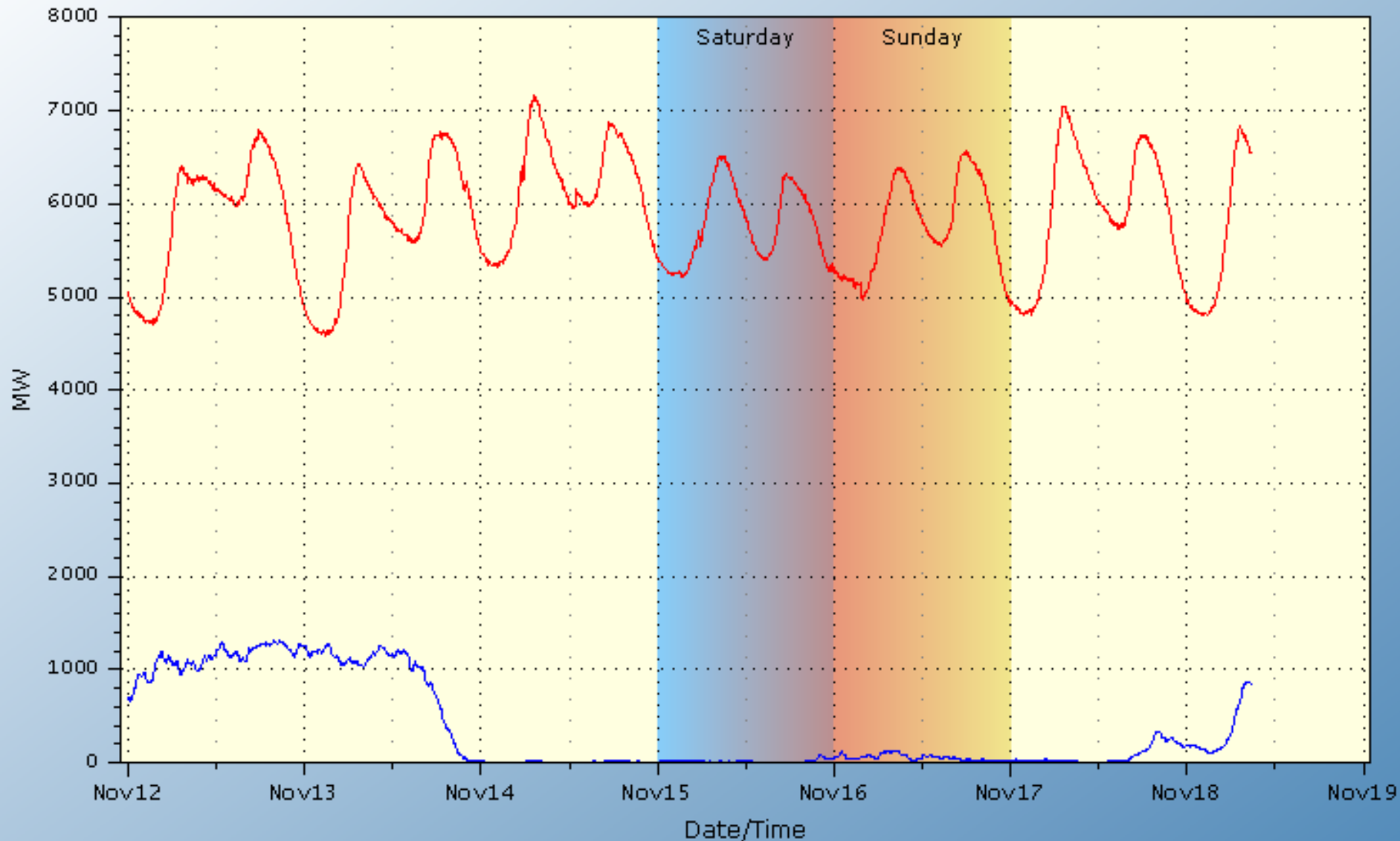BPA Balancing Authority Load & Total Wind Generation, Last 7 days
12Nov2008 - 19Nov2008 (last updated 18Nov2008 08:51:30)



Based on 5-min readings from the BPA SCADA system for points 45583, 79687
Balancing Authority Load in Red, Wind Generation in Blue; Installed Wind Capacity=1489 MW
BPA Technical Operations: Roy Ellis (rcellis@bpa.gov)




Review of Electric Circuits

- Voltage in AC circuits:
 - $v(t) = V_{\max} \cos(\omega t + \theta_V)$
 - V_{\max} : voltage amplitude (Volts)
 - ω : frequency (rad/sec)
 - θ_V : phase angle of the voltage (rad)
- Current in AC circuits:
 - $i(t) = I_{\max} \cos(\omega t + \theta_i)$
 - I_{\max} : amplitude (Amperes)
 - θ_i : phase angle of the voltage (rad)



Review of Electric Circuits

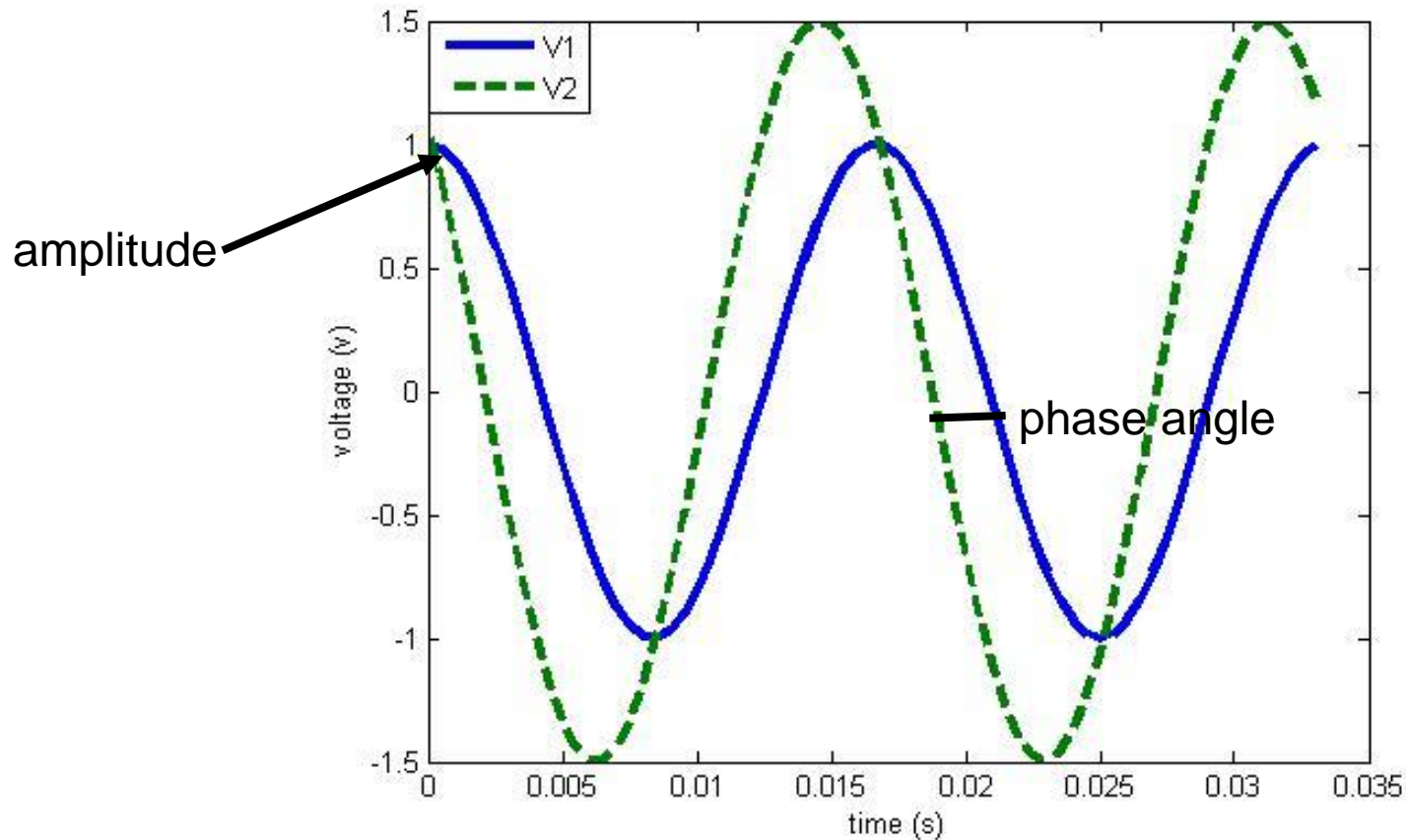

$$v_1(t) = 1.0 \cos(377t + 0^\circ) \quad v_2(t) = 1.5 \cos(377t + 45^\circ)$$



Review of Electric Circuits

- Conversion of radians (θ_{rad}) to degrees (θ_{deg})

$$\theta_{\text{deg}} = \theta_{\text{rad}} \frac{180^\circ}{\pi}$$

- Conversion of degrees to radians

$$\theta_{\text{rad}} = \theta_{\text{deg}} \frac{\pi}{180^\circ}$$



Review of Electric Circuits

- Frequency in North American power systems is 60 Hz
 - f : frequency (Hertz)
 - $\omega = 2\pi f \sim 377$ rad/sec
- Other parts of the world 50 Hz is common
- We assume 60 Hz unless otherwise noted
- Voltage waveform is set as a reference, so $\theta_V = 0^\circ$



Phasor Transform

- Shorthand for writing sinusoidal functions
- Used for steady-state calculations
- Contains **amplitude** and **phase angle** information
 - Assumed that frequency is known
- Relies on Euler's Identity

$$v(t) = v_{\max} \cos(\omega t + \theta_v) \longrightarrow \text{Phasor Transform} \longrightarrow \frac{V_{\max}}{\sqrt{2}} \angle \theta_v$$

Note: division by square root of 2
is used in power system analysis ("effective phasor")



Example

- Write the phasor representation of $v_1(t) = 1.41 \cos(377t + 0)$
- Write the phasor representation of $v_2(t) = 2.12 \cos(377t + 45)$
- Write the phasor representation of $v_3(t) = 1.41 \cos(t + 0)$



Example

- write the phasor representation of $v_1(t) = 1.41 \cos(377t + 0)$
- write the phasor representation of $v_2(t) = 2.12 \cos(377t + 45)$
- write the phasor representation of $v_3(t) = 1.41 \cos(t + 0)$

solution

$$\mathbf{v}_1 = 1\angle 0^\circ$$

solution

$$\mathbf{v}_2 = 1.5\angle 45^\circ$$

solution

$$\mathbf{v}_3 = 1\angle 0^\circ$$



Notation

- Lecture slides use bold uppercase variables (e.g. **V**, **I**) for phasors and other vectors
- Capital letters (e.g. V, I) or absolute values of phasors (**|V|**, **|I|**) are used to indicate the magnitude of the phasor
$$\mathbf{V} = V \angle \theta$$
- Lowercase variables (e.g. v, i) are preferred to represent scalars not associated with phasors and vectors
 - Notable exceptions P, Q for real and imaginary power



Phasor Transform

- We use the effective phasor because

$$P = v_{\text{rms}} i_{\text{rms}} \cos(\phi)$$

- So we can then write $P = VI \cos(\phi)$

- Unless otherwise specified, assume that voltages and currents are given in RMS and all phasors are "effective phasors"

- Also note:

$$e^{-j90^\circ} = \cos(-90^\circ) + j \sin(-90^\circ) = j \sin(-90^\circ) = -j$$

where j is the imaginary operator $j = \sqrt{-1}$



Phasor Transform

- Different expressions of a voltage phasor

$$\frac{V_{\max}}{\sqrt{2}} \angle \theta_v = V_{\text{rms}} \angle \theta_v = |\mathbf{V}| \angle \theta_v = V \angle \theta_v = \mathbf{V} e^{j\theta_v}$$

- Current:

$$\frac{I_{\max}}{\sqrt{2}} \angle \theta_i = I_{\text{rms}} \angle \theta_i = |\mathbf{I}| \angle \theta_i = I \angle \theta_i = \mathbf{I} e^{j\theta_i}$$

- Impedance:

$$|\mathbf{Z}| \angle \theta_z = Z \angle \theta_z = \mathbf{Z} e^{j\theta_z}$$


- Define: $\phi \triangleq \theta_v - \theta_i$ (remember this!)



Phasors

Phasors have a direct geometric interpretation

- Polar form

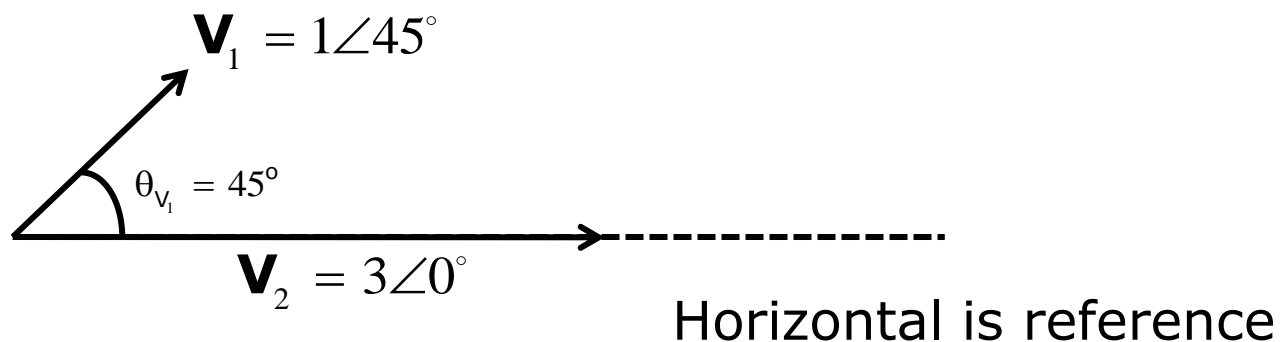




Phasors

- Another way of specifying phasors is in rectangular form
 - Let the Y-axis be the imaginary (j) axis
 - Let the X-axis be the real axis
- Resolving into real and imaginary components


$$\mathbf{V}_1 = 1\angle 45^\circ = 0.707 + j0.707$$
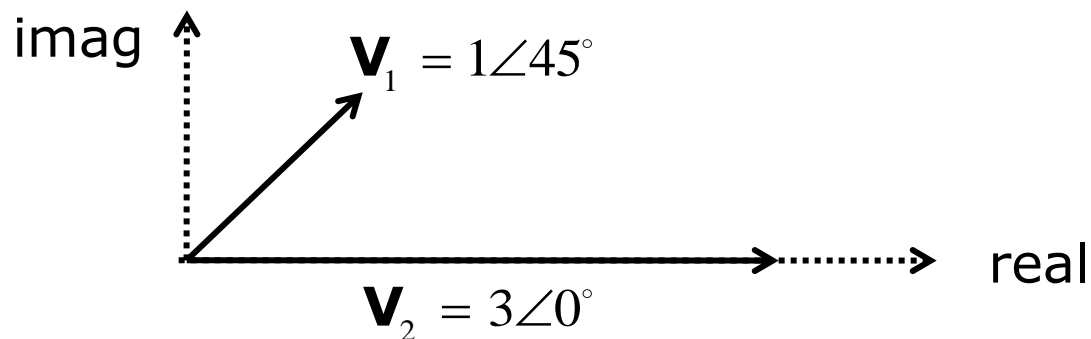
$$\mathbf{V}_2 = 3\angle 0^\circ = 3 + j0$$





Phasors

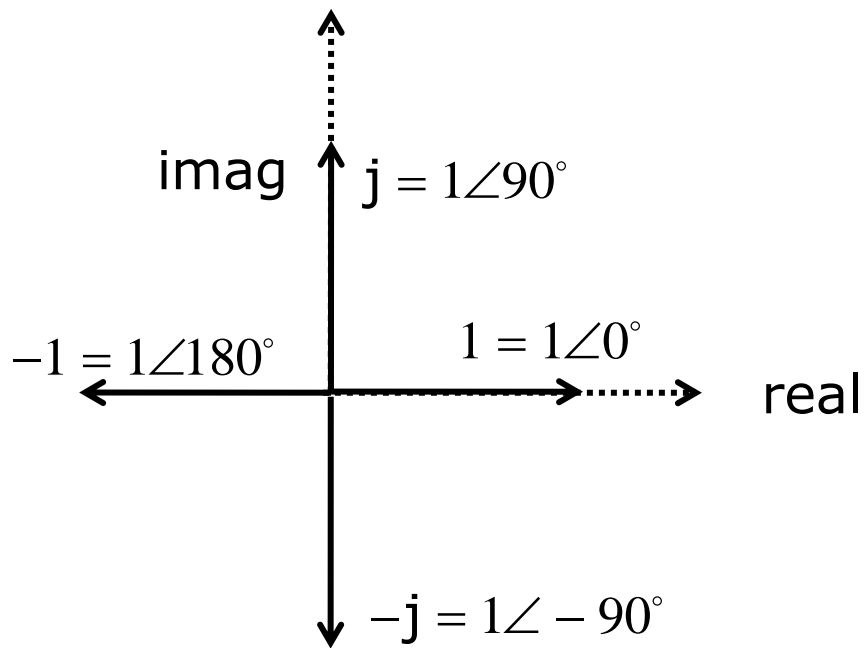




Addition of Phasors

- Addition and subtraction of phasors are simple using rectangular form
 - Simply add/subtract the real values and add/subtract the imaginary values

$$\mathbf{V}_3 = \mathbf{V}_1 + \mathbf{V}_2 = 3.707 + j0.707$$

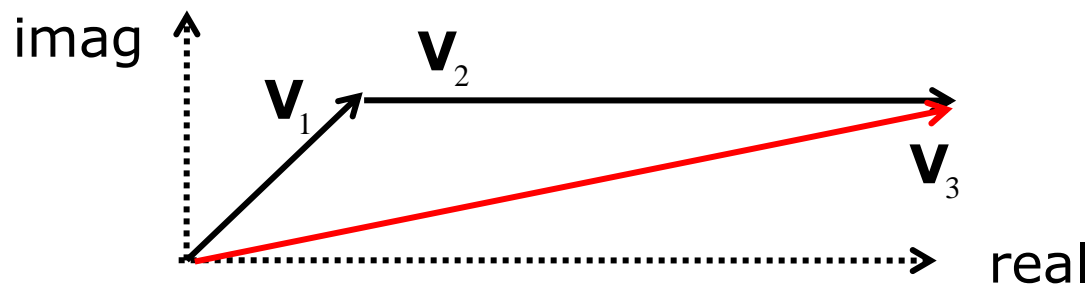Addition is "tip to tail"
Subtraction is "tail to tip"





Multiplication of Phasors


- Multiplication and division are easier in polar form
 - For multiplication: multiply magnitudes, add angles
 - For division: divide magnitudes, subtract angles

$$\mathbf{V}_4 = \mathbf{V}_1 \mathbf{V}_2 = (1\angle 45^\circ)(3\angle 0^\circ)$$

$$\mathbf{V}_4 = 3\angle 45^\circ$$

← add angles

multiply magnitudes

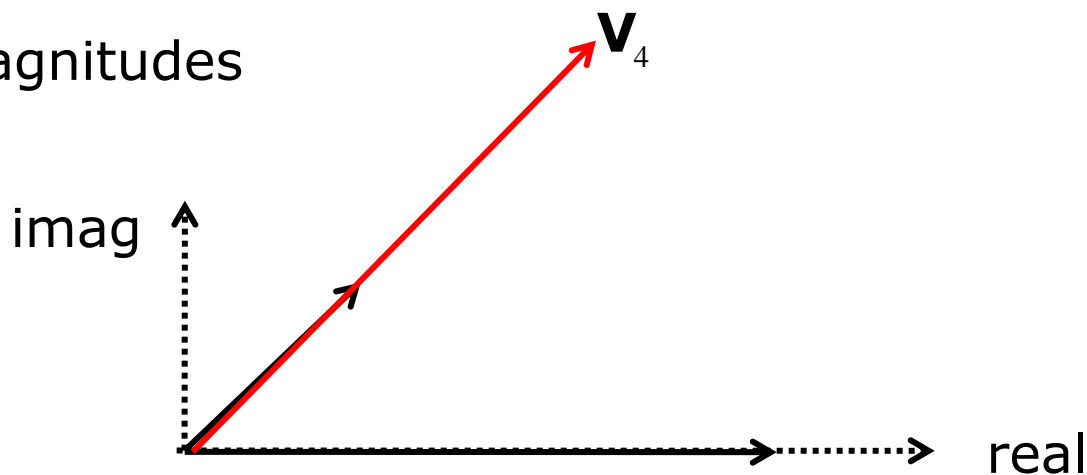



Example

If $\mathbf{v} = 1\angle 10^\circ$, what is $j\mathbf{v}$?

A. $1\angle 10^\circ$

B. $1\angle 100^\circ$

C. $1\angle 190^\circ$

D. 0



Example

If $\mathbf{v} = 1\angle 10^\circ$, what is $j\mathbf{v}$?

A. $1\angle 10^\circ$

B. $1\angle 100^\circ$

C. $1\angle 190^\circ$

D. 0

$$j\mathbf{v} = (1\angle 90^\circ)(1\angle 10^\circ) = 1\angle 100^\circ$$




Phasors

- Another way of specifying phasors is in rectangular form
 - Let the Y-axis be the imaginary (j) axis
 - Let the X-axis be the real axis
- Resolving into real and imaginary components

$$\mathbf{V}_1 = 1\angle 45^\circ = 0.707 + j0.707$$
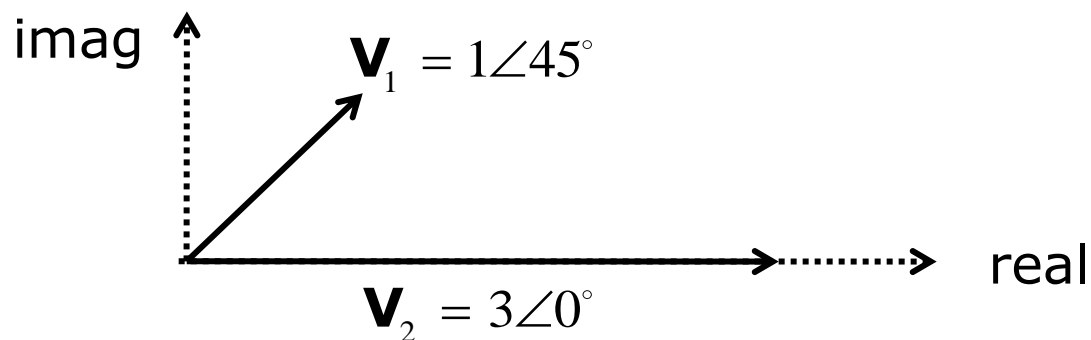
$$\mathbf{V}_2 = 3\angle 0^\circ = 3 + j0$$





Phasor Analysis of Resistors

- For resistors

$$i(t) = i_{\max} \cos(\omega t + \theta_i)$$

$$v(t) = i(t)R$$


$$v(t) = Ri_{\max} \cos(\omega t + \theta_i)$$

- Transforming into phasor form:

$$\mathbf{V} = R\mathbf{I}e^{j\theta_i}$$

$$\mathbf{V} = R\mathbf{I}$$

Voltage and current are in phase

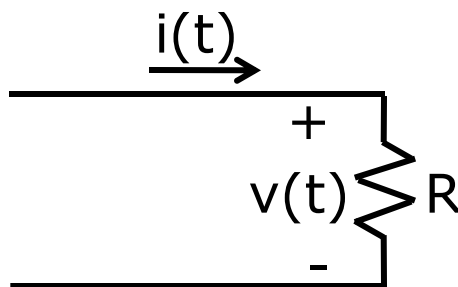



Phasor Analysis of Inductors

- For inductors

$$i(t) = i_{\max} \cos(\omega t + \theta_i)$$

$$v(t) = L \frac{di}{dt}$$

$$v(t) = -L\omega i_{\max} \sin(\omega t + \theta_i) = -L\omega i_{\max} \cos(\omega t + \theta_i - 90^\circ)$$


- Transforming into phasor form:

$$v(t) = -L\omega i_{\max} \cos(\omega t + \theta_i - 90^\circ)$$

$$\Rightarrow \mathbf{V} = -L\omega \mathbf{I} e^{j\theta_i} e^{-j90^\circ}$$

$$\mathbf{V} = jL\omega \mathbf{I} e^{j\theta_i} = jL\omega \mathbf{I}$$

$$\text{using } e^{j-90^\circ} = -j$$

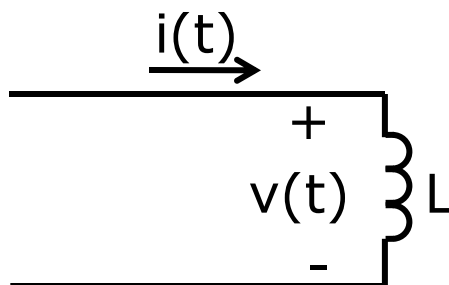



Phasor Analysis

$$\mathbf{V} = j\omega L\mathbf{I}$$

- Define $X_L = \omega L$ (inductive reactance)
- Therefore
 - $\mathbf{V} = jX_L\mathbf{I}$ **\mathbf{I} lags \mathbf{V} by 90 deg.**
- A similar derivation for capacitors yields
 - $X_C = 1/(\omega C)$ (capacitive reactance)
 - $\mathbf{V} = -jX_C\mathbf{I}$ **\mathbf{I} leads \mathbf{V} by 90 deg.**



Phasor Analysis

- We can rewrite Ohm's Law to include complex impedances
- **$\mathbf{V} = \mathbf{IZ}$**
 - **\mathbf{Z}** : complex impedance (Ohms)
 - **$\mathbf{Z} = R + jX_L - jX_C$** (if in series)
 - **$1/\mathbf{Z} = 1/R + j/X_L - j/X_C$** (if in parallel)
- **\mathbf{Z}** will have a magnitude and phase associated with it **$\mathbf{z} = Z\angle\theta_z$**



Complex Power

P is also known as Real Power, Active Power, Average Power

$$P = |\mathbf{V}_s| |\mathbf{I}| \cos(\phi)$$

$$P = \operatorname{Re} \{ \mathbf{V} \mathbf{I}^* \}$$

* is the complex conjugate operator,
it denotes a change in sign of the imaginary part

Conjugation is needed so that the difference in phase between voltage and current is considered, rather than their sum



Complex Power

- Let **S** be the complex power defined as

$$\mathbf{S} = \mathbf{VI}^*$$

then

$$P = \operatorname{Re}\{\mathbf{VI}^*\} = \operatorname{Re}\{\mathbf{S}\}$$

- Let Q be the reactive power defined as

$$Q = \operatorname{Im}\{\mathbf{VI}^*\}$$

- Then

$$Q = \operatorname{Im}\{\mathbf{S}\}$$

- And therefore:

$$\mathbf{S} = P + jQ$$

Q is also known as
imaginary power

S is also known as
apparent power



Complex Power


- Technically, units of \mathbf{S} , Q and P are watts*
- To avoid confusion, alternate units are used in practice
 - S : Volt-Amps (VA)
 - Q : Volt-Amps Reactive (VAR)
- Inductors, capacitors consume/supply reactive power, Q
- S and Q are defined values
 - a meaningful physical interpretation is elusive

*See C. Gross "On VA's, VAR's, and Other Traditions in Electric Power Engineering"



Power Triangle

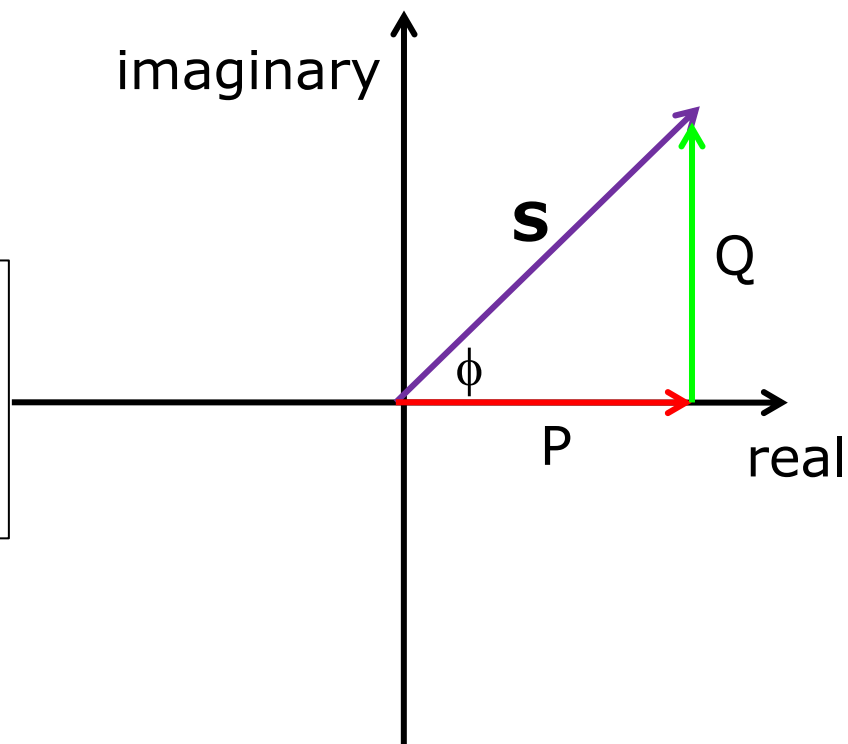- Relationships between \mathbf{S} , P and Q can be shown graphically
- $\mathbf{S} = P + jQ$




Note:
 P , Q are scalars
representing the real
and imaginary parts
of \mathbf{S}



Power Triangle


- Consider $P = |\mathbf{V}||\mathbf{I}|\cos(\phi)$
- Since $|\mathbf{S}| = |\mathbf{VI}^*| = |\mathbf{VI}| = |\mathbf{V}||\mathbf{I}|$
- Then $P = |\mathbf{S}|\cos(\phi)$
 - P is the projection of S onto the real axis

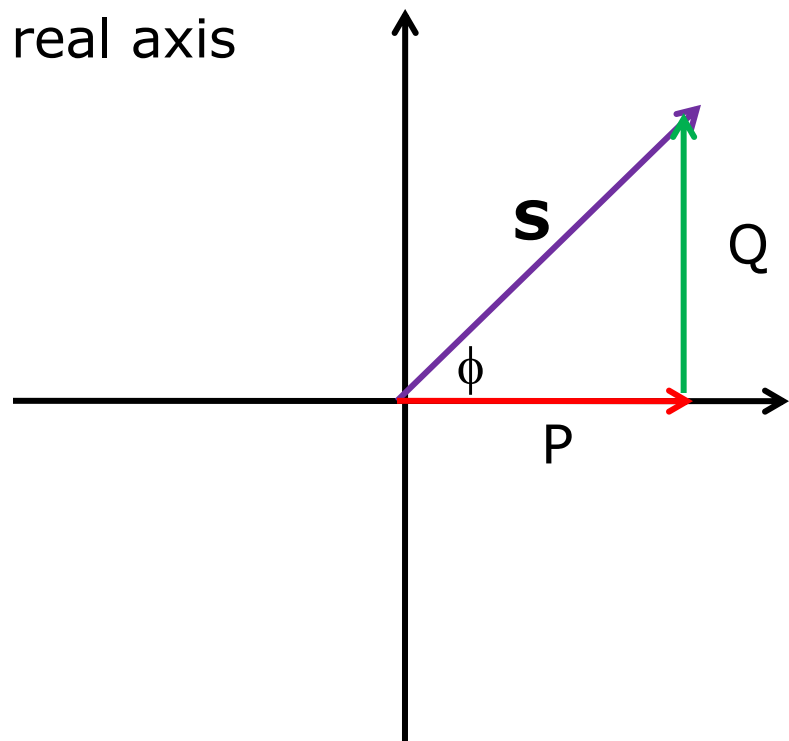



Complex Power

- A similar result can be found for Q
 - $P = |\mathbf{S}|\cos(\phi)$
 - $Q = |\mathbf{S}|\sin(\phi)$
- Q is the projection of \mathbf{S} onto the imaginary axis

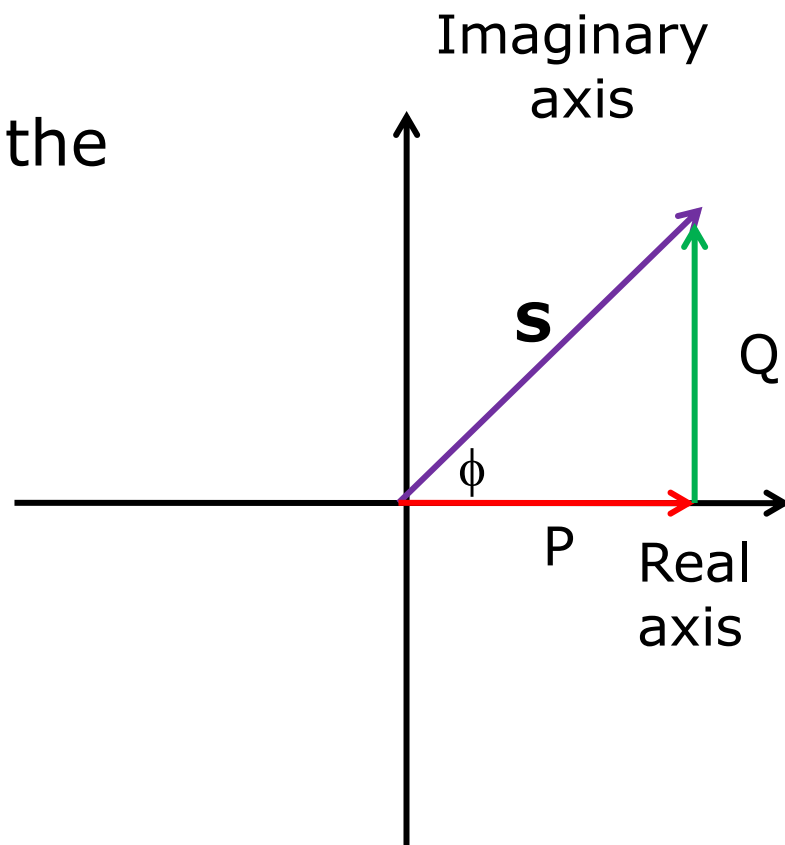



Complex Power Cheat Sheet

$$P = \operatorname{Re}\{\mathbf{V}\mathbf{I}^*\}$$
$$= \operatorname{Re}\{\mathbf{I}\mathbf{Z}\mathbf{I}^*\} = |\mathbf{I}|^2 \operatorname{Re}\{\mathbf{Z}\}$$

$$P = |\mathbf{I}|^2 R$$

$$P = |\mathbf{V}| |\mathbf{I}| \cos \phi$$

$$P = |\mathbf{I}|^2 |\mathbf{Z}| \cos \phi$$

$$Q = \operatorname{Im}\{\mathbf{V}\mathbf{I}^*\}$$

$$Q = |\mathbf{I}|^2 X$$

$$Q = |\mathbf{V}| |\mathbf{I}| \sin \phi$$

$$Q = |\mathbf{I}|^2 |\mathbf{Z}| \sin \phi$$

$$\mathbf{S} = P + jQ$$


$$\phi = \tan^{-1}\left(\frac{Q}{P}\right)$$

$$\cos \phi = \frac{P}{\sqrt{P^2 + Q^2}}$$



Power Factor

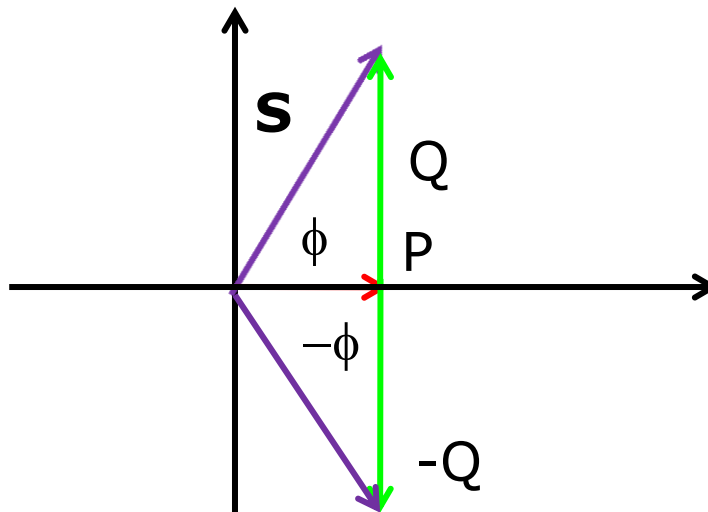- Power factor is non-negative
- $\cos(\phi) = \cos(-\phi)$
- Need to distinguish between ϕ and $-\phi$





Power Factor


- For example let $\theta_v = 0^\circ$
 - Case 1: $\theta_i = 30^\circ$
 - Capacitive circuit
 - PF = 0.866
 - Case 2: $\theta_i = -30^\circ$
 - Inductive circuit
 - PF = 0.866
- ← Same power factor



Leading/Lagging Power Factor

Must describe the PF value along with whether the current leads or lags voltage

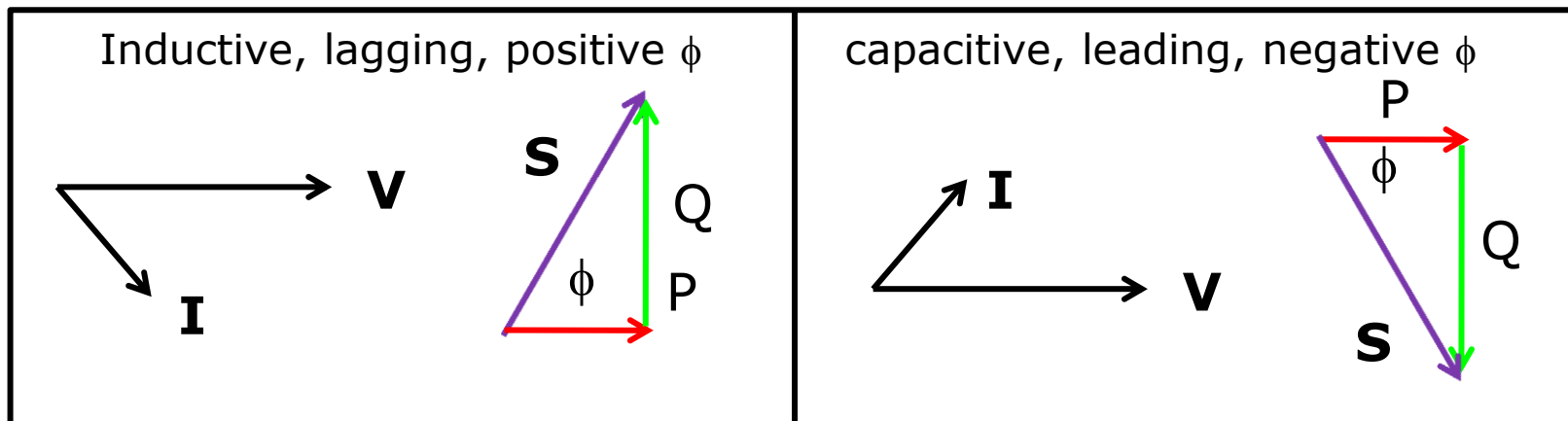- Lagging: current **lags** voltage (inductive)
- Leading: current **leads** voltage (capacitive)
- Useful mnemonic: ELI the ICE man





Why are Inductive Circuits Lagging?

Recall

$$\mathbf{V} = jX_L \mathbf{I}$$

$$\mathbf{I} = \mathbf{V} / (jX_L) = -j\mathbf{V} / X_L$$


$$\mathbf{S} = \mathbf{V} \mathbf{I}^*$$



therefore

$$\mathbf{I}^* = j\mathbf{V}^* / X_L$$

$$\mathbf{S} = j\mathbf{V}\mathbf{V}^* / X_L = j|\mathbf{V}|^2 / X_L$$

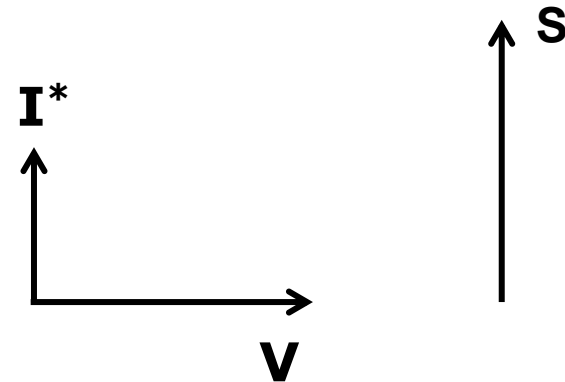

angle is always +90 degrees
for purely inductive circuits




Leading/Lagging Power Factor

- Similar result for capacitive circuits
 - $\mathbf{S} = -j|\mathbf{V}|^2/X_C$
- Note:
 - the presence of resistance does not affect whether or not a circuit is leading or lagging, but it does affect the magnitude of the power factor
 - circuits with L and C (or L, C and R) must be analyzed before leading or lagging can be determined



Phasor Analysis

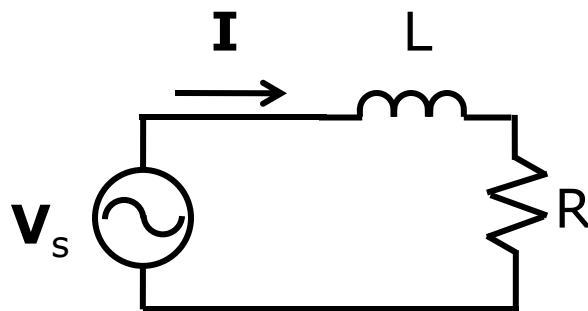
- Find the current out of the source, the power out of the source, and power consumed by the resistor assuming:
 - $V_s = 120$ Volts at 60 Hz
 - $L = 0.01$ Henry
 - $R = 10$ Ohms





Phasor Analysis

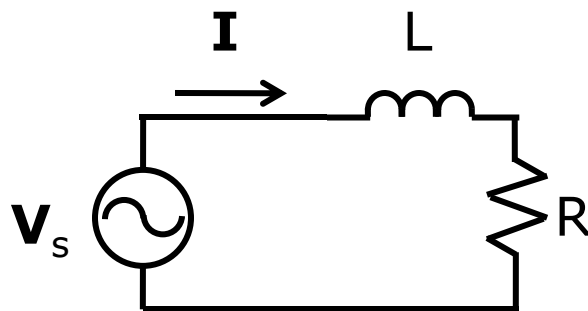- $V_s = 120$ Volts (RMS) at 60 Hz
- $L = 0.01$ Henry
 - $jX_L = j\omega L = j(60 \times 2\pi) \times 0.01 = j3.77$
- $R = 10$ Ohms





Phasor Analysis


$$\mathbf{Z} = (3.77j + 10) = \sqrt{3.77^2 + 10^2} \angle \tan^{-1} \left(\frac{3.77}{10} \right)$$

$$\mathbf{Z} = 10.69 \angle 20.7^\circ \Omega$$

$$\mathbf{V}_s = \mathbf{I}\mathbf{Z}$$

$$\mathbf{I} = \frac{120 \angle 0^\circ}{10.69 \angle 20.7^\circ} = 11.22 \angle -20.7^\circ \text{ A}$$

phasor diagram

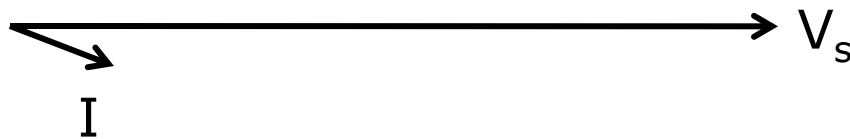



Phasor Analysis


- Power from the source

$$P = |\mathbf{V}_s| |\mathbf{I}| \cos(\phi) = (120)(11.22) \cos(20.7^\circ) = 1.26\text{kW}$$

- Power consumed by the load resistor

$$P = |\mathbf{I}|^2 R = 11.22^2 \times 10 = 1.26\text{kW}$$

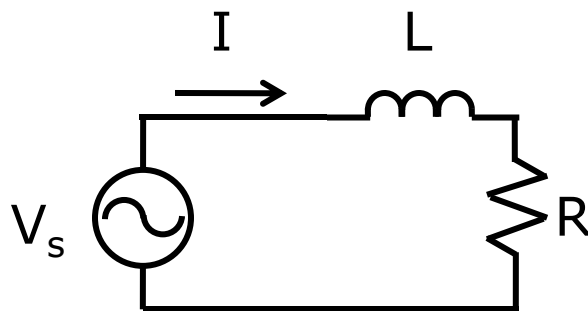
- The inductor does not consume any power P





Summary

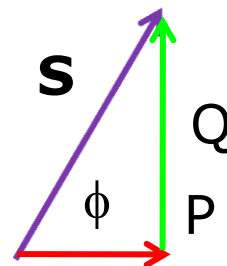- P , Q , \mathbf{S} related by power triangle



- P has a physical interpretation, Q and \mathbf{S} do not
- \mathbf{S} is a vector, Q and P are scalars
- Resistors associated with P ; inductors/capacitors associated with Q