

11-Inverters, Interconnection and Other Considerations

ECEGR 4530

Renewable Energy Systems





Overview

- Inverters
- Grid-Tied Considerations
- PV Panel Discharge Protection
- PV Shading



Inverters

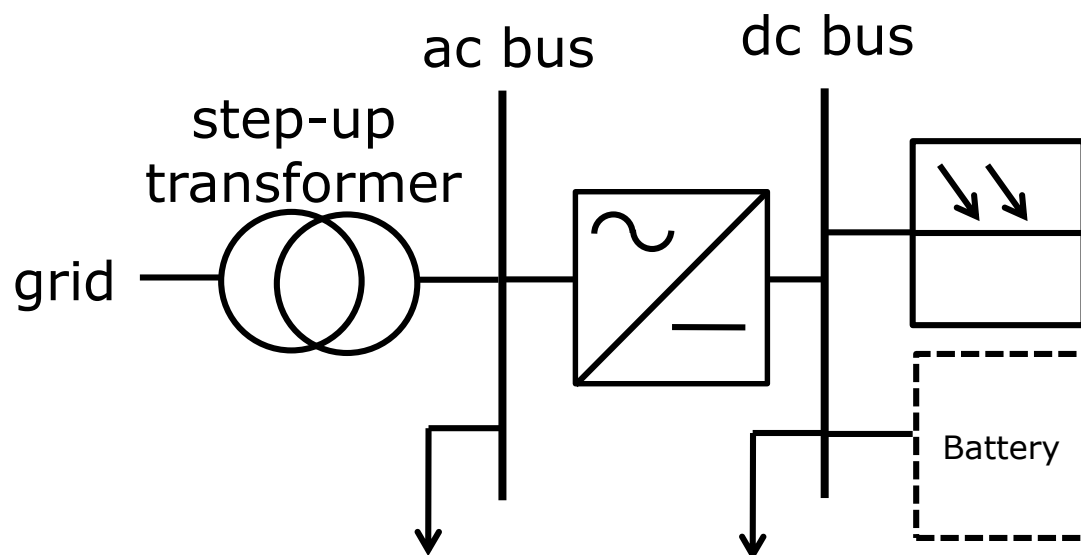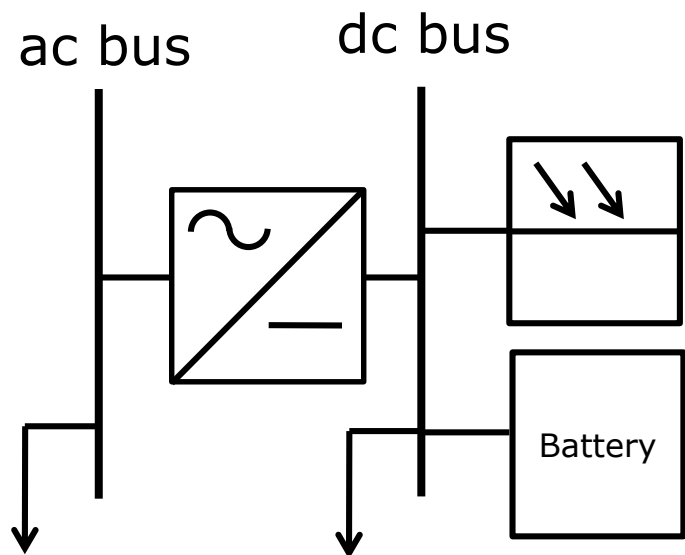- Inverters are required in stand-alone systems if AC load is to be served OR
- If the systems is grid connected




Consider Stand-alone inverters first



Inverter

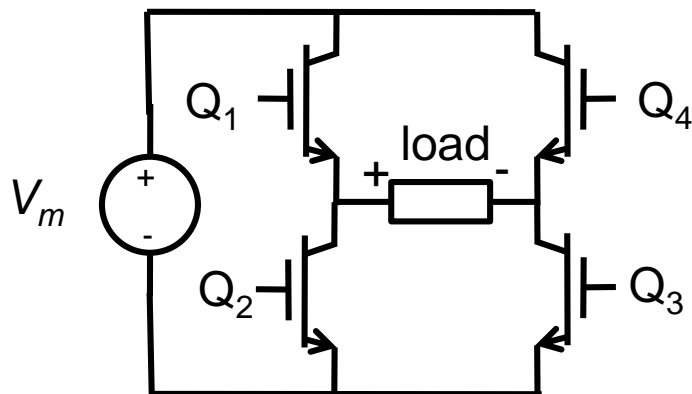
- Power MOSFETs or SCRs (Silicon-Controlled Rectifier) used as switches
- Full-bridge inverter
- Square wave inverter switching pairs
 - Q_1, Q_3
 - Q_2, Q_4
- To avoid a dc offset, duty ratio of each switch = 0.50





Inverter

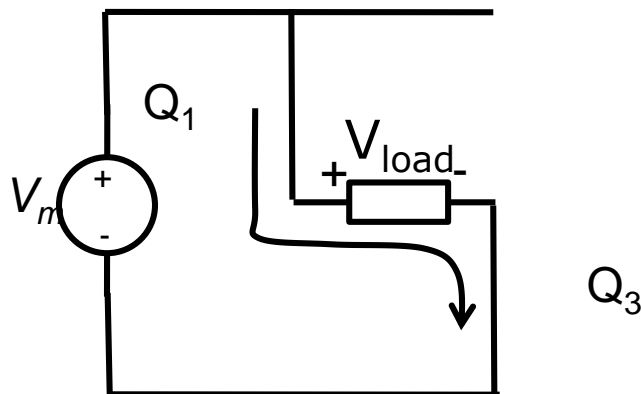
- When $Q_1 = Q_3 = 1$
 - $Q_2 = Q_4 = 0$
- Positive voltage applied to load
- Positive current flows






Inverter

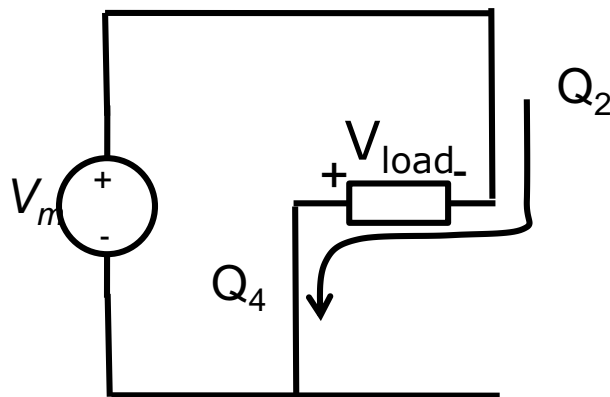- When $Q_2 = Q_4 = 1$
 - $Q_1 = Q_3 = 0$
- Negative voltage applied to load
- Negative current flows






Inverter

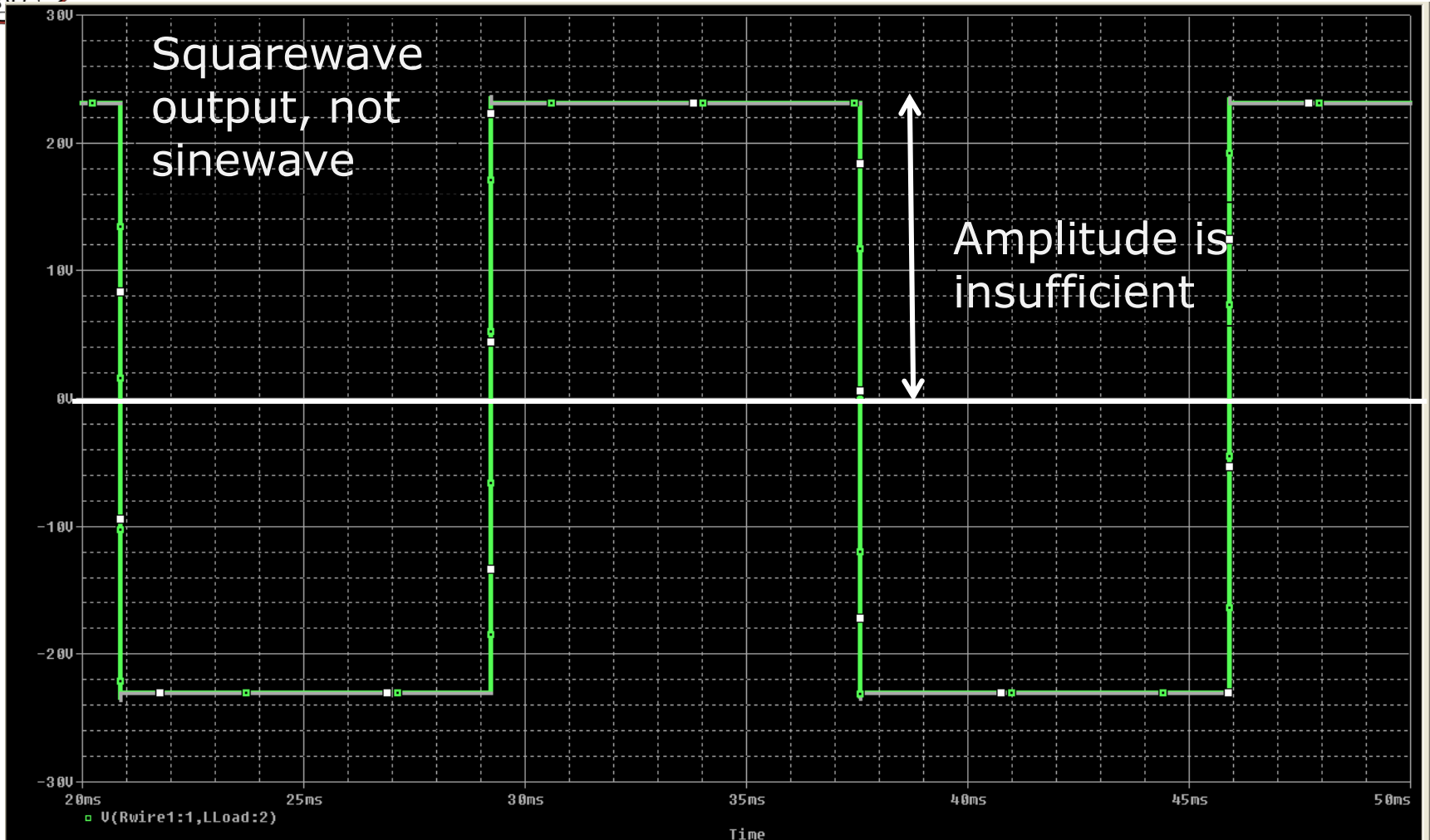




Inverter

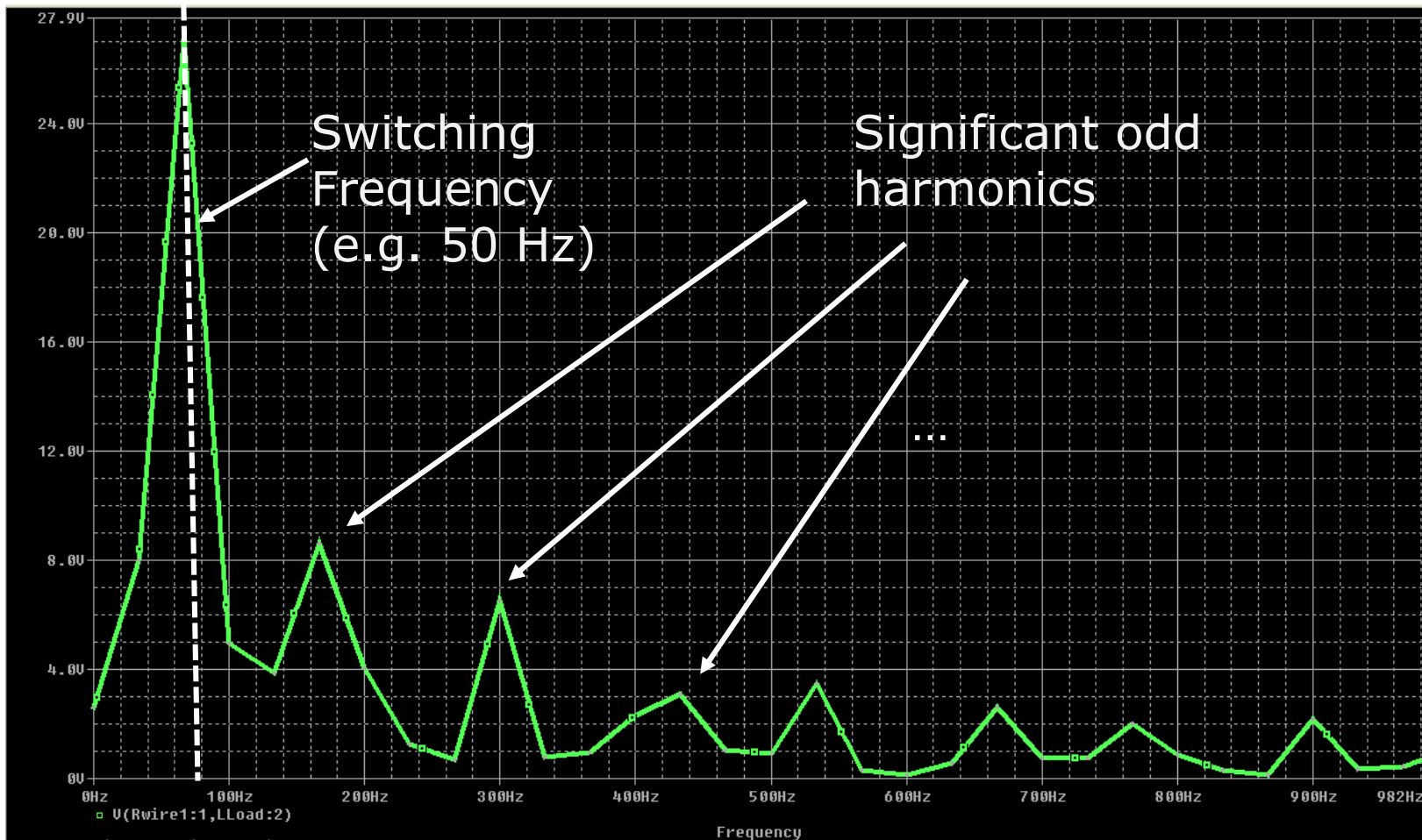




Squarewave Inverter

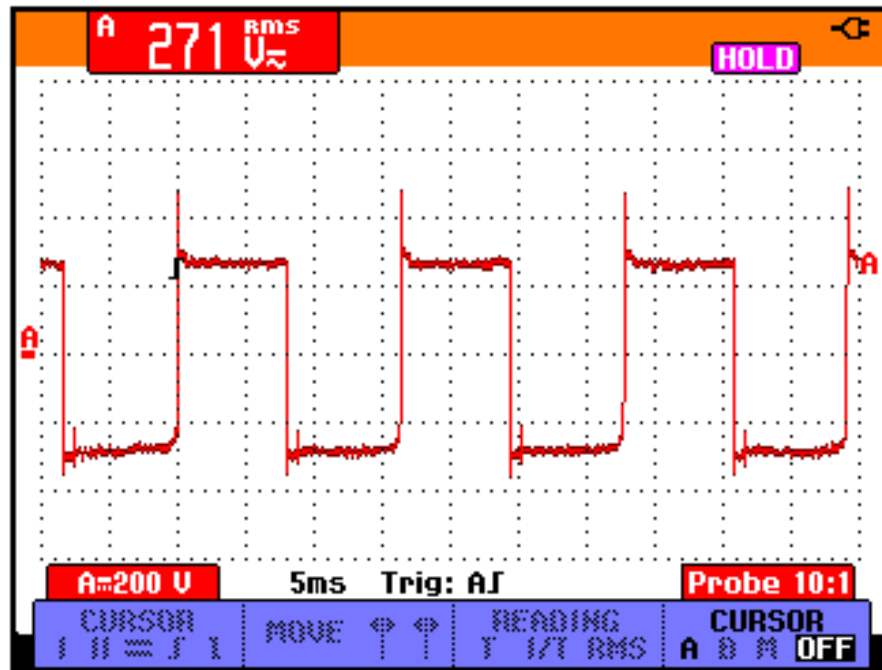




Poor Voltage Regulation

$$V_{\text{batt}} = 12.4$$

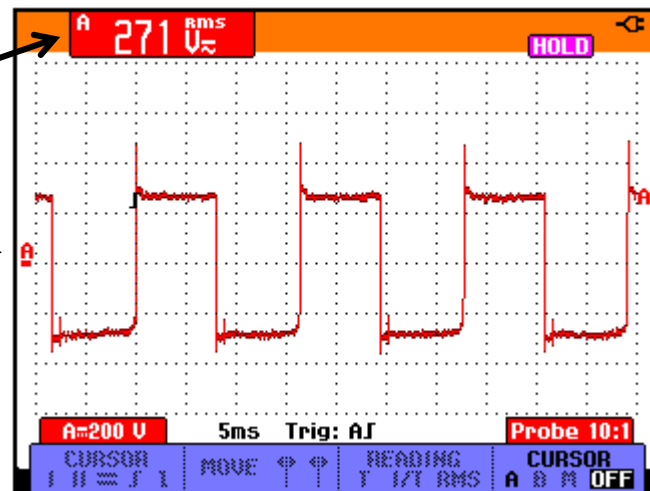

$$V_{\text{batt}} = 9$$

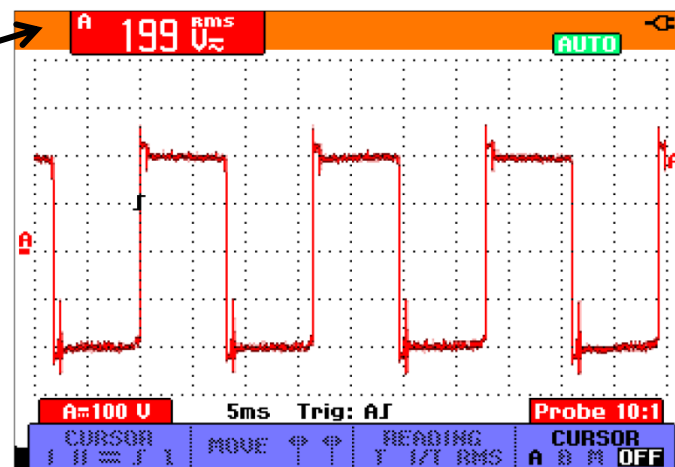



Inverter

- MPPT can be used between PV and inverter
- Voltage can be stepped up to 120 Vac using a transformer
- Some ac loads can handle “dirty” power, many cannot



Inverter

- Full bridge inverter output may be filtered to better approximate a sine wave
 - Significant harmonics are close to fundamental
 - Large capacitor is required
- A better approach is to use pulse width modulation (PWM) to control the switches




PWM Inverter

- Switching frequency should be much greater (4kHz - 10kHz) than fundamental frequency (60 Hz or 50 Hz)
- Basic idea: vary the duty ratios within each switching period to replicate a sine wave




PWM Inverter

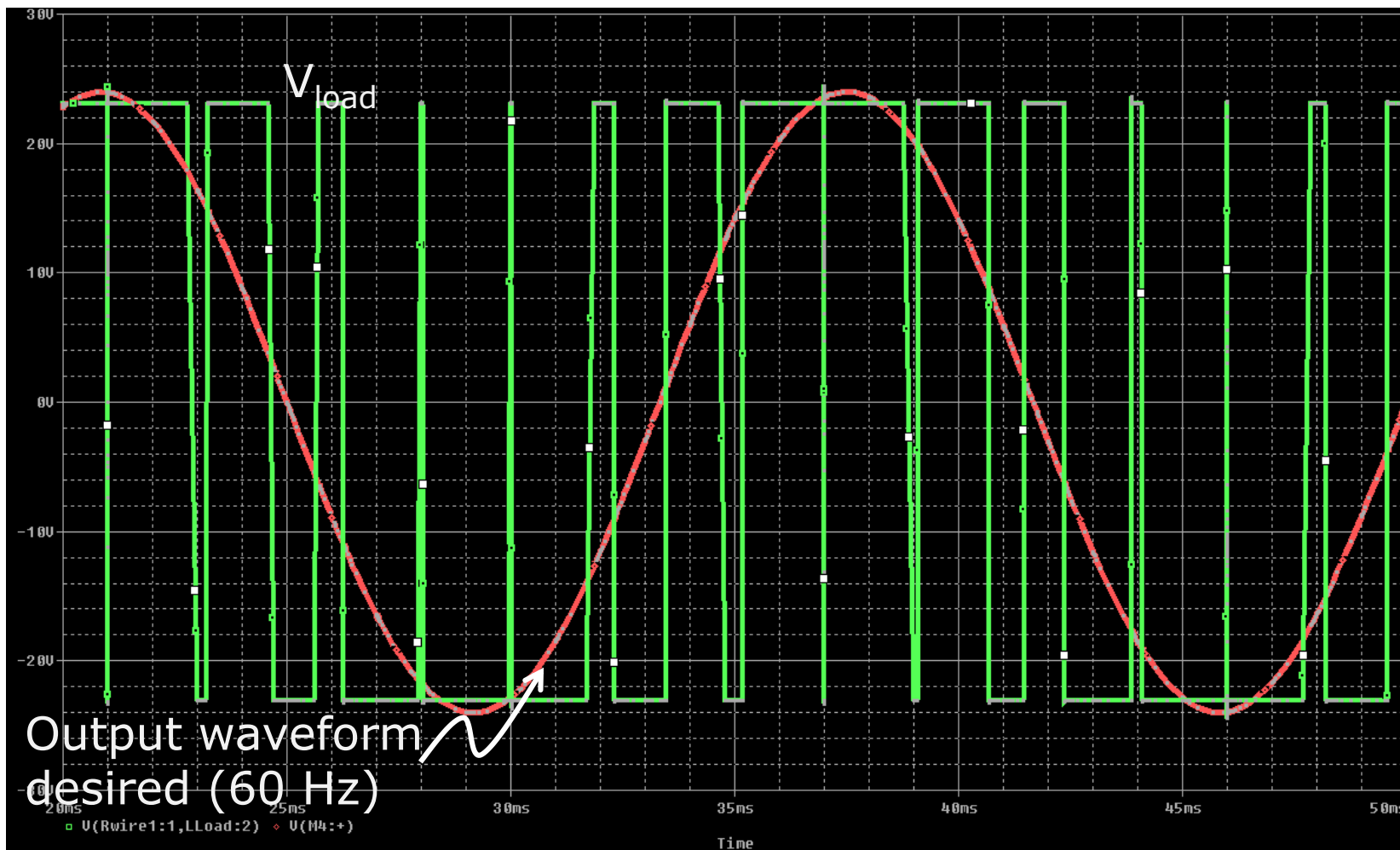




PWM Inverter

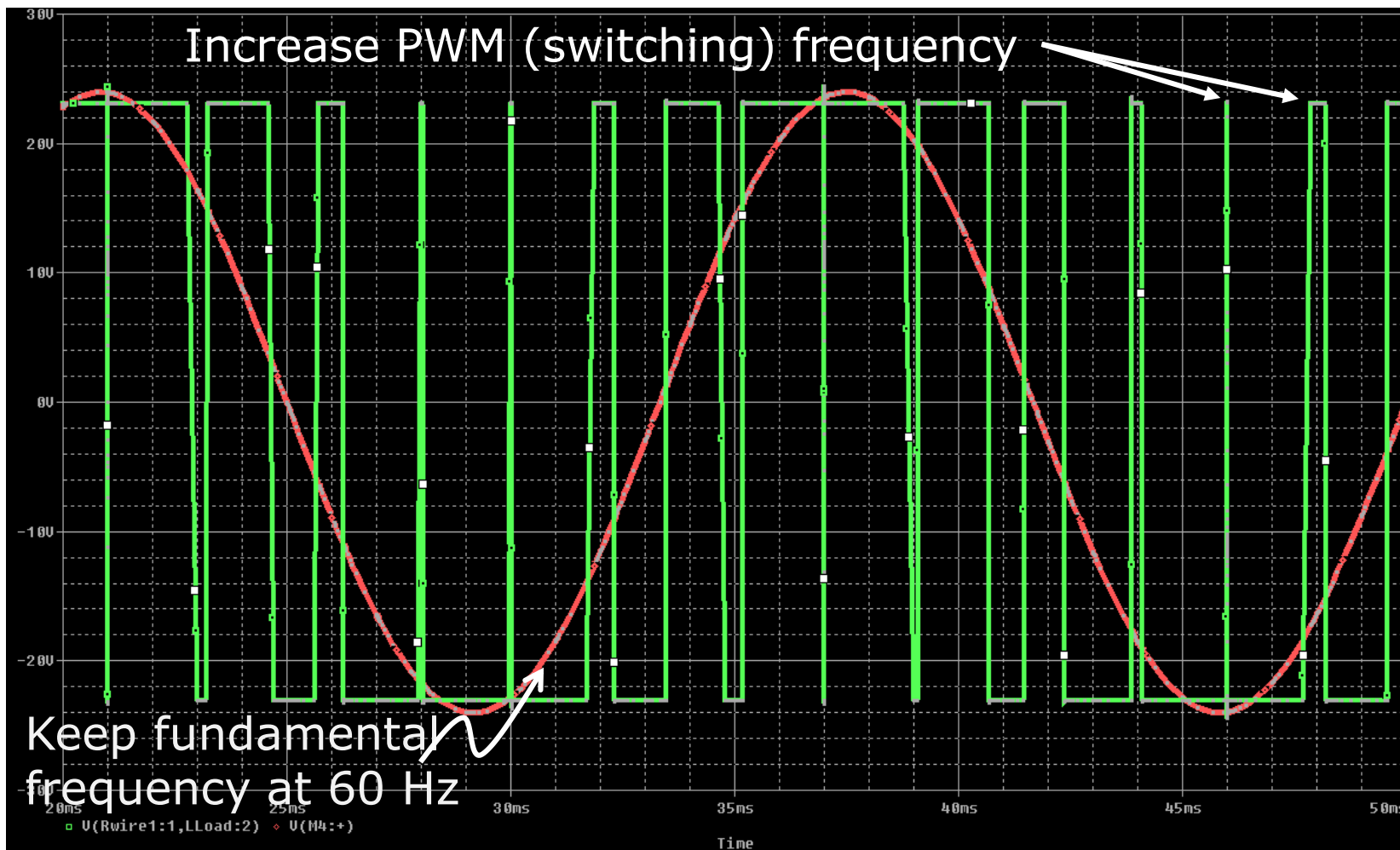



PWM Inverter

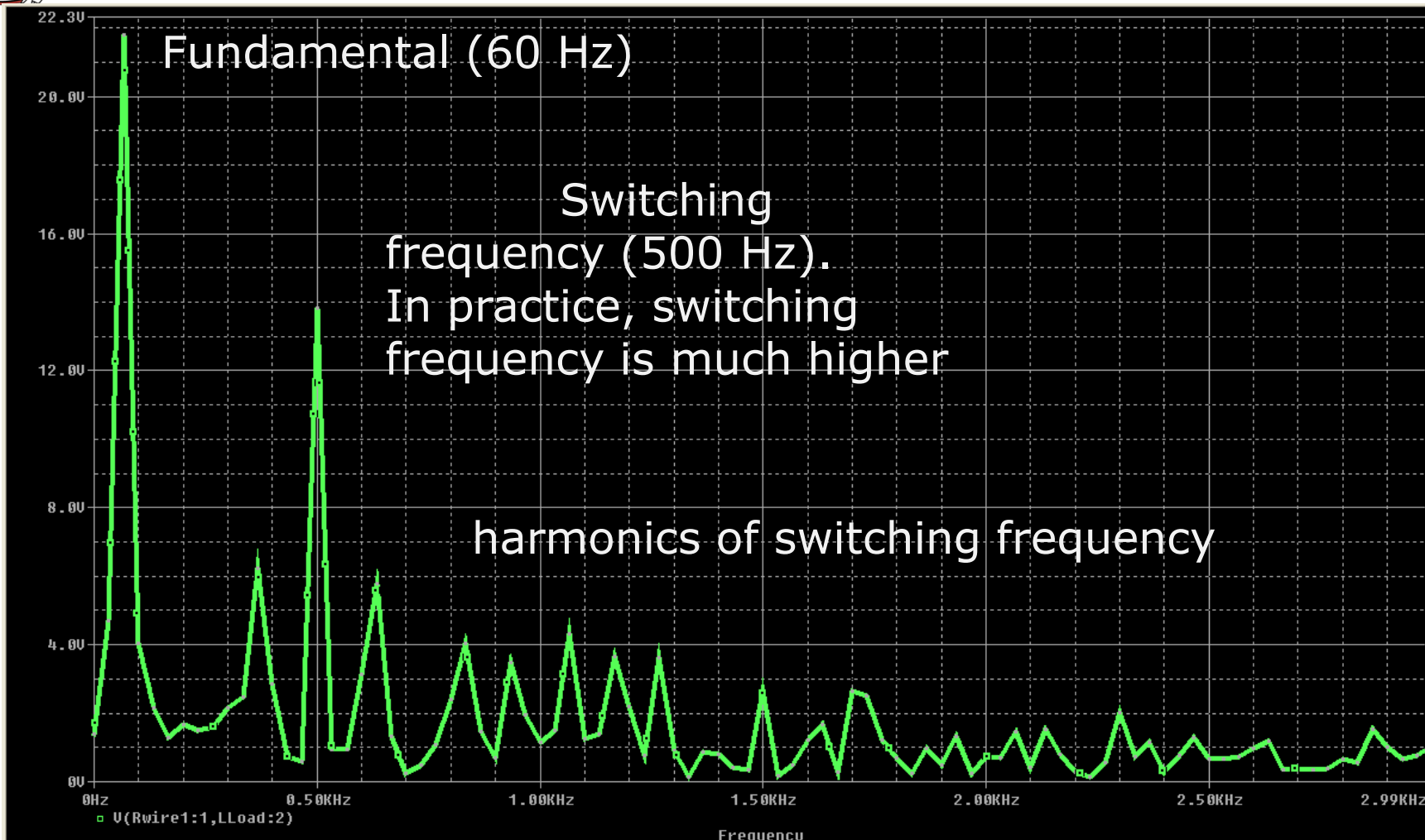




PWM Inverter

- Use a low-pass filter to remove frequency components greater than the switching frequency
- Result should closely approximate a sine wave




PWM Inverter

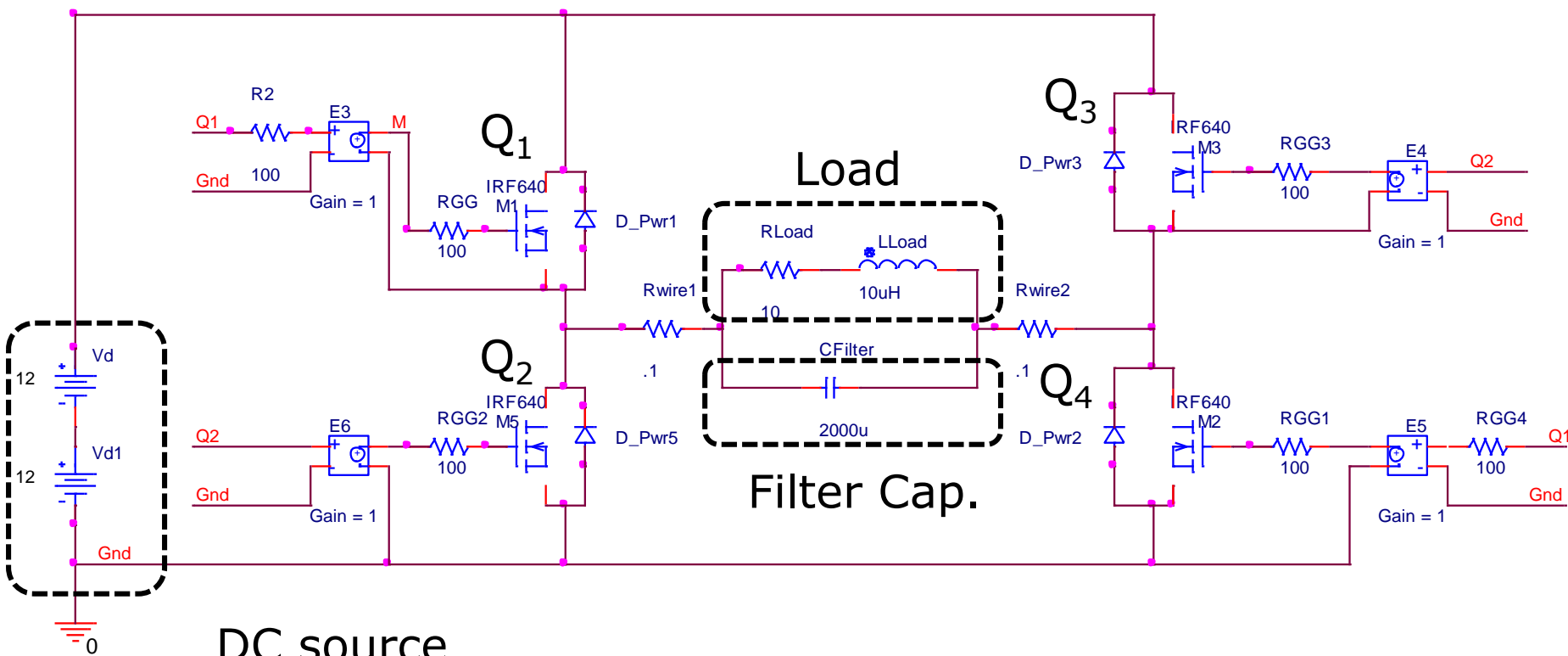

DC source
(Battery or PV with MPPT
or capacitor DC link)




PWM Inverter

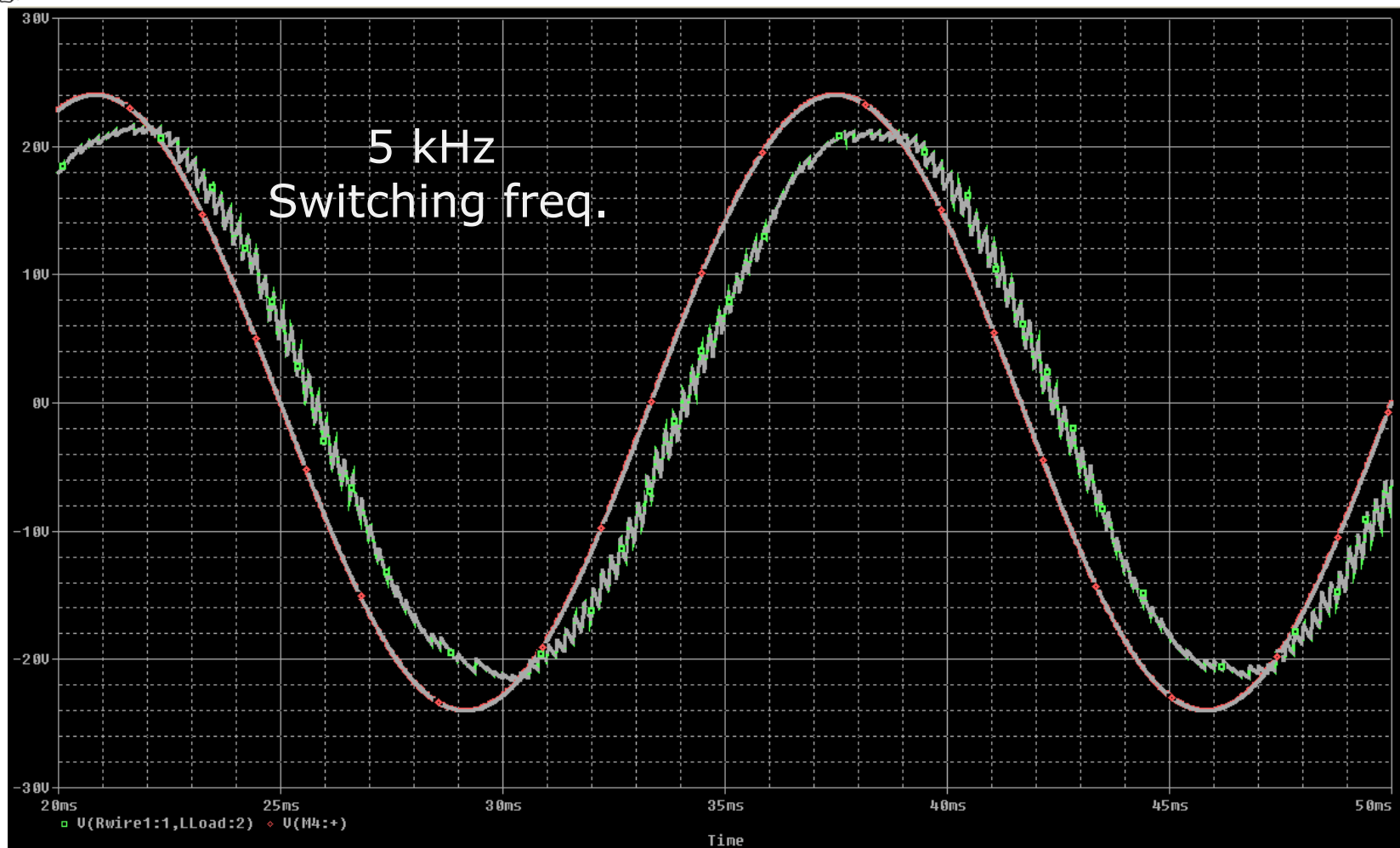




PWM Inverter

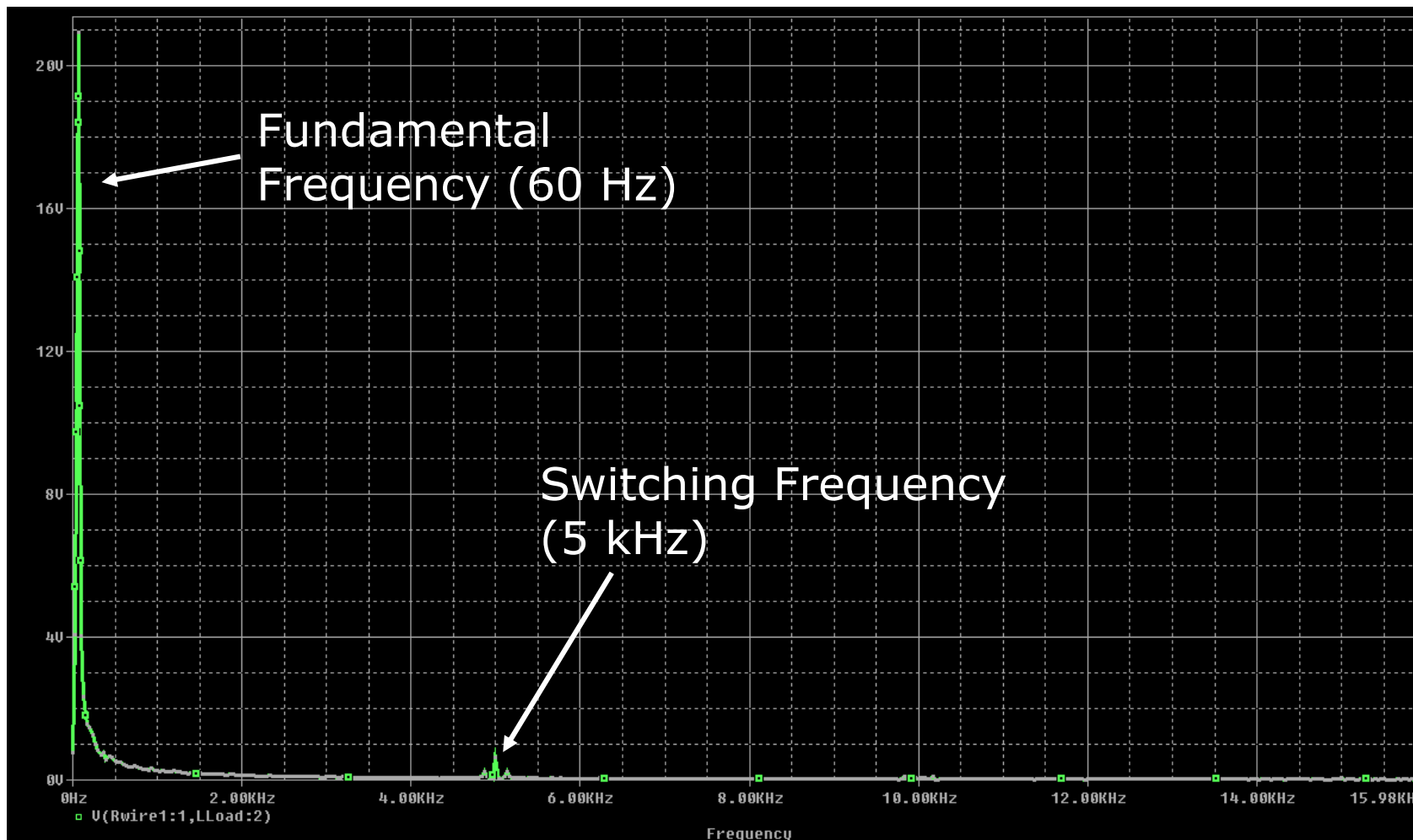




PWM Inverter

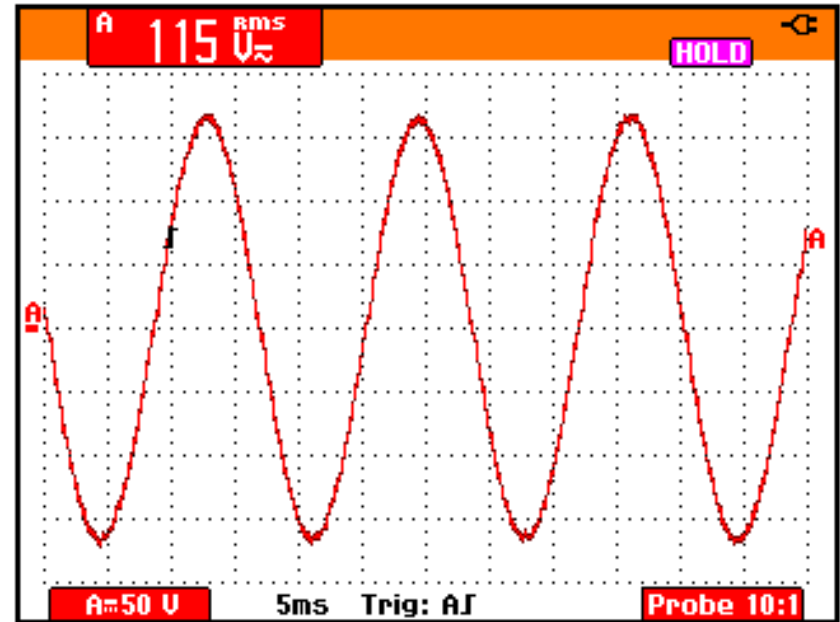



Grid Connected System

- Now connect to the grid

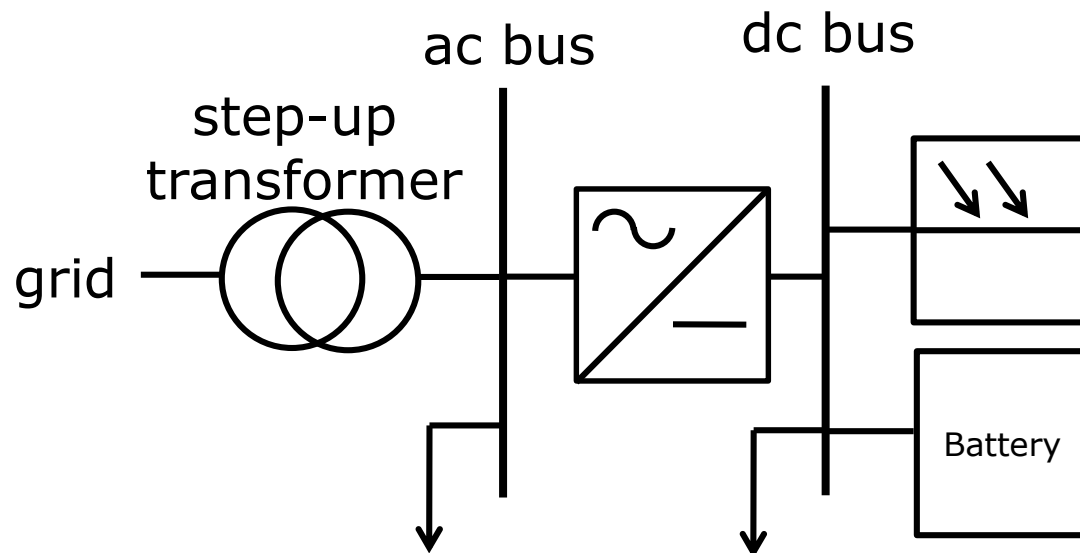




Inverters

- Inverters tied to the grid require special performance characteristics
 - Must be able to synchronize with the grid
 - Closely follow voltage amplitude AND frequency
 - Must disconnect if the grid losses power
 - Must have acceptable power quality



Grid Connection

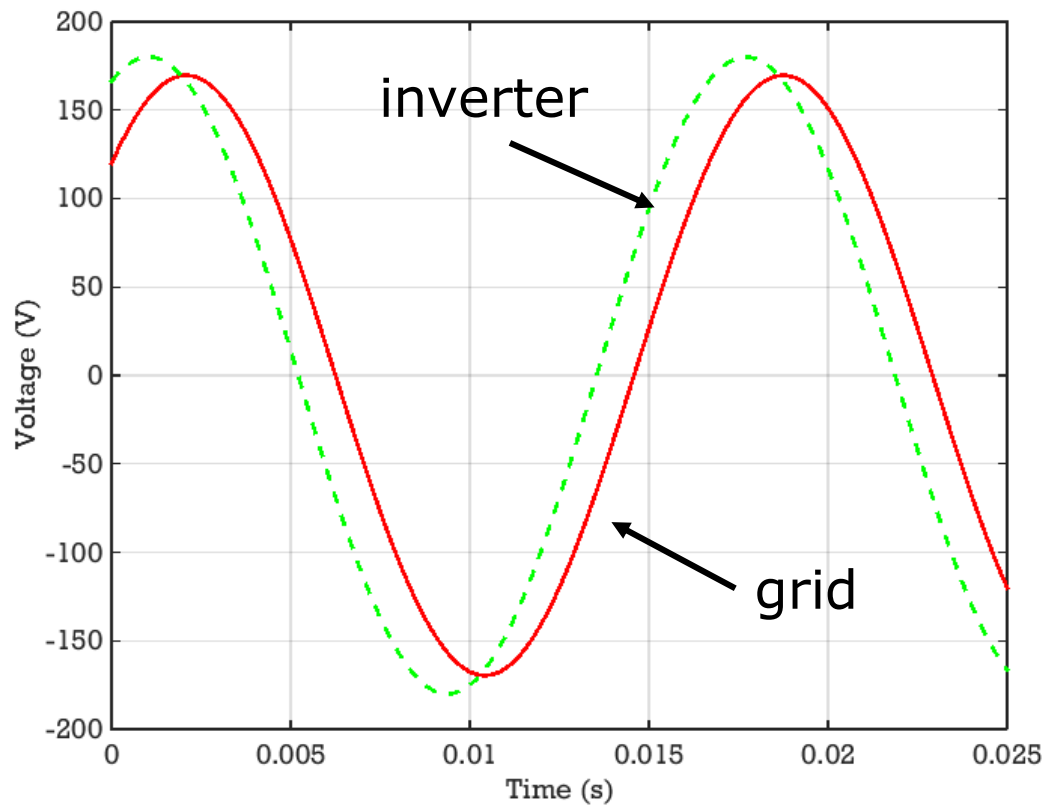


By adjusting the timing (phase) of the inverter switching, it is possible to make inverter voltage lead or lag grid Voltage, as well as make the magnitude larger or smaller.



Grid Connection

- Consider the output of a PV inverter with voltage \mathbf{V}_{inv}
- Assume that \mathbf{V}_{inv} is controllable within the limits of the inverter:
 - $|\mathbf{V}_{inv}|$, θ_{inv} , ω_{inv} are controllable
- The grid voltage is fixed \mathbf{V}_{grid}
- The distribution line connecting the inverter to the grid is $Z = R + jX$, with $X \gg R$

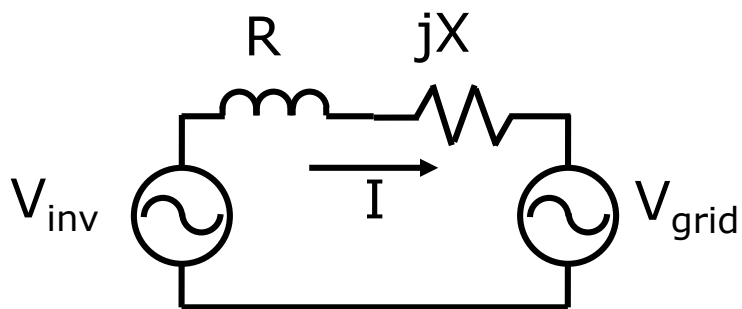




Grid Connection

- Using phasor analysis:

$$\mathbf{V}_{\text{inv}} = \mathbf{I}\mathbf{Z} + \mathbf{V}_{\text{grid}}$$

$$P_{\text{inv}} = \text{Re} \{ \mathbf{V}_{\text{inv}} \mathbf{I}^* \}$$
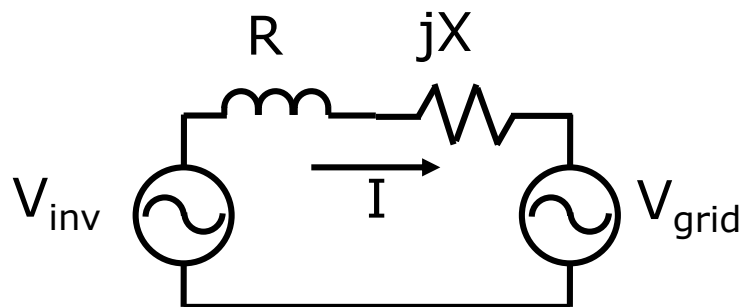
$$Q_{\text{inv}} = \text{Im} \{ \mathbf{V}_{\text{inv}} \mathbf{I}^* \}$$





Grid Connection


- Let
$$\mathbf{Z} = 0.1 + j1\Omega$$
$$\mathbf{V}_{\text{grid}} = 120\angle 0^\circ \text{V}$$
$$P = 6000\text{W}$$
$$Q = 0\text{VAR}$$

} Production from PV

- We can show that:


$$\mathbf{V}_{\text{inv}} = 113\angle 26.2^\circ \text{V}$$
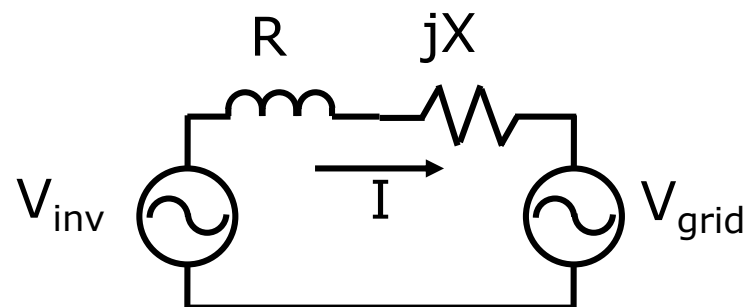
$$\mathbf{I} = 53.1\angle 26.2^\circ \text{A}$$





Inverter Waveforms

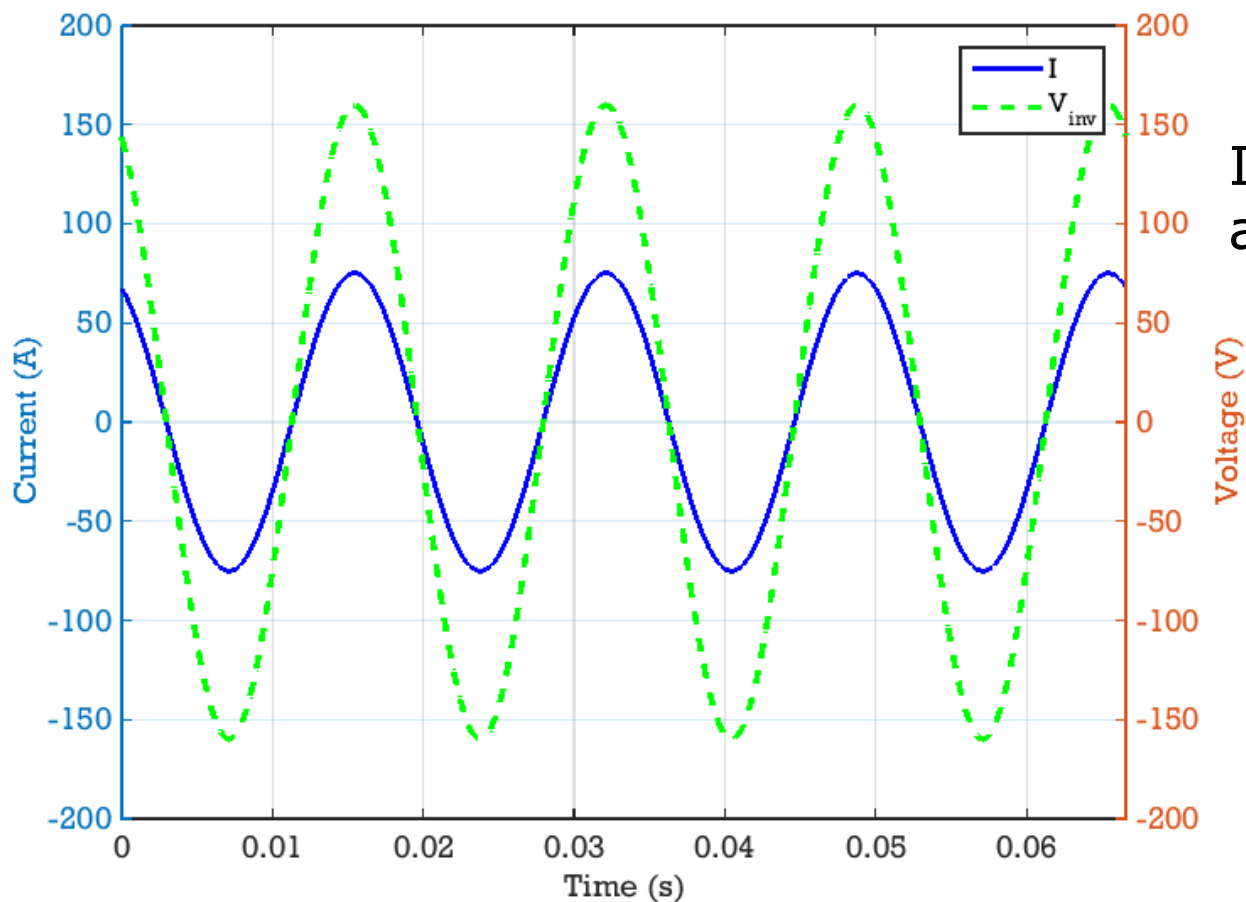

Inverter producing
at unity power factor




Grid Connection

- Note: voltage at the inverter end of the distribution line is low (113V)
 - Other customers on the line will be affected
- Some inverters are able to adjust phase so that the power factor can be controlled (e.g. supply power at unity power factor, or leading/lagging)
- See IEEE 1547 (Standard for Interconnecting Distributed Resources with Electric Power Systems)



Grid Connection

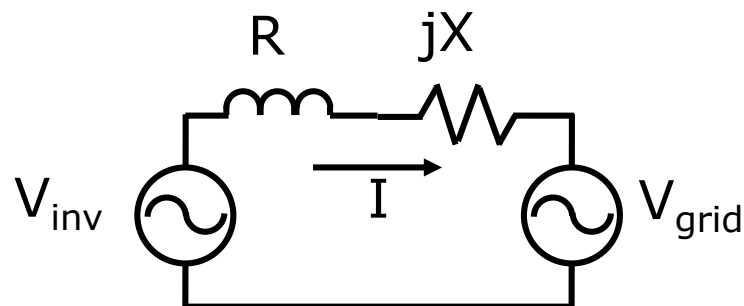- Now let $\mathbf{Z} = 0.1 + j1\Omega$ } Same as before
 $\mathbf{V}_{\text{grid}} = 120\angle 0^\circ \text{V}$ }
 $\mathbf{P} = 6000\text{W}$ } PV supplying
 $\mathbf{Q} = 1500\text{VAR}$ } reactive power




- We can show that:

$$\mathbf{V}_{\text{inv}} = 127.3\angle -22.5^\circ \text{V}$$

$$\mathbf{I} = 48.6\angle -36.5^\circ \text{A}$$



Inverter Waveforms

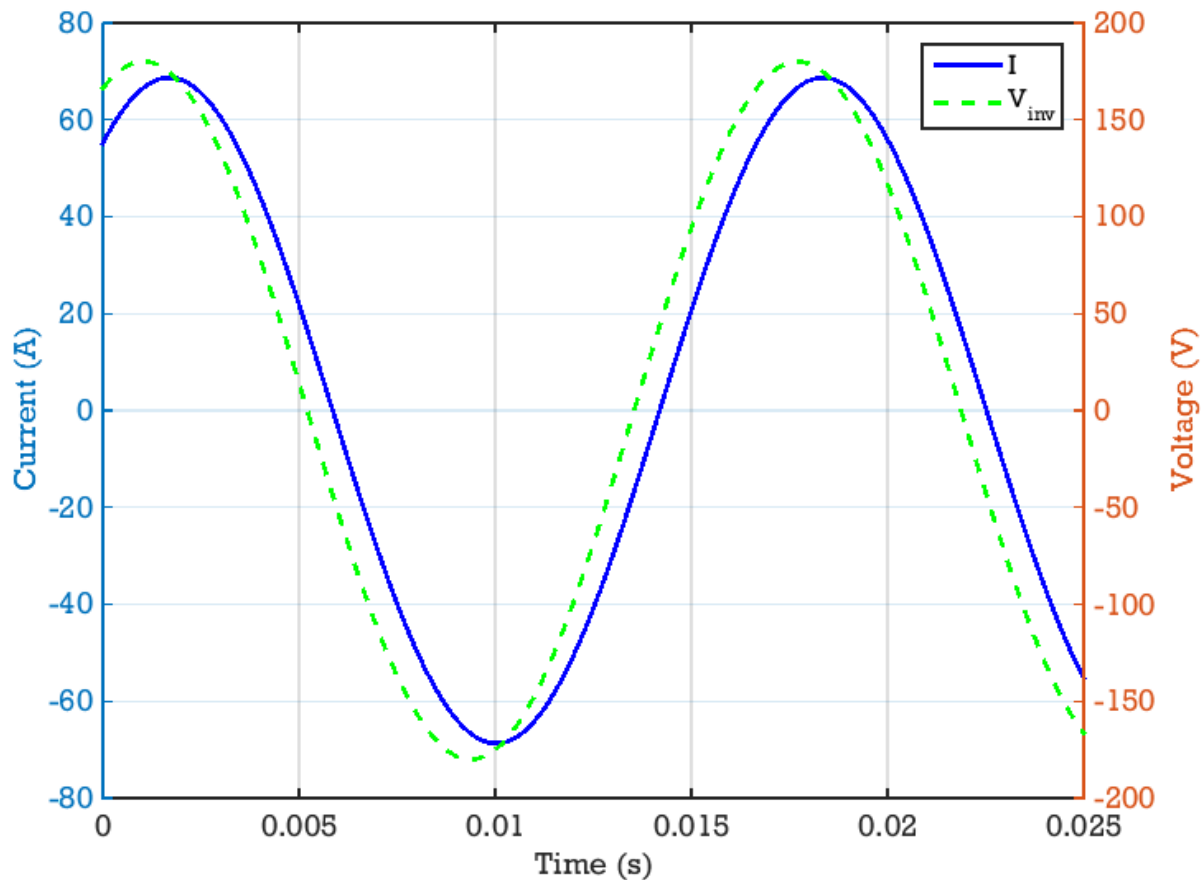

Inverter current and voltage are out of phase.




Reactive Power Control

- The voltage at the end of the line is improved
- Inverter is supplying reactive power (PF = 0.97)
- In general, the voltage magnitude at a node is more sensitive to the reactive power than the active power
- Adjust inverter power factor to enhance voltage regulation of the line



Example Control Scheme

Inject reactive power
for low voltage

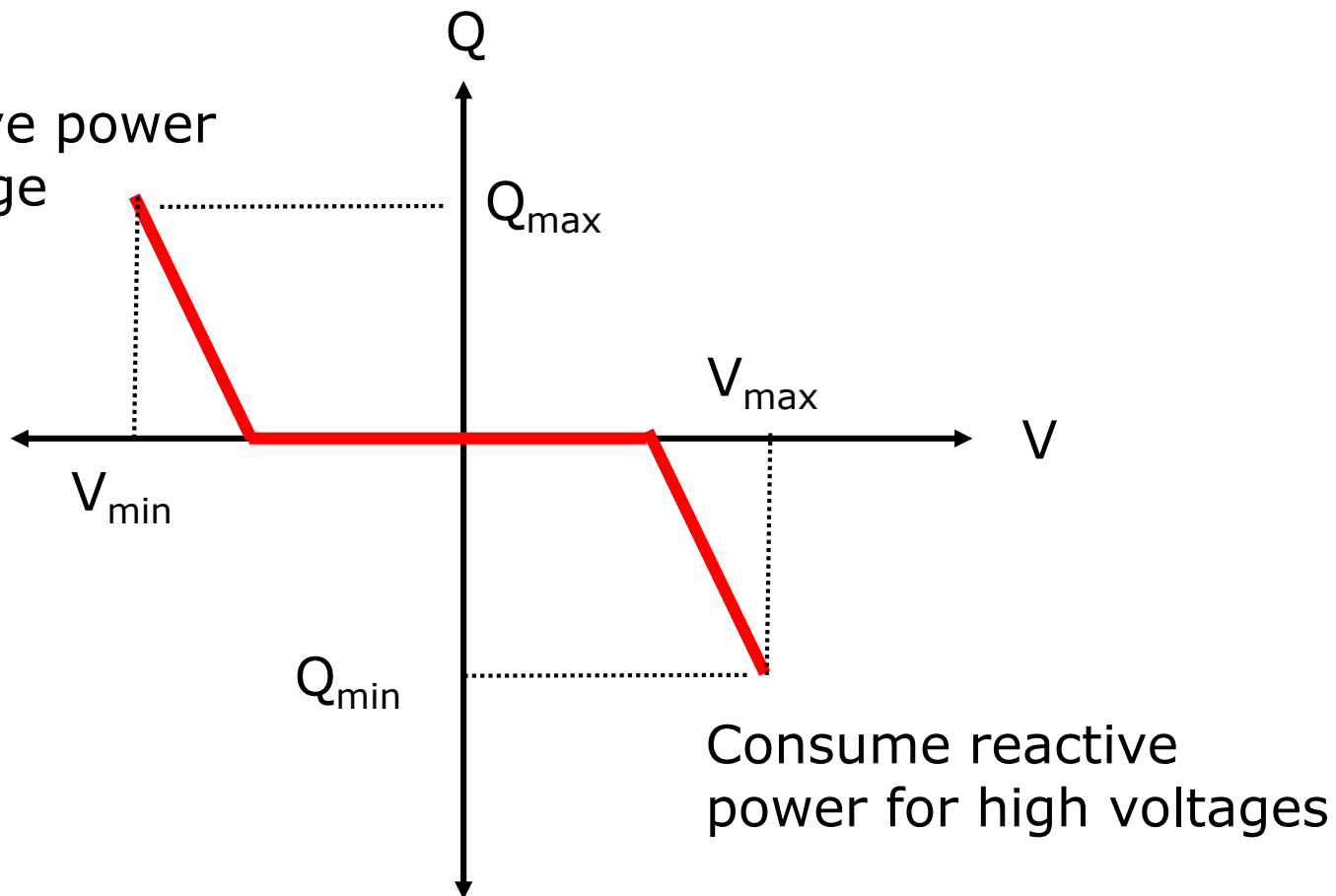





Reading

- <http://spectrum.ieee.org/green-tech/solar/how-rooftop-solar-can-stabilize-the-grid>



Discharge Protection

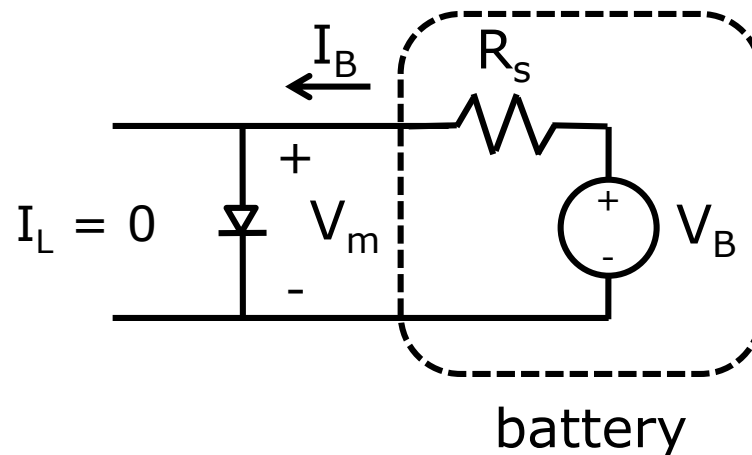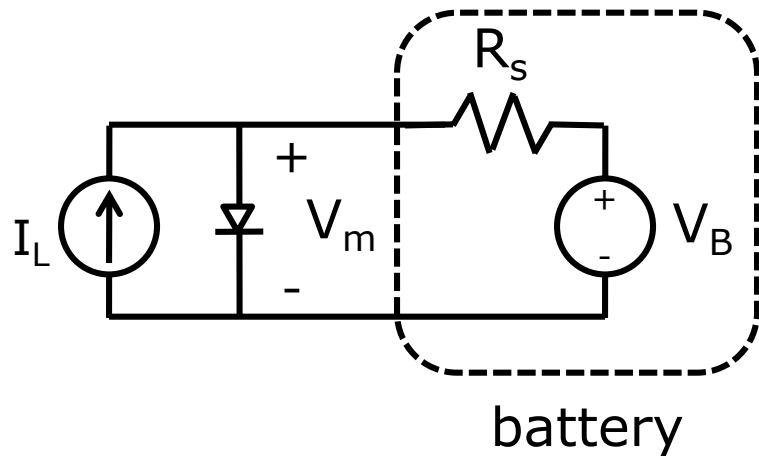
- Consider a PV panel connected to a battery
- What happens at night?
 - $I_L = 0$
 - Diode can be forward biased
 - depends on number of cells in series in the module
 - Battery discharges through PV
 - How can we prevent this?





Battery Charging

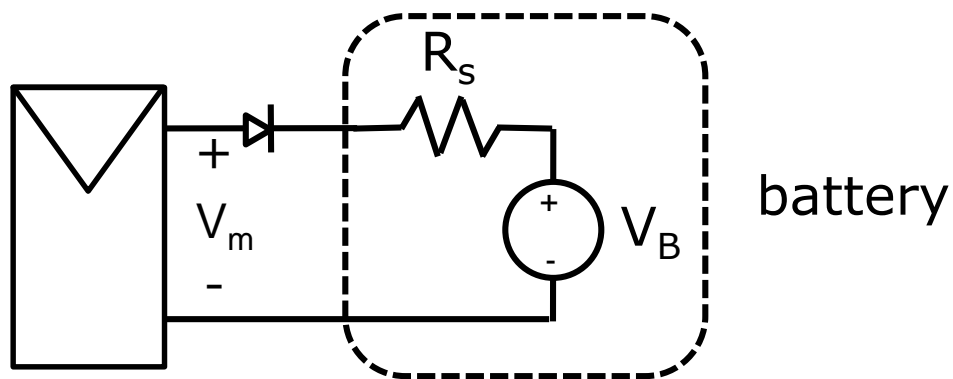- Add a blocking diode
- Less efficient operation during charging
 - Power loss due to diode voltage drop
- Prevents discharging when $V_m < V_B$






Shading

- What happens when a portion of a PV module is shaded?




Shading

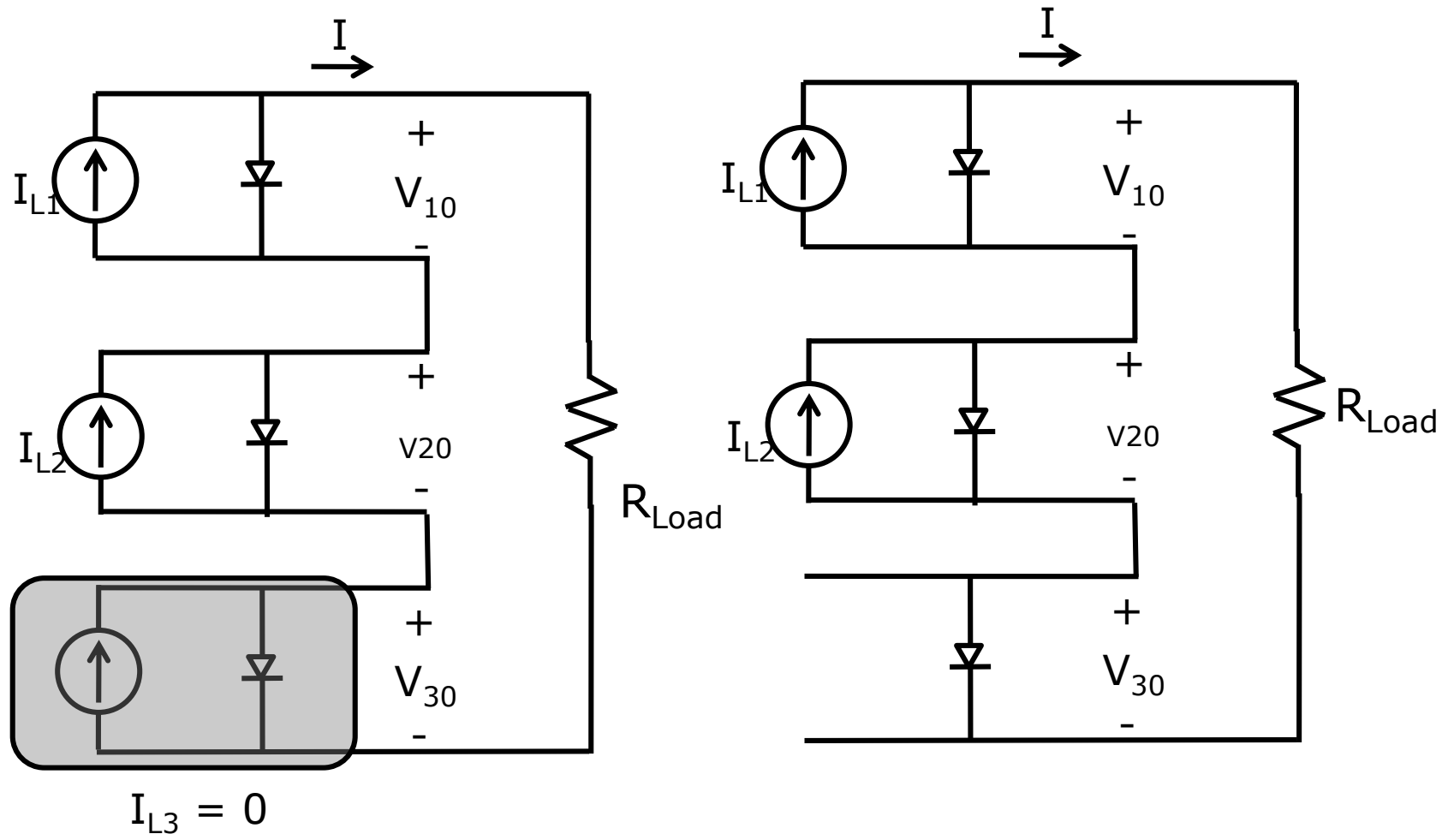



Shading

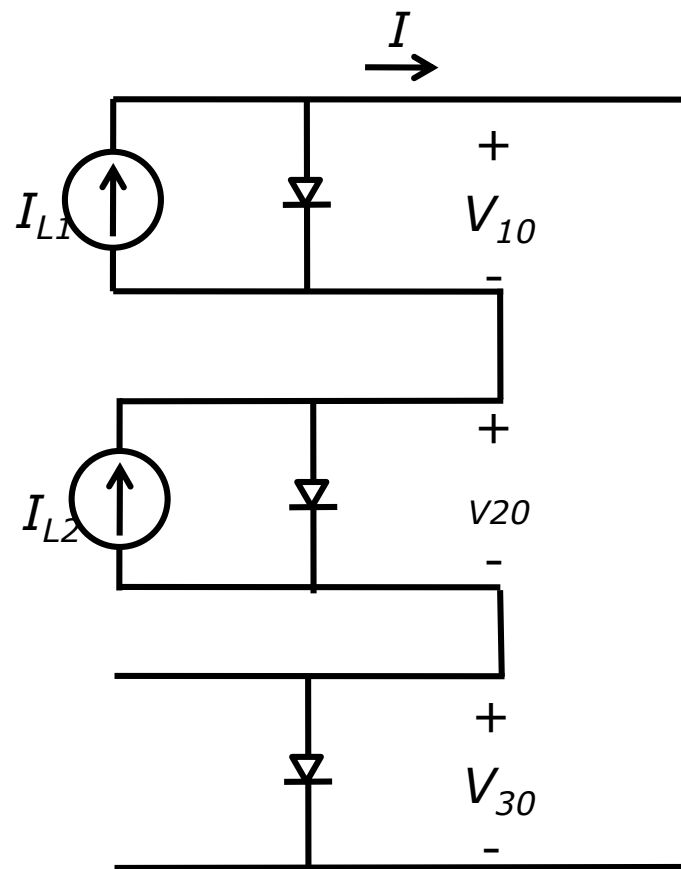- Voltage across shaded cell
 - $V_{30} = -V_{10} - V_{20}$
- Shaded cell is a reversed biased diode
- Power is dissipated
 - Overheating and damage can occur
- Output current is severely reduced





Shading

- Solution to shading is to use bypass diodes

