

06-Three Phase Circuits

Text: Chapter 8.2
ECEGR 3500
Electrical Energy Systems
Professor Henry Louie

Dr. Henry Louie

1

» Overview

- Three Phase Voltage
- Delta, Wye Connections
- Load Connections

Questions

- How is three phase different from single phase?
- How can circuit elements be connected to make three phase systems?
- Why do some electrical panels say 208/120 or 480/277?


3

Dr. Louie


SEATTLEU

Single Phase

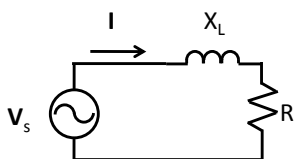- We have analyzed single phase circuits
- Recall:
 - Power pulsates at twice the frequency of voltage, current
 - Two conductors are needed



Instantaneous
power

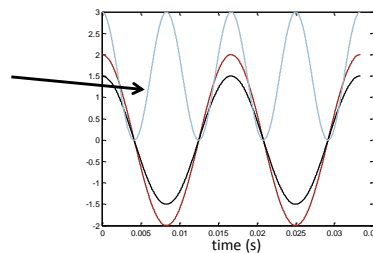

4

Dr. Louie

SEATTLEU




5

Dr. Louie

SEATTLEU

Three Phase

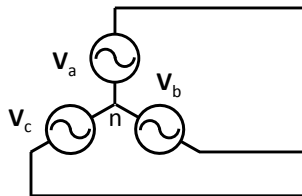- Consider the connection of three, single phase voltage sources V_a , V_b , and V_c
- Known as Three Phase




6

Dr. Louie


SEATTLEU

Three Phase

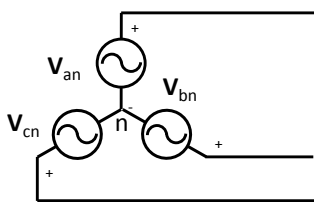- Subscript n (neutral) notes that voltages are referenced to a common node
- Magnitude of phase voltage to neutral is equal for any phase



vector diagram

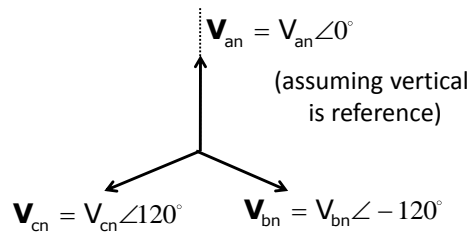


7

Dr. Louie

SEATTLEU

Three Phase

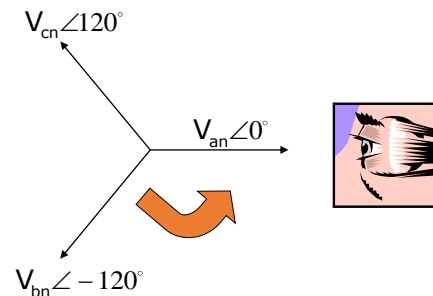- Power systems use 3-phase
- We are concerned with **balanced 3-phase**
- Balanced circuit conditions:
 - impedances are equal for each phase
 - voltage source phasors have equal magnitude and have a 120 deg. phase shift
 - a, b, c phase rotation




8

Dr. Louie

SEATTLEU

Three Phase Voltage

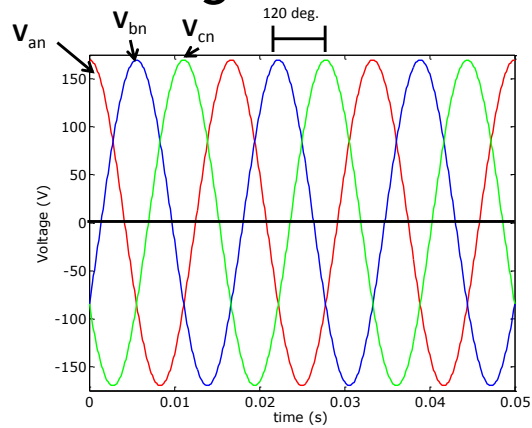



9

Dr. Louie

SEATTLEU

Three Phase Voltage

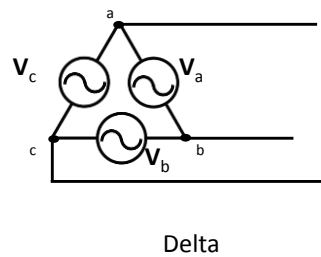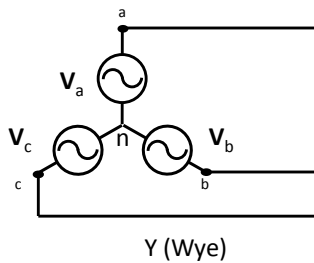Two common configuration of three phase voltage sources:



10



Dr. Louie

SEATTLEU

Three Phase Voltage

Neutral point in Delta-connected sources

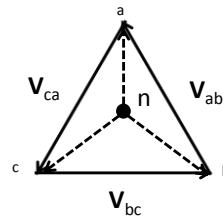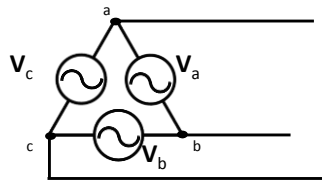- Equidistant between points a, b and c
- Voltage magnitude between a-n, b-n, and c-n are equal (and less than V_{ab} , V_{bc} and V_{ca})




11

Dr. Louie


SEATTLEU

Three Phase Voltage

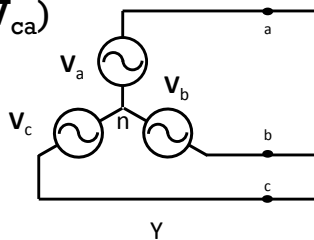- **Phase voltage:** the voltage across each source (e.g.: V_a , V_b , and V_c)
- **Line voltage:** the voltage between the lines of the conductors (also called “Line-to-Line voltage”) for example (e.g.: V_{ab} , V_{bc} , and V_{ca})



Y

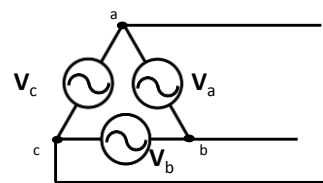

Delta

12

Dr. Louie


SEATTLEU

Three Phase Voltage

For Y-connected sources:

Phase Voltages

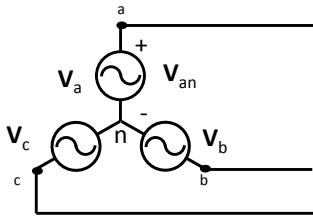
$$\begin{aligned}\mathbf{V}_{an} &= \mathbf{V}_a \\ \mathbf{V}_{bn} &= \mathbf{V}_b \\ \mathbf{V}_{cn} &= \mathbf{V}_c\end{aligned}$$



Line Voltages

by KVL
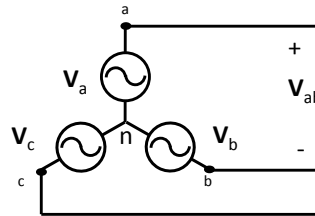
$$\begin{cases} \mathbf{V}_{ab} = \mathbf{V}_a - \mathbf{V}_b = \mathbf{V}_{an}(\sqrt{3}\angle 30^\circ) \\ \mathbf{V}_{bc} = \mathbf{V}_b - \mathbf{V}_c = \mathbf{V}_{bn}(\sqrt{3}\angle 30^\circ) \\ \mathbf{V}_{ca} = \mathbf{V}_c - \mathbf{V}_a = \mathbf{V}_{cn}(\sqrt{3}\angle 30^\circ) \end{cases}$$



13


Dr. Louie

SEATTLEU

Three Phase Voltage

Generically:

- $\beta = 30^\circ$
 - $|\mathbf{V}_{ab}| = 2|\mathbf{V}_{an}|\cos 30^\circ = \sqrt{3}|\mathbf{V}_{an}|$
- So that $\mathbf{V}_{ab} = (\sqrt{3}\angle 30^\circ)\mathbf{V}_{an}$

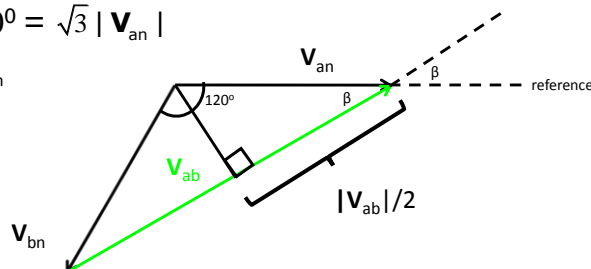

14


Dr. Louie

SEATTLEU

Three Phase Voltage

$$\left. \begin{aligned} \mathbf{V}_{an} &= \mathbf{V}_{bn}(1\angle 120^\circ) \\ \mathbf{V}_{bn} &= \mathbf{V}_{cn}(1\angle 120^\circ) \\ \mathbf{V}_{cn} &= \mathbf{V}_{an}(1\angle 120^\circ) \\ \mathbf{V}_{ab} &= \mathbf{V}_{bc}(1\angle 120^\circ) \\ \mathbf{V}_{bc} &= \mathbf{V}_{ca}(1\angle 120^\circ) \\ \mathbf{V}_{ca} &= \mathbf{V}_{ab}(1\angle 120^\circ) \end{aligned} \right\} \text{Balanced sets}$$

Vector Diagram

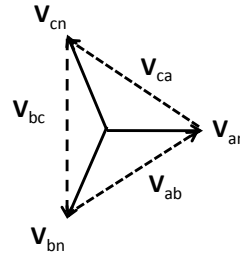

Three Phase Voltage For Delta-connected sources:



Phase Voltages

$$\begin{aligned} \mathbf{V}_a \\ \mathbf{V}_b \\ \mathbf{V}_c \end{aligned}$$

Phase voltage and line voltages are the same in Delta connections

Line Voltages
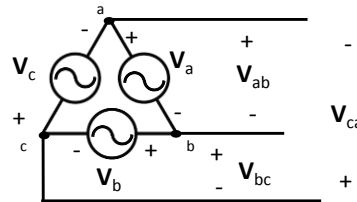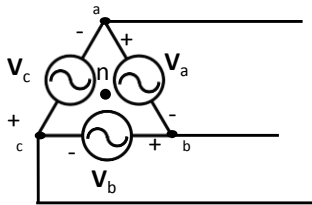
$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_a \\ \mathbf{V}_{bc} &= \mathbf{V}_b \\ \mathbf{V}_{ca} &= \mathbf{V}_c \end{aligned}$$



Three Phase Voltage

- We can convert to and from line-neutral and line-line voltages as:

$$\mathbf{V}_{an} = \frac{\mathbf{V}_{ab}}{\sqrt{3}} \angle -30^\circ$$

$$\mathbf{V}_{bn} = \frac{\mathbf{V}_{bc}}{\sqrt{3}} \angle -30^\circ$$

$$\mathbf{V}_{cn} = \frac{\mathbf{V}_{ca}}{\sqrt{3}} \angle -30^\circ$$

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3} \angle 30^\circ)$$

$$\mathbf{V}_{bc} = \mathbf{V}_{bn}(\sqrt{3} \angle 30^\circ)$$

$$\mathbf{V}_{ca} = \mathbf{V}_{cn}(\sqrt{3} \angle 30^\circ)$$

17

Dr. Henry Louie

SEATTLEU




Three Phase Voltage

Voltages (line or phase) sum to zero

$$\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c = 0$$

$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$
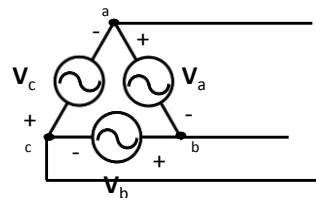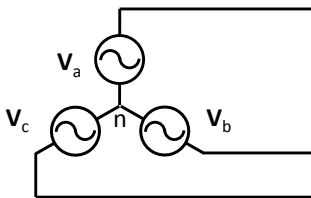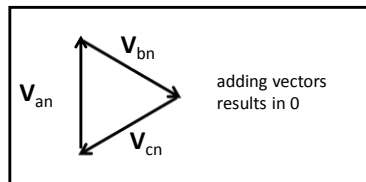
$$\mathbf{V}_{ab} + \mathbf{V}_{bc} + \mathbf{V}_{ca} = 0$$




18

Dr. Louie

SEATTLEU

Three Phase Voltage

- Consider a voltmeter placed as shown
- If $|\mathbf{V}_{an}| = 120 \text{ V}$, then what value is displayed on the voltmeter?

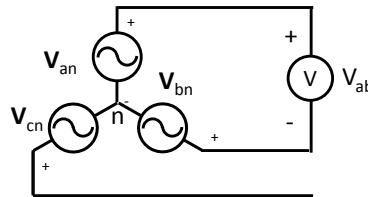

19

Dr. Louie

SEATTLEU

Three Phase Voltage


- Analytically:

$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = 120\angle 0^\circ - 120\angle -120^\circ$$

$$\mathbf{V}_{ab} = (120 + j0) - (-60 - j103.92) = 180 + j103.92 = 120\angle -120^\circ = 208\angle 30^\circ \text{ V}$$

- 208V is displayed and the phasor leads \mathbf{V}_{an} by 30 degrees
- By inspection:

$$|\mathbf{V}_{ab}| = 2V_{an} \cos 30^\circ = \sqrt{3} |\mathbf{V}_{an}|$$

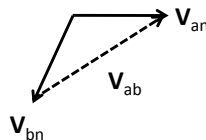

20

Dr. Louie

SEATTLEU

Three Phase Current

- **Phase current:** current flowing through the voltage sources in a three-phase circuit
- **Line current:** current flowing from a three-phase source to a load
- Each set of phase currents and sets of line currents are balanced:
 - Sum to zero
 - Equal in magnitude
 - Displaced by 120 degrees


21

Dr. Louie


SEATTLEU

Three Phase Current

Phase currents in Y-connected sources:

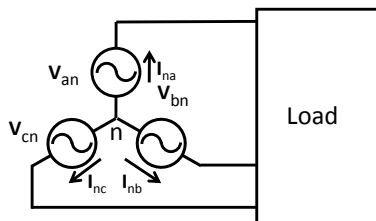

Vector Diagram

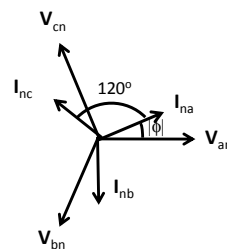

V_{an} is used as reference


22

Dr. Louie

SEATTLEU

Three Phase Current

Phase currents in Y-connected sources:

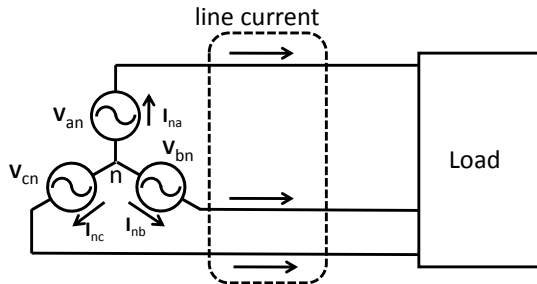

Y-connections:
phase current = line current


23

Dr. Louie


SEATTLEU

Three Phase Current

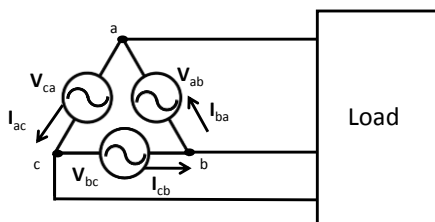Phase currents in Delta-connected sources:



Vector Diagram

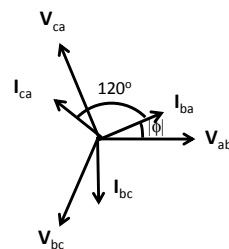

V_{ab} is used as reference

24


Dr. Louie

SEATTLEU

Three Phase Current

Line currents in Delta-connected sources:
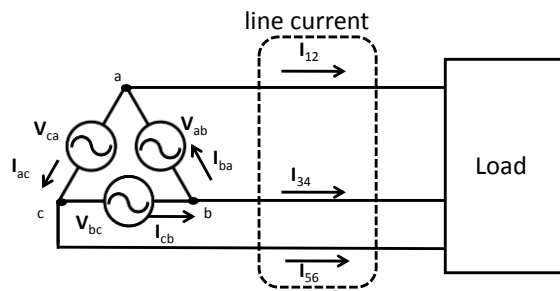
$$\left. \begin{aligned} \mathbf{I}_{12} &= \mathbf{I}_{ba} - \mathbf{I}_{ac} = \mathbf{I}_{ba}(\sqrt{3}\angle -30^\circ) \\ \mathbf{I}_{34} &= \mathbf{I}_{cb} - \mathbf{I}_{ba} = \mathbf{I}_{cb}(\sqrt{3}\angle -30^\circ) \\ \mathbf{I}_{56} &= \mathbf{I}_{ac} - \mathbf{I}_{cb} = \mathbf{I}_{ac}(\sqrt{3}\angle -30^\circ) \end{aligned} \right\} \text{KCL at nodes a, b, c}$$



25


Dr. Louie

SEATTLEU

Three Phase Current

Using \mathbf{I}_{ba} as reference
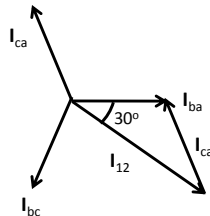
$$\mathbf{I}_{12} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = \mathbf{I}_{ba}\sqrt{3}\angle -30^\circ$$



26

Dr. Louie

SEATTLEU


Summary

Line Current = I_a

Phase Current = I_a

Line Voltage = $V_a \times \sqrt{3} \angle 30^\circ$

Phase Voltage = V_a

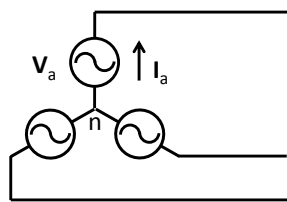


Y (Wye)

Line Current = $I_a \times \sqrt{3} \angle -30^\circ$

Phase Current = I_a

Line Voltage = V_a

Phase Voltage = V_a

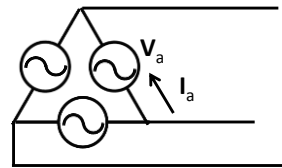


Delta

Dr. Louie


27

Three Phase Loads

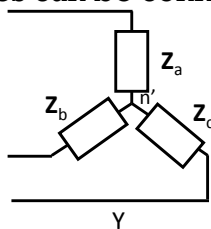- Three phase sources are connected to three phase loads in two common configurations
 - Y (wye)
 - Delta
- Y sources can be connected to delta and/or Y loads
- Delta sources can be connected to delta and/or Y loads




Y

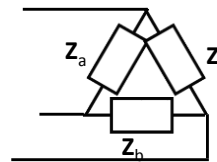

Delta

Three Phase Loads

Examples with a Y source

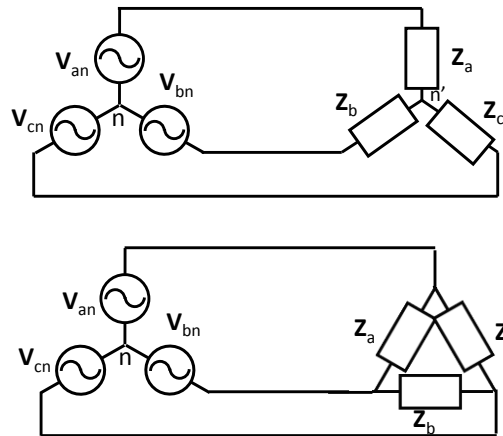

29

Dr. Louie

SEATTLEU

Three Phase Loads

- Circuit analysis is easier if loads are connected as Y
- We can transform balanced Delta connected loads into balanced Y connected loads mathematically by

$$\mathbf{Z}_Y = \frac{\mathbf{Z}_\Delta}{3}$$

- \mathbf{Z}_Y : complex impedance of Y-connected load (Ohms)
- \mathbf{Z}_Δ : complex impedance of a Delta-connected load (Ohms)
- Results only apply to terminal conditions



30

Dr. Louie

SEATTLEU

Three Phase Loads Example

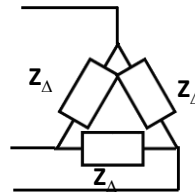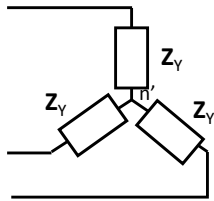Each phase of a Y-connected load has an impedance of $6 + j12$. Find the impedance of the equivalent delta-connected load.



31



Dr. Louie

SEATTLEU

Three Phase Loads Example

- Each phase of a Y-connected load has an impedance of $6 + j12$. Find the impedance of the equivalent delta-connected load.

Answer: $Z_{\Delta} = 18 + j36\Omega$

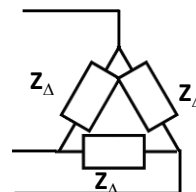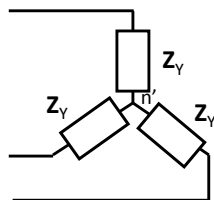

32

Dr. Louie

SEATTLEU

Summary

- Three phase systems: more efficient use of conductors; provides rotating magnetic fields; non-pulsating power delivery
- Balanced three phase: a,b,c (voltage, current) phases displaced by 120 degrees and have equal magnitude
- Line-line and line-neutral voltage relationship: $\mathbf{V}_{LL} = \mathbf{V}_{LN}(\sqrt{3}\angle 30^\circ)$