

10-Home Electrical Safety

Text: Chapter 9.4
ECEGR 3500
Electrical Energy Systems
Professor Henry Louie



Dr. Henry Louie

1

» Overview

- Typical Residential Electricity Service
- Neutral vs. Ground
- Ground Fault Circuit Interrupter


Typical Residential Electricity Service

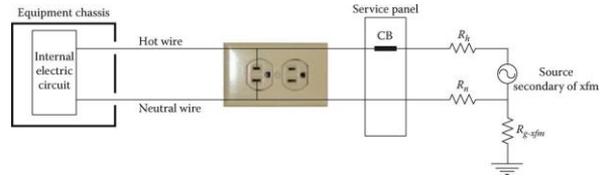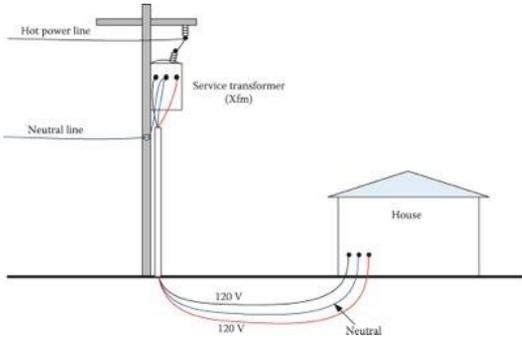

3


Dr. Henry Louie

SEATTLEU

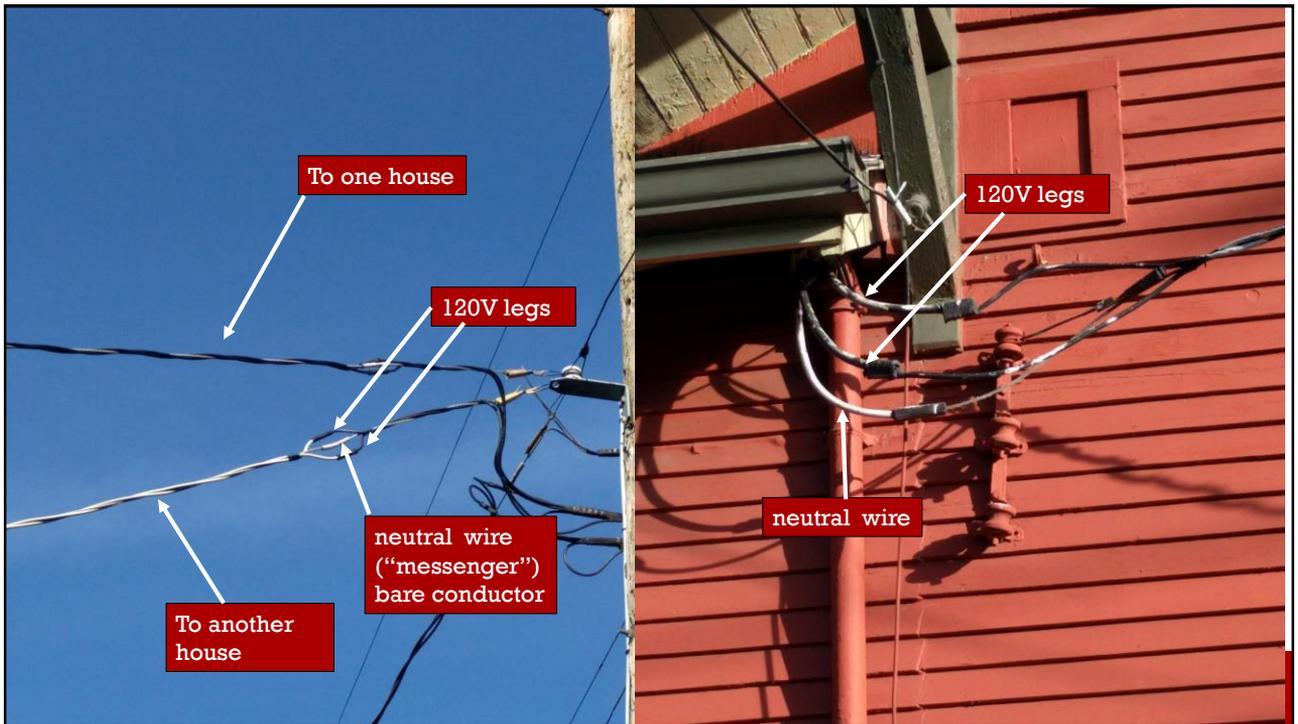

Typical Residential Electricity Service

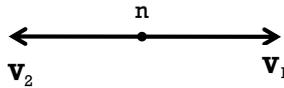- The service transformer is center tapped, which provides two 120V phases, that are 180 degrees out of phase
- The voltage V_{1n} and V_{2n} is 120V
- The voltage from V_1 to V_2 is 240, and is used to serve high power loads, such as dryers



5

Dr. Henry Louie

SEATTLEU

Neutral and Ground


- Under normal operation (which in a home is not assumed to be balanced), the neutral carries return current and the ground does not
- Ground and neutral are connected at the service transformer, and the entrance of the residence
- The purpose of the ground wire is for protection, the purpose of the neutral is provide a path back to the source

6

Dr. Henry Louie

SEATTLEU

Neutral and Ground

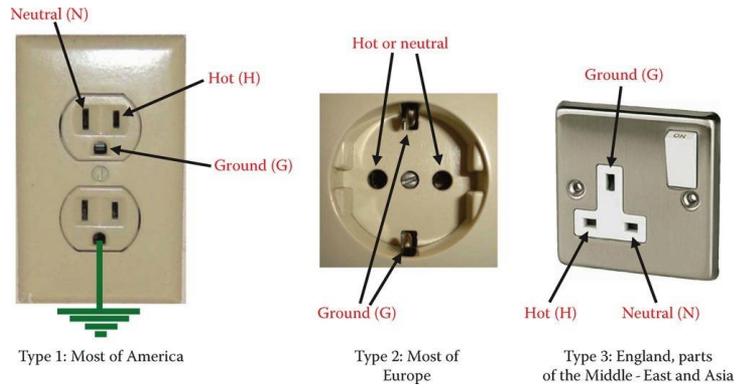

7

Dr. Henry Louie

SEATTLEU

Neutral and Ground



(a)



(b)



(c)

Why do some plugs have a ground prong, and others do not?

8

Dr. Henry Louie

SEATTLEU

»» What could go wrong?



What happens if the "hot" wire touches the case of the metallic toaster?

9

Dr. Henry Louie

SEATTLEU

»» What could go wrong?

- If the toaster is connected only by the hot wire and neutral, the toaster's case becomes energized (at or near 120V)
- This is a hazardous condition
- What happens if someone touches the toaster?




10

Dr. Henry Louie

SEATTLEU

What could go wrong?

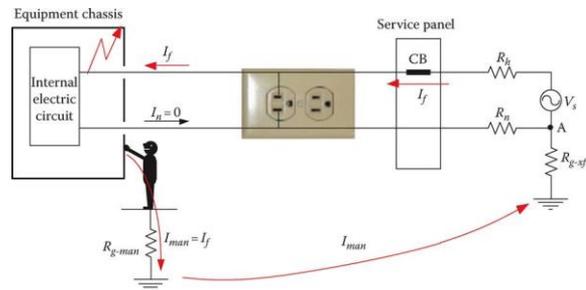- If the person is grounded, current will flow through them and they could be harmed




11

Dr. Henry Louie

SEATTLEU

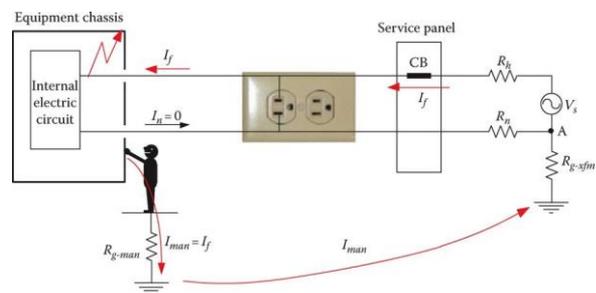Exercise (Example 9.9)

Assume that the circuit breaker is rated 20 A, the source voltage is 120 V, $R_n = R_h = 0.5 \Omega$, $R_{g-man} = 500 \Omega$, $R_{man} = 1000 \Omega$, and $R_{g-xfm} = 20 \Omega$. Compute the current through the person touching the chassis.



12

Dr. Henry Louie


SEATTLEU

Exercise (Example 9.9)

Assume that the circuit breaker is rated 20 A, the source voltage is 120 V, $R_n = R_h = 0.5 \Omega$, $R_{g-man} = 500 \Omega$, $R_{man} = 1000 \Omega$, and $R_{g-xfm} = 20 \Omega$. Compute the current through the person touching the chassis.

$$I_{man} = I_f = \frac{V_s}{R_h + R_{man} + R_{g,man} + R_{g,xfmr}} = 78.92\text{mA}$$

This can cause death.

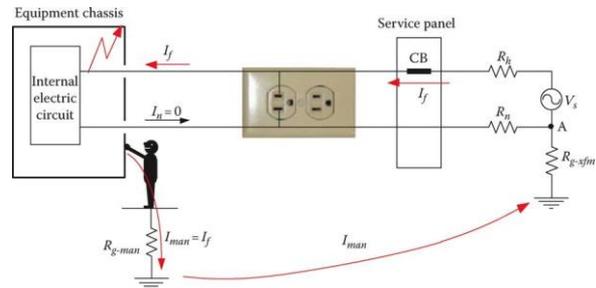

13


Dr. Henry Louie

SEATTLEU

Grounded Chassis

- Let's see what happens if we use a three prong plug and connect the chassis to ground
- Equipment Grounding Conductor (EGC): connection between the device and the ground

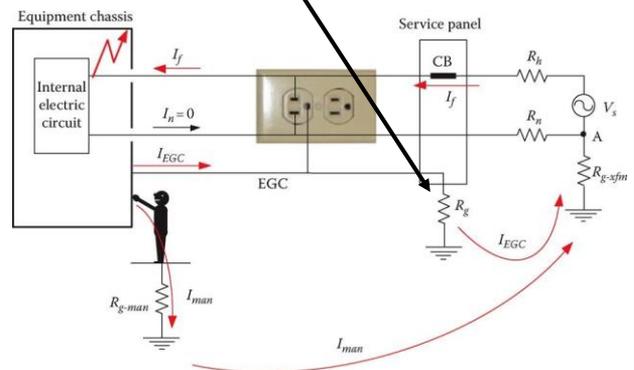Each house has a dedicated ground rod to establish a local ground. Sometimes water pipes are used




14

Dr. Henry Louie

SEATTLEU

Grounded Chassis

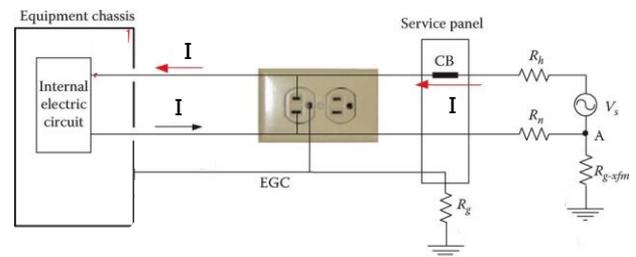- Let's see what happens if we use a three prong plug and connect the chassis to ground
- Equipment Grounding Conductor (EGC): connection between the device and the ground



15

Dr. Henry Louie

SEATTLEU



Ground rod buried near service panel



16

Dr. Henry Louie

SEATTLEU

Grounded Chassis

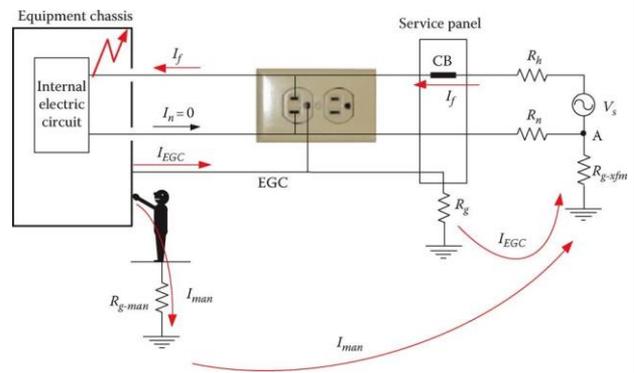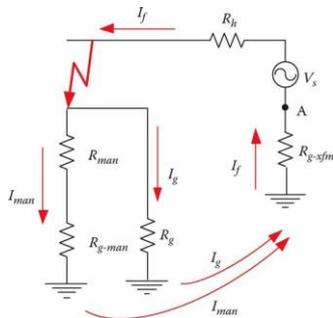- In this situation, there is a current divider (through the person and through the EGC)



17

Dr. Henry Louie


SEATTLEU

Exercise (Example 9.10)

Now assume that the circuit breaker is rated 20 A, the source voltage is 120 V. The system parameters are $R_n = R_h = 0.5 \Omega$, $R_{g-man} = 500 \Omega$, $R_{man} = 1000 \Omega$, $R_g = 10 \Omega$, and $R_{g-xfm} = 20 \Omega$. Compute the fault current and the current through the person touching the chassis.

Resistance of the man and ground is 1500Ω
The equivalent resistance including EGC is
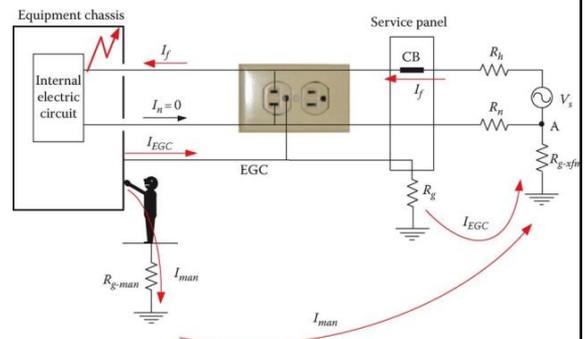
$$R_{eq} = \frac{R_g 1500}{R_g + 1500} = 9.93 \Omega$$



18

Dr. Henry Louie

SEATTLEU

Exercise (Example 9.10)

Now assume that the circuit breaker is rated 20 A, the source voltage is 120 V. The system parameters are $R_n = R_h = 0.5 \Omega$, $R_{g-man} = 500 \Omega$, $R_{man} = 1000 \Omega$, $R_g = 10 \Omega$, and $R_{g-xfm} = 20 \Omega$. Compute the fault current and the current through the person touching the chassis.


The fault current is:

$$I_f = \frac{V_s}{R_h + R_{eq} + R_{g,xfmr}} = 3.94A$$

This is divided between the man and EGC. By current divider

$$I_{man} = I_f \frac{R_g}{R_g + (R_{man} + R_{g,man})} = 26.1mA$$

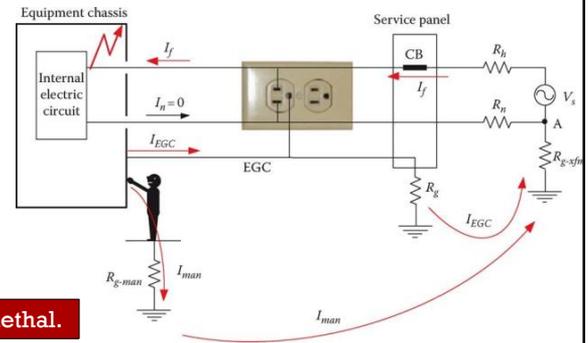This is lower than the last example, but still can be lethal.




19

Dr. Henry Louie

SEATTLEU

Bonded Neutral

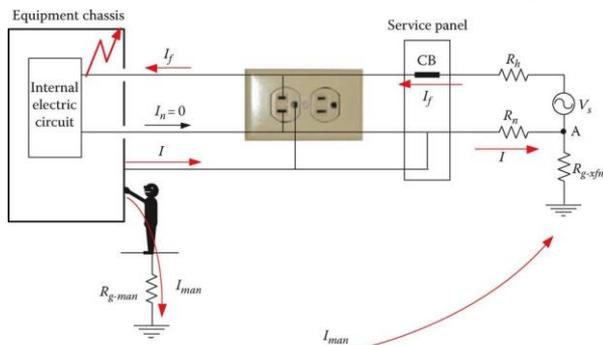- Now examine what happens if the neutral is bonded to ground, and there is no local ground





The situation is improved because R_n is generally much smaller than $R_{gman} + R_{gxfmr}$. There is a low resistance path back to the source, so a large current flows. The circuit breaker should trip.

20

Dr. Henry Louie

SEATTLEU

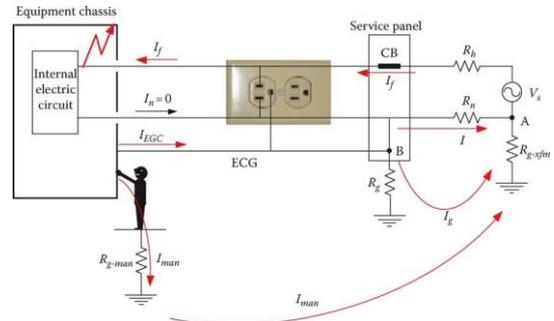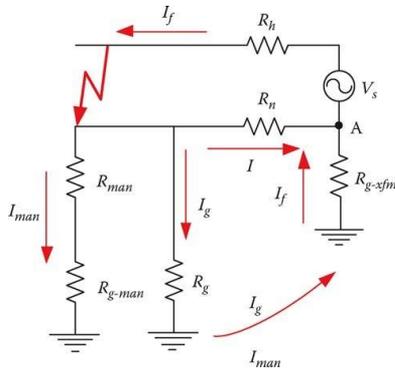A better way...bond neutral and ground chassis





23

Dr. Henry Louie

SEATTLEU

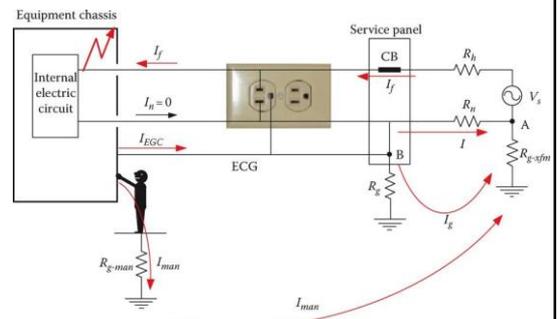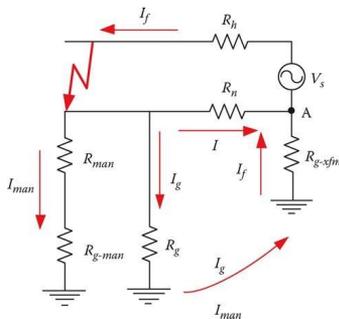Exercise (Example 9.13)

Now assume that the circuit breaker is rated at 20 A and the source voltage is 120 V. The system parameters are $R_n = R_h = 0.5 \Omega$, $R_{g-man} = 500 \Omega$, $R_{man} = 1000 \Omega$, $R_g = 10 \Omega$, and $R_{g-xfm} = 20 \Omega$. Compute the fault current.



24



Dr. Henry Louie

SEATTLEU

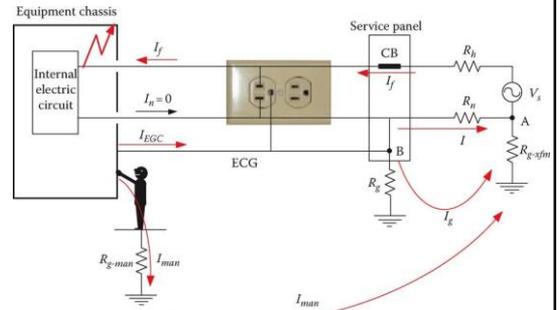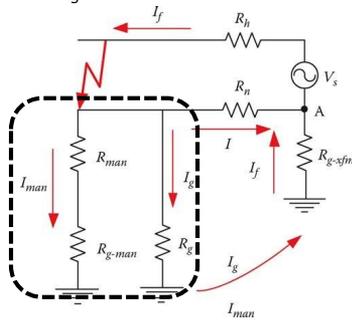Exercise (Example 9.13)

From before, the resistance of the man and ground is 1500Ω . The equivalent resistance including EGC is

$$R_{eq1} = \frac{R_g \cdot 1500}{R_g + 1500} = 9.93\Omega$$



25



Dr. Henry Louie

SEATTLEU

Exercise (Example 9.13)

R_{eq1} is in series with $R_{g,xfrm}$

$$R_{eq2} = 29.93\Omega$$

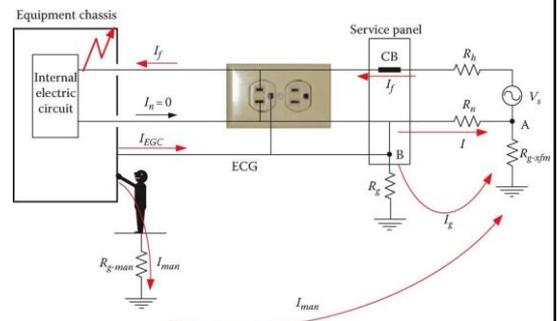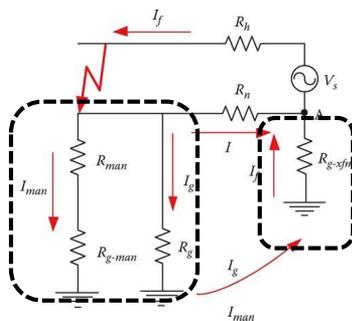

26



Dr. Henry Louie

SEATTLEU

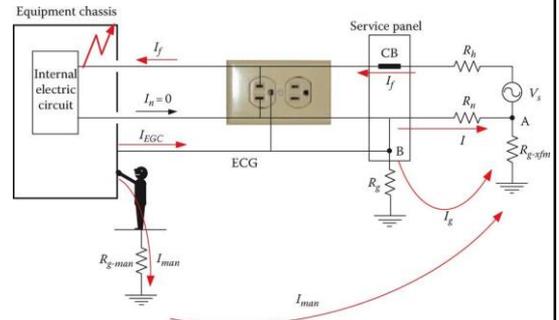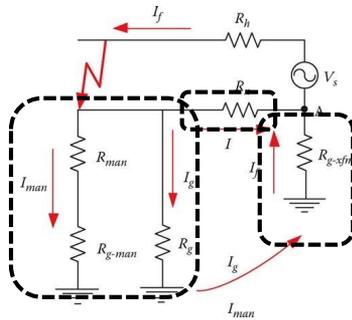Exercise (Example 9.13)

R_{eq2} is in parallel with R_n

$$R_{eq} = R_n \parallel R_{eq2} = 0.492\Omega$$



27



Dr. Henry Louie

SEATTLEU

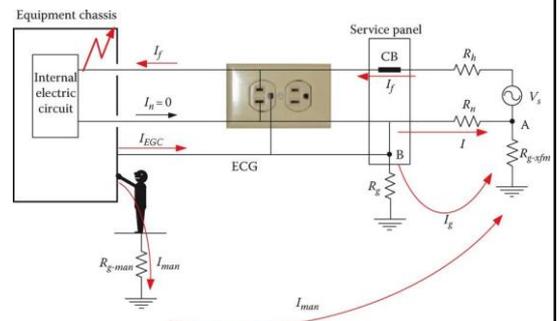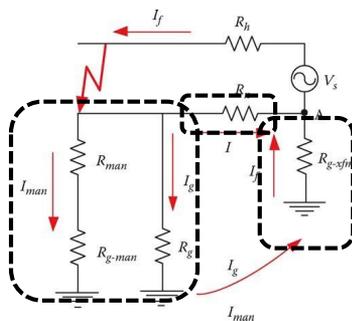Exercise (Example 9.13)

The fault current is then

$$I_f = \frac{V_s}{R_h + R_{eq}} = 120.97A \quad \text{This is high enough to trip the circuit breaker}$$



28

Dr. Henry Louie

SEATTLEU

Exercise (Example 9.13)

- In the previous example, the current through the person is $>10\text{mA}$ (computed by two current dividers)
- However the circuit breaker will trip (and would trip as soon as the internal fault happens—hopefully not at the same time the person touches the appliance!)


29

Dr. Henry Louie

SEATTLEU

Normal Operation

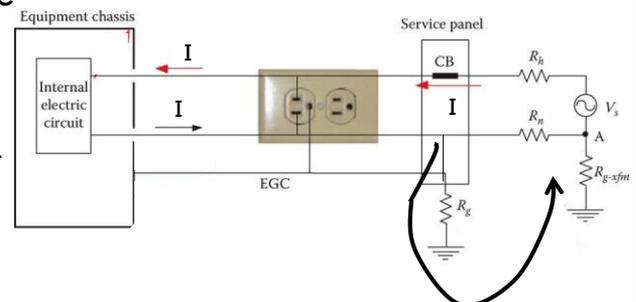- During normal operation, current flows from appliance back to service panel on the neutral conductor
- Due to the parallel path, some (usually small) current will flow through R_g back to the xfmr through R_{g-xfmr}




30

Dr. Henry Louie

SEATTLEU

Household Distribution System (U.S.)

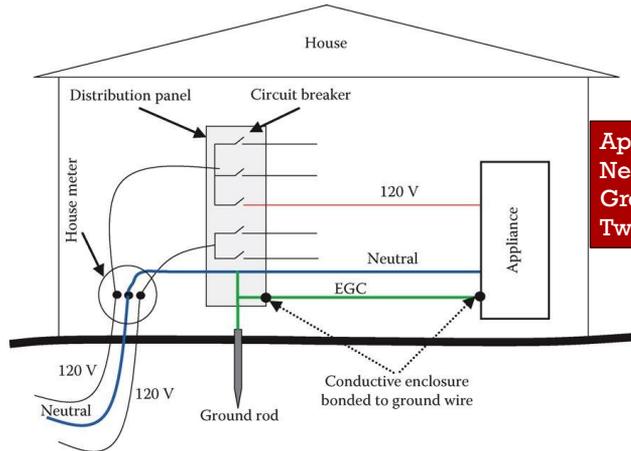

Appliance chassis attached to ground conductor;
Neutral is bonded to ground conductor at service panel;
Ground rod is buried near service panel.
Two hot wires + 1 neutral wire is provided from xmfr

31

Dr. Henry Louie

SEATTLEU

Broken Neutral


- Broken or deteriorated (high impedance) neutrals can cause safety hazards, especially when several homes share an transformer

32

Dr. Henry Louie

SEATTLEU

Two houses served by the same xfmr

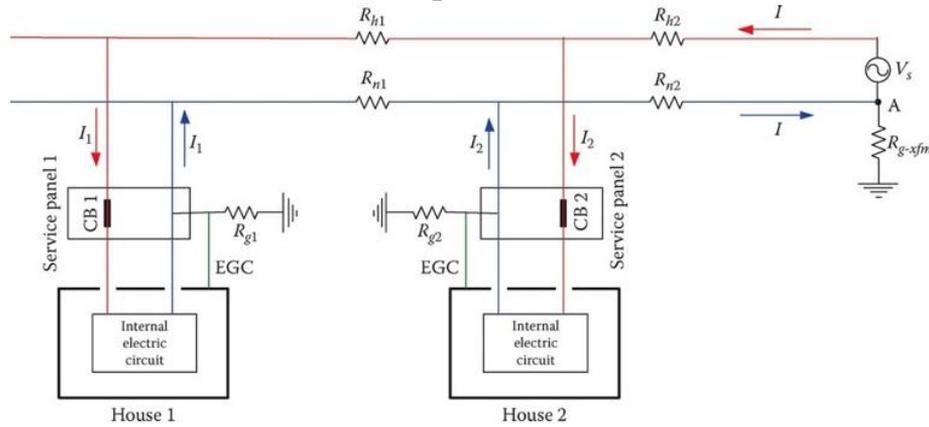


33

Dr. Henry Louie

SEATTLEU

With neutral broken

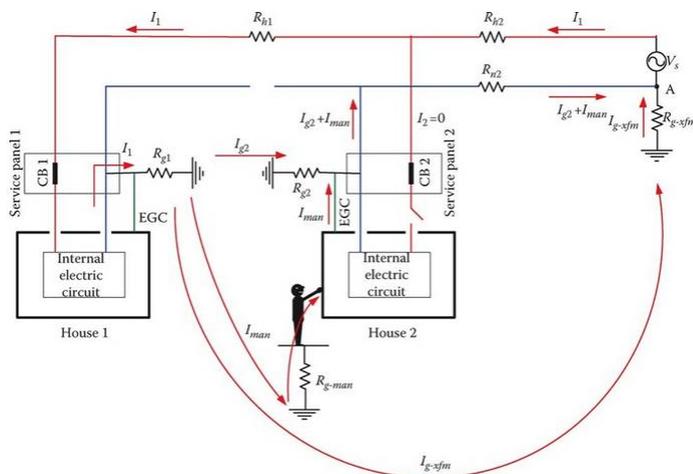

Neutral of House 1 is broken.
Current returns through the EGC,
and up through the EGC of the
Appliance in House 2, causing a
shock hazard.

34

Dr. Henry Louie

SEATTLEU

Ground Fault Circuit Interrupter

- GFCI are devices used to protect human life (circuit breakers are design primarily to protect equipment)
- GCFI's are used in high risk areas, for example where there are outlets and water (kitchen, bathroom, outdoors)
- There is also a reasonable chance that the person is wet, and are touching another grounded object (like a part of the plumbing system)




35

Dr. Henry Louie

SEATTLEU

Ground Fault Circuit Interrupter

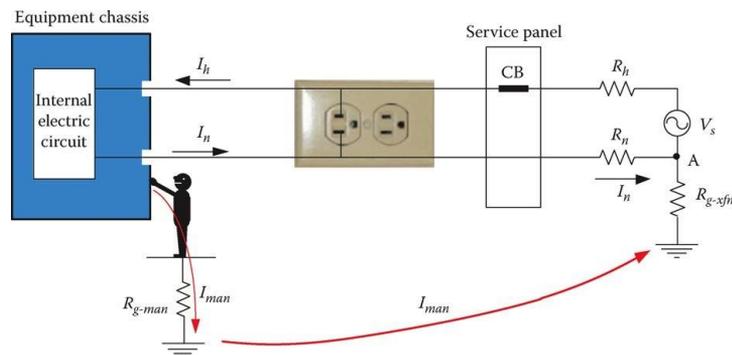

36

Dr. Henry Louie

SEATTLEU

Ground Fault Circuit Interrupter


- GFCIs work by “counting” the electrons flowing through the hot and “counting” the electrons flowing back on the neutral
- If the two values do not sum to zero at any instant, then there must be a fault to ground
- The GFCI is very sensitive and operates quickly
- Number of house hold consumer product electrocutions dropped dramatically after GFCIs became mandatory

37

Dr. Henry Louie

SEATTLEU

Ground Fault Circuit Interrupter

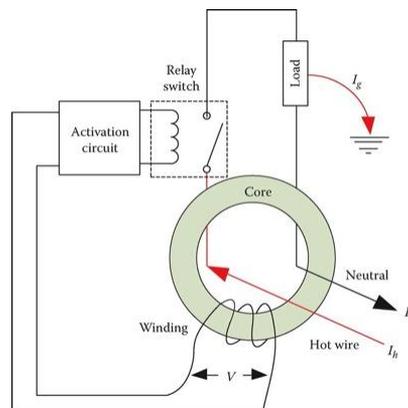

38

Dr. Henry Louie

SEATTLEU

» Read also

- Chapter 9.4.5 (World's Residential Grounding Practices)
- Chapter 9.5 (Low Frequency Magnetic Field and Its Health Effects)