

15-Intro. to Three Phase Transformers

ECEGR 3500

Text: 11.4

Electrical Energy Systems

Professor Henry Louie

Dr. Henry Louie

1

» Overview

- Y-Y Transformer Connection
- Delta-Delta Transformer Connection
- Y-Delta Transformer Connection
- Delta-Y Transformer Connection

Three-Phase Transformer Connections

- We are generally more concerned with three phase transformers
- Three-phase transformers can be composed of three single-phase transformers or be wound on the same core
- Many combinations are possible:
 - Y-Y
 - Delta-Delta
 - Y-Delta
 - Delta-Y


3

Dr. Louie

SEATTLEU

Y-Connected Circuits

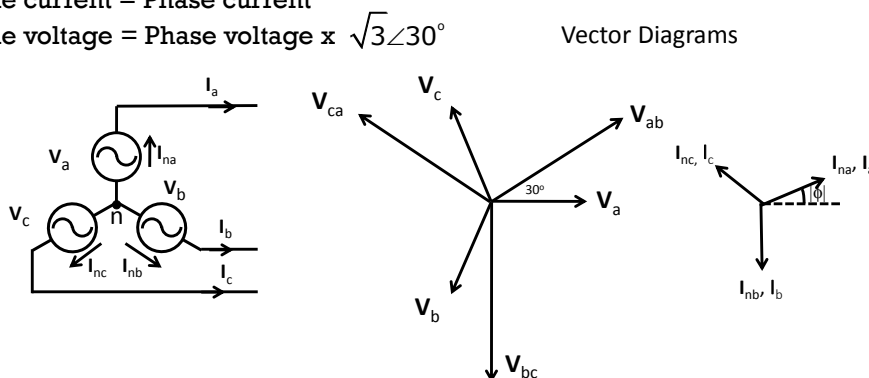- Recall from previous lectures:
 - Line current = Phase current
 - Line voltage = Phase voltage $\times \sqrt{3} \angle 30^\circ$



4


Dr. Louie

SEATTLEU

Y-Y Transformer

- Each side has a common point, n or n'
- Neutral points usually grounded
- Tertiary winding (Delta) sometimes connected to avoid distortion if harmonics are present
- Line-neutral voltages appear across the coils on each side
- Insulation is stressed to only 58% of line voltage

Do not confuse this n with $1/a$

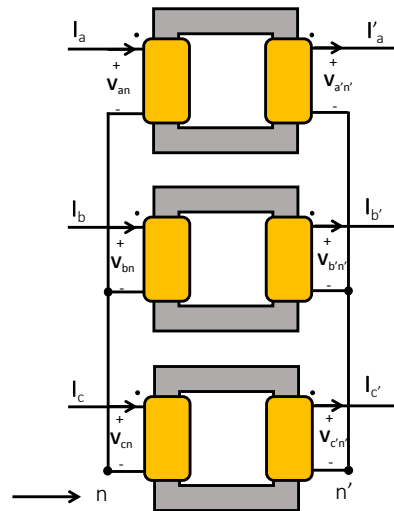


5

Dr. Louie

SEATTLEU

Y-Y Transformer Analysis

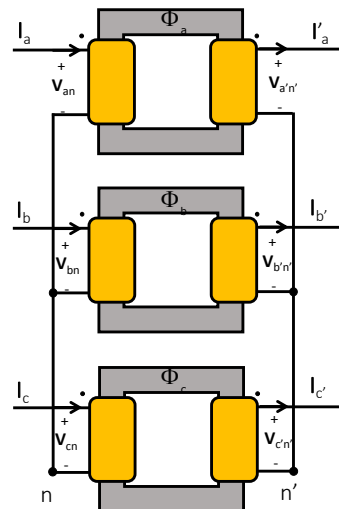- Mutual flux in each core are out of phase by 120°
- Φ_a links primary and secondary
- Faraday's law: \mathbf{V}_{an} and $\mathbf{V}'_{a'n'}$ must be in phase and lead Φ_a by 90°
 - similar result for b, c phases
- Ampere's Law: \mathbf{I}_a and \mathbf{I}'_a are also in phase
 - similar result for b, c phases




6

Dr. Louie

SEATTLEU

Y-Y Transformer Analysis

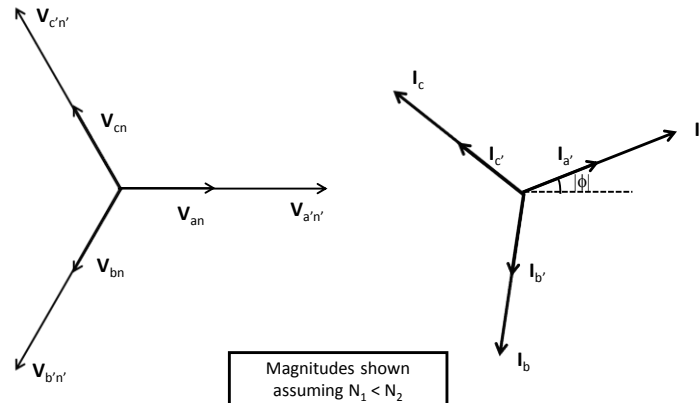Phasor Diagram for Ideal Y-Y Connected Transformer



7

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Y-Y

- Let k be the transformer voltage gain

- For Y-Y transformers:

$$\mathbf{V}_{a'n'} = k\mathbf{V}_{an} = \frac{N_2}{N_1} \mathbf{V}_{an}$$

therefore $k = n$ ← Do not confuse this n with the neutral point

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{k} = \frac{\mathbf{I}_a}{n}$$

$$\mathbf{V}_{a'b'} = \mathbf{V}_{a'n'} \sqrt{3} e^{j\frac{\pi}{6}} = (n\mathbf{V}_{an}) \sqrt{3} e^{j\frac{\pi}{6}} \quad (\text{secondary line voltage})$$

$$= \sqrt{3} \left(n \frac{\mathbf{V}_{ab}}{\sqrt{3}} e^{-j\frac{\pi}{6}} \right) e^{j\frac{\pi}{6}} = n\mathbf{V}_{ab}$$

$$\text{Recall: } e^{j\frac{\pi}{6}} = 1 \angle 30^\circ$$

8

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Y-Y

Line-neutral voltages

$$\mathbf{V}_{a'n'} = n\mathbf{V}_{an}, \quad \mathbf{V}_{a'b'} = n\mathbf{V}_{ab}$$

$$\mathbf{V}_{b'n'} = n\mathbf{V}_{bn}, \quad \mathbf{V}_{b'c'} = n\mathbf{V}_{bc}$$

$$\mathbf{V}_{c'n'} = n\mathbf{V}_{cn}, \quad \mathbf{V}_{c'a'} = n\mathbf{V}_{ca}$$


Line currents

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{n}$$

$$\mathbf{I}_{b'} = \frac{\mathbf{I}_b}{n}$$

$$\mathbf{I}_{c'} = \frac{\mathbf{I}_c}{n}$$

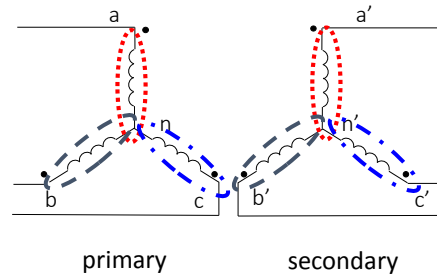Recall: phase currents =
line current for Y
connections




9

Dr. Louie

SEATTLEU

Delta-Connected Circuits

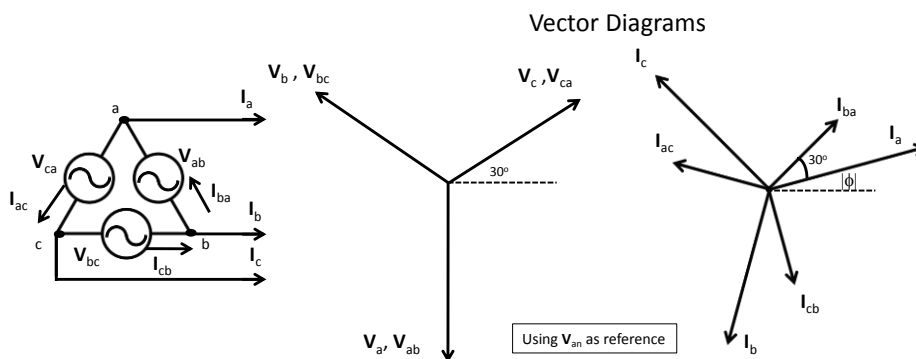


10

Dr. Louie

SEATTLEU

Δ-Δ Transformer

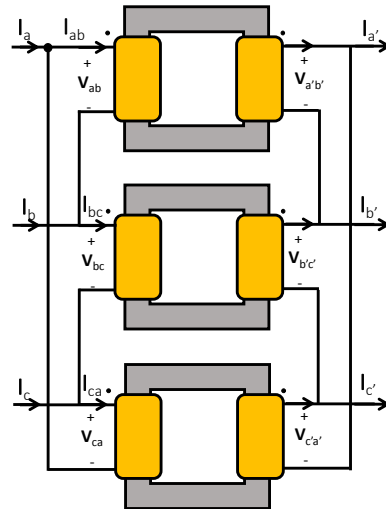- No neutral point
- $\mathbf{V}_{ab}, \mathbf{V}_{a'b'}$ in phase
- $\mathbf{I}_{ab}, \mathbf{I}_{a'b'}$ in phase
 - Similar results for b, c phase
- Line-line voltages appear across the coils on primary and secondary
- Best suited for lower voltage applications



11

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Δ-Δ

- Let k be the transformer voltage gain
- For Δ-Δ transformers: $\mathbf{v}_{a'b'} = k\mathbf{v}_{ab} = \frac{N_2}{N_1} \mathbf{v}_{ab}$

therefore $k = n$

$$\mathbf{I}_{a'b'} = \frac{\mathbf{I}_{ab}}{k} = \frac{\mathbf{I}_{ab}}{n}$$

$$\mathbf{v}_{a'n'} = \frac{\mathbf{v}_{a'b'} e^{-j\pi/6}}{\sqrt{3}} = \frac{n\mathbf{v}_{ab} e^{-j\pi/6}}{\sqrt{3}}$$

$$= \frac{n(\sqrt{3}\mathbf{v}_{an} e^{j\pi/6}) e^{-j\pi/6}}{\sqrt{3}} = n\mathbf{v}_{an} \quad (\text{line-neutral voltage})$$

12

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Δ - Δ

Voltage Relationships

$$\mathbf{V}_{a'b'} = n\mathbf{V}_{ab}$$

$$\mathbf{V}_{b'c'} = n\mathbf{V}_{bc}$$


$$\mathbf{V}_{c'a'} = n\mathbf{V}_{ca}$$

Current Relationships

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{n}, \quad \mathbf{I}_{b'a'} = \frac{\mathbf{I}_{ab}}{n}$$

$$\mathbf{I}_{b'} = \frac{\mathbf{I}_b}{n}, \quad \mathbf{I}_{c'b'} = \frac{\mathbf{I}_{bc}}{n}$$
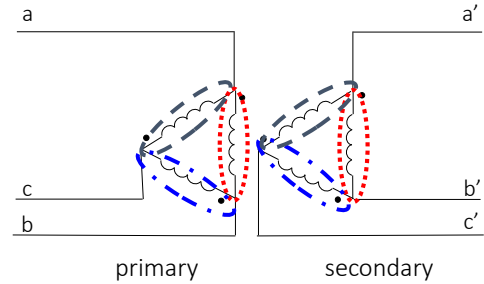
$$\mathbf{I}_{c'} = \frac{\mathbf{I}_c}{n}, \quad \mathbf{I}_{a'c'} = \frac{\mathbf{I}_{ca}}{n}$$




13

Dr. Louie

SEATTLEU

Δ -Y Transformer

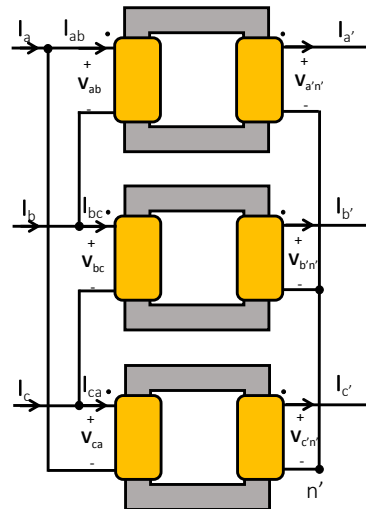- Secondary has a neutral connection
- Primary connected "top-to-bottom"
- Line-line voltages appear on the coils on primary
- Phase voltages appear on the coils on the secondary
- Less insulation needed on HV winding




14

Dr. Louie

SEATTLEU

Δ-Y Transformer Analysis

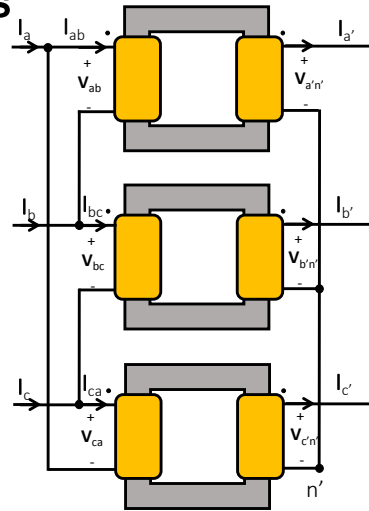- By Faraday's Law:
 - V_{ab} will be in-phase with $V_{a'n'}$
 - Phase shift introduced
- By KCL:
 - $I_a = I_{ab} - I_{ca}$
- By Ampere's Law:
 - I_{ab} will be in-phase with I_a
 - Phase shift introduced
- Similar results for b, c phases




15

Dr. Louie

SEATTLEU

Δ-Y Transformer Analysis

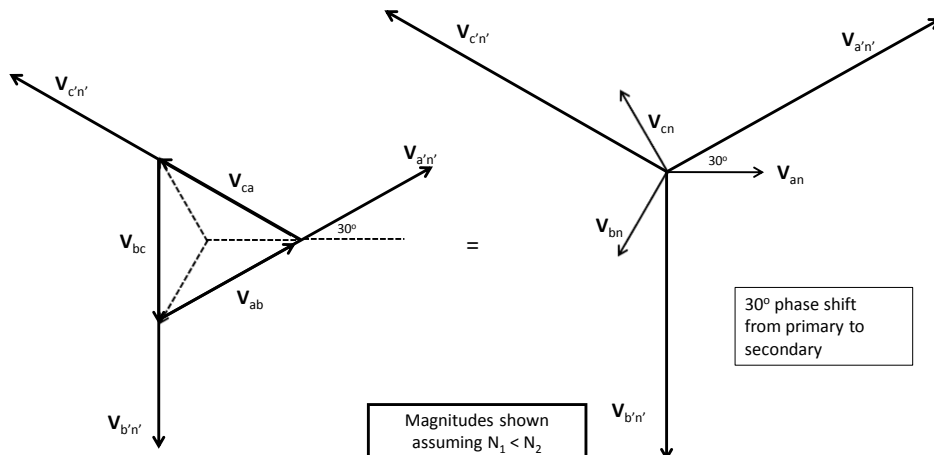Phasor Diagram for Ideal Delta-Y Connected Transformer



16


Dr. Louie

SEATTLEU

Delta-Y Transformer Analysis

Phasor Diagram for Ideal Delta-Y Connected Transformer
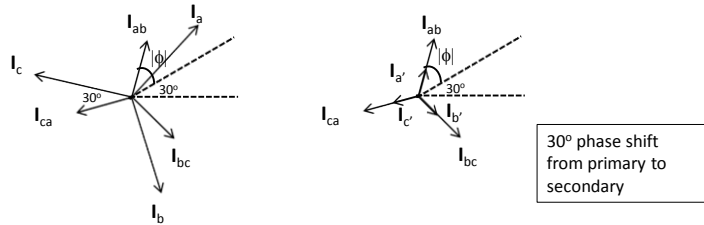
$$\begin{aligned}\mathbf{I}_a &= \mathbf{I}_{ab} - \mathbf{I}_{ca} \\ \mathbf{I}_b &= \mathbf{I}_{bc} - \mathbf{I}_{ab} \\ \mathbf{I}_c &= \mathbf{I}_{ca} - \mathbf{I}_{bc}\end{aligned}$$



17

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Delta-Y

- Let k be the transformer voltage gain
- For Δ -Y transformers:

$$\mathbf{V}_{a'n'} = n\mathbf{V}_{ab} = n\mathbf{V}_{an}\sqrt{3}e^{j\frac{\pi}{6}} = k\mathbf{V}_{an}$$

$$\text{therefore } k = n\sqrt{3}e^{j\frac{\pi}{6}} \quad \text{Important result!}$$

$$\begin{aligned}\mathbf{I}_{a'} &= \frac{\mathbf{I}_{ab}}{n} = \frac{\mathbf{I}_a e^{j\frac{\pi}{6}}}{\sqrt{3}n} \\ &= \frac{\mathbf{I}_a}{k^*} \end{aligned} \quad \left. \vphantom{\frac{\mathbf{I}_a}{k^*}} \right\} \text{ same phase shift as voltage}$$

18

Dr. Louie

SEATTLEU

Delta-Y Transformer Analysis

- Voltage relationships

$$\mathbf{V}_{a'n'} = k\mathbf{V}_{an'} \quad \mathbf{V}_{a'b'} = k\mathbf{V}_{ab}$$

$$\mathbf{V}_{b'n'} = k\mathbf{V}_{bn'} \quad \mathbf{V}_{b'c'} = k\mathbf{V}_{bc}$$


$$\mathbf{V}_{c'n'} = k\mathbf{V}_{cn'} \quad \mathbf{V}_{c'a'} = k\mathbf{V}_{ca}$$

- Line current relationships

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{k^*}$$

$$\mathbf{I}_{b'} = \frac{\mathbf{I}_b}{k^*}$$
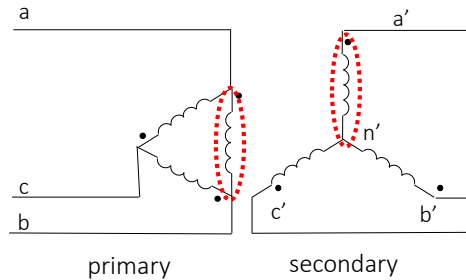
$$\mathbf{I}_{c'} = \frac{\mathbf{I}_c}{k^*}$$



19

Dr. Louie

SEATTLEU

Exercise

- Consider an ideal Delta-Y transformer, with 20 turns on each primary coil, and 80 turns on each secondary coil. If the primary side values are:

$$\mathbf{V}_{ab} = 208\angle 0^\circ \text{ V}$$

$$\mathbf{I}_a = 10\angle 5^\circ \text{ A}$$

- Compute: $\mathbf{V}_{a'b'}$, $\mathbf{V}_{a'n'}$, and $\mathbf{I}_{a'}$

20

Dr. Louie

SEATTLEU

Exercise

- Consider an ideal Delta-Y transformer, with 20 turns on each primary coil, and 80 turns on each secondary coil. If the primary side values are:

$$\mathbf{V}_{ab} = 208\angle 0^\circ \text{ V}$$

$$\mathbf{I}_a = 10\angle 5^\circ \text{ A}$$

- Compute: $\mathbf{V}_{a'b'}$, $\mathbf{V}_{a'n'}$, and $\mathbf{I}_{a'}$

$$k = n\sqrt{3}e^{\frac{j\pi}{6}} = 4\sqrt{3}e^{\frac{j\pi}{6}} = 6.92\angle 30^\circ$$

$$\mathbf{V}_{a'b'} = \mathbf{V}_{ab}k = 1436\angle 30^\circ \text{ V}$$

$$\mathbf{V}_{a'n'} = \mathbf{V}_{an}k = (120\angle -30^\circ)(6.92\angle 30^\circ) = 830.4\angle 0^\circ \text{ V}$$

$$\mathbf{I}_{a'} = \frac{\mathbf{I}_a}{k^*} = \frac{10\angle 5^\circ}{6.92\angle -30^\circ} = 1.45\angle 35^\circ \text{ A}$$


21

Dr. Louie

SEATTLEU

Y-Δ Transformer

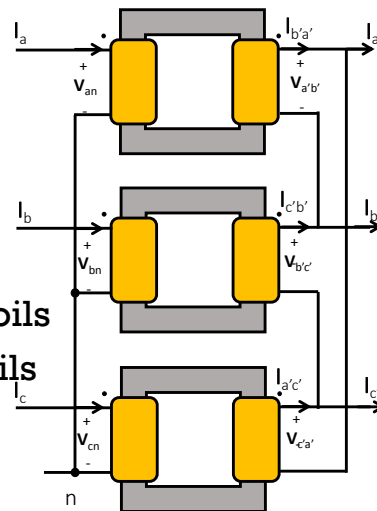- No neutral point on secondary
- \mathbf{V}_{an} , $\mathbf{V}_{a'b'}$ in phase
- \mathbf{I}_{an} , $\mathbf{I}_{b'a'}$ in phase
 - Similar results for b, c phase
- Line-neutral voltage across primary coils
- Line-line voltage across secondary coils



22

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Y-Δ

- Let k be the transformer voltage gain
- For Y-Δ transformers:

$$\mathbf{v}_{a'b'} = n\mathbf{v}_{an} = \frac{n\mathbf{v}_{ab}e^{-j\frac{\pi}{6}}}{\sqrt{3}} = k\mathbf{v}_{ab}$$

$$\text{therefore } k = \frac{ne^{-j\frac{\pi}{6}}}{\sqrt{3}} \quad \boxed{\text{Important result}}$$

Note: phase shift is -30° , whereas for Delta-Y transformer connection in previous slides it is $+30^\circ$

23

Dr. Louie

SEATTLEU

Three-Phase Transformer Analysis: Y-Δ

- Voltage relationship


$$\mathbf{v}_{ab'} = -n\mathbf{v}_{bn} = \frac{n}{\sqrt{3}}\mathbf{v}_{ab}e^{j\frac{\pi}{6}} = k\mathbf{v}_{ab}$$

$$\text{therefore } k = \frac{n}{\sqrt{3}}e^{j\frac{\pi}{6}}$$

$$\mathbf{v}_{a'n'} = \frac{\mathbf{v}_{ab'}}{\sqrt{3}}e^{-j\frac{\pi}{6}} = \frac{n\mathbf{v}_{an}}{\sqrt{3}}e^{j\frac{\pi}{6}} = k\mathbf{v}_{an}$$

- For the other phases
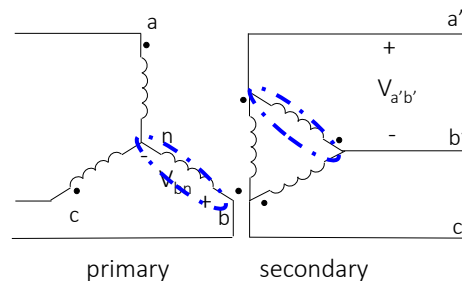
$$\begin{aligned} \mathbf{v}_{a'n'} &= k\mathbf{v}_{an} \\ \mathbf{v}_{b'n'} &= k\mathbf{v}_{bn} \\ \mathbf{v}_{c'n'} &= k\mathbf{v}_{cn} \end{aligned}$$



Phase shift is now $+30^\circ$


24

Dr. Louie

SEATTLEU

Practical Considerations

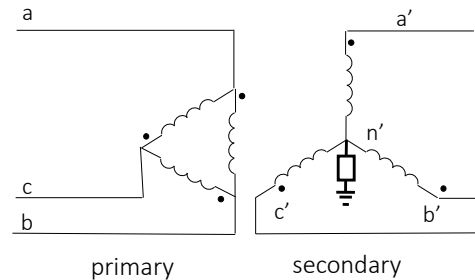- Medium-voltage industrial facilities often use Δ -Y incoming transformers
- Y-side is grounded through a resistor
 - Reduces ground current during fault
 - Reduces voltage dip during fault



25

Dr. Louie

SEATTLEU

Summary

- Y-Y, Delta-Delta transformers result in magnitude changes of $k = n$ from primary to secondary
 - No phase shifting occurs
- Y-Y transformers grant access to neutral point, which is usually grounded to prevent distortion
- Delta-Delta transformers have no neutral point, but are less prone to distortion
- Per phase analysis can be used on Y-Y, Delta-Delta transformers
 - Ensure impedances and voltages are properly converted
- There is a complex gain (magnitude and phase angle shift) associated with Y-Delta and Delta-Y transformers

26

Dr. Louie

SEATTLEU

» Reading

- Also read:
 - 11.2 (Multi-Winding Transformer)
 - 11.3 (Autotransformer)