

21-Converter and Controller Overview

Off-Grid Electrical Systems in Developing Countries

Chapter 9.1-9.3



ALSTOM FOUNDATION
FOR THE ENVIRONMENT



Community
Solutions
Initiative

SEATTLE UNIVERSITY

Electrical & Computer Engineering




Learning Outcomes

At the end of this lecture, you will be able to:

- ✓ describe the role of converters and controllers in off-grid systems
- ✓ understand the significance of distortion in off-grid systems
- ✓ describe the operation of boost DC-DC converters

Why use converters and controllers?

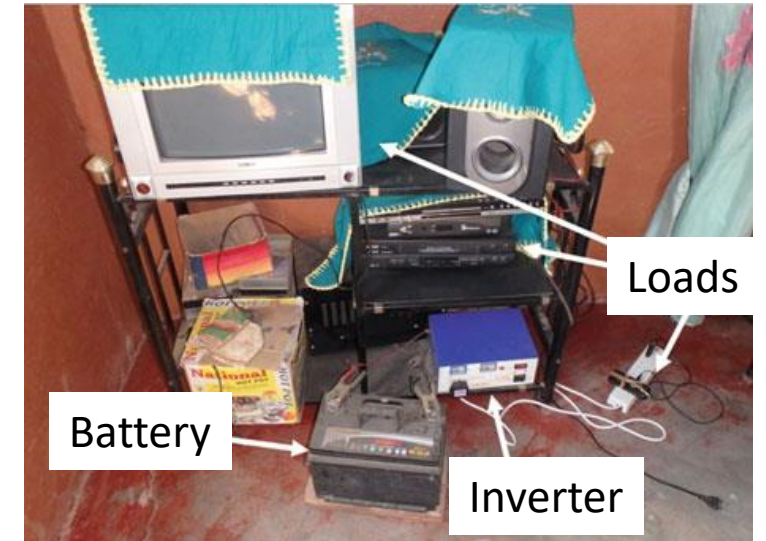
- Simple, improvised or non-engineered off-grid systems often do not use converters or controllers
- Converters and controllers can improve efficiency and utilization of components, and prolong their life




Converters & Controllers Found in Off-Grid Systems

| Converter | Basic Function |
|------------------------------------|------------------------------------------------------------------------------------------|
| DC-DC converter | Increases or decrease output voltage relative to input voltage |
| Maximum power point tracker (MPPT) | Increases the power produced by PV arrays or WECS |
| Solar battery charger | Charges batteries directly from PV sources |
| AC battery charger | Converters AC produced by generators or other sources to DC and manages battery charging |
| Rectifier | Converts AC to DC |
| Automatic voltage regulator (AVR) | Adjusts excitation to synchronous generators |
| Electronic load controller (ELC) | Controls power to ballast load to regulate frequency |
| Inverter | Converts DC to AC |
| Grid-tied inverter | Converts DC to AC and synchronizes with AC bus |
| Bi-directional inverter | Allows power to be exchanged between DC and AC buses |


Solid-State Switching Elements

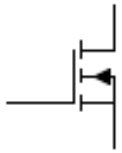

Power MOSFET

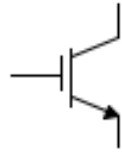

IGBT

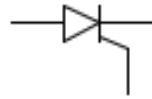

Thyristor




Diode


Some switches are operated by a control signal $q(t)$.
We will use the convention:

$q(t) = 1$: switch has received closed signal

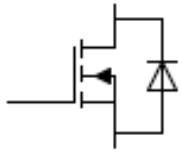$q(t) = 0$: switch has received open signal



Power MOSFET
with anti-parallel
diode

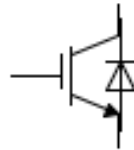

IGBT
with anti-parallel
diode




Generic Switch

Note: in some cases a switch will receive an open signal and remain closed, and vice-versa

Distortion

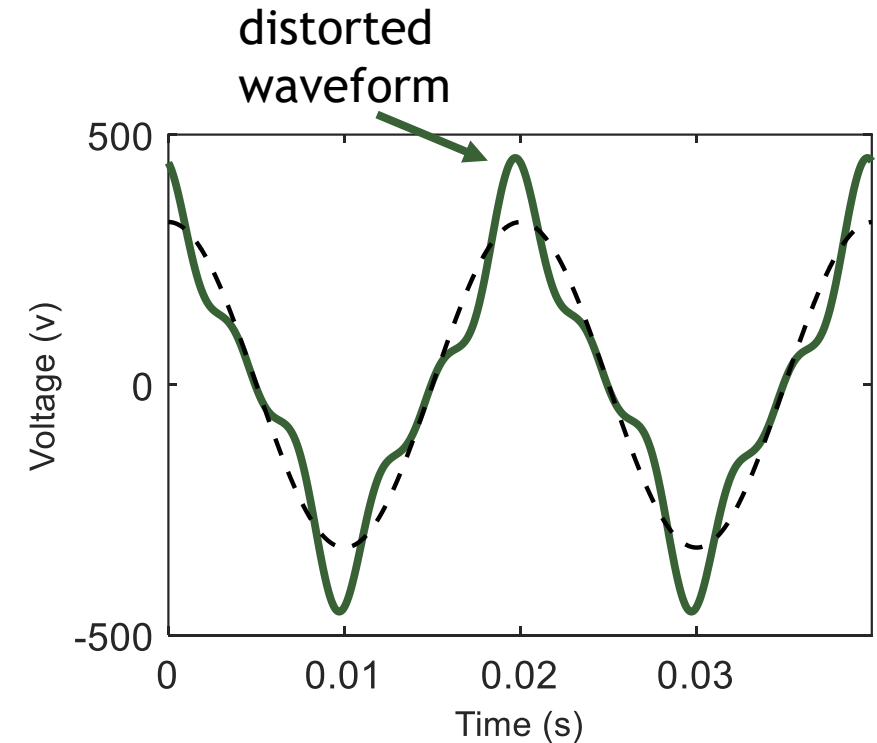- Many converters have non-linear characteristics resulting in distorted waveforms
 - Time-varying, non-sinusoidal voltage and current
- Deleterious effects of distortion
 - Generators and conductors overheat
 - Humming
 - Visible flicker
 - Malfunction of sensitive electronic devices



Distortion

- Analysis of distorted waveforms is challenging in the time domain, and phasor analysis does not apply
- Basic approach:
 - Decompose distorted waveform into its harmonic components using Fourier Series
 - Analyze each harmonic separately, for example using phasor analysis
 - Combine results from each harmonic

Fourier Series

Recall that any periodical zero-mean signal $f(t)$ can be decomposed into its harmonic components as:

$$f(t) = \sum_{k=1}^{\infty} F_k \sin(k\omega_0 t + \delta_k)$$

ω_0 : fundamental frequency of $f(t)$, rad/s




k : harmonic number

F_k : magnitude of the k th harmonic

δ_k : angle of the k th harmonic

Waveforms with little distortion will have
 $F_1 \gg F_2, \dots, F_{\infty}$

Fourier Series

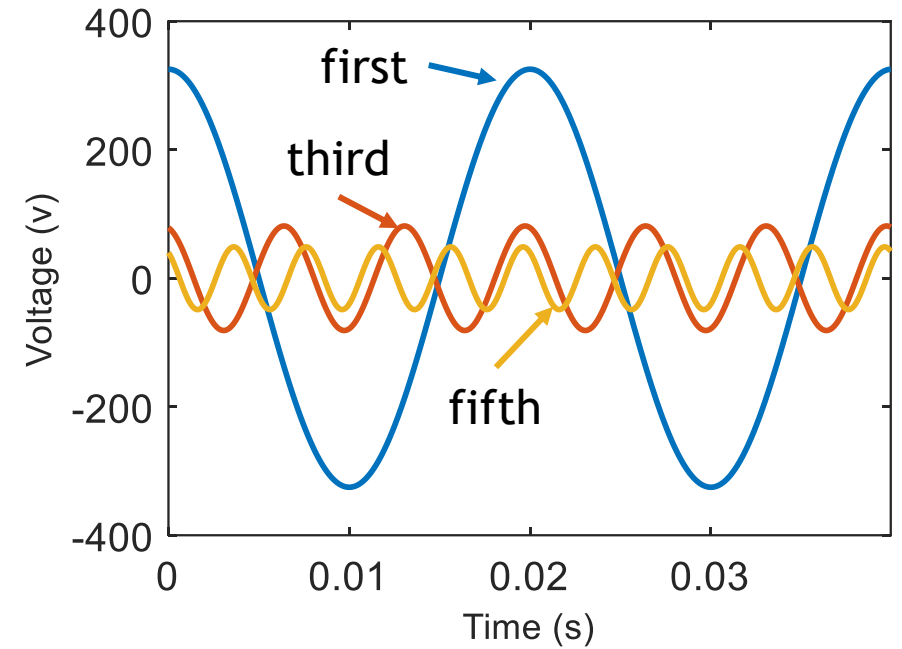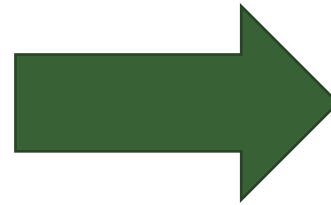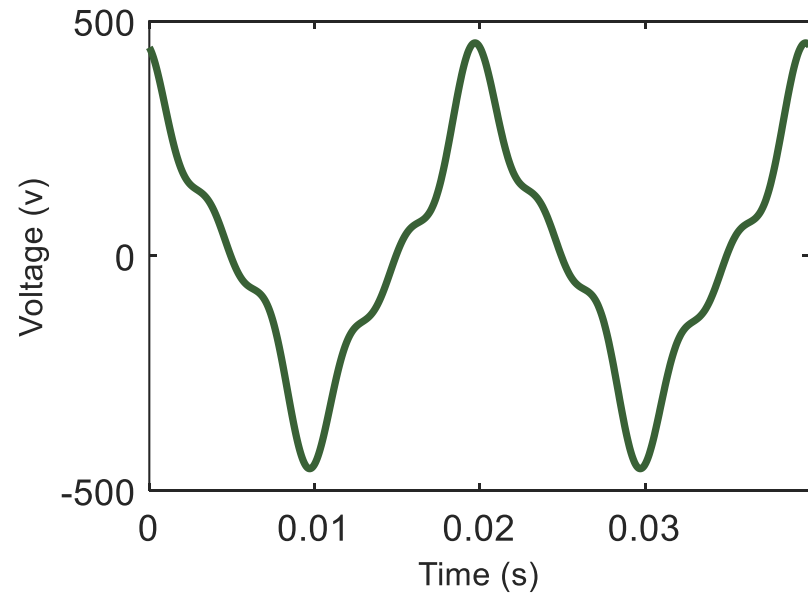

$$F_1 = 325.3 \text{ V}$$

$$\delta_1 = 0^\circ$$

$$F_3 = 81.3 \text{ V}$$

$$\delta_3 = 15^\circ$$

$$F_5 = 48.8 \text{ V}$$

$$\delta_5 = 35^\circ$$

Total Harmonic Distortion

- Distortion is commonly quantified using the Total Harmonic Distortion (THD) (commonly expressed as a percent)

$$THD = \frac{\sqrt{\sum_{k=2}^{\infty} F_k^2}}{F_1}$$


- THD usually reported by gen sets and inverters
- Higher quality gen sets and inverters will have a THD of less than 5%

Filtering

- Distortion can be reduced by using a passive filter at the output of a converter
- For example, use a low pass filter (capacitor) to filter out harmonics higher than the fundamental



Pulse Width Modulation (PWM)

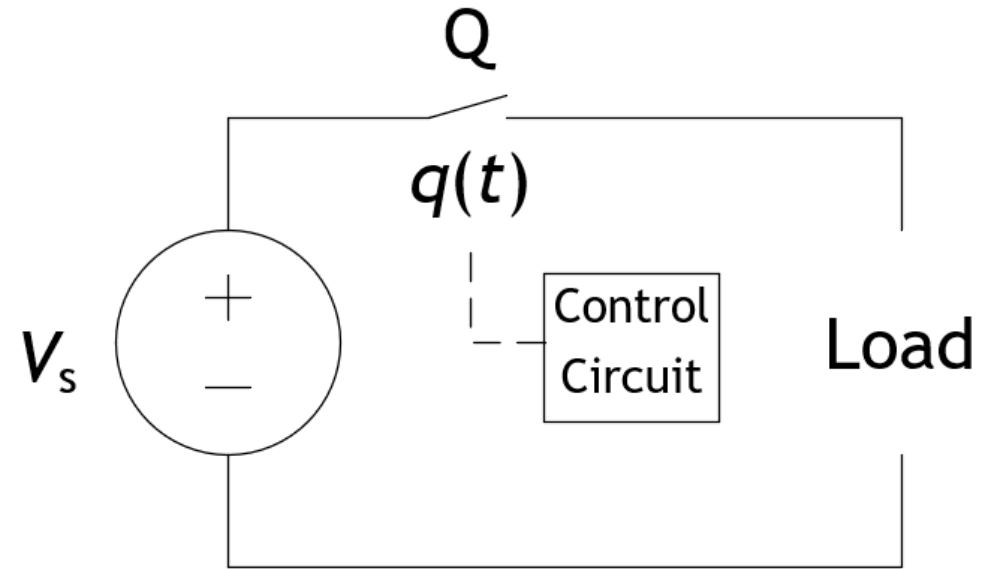- Technique in which the width of a pulse is varied to achieve a desired average value
- Allows for control of an independent DC source



simple “chopper” circuit

Pulse Width Modulation (PWM)

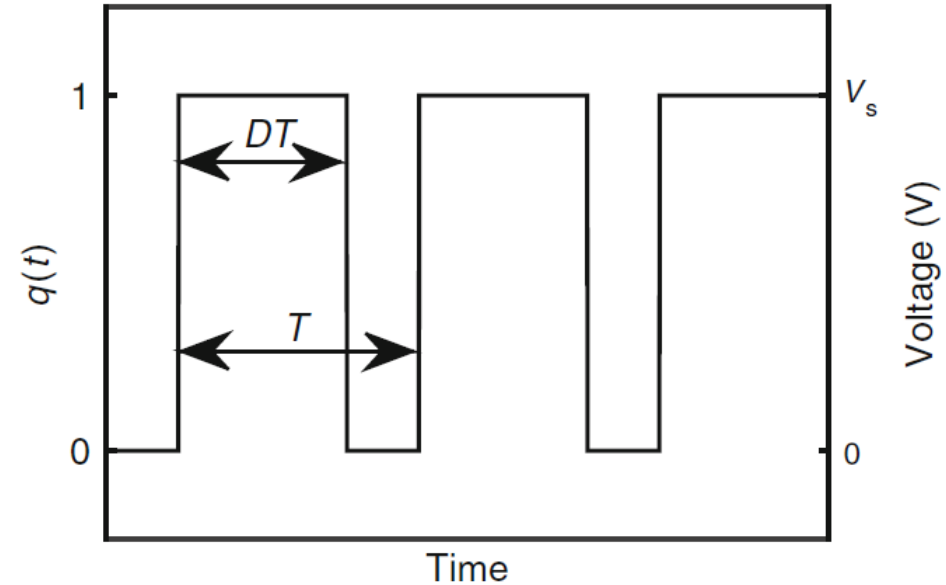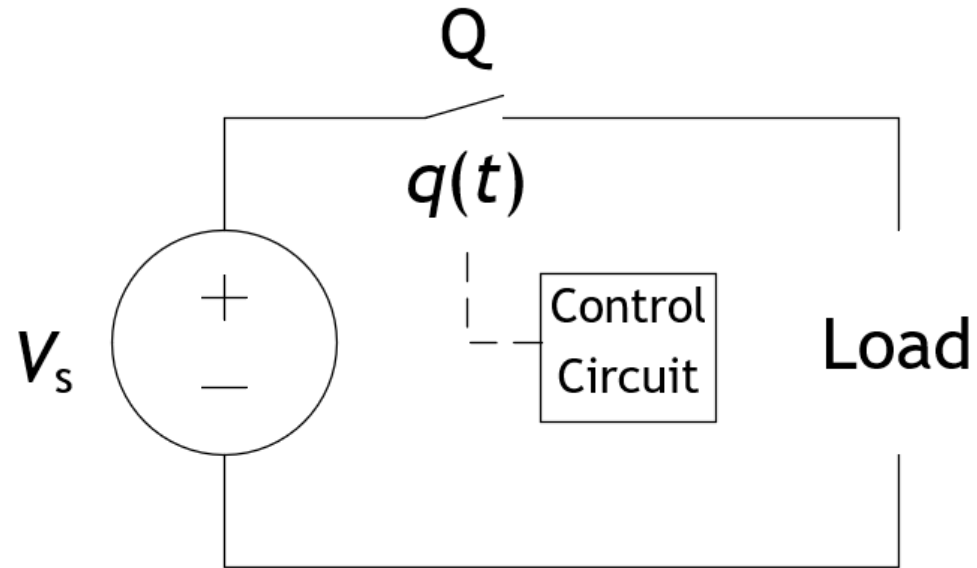


T : period, s
 D : duty cycle, often expressed as proportion or percent

Average Value

- The average value of the voltage waveform applied to the load is:
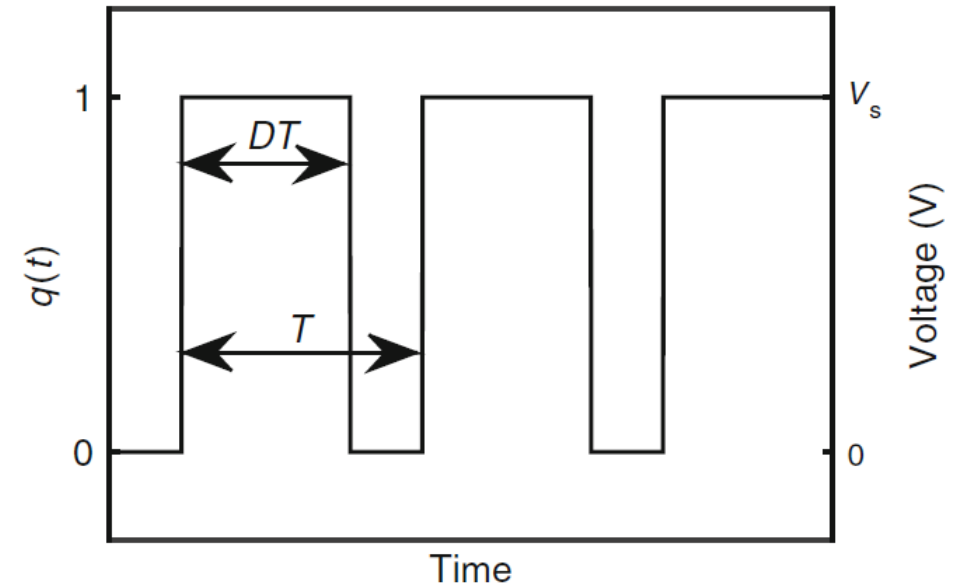
$$\bar{V}_{Load} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \int_0^{DT} V_s dt = DV_s$$




Pulse Width Modulation

- The voltage of a more general pulse train, which varies between a voltage V_{\max} and V_{\min} is:

$$\bar{V}_{Load} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \left(\int_0^{DT} V_{\max} dt + \int_{DT}^T V_{\min} dt \right) = DV_{\max} + (1-D)V_{\min}$$

DC-DC Converters

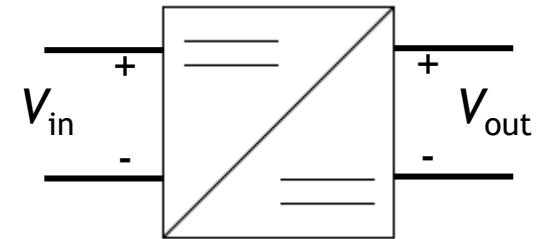- Conceptually similar to AC transformers, where the output voltage can be greater than, equal to, or less than the input voltage
- Unlike transformers, the ratio between output voltage and input can be easily adjusted by changing the duty cycle of a solid-state switch




DC-DC Converters

- The input and output quantities are related to the power output as:

$$P = \eta_{\text{DC-DC}} V_{\text{in}} I_{\text{in}} = V_{\text{out}} I_{\text{out}}$$

$\eta_{\text{DC-DC}}$: efficiency of the converter

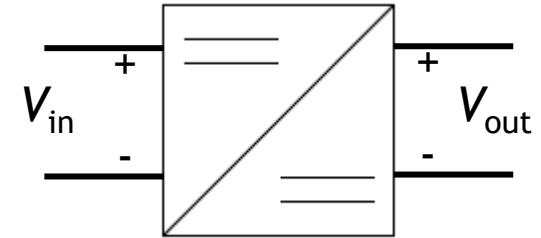
- Increasing the output voltage decreases the output current and vice versa
- DC-DC converters have efficiencies of approx. 90%



Boost Converter

- We will examine one type of DC-DC converter known as a “boost converter” to explain the general principles of DC-DC converter operation
- Boost converters are common DC-DC converters and are found internal to many off-grid converters and controls
- Boost converters increase the output voltage

Boost Converter Circuit

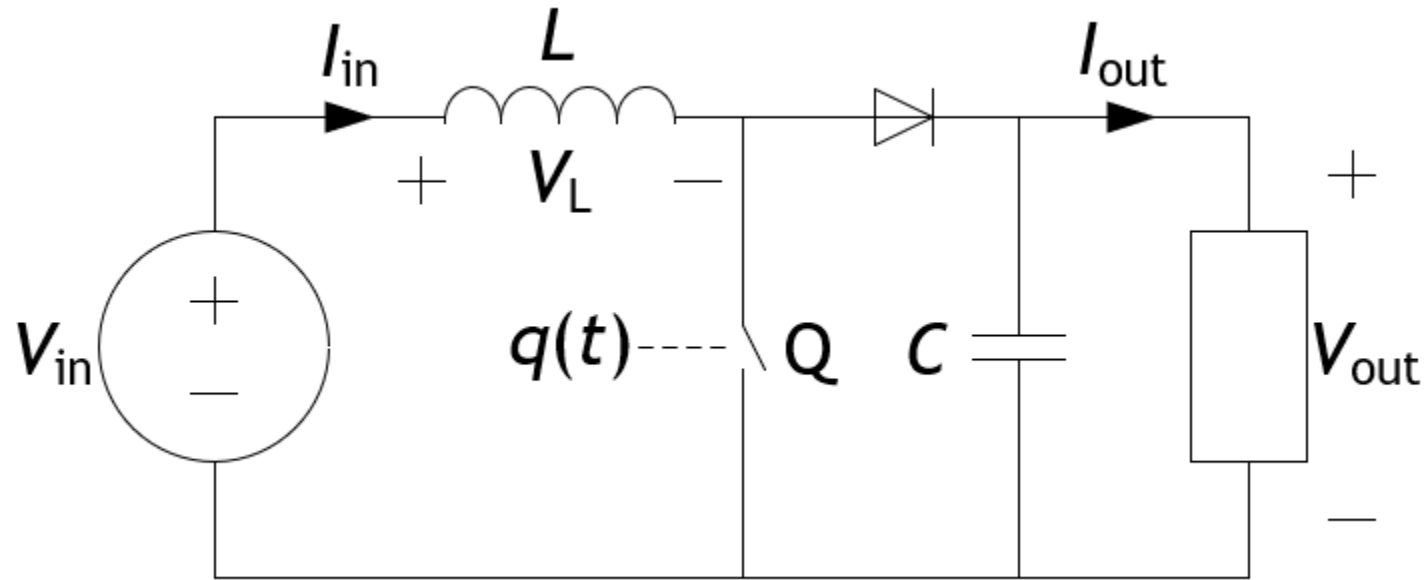


Boost Converter Circuit ($Q = 1$)

When switch is closed, the voltage across the inductor is V_{in} , and the current through it rises according to:

$$I_{in}(t) = \frac{1}{L} \int V_L dt$$


Energy stored in the inductor increases

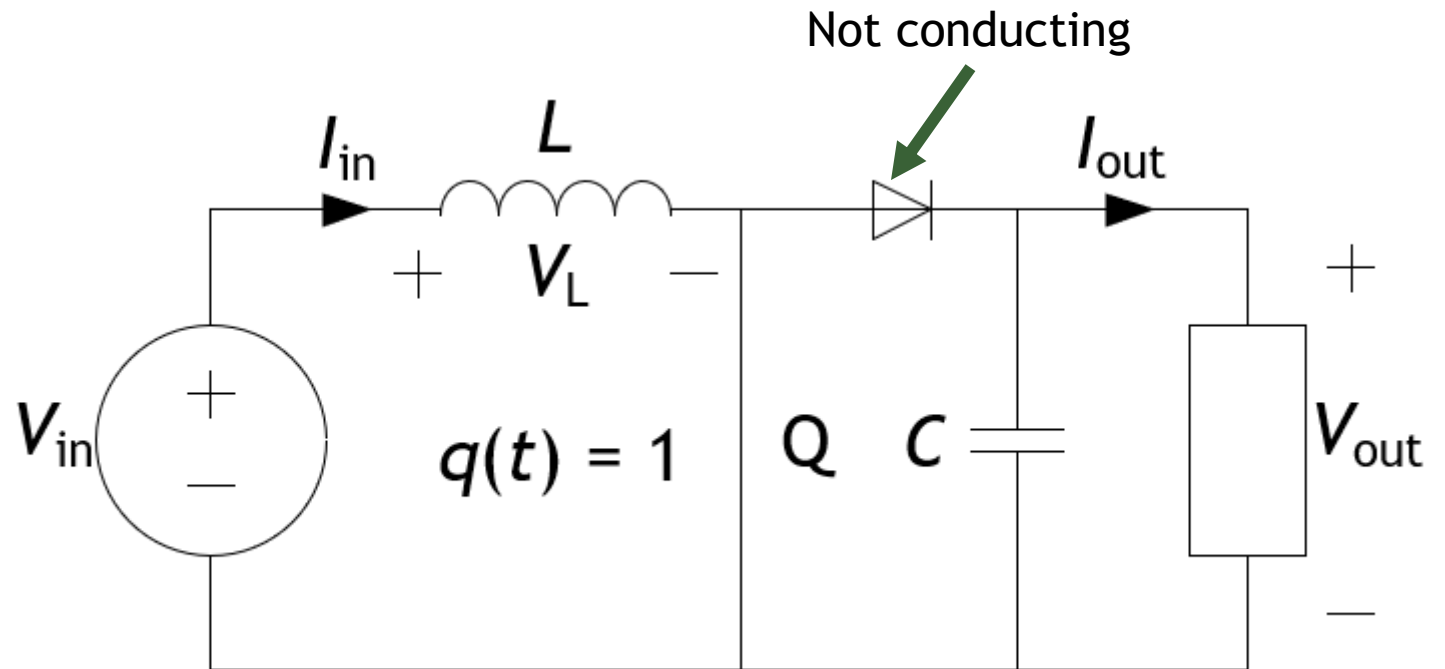

Boost Converter Circuit ($Q = 0$)

- Now the switch opens
- Current through inductor cannot instantly drop to zero
- Diode must be conducting
- KVL shows that:

$$V_{\text{in}} = V_L + V_{\text{out}}$$

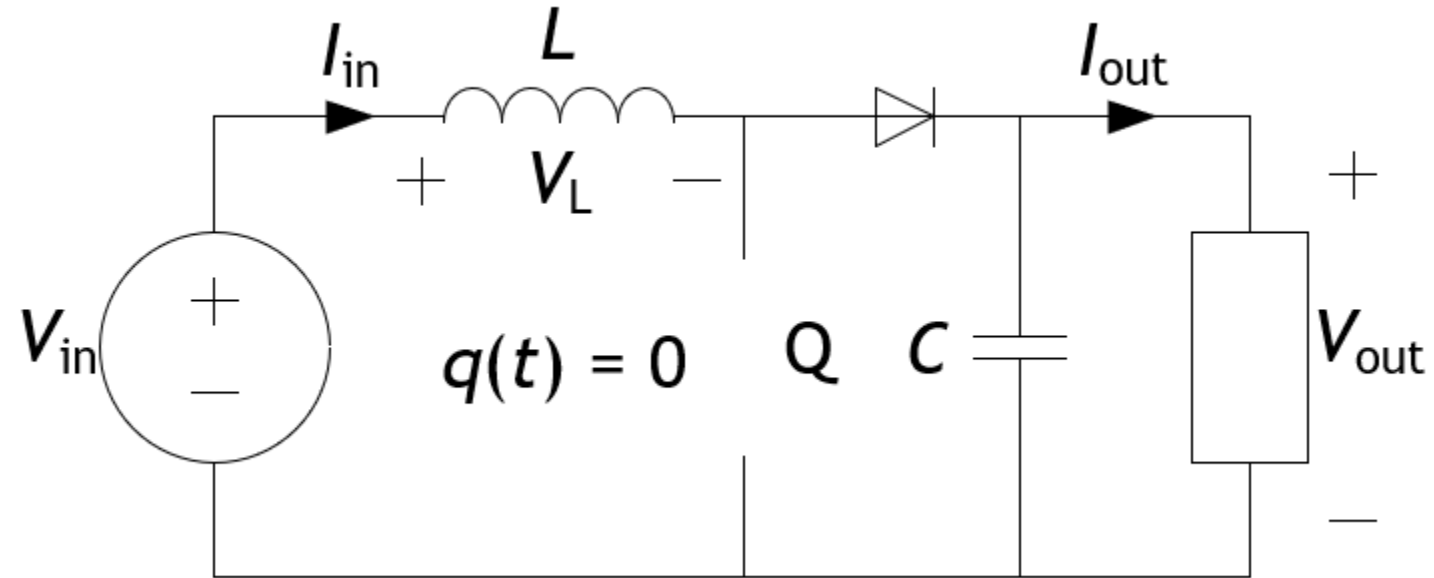

Ignoring the diode voltage drop

Boost Converter Circuit ($Q = 0$)

- Inductor current decreases (energy transferred to load)
- Inductor voltage becomes negative due to


$$V_L = L \frac{di_L}{dt}$$

- The output voltage is therefore:

$$V_{in} = V_L + V_{out}$$

$$V_{out} = V_{in} - V_L$$

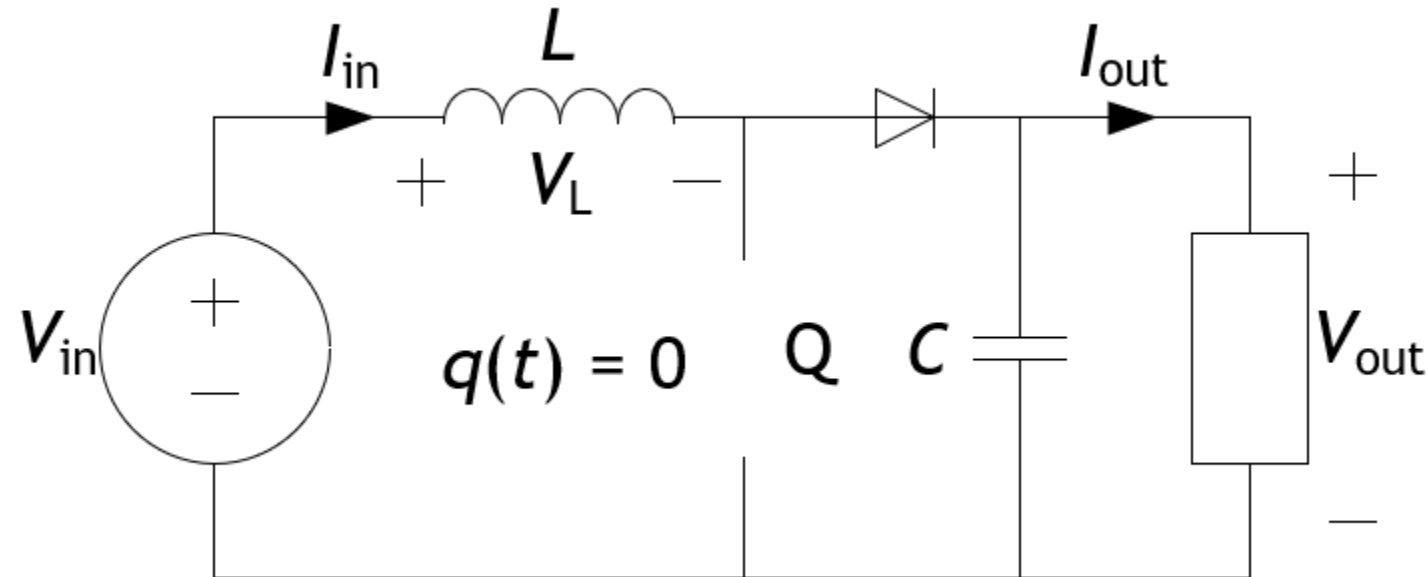The output voltage is therefore greater than the input



Boost Converter Output Voltage

- When $Q = 0$, the voltage across inductor is V_{in}
- When $Q = 1$, the voltage across inductor is $V_L = V_{in} - V_{out}$
- Since $Q = 0$ for D percent of the time, and $Q = 1$ for $1 - D$ percent of the time, the average is:

$$DV_{in} + (1 - D)(V_{in} - V_{out}) = \bar{V}_L$$

$$DV_{in} + (1 - D)(V_{in} - V_{out}) = 0$$

$$V_{out} = \frac{1}{1 - D} V_{in}$$

The average inductor voltage must be 0 (otherwise its energy would be increasing or decreasing on average over time)

DC-DC Converters

Other converters use different topologies to achieve voltage gain or reduction

| Converter | Relationship |
|------------|-------------------------------------------------|
| Boost | $V_{\text{out}} = \frac{1}{1-D} V_{\text{in}}$ |
| Buck | $V_{\text{out}} = D V_{\text{in}}$ |
| Buck–boost | $V_{\text{out}} = \frac{-D}{1-D} V_{\text{in}}$ |

Contact Information

Henry Louie, PhD

Professor

Seattle University



@henrylouie

hlouie@ieee.org

Office: +1-206-398-4619