

1



Learning Outcomes


At the end of this lecture, you will be able to:

- ✓ describe the role of converters and controllers in off-grid systems
- ✓ understand the significance of distortion in off-grid systems
- ✓ describe the operation of boost DC-DC converters

2

Why use converters and controllers?

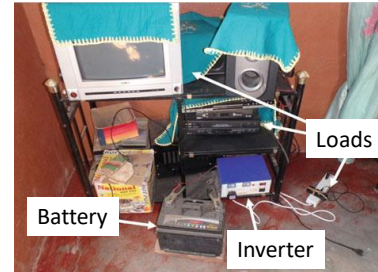- Simple, improvised or non-engineered off-grid systems often do not use converters or controllers
- Converters and controllers can improve efficiency and utilization of components, and prolong their life



copyright 2019 www.drhenrylouie.com

3

3

Converters & Controllers Found in Off-Grid Systems

Converter	Basic Function
DC-DC converter	Increases or decrease output voltage relative to input voltage
Maximum power point tracker (MPPT)	Increases the power produced by PV arrays or WECS
Solar battery charger	Charges batteries directly from PV sources
AC battery charger	Converts AC produced by generators or other sources to DC and manages battery charging
Rectifier	Converts AC to DC
Automatic voltage regulator (AVR)	Adjusts excitation to synchronous generators
Electronic load controller (ELC)	Controls power to ballast load to regulate frequency
Inverter	Converts DC to AC
Grid-tied inverter	Converts DC to AC and synchronizes with AC bus
Bi-directional inverter	Allows power to be exchanged between DC and AC buses

copyright 2019 www.drhenrylouie.com

4

4

Solid-State Switching Elements



Power MOSFET



IGBT



Thyristor



Diode

Power MOSFET
with anti-parallel
diodeIGBT
with anti-parallel
diode

Generic Switch


Some switches are operated by a control signal $q(t)$.
We will use the convention:

$q(t) = 1$: switch has received closed signal
 $q(t) = 0$: switch has received open signal

Note: in some cases a switch will receive an open signal and remain closed, and vice-versa

Distortion

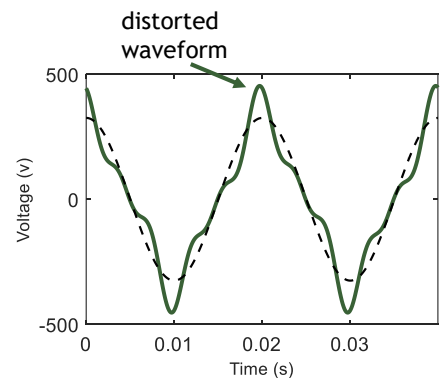- Many converters have non-linear characteristics resulting in distorted waveforms
 - Time-varying, non-sinusoidal voltage and current
- Deleterious effects of distortion
 - Generators and conductors overheat
 - Humming
 - Visible flicker
 - Malfunction of sensitive electronic devices



Distortion

- Analysis of distorted waveforms is challenging in the time domain, and phasor analysis does not apply
- Basic approach:
 - Decompose distorted waveform into its harmonic components using Fourier Series
 - Analyze each harmonic separately, for example using phasor analysis
 - Combine results from each harmonic

Fourier Series

Recall that any periodical zero-mean signal $f(t)$ can be decomposed into its harmonic components as:

$$f(t) = \sum_{k=1}^{\infty} F_k \sin(k\omega_0 t + \delta_k)$$

ω_0 : fundamental frequency of $f(t)$, rad/s

k : harmonic number



F_k : magnitude of the k th harmonic

δ_k : angle of the k th harmonic

Waveforms with little distortion will have

$$F_1 \gg F_2, \dots, F_{\infty}$$

Fourier Series

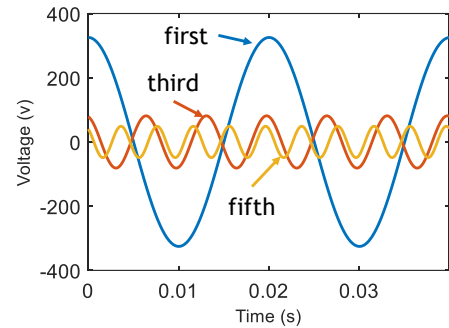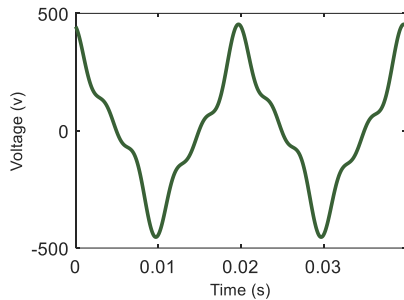

$$\begin{aligned}
 F_1 &= 325.3 \text{ V} & \delta_1 &= 0^\circ \\
 F_3 &= 81.3 \text{ V} & \delta_3 &= 15^\circ \\
 F_5 &= 48.8 \text{ V} & \delta_5 &= 35^\circ
 \end{aligned}$$

copyright 2019 www.drhenrylouie.com

9

9

Total Harmonic Distortion

- Distortion is commonly quantified using the Total Harmonic Distortion (THD) (commonly expressed as a percent)

$$THD = \frac{\sqrt{\sum_{k=2}^{\infty} F_k^2}}{F_1}$$

- THD usually reported by gen sets and inverters
- Higher quality gen sets and inverters will have a THD of less than 5%

copyright 2019 www.drhenrylouie.com

10


10

Filtering

- Distortion can be reduced by using a passive filter at the output of a converter
- For example, use a low pass filter (capacitor) to filter out harmonics higher than the fundamental



Pulse Width Modulation (PWM)

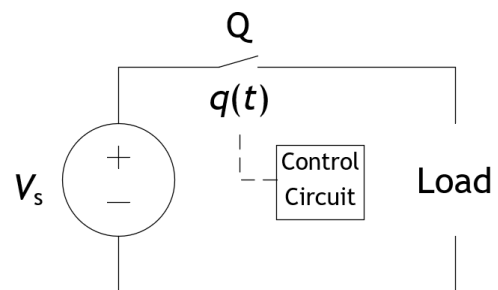- Technique in which the width of a pulse is varied to achieve a desired average value
- Allows for control of an independent DC source



simple "chopper" circuit

Pulse Width Modulation (PWM)

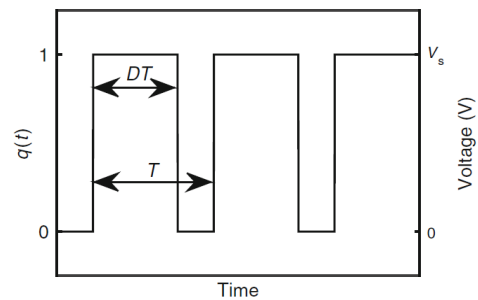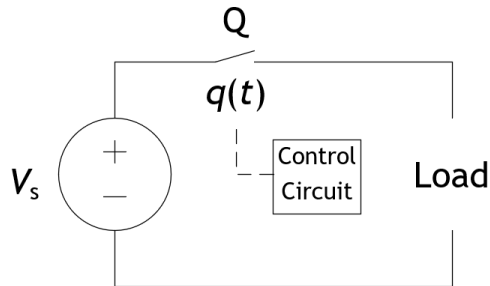

T : period, s
 D : duty cycle, often expressed as proportion or percent

copyright 2019 www.drhenrylouie.com


13

13

Average Value

- The average value of the voltage waveform applied to the load is:
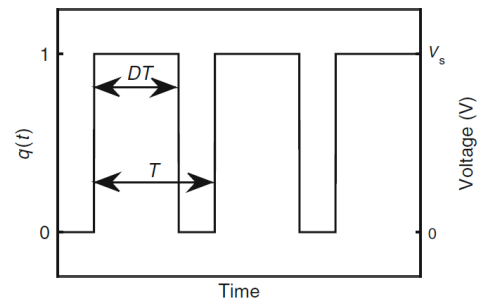
$$\bar{V}_{Load} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \int_0^{DT} V_s dt = DV_s$$



copyright 2019 www.drhenrylouie.com

14

14


Pulse Width Modulation

- The voltage of a more general pulse train, which varies between a voltage V_{\max} and V_{\min} is:

$$\bar{V}_{Load} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \left(\int_0^{DT} V_{\max} dt + \int_{DT}^T V_{\min} dt \right) = DV_{\max} + (1-D)V_{\min}$$

DC-DC Converters

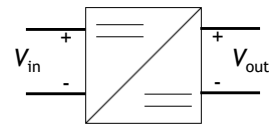- Conceptually similar to AC transformers, where the output voltage can be greater than, equal to, or less than the input voltage
- Unlike transformers, the ratio between output voltage and input can be easily adjusted by changing the duty cycle of a solid-state switch




DC-DC Converters

- The input and output quantities are related to the power output as:

$$P = \eta_{\text{DC-DC}} V_{\text{in}} I_{\text{in}} = V_{\text{out}} I_{\text{out}}$$

$\eta_{\text{DC-DC}}$: efficiency of the converter

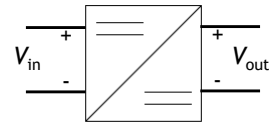
- Increasing the output voltage decreases the output current and vice versa
- DC-DC converters have efficiencies of approx. 90%



Boost Converter

- We will examine one type of DC-DC converter known as a “boost converter” to explain the general principles of DC-DC converter operation
- Boost converters are common DC-DC converters and are found internal to many off-grid converters and controls
- Boost converters increase the output voltage

Boost Converter Circuit

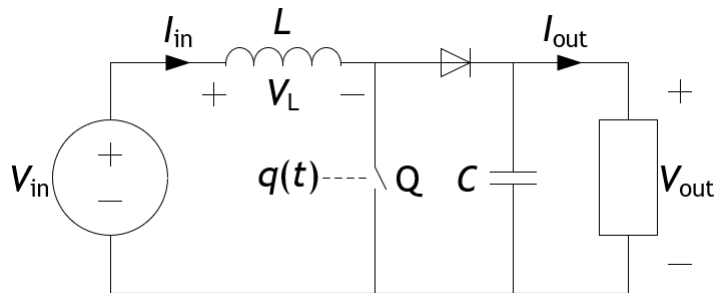

copyright 2019 www.drhenrylouie.com

19


19

Boost Converter Circuit ($Q = 1$)

When switch is closed, the voltage across the inductor is V_{in} , and the current through it rises according to:

$$I_{in}(t) = \frac{1}{L} \int V_L dt$$

Energy stored in the inductor increases

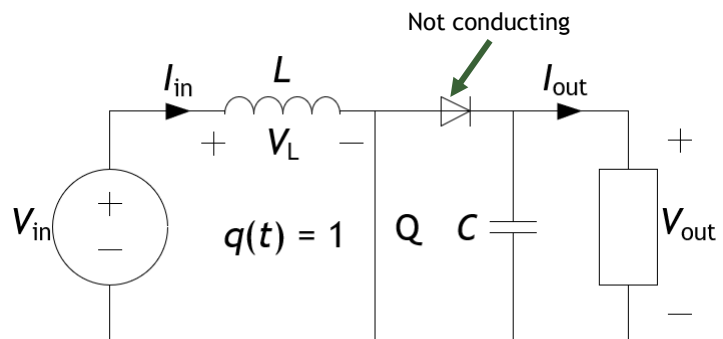

copyright 2019 www.drhenrylouie.com


20

20

Boost Converter Circuit ($Q = 0$)

- Now the switch opens
- Current through inductor cannot instantly drop to zero
- Diode must be conducting
- KVL shows that:

$$V_{in} = V_L + V_{out}$$

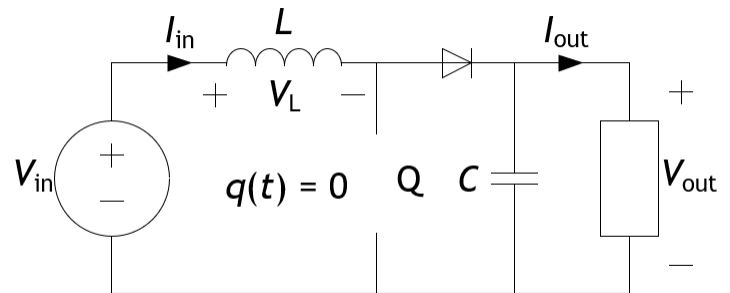

Ignoring the diode voltage drop

copyright 2019 www.drhenrylouie.com

21

21

Boost Converter Circuit ($Q = 0$)

- Inductor current decreases (energy transferred to load)
- Inductor voltage becomes negative due to


$$V_L = L \frac{di_L}{dt}$$

- The output voltage is therefore:

$$V_{in} = V_L + V_{out}$$

$$V_{out} = V_{in} - V_L$$

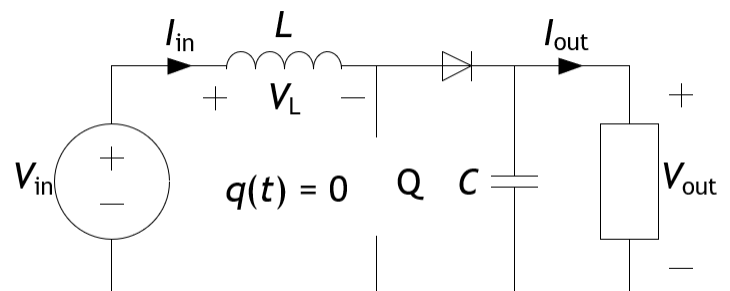The output voltage is therefore greater than the input



copyright 2019 www.drhenrylouie.com

22

22

Boost Converter Output Voltage

- When $Q = 0$, the voltage across inductor is V_{in}
- When $Q = 1$, the voltage across inductor is $V_L = V_{in} - V_{out}$
- Since $Q = 0$ for D percent of the time, and $Q = 1$ for $1 - D$ percent of the time, the average is:

$$DV_{in} + (1-D)(V_{in} - V_{out}) = \bar{V}_L$$

$$DV_{in} + (1-D)(V_{in} - V_{out}) = 0$$

$$V_{out} = \frac{1}{1-D} V_{in}$$

The average inductor voltage must be 0 (otherwise its energy would be increasing or decreasing on average over time)

23

copyright 2019 www.drhenrylouie.com

23

DC-DC Converters

Other converters use different topologies to achieve voltage gain or reduction

Converter	Relationship
Boost	$V_{out} = \frac{1}{1-D} V_{in}$
Buck	$V_{out} = DV_{in}$
Buck-boost	$V_{out} = \frac{-D}{1-D} V_{in}$

24

copyright 2019 www.drhenrylouie.com

24


Contact Information

Henry Louie, PhD

Associate Professor

Fr. Wood Endowed Research Chair

Seattle University

 @henrylouie

hlouie@ieee.org

Office: +1-206-398-4619

copyright 2019 www.drhenrylouie.com

25