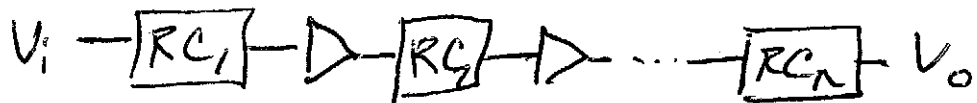


Shifting n independent & equal RC poles



Starting from the 2nd; equal pole solution

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1+(\omega RC)^2}} \times \frac{1}{\sqrt{1+(\omega RC)^2}} \times \dots = \frac{1}{\sqrt{1+(\omega RC)^2}} \times \dots$$

By symmetry

$$\frac{1}{\sqrt{1+(\omega RC)^2}} = \frac{1}{\sqrt{1+(\omega RC)^2}} \quad \text{and as } \sqrt{\frac{1}{2}} = \sqrt{1+(\omega RC)^2}$$

Now

$$\left(\frac{1}{\sqrt{2}}\right)^2 = 1 + (\omega RC)^2$$

$$\sqrt{\left(\frac{1}{\sqrt{2}}\right)^2 - 1} = 2\pi f_c RC$$

$$\text{Again } 2\pi f_c RC = 1$$

$$x = \sqrt{\left(\frac{1}{\sqrt{2}}\right)^2 - 1} \quad ; \text{ This looks like a Russian Nesting Breakout the calculator!! lol}$$

$$n=3, x=0.5098, \frac{1}{x}=1.961$$

$$n=4, x=0.435, \frac{1}{x}=2.2989$$

$$n=5, x=0.3856, \frac{1}{x}=2.593$$

Conclusion: If we want $f_c=10\text{Hz}$ and we have 3 equal & independent RC poles; we calculate the RC values using $1.96 f_c$.

$$\text{Using a } 1\mu\text{F capacitor } R = \frac{1}{2\pi \cdot 1.96 f_c C} = 8.12\text{ k ohm}$$

$$\text{Checking our work any 1 RC at } f_c = \frac{1}{\sqrt{1+(2\pi f_c RC)^2}} = 0.89076$$

$$\text{for the system } (0.89076)^3 = 0.707 = \frac{1}{\sqrt{2}} \quad \checkmark$$